

In-class assignment and Homework (due 9/18)

- Download and install KiCAD (<https://www.kicad.org/download/>)
- Finish the lock-in amplifier PCB
- Finish the 2N3904 transistor amplifier simulation
- email finished KiCAD projects to jcl11@illinois.edu