

In-class assignment and Homework (due 9/17)

- Download and install KiCAD (<https://www.kicad.org/download/>)
- Finish the lock-in amplifier PCB
- email finished KiCAD project (schematic, PCB layout, Gerber files) to jcl11@illinois.edu

Homework (due 9/24)

- Build and run the 2N3904 transistor amplifier simulation
- email finished KiCAD project (schematic, simulation) to jcl11@illinois.edu