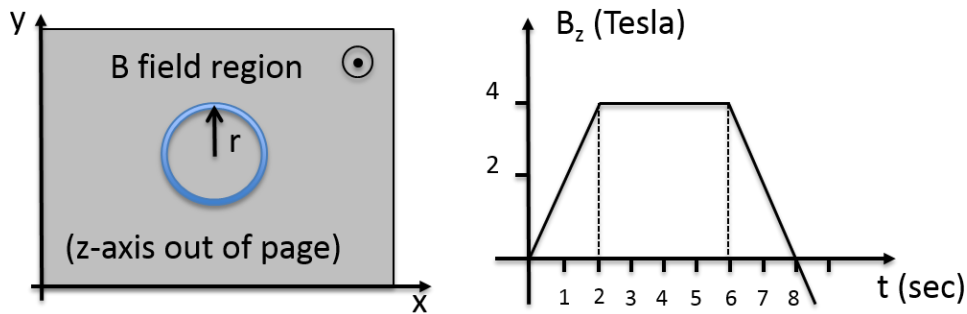


The next three questions pertain to the situation described below.



A loop of wire of radius $r = 0.25$ m and resistivity 8 Ohms per meter lies in the x-y plane. The loop is fully contained in a spatially constant, but time-varying magnetic field. A graph of the time-dependence of the magnetic field is shown.

1) What is the direction of the induced current in the loop at $t = 8$ seconds?

- a. The induced current is zero at $t = 8$ seconds
- b. Counter-clockwise
- c. Clockwise

2) What is the magnitude of the induced current at $t = 1.5$ seconds?


- a. $I_{1.5} = 0$ A
- b. $I_{1.5} = 0.0468$ A
- c. $I_{1.5} = 0.0156$ A
- d. $I_{1.5} = 0.0312$ A
- e. $I_{1.5} = 0.159$ A

3) Compare the magnitude of the current at $t = 4$ seconds to the magnitude of the current at $t = 7$ seconds.

- a. $|I_4| = |I_7|$
- b. $|I_4| < |I_7|$
- c. $|I_4| > |I_7|$

The next four questions pertain to the situation described below.

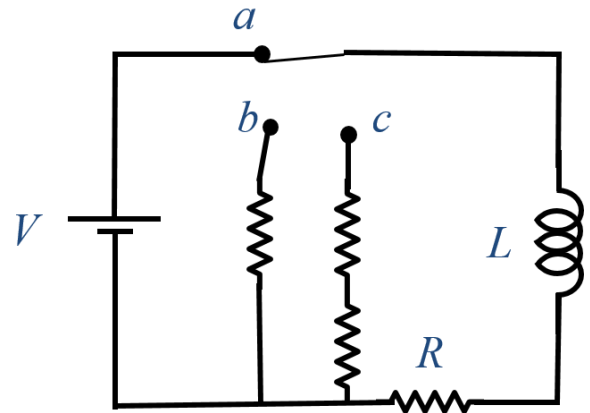Consider the electrical circuit shown. It consists of an ideal 18 Volt battery and four $36\ \Omega$ resistors and an $24\ \text{mH}$ inductor. The switch has been in position **a** as shown for a long time.



4) What is the voltage across the inductor after the switch has been in position **a** for a long time?

- a. $V_L = 9$ Volts
- b. $V_L = 18$ Volts
- c. $V_L = 0$ Volts

5) How much energy is stored in the inductor after the switch has been in position **a** for a long time?

- a. $U_L = 0.003$ Joules
- b. $U_L = 9$ Joules
- c. $U_L = 0$ Joules

6) After being in position **a** for a long time, the switch is instantaneously moved to position **c**. What is the voltage across the inductor immediately after the switch is in position **c**?


- a. $V_L = 6$ Volts
- b. $V_L = 54$ Volts
- c. $V_L = 18$ Volts

7) After being in position **a** for a long time, you have the option to instantaneously move the switch to either position **b** or position **c**. Which position will result in the energy in the inductor being dissipated the fastest?

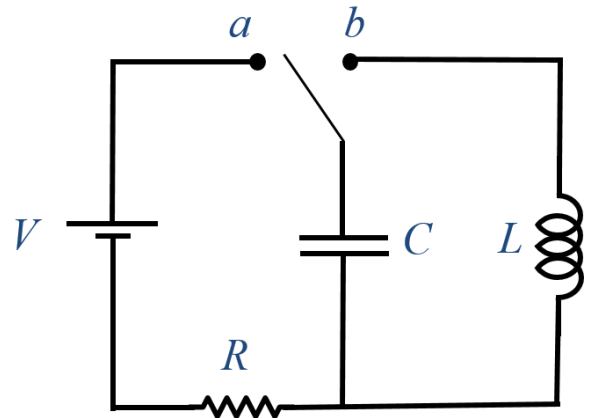- a. Position **b**
- b. Both positions will dissipate energy at the same rate.
- c. Position **c**

The next three questions pertain to the situation described below.

Consider the electrical circuit shown. It consists of an ideal 18 Volt battery a 3.6Ω resistor a 15 mF capacitor and a 24 mH inductor. The switch has been in position **a** for a long time.



8) After being in position **a** for a long time, the switch is moved to position **b**. What is the rate at which the current through the inductor is changing immediately after the switch is in position **b**?

- a. $dI_L/dt = 5 \text{ A/s}$
- b. $dI_L/dt = 750 \text{ A/s}$
- c. $dI_L/dt = 0.675 \text{ A/s}$

9) Let I_{\max} represent the maximum current that flows through the inductor while the switch is in position **b**. After the switch is moved to position **b**, what is the current through the inductor when the charge on the capacitor is $1/4$ its maximum value?


- a. $I_{1/4} = 0.97 I_{\max}$
- b. $I_{1/4} = 0.5 I_{\max}$
- c. $I_{1/4} = 0.063 I_{\max}$
- d. $I_{1/4} = 0.75 I_{\max}$
- e. $I_{1/4} = 0.25 I_{\max}$

10) Which expression best represents the charge on the top plate of the capacitor if $t=0$ corresponds to the moment the switch was moved from position **a** to position **b**?

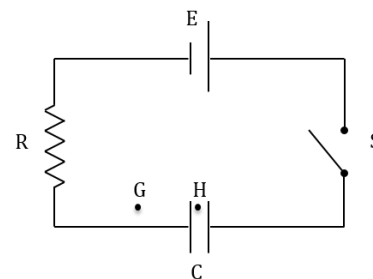- a. $Q(t) = +Q_{\max} \sin(\omega t)$
- b. $Q(t) = +Q_{\max} \cos(\omega t)$
- c. $Q(t) = 0$
- d. $Q(t) = -Q_{\max} \sin(\omega t)$
- e. $Q(t) = -Q_{\max} \cos(\omega t)$

The next two questions pertain to the situation described below.

Consider the RC circuit shown. It consists of an ideal 18 Volt battery a $30\ \Omega$ resistor and a 15 mF capacitor. The capacitor consists of two circular plates separated by a small distance, and is initially uncharged. At time $t=0$, the switch is closed.




11) Compare the magnitude of the magnetic field at point G, a distance d above the wire, and point H, midway between the plates of the capacitor and a distance d above its center just after the switch is closed. Note $d < r$ the radius of the capacitor plate.

- a. $B_G > B_H$
- b. $B_G < B_H$
- c. $B_G = B_H$

12) How fast is the electric flux between the capacitor plates changing just after the switch is closed?

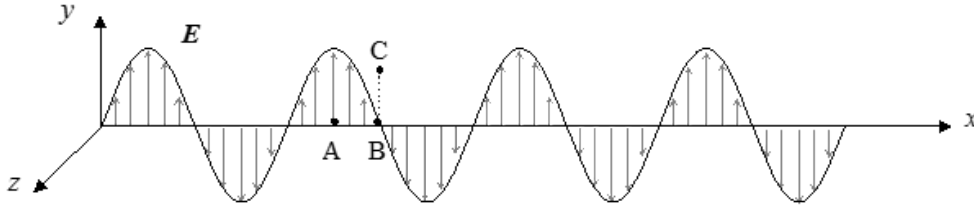- a. $d\Phi_E/dt = 3.39 \times 10^{10} \text{ Nm}^2\text{C}^{-1}\text{s}^{-1}$
- b. $d\Phi_E/dt = 6.78 \times 10^{10} \text{ Nm}^2\text{C}^{-1}\text{s}^{-1}$
- c. $d\Phi_E/dt = 4.79 \times 10^{10} \text{ Nm}^2\text{C}^{-1}\text{s}^{-1}$

The next three questions pertain to the situation described below.



A linearly polarized electromagnetic wave propagates in vacuum. The electric field associated with the wave is:

$$\vec{E} = E_0 \sin(kx + \omega t)\hat{y}$$

The figure above shows a snapshot of the electric field at $t=0$.

13) At $t = 0$, which option best describes the relative magnitudes of the electric field at points A, B and C? Note that A, B and C lie on the x-y plane.

- a. $E_C > E_A = E_B = 0$;
- b. $E_A > E_C > E_B = 0$;
- c. $E_A > E_C = E_B = 0$


14) Which of the following best describes the magnetic field associated with the electromagnetic wave? Note $E_0 > 0$ and $B_0 > 0$.

- a. $\vec{B} = -B_0 \sin(kx - \omega t)\hat{y}$
- b. $\vec{B} = -B_0 \sin(kx + \omega t)\hat{z}$
- c. $\vec{B} = B_0 \cos(kx + \omega t)\hat{y}$
- d. $\vec{B} = B_0 \sin(kx + \omega t)\hat{z}$
- e. $\vec{B} = -B_0 \sin(kx + \omega t)\hat{y}$

15) If the amplitude of the magnetic field is $B_0 = 6 \times 10^{-5}$ T, what is the average intensity of the wave?

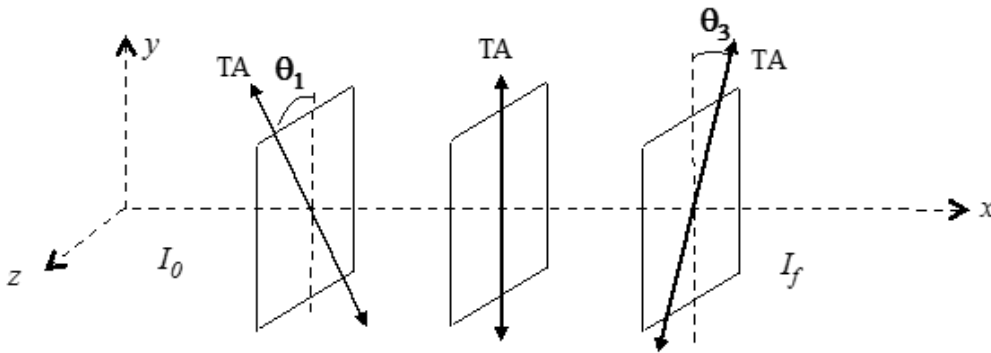- a. 6.08×10^5 W/m²
- b. 2.05×10^5 W/m²
- c. 3.04×10^5 W/m²
- d. 4.3×10^5 W/m²
- e. 7.74×10^5 W/m²

The next three questions pertain to the situation described below.



Consider a beam of unpolarized light with initial intensity I_0 traveling in the $+x$ direction. The beam traverses three linear polarizers parallel to the yz plane whose transmission axes (TA) are indicated in the figure above with $\theta_1 = 25^\circ$ and $\theta_3 = 65^\circ$.


16) Which of the following best describes the relationship between the initial intensity I_f and the final intensity I_f ?

- a. $I_f = 0.121 I_0$
- b. $I_f = 0$
- c. $I_f = 0.0734 I_0$

17) Consider the situation where the 2nd and 3rd polarizers are exchanged with each other, how does the final intensity change?

- a. I_f will be zero.
- b. I_f will not change.
- c. I_f will increase.

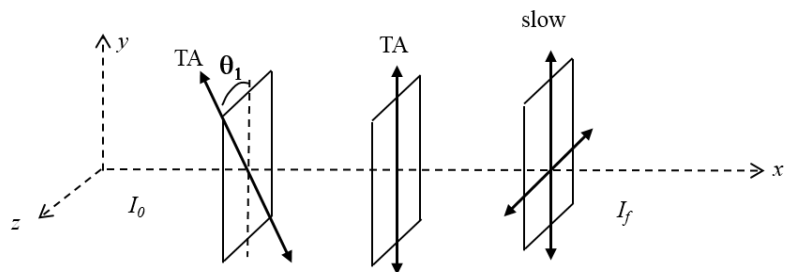
18) Now consider the situation where the third polarizer is replaced with a birefringent material whose slow and fast axes are aligned with the y and z axes respectively as shown in the figure. What is the polarization of the outgoing wave?



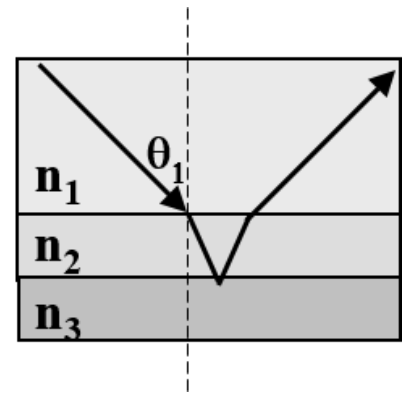- a. Right circularly polarized.
- b. Left circularly polarized.
- c. Linearly polarized.

The next two questions pertain to the situation described below.

Consider the case of light traveling through three different materials in layers with indices of refraction n_1 , n_2 and n_3 , as shown in the figure.



19) Given the transition between layers 1 and 2 shown in the figure above, what can be concluded about these two materials?


- a. $n_1 > n_2$
- b. $n_1 = n_2$
- c. $n_1 < n_2$

20) If the light is totally reflected between material 2 and 3, which of the following holds?

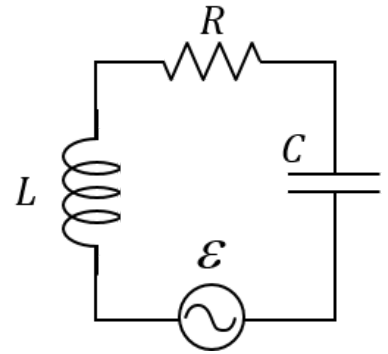- a. $n_3 \leq n_1 \sin(\theta_1)$
- b. $n_3 \geq n_1 \sin(\theta_1)$
- c. $n_3 \geq n_1$

The next five questions pertain to the situation described below.

Consider the electrical AC circuit shown. It consists of a variable frequency AC generator providing a voltage $V(t) = 18 \sin(\omega t)$ Volts, a 10Ω resistor, a $15 \mu\text{F}$ capacitor, and a 24 mH inductor.



- 21) To what frequency ω should the generator be set in order to maximize the peak voltage across the resistor?
- $\omega = 1670 \text{ rad/s}$
 - $\omega = 0 \text{ rad/s}$
 - The peak voltage across the resistor does not depend on the frequency of the generator.
- 22) The generator is now set to the resonant frequency for this circuit. What is the maximum energy stored in the inductor at this frequency?
- $U_{\text{max}} = 32.4 \text{ J}$
 - $U_{\text{max}} = 0.0389 \text{ J}$
 - $U_{\text{max}} = 16.2 \text{ J}$
- 23) With the generator set to the resonant frequency for this circuit, what is the average power dissipated by the resistor?
- $\langle P_R \rangle = 64.8 \text{ W}$
 - $\langle P_R \rangle = 16.2 \text{ W}$
 - $\langle P_R \rangle = 32.4 \text{ W}$
- 24) The generator frequency is now set to 1330 rad/s . Which element has the largest peak voltage?
- generator
 - capacitor
 - inductor
 - They all have the same peak voltage.
 - resistor
- 25) With the generator frequency still set to 1330 rad/s , what is the first time after $t=0$, that the magnitude of the voltage across the resistor is a maximum?
- $t = 3.78 \times 10^{-4} \text{ s}$
 - $t = 8.03 \times 10^{-4} \text{ s}$
 - $t = 0.00118 \text{ s}$