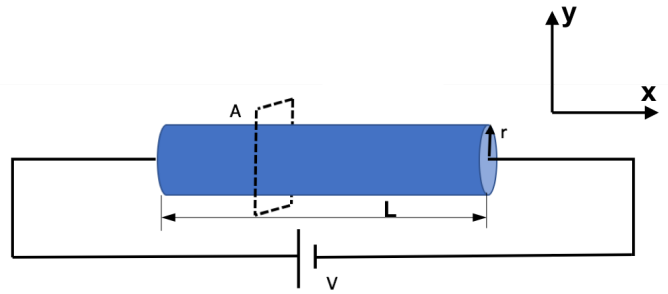


The next two questions pertain to the situation described below.

A cylindrical resistor with length  $L = 9$  cm, radius  $r = 0.5$  cm and resistivity  $\rho = 2 \times 10^{-4} \Omega \cdot \text{m}$ , is connected to a battery of voltage  $V = 6$  V, as shown in the Figure to the right:



1) What is the electric field inside the resistor?


- a.  $12 \hat{x}$  V/cm
- b.  $-12 \hat{x}$  V/cm
- c.  $0.667 \hat{x}$  V/cm
- d.  $3 \times 10^4 \hat{x}$  V/cm
- e.  $-0.667 \hat{x}$  V/cm

2) (On average) How much charge passes through the surface A in 1 second?

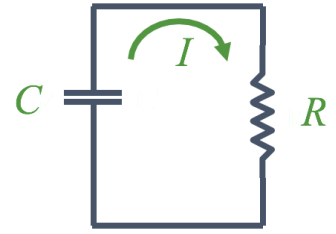- a.  $3 \times 10^4$  C
- b. 26.2 C
- c.  $-3 \times 10^4$  C

The next three questions pertain to the situation described below.

A capacitor with capacitance  $C = 10^{-5}$  F is initially charged by connecting it to a battery of voltage 9 V and waiting for a long time. The capacitor is then disconnected from the battery after which it is connected to a resistor with resistance  $5 \Omega$  as shown:



3) Immediately after the resistor is connected what is the current through the resistor?


- a.  $9 \times 10^{-5}$  Amps
- b. 1.8 Amps
- c.  $5 \times 10^{-5}$  Amps

4) How long after the resistor is connected does it take for the charge on the capacitor to reach the value 1/5 of the initial charge?

- a.  $4.7 \times 10^{-4}$  sec
- b.  $8 \times 10^{-5}$  sec
- c.  $5 \times 10^{-5}$  sec

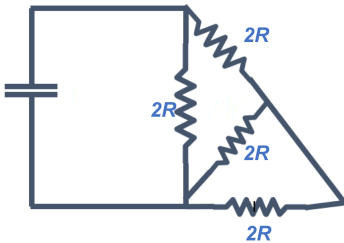5) We now connect an identical charged up capacitor to a network of resistors shown in the figure below.


Compare the new time the capacitor takes to discharge to 1/5 of the initial charge, with the time from the previous problem:



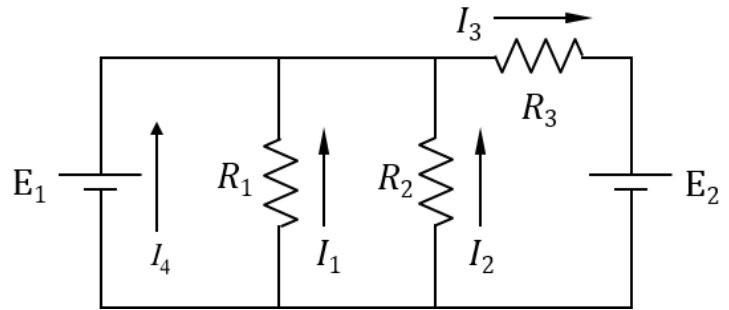- a. It now takes longer
- b. It now takes less time
- c. It takes the same time

The next three questions pertain to the situation described below.

Three resistors ( $R_1 = 10 \Omega$ ,  $R_2 = 15 \Omega$ ,  $R_3 = 25 \Omega$ ) are connected to two batteries ( $E_1$  is unknown,  $E_2 = 11 \text{ V}$ ) as shown in the figure.



6) Which of the following equations is NOT correct:

- a.  $I_1 R_1 + E_1 = 0$
- b.  $-I_3 R_3 + E_1 - E_2 = 0$
- c.  $-I_3 R_3 + I_1 R_1 - E_2 = 0$
- d.  $-I_2 R_2 - E_1 = 0$
- e.  $-I_3 R_3 - I_2 R_2 - E_2 = 0$

7) The current  $I_3$  through resistor  $R_3$  is measured to be 0.48 amps, in the direction shown by the arrow. What is the voltage across battery  $E_1$ ?


- a.  $E_1 = 11 \text{ V}$
- b.  $E_1 = 23 \text{ V}$
- c.  $E_1 = 1 \text{ V}$

8) What is  $I_4$  the current through battery  $E_1$ ?

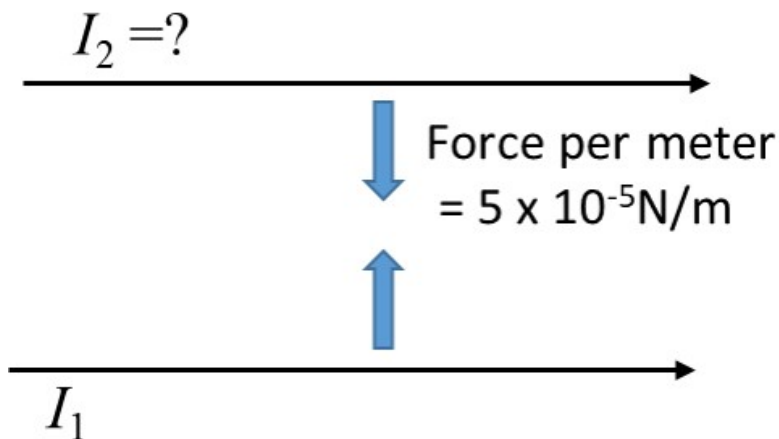- a.  $I_4 = 2 \text{ A}$
- b.  $I_4 = 2.8 \text{ A}$
- c.  $I_4 = 2.5 \text{ A}$
- d.  $I_4 = 0.92 \text{ A}$
- e.  $I_4 = 4.3 \text{ A}$

The next two questions pertain to the situation described below.

Two long parallel wires are separated by a distance of 2.5 cm. The force per meter that each wire exerts on the other is  $5 \times 10^{-5} \text{ N/m}$ , and the wires attract each other. The current in one of the wires,  $I_1$ , is 0.5 A.



9) What is the current  $I_2$  in the other wire?


- a. 12.5 A
- b. 2.5 A
- c. 0.5 A
- d. 6.25 A
- e. 4.81 A

10) Are the currents in the two wires flowing in the same direction or in opposite directions?

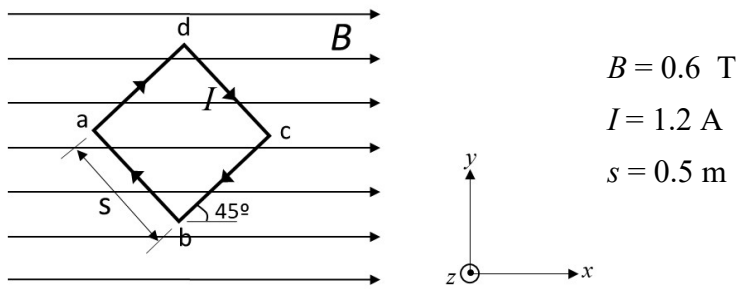- a. the same direction
- b. not enough information is given in the problem to answer this question
- c. opposite directions

The next three questions pertain to the situation described below.

A square loop of side  $s = 0.5$  m lies in the  $x$ - $y$  plane and carries a current of  $I = 1.2$  A flowing in the clockwise direction (as viewed from  $z > 0$ ). A constant, uniform magnetic field of magnitude  $B = 0.6$  T points in the  $+x$  direction, as shown in the figure.




11) The torque exerted by the magnetic force on this loop is pointing in the direction:

- a.  $+y$
- b.  $-x$
- c.  $+z$
- d.  $-y$
- e.  $+x$

12) The amount of work required to rotate this loop to an orientation which has the maximum potential energy is:

- a. 0 J
- b. 0.18 J
- c. 0.36 J

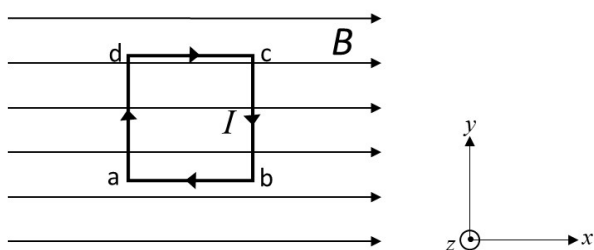
13) How much work is required to rotate the loop by 45 degrees around the  $z$ -axis such that the segment  $ab$  is now oriented along the  $x$ -axis (see figure below)?



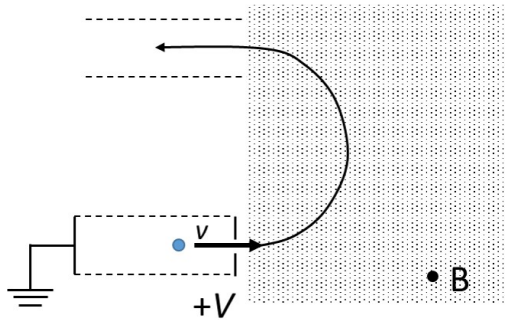- a. 0.18 J
- b. 0.09 J
- c. 0 J

The next two questions pertain to the situation described below.

An electron of mass  $m$  and charge  $q$  is put in a track and accelerated to the right (in the plane of the paper) from rest through a potential difference  $V$ . The electron then enters a region containing a uniform magnetic field (direction of  $B$  is out of the page). The electron makes a  $180^\circ$  turn in the field to enter a track that is parallel to its initial trajectory.



$$V = 300 \text{ V}$$

$$B = 0.2 \text{ T out of page}$$

$$q = -1.6 \times 10^{-19} \text{ C}$$

$$m = 9.1 \times 10^{-31} \text{ kg}$$

14) When the electron is in the magnetic field region, its speed  $v$ :


- a. remains constant.
- b. increases.
- c. decreases.

15) How much time does the electron spend in the magnetic field region?

[Hint:  $\Delta t = \text{distance}/\text{speed}$ ]

- a.  $2.2 \times 10^{-45} \text{ s}$
- b.  $9.5 \times 10^{-6} \text{ s}$
- c.  $4.7 \times 10^{-23} \text{ s}$
- d.  $2.8 \times 10^{-11} \text{ s}$
- e.  $8.9 \times 10^{-11} \text{ s}$

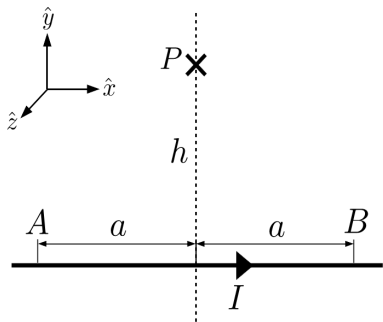
- 16) An infinitely long, thin wire carries a current  $I$  along the  $x$  axis. What is the contribution to the magnetic field at a point  $P = (0, h)$  due to **only** the segment of the wire between point  $A = (-a, 0)$  and point  $B = (a, 0)$ ?



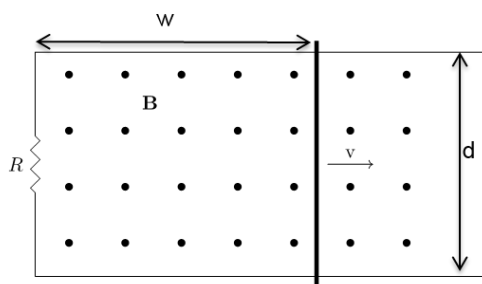- a.  $\vec{B}(P) = \int_{-a}^a \frac{\mu_0 I}{4\pi} \frac{h}{(x^2+h^2)^{3/2}} dx \hat{z}$   
 b.  $\vec{B}(P) = \int_{-a}^a \frac{\mu_0 I}{4\pi} \frac{-x}{h(x^2+h^2)} dx \hat{z}$   
 c.  $\vec{B}(P) = \int_{-a}^a \frac{\mu_0 I}{4\pi} \frac{1}{x^2+h^2} dx \hat{z}$   
 d.  $\vec{B}(P) = \int_{-a}^a \frac{\mu_0 I}{4\pi} \frac{h}{x(x^2+h^2)} dx \hat{z}$   
 e.  $\vec{B}(P) = \int_{-a}^a \frac{\mu_0 I}{4\pi} \frac{-x}{(x^2+h^2)^{3/2}} dx \hat{z}$

The next two questions pertain to the situation described below.

A conducting bar of mass  $m = 0.3$  kg slides with negligible friction along a pair of horizontal conducting tracks separated by a distance  $d = 0.15$  m, as shown in the figure below. The left side of the loop contains a resistor with resistance  $R = 20 \Omega$ . There is a constant magnetic field,  $B = 2$  T, directed out of the page.



- 17) What is the current through the resistor when the metallic bar is a distance  $w = 0.225$  m from the end sliding with a constant speed  $v = 4$  m/s?

- a.  $I = 0.00338$  A  
 b.  $I = 0.09$  A  
 c.  $I = 0.06$  A


18) What direction does the current flow, when the bar is sliding to the right at a constant speed?

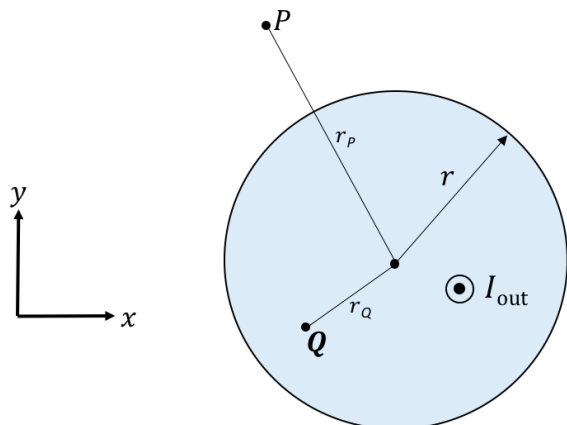- a. Counter clockwise, down through the resistor.
- b. Cannot determine the direction of the current.
- c. Clockwise, up through the resistor.



The next two questions pertain to the situation described below.

A wire of radius  $r = 11.1$  cm is centered at the origin carries a uniform current  $I_{out} = 0.295$  A out of the page. Points  $P$  and  $Q$  are placed at distances of  $r_P = 18$  cm and  $r_Q = 5$  cm from the origin respectively, as shown in the figure below.



19) What is the magnitude of the magnetic field at Point  $P$ ?

- a.  $|\vec{B}| = 2.6 \times 10^{-7}$  T
- b.  $|\vec{B}| = 5.3 \times 10^{-7}$  T
- c.  $|\vec{B}| = 3.3 \times 10^{-7}$  T


20) What is the magnitude of the magnetic field at Point  $Q$ ?

- a.  $|\vec{B}| = 2.9 \times 10^{-9}$  T
- b.  $|\vec{B}| = 2.4 \times 10^{-7}$  T
- c.  $|\vec{B}| = 4.75 \times 10^{-7}$  T
- d.  $|\vec{B}| = 8.6 \times 10^{-8}$  T
- e.  $|\vec{B}| = 1.2 \times 10^{-6}$  T

The next three questions pertain to the situation described below.

A circular wire with radius  $r$  and resistance  $R$  is placed within a time-dependent but uniform magnetic field at  $t = 0$  sec, as seen in the figure below. The magnetic field is given by  $B(t) = B_0 t^2$  and points out of the page.

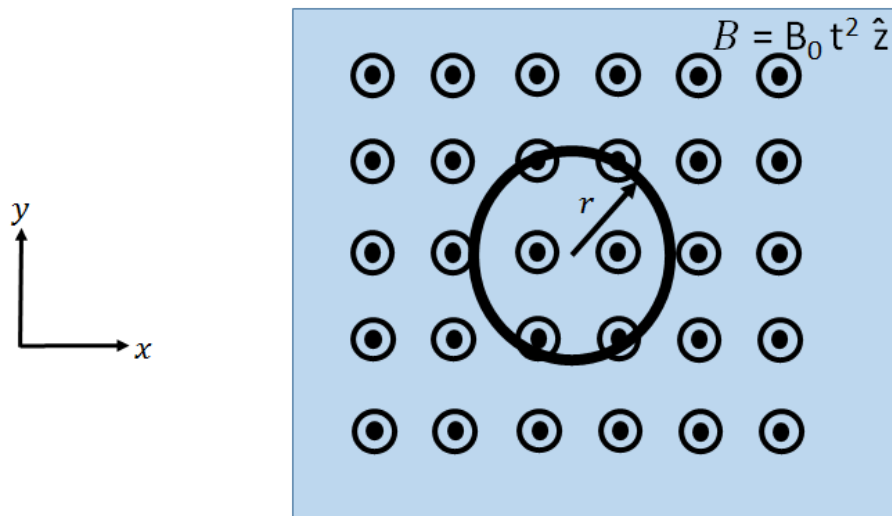Here,  $r = 5.5$  cm,  $R = 7 \Omega$ , and  $B_0 = 5$  mT/s<sup>2</sup>.



21) What is the magnetic flux through the wire at  $t = 5.1$  sec?

- a.  $\Phi = 0.0012 T \cdot m^2$
- b.  $\Phi = 4.8 \times 10^{-5} T \cdot m^2$
- c.  $\Phi = 0.0095 T \cdot m^2$

22) What is the magnitude of the induced current at  $t = 3.7$  sec?


- a.  $I = 1.8 \times 10^{-4} A$
- b.  $I = 5 \times 10^{-5} A$
- c.  $I = 6.5 \times 10^{-4} A$
- d.  $I = 0 A$
- e.  $I = 3.5 \times 10^{-4} A$

23) As time increases, the heat dissipated in the loop :

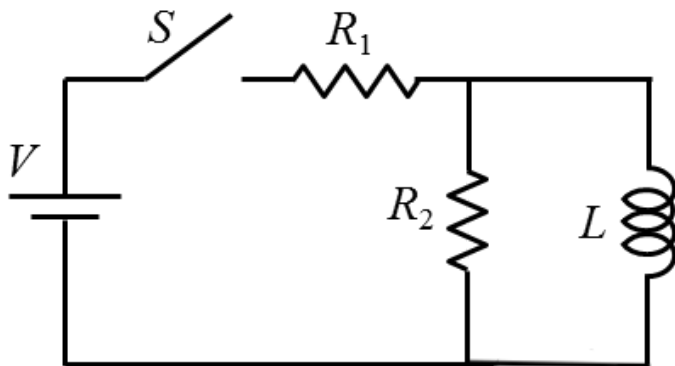- a. Stays the same
- b. Decreases
- c. Increases

The next two questions pertain to the situation described below.

A circuit is constructed with two resistors and one inductor as shown in the Figure below. The values for the resistors are:  $R_1 = 3.5 \Omega$  and  $R_2 = 6 \Omega$ . The battery voltage is  $V = 13 \text{ V}$ . The switch  $S$  is initially open.



24) After the switch has been opened a long time, it is closed. What is the magnitude of the voltage across  $L$  immediately after the switch is closed?

- a. 8.2 V
- b. 0 V
- c. 4.8 V
- d. 7.6 V
- e. 13 V

25) After the switch has been closed a long time it is opened again. What is the magnitude of the current through  $R_2$  immediately after the switch is opened?

- a. 5.6 A
- b. 2.2 A
- c. 0 A
- d. 3.7 A
- e. 1.4 A