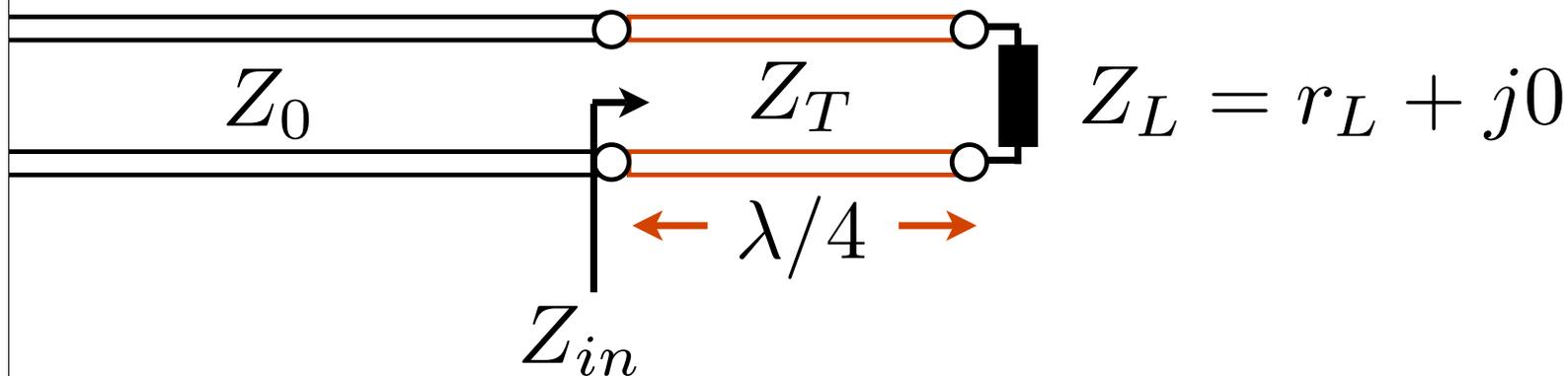


# Impedance matching via QWT

**Goal:** Design a QWT matching network such that:  $Z_{in} = Z_0$   
 $z_{in} = 1 + j0$

For  $Z_L$  purely real:



Since  $Z_{in}Z_L = Z_T^2$


a match is achieved with a T.L having:

$$Z_T = \sqrt{Z_0 Z_L}$$

# Impedance matching via QWT

**Goal:** Design a QWT matching network such that:  $Z_{in} = Z_0$


For complex  $Z_L$ :

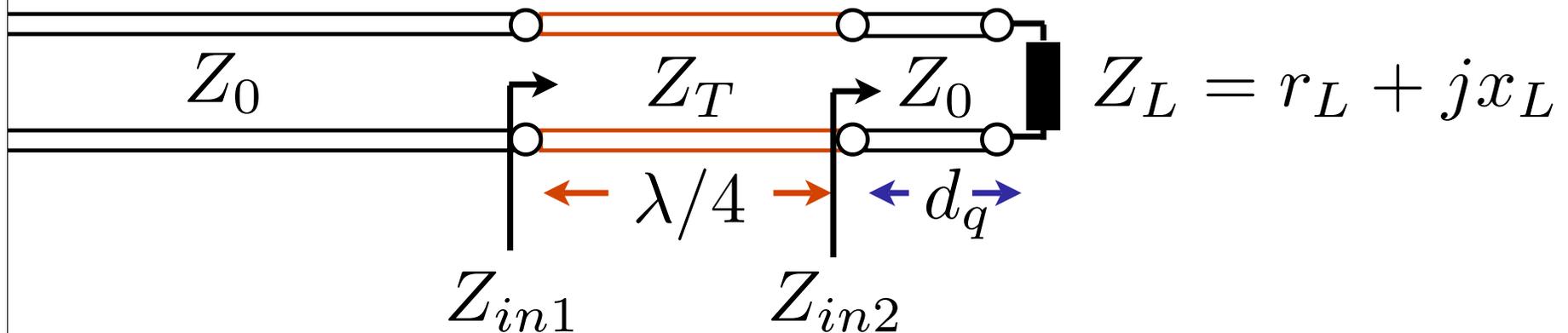

Now,  $Z_{in1} Z_{in2} = Z_0 Z_{in2} = Z_T^2$

So that  $Z_{in2} = Z_T^2 / Z_0$  must be purely real

# Single stub tuning

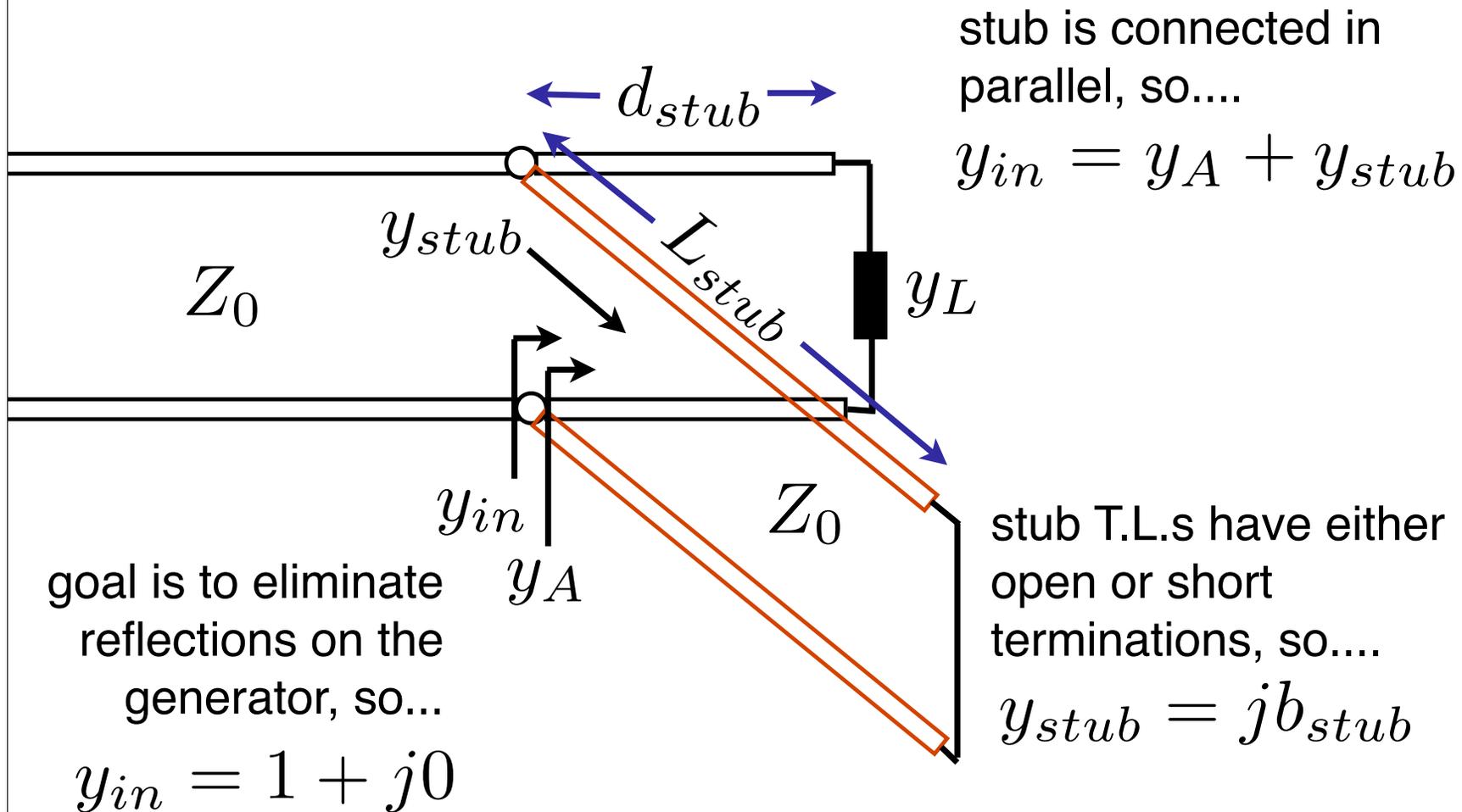


# Steps to Solve a Single-Stub Matching Problem

**Goal:** Design a single-stub matching network such that


$$Y_{IN} = Y_{STUB} + Y_A = Y_0$$

- 1) Convert the load to a normalized admittance:  $y_L = g + jb$
- 2) Transform  $y_L$  along constant  $\Gamma$  *towards generator* until  $y_A = 1 + jb_A$ 
  - This matches the network's conductance to that of the transmission line and determines  $d_{stub}$
- 3) Find  $y_{stub} = -jb_A$  on Smith Chart
- 4) Transform  $y_{STUB}$  along constant  $\Gamma$  *towards load* until we reach  $P_{SC}$  (for short-circuit stub) or  $P_{OC}$  (for open-circuit stub)
  - This cancels susceptance from (2) and determines  $L_{STUB}$

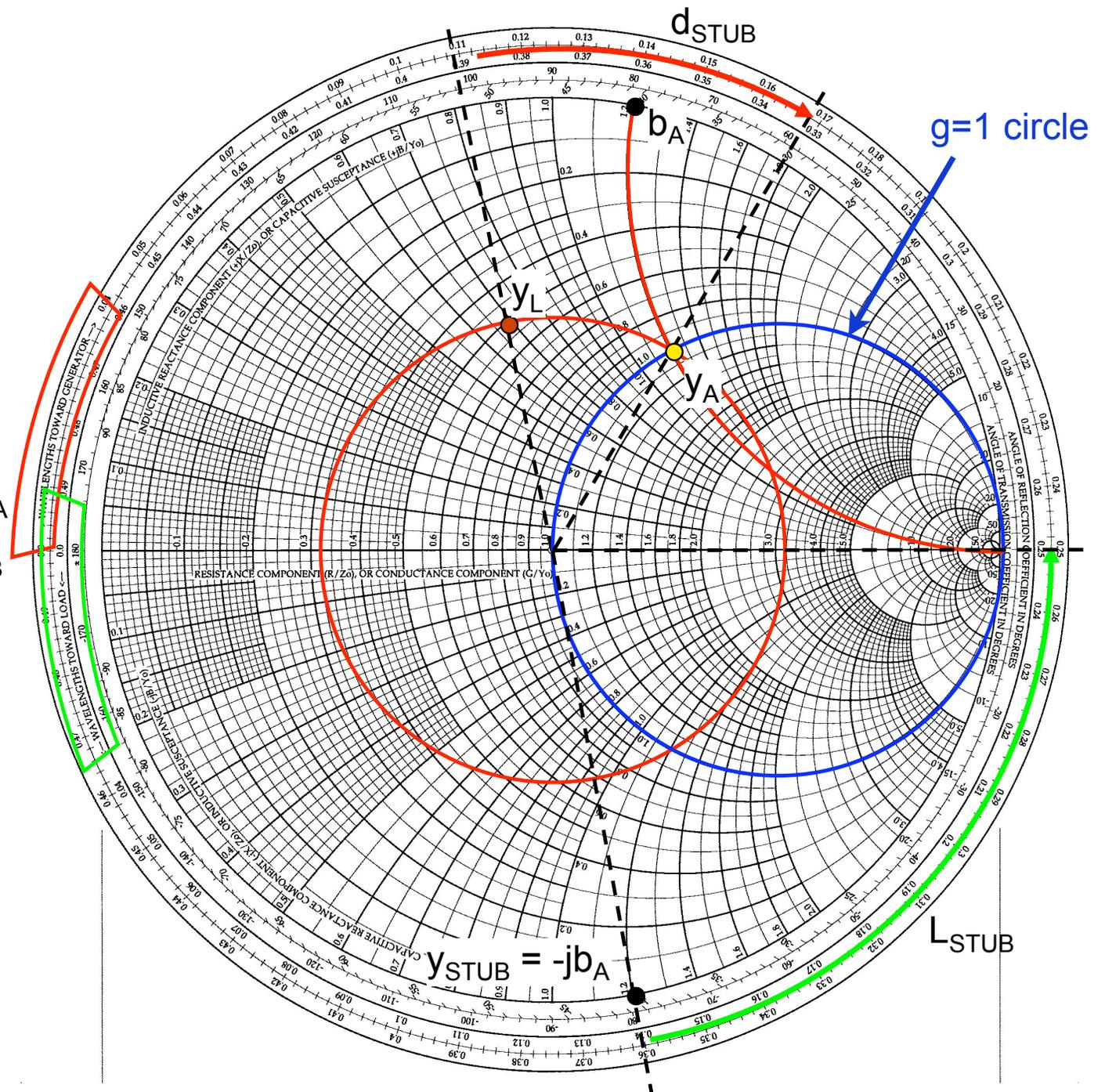
- 1) Find  $y_L$
- 2) Transform  $y_L$  to  $y_A = 1 + jb_A$
- 3) Find  $y_{STUB} = -jb_A$
- 4) Transform  $y_{STUB}$  to  $P_{SC}$  (or  $P_{OC}$ )



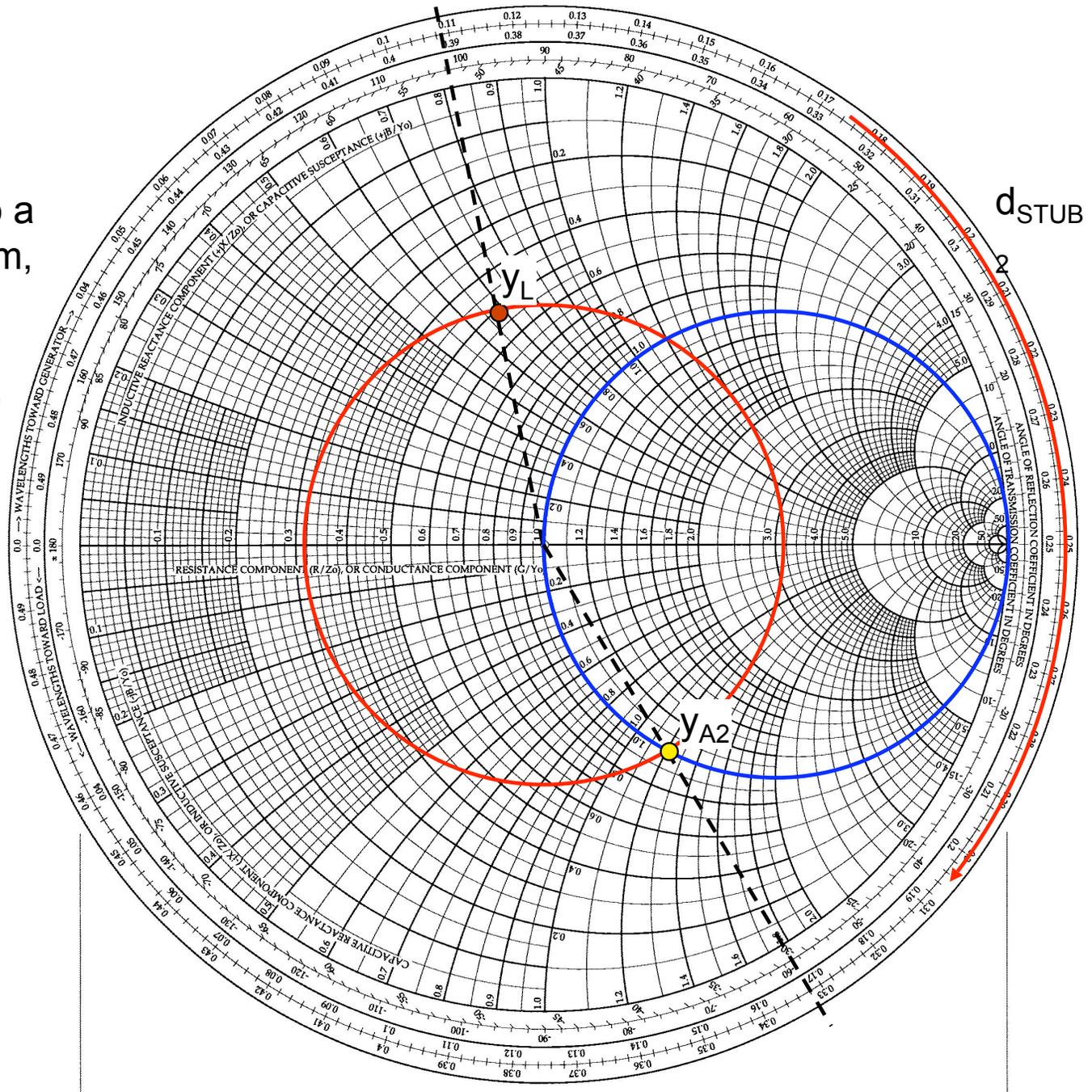There is a second solution where the  $\Gamma$  circle and  $g=1$  circle intersect. This is also a solution to the problem, but requires a longer  $d_{\text{STUB}}$  and  $L_{\text{STUB}}$  so is less desirable, unless practical constraints require it.




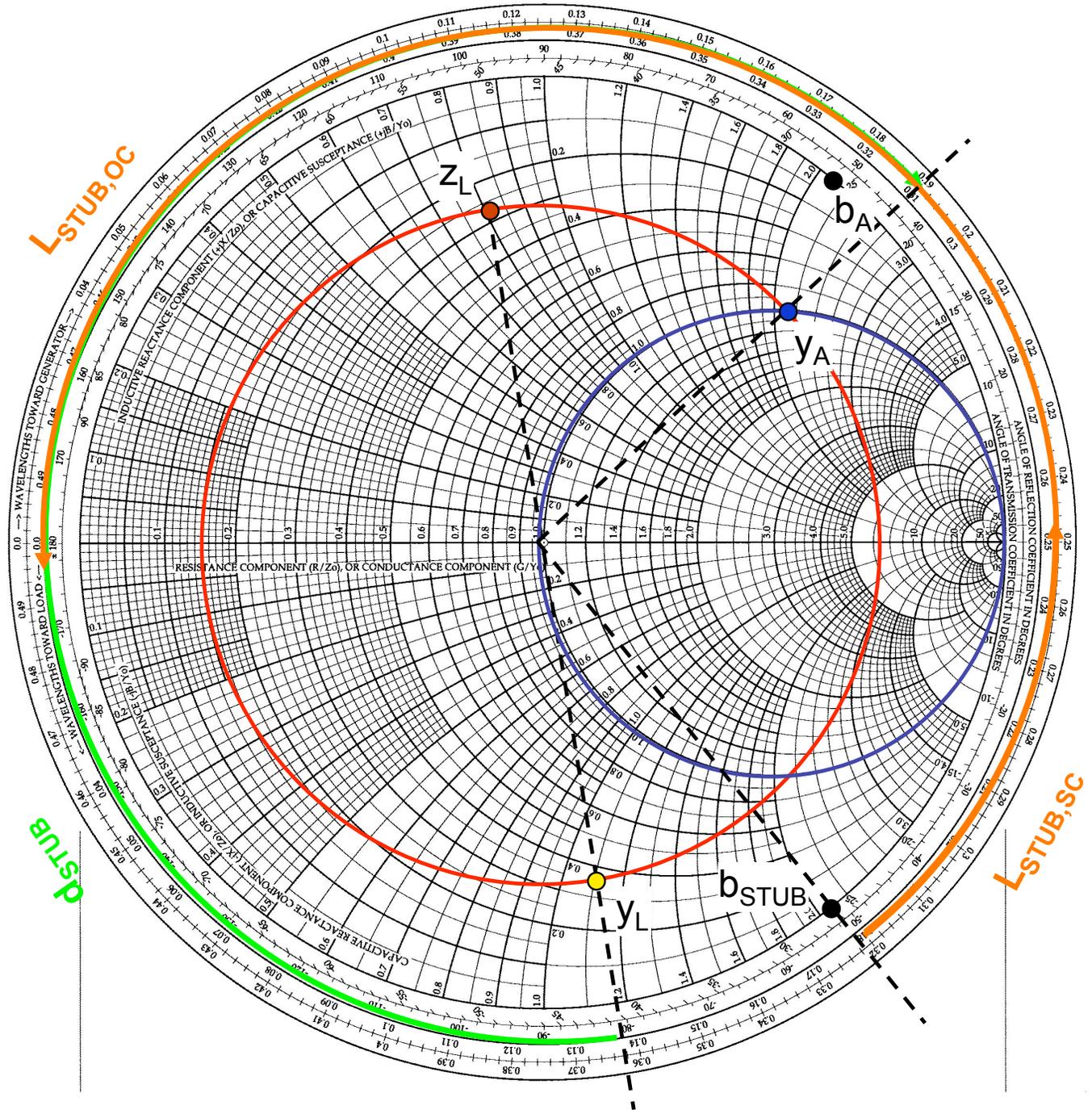- 1) Find  $y_L$
- 2) Rotate towards generator until intersection with  $g=1$  circle ( $d_{STUB}$ )
- 3) Read off  $b_A$
- 4) Find  $b_{STUB}$
- 5) Rotate towards load until stub termination is reached ( $L_{STUB}$ )



A  $50\text{-}\Omega$  T-L is terminated in an impedance of  $Z_L = 35 - j47.5$ . Find the position and length of the short-circuited stub to match it.

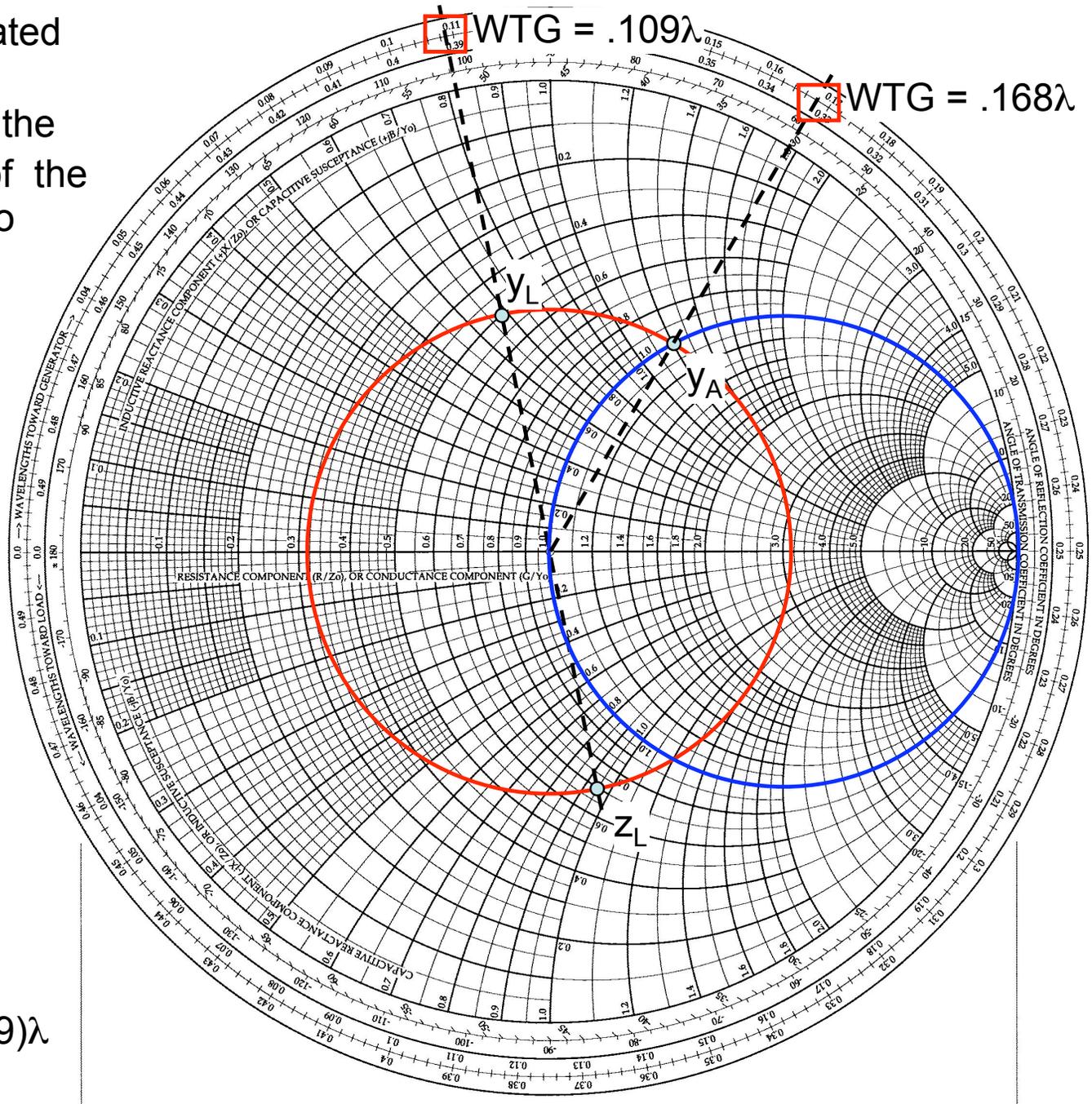- 1) Normalize  $Z_L$   
 $z_L = 0.7 - j0.95$
- 2) Find  $z_L$  on S.C.
- 3) Draw  $\Gamma$  circle
- 4) Convert to  $y_L$
- 5) Find  $g=1$  circle
- 6) Find intersection of  $\Gamma$  circle and  $g=1$  circle ( $y_A$ )
- 7) Find distance traveled (WTG) to get to this admittance
- 8) This is  $d_{\text{STUB}}$   
 $d_{\text{STUB}} = (.168 - .109)\lambda$   
 $d_{\text{STUB}} = .059\lambda$




A  $50\text{-}\Omega$  T-L is terminated in an impedance of  $Z_L = 35 - j47.5$ . Find the position and length of the short-circuited stub to match it.

- 9) Find  $b_A$
- 10) Locate  $P_{SC}$
- 11) Set  $b_{STUB} = b_A$  and find  $y_{STUB} = -jb_{STUB}$

- 12) Find distance traveled (WTG) to get from  $P_{SC}$  to  $b_{STUB}$

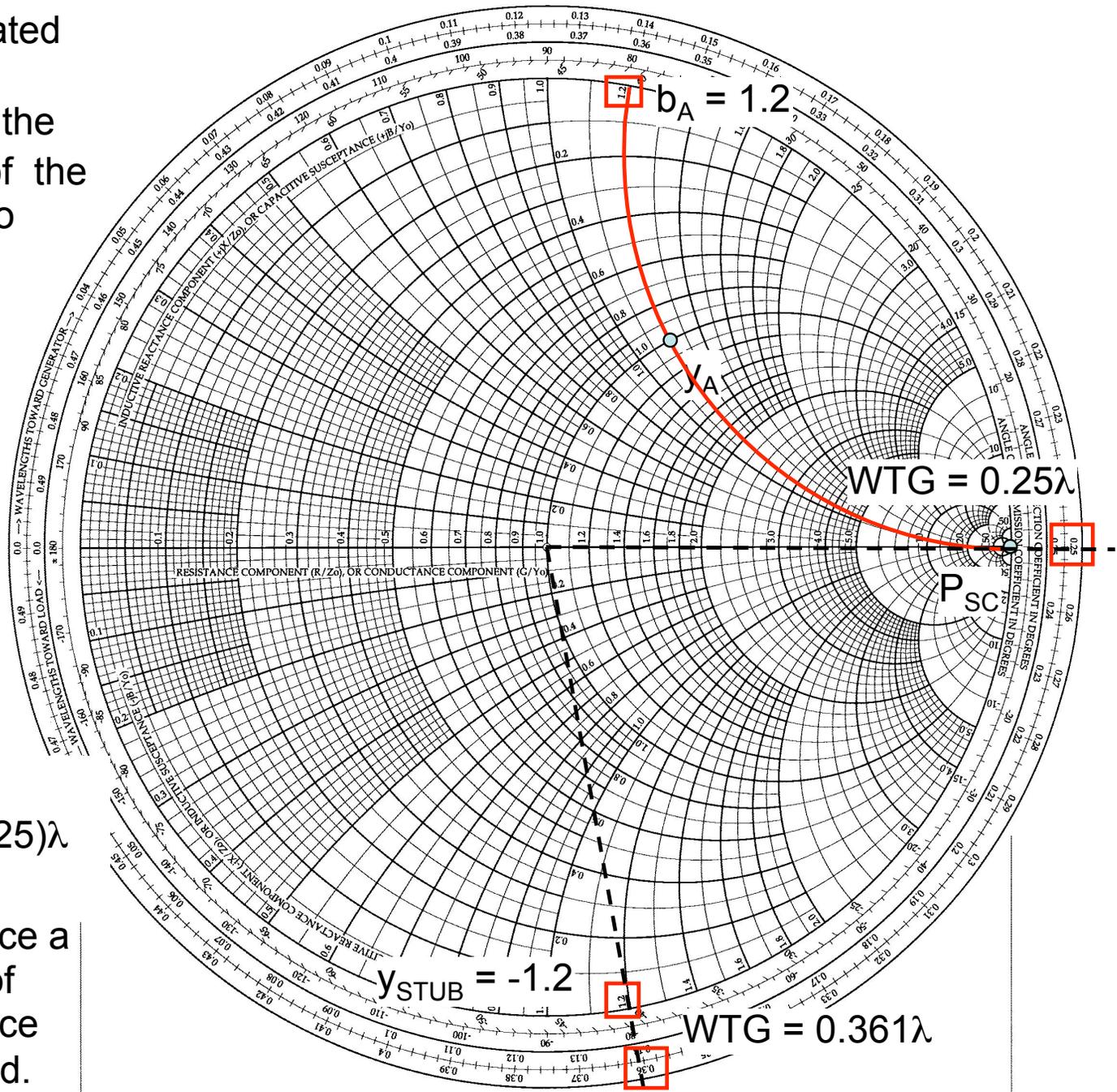- 13) This is  $L_{STUB}$   
 $L_{STUB} = (0.361 - 0.25)\lambda$   
 $L_{STUB} = .111\lambda$

Our solution is to place a short-circuited stub of length  $.111\lambda$  a distance of  $.059\lambda$  from the load.




There is a second solution where the  $\Gamma$  circle and  $g=1$  circle intersect. This is also a solution to the problem, but requires a longer  $d_{\text{STUB}}$  and  $L_{\text{STUB}}$  so is less desirable, unless practical constraints require it.

$$d_{\text{STUB}} = (.332 - .109)\lambda$$

$$d_{\text{STUB}} = .223\lambda$$


$$L_{\text{STUB}} = (.25 + .139)\lambda$$

$$L_{\text{STUB}} = .389\lambda$$

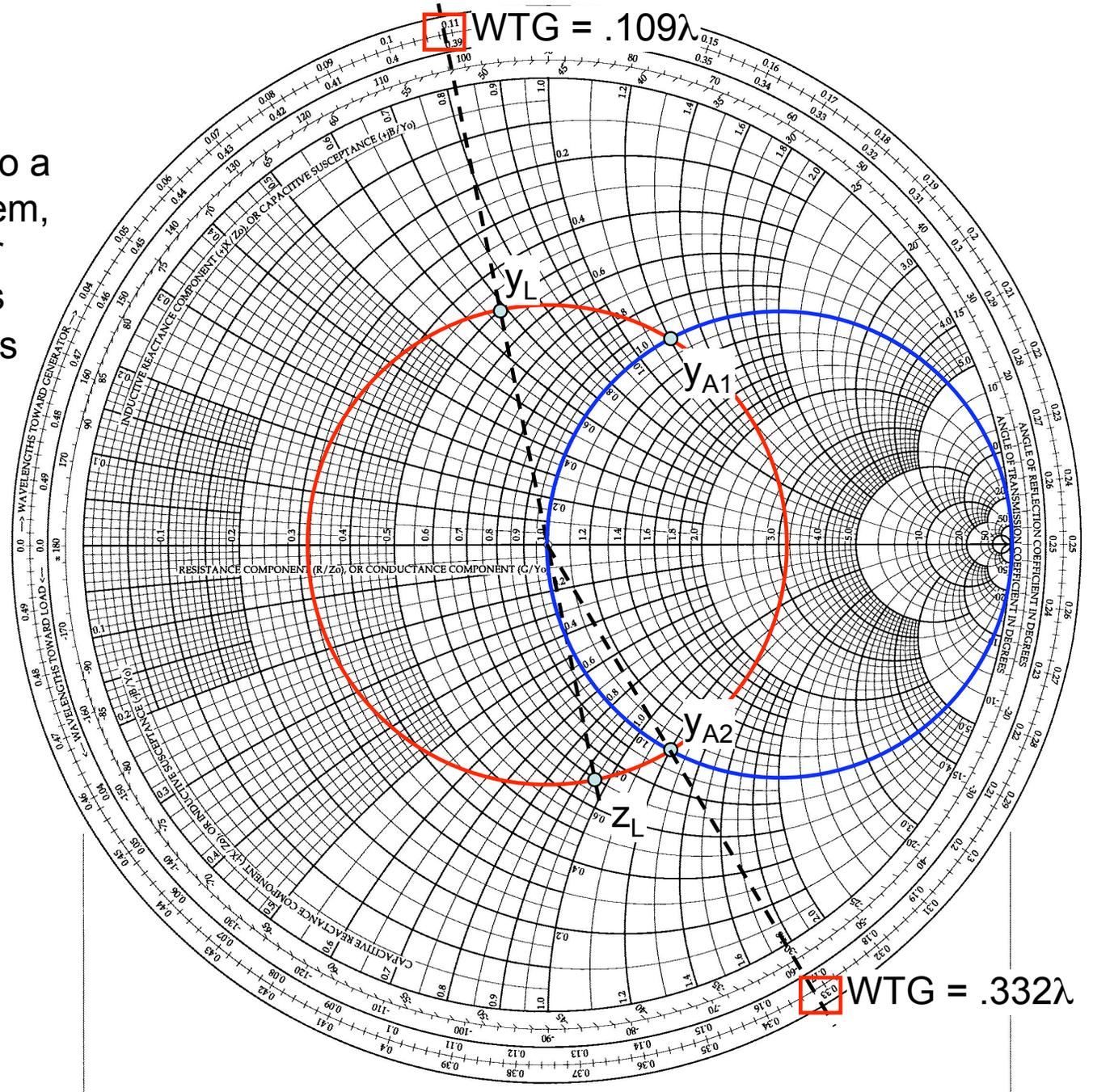
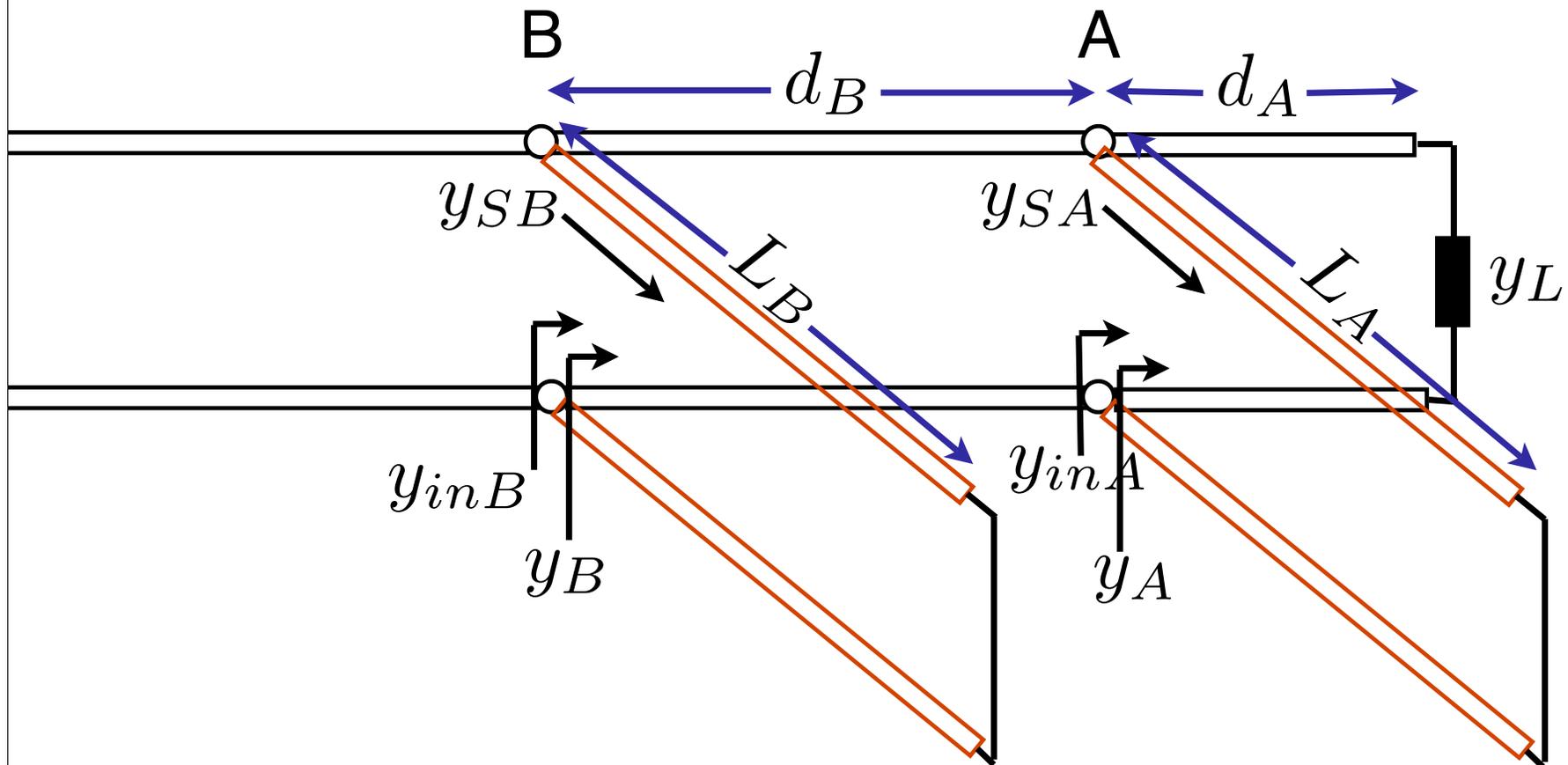
# Double stub tuning

the goal still is to  
achieve a match, so  
 $y_{inB} = 1 + j0$



# Steps to Solve a Double-Stub Matching Problem


**Goal:** Design a double-stub matching network such that

$$Y_{IN,A} = Y_0$$

- 1) Convert the load to a normalized admittance:  $y_L = g + jb$
- 2) Transform  $y_L$  along constant  $\Gamma$  *towards generator* by distance  $d_A$  to reach  $y_A = g_A + jb_A$
- 3) Draw auxiliary circle (pivot of  $g=1$  circle by distance  $d_B$ )
- 4) Add susceptance ( $b$ ) to  $y_A$  to get to  $y_{IN,A}$  on auxiliary circle. The amount of susceptance added is equal to  $-b_{SA}$ , the input susceptance of stub A.
- 5) Find  $y_{SA} = -jb_{SA}$ . Determine  $L_A$  by transforming  $y_{SA}$  along constant  $\Gamma$  *towards load* until we reach  $P_{SC}$  (for short-circuit stub) or  $P_{OC}$  (for open-circuit stub).
- 6) Transform  $y_{IN,A}$  along constant  $\Gamma$  *towards generator* by distance  $d_B$  to reach  $y_B$  on auxiliary circle. The susceptance of  $y_B$  ( $b_B$ ) is equal to  $-b_{SB}$ , the input susceptance of stub B.
- 7) Find  $y_{SB} = -jb_{SB}$ . Determine  $L_B$  by transforming  $y_{SB}$  along constant  $\Gamma$  *towards load* until we reach  $P_{SC}$  (for short-circuit stub) or  $P_{OC}$  (for open-circuit stub).

To solve a double-stub tuner problem:

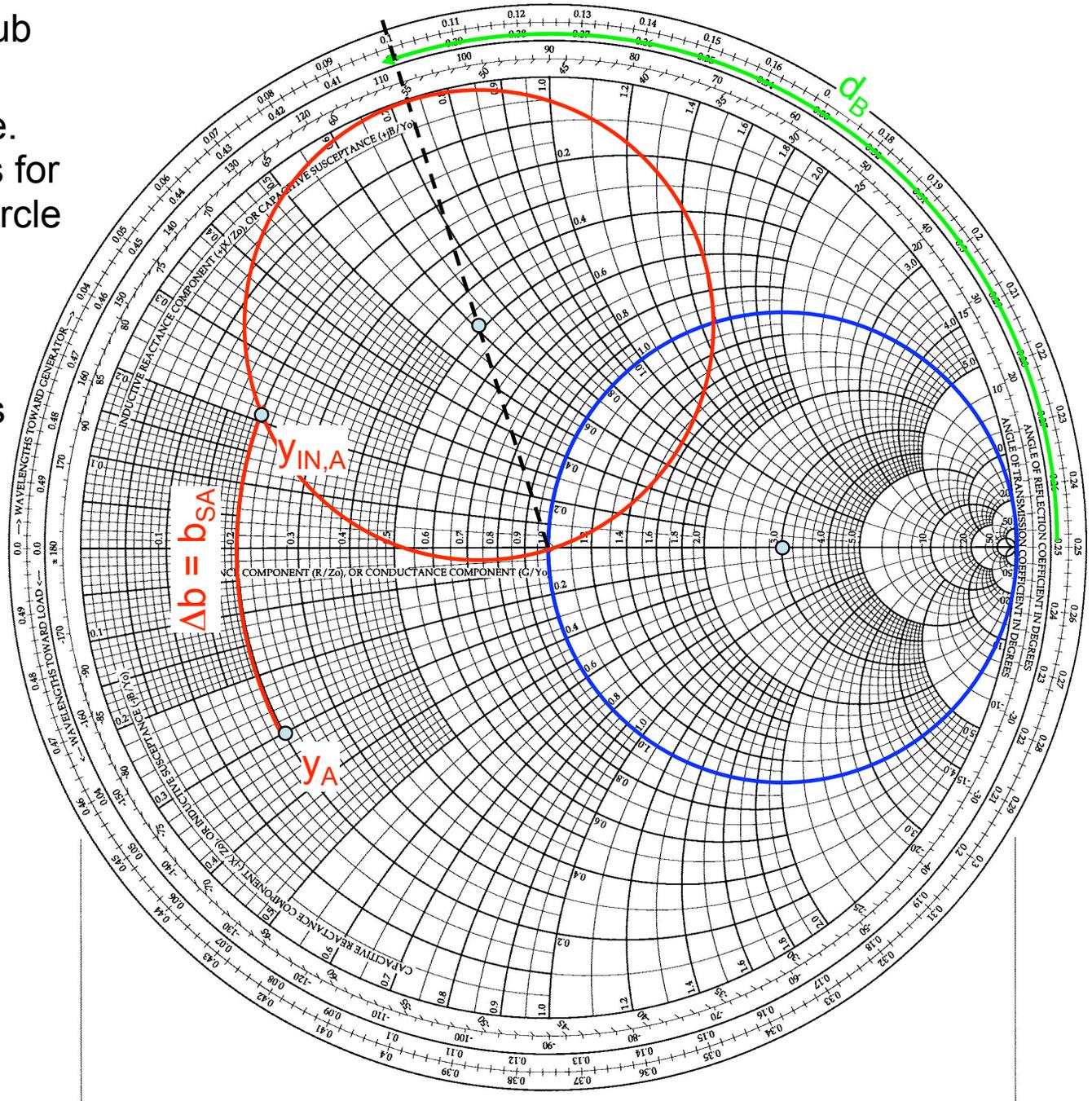- 1) Find the  $g=1$  circle. All possible solutions for  $y_B$  must fall on this circle
- 2) Rotate the  $g=1$  circle a distance  $d_B$  towards the load. These are the values at the input to the **A** junction that will transform to the  $g=1$  circle at junction **B**
- 3) Find  $y_A$  on chart
- 4) Rotate along the constant  $g$  circle to find the intersection with the rotated  $g=1$  circle. The change in  $b$  to do this is the susceptance at the input to the stub at junction **A**




5) To find the admittance at junction B ( $y_B$ ), rotate  $y_{IN,A}$  towards the generator by  $d_B$ . If we've drawn everything right, this will intersect the  $g=1$  circle.

6) Read off the value for  $b_B$ . This is  $-b_{SB}$  for the stub at junction B

6) Calculate the length of the B stub by rotating towards the load from  $b_{SB}$  to the appropriate stub termination ( $P_{SC}$  or  $P_{OC}$ )

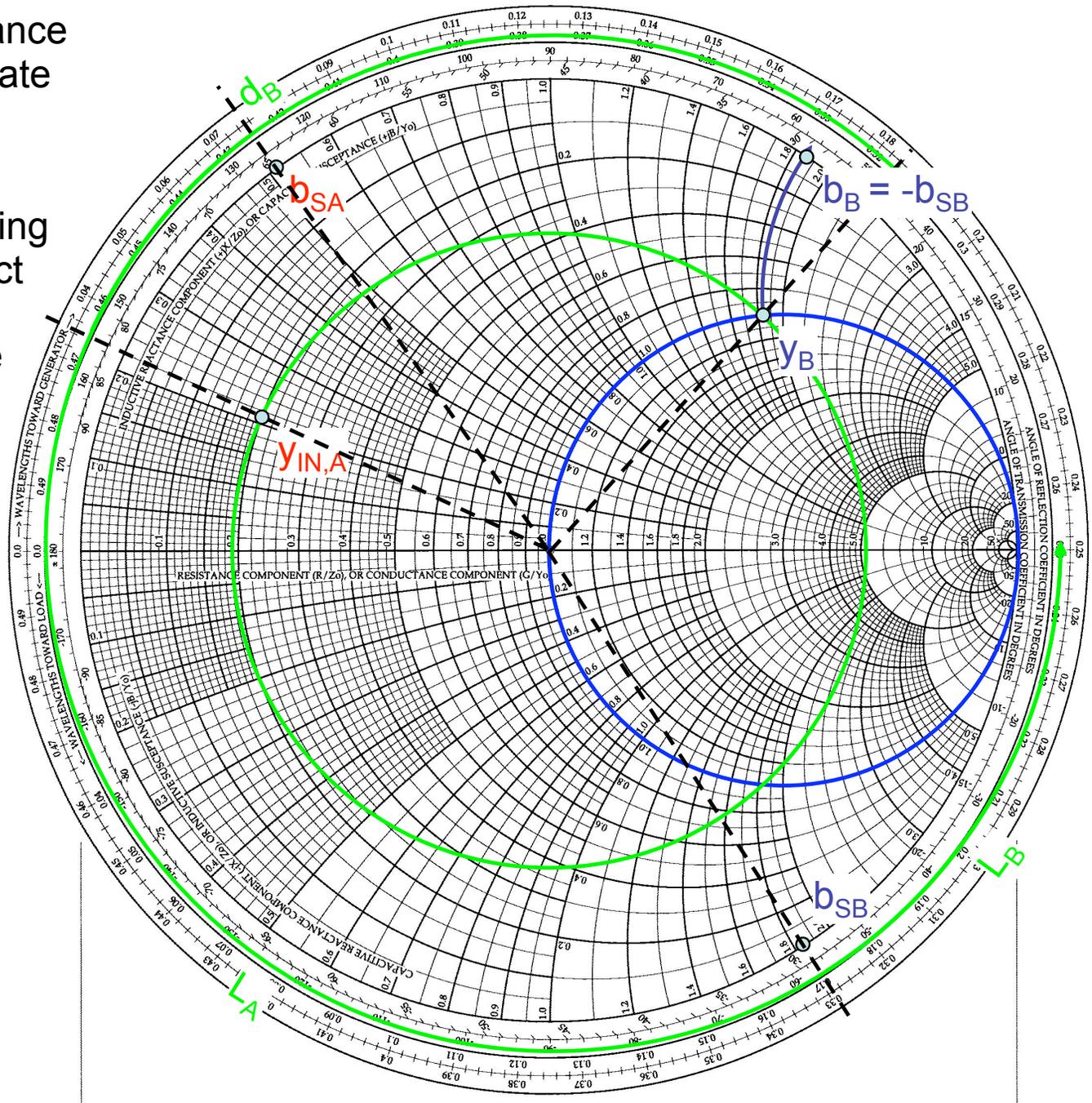6) Calculate the length of the A stub in the same way starting from  $b_{SA}$



Similar to the single-stub network, there are multiple lengths for the stubs that will work.

There is a range of  $y_A$  that cannot be matched  
Irregardless of the short/open stub properties, we will never intersect the rotated  $g=1$  circle.

