

ECE 330

POWER CIRCUITS AND ELECTROMECHANICS

LECTURE 2

ACTIVE, REACTIVE, AND COMPLEX POWER

Acknowledgment-These handouts and lecture notes given in class are based on material from Prof. Peter Sauer's ECE 330 lecture notes. Some slides are taken from Ali Bazi's presentations

Disclaimer- These handouts only provide highlights and should not be used to replace the course textbook.

8/30/2017


ECE ILLINOIS

Copyright © 2017 Hassan Sowidan

 ILLINOIS

TWO-TERMINAL NETWORK

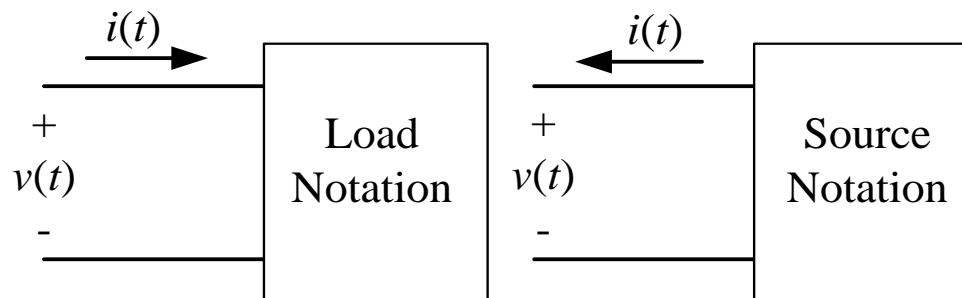- A two-terminal electrical network has voltage at its terminals and current flowing in and out of its terminals.



- The instantaneous power is $p(t) = v(t) i(t)$.
- For $i(t) = I_m \cos(\omega t + \theta_i)$ A and $v(t) = V_m \cos(\omega t + \theta_v)$ V we get

$$p(t) = V_m I_m \cos(\omega t + \theta_v) \cos(\omega t + \theta_i)$$

TWO-TERMINAL NETWORK

$$\cos \alpha \cos \beta = \frac{1}{2} [\cos(\alpha - \beta) + \cos(\alpha + \beta)]$$

$$p(t) = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) + \frac{V_m I_m}{2} \cos(2\omega t + \theta_v + \theta_i) \quad \text{W}$$

The first term is time-independent, while the second term is a sinusoid at double frequency.

TWO-TERMINAL NETWORK

- The average power is thus

$$P = \frac{1}{T} \int_0^T P(t) dt, \quad T = \frac{2\pi}{\omega}$$

$$P_{in} = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i).$$


- This is called the active or real power and its unit is watts (W).
- The power factor is the cosine of the phase angle between $v(t)$ and $i(t)$.

POWER FACTOR

- The power factor ($P.F.$) is thus $P.F. = \cos(\theta_v - \theta_i)$.
- The power factor can be:

- Lagging: $0^\circ < \theta_v - \theta_i < 90^\circ$
- Leading: $-90^\circ < \theta_v - \theta_i < 0^\circ$
- Unity: $\theta_v - \theta_i = 0$

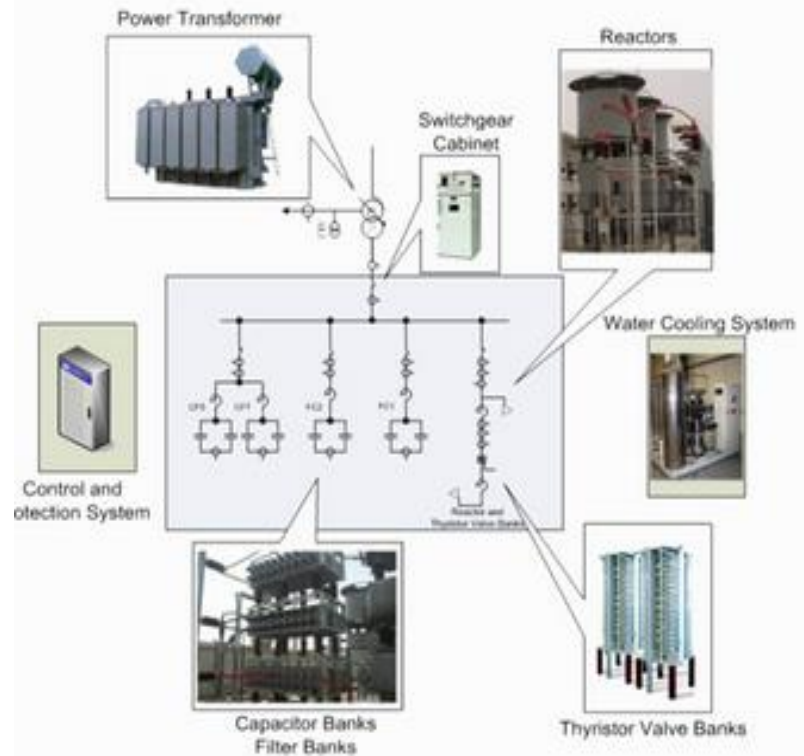Therefore, $0 \leq P.F. \leq 1$,
and the highest real power
exists when $P.F.=1$.



Source: grupovision.com

APPARENT POWER AND REACTIVE POWER

- The apparent power is $S = \frac{V_m I_m}{2}$
- The apparent power unit is volt-amps (VA).
- The reactive power is $Q_{in} = \frac{V_m I_m}{2} \sin(\theta_v - \theta_i)$.
- The reactive power unit is volt-amps-reactive (VARs).

COMPLEX POWER

- The instantaneous power is

$$p(t) = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) + \frac{V_m I_m}{2} \cos(2\omega t + \theta_v + \theta_i) \quad \text{W}$$

- The time varying component

$$\begin{aligned} \frac{V_m I_m}{2} \cos(2\omega t + \theta_v + \theta_i) &= \frac{V_m I_m}{2} \left\{ \cos[(2\omega t + 2\theta_i) + (\theta_v - \theta_i)] \right\} \\ &= \frac{V_m I_m}{2} \cos(2\omega t + 2\theta_i) \cos(\theta_v - \theta_i) - \frac{V_m I_m}{2} \sin(2\omega t + 2\theta_i) \sin(\theta_v - \theta_i) \end{aligned}$$

COMPLEX POWER

- Define

$$Q_{in} = \frac{V_m I_m}{2} \sin(\theta_v - \theta_i), \quad (\text{Reactive power})$$

$$\begin{aligned} p(t) &= P_{in} + P_{in} \cos(2\omega t + 2\theta_i) - Q_{in} \sin(2\omega t + \theta_i) \\ &= P_{in} (1 + \cos(2\omega t + \theta_i)) - Q_{in} \sin(2\omega t + 2\theta_i) \end{aligned}$$

- The real power can be written as

$$P_{in} = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) = V_{rms} I_{rms} \cos(\theta_v - \theta_i)$$

PHASOR REPRESENTATION

$$P_{in} = \text{Re}\left\{\frac{V_m I_m}{2} e^{j\theta_v} e^{-j\theta_i}\right\} = \text{Re}\{V_{rms} e^{j\theta_v} I_{rms} e^{-j\theta_i}\}$$

- The reactive power can be written as


$$Q_{in} = \text{Im}\left\{\frac{V_m I_m}{2} e^{j\theta_v} e^{-j\theta_i}\right\} = \text{Im}\{V_{rms} e^{j\theta_v} I_{rms} e^{-j\theta_i}\}$$

- The voltages and currents can be written as phasors:

$$V_{rms} e^{j\theta_v} = \bar{V} \quad \text{and} \quad I_{rms} e^{j\theta_i} = \bar{I}.$$

$$P_{in} = \text{Re}(\bar{V} \bar{I}^*) = V_{rms} I_{rms} \cos(\theta_v - \theta_i)$$
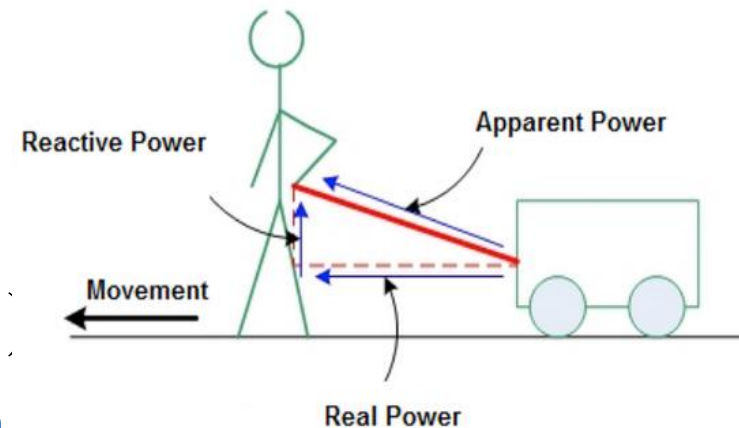
$$Q_{in} = \text{Im}(\bar{V} \bar{I}^*) = V_{rms} I_{rms} \sin(\theta_v - \theta_i)$$



Source: Tonex.com


Complex Power

- Define the complex power as $\bar{S} = P_{in} + jQ_{in}$
- Then \bar{S} can be written as $\bar{S} = \bar{V} \bar{I}^*$
- The quantity \bar{I}^* is the complex conjugate of \bar{I} .
- \bar{S} can also be written as

$$\bar{S} = S \angle(\theta_v - \theta_i)$$

- Note that
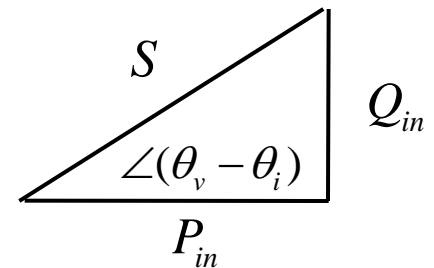
$$S = \frac{V_m I_m}{2} = \sqrt{P_{in}^2 + Q_{in}^2}$$




ALTERNATE FORMS OF COMPLEX POWER

- If the load is $\bar{Z} = R + jX$, connected across the source \bar{V}
By Ohm's law: $\bar{V} = \bar{Z} \bar{I}$, but $\bar{S} = \bar{V} \bar{I}^*$
Then \bar{S} can be written as $\bar{S} = I^2 R + jI^2 X$ Also,
 $P = I^2 R$ and $Q = I^2 X$, \bar{Z} and $P.F. = \cos(\text{angle}(\bar{Z}))$.
- Thus, $Q > 0$ when \bar{Z} is inductive, $X = \omega L$
and $Q < 0$ when \bar{Z} is capacitive, $X = -\frac{1}{\omega C}$
- \bar{S} and \bar{Z} are not phasors but complex quantities.

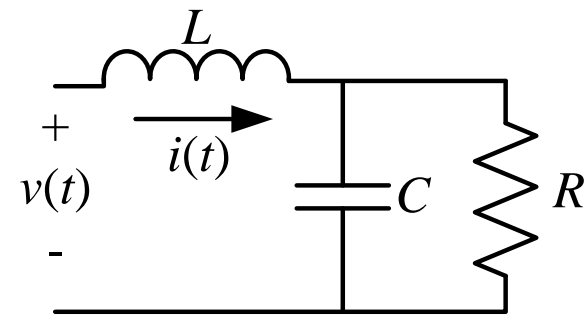EXAMPLE: LC FILTER AND R LOAD

- The circuit shown is commonly used as an LC filter to supply a load, which is resistive in this case.
- Find the current, real, reactive, and complex powers, and the P.F. for $v(t) = \sqrt{2}V_{rms} \cos(377t)$

$$\bar{Z} = j\omega L + \left(R // \frac{-j}{\omega C} \right)$$
$$\bar{Z} = \frac{\omega L + j(\omega^2 RLC - R)}{\omega RC - j}$$



EXAMPLE: LC FILTER AND R LOAD

- Let $V_{rms} = 120V$, $L = 1mH$, $C = 6.8mF$, and $R = 10\Omega$.

$$\bar{Z} = 0.0197 \angle -39.41^\circ = 0.0152 - j0.0125\Omega$$

$$\bar{I} = \frac{\bar{V}}{\bar{Z}} = \frac{120 \angle 0^\circ}{0.0197 \angle -39.41^\circ} = 6091.4 \angle 39.41^\circ \text{ A}$$


$$i(t) = 6091.4\sqrt{2} \cos(377t + 39.41^\circ)$$

$$\bar{S} = \bar{V} \bar{I}^* = 731 \angle -39.41^\circ \text{ kVA}$$

$$P_{in} = 731 \cos(-39.41^\circ) = 564.8 \text{ kW}$$

$$Q_{in} = 731 \sin(-39.41^\circ) = -464.1 \text{ kVAR}$$
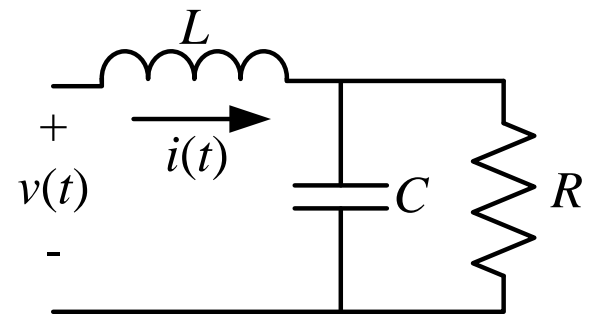
$$\text{P.F.} = \cos(-39.41^\circ) = 0.773 \text{ leading } (\theta_v - \theta_i = -39.41^\circ)$$



READING MATERIAL

- Reading material: Chapter 2 sections 2.1 – 2.3.
- Recommended reading for next time: section 2.4.