

2018-08-29-1

* No Class
Friday November 16, 2018

* Sections 2.1-2.3 in textbook

Last time:

$$v(t) = V_m \cos(\omega t + \theta_v)$$

$$i(t) = I_m \cos(\omega t + \theta_i)$$


$$V_{RMS} = \frac{V_m}{\sqrt{2}} \quad I_{RMS} = \frac{I_m}{\sqrt{2}}$$

$$\mathbf{V} = V_{RMS} \angle \theta_v$$

$$\mathbf{I} = I_{RMS} \angle \theta_i$$

* Today: Why use RMS values instead of peak values?

What is complex power?

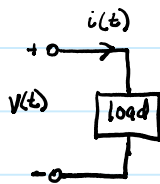

* Single phase: 1 voltage and 1 current

Instantaneous power: $p(t) = v(t)i(t)$

$$\text{let } v(t) = V_m \cos(\omega t + \theta_v)$$

$$i(t) = I_m \cos(\omega t + \theta_i)$$

$$p(t) = V_m I_m \cos(\omega t + \theta_v) \cos(\omega t + \theta_i)$$

Recall: $\cos(A+B) = \cos A \cos B - \sin A \sin B$

$$\cos(A-B) = \cos A \cos B + \sin A \sin B$$

$$\cos A \cos B = \frac{\cos(A+B) + \cos(A-B)}{2}$$

$$\Rightarrow p(t) = \frac{V_m I_m}{2} \left[\cos(2\omega t + \theta_v + \theta_i) + \cos(\theta_v - \theta_i) \right]$$

$$\begin{aligned} \cos(2\omega t + \theta_v + \theta_i) &= \cos(2\omega t + 2\theta_i + \theta_v - \theta_i) = \cos(2(\omega t + \theta_i) + (\theta_v - \theta_i)) \\ &= \cos(2(\omega t + \theta_i)) \cos(\theta_v - \theta_i) - \sin(2(\omega t + \theta_i)) \sin(\theta_v - \theta_i) \end{aligned}$$

* $\cos(2\omega t + \theta_v + \theta_i)$ term
causes pulses in power
 \Rightarrow pulses in torque for
motors and generators
BAD!!

$$p(t) = \frac{V_m I_m}{2} \left[(1 + \cos(2\omega t + 2\theta_i)) \cos(\theta_v - \theta_i) \right] - \frac{V_m I_m}{2} \sin(2\omega t + 2\theta_i) \sin(\theta_v - \theta_i)$$

2018-08-29-2

Recall: $V_{RMS} = \frac{V_m}{\sqrt{2}}$ $I_{RMS} = \frac{I_m}{\sqrt{2}}$

$$\frac{V_m I_m}{2} = \left(\frac{V_m}{\sqrt{2}}\right) \left(\frac{I_m}{\sqrt{2}}\right) = V_{RMS} I_{RMS}$$

$$p(t) = V_{RMS} I_{RMS} \left[(1 + \cos(2\omega t + 2\theta_i)) \cos(\theta_v - \theta_i) - \sin(2\omega t + 2\theta_i) \sin(\theta_v - \theta_i) \right]$$

* Using RMS values simplifies the power calculation. No longer have $\frac{1}{2}$ front factor.

* Leads to the question: what is the average power P over a cycle?

$$P = \frac{1}{T} \int_0^T p(t) dt \Rightarrow P = \frac{1}{T} \int_0^T V_{RMS} I_{RMS} \left[\cos(\theta_v - \theta_i) + \cos(2\omega t + 2\theta_i) \cos(\theta_v - \theta_i) - \sin(2\omega t + 2\theta_i) \sin(\theta_v - \theta_i) \right] dt$$

* The integral of a sinusoid over a multiple of its period is 0

$$\Rightarrow P = \frac{V_{RMS} I_{RMS}}{T} \cos(\theta_v - \theta_i) T \Rightarrow \boxed{P = V_{RMS} I_{RMS} \cos(\theta_v - \theta_i)}$$

We can use this to rewrite the instantaneous power as

$$p(t) = P(1 + \cos(2\omega t + 2\theta_i)) - Q \sin(2\omega t + 2\theta_i)$$

* Now, define the Reactive Power Q


$$Q = V_{RMS} I_{RMS} \sin(\theta_v - \theta_i)$$

$$p(t) = P(1 + \cos(2\omega t + 2\theta_i)) - Q \sin(2\omega t + 2\theta_i)$$

$$P = V_{RMS} I_{RMS} \cos(\theta_v - \theta_i)$$

$$Q = V_{RMS} I_{RMS} \sin(\theta_v - \theta_i)$$

Recall the complex plane

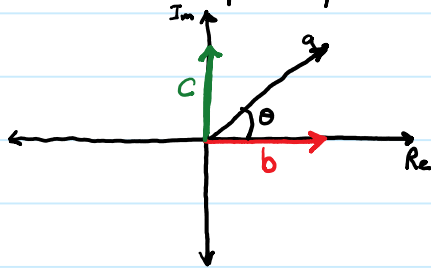

$$b = \operatorname{Re} \{ a e^{j\theta} \} = a \cos(\theta)$$

$$c = \operatorname{Im} \{ a e^{j\theta} \} = a \sin(\theta)$$

$$P = V_{\text{RMS}} I_{\text{RMS}} \cos(\theta_v - \theta_i) = \operatorname{Re} \{ V_{\text{RMS}} I_{\text{RMS}} e^{j(\theta_v - \theta_i)} \}$$

$$Q = V_{\text{RMS}} I_{\text{RMS}} \sin(\theta_v - \theta_i) = \operatorname{Im} \{ V_{\text{RMS}} I_{\text{RMS}} e^{j(\theta_v - \theta_i)} \}$$

$$P = \operatorname{Re} \{ V_{\text{RMS}} e^{j\theta_v} I_{\text{RMS}} e^{-j\theta_i} \} = \operatorname{Re} \{ (V_{\text{RMS}} \angle \theta_v) (I_{\text{RMS}} \angle -\theta_i) \} = \operatorname{Re} \{ \bar{V} \bar{I}^* \}$$

$$Q = \operatorname{Im} \{ V_{\text{RMS}} e^{j\theta_v} I_{\text{RMS}} e^{-j\theta_i} \} = \operatorname{Im} \{ (V_{\text{RMS}} \angle \theta_v) (I_{\text{RMS}} \angle -\theta_i) \} = \operatorname{Im} \{ \bar{V} \bar{I}^* \}$$

Note: \bar{I}^* means the complex conjugate of \bar{I} . Switch the sign of the imaginary terms to compute.

So, P and Q are the real and imaginary parts of some phasor $\bar{V} \bar{I}^*$.

This is called the complex power \bar{S}

$$\boxed{\bar{S} = \bar{V} \bar{I}^* = V_{\text{RMS}} I_{\text{RMS}} \angle (\theta_v - \theta_i) = P + jQ}$$

Units: \bar{S} : VA
 P : W
 Q : VAR

} Different units to emphasize different meanings

Other Nomenclature

$|\bar{S}| = S = VI$: apparent power

$\theta = \theta_v - \theta_i$: power factor angle


$\cos(\theta) = \cos(\theta_v - \theta_i)$: Power factor

2018-08-29-4

Recall $\cos(\theta)$ is an even function, meaning that $\cos(\theta) = \cos(-\theta)$.


How to distinguish between the two for the PF?

$$\theta = \theta_v - \theta_i > 0$$

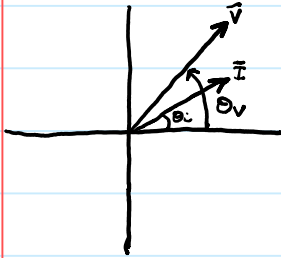

Current lags the voltage
 \Rightarrow lagging PF

$$\theta = \theta_v - \theta_i < 0$$

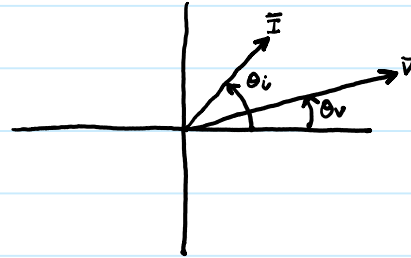


Current leads the voltage
 \Rightarrow leading PF

* Talk about current lagging or leading the voltage

$$\vec{S} = \vec{V} \vec{I}^* = V_{RMS} I_{RMS} \angle \theta_v - \theta_i = P + jQ$$

Another way to view complex power:

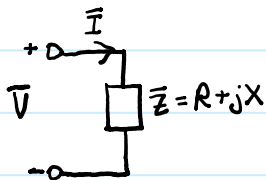

* Note: \vec{Z} is a complex number, but not a phasor. No time dependence

$$\vec{V} = \vec{Z} \vec{I}$$

$$\vec{S} = \vec{V} \vec{I}^* = (\vec{Z} \vec{I}) \vec{I}^* = \vec{Z} (\vec{I} \vec{I}^*) = \vec{Z} (I_{RMS}^2) = \vec{Z} I^2$$

$$\vec{S} = I^2 \vec{Z}$$

$$\vec{Z} = R + jX$$

$$\boxed{\vec{S} = I^2 R + j I^2 X = P + jQ}$$

P: power dissipated by resistors

Q: power dissipated by reactances (hence the name reactive power)

2018-08-29-5

* Note: when calculating an impedance $\bar{Z} = R + jX = Z \angle \theta_z$

the power factor angle $\theta = \theta_z$


$$\bar{I} = \frac{V \angle \theta_v}{Z \angle \theta_z} = \frac{V}{Z} \angle (\theta_v - \theta_z)$$

$$\bar{S} = S \angle (\theta_v - \theta_i) \Rightarrow \bar{S} = S \angle (\theta_v - \theta_z)$$

$$\boxed{\bar{S} = S \angle \theta_z}$$


* We can use this other method of viewing the complex power to understand the PF:

$$\theta = \theta_v - \theta_i > 0$$

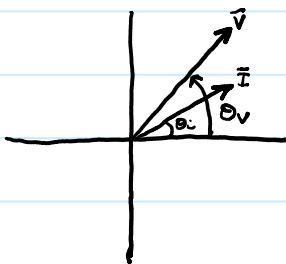

Current lags the voltage
 \Rightarrow lagging PF

$$\theta = \theta_v - \theta_i < 0$$

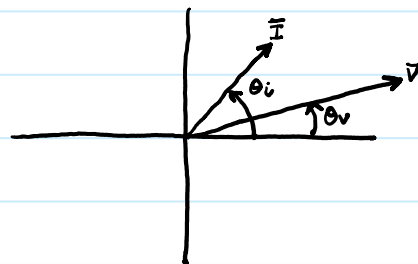

Current leads the voltage
 \Rightarrow leading PF

Lagging PF: $\theta > 0 \Rightarrow Q > 0$ (X is like an inductor)

Leading PF: $\theta < 0 \Rightarrow Q < 0$ (X is like a capacitor)

$$Q = I^2 X$$

Inductor: $X = \omega L \Rightarrow Q > 0$

Capacitor: $X = -\frac{1}{\omega C} \Rightarrow Q < 0$

Ex

$$v(t) = \sqrt{2}(10)\cos(\omega t + 30^\circ) \Rightarrow \bar{V} = 10 \angle 30^\circ \text{ V}$$

$$i(t) = \sqrt{2}(5)\cos(\omega t - 20^\circ) \Rightarrow \bar{I} = 5 \angle 20^\circ \text{ A}$$

Find: a) The complex power \bar{S}
b) The power factor

$$a) \bar{S} = \bar{V} \bar{I}^* = (10 \angle 30^\circ \text{ V})(5 \angle 20^\circ \text{ A})$$

$$\bar{S} = 50 \angle 50^\circ \text{ VA}$$

$$\bar{S} = 32.14 + j38.30 \text{ VA}$$

$$b) \text{PF} = \cos(\theta) = \cos(50^\circ)$$

$$\text{PF} = 0.643 \text{ lagging}$$

Ex

$$v(t) = \sqrt{2}(10)\cos(\omega t + 10^\circ)$$

$$i(t) = \sqrt{2}(5)\sin(\omega t + 130^\circ)$$

Find: a) complex power
b) PF

$$a) \sin(\omega t + 130^\circ) = \cos(\omega t + 130^\circ - 90^\circ) = \cos(\omega t + 40^\circ)$$

$$\bar{V} = 10 \angle 10^\circ$$

$$\bar{I} = 5 \angle 40^\circ$$

$$\bar{S} = \bar{V} \bar{I}^* = (10 \angle 10^\circ \text{ V})(5 \angle 40^\circ \text{ A})$$

$$\bar{S} = 50 \angle -30^\circ \text{ VA}$$

$$\bar{S} = 43.30 - j25 \text{ VA}$$

$$b) \text{PF} = \cos(-30^\circ)$$

$$\text{PF} = 0.866 \text{ lead}$$

$$\text{Ex} \quad v(t) = \sqrt{2}(10)\cos(\omega t + 30^\circ) = \bar{V} = 10 \angle 30^\circ \text{ V}$$

$$i(t) = \sqrt{2}(5)\cos(\omega t - 90^\circ) = \bar{I} = 5 \angle 90^\circ$$

$$\bar{S} = \bar{V} \bar{I}^* \Rightarrow \bar{S} = 50 \angle 120^\circ \text{ VA}$$

$$\bar{S} = -25 + j43.3 \text{ VA}$$

* Notes: 1) $P < 0$ means power is delivered by network rather than consumed

2) PF only defined for $|\theta| < 90^\circ$, so we can't define a PF here.