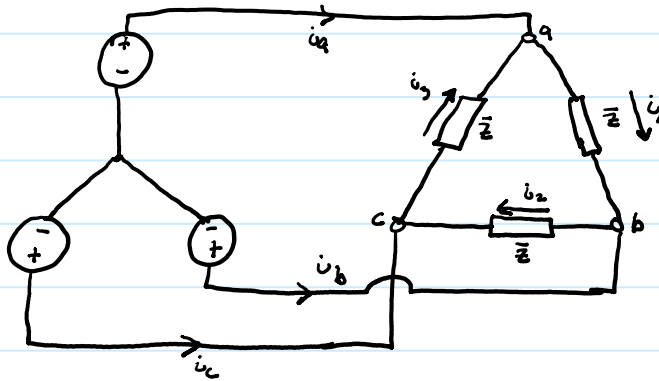


* Section 2.5 in textbook

Wye-Delta Connection




* How does i_a relate to i_1 ? or, how does line current relate to phase current?

$$\bar{I}_1 = \frac{V_{ab}}{Z} \Rightarrow \bar{I}_1 = \frac{V_L \angle 0}{Z \angle \theta} \Rightarrow \bar{I}_1 = \frac{V_L}{Z} \angle -\theta \Rightarrow \bar{I}_1 = I_\phi \angle -\theta$$


$$\bar{I}_2 = I_\phi \angle 120^\circ - \theta$$
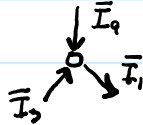
$$\bar{I}_3 = I_\phi \angle 240^\circ - \theta$$



$$\bar{I}_a = \bar{I}_1 - \bar{I}_3 \Rightarrow \bar{I}_a = \bar{I}_1 + (-\bar{I}_3)$$
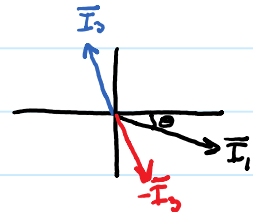
$$-\bar{I}_3 = I_\phi \angle 120^\circ - \theta + 180^\circ \Rightarrow -\bar{I}_3 = I_\phi \angle -60^\circ - \theta$$



$$\bar{I}_a = I_\phi \angle -\theta + I_\phi \angle -60^\circ - \theta$$

$$= I_\phi (\cos(\theta) - j \sin(\theta) + \cos(60^\circ + \theta) - j \sin(60^\circ + \theta))$$

$$= I_\phi (\cos(\theta) + \cos(60^\circ) \cos(\theta) - \sin(60^\circ) \sin(\theta) + j(\sin(\theta) - \sin(60^\circ) \cos(\theta) - \cos(60^\circ) \sin(\theta)))$$

$$= I_\phi \left(\frac{3}{2} \cos(\theta) - \frac{\sqrt{3}}{2} \sin(\theta) + j \left(-\frac{3}{2} \sin(\theta) - \frac{\sqrt{3}}{2} \cos(\theta) \right) \right)$$

$$\bar{I}_a = I_\phi \left[\left[\frac{3}{2} \cos(\theta) - \frac{\sqrt{3}}{2} \sin(\theta) \right] - j \left[\frac{3}{2} \sin(\theta) + \frac{\sqrt{3}}{2} \cos(\theta) \right] \right]$$

$$|\bar{I}_a| = I_\phi \sqrt{\left[\frac{3}{2} \cos(\theta) - \frac{\sqrt{3}}{2} \sin(\theta) \right]^2 + \left[\frac{3}{2} \sin(\theta) + \frac{\sqrt{3}}{2} \cos(\theta) \right]^2}$$

$$= I_\phi \sqrt{\frac{9}{4} + \frac{3}{4}}$$

$$|\bar{I}_a| = I_\phi \sqrt{3}$$

$$\theta_L = \tan^{-1} \left(\frac{-\left(\frac{3}{2} \sin(\theta) + \frac{\sqrt{3}}{2} \cos(\theta)\right)}{\frac{3}{2} \cos(\theta) - \frac{\sqrt{3}}{2} \sin(\theta)} \right)$$

$$= \tan^{-1} \left(-\frac{\left(\frac{\sqrt{3}}{2} \sin(\theta) + \frac{1}{2} \cos(\theta)\right)}{\frac{\sqrt{3}}{2} \cos(\theta) - \frac{1}{2} \sin(\theta)} \right) \Rightarrow \theta_L = \tan^{-1}(\tan(-\theta - 30^\circ)) \Rightarrow$$

$$\Rightarrow \boxed{|\bar{I}_L| = I_\phi \sqrt{3}}$$

$$\boxed{\theta_L = -30^\circ - \theta}$$



* can verify others are 120° apart.

Complex Power:

$$\begin{aligned}\bar{S} &= \bar{S}_{ab} + \bar{S}_{bc} + \bar{S}_{ca} \\ &= \bar{V}_a \bar{I}_1^* + \bar{V}_b \bar{I}_2^* + \bar{V}_c \bar{I}_3^* \\ &= (V_L \angle 0)(I_\phi \angle \theta) + (V_L \angle -120^\circ)(I_\phi \angle 120^\circ + \theta) + (V_L \angle 120^\circ)(I_\phi \angle \theta - 120^\circ)\end{aligned}$$

$$\boxed{\bar{S} = 3V_L I_\phi \angle \theta}$$

$$I_\phi = \frac{I_L}{\sqrt{3}}$$

$$\begin{aligned}\bar{S} &= \sqrt{3} V_L I_L \angle \theta \\ P &= \sqrt{3} V_L I_L \cos(\theta) \\ Q &= \sqrt{3} V_L I_L \sin(\theta)\end{aligned}$$

* Same as for
wye connected load!!

Ex | Delta connected load

$$P = 24 \text{ kW} \quad \text{PF} = 0.8 \text{ lag}$$

$$V_L = 480 \text{ V}$$

Find: a) I_L and I_ϕ

b) \bar{S}

Solution: a) $P = \sqrt{3} V_L I_L (\text{PF})$

$$I_L = \frac{P}{\sqrt{3} V_L (\text{PF})} \Rightarrow \boxed{I_L = 36.08 \text{ A}}$$

$$I_L = I_\phi \sqrt{3}$$

$$I_\phi = \frac{I_L}{\sqrt{3}} \Rightarrow \boxed{I_\phi = 20.83 \text{ A}}$$

b) $\cos(\theta) = 0.8$

$$\theta = 36.87^\circ$$

$$\bar{S} = \sqrt{3} V_L I_L \angle 36.87^\circ$$

$$\boxed{\bar{S} = 30,000 \angle 36.87^\circ \text{ VA}}$$

$$\boxed{\bar{S} = 24,000 + j18,000 \text{ VA}}$$

* This is the same as the wye load
* For balanced loads, I_L and \bar{S}_{tot}
don't change if P and PF don't change.


2018-09-10-3

Ex] Problem 2.23

$$S_{\text{TOT}} = 1000 \text{ kVA}$$

$$V_L = 4160 \text{ V}$$

$$\text{PF} = 0.8 \text{ lag}$$

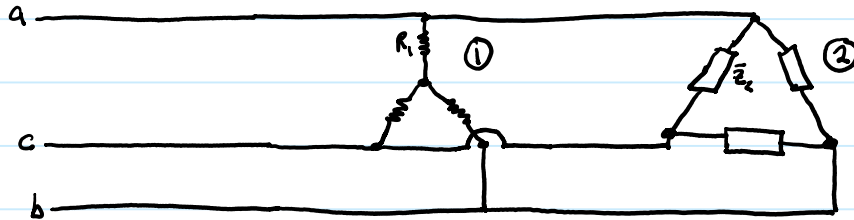

$$P_1 = 200 \text{ kW}$$

Find: a) \bar{S}_2

b) \bar{Z}_2

$$a) \bar{S}_{\text{TOT}} = \bar{S}_1 + \bar{S}_2$$

$$\bar{S}_2 = \bar{S}_{\text{TOT}} - \bar{S}_1$$

$$\bar{S}_2 = 1000 \text{ kVA} (0.8 + j0.6) - (200 \text{ kW} + j0)$$

$$\bar{S}_2 = 800 + j600 - 200 \text{ VA}$$

$$\bar{S}_2 = 600 + j600 \text{ kVA}$$

$$= 600\sqrt{2} \angle 45^\circ \text{ kVA}$$

b) Single Phase Power in Delta load

$$\bar{S}_{1\phi} = \frac{\bar{S}_2}{3}$$

$$\bar{S}_{1\phi} = \frac{V_L^2}{\bar{Z}^*} \Rightarrow \bar{Z} = \frac{V_L^2}{\bar{S}_{1\phi}^*}$$

$$\bar{Z} = \frac{3V_L^2}{\bar{S}_2^*} \Rightarrow \bar{Z} = \frac{4160^2 (3)}{600\sqrt{2} \angle -45^\circ \text{ kVA}}$$

$$\bar{Z} = 61.2 \angle 45^\circ \Omega$$
$$\bar{Z} = 43.3 + j43.3 \Omega$$