

2018-09-12-1

Last time:

$$\overline{S}_{3\phi} = 3V_\phi I_\phi \angle \theta = \sqrt{3} V_L I_L \angle \theta \text{ for both wye and delta loads}$$

$$P_{3\phi} = 3V_\phi I_\phi \cos(\theta) = \sqrt{3} V_L I_L \cos(\theta)$$

$$Q_{3\phi} = 3V_\phi I_\phi \sin(\theta) = \sqrt{3} V_L I_L \sin(\theta)$$

Answers to Questions:

Why Wye or Delta Connection?

Voltages: Wye gives  $V_\phi$

Delta gives  $V_L$

\* If  $V_\phi$  needed, use wye connection.

Power triangle still works?


\* Yes: just remember  $\overline{S}_{3\phi} = 3V_\phi I_\phi = \sqrt{3} V_L I_L$

Today: 1) Per phase equivalents

Section 2.6 in Textbook


2) HW set up

Wye Source to Wye Load

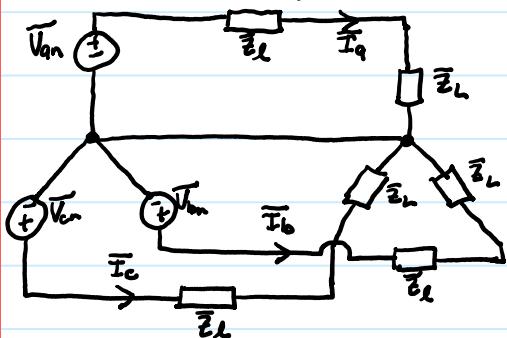

\* We want to calculate  $\overline{I}_a, \overline{I}_b, \overline{I}_c$

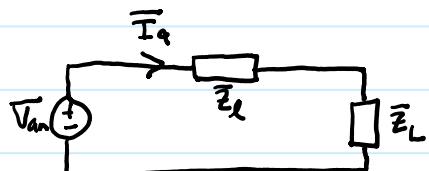\* Simplify calculations by first examining only a phase




$$\boxed{\overline{I}_a = \frac{\overline{V}_{an}}{\overline{Z}_L + \overline{Z}_L}}$$

\* To get  $\overline{I}_b$  and  $\overline{I}_c$ , just rotate by  $120^\circ$ .

2018-09-12-2

### Wye Source to Delta Load

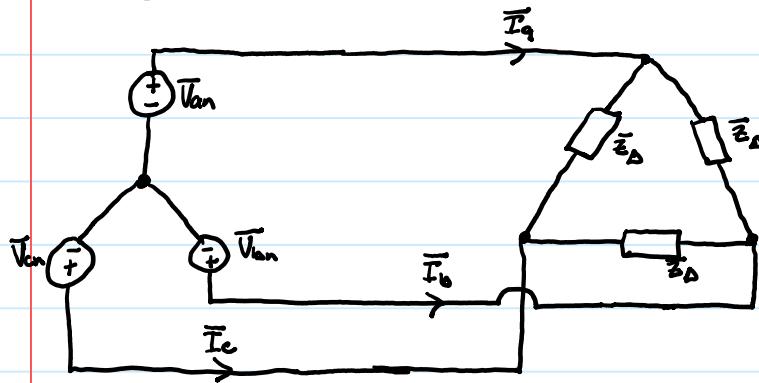

$$\begin{aligned} \bar{V}_{an} &= V_\phi / \Delta \Rightarrow \bar{V}_{ab} = V_\phi \sqrt{3} / 30^\circ \\ \bar{V}_{bc} &= V_\phi \sqrt{3} / -90^\circ \\ \bar{V}_{ca} &= V_\phi \sqrt{3} / 150^\circ \end{aligned} \quad \left. \right\} \text{Wye Rules}$$

$$\bar{I}_{ab} = \frac{\bar{V}_{ab}}{\bar{Z}_\Delta} = \frac{\sqrt{3} V_\phi}{\bar{Z}_\Delta} / 30^\circ$$

$$\bar{I}_a = \underbrace{(\sqrt{3} / 30^\circ) \bar{I}_{ab}}_{\Delta \text{ rules}} = \frac{3 V_\phi / \Delta}{\bar{Z}_\Delta} \Rightarrow \bar{I}_a = \frac{V_\phi / \Delta}{\bar{Z}_\Delta / 3}$$

$$\bar{Z}_y = \frac{\bar{Z}_\Delta}{3}$$




\* Then rotate by 120° for  $\bar{I}_b$  and  $\bar{I}_c$

2018-09-12-3

### Homework Setup

2.1(b)

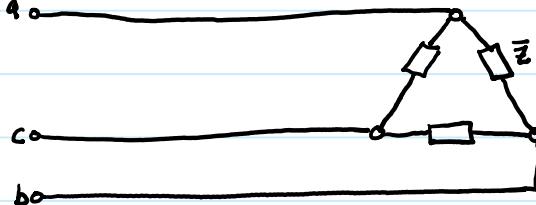

Given:  $V_L = 345 \text{ V}$        $S_{3\phi} = 750 \text{ MVA}$        $\text{PF} = 0.8 \text{ lag}$

- Find: a)  $\bar{Z}$       c)  $P_{1\phi}$  and  $Q_{1\phi}$   
 b)  $I_L$  and  $I_\phi$       d)  $\bar{S}_{3\phi}$

Solution: a)  $S_{3\phi} = \sqrt{3} V_L I_L = 3 V_L I_\phi$

$$S_{3\phi} = 3 V_L I_\phi$$


$$\bar{I}_\phi = I_\phi L^\theta = \frac{\bar{V}_L}{\bar{Z}}$$

b)  $I_\phi$  from (a).       $I_L = \sqrt{3} I_\phi$

c)  $P_{1\phi} = \frac{P_{3\phi}}{3} = \frac{S_{3\phi} \cos(\theta)}{3}$

$$Q_{1\phi} = Q_{3\phi} = \frac{S_{3\phi} \sin(\theta)}{3}$$

2.17)

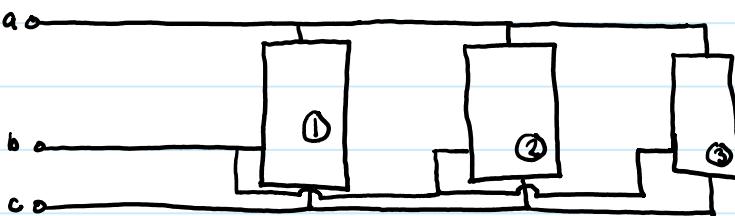

Given:  $V_L = 2400 \text{ V}$ ,       $S_1 = 120 \text{ kVA}$        $\text{PF}_1 = 0.8 \text{ lead}$ ,       $P_2 = 180 \text{ kW}$        $\text{PF}_2 = 0.6 \text{ lag}$ ,       $P_3 = 30 \text{ kW}$        $\text{PF}_3 = 1$

Find: a)  $\bar{S}_{\text{TOT}} = \bar{S}_1 + \bar{S}_2 + \bar{S}_3$


c)  $I_L = \frac{S_{\text{TOT}}}{\sqrt{3} V_L}$

b)  $\text{PF}_{\text{TOT}}$

d) QC for  $\text{PF}_{\text{TOT}} = 1$ ,  $I_L = \frac{S_{\text{TOT,new}}}{\sqrt{3} V_L}$

2018-09-12-4

2.19)

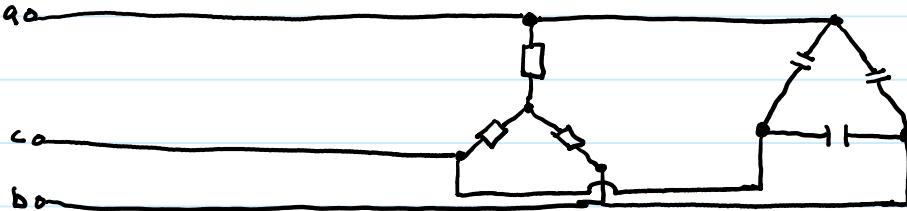

Given:  $V_L = 440 \text{ V}$        $P_{3\phi} = 120 \text{ kW}$        $\text{PF} = 0.85 \text{ lag}$  before adding capacitors

$$Q_{1\phi} = -50/3 \text{ kVAR}$$

Find: a)  $I_L$  before and after adding capacitors  
b) PF after capacitors added

Solution: a)  $P_{3\phi} = \sqrt{3} V_L I_L (\text{PF})$

$$I_L = \frac{P_{3\phi}}{\sqrt{3} V_L (\text{PF})}$$

$$\text{b) } \theta_N = \tan^{-1}\left(\frac{Q_N}{P}\right)$$

$$\text{PF}_N = \cos(\theta_N)$$

$$Q_{3\phi,0} = \sqrt{3} V_L I_L \sin(\theta_0)$$


$$Q_C = 3 Q_{1\phi}$$

$$Q_N = Q_{3\phi,0} + Q_C$$

$$S_N = \sqrt{P^2 + Q^2} = \sqrt{3} V_L I_L$$

2.20) See section on per phase equivalents

2.25)

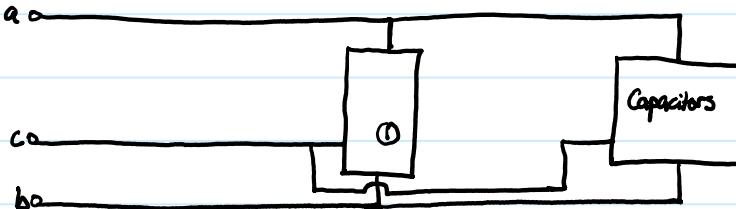

Given:  $P_i = 300 \text{ kW}$        $\text{PF}_i = 0.6 \text{ lag}$

Find:  $Q_C$  for  $\text{PF} = 0.9 \text{ lag}$

Solution: Use Power triangle

2018-09-12-5

SP1)  $V_L = 480 \text{ V}$

$$I_L = 23 \text{ A}$$

Then, capacitors added

$$Q_C = -8 \text{ kVAR}$$

$$I_L = 18 \text{ A} \quad V_L = 480 \text{ V}$$

Find: P and Q before capacitors added

Solution:  $S_1 = \sqrt{3} V_L I_{L1}$

$$S_2 = \sqrt{3} V_L I_{L2}$$

$$S_1^2 = P_1^2 + Q_1^2$$

$$S_2^2 = P_2^2 + Q_2^2$$

$$P_1^2 = S_1^2 - Q_1^2$$

$$S_2^2 = P_2^2 + (Q_1 + Q_2)^2$$

\* Substitute and solve for  $Q_1$ ,  
then get P.

SP2) Similar to other problems