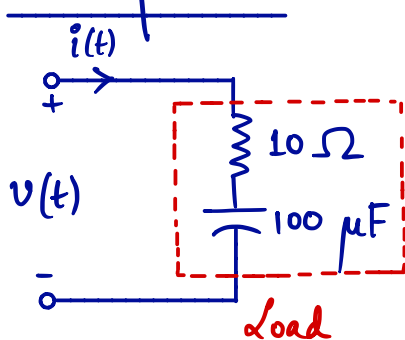


Let us put our knowledge to good use.

### Example 1



Suppose  $v(t) = 120\sqrt{2}\cos(377t)$ , where  $t$  is measured in seconds.

Compute  $i(t)$ , the apparent power drawn by the load, and its power factor

Remark: If we do not use phasors, notice that we have to utilize  $i(t) = C \cdot \frac{d}{dt} v_c$ , where  $C = 100\ \mu\text{F}$ , and  $v_c$  equals the voltage across the capacitor. Computing the current may require the solution of a differential equation. Using phasors, that computation becomes extremely simple!

$$\text{Impedance of load } (\bar{Z}) := 10 \Omega + \frac{1}{j\omega(100 \mu\text{F})},$$

$$\text{where } \omega = 377 \text{ rad/s.}$$

$$\therefore \bar{Z} = (10.00 - j 26.53) \Omega$$

Voltage phasor  $\bar{V}$  corresponding to  $v(t)$  is given by  $120 e^{j0}$  .... written as  $120 \angle 0$ .

$$\Rightarrow \bar{I} = \frac{\bar{V}}{\bar{Z}} = \frac{120 \angle 0}{10.00 - j 26.53} \text{ A} = (1.49 + j 3.96) \text{ A}$$

$$\begin{aligned} \text{In "polar" form, } \bar{I} &= 4.23 \angle 1.21 \text{ A} \\ &= 4.23 \angle 69.33^\circ \text{ A.} \end{aligned}$$

$$\begin{aligned} \Rightarrow i(t) &= 4.23 \sqrt{2} \cos(377t + 1.21). \\ &= 5.98 \cos(377t + 1.21). \end{aligned}$$

$$\begin{aligned} \bar{S} &= \bar{V} \bar{I}^* \\ &= (120 \angle 0) \cdot (4.23 \angle 69.33^\circ)^* \text{ VA} \\ &= 507.60 \angle -69.33^\circ \text{ VA.} \end{aligned}$$

$$\text{Power factor} = \cos(-69.33^\circ) = 0.35$$

leading.

---

### Example #2


Consider a parallel array of loads drawing :

- 240 kVA at a power factor of 0.5 lagging
- 150 kW at a power factor of 0.9 leading
- $200 + j100$  kVA.


Q1. Find the net apparent power drawn by the load array.

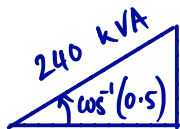Q2. How much VAR should be injected in parallel to the load array to make the resulting load have a power factor of 0.5 leading.

Let the apparent power draws of the three loads be given by  $\bar{S}_1$ ,  $\bar{S}_2$ , and  $\bar{S}_3$ .


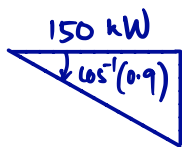
$$\bar{S}_1 = 240 \angle +60^\circ \text{ kVA}.$$



$$\bar{S}_2 = \frac{150}{0.9} \angle -\cos^{-1}(0.9) \text{ kVA}.$$

*why? answer it yourself!*


$$= 166.67 \angle -25.8^\circ \text{ kVA}.$$

$$\begin{aligned} \bar{S}_3 &= 200 + j100 \text{ kVA} \\ &= 223.61 \angle 26.57^\circ \end{aligned}$$

$\therefore$  Total power consumed by the load array is

$$\begin{aligned} \bar{S}_{\text{tot}} &= 240 \angle 60^\circ + 166.67 \angle -25.8^\circ + 223.61 \angle 26.57^\circ \\ &\quad \text{kVA} \\ &= 525.67 \angle 26.6^\circ \text{ kVA} \\ &= (470 + j235) \text{ kVA} \end{aligned}$$

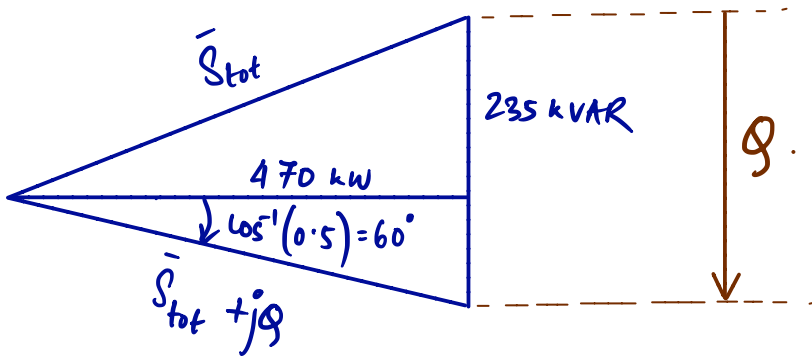To answer the second question, we need  $Q$  such that  $\bar{S}_{tot} + jQ$  has a power factor of 0.5 leading. Let's solve graphically.



$$235 \text{ kVAR} + Q = -470 \tan 60^\circ \text{ kVAR.}$$

$$\Rightarrow Q = -1049 \text{ kVAR.}$$

$\therefore$  Reactive power to the tune of 1049 kVAR needs to be extracted to achieve the desired power factor.