

# ECE 330

# POWER CIRCUITS AND ELECTROMECHANICS

## LECTURE 10

## TRANSFORMERS (4)

Acknowledgment-These handouts and lecture notes given in class are based on material from Prof. Peter Sauer's ECE 330 lecture notes. Some slides are taken from Ali Bazi's presentations

Disclaimer- These handouts only provide highlights and should not be used to replace the course textbook.

2/19/2018

**ECE ILLINOIS**

Copyright © 2017 Hassan Sowidan

 **ILLINOIS**

# EFFICIENCY

- Efficiency ( $\eta$ ) is defined as the ratio of the output power ( $P_{out}$ ) to the input power ( $P_{in}$ ).

$$\eta = \frac{P_{out}}{P_{in}} \times 100 = \frac{P_{out}}{P_{out} + P_{loss}} \times 100 = \frac{P_{in} - P_{loss}}{P_{in}} \times 100$$

- Efficiency is usually expressed as a percentage:  $\eta$  % of the input power is seen at the output.

# LOSSES

- Copper losses due to wire resistance are usually calculated as  $I^2R$  where  $I$  is the current and  $R$  is the resistance.

$$P_c = I^2 R$$

- $I$  and  $R$  on both the primary and secondary sides are considered.
- Core losses are due to hysteresis and eddy currents in the transformer.

# LOSSES

- Can be simply found as  $P_i = \frac{V_m^2}{R_c}$  where  $V_m$  is the voltage across  $R_c$ .
- Core losses are usually nonlinear, so this equation is an approximation.
- Some empirical approximations.
  - Hysteresis Losses:  $P_h = k_h f B^{1.6}$ .
  - Eddy Current Losses:  $P_e = k_e f^2 B^2$ .

# TRANSFORMER EFFECIENCHY

- In a transformer, efficiency can be calculated as follows:

$$P_c = I_1^2 R_1 + I_2'^2 R_2'$$

$$P_i = \frac{V_m^2}{R_c}$$

$$P_{in} = V_{in} I_{in} \cos(\theta_v - \theta_i)$$

$$P_{out} = I_2^2 R_L$$

$$\eta = \frac{P_{out}}{P_{in}} \times 100 = \frac{P_{out}}{P_{out} + P_c + P_i} \times 100 = \frac{P_{in} - P_c - P_i}{P_{in}} \times 100$$

# VOLTAGE REGULATION

- Voltage regulation is used to determine how well a transformer regulates its load voltage when the load varies from a certain value to no load (open circuit).

$$\%VR = \frac{|V_{no\ load} - V_{load}|}{|V_{load}|} \times 100\%$$

- Notice that the output voltage depends on the currents as they affect the voltage drop.
- Good VR is close to zero.

# TRANSFORMER NAMEPLATE

- The “Nameplate” can be found on a transformer and shows basic information about its ratings.

- Rated  $V_1/V_2$ .


- Rated kVA.

- %Z (% impedance)

$$\%Z = \frac{|Z_{eq}|}{Z_{rated}} \times 100 = \frac{\sqrt{R_{eq}^2 + X_{eq}^2}}{Z_{rated}} \times 100$$

$$Z_{rated} = \frac{|V_{rated}|}{|I_{rated}|} = \frac{V_{rated}^2}{S_{rated}}$$

# TRANSFORMER NAMEPLATE

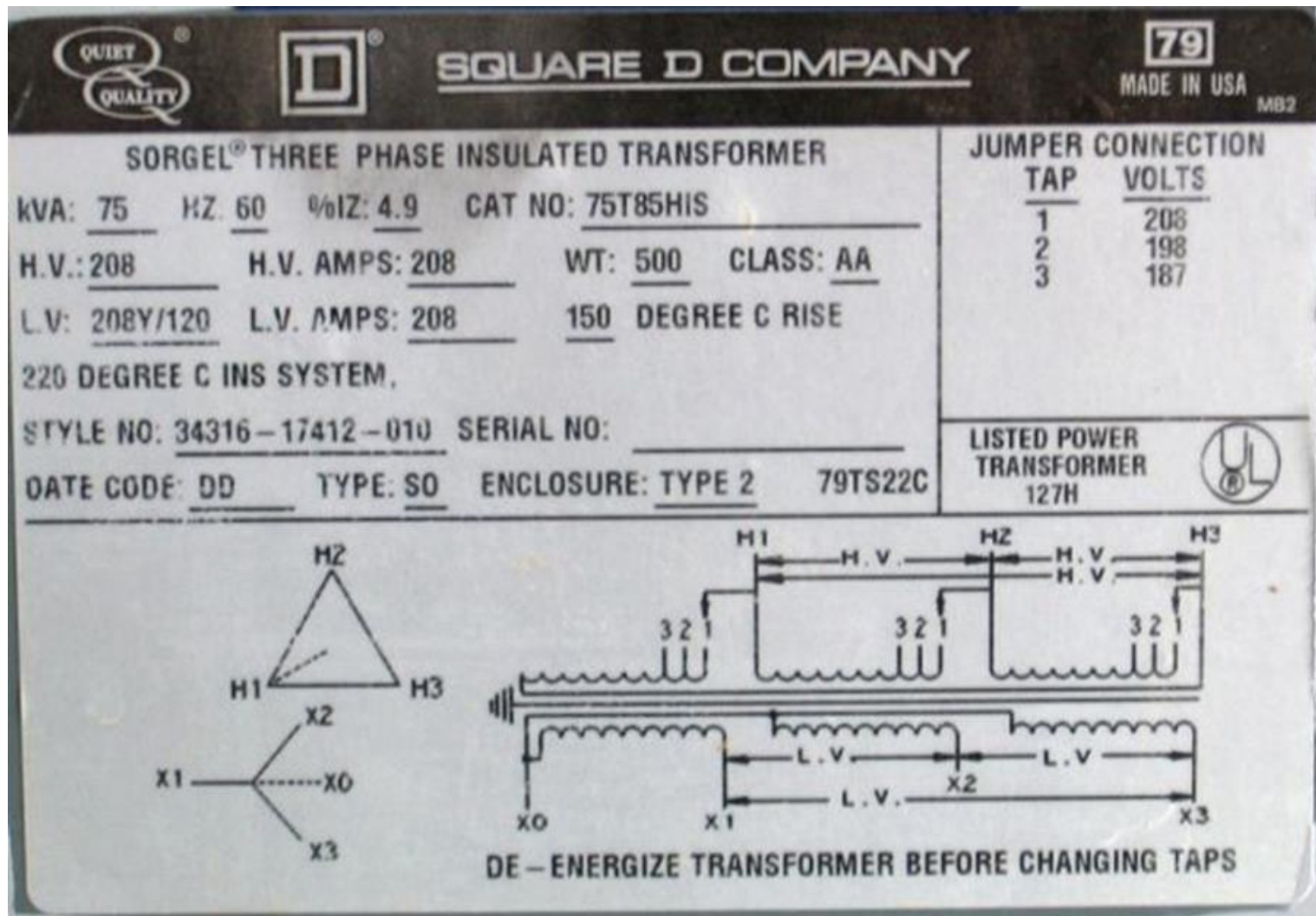

Source: emadrhc.blogspot.com

2/19/2018

**ECE ILLINOIS**

Copyright © 2017 Hassan Sowidan

**I ILLINOIS**



# SHORT-CIRCUIT CURRENT

- The short-circuit current ( $I_{sc}$ ) is a characteristic of the transformer:

$$I_{sc} = \frac{100}{\%Z} I_{rated}$$

- Example: Given  $I_{1,rated}=10$  A,  $V_{2,rated}=120$  V,  $a=2$ , find  $\%Z$  and  $I_{sc}$  for  $|Z_{eq}|$  seen from side 1 to be  $0.12 \Omega$ .

$$V_{1,rated} = aV_{2,rated} = 240 \text{ V}$$

$$Z_{1,rated} = \frac{240}{10} = 24 \Omega$$

$$\%Z = \frac{0.12}{24} \times 100 = 0.5\%$$

$$I_{sc} = \frac{100}{0.5} \times I_{rated} = 2000 \text{ A}$$