

ECE 330

POWER CIRCUITS AND ELECTROMECHANICS

LECTURE 2


CONSERVATION OF COMPLEX POWER

Acknowledgment-These handouts and lecture notes given in class are based on material from Prof. Peter Sauer's ECE 330 lecture notes. Some slides are taken from Ali Bazi's presentations

Disclaimer- These handouts only provide highlights and should not be used to replace the course textbook.

SIMPLE NETWORK

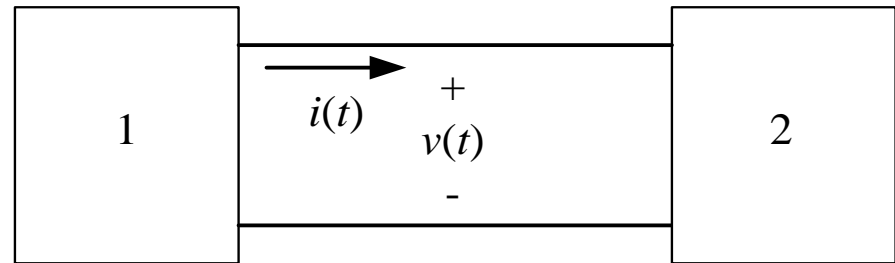- Complex power is conserved in a network.
- This can be proved in this simple network.
- Given the current direction,



$$\bar{S}_{in,1} = -\bar{V} \bar{I}^* \text{ and } \bar{S}_{out,1} = \bar{S}_{in,2} = \bar{V} \bar{I}^* \text{ and } \bar{S}_{out,2} = -\bar{V} \bar{I}^*$$


Thus, $\bar{S}_{in,1} = \bar{S}_{out,2}$, $\bar{S}_{in,1} + \bar{S}_{out,1} = 0$, and $\bar{S}_{in,2} + \bar{S}_{out,2} = 0$.

- Electric charge is conserved. All the charge that passes any point of the circuit in a given time interval must pass any other point in the same time interval.

SERIES AND PARALLEL NETWORKS


- Series network:
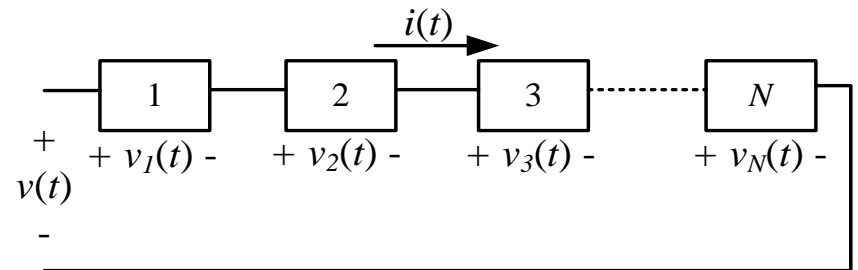
$$\begin{aligned}\bar{S}_{in} &= \bar{V}_1 \bar{I}^* + \bar{V}_2 \bar{I}^* + \bar{V}_3 \bar{I}^* + \dots + \bar{V}_N \bar{I}^* \\ &= \bar{S}_1 + \bar{S}_2 + \bar{S}_3 + \dots + \bar{S}_N\end{aligned}$$



- Parallel network

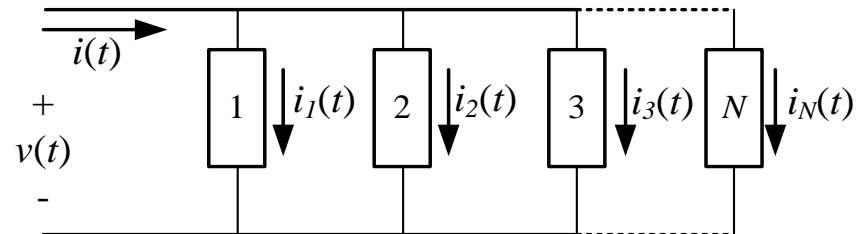
$$\begin{aligned}\bar{S}_{in} &= \bar{V} \bar{I}_1^* + \bar{V} \bar{I}_2^* + \bar{V} \bar{I}_3^* + \dots + \bar{V} \bar{I}_N^* \\ &= \bar{S}_1 + \bar{S}_2 + \bar{S}_3 + \dots + \bar{S}_N\end{aligned}$$



The total complex power is the sum of the complex powers in individual elements (power is conserved).

POWER TRIANGLE

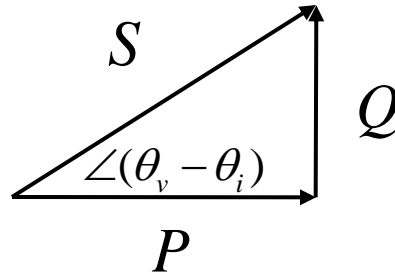- The complex power can be represented in a power triangle where $\bar{S} = P + jQ = S \angle(\theta_v - \theta_i) = S \angle \theta$




- Example:

$$\bar{V} = 120 \angle 25^\circ \text{ V}, \bar{I} = 5 \angle -15^\circ \text{ A}$$

$$\bar{S} = \bar{V} \bar{I}^* = 600 \angle 40^\circ \text{ VA}$$

$$\bar{S} = 459.6 + j385.7 \text{ VA}$$

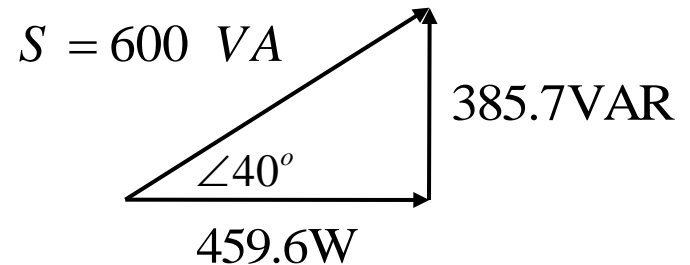

POWER TRIANGLE


- The P.F. in this example is $\cos(40^\circ)$. How can we make it unity?
- The power triangle is very useful in such an application.
- How can we make the P.F.= 0.9 lagging?

$$\theta = \cos^{-1}(0.9) = 25.84^\circ, S = \frac{459.6}{0.9} = 510.7\text{VA}$$

$$Q_{\text{new}} = 510.7 \sin(25.84^\circ) = 222.6\text{VAR}$$

$$Q_{\text{added}} = Q_{\text{new}} - Q = -163.1\text{VAR}$$
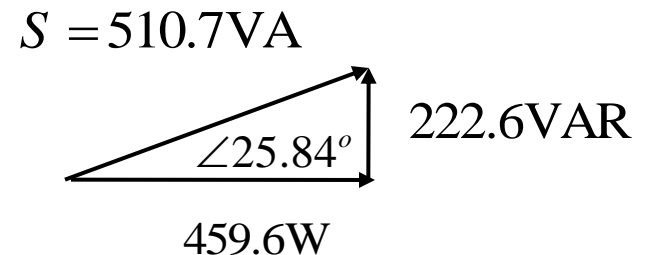
$$\text{Check: } \cos(\tan^{-1}(Q_{\text{new}} / P)) = 0.899$$



LOAD

- The load can be represented using any of these combinations:

$S(VA)$ and $P.F.$

$S(VA)$ and $P(W)$

$S(VA)$ and $Q(VAR)$

$P(W)$ and $Q(VAR)$

$\bar{V}(V)$ and $\bar{I}(A)$

$\bar{V}(V)$ and $\bar{Z}(\Omega)$

$\bar{I}(A)$ and $\bar{Z}(\Omega)$

LOAD

- Since there is need for a reference in phasor analysis, we take $\bar{V} = V \angle 0^\circ$. The power factor $PF = \cos \theta$ and $\theta = \pm \cos^{-1}(PF)$ (+ for lag and - for lead).

The current is given by $\bar{I} = I \angle -\theta$.

If \bar{V} and \bar{I} are specified it is equivalent to specifying V , I , and the PF.

LOAD

Another way is to specify V , PF , and P . Then

$$\theta = \pm \cos^{-1}(PF) (+ \text{for lag and } - \text{for lead})$$

$$P = VI \cos \theta$$

$$I = \frac{P}{V \cos \theta}$$

$$Q = VI \sin \theta$$

$$\bar{S} = P + jQ$$