

# ECE 330

# POWER CIRCUITS AND ELECTROMECHANICS

## LECTURE 4

## THREE-PHASE CONNECTIONS (2)

Acknowledgment-These handouts and lecture notes given in class are based on material from Prof. Peter Sauer's ECE 330 lecture notes. Some slides are taken from Ali Bazi's presentations

Disclaimer- These handouts only provide highlights and should not be used to replace the course textbook.


1/25/2018

**ECE ILLINOIS**

Copyright © 2017 Hassan Sowidan

 **ILLINOIS**

## Y-Δ Connection

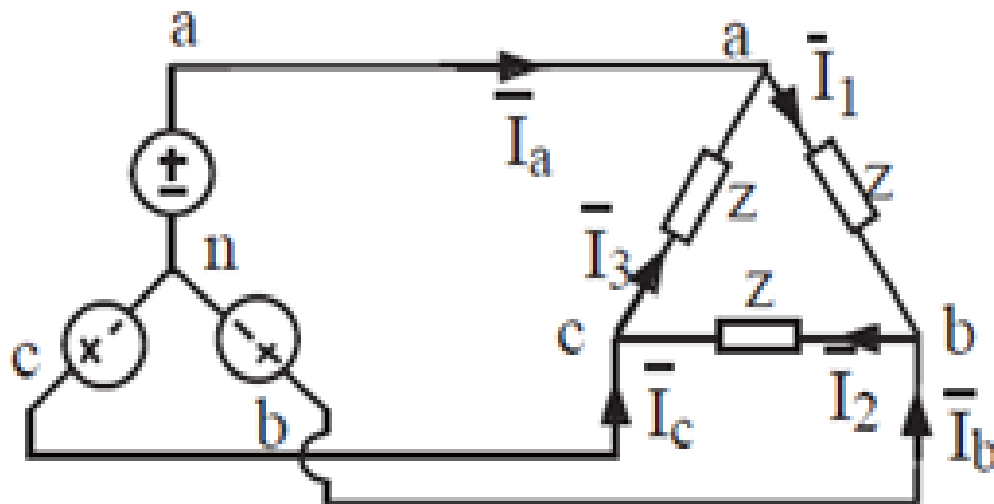

- $V_{ab}$  is assumed to be at  $0^\circ$ (reference).

$$\bar{V}_{ab} = V_{ll} \angle 0^\circ$$

$$\bar{V}_{bc} = V_{ll} \angle -120^\circ$$

$$\bar{V}_{ca} = V_{ll} \angle +120^\circ$$

## Y-Δ Connection

- Assuming  $Z = |Z| \angle \theta$ , the currents  $\bar{I}_1$ ,  $\bar{I}_2$ , and  $\bar{I}_3$  in the three phases or legs of the delta connection lag the respective voltages by  $\theta$  and called phase currents.

$$\bar{I}_1 = I_\phi \angle -\theta$$

$$\bar{I}_2 = I_\phi \angle -120^\circ - \theta$$

$$\bar{I}_3 = I_\phi \angle 120^\circ - \theta$$

- The line currents are obtained by applying KCL:

$$\bar{I}_a = \bar{I}_1 - \bar{I}_3$$

$$\bar{I}_b = \bar{I}_2 - \bar{I}_1$$

$$\bar{I}_c = \bar{I}_3 - \bar{I}_2$$

## Y-Δ Connection

- Using  $I_a$  as an example:

$$\begin{aligned}\bar{I}_a &= I_\phi \angle -\theta - I_\phi \angle 120^\circ - \theta \\&= I_\phi \cos(-\theta) + jI_\phi \sin(-\theta) - I_\phi \cos(120^\circ - \theta) - jI_\phi \sin(120^\circ - \theta) \\&= I_\phi [\cos(-\theta) - \cos(120^\circ - \theta)] + jI_\phi [\sin(-\theta) - \sin(120^\circ - \theta)] \\&= -2I_\phi \sin\left(\frac{-2\theta + 120^\circ}{2}\right) \sin(-60^\circ) + 2jI_\phi \cos\left(\frac{-2\theta + 120^\circ}{2}\right) \sin(-60^\circ) \\&= \sqrt{3}I_\phi \sin(60^\circ - \theta) - \sqrt{3}jI_\phi \cos(60^\circ - \theta) \\&\Rightarrow j\bar{I}_a = j\sqrt{3}I_\phi \sin(60^\circ - \theta) + \sqrt{3}I_\phi \cos(60^\circ - \theta) \\&= \sqrt{3}I_\phi \angle 60^\circ - \theta \\&\therefore \bar{I}_a = \sqrt{3}I_\phi \angle 60^\circ - \theta - 90^\circ = \sqrt{3}I_\phi \angle -\theta - 30^\circ\end{aligned}$$

# Y-Δ Connection

- Then,

$$\bar{I}_a = \sqrt{3}I_\phi \angle -\theta - 30^\circ$$


$$\bar{I}_b = \sqrt{3}I_\phi \angle -\theta - 150^\circ$$

$$\bar{I}_c = \sqrt{3}I_\phi \angle -\theta + 90^\circ$$

- Therefore,

$$|I_l| = \sqrt{3} |I_\phi|$$
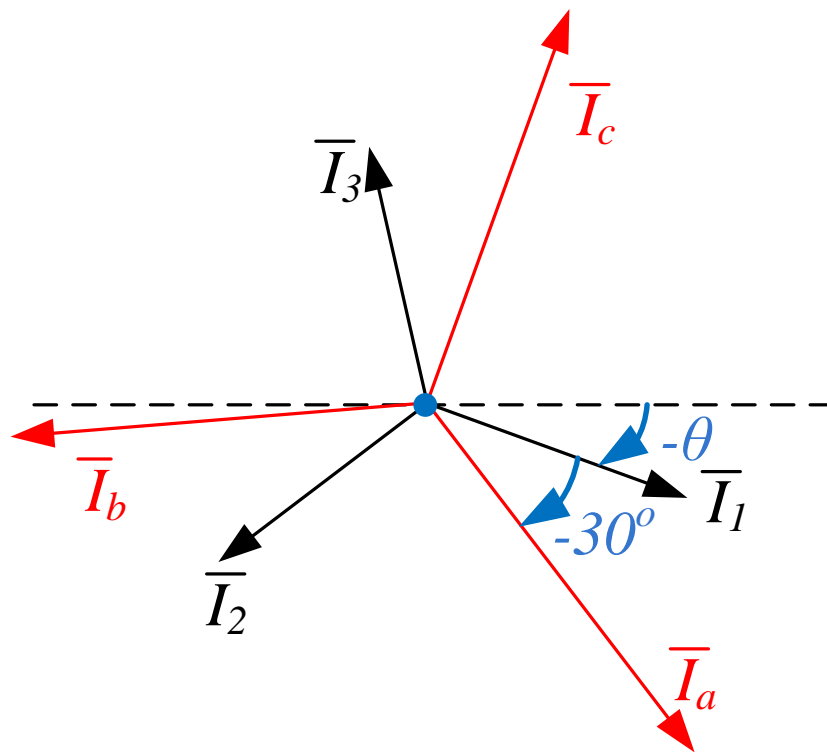
$$\angle I_l = \angle I_\phi - 30^\circ \text{ where } \{l, \phi\} \text{ are either } \{a, 1\}, \{b, 2\}, \text{ or } \{c, 3\}.$$



## Y-Δ Connection

- What about complex power?

$$\begin{aligned}\bar{S}_{3\phi} &= \bar{S}_a + \bar{S}_b + \bar{S}_c \\ &= \bar{V}_{ab} \bar{I}_1^* + \bar{V}_{bc} \bar{I}_2^* + \bar{V}_{ca} \bar{I}_3^* \\ &= V_\phi \angle 0^\circ I_\phi \angle \theta + V_\phi \angle -120^\circ I_\phi \angle (120^\circ + \theta) + V_\phi \angle 120^\circ I_\phi \angle (-120^\circ + \theta) \\ &= 3V_\phi I_\phi \angle \theta\end{aligned}$$

$$\Leftrightarrow \bar{S}_{3\phi} = \sqrt{3}V_{ll} I_l \angle \theta$$

$$\Rightarrow P_{3\phi} = \sqrt{3}V_{ll} I_l \cos(\theta)$$

$$\text{and } Q_{3\phi} = \sqrt{3}V_{ll} I_l \sin(\theta)$$

- Note that these are the same expressions as in a Y-connected load.

## Y- $\Delta$ Connection

- Example: three-phase 208 V source supplies a 900 VA load at 0.9 lagging P.F.

a) Find the load per phase.

$$|S_{3\phi}| = 3 \times 208 \times |I_{\phi}| = 900 \text{ VA}$$

$$\Rightarrow |I_{\phi}| = 1.44 \text{ A}$$

$$\text{but } \angle I_{\phi} = -\angle S_{3\phi}$$

$$\text{then } \bar{I}_{\phi} = 1.44 \angle -25.84^{\circ}$$

$$\bar{Z}_{\phi} = \frac{\bar{V}_{\phi}}{\bar{I}_{\phi}} = \frac{208 \angle 0}{1.44 \angle -25.84^{\circ}} = 138.9 \angle 25.84^{\circ} \Omega$$

## Y-Δ Connection

b) Find the line and phase current magnitudes.

$$|I_{\phi}| = 1.44 \text{ A}$$

$$|I_l| = \sqrt{3} |I_{\phi}| = 2.5 \text{ A}$$

c) Find the real and reactive power per phase.

$$\bar{S}_{3\phi} = 900 \angle 25.84^\circ \text{ VA}$$

$$\bar{S}_{1\phi} = 900 / 3 = 300 \angle 25.84^\circ \text{ VA}$$

$$\Rightarrow P_{1\phi} = 300 \cos(25.84^\circ) = 270 \text{ W.}$$

$$Q_{1\phi} = 300 \sin(25.84^\circ) = 130.76 \text{ VAR.}$$

Or,

$$P_{1\phi} = |V_{\phi}| |I_{\phi}| \cos(25.84^\circ) = 270 \text{ W.}$$

$$Q_{1\phi} = |V_{\phi}| |I_{\phi}| \sin(25.84^\circ) = 130.76 \text{ VAR.}$$



## Y- $\Delta$ Connection

d) Compute the total complex power.

$$\bar{S}_{3\phi} = 3 \times (270 + j130.76) = 810 + j392.28 = 900 \angle 25.84^\circ \text{ VA (check)}$$

- Other important examples are 2.12 and 2.13 in the textbook, in addition to problem 2.22.
- The answers to 2.22 are:

$$\bar{S}_{3\phi} = 95300 \angle 28^\circ \text{ VA}$$

$$\text{P.F.} = 0.88 \text{ lagging}$$

$$Q_{3\phi} = 45200 \text{ VAR}$$