



Controllable, User-Friendly 3-Phase Inverter

Group 81

Alex Chirita, Johnathan Vogt, Shyam Peden

Project Introduction




- Creating an inverter system that is capable of creating three AC waveforms with controllable phase angles
- Phase A will serve as the reference 0-degree phase, while the B and C phases will be controllable with respect to this reference phase
- Adjustments made using encoders for analog input, phases constantly adjust
- Switching control handled by the microcontroller board, which responds to analog input changes in real time

Project Objective




- Use this inverter to test fault conditions of small AC and brushless DC motors, as well as other equipment
- Ideal 3-phase systems have consistent phase angles of 120 between the three phases
- Sometimes a 3-phase system might be slightly out of phase by a few degrees, making the system unbalanced and potentially dangerous to operate
- This project allows testing of unbalanced AC systems, which is useful for many research and product development purposes

Block Diagram

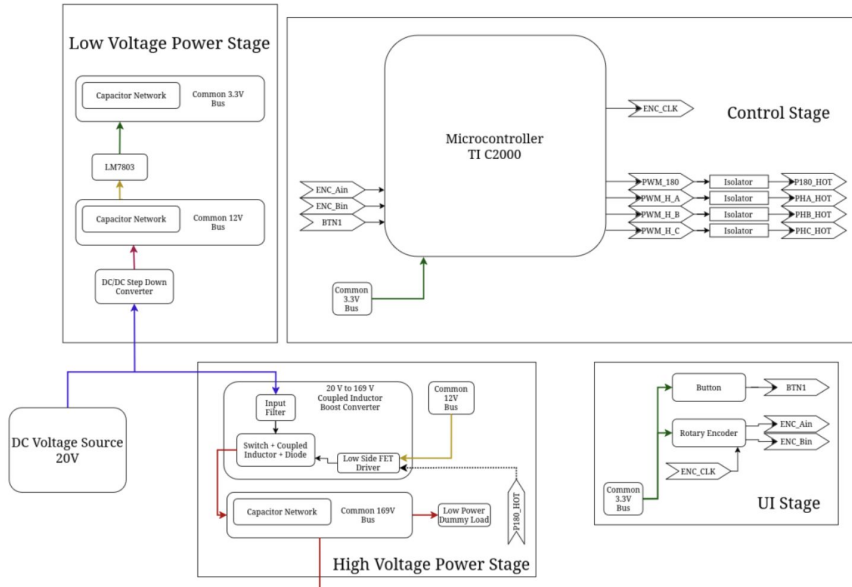

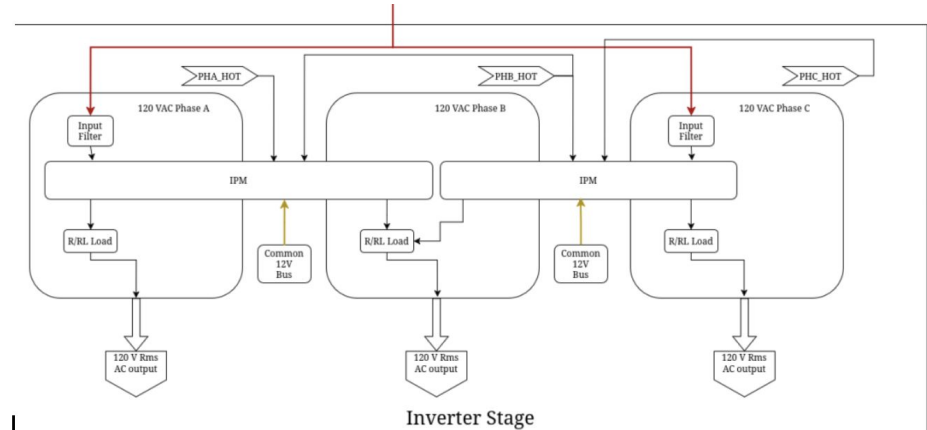Boost, User Interface, and Microcontroller




Bridge Subsystem

Boost Subsystem




- Trying to boost the input voltage as much as possible
- We will be using a constant DC supply instead of a solar panel (reduced cost and complexity)
- To achieve this, we decided to implement an asynchronous coupled inductor boost converter, pictured below

Populated PCB Side 2

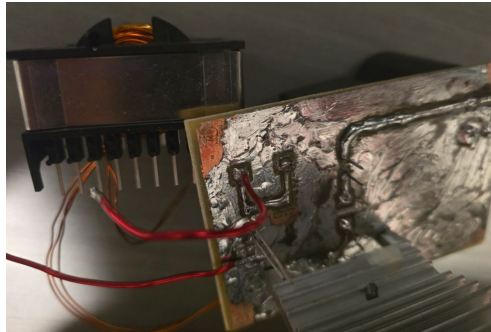

Topology Schematic

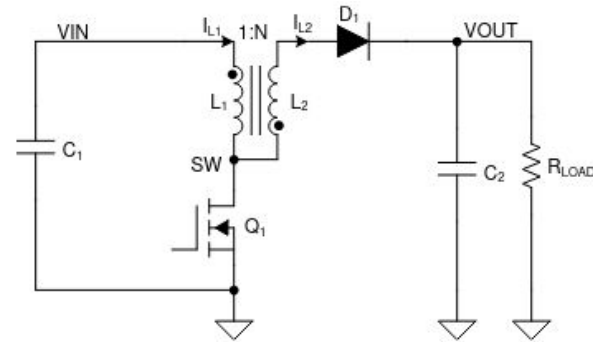


Boost Subsystem




- Results

- We were able to create a converter that boosts the voltage by a scale of about 9.425 (20V to 188.49V) [8.7 at high load 20 to 174V]
- 2 Degrees of freedom: Turns Ratio [20:60] and Duty Ratio [67%].
- Must have load at all times
- Added Bonus
 - Minimal heat generated
 - 85% efficiency across the board
 - Capable of delivering high power
 - 100W Max before dropping below 100V
 - Extremely low voltage ripple

Efficiency vs. Output Voltage

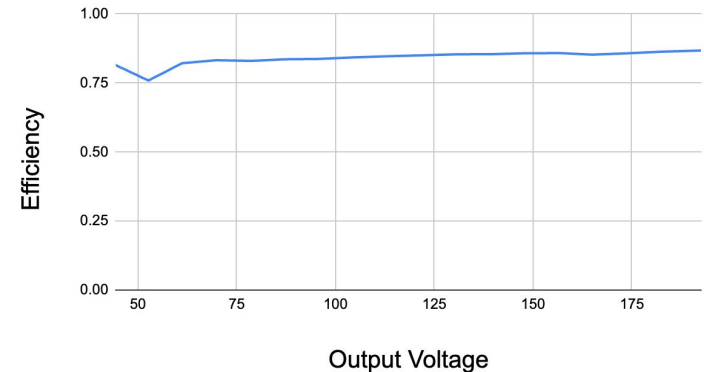

Boost Converter Results

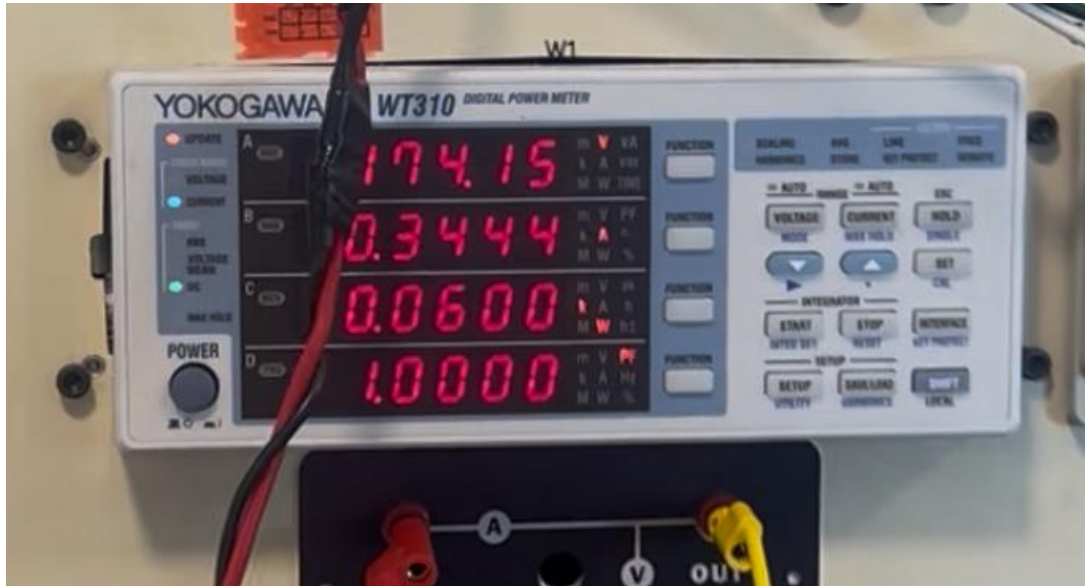


Power Meter Output

- 20V input
- 174V output
- 0.344A output
- 500 Ohm load
- 60W at the output

Bridge Subsystem



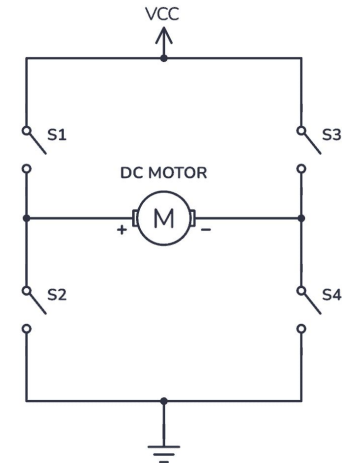- Switching of boosted DC voltage into variable AC waveform
- Receives what the voltage should be and uses a system of h-bridges to achieve the proper voltage
- 3 full H-bridges for three phases (A, B, and C)
- Phase A will not change as we want it to stay 0 degree phase
 - Only phases B and C will change





H-Bridge Diagram

Bridge Subsystem




IPMs

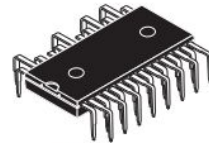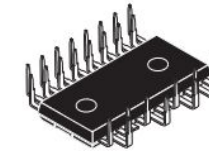- High voltage rating while being able to be wired as 3 H-bridges
- Integrated



NDIP-26L

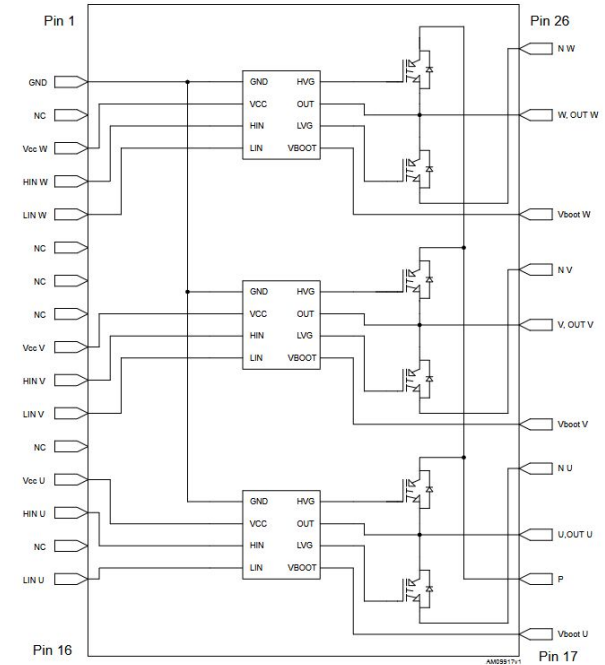


PCB Production


- Flipped image of Kicad schematic is printed on glossy paper using a laser printer
- The toner is transferred to the copper using iron
- The toner protects copper from being dissolved




Raw PCB after toner transfer

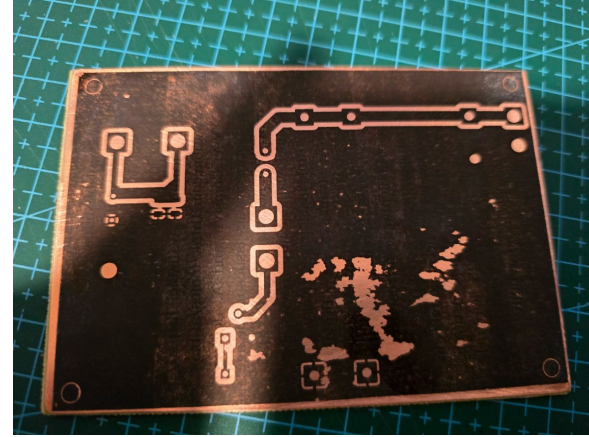

Raw PCB after solution

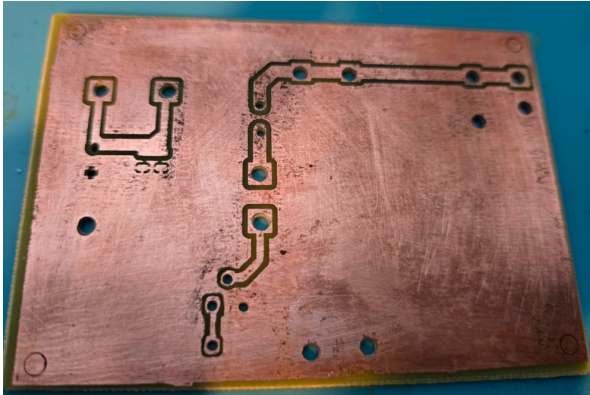


Populated PCB Side 1

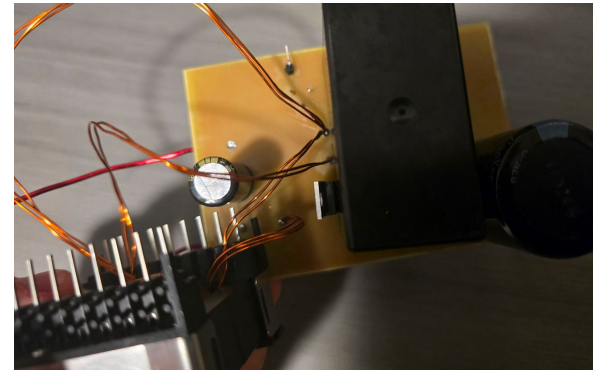


PCB Production

- 3% Hydrogen peroxide, citric acid and table salt solution is used to dissolve unwated copper
- After sultion the toner is sanded off with 300 sandpaper
- The copper is heated up with liquid flux and tinned with 63/37 tin/lead wire
- Components are soldered in at the end


Populated PCB Side 1

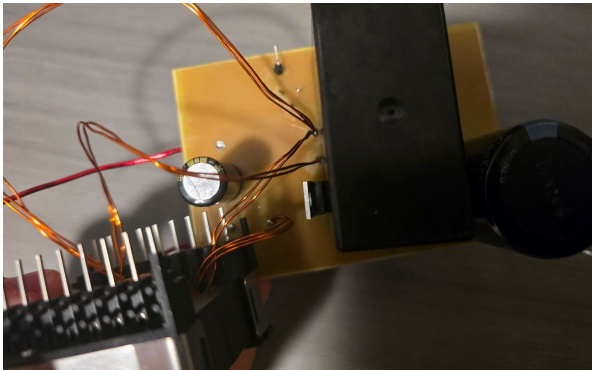

Inverter Board Kicad Layout

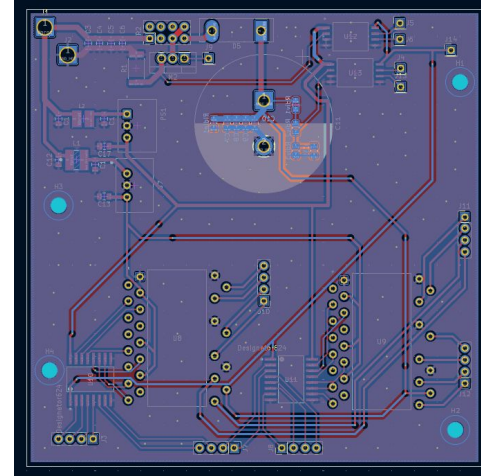


Populated PCB Side 2

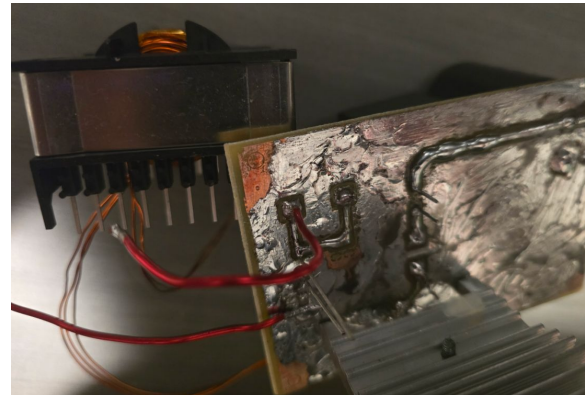


User Interface Subsystem



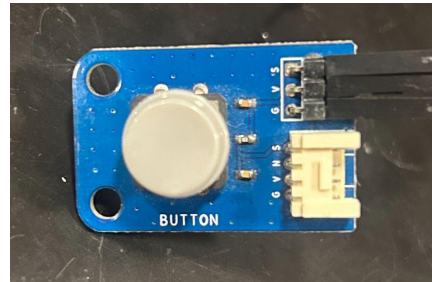- 2 encoders and a button.
- Each encoder will correspond to Phase B and C to adjust the desired phase.
- The button confirms that we want to update the display with the new values from the encoder
- Future development would involve the integration of further user control



Button Encoder

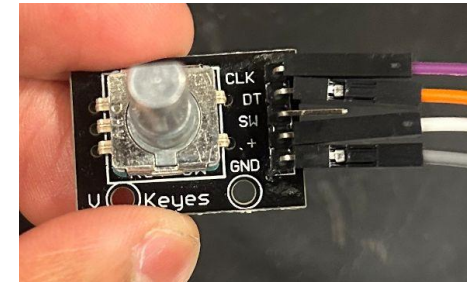


Rotary Encoder


Input Control Subsystem



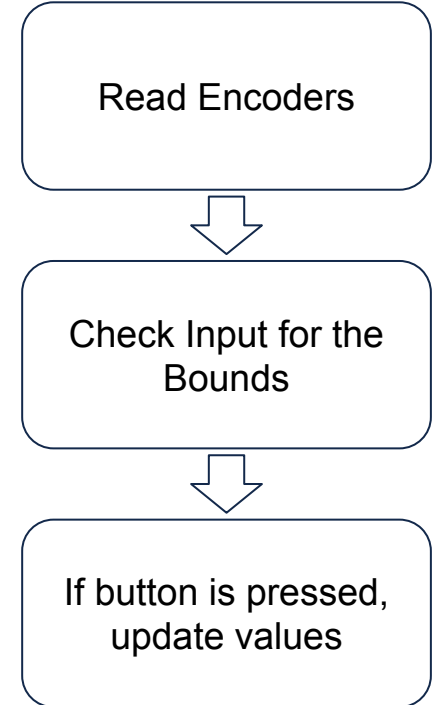- Checks whether the input values from the encoders are valid
- If this is the case and the button is being pressed down, it updates the values that will get sent into the switching control subsystem
- Programmed into the microcontroller
- Used quadrature decoding logic to read encoders
 - Uses 2 square waves produced by encoder



TIC2000 Microcontroller

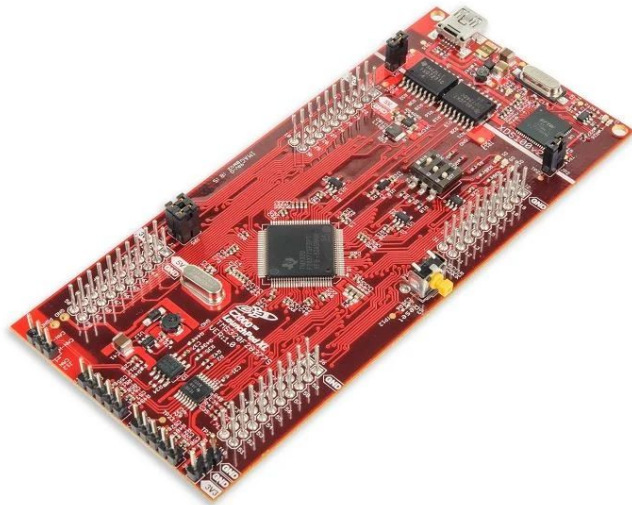

Why?

- The number of input and output channels and familiarity with the TI microcontrollers were appealing
- Integrated firmware development environment as this project is very control-focused
- Integration of microcontroller

Switching Control Subsystem



- Also coded in the microcontroller
- Follows timers to control the inverter and DC-DC switching
- Initial phase angles
 - Phase B: 120 degrees
 - Phase C: 240 degrees = -120 degrees
- As the 2 phases change, the timing gets shifted with respect to phase A by the desired phase




Default 3-Phase Output

Switching Control Subsystem



- Each phase produces 4 square waves
 - High signal, Low signal, and their complements
- DC-DC switching control is open-loop, will boost any voltage by some given ratio
 - In the future, the microcontroller will read AC output and respond accordingly to produce the needed DC voltage
 - Allows for more stable output that could be tied to a larger power grid as a regular inverter

Efficiency vs. Resistive Load

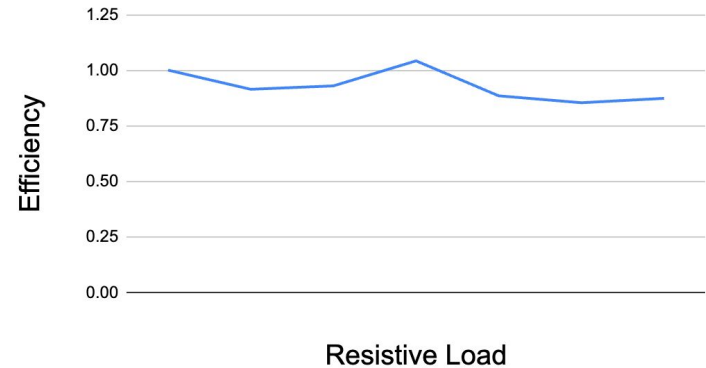

Successes and Challenges



- Successes
 - 3 phases that increase and decrease in amplitude according to the input voltage
 - Boost converter with minimal heat generated
- Challenges
 - ICs fried
 - Navigating TI CCS software
 - Parts placed on backorder
 - Use of lab equipment




Final 3-phase Waveforms

Conclusion



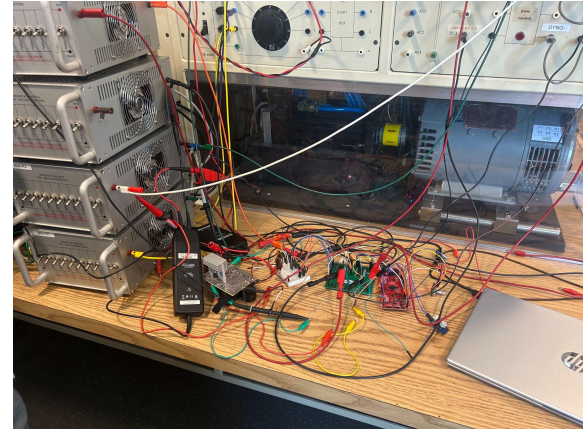- Generally met our goals at the start of the semester
- Very good experience working with high voltage and microcontrollers
- Potential Redesigns
 - Use of large inductors for smoother sine wave
 - Placing everything onto a single PCB
 - Design around a more enclosed structure
- Future Work
 - Integration of closed-loop boost conversion
 - Allow the user to input a range of DC input voltages



Final Demo Setup



I ILLINOIS