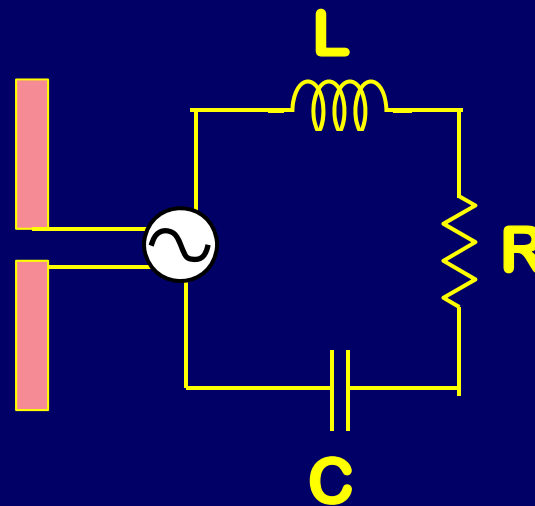


Exam 2 Monday March 11!


- **Lecture material**
 - Magnetism (Lect. 8) – AC circuits (Lect. 12, up to & including inductance)
- **Discussion/HW material**
 - Discussion 4 – 6 & HW 4 – 6
- **Review session Sunday, March 10, 3pm, 141 Loomis**
 - Will review HE2 from Fall '12 (Note: will skip questions pertaining to Lect. 13 – 15 in exam)
- **Daylight Savings starts March 10!!!**

Physics 102: Lecture 13

RLC circuits & Resonance



Review: AC Circuit

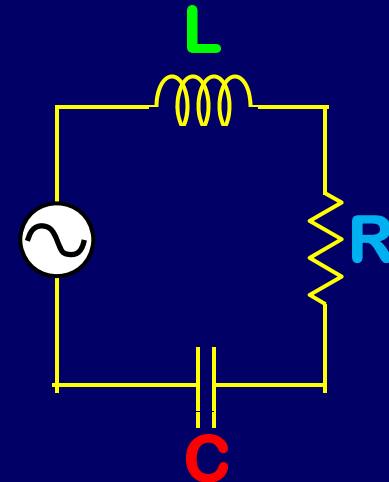

- $I = I_{\max} \sin(2\pi ft) = I_L = I_R = I_C$

- $V_R = I_{\max} R \sin(2\pi ft)$

V_R in phase with I

- $V_C = I_{\max} X_C \sin(2\pi ft - \pi/2)$ *1/4 cycle lag*


V_C lags I “ICE”

$$V_{C,\max} = I_{\max} X_C \quad X_C = 1/\omega C$$

- $V_L = I_{\max} X_L \sin(2\pi ft + \pi/2)$

V_L leads I “ELI” *1/4 cycle lead*
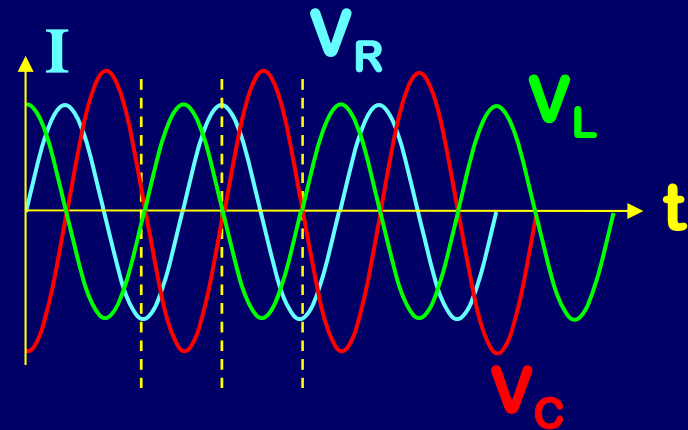
$$V_{L,\max} = I_{\max} X_L \quad X_L = \omega L$$




Goal:

write down equations for all of the voltages

$$V_R = I_{\max} R \sin(2\pi ft) \quad \text{~}$$

$$V_L = I_{\max} X_L \sin(2\pi ft + \pi/2) \quad \text{~}$$
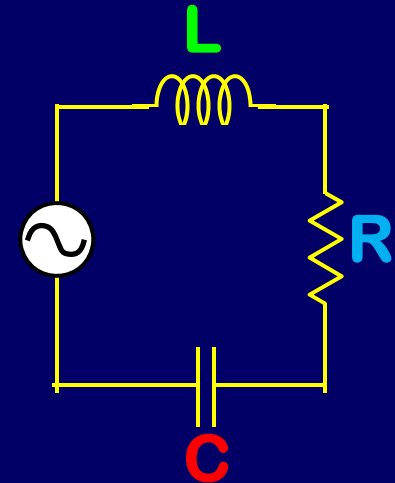
$$V_C = I_{\max} X_C \sin(2\pi ft - \pi/2) \quad \text{~}$$



The only element left: generator!




$$V_{gen} = V_{gen,max} \sin(2\pi ft + \phi)$$

ϕ : "phase angle"

Like a shift in time!

$\phi < 0$: shift forward lag


$\phi > 0$: shift backward lead

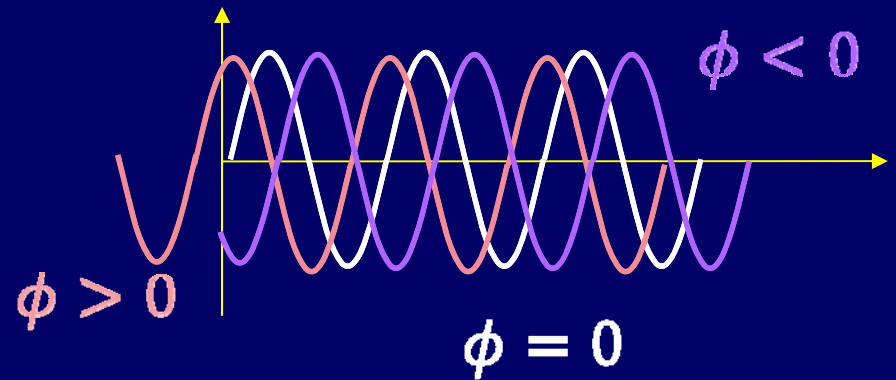

Kirchhoff: generator voltage




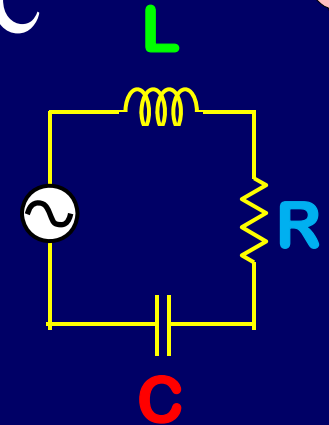- Instantaneous voltage across generator (V_{gen}) must equal sum of voltage across all of the elements at all times:



$$V_{\text{gen}}(t) = V_R(t) + V_C(t) + V_L(t)$$
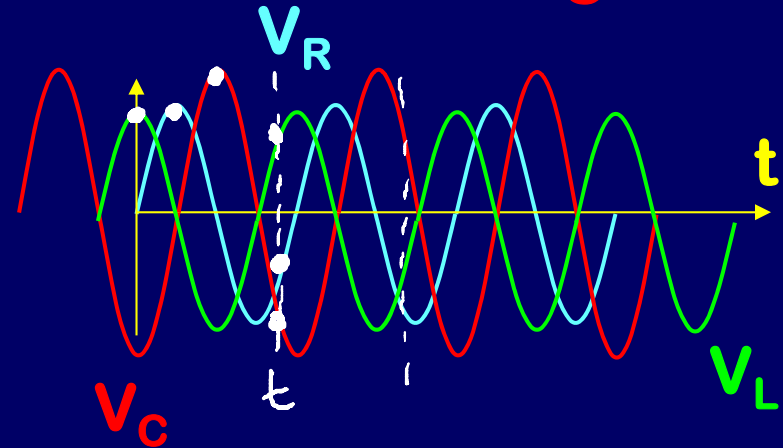
$$V_{\text{gen,max}} \neq V_{L,\text{max}} + V_{R,\text{max}} + V_{C,\text{max}}$$



What is $V_{\text{gen,max}}$?

Define impedance Z : $V_{\text{gen,max}} \equiv \textcircled{I_{\text{max}}} Z$

Like: $V=IR$


$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

One last ingredient: is the generator voltage leading or lagging the current?

$$I = I_{max} \sin(2\pi ft)$$

$$V_{gen} = I_{max} Z \sin(2\pi ft + \phi)$$

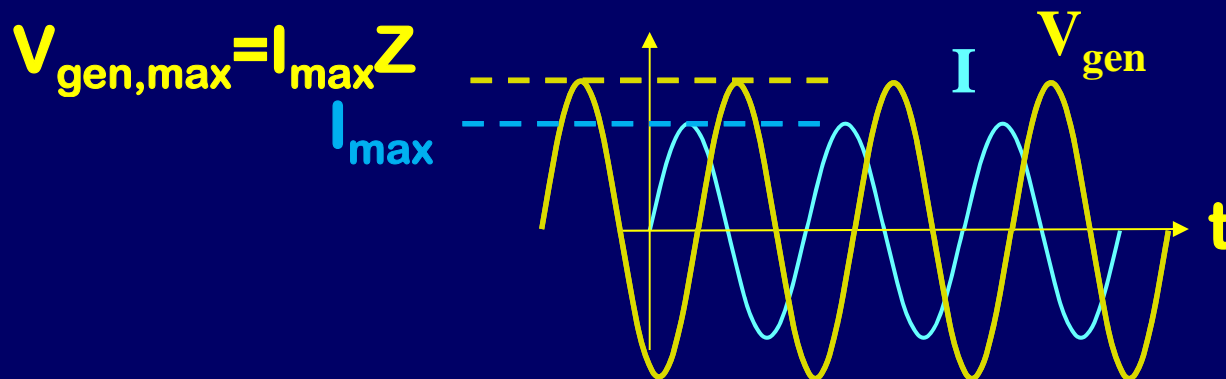Phase angle: $\tan(\phi) = \frac{(X_L - X_C)}{R}$



This example:
 $\phi < 0$, voltage
is lagging

Example




Problem Time!

An AC circuit with $R = 2 \Omega$, $C = 15 \text{ mF}$, and $L = 30 \text{ mH}$ is driven by a generator with voltage $V(t) = 2.5 \sin(8\pi t)$ Volts. Calculate the maximum current in the circuit, and the phase angle.

$V_{\text{gen,max}}$

$2\pi f$

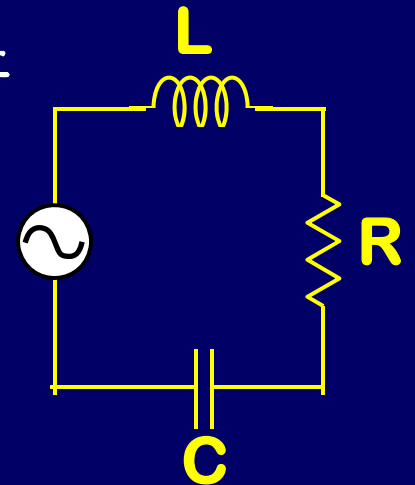

$$I_{\text{max}} = V_{\text{gen,max}} / Z$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$Z = \sqrt{2^2 + \left(8\pi \times .030 - \frac{1}{8\pi \times .015}\right)^2} = 2.76 \Omega$$


$$I_{\text{max}} = 2.5 / 2.76 = 0.91 \text{ Amps}$$

$$\tan(\phi) = \frac{X_L - X_C}{R} = \frac{(8\pi \times .030 - \frac{1}{8\pi \times .015})}{2} \Rightarrow \phi = -43.5^\circ$$

Power in RLC circuits

- The voltage generator supplies power.
 - Only resistor dissipates power.
 - Capacitor and Inductor store and release energy.
- $P(t) = I(t)V_R(t)$ oscillates so sometimes power loss is large, sometimes small.
- Average power dissipated by resistor:
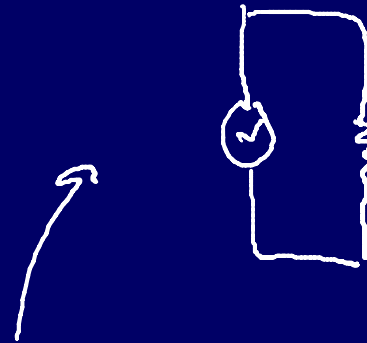
$$\begin{aligned}\bar{P} &= \frac{1}{2} I_{\max} V_{R,\max} \\ &= \frac{1}{2} I_{\max} V_{\text{gen},\max} \cos(\phi) \\ &= I_{\text{rms}} V_{\text{gen,rms}} \cos(\phi)\end{aligned}$$




If there is only a resistor, $\phi = 0$




ACT: Power dissipation

Which one of these circuits dissipates the most power?
on average


$$V_{\text{gen,max}} = 10 \text{ V}$$

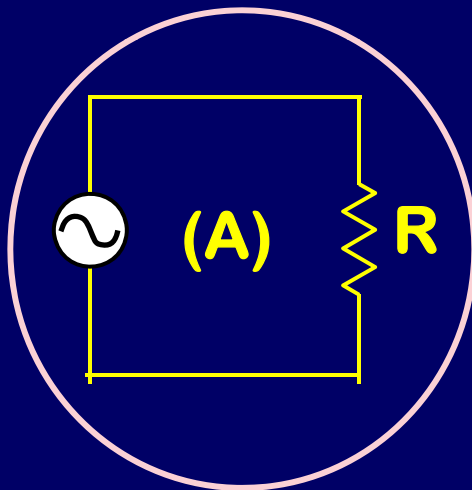

$$V_{\text{gen,max}} = 100 \text{ V}$$

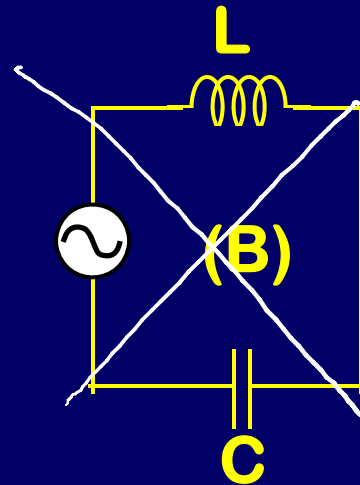


$$\varepsilon = 1 \text{ V}$$

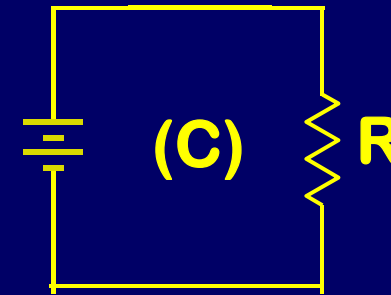

$$\begin{aligned} \overline{P}_A &= \frac{1}{2} I_{\text{max}} V_{R,\text{max}} \\ &= \frac{1}{2} I_{\text{max}} V_{\text{gen,max}} \\ &= \frac{1}{2} \frac{V_{\text{gen,max}}^2}{Z} = \frac{1}{2} \frac{10^2}{R} \end{aligned}$$

$$\begin{aligned} P_C &= I V_R = I \varepsilon \\ &= \frac{\varepsilon^2}{R} = \frac{1^2}{R} \end{aligned}$$

Kirchhoff: generator voltage

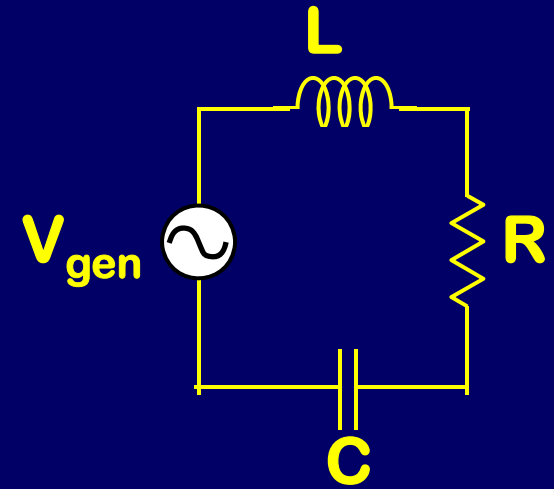


Write down Kirchhoff's Loop Equation:

$$V_{\text{gen}}(t) = \cancel{V_L(t)} + V_R(t) + \cancel{V_C(t)} \text{ at every instant of time}$$


If the frequency is just right...

$$V_{\text{gen}}(t) = V_R(t)$$

Resonance!

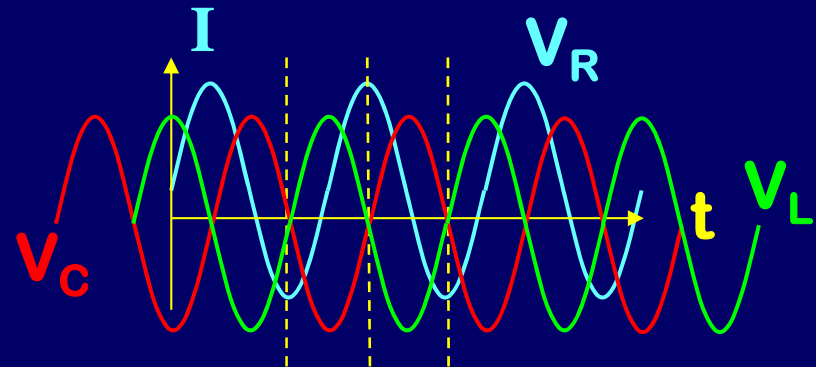


Examples of mechanical resonance

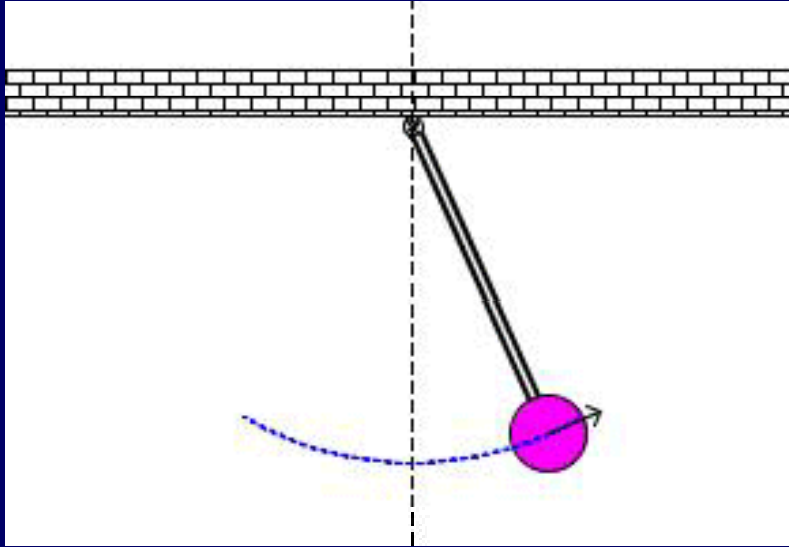

Pendulum:

$$\omega_0 = \sqrt{g/l}$$

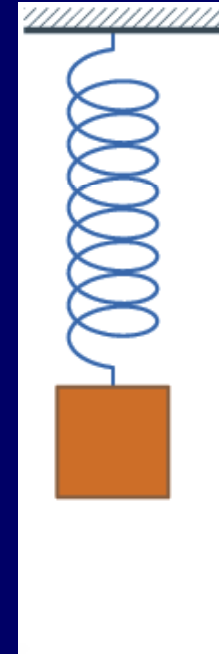

Mass on a spring:

$$\omega_0 = \sqrt{k/m}$$

Common features:

- **Energy converts between two forms (kinetic & potential)**
- **Weak input at ω_0 leads to a big response!**

Resonance!




Tacoma Narrows Bridge





Millennium Bridge

Electric energy

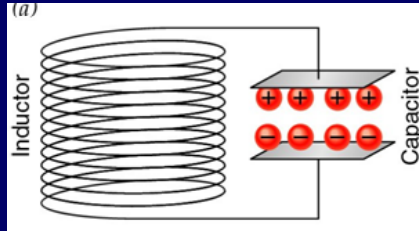


$$V_C = V_{C,max}$$

$$V_L = -V_{L,max}$$

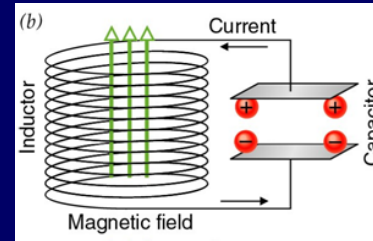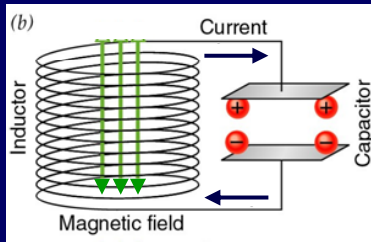


Magnetic energy

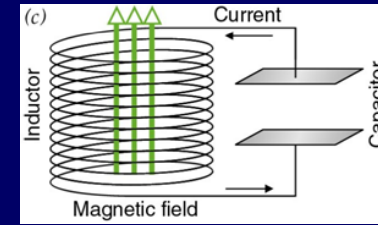



$$V_C = 0$$

$$V_L = 0$$

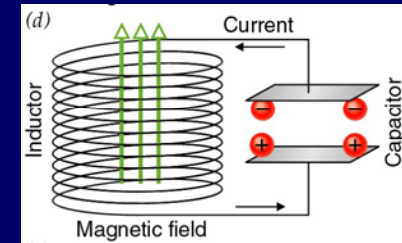


RLC circuit:
Electrical
resonance

$$f_0$$

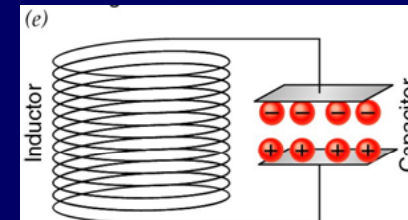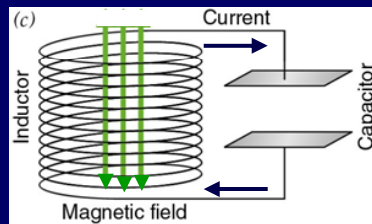


Magnetic energy

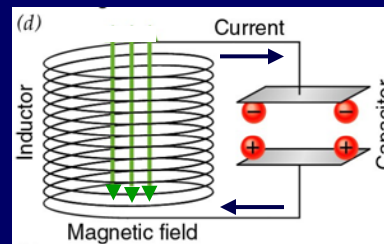

Electric energy

$$V_C = -V_{C,max}$$

$$V_L = +V_{L,max}$$

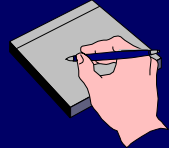

Resonance

R is independent of **f**

X_L increases with **f**


$$X_L = 2\pi fL$$

X_C decreases with **f**

$$X_C = 1/(2\pi fC)$$

Z: **X_L** and **X_C** subtract

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

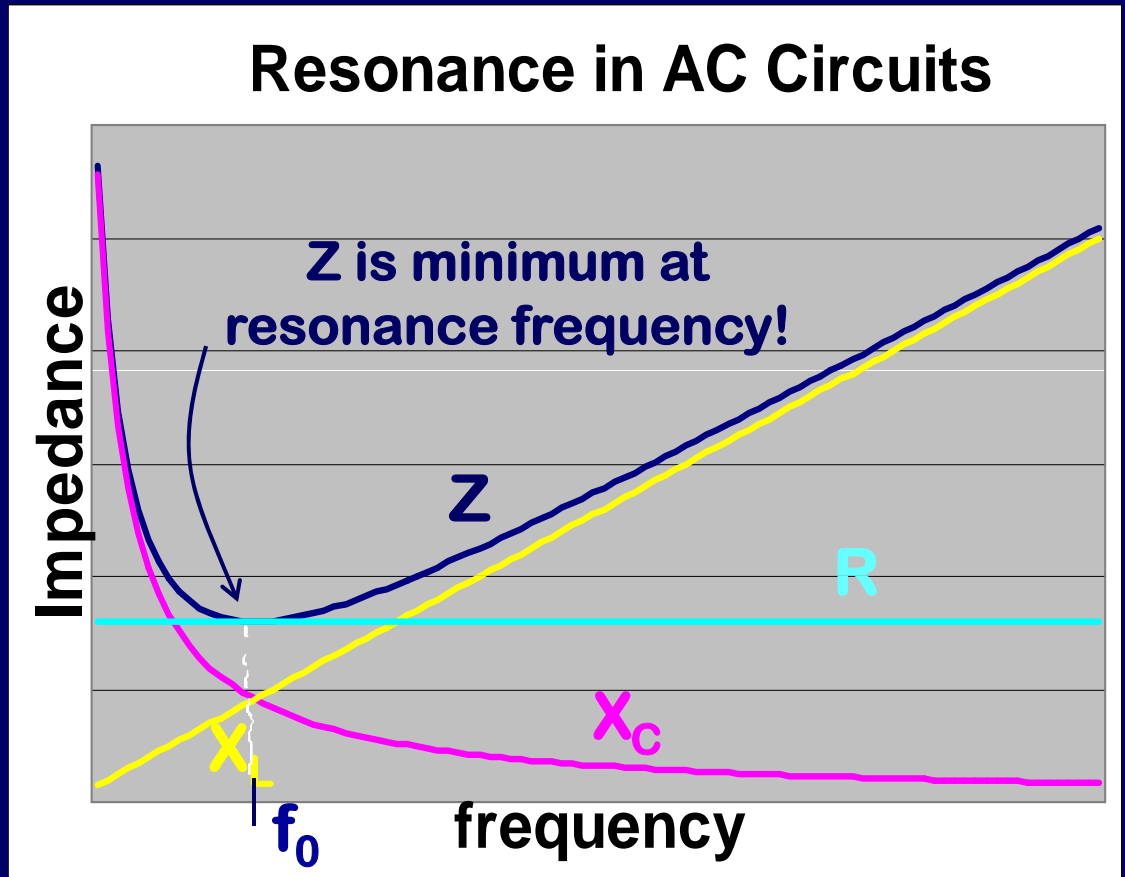


$$V_{L,max} = V_{C,max}$$

Resonance: X_L = X_C

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

$$\begin{aligned}
 & \leftarrow X_L = 2\pi f_0 L \\
 & \leftarrow X_C = \frac{1}{2\pi f_0 C}
 \end{aligned}$$

Resonance

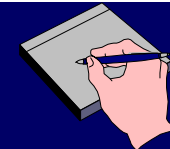

R is independent of **f**

X_L increases with **f**

$$X_L = 2\pi fL$$

X_C decreases with **f**

$$X_C = 1/(2\pi fC)$$


Z: **X_L** and **X_C** subtract

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

Resonance: X_L = X_C


$$f_0 = \frac{1}{2\pi\sqrt{LC}} \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

Resonance in AC Circuits

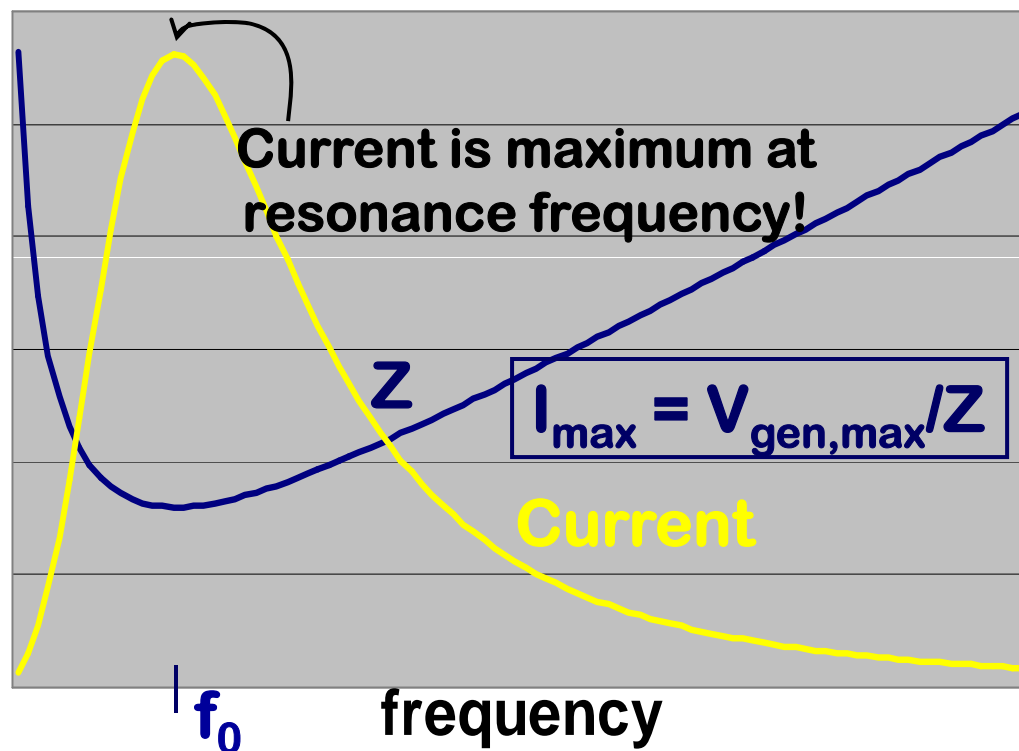

CheckPoint 14.1

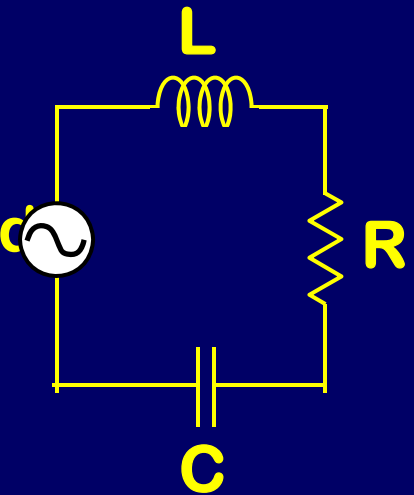As the frequency of the circuit is either raised above or lowered below the resonant frequency, the impedance of the circuit:




48% Always increases

27% Only increases for lowering the frequency



25% Only increases for raising the frequency

Z is minimum at f_0 !

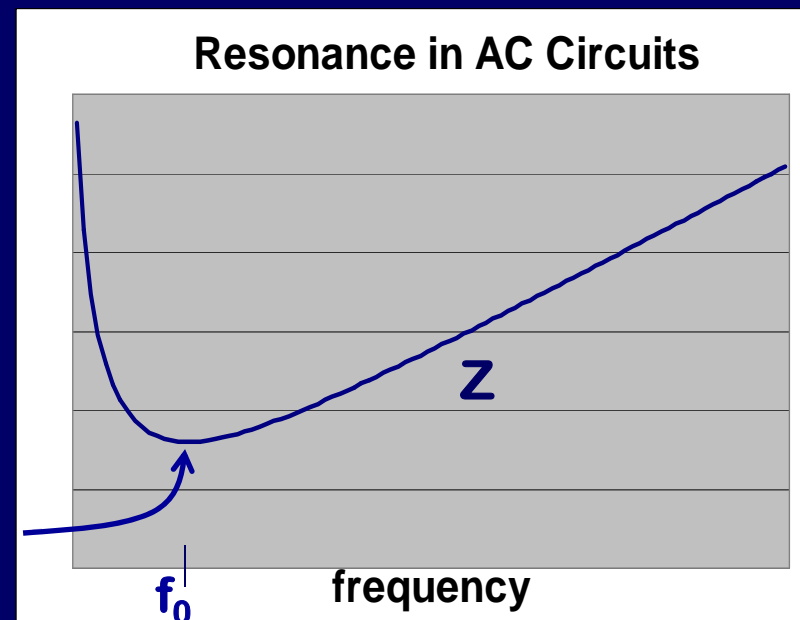

Any other frequency will have higher Z!

What is it good for?

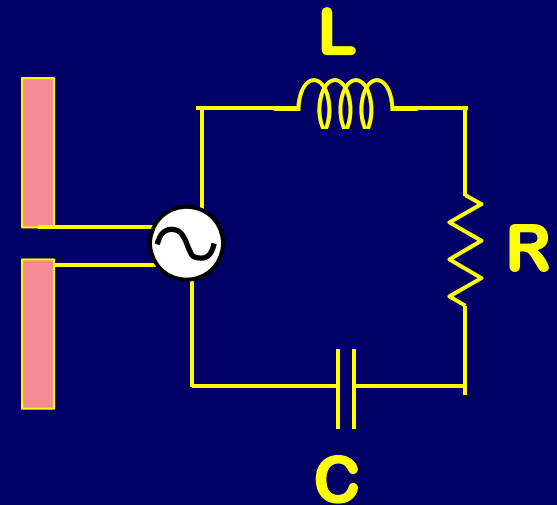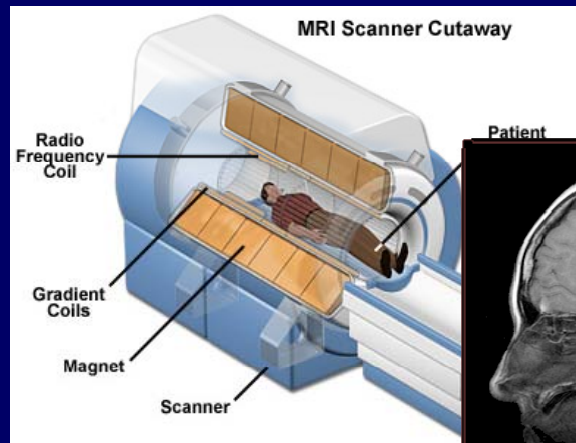

- Current through circuit depends on frequency (maximum at resonance frequency f_0)
 - Radio receiver
 - NMR/MRI
 - Picks out radio station freq f_0
 - Picks out signal from protons at f_0

Magnetic Resonance Imaging



Nobel Prize Medicine, 2003



Lauterbur, UIUC



Mansfield

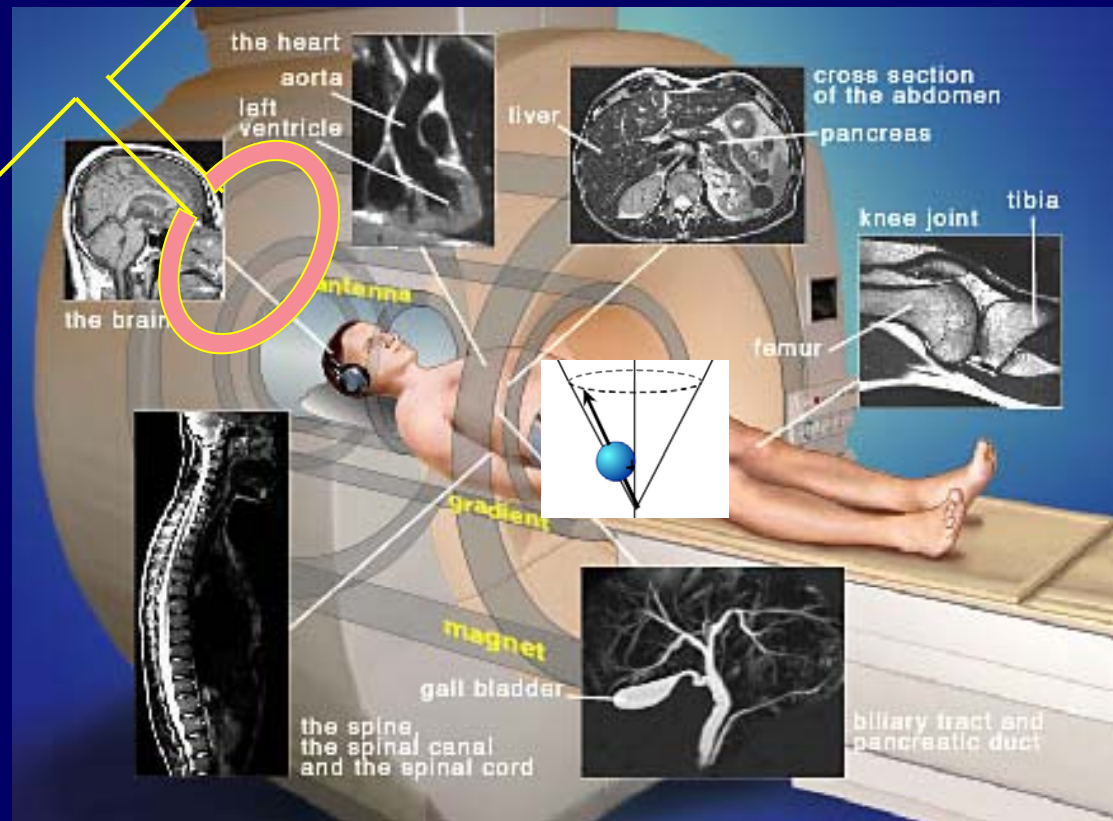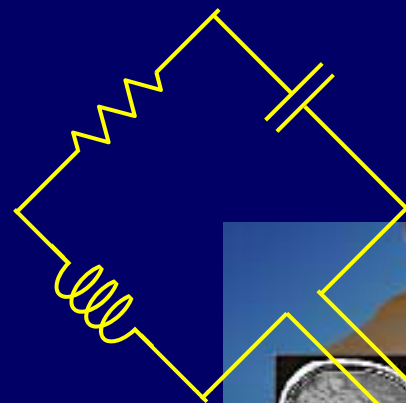


Faraday's Law + RLC circuit!

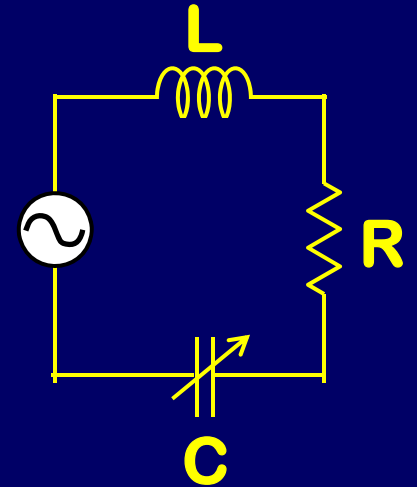Example

Resonance in Radios



An AC circuit with $R = 2 \Omega$, $L = 0.30 \mu\text{H}$ and variable capacitance is connected to an antenna to receive radio signals at the resonance frequency. If you want to listen to music broadcasted at 96.1 MHz, what value of C should be used?



$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

$$C = \frac{1}{(2\pi f_0)^2 L} = \frac{1}{(2\pi \times 96.1 \times 10^6)^2 \times 0.30 \times 10^{-6}} = 9.1 \times 10^{-12} \text{ F}$$



ACT: Radios



Your radio is tuned to FM 96.1 MHz and want to change it to FM 105.9 MHz, which of the following will work.

1. Increase Capacitance
2. Decrease Capacitance
3. Neither, you need to change R

$$\uparrow f_0 = \frac{1}{2\pi\sqrt{LC}} \downarrow$$

Higher frequency needs smaller capacitor so it can develop voltage quicker.

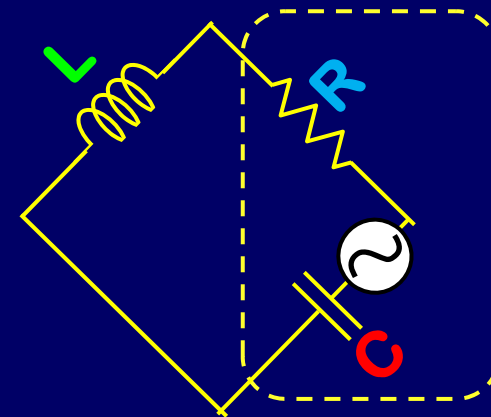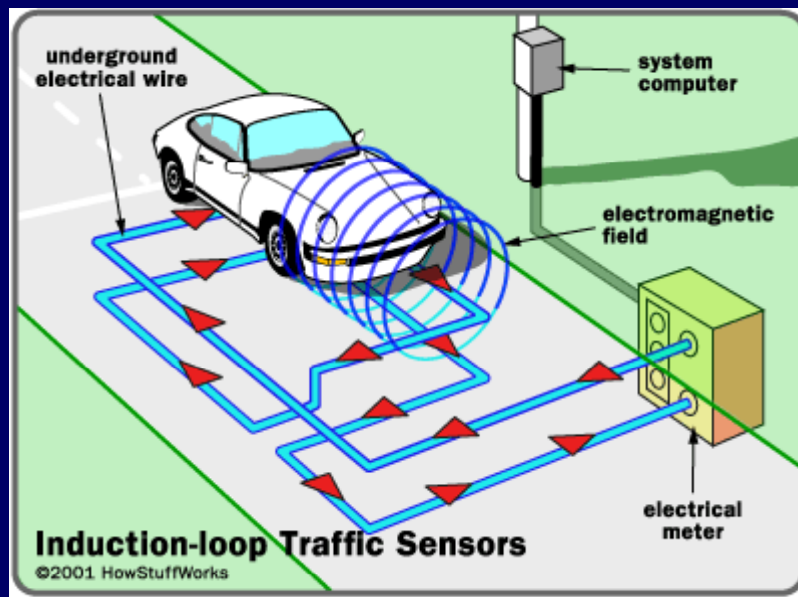Another use for RLC circuits: traffic sensors



AC Summary

Resistors: $V_{R,\max} = I_{\max} R$

In phase with I

Capacitors: $V_{C,\max} = I_{\max} X_C$ $X_C = 1/(2\pi f C)$

Lags I

Inductors: $V_{L,\max} = I_{\max} X_L$ $X_L = 2\pi f L$

Leads I

Generator: $V_{\text{gen},\max} = I_{\max} Z$ $Z = \sqrt{R^2 + (X_L - X_C)^2}$

Can lead or lag I

$$\tan(\phi) = (X_L - X_C)/R$$

Power is only dissipated in resistor:

$$\bar{P} = \frac{1}{2} I_{\max} V_{\text{gen},\max} \cos(\phi)$$