
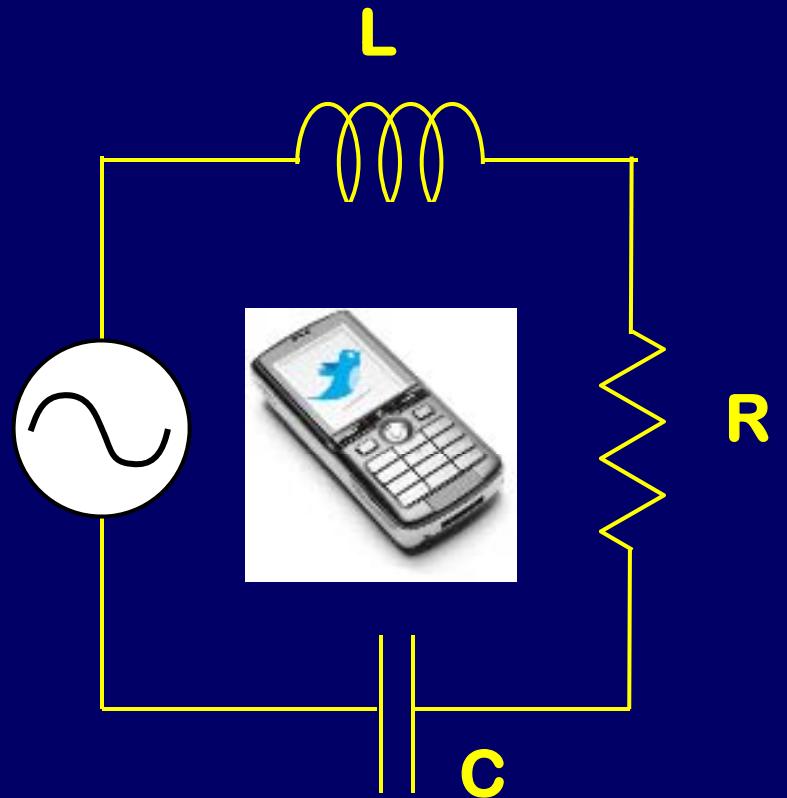


# Physics 102: Lecture 12



## AC & RLC Circuits

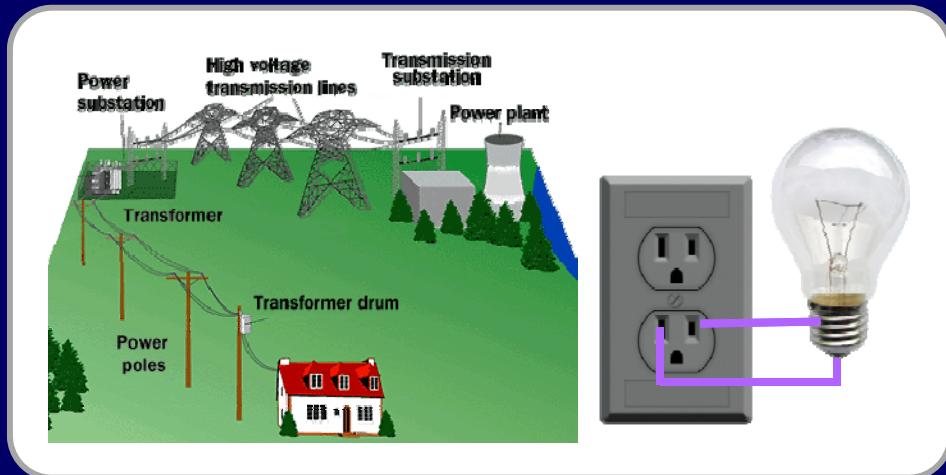

# DC vs. AC circuits

**DC**



Direct Current

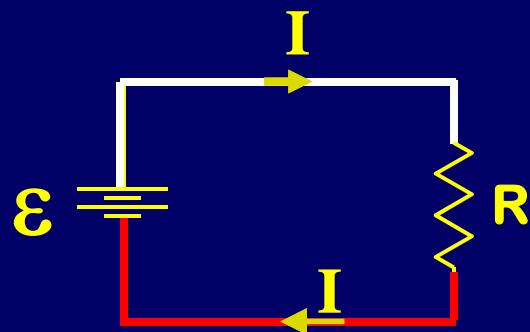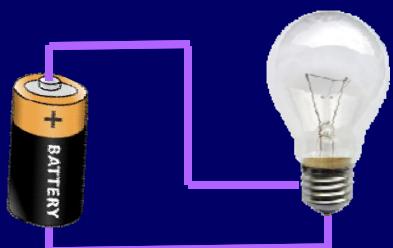


**Direction  
of current is fixed**

**AC**


Alternating Current

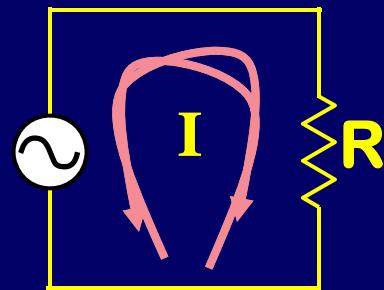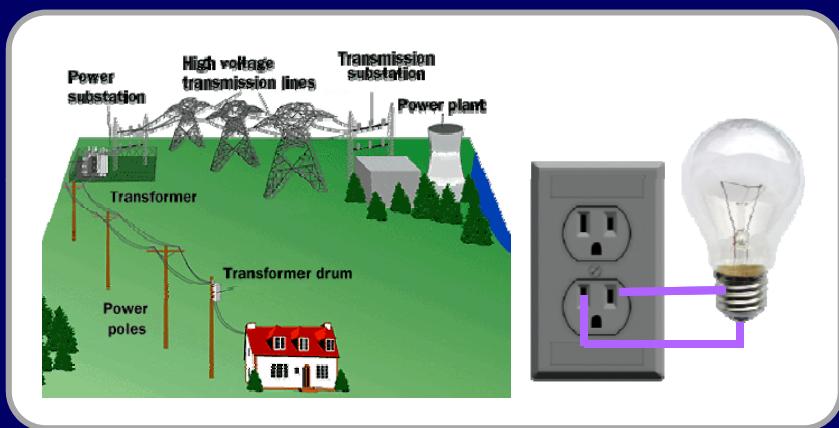

**Direction of current  
alternates!**

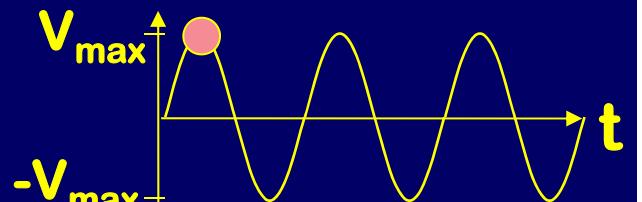

# Review: Generators and EMF

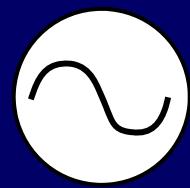



**Voltage across generator:**

$$\varepsilon = \omega A B \sin(\theta)$$

$$\varepsilon = \omega A B \sin(\omega t)$$

$$\varepsilon = V_{\max} \sin(\omega t)$$

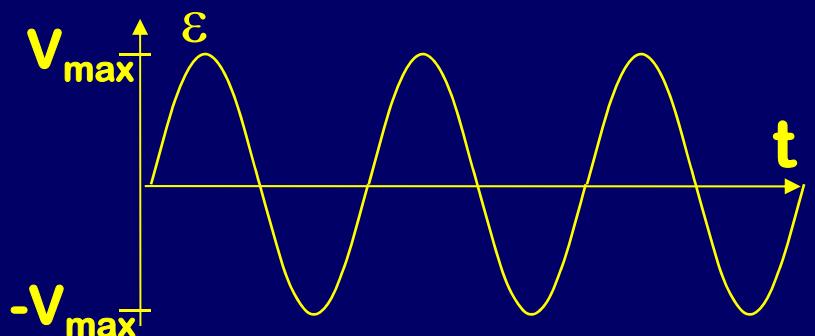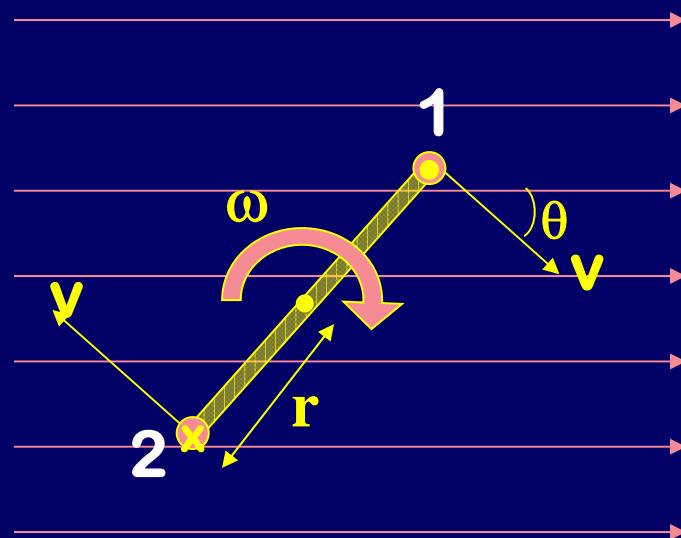**$V_{\max}$  = Amplitude**  
**= Maximum voltage**



# Example

## AC Source



$$V(t) = V_{\max} \sin(\omega t) = V_{\max} \sin(2\pi f t)$$

$V_{\max}$  = maximum voltage


$f$  = frequency (cycles/second)

$$V(t) = 24 \sin(8\pi t)$$

$$2\pi f t = 8\pi t$$


$$f = 4 \text{ Hz}$$

$$T = (1/4) \text{ seconds}$$

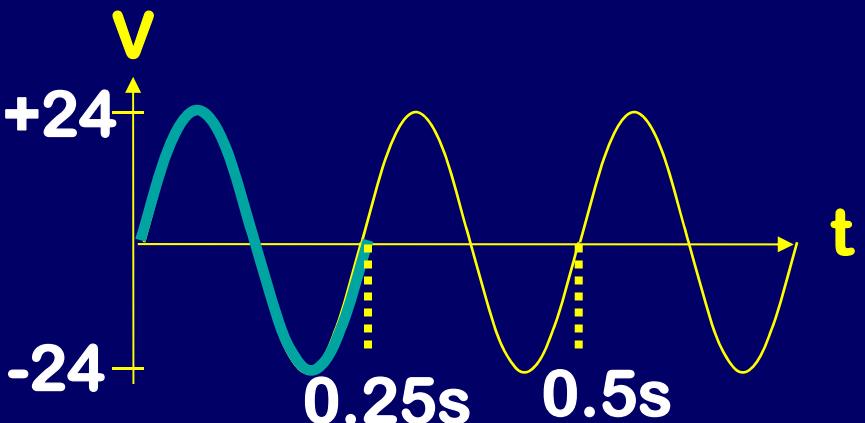


RMS: Root Mean Square  $V_{\text{rms}} = V_{\max} / \sqrt{2}$

# RMS?

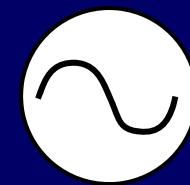


$$V(t) = V_{\max} \sin(2\pi f t)$$

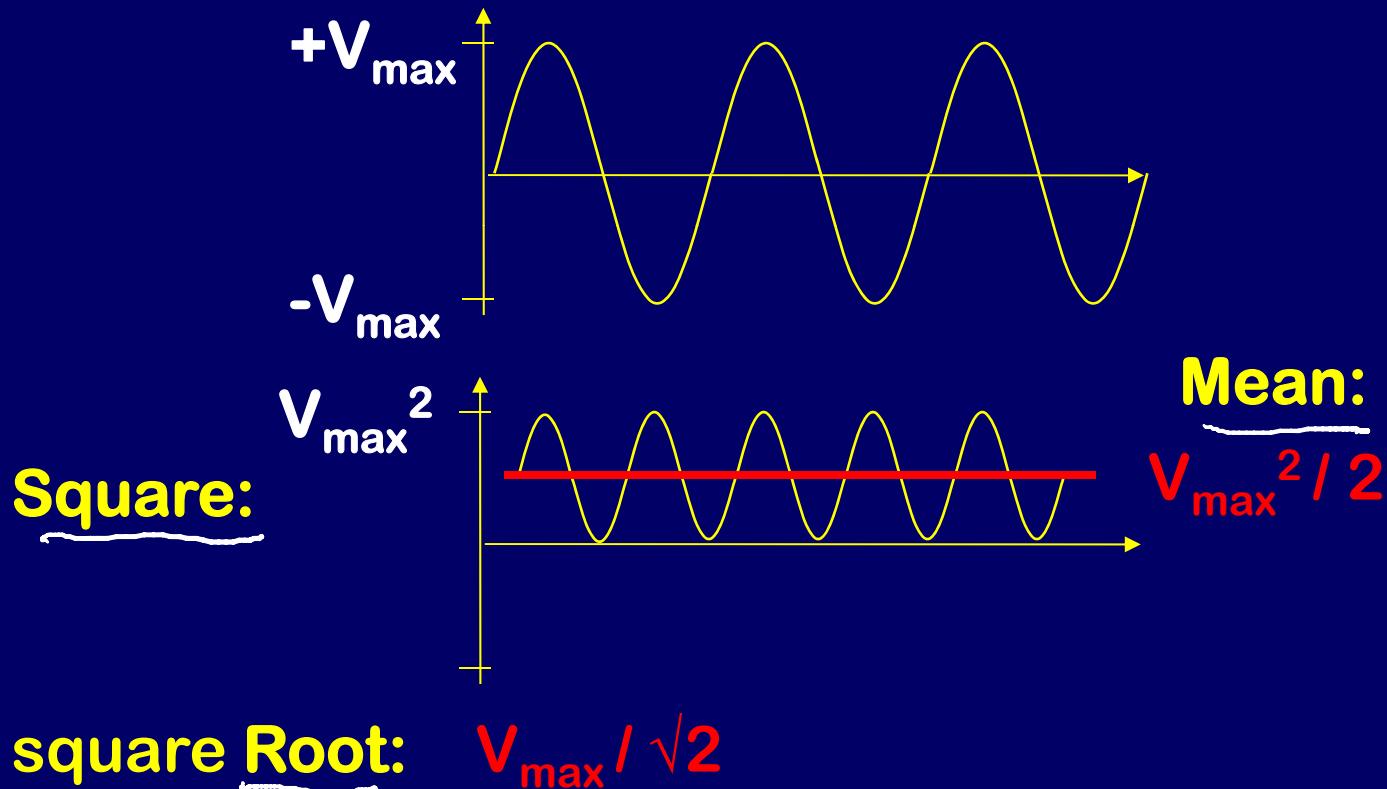

RMS: Root Mean Square  $V_{\text{rms}} = V_{\max} / \sqrt{2}$
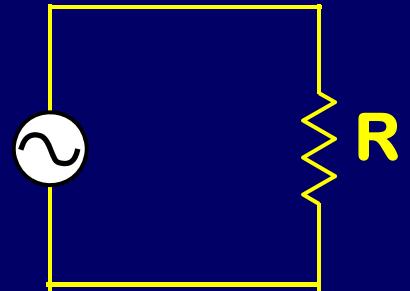
# CheckPoint 2.1, 2.2

$$I(t) = \frac{V_{max}}{R} \sin(377t) = 10 \sin(377t)$$



Find  $I_{max}$

Well... We know that the maximum value of sin is 1. So the maximum current is 10!

$$I_{max} = 10 \text{ A}$$

Find  $I_{rms}$

Just like  $V_{rms} = V_{max}/\sqrt{2} \dots$



$$I_{rms} = I_{max}/\sqrt{2} = 10/\sqrt{2} \text{ A} = 7.07 \text{ A}$$

Average power dissipated:  $\bar{P} = I_{rms}V_{rms} = \frac{1}{2}I_{max}V_{max}$

(For an AC circuit with only a resistor)



## ACT: AC power dissipation

When your hair dryer is plugged in and running, it uses 1200 W of average power. If the max voltage delivered by the wall outlet is 120V, what is the max current delivered to the hair dryer?




(A) 0.05 A      (B) 10 A      (C) 20 A

$$P_{avg} = \frac{1}{2} I_{max} V_{max}$$

$$I_{max} = \frac{2P_{avg}}{V_{max}} = \frac{2400}{120} = 20 \text{ A}$$


# Inductors

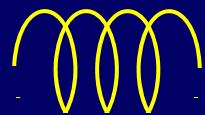


Inductors: a solenoid  
used as a circuit element



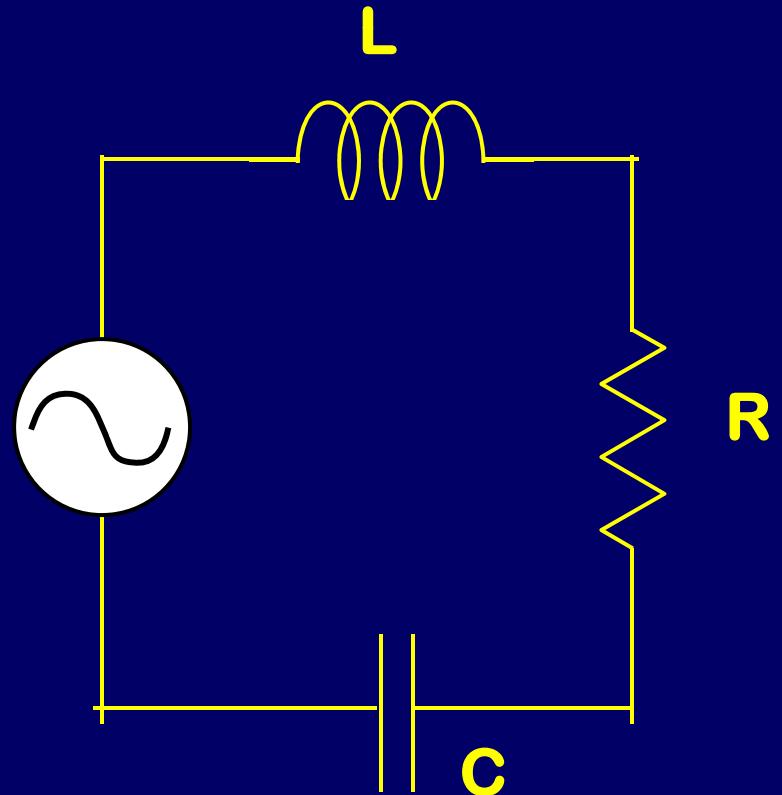Inductors enable circuits to  
have a resonance...




# Self-Inductance

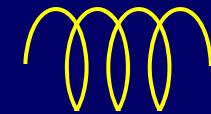

Recall the solenoid cannon

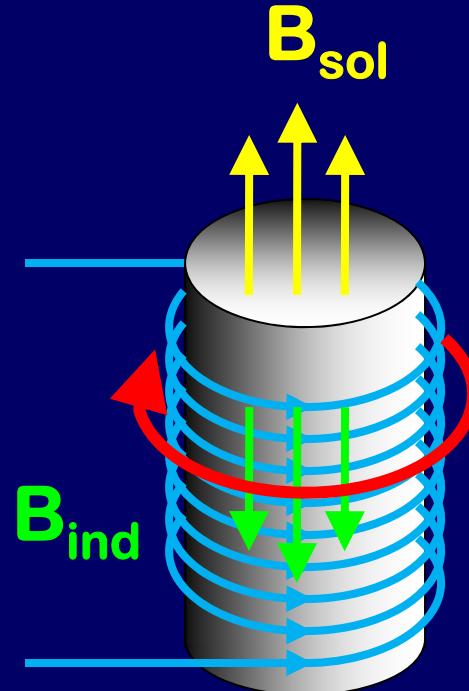
- Changing current ↑
- Changing  $B_{\text{sol}}$  field ↑
- Changing  $\Phi$  through itself! ↑  $\Phi \propto B_{\text{sol}} \propto I$ 
  - $\Phi$  proportional to  $I$ :  $\Phi = LI$
- Induced EMF (voltage)  
– Recall Faraday's law:
- Direction
  - Given by Lenz's Law
  - Opposes change in current!



$$\varepsilon = -\frac{\Delta\Phi}{\Delta t} = -L \frac{\Delta I}{\Delta t} = -L \frac{I_f - I_i}{t_f - t_i}$$

Units:  $L = \varepsilon t / I$   
 $1 \text{ H} = 1 \text{ V-sec/amp}$

# Physical Inductor

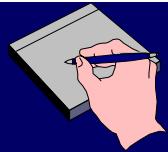

tries to maintain a constant  $I_{\text{normal}}$

$$L \equiv \frac{\Phi}{I}$$

Recall:  $\Phi = NBA \cos \phi$


$$L = \frac{NBA}{I}$$

Recall:  $B = \mu_0 nI$

~~$$L = \frac{N\mu_0 nIA}{I}$$~~

$$L = N\mu_0 nA$$
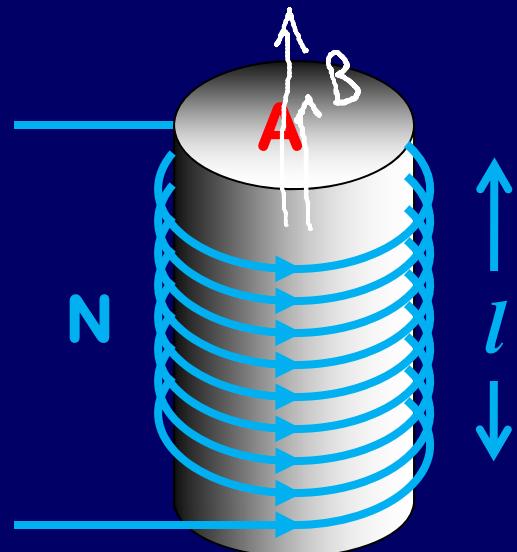
$$L = \mu_0 n^2 l A$$
$$= \mu_0 \frac{N^2}{l} A$$



(# turns) = (# turns/meter) x (# meters)

$$N = n l$$

Energy stored:

$$U = \frac{1}{2} LI^2$$



## ACT: Inductors


A  $10\ \Omega$  resistor is wired in series with a  $10\text{ V}$  battery and a  $1\text{ H}$  inductor. What is the voltage across the inductor?

(A)  $0\text{ V}$

(B)  $0.1\text{ V}$

(C)  $10\text{ V}$

$$|V_L| = L \frac{\Delta I}{\Delta t} = 0$$

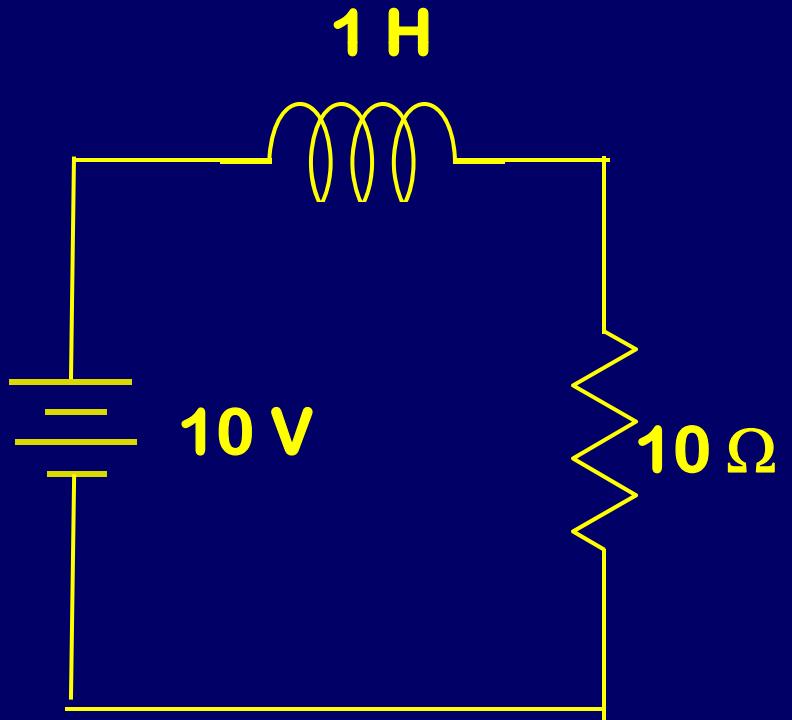


# RLC circuits

A circuit with an inductor, resistor, and capacitor in series!

Used in:

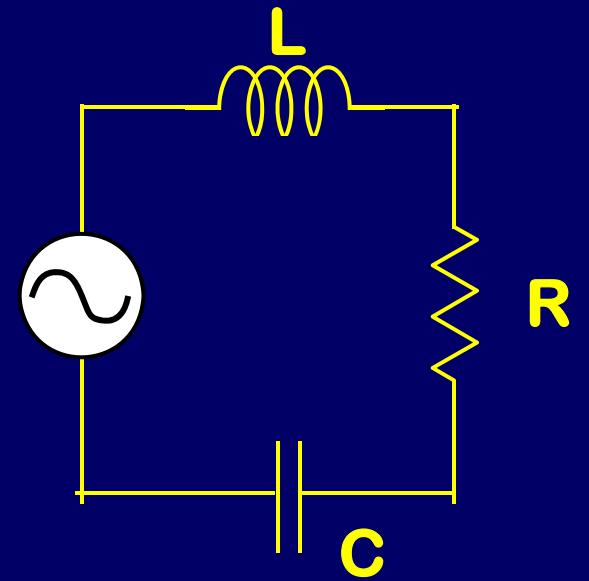- Cell phones / radios
- Computers
- Watches / clocks




First: Understand each element individually
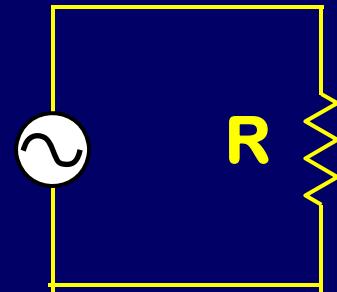
# Resistors in AC circuit





$$V_R = I R \text{ always true – Ohm's Law}$$




$$\bullet V_{R,\max} = I_{\max} R \quad \sqrt{V_{R,\text{rms}}} = I_{\text{rms}} R$$

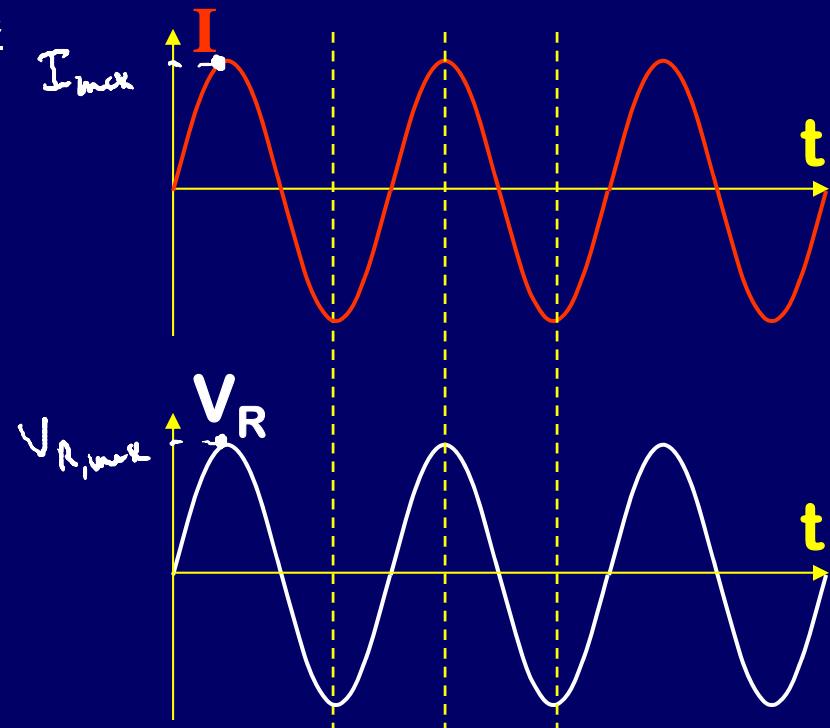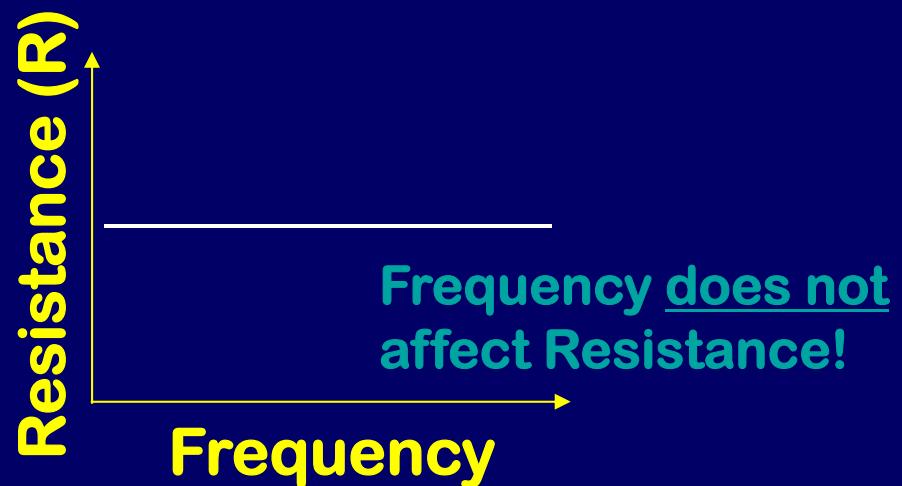- Voltage across resistor is “IN PHASE” with current.
  - $V_R$  goes up and down at the same times as  $I$  does.




# Capacitors in AC circuit


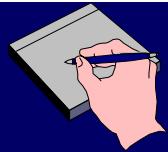


$$V_C = Q/C \text{ always true}$$

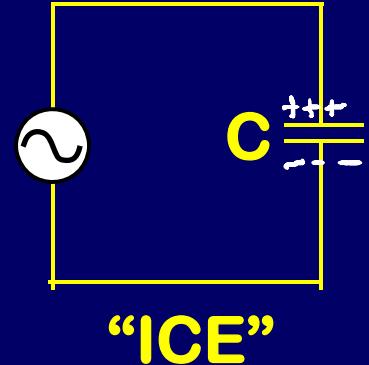- $V_{C,\max} = I_{\max} X_C$
- Capacitive Reactance: 
$$X_C = 1/(2\pi f C)$$
- Voltage across capacitor “LAGS” current.
  - $V_C$  goes up and down just after  $I$  does.



“ICE”

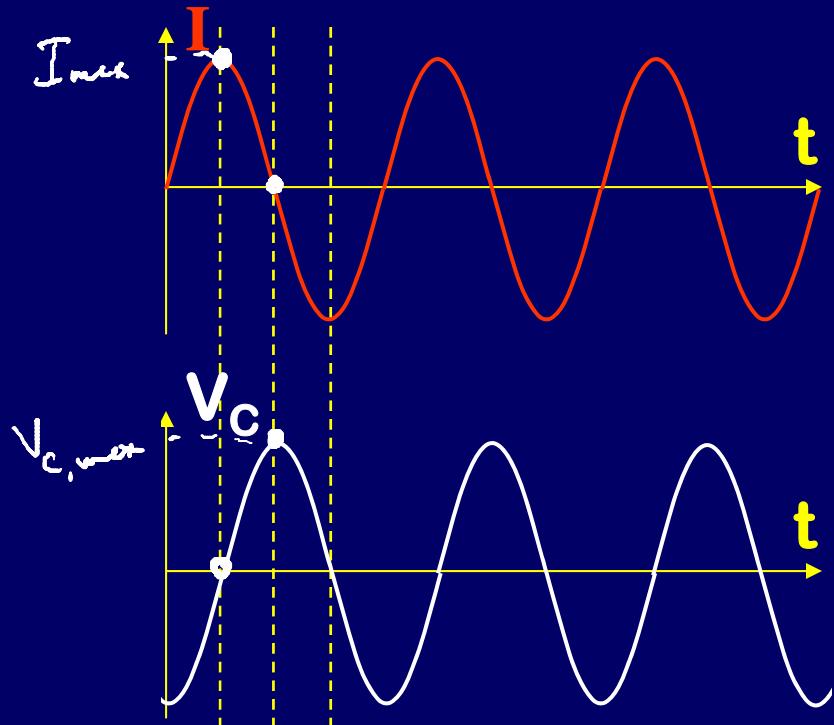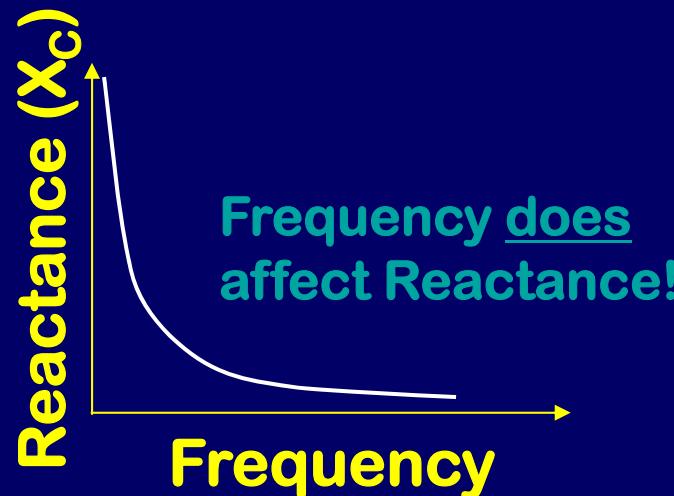

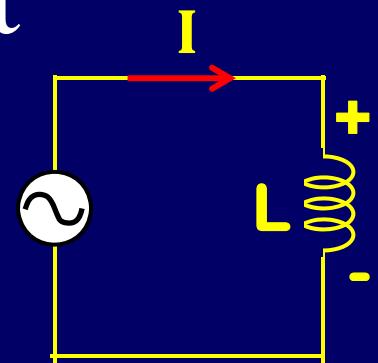
# Inductors in AC circuit





$$V_L = +L(\Delta I)/(\Delta t) \text{ always true}$$

- $V_{L,\max} = I_{\max} X_L$
- Inductive Reactance: 
$$X_L = 2\pi f L$$
- Voltage across inductor “LEADS” current.
  - $V_L$  goes up and down just before  $I$  does.



“ELI”

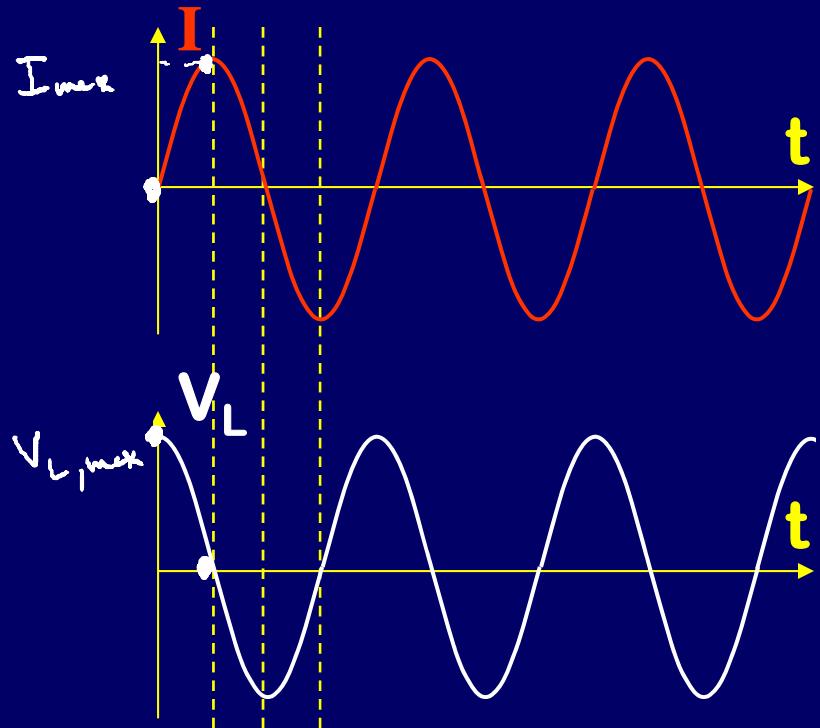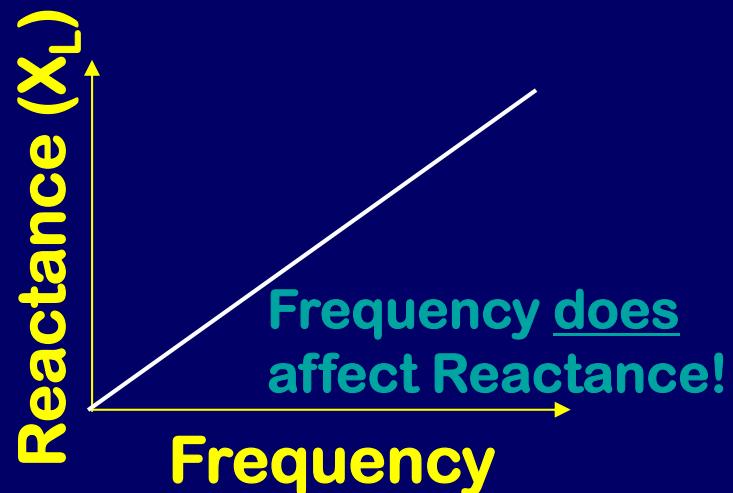





## ACT/CheckPoints 3.1, 3.2

The **capacitor** can be ignored when...

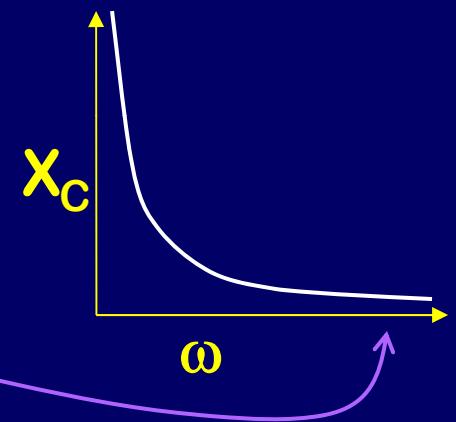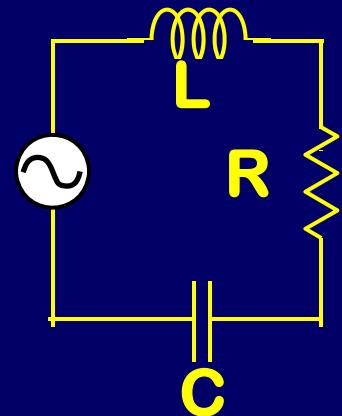- (a) frequency is very large
- (b) frequency is very small


very large  $\omega$  gives very small  $X_C$



The **inductor** can be ignored when...

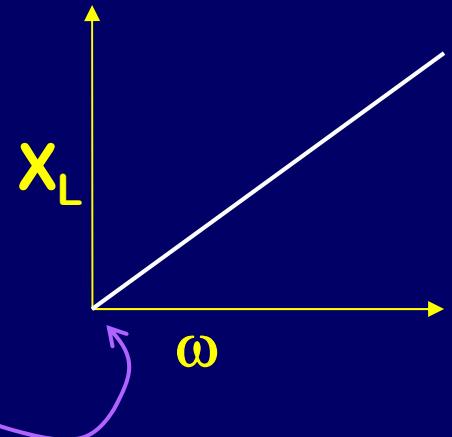- (a) frequency is very large
- (b) frequency is very small

very small  $\omega$  gives very small  $X_L$



# Example

# AC Circuit Voltages



An AC circuit with  $R = 2 \Omega$ ,  $C = 15 \text{ mF}$ , and  $L = 30 \text{ mH}$  has a current  $I(t) = 0.5 \sin(8\pi t)$  amps. Calculate the maximum voltage across  $R$ ,  $C$ , and  $L$ .



$$V_{R,\max} = I_{\max} R = 0.5 \times 2 = 1 \text{ Volt}$$

$$V_{C,\max} = I_{\max} X_C = 0.5 \times 1/(8\pi \times 0.015) = 1.33 \text{ Volts}$$

$$V_{L,\max} = I_{\max} X_L = 0.5 \times 8\pi \times 0.03 = 0.38 \text{ Volts}$$

$$X_C = \frac{1}{2\pi f C} = \frac{1}{\omega C}$$


$$X_L = 2\pi f L = \omega L$$

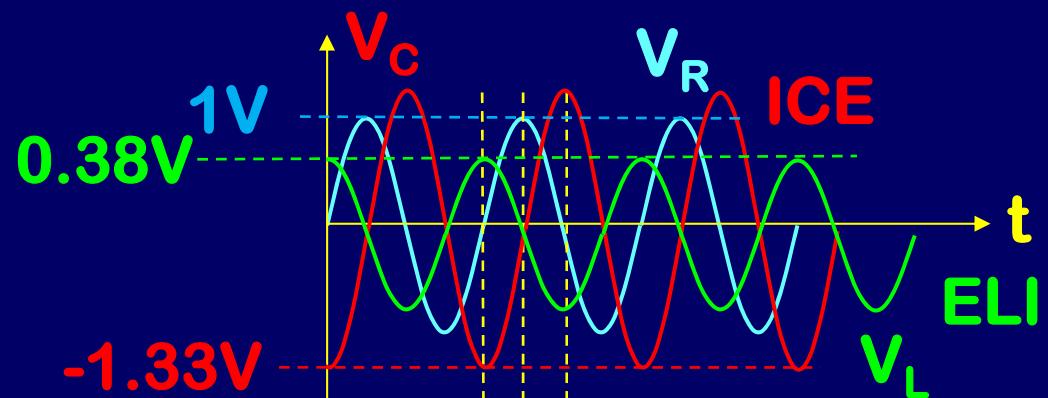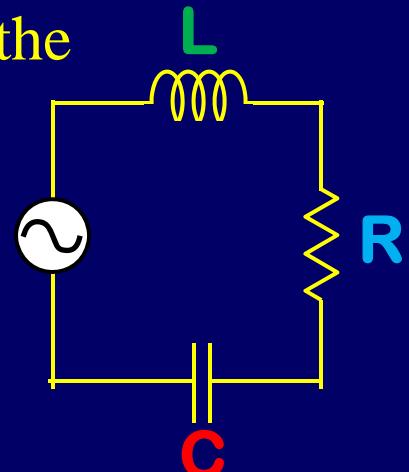


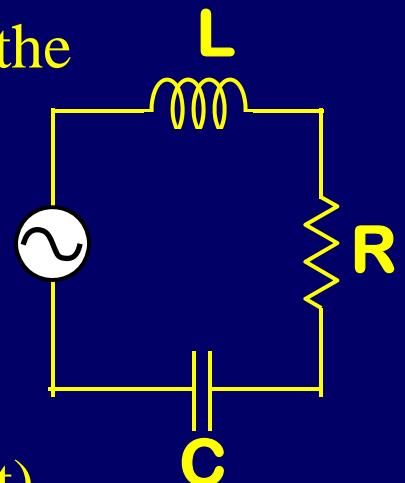
# ACT: AC Circuit Voltages

An AC circuit with  $R = 2 \Omega$ ,  $C = 15 \text{ mF}$ , and  $L = 30 \text{ mH}$  has a current  $I(t) = 0.5 \sin(8\pi t)$  amps. Calculate the maximum voltage across R, C, and L.



Now the frequency is increased so  $I(t) = 0.5 \sin(16\pi t)$ .

Which element's maximum voltage decreases?

- 1)  $V_{R,\max}$
- 2)  $V_{C,\max}$
- 3)  $V_{L,\max}$

**Stays same: R doesn't depend on f**

**Decreases:  $X_C = 1/(2\pi f C)$**

**Increases:  $X_L = 2\pi f L$**

# Summary so far...

- $I = I_{\max} \sin(2\pi ft)$
- $V_R = I_{\max} R \sin(2\pi ft)$ 
  - $V_R$  in phase with  $I$
- $V_C = I_{\max} X_C \sin(2\pi ft - \pi/2)$ 
  - $V_C$  lags  $I$     $X_C = \frac{1}{2\pi f C} = \frac{1}{\omega C}$   
“ICE”
- $V_L = I_{\max} X_L \sin(2\pi ft + \pi/2)$ 
  - $V_L$  leads  $I$     $X_L = 2\pi f L = \omega L$   
“ELI”

