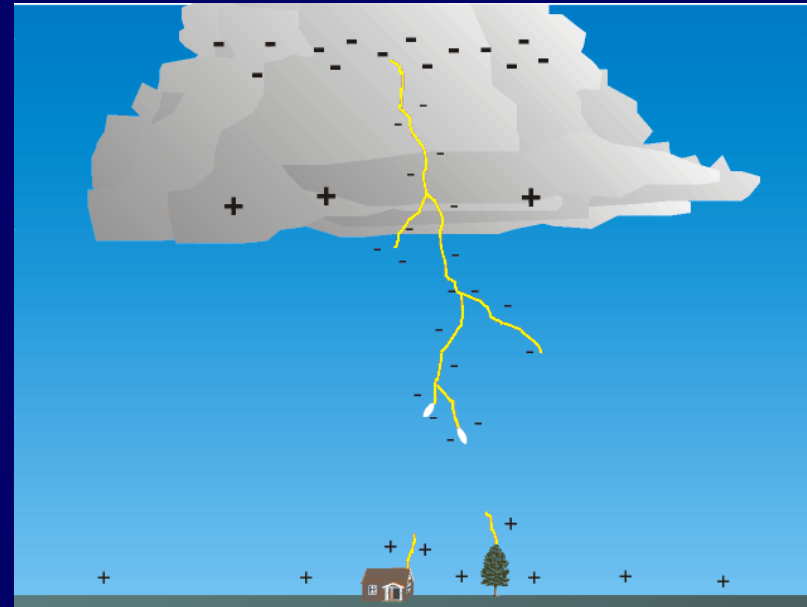


# Physics 102: Lecture 04

## Capacitors (& batteries)





# Physics 102 so far

## Basic principles of electricity

- Lecture 1 – electric charge & electric force
- Lecture 2 – electric field
- Lecture 3 – electric potential energy and electric potential
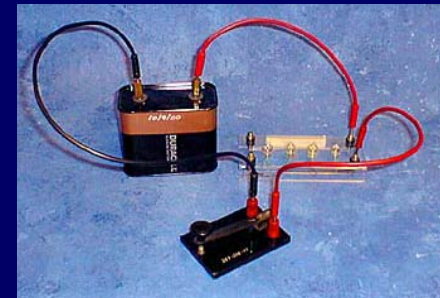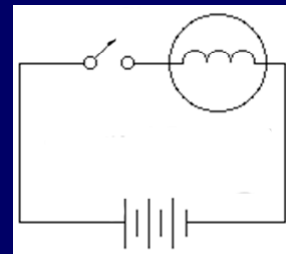
## Applications of electricity – circuits

- Lecture 4 – capacitance
- Lecture 5 – resistance
- Lecture 6 – Kirchhoff's rules
- Lecture 7 – RC circuits
- Lecture 12 & 13 – AC circuits



Recall from last lecture.....  
Electric Fields, Electric Potential

# Comparison:

## Electric *Potential Energy* vs. Electric *Potential*



$\Delta V_{AB}$  : the difference in electric potential between points B and A

$\Delta U_{AB}$  : the change in electric potential energy of a charge  $q$  when moved from A to B


$$\Delta U_{AB} = q \Delta V_{AB}$$

# Electric Potential: Summary

- E field lines point from **higher** to **lower** potential
- For positive charges, going from **higher to lower** potential is “downhill”

Positive charges tend to go “downhill”, from + to –

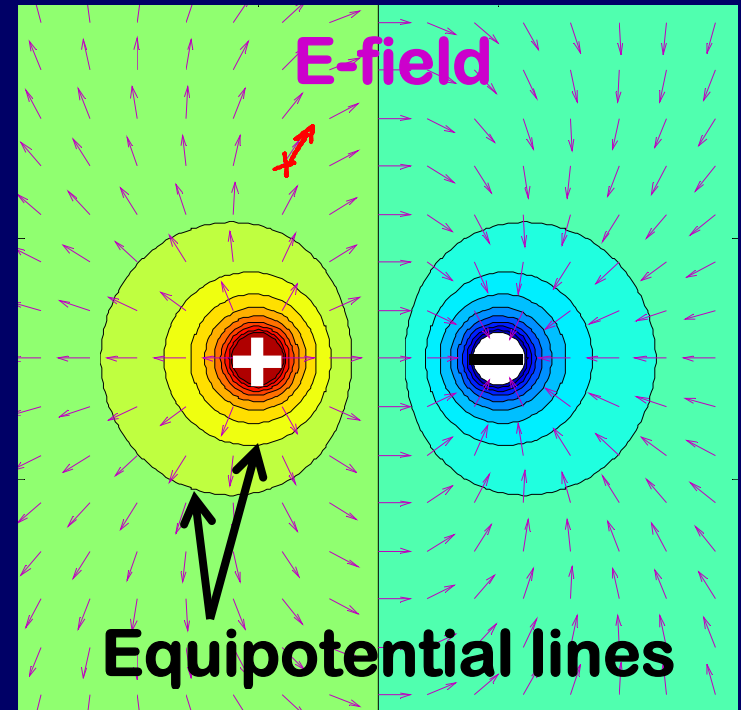Negative charges go in the opposite direction, from – to +



$$\Delta U_{AB} = q \Delta V_{AB}$$

# Uniform Electric Field: Important Special Case

Two large parallel conducting plates of area  $A$


- + $Q$  on one plate
- $Q$  on other plate

Then  $E$  is

- **uniform** between the two plates:  
 $E=4\pi kQ/A$
- **zero** everywhere else
- This result is **independent of plate separation**

*only for very large plates*

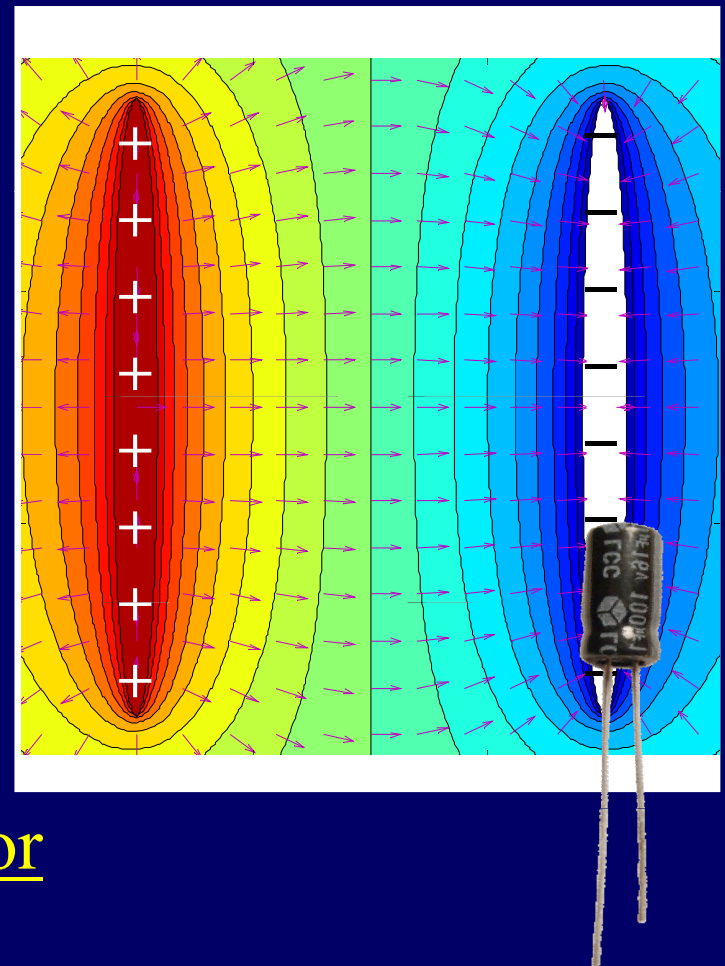This is called a parallel plate capacitor






# Parallel Plate Capacitor: Potential Difference


Charge  $Q$  on plates

$$V = V_A - V_B = +E d \quad (\text{like } W = qEd = \Delta U; \Delta V = \Delta U/q)$$
$$= 4 \pi k Q d / A \quad V \propto Q$$

Voltage is proportional  
to the charge!

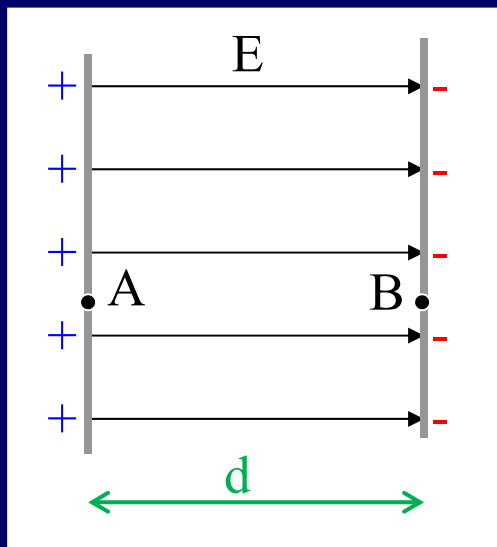

## PhET Simulation

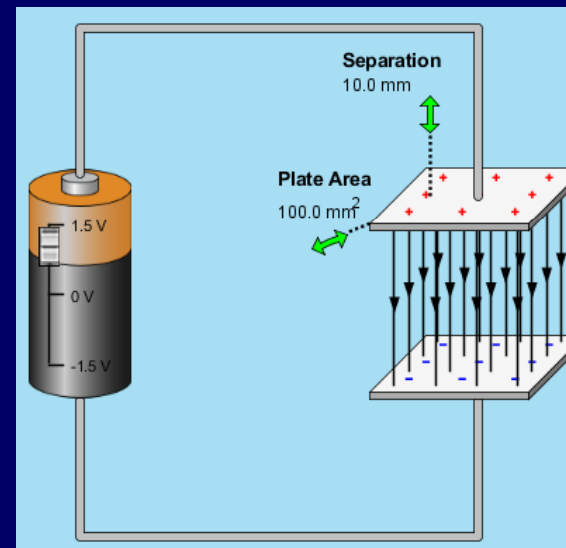

# Capacitance: The ability to store separated charge $C \equiv Q/V$


- Any pair conductors separated by a small distance. (e.g. two metal plates)
- Capacitor stores separated charge  $Q = CV$ 
  - Positive  $Q$  on one conductor, negative  $Q$  on other
  - Net charge is zero

- Stores Energy  $U_c = \frac{1}{2} Q V$

$$U_c = \frac{1}{2} C V^2 = \frac{1}{2} \frac{Q^2}{C}$$

Units:

1 Coulomb/Volt  
= 1 Farad (F)

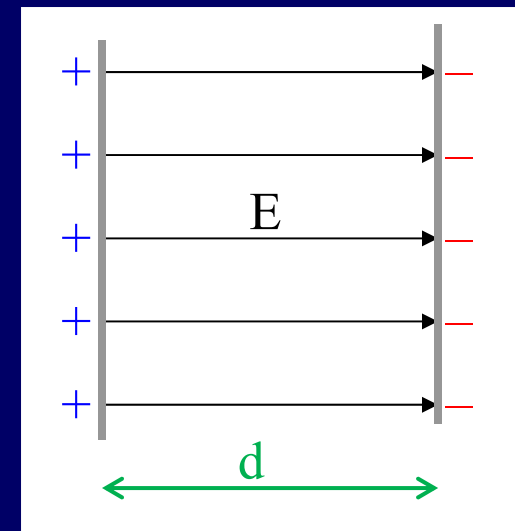



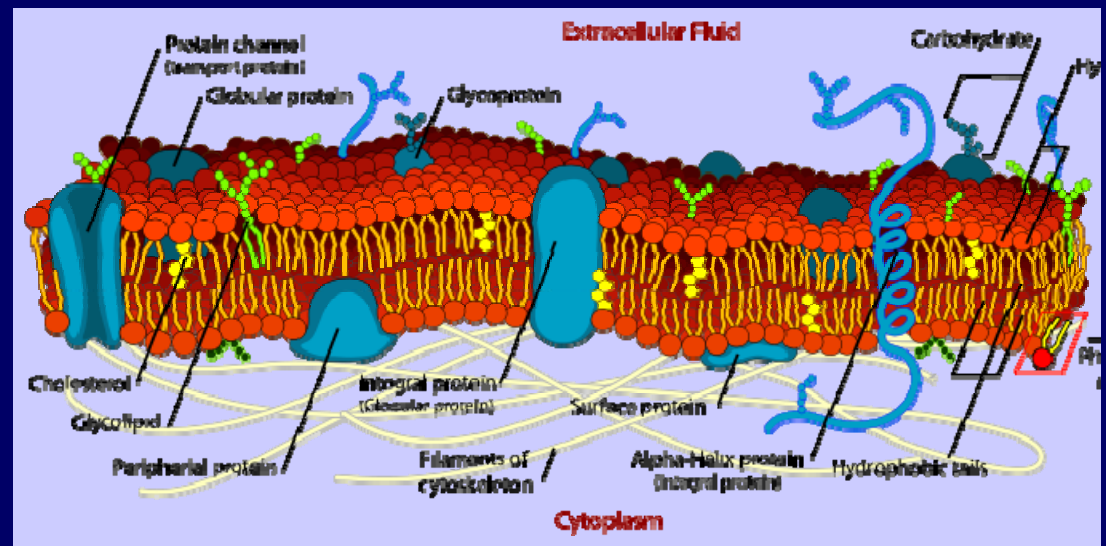
# Why Separate Charge?

*A way to store and release energy!*

- Camera Flash
- Defibrillator
- AC  $\rightarrow$  DC
- Tuners / resonant circuits
  - Radio
  - Cell phones
- Cell membranes



# Capacitance of Parallel Plate Capacitor



$$V = Ed \quad E = 4\pi kQ/A$$

(Between two large plates)

$$\text{So: } V = 4\pi kQd/A$$

$$\text{Recall: } C \equiv Q/V$$



$$\text{So: } C = A/(4\pi kd)$$

Recall: Lect. 1

$$\epsilon_0 = 1/(4\pi k) = 8.85 \times 10^{-12} \text{ C}^2/\text{Nm}^2$$


$$C = \epsilon_0 A/d$$

Parallel plate capacitor

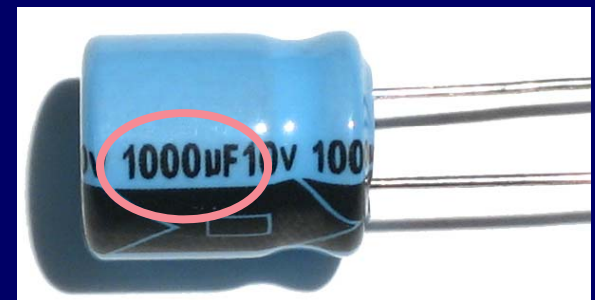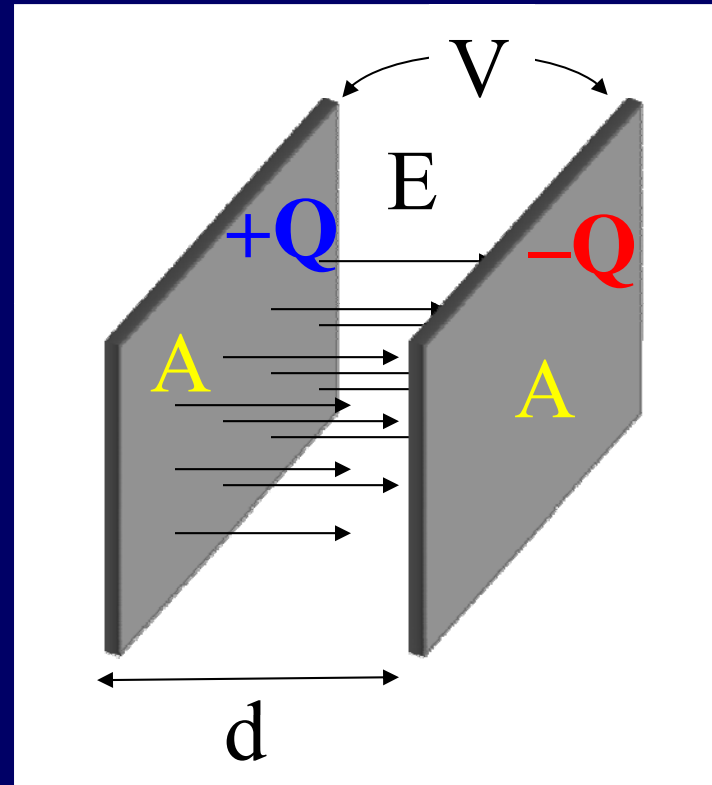
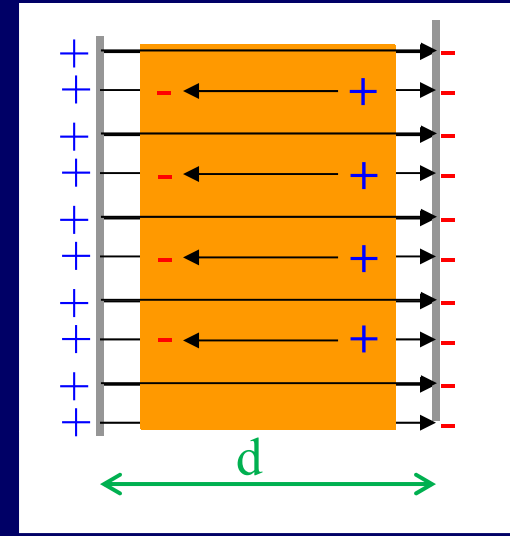
# Dielectric

- Placing a dielectric (insulator) between the plates increases the capacitance.




Dielectric constant ( $\kappa > 1$ )

$$C = \kappa C_0$$

Capacitance without dielectric


Capacitance with dielectric

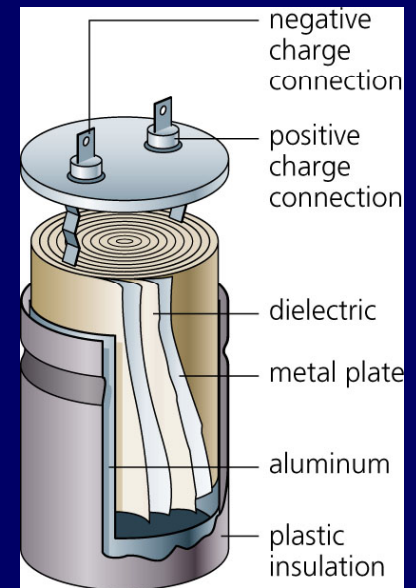For same charge  $Q$ ,  $E$  (and  $V$ ) is reduced so  $C = Q/V$  increases





# ACT: Parallel Plates

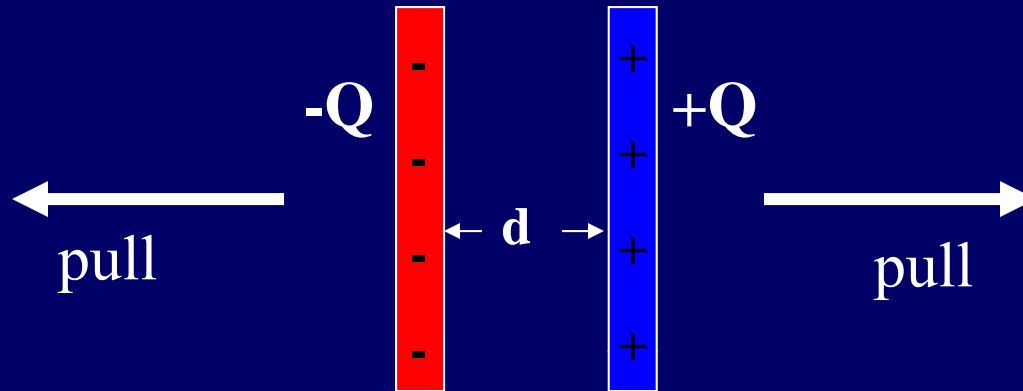

A parallel plate capacitor given a charge  $Q$ . The plates are then pulled a **small** distance further apart. What happens to the charge  $Q$  on each plate of the capacitor?


A) Increases

B) Constant

C) Decreases

Remember charge is real/physical. There is no place for the charges to go.

# CheckPoint 4.1

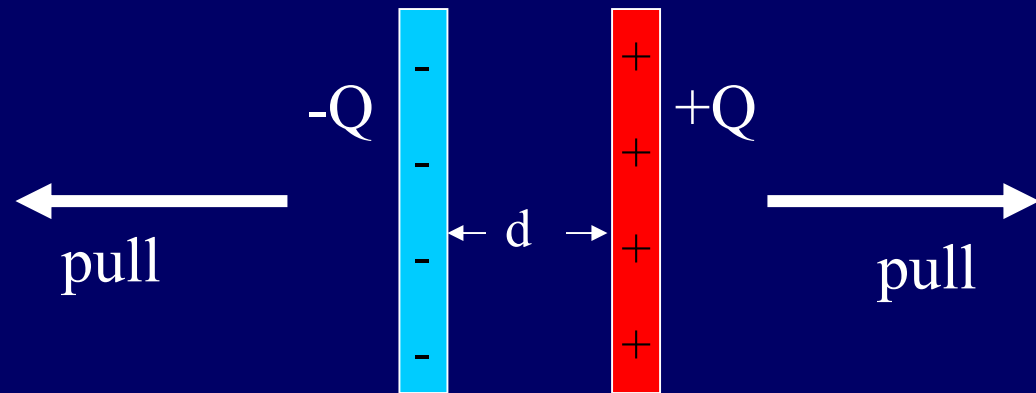

A parallel plate capacitor given a charge  $Q$ . The plates are then pulled a **small** distance further apart. Which of the following apply to the situation after the plates have been moved?

1) The capacitance increases

87%

True

**False**

$C = \epsilon_0 A / d$        **$C$  decreases!**

2) The electric field increases

92%

True

**False**

$E = Q / (\epsilon_0 A)$       **Constant**

3) The voltage between the plates increases

19%


**True**

False

$V = Ed$



# ACT/CheckPoint 4.1

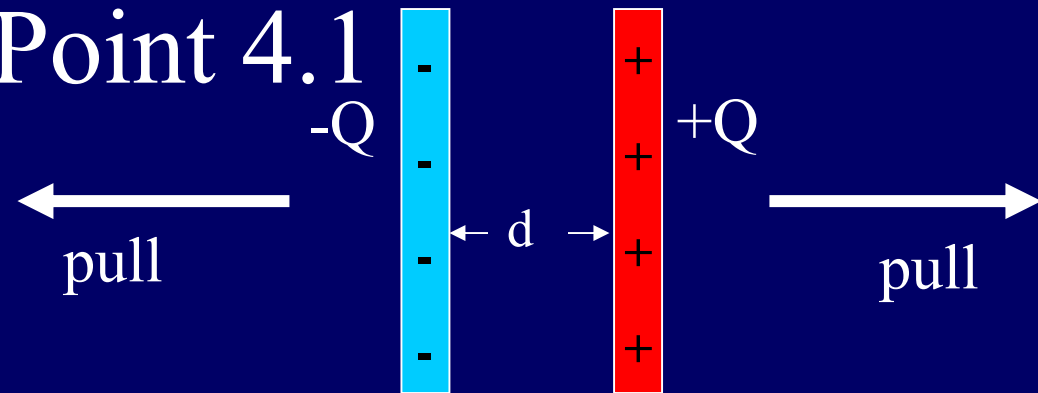

A parallel plate capacitor given a charge  $Q$ . The plates are then pulled a **small** distance further apart. Which of the following apply to the situation after the plates have been moved?

The energy stored in the capacitor

A) increases

B) constant


C) decreases

$$U = \frac{1}{2} QV \quad Q \text{ constant, } V \text{ increased}$$



$$U = \frac{1}{2} C V^2$$

Plates are attracted to each other, you must pull them apart, so the potential energy of the plates increases.


# Capacitors are used in circuits!

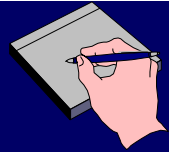

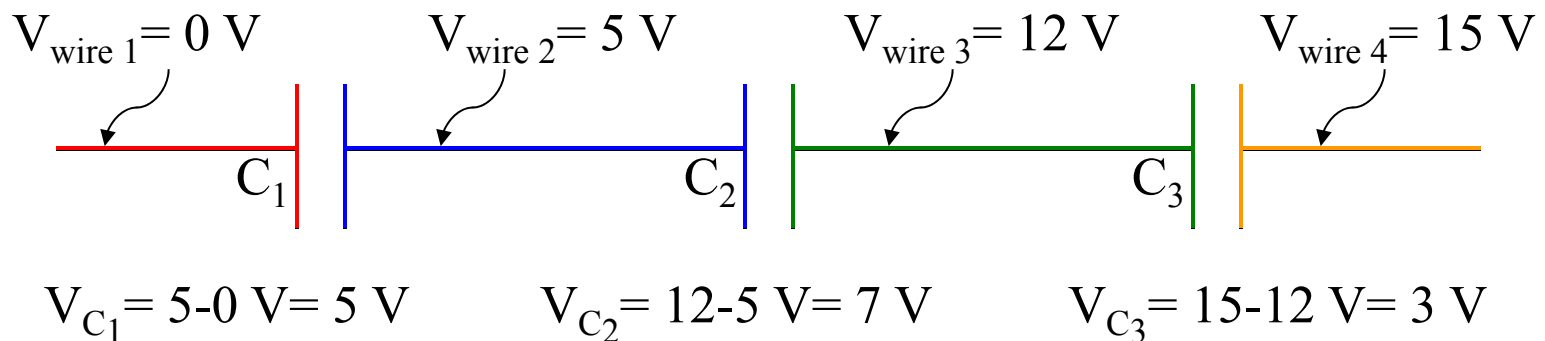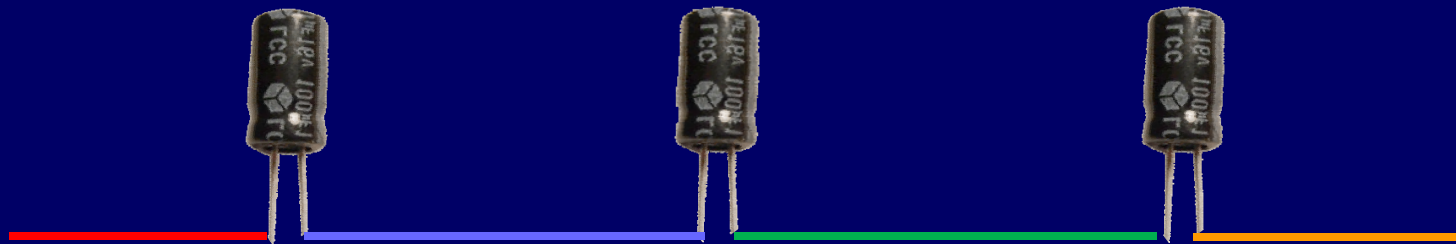
- In circuits, elements are connected by wires.
- Any connected region of wire has the same potential.
- The potential difference across an element is the *element's* “voltage.”



To understand complex circuits...

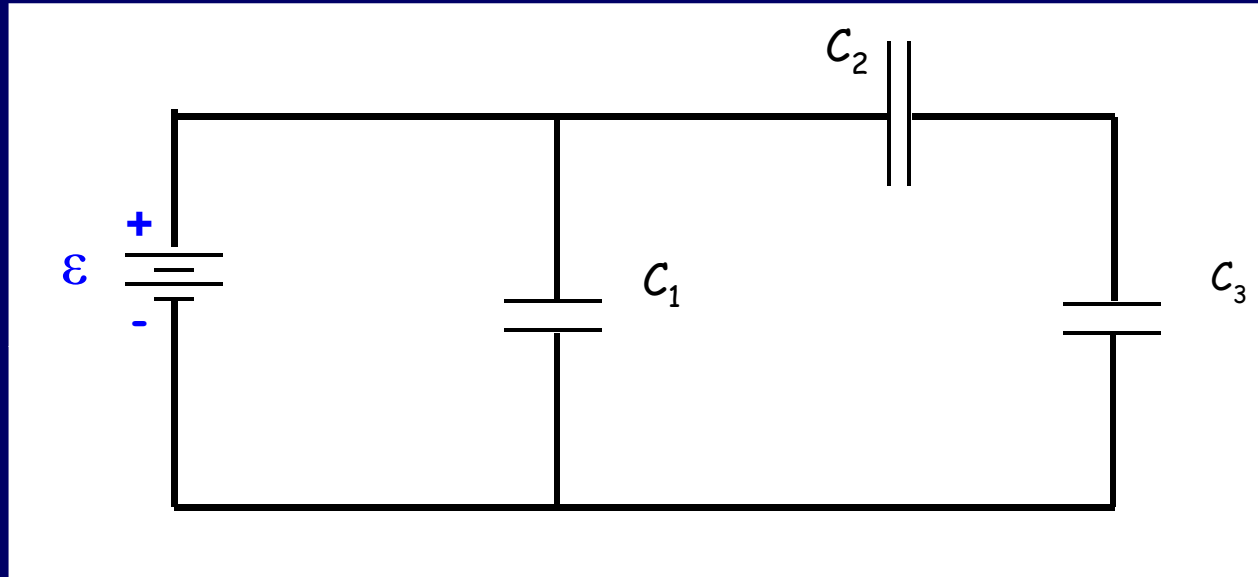

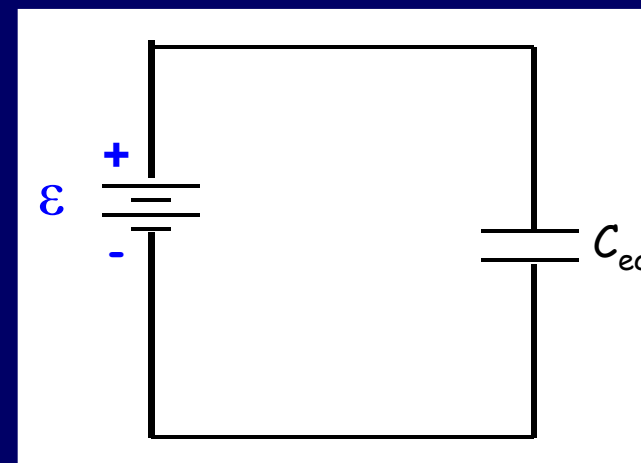
...treat capacitors in series and parallel as a fictitious equivalent capacitor!





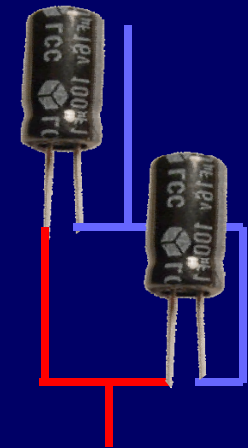
# Capacitors in Parallel


- Both ends connected together by wire
- Same voltage:  $V_1 = V_2 = V_{eq}$
- Share Charge:  $Q_{eq} = Q_1 + Q_2$   $C = Q/V$
- Equivalent C:  $C_{eq} = C_1 + C_2$



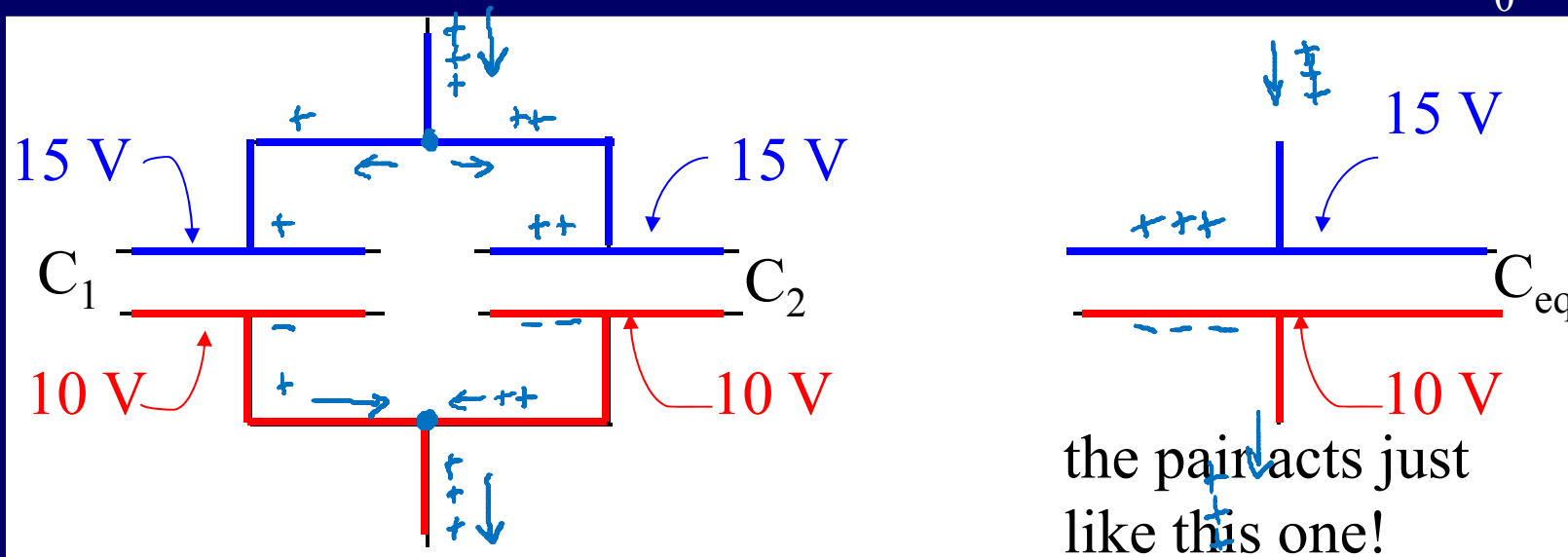Add areas – remember  $C = \epsilon_0 A/d$



# Example

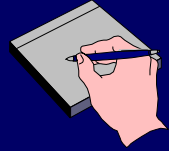

## Parallel Practice


A  $4 \mu\text{F}$  capacitor and  $6 \mu\text{F}$  capacitor are connected in parallel and charged to 5 volts. Calculate  $C_{\text{eq}}$ , and the charge on each capacitor.

$$C_{\text{eq}} = C_4 + C_6 = 4 \mu\text{F} + 6 \mu\text{F} = 10 \mu\text{F}$$

$$Q_4 = C_4 V_4 = (4 \mu\text{F})(5 \text{ V}) = 20 \mu\text{C}$$

$$Q_6 = C_6 V_6 = (6 \mu\text{F})(5 \text{ V}) = 30 \mu\text{C}$$
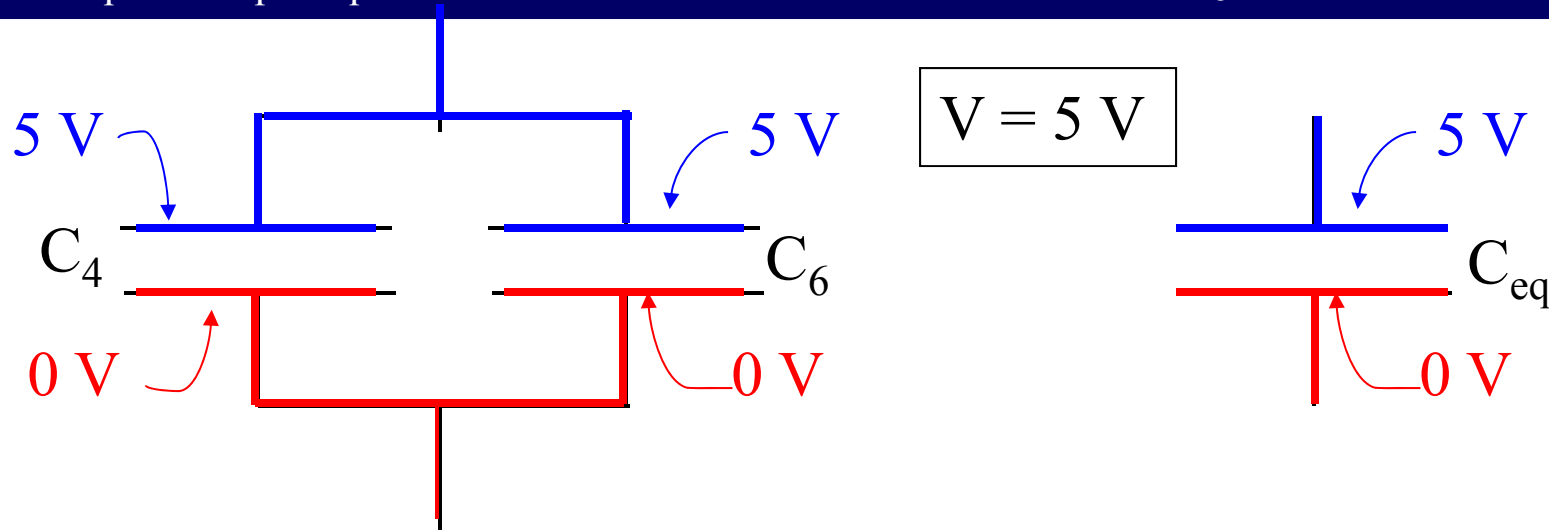
$$Q_{\text{eq}} = C_{\text{eq}} V_{\text{eq}} = (10 \mu\text{F})(5 \text{ V}) = 50 \mu\text{C} = Q_4 + Q_6$$





# Capacitors in Series

- Connected end-to-end with NO other exits

- Same Charge:  $Q_1 = Q_2 = Q_{eq}$


- Share Voltage:  $V_1 + V_2 = V_{eq}$   
 $\frac{1}{C_1} + \frac{1}{C_2} = \frac{1}{C_{eq}}$

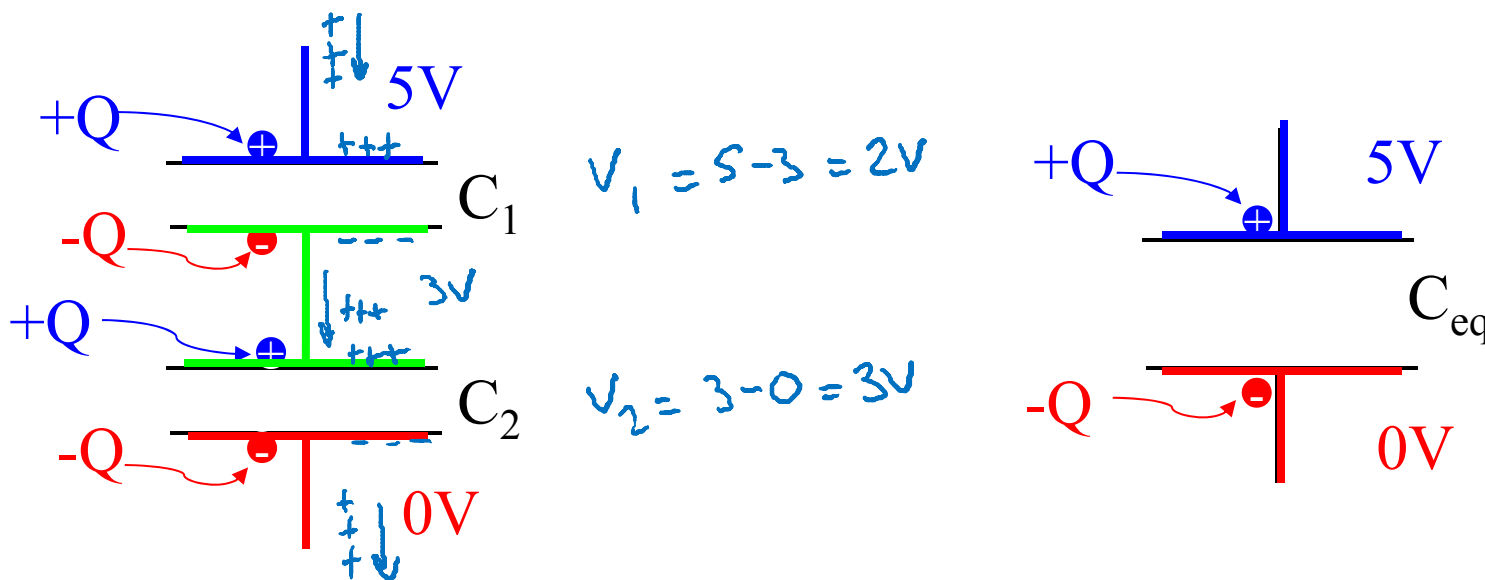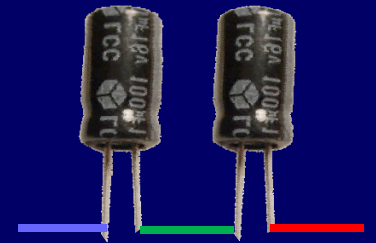- Equivalent C:  $\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2}$  Add d – remember  $C = \epsilon_0 A/d$



# Example

## Series Practice

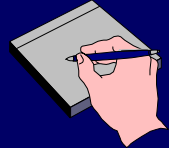


A  $4\ \mu\text{F}$  capacitor and  $6\ \mu\text{F}$  capacitor are connected in series and charged to 5 volts. Calculate  $C_{eq}$ , and the charge on the  $4\ \mu\text{F}$  capacitor.

$$C_{eq} = \left( \frac{1}{C_4} + \frac{1}{C_6} \right)^{-1} = \left( \frac{1}{4\ \mu\text{F}} + \frac{1}{6\ \mu\text{F}} \right)^{-1} = \underline{\underline{2.4\ \mu\text{F}}}$$

$$Q = CV$$
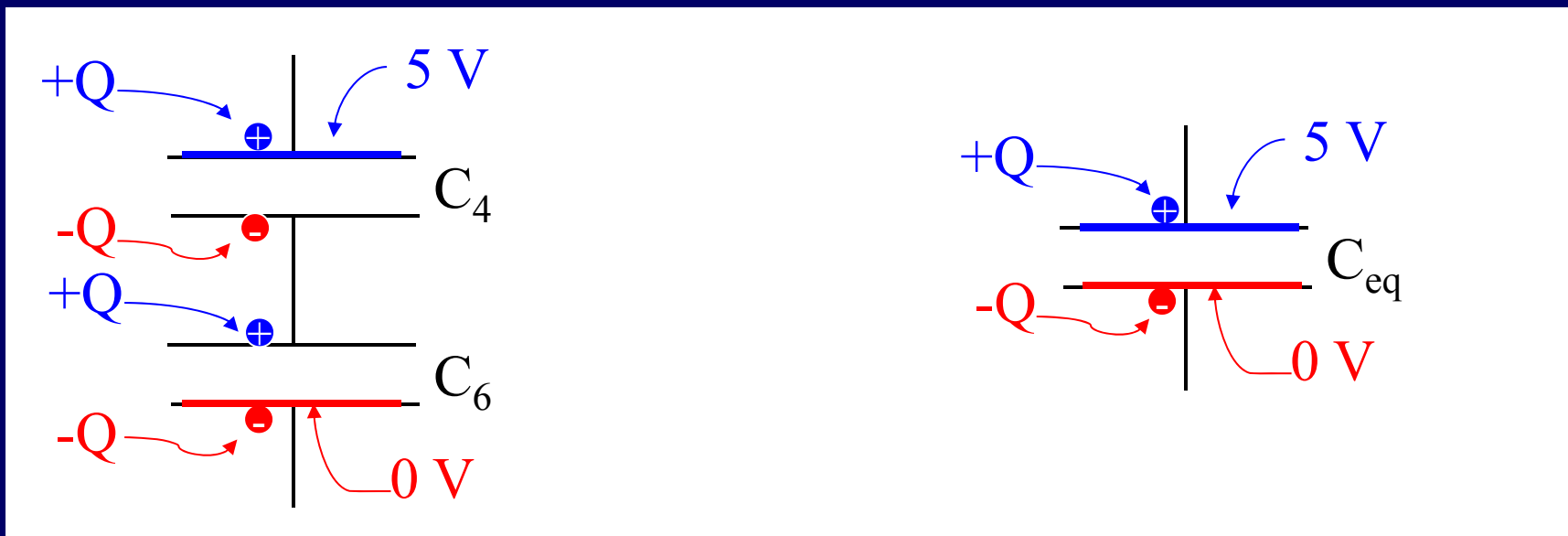
$$Q_4 = Q_6 = Q_{eq} = C_{eq}V = (2.4\ \mu\text{F})(5\text{V}) = 12\ \mu\text{C}$$





# Comparison: *Series vs. Parallel*

## Series

- Can follow a wire from one element to the other with no branches in between.
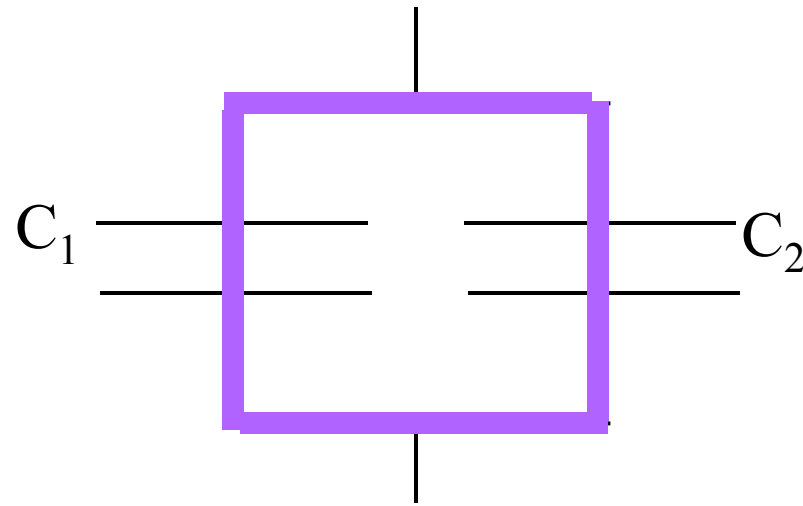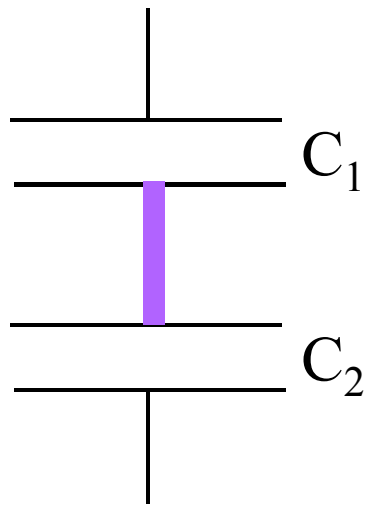
## Parallel

- Can find a loop of wire containing both elements but no others (may have branches).




# Electromotive Force

- **Battery**

- Maintains constant potential difference  $V$  (electromotive force – emf  $\epsilon$ )
- Does NOT produce or supply charges, just “pushes” them.

Like a pump for charge!

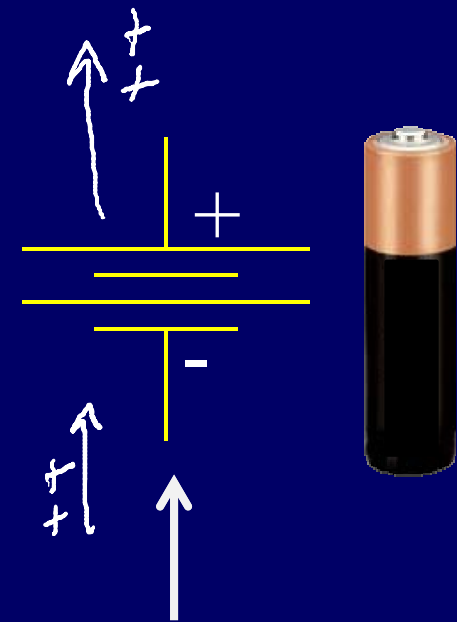


Usually “0V”  
by convention

# CheckPoint 4.4

A circuit consists of three initially uncharged capacitors  $C_1$ ,  $C_2$ , and  $C_3$ , which are then connected to a battery of emf  $\varepsilon$ . The capacitors obtain charges  $q_1$ ,  $q_2$ ,  $q_3$ , and have voltages across their plates  $V_1$ ,  $V_2$ , and  $V_3$ .  $C_{eq}$  is the equivalent capacitance of the circuit. Which of these are true?

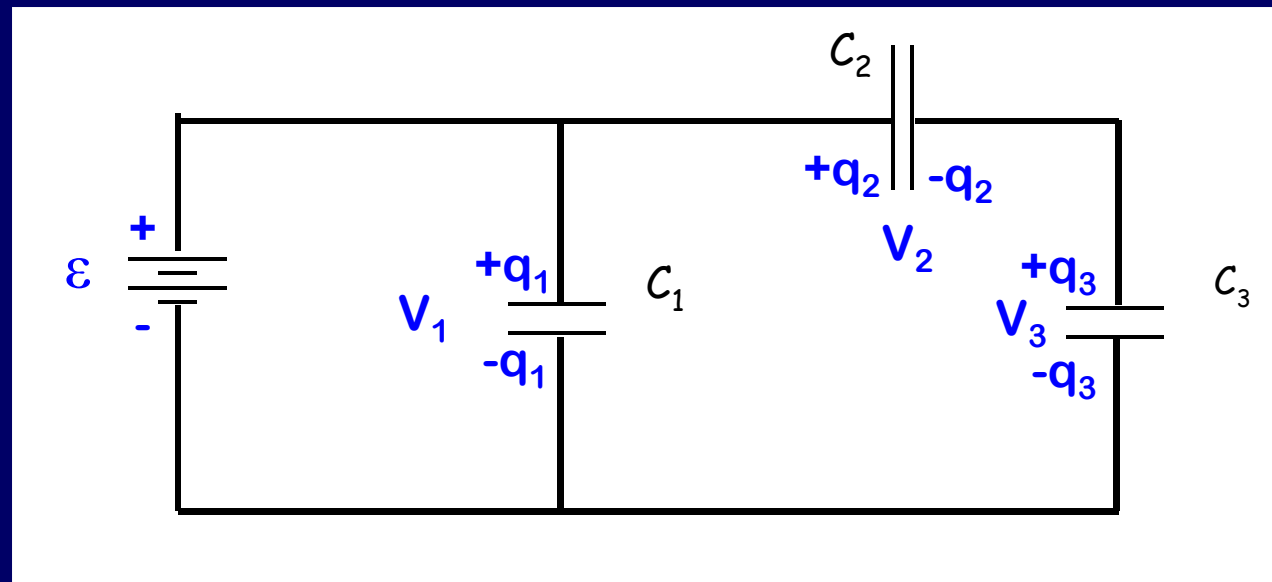
- 1)  $q_1 = q_2$
- 2)  $q_2 = q_3$
- 3)  $V_2 = V_3$
- 4)  $\varepsilon = V_1$
- 5)  $V_1 < V_2$




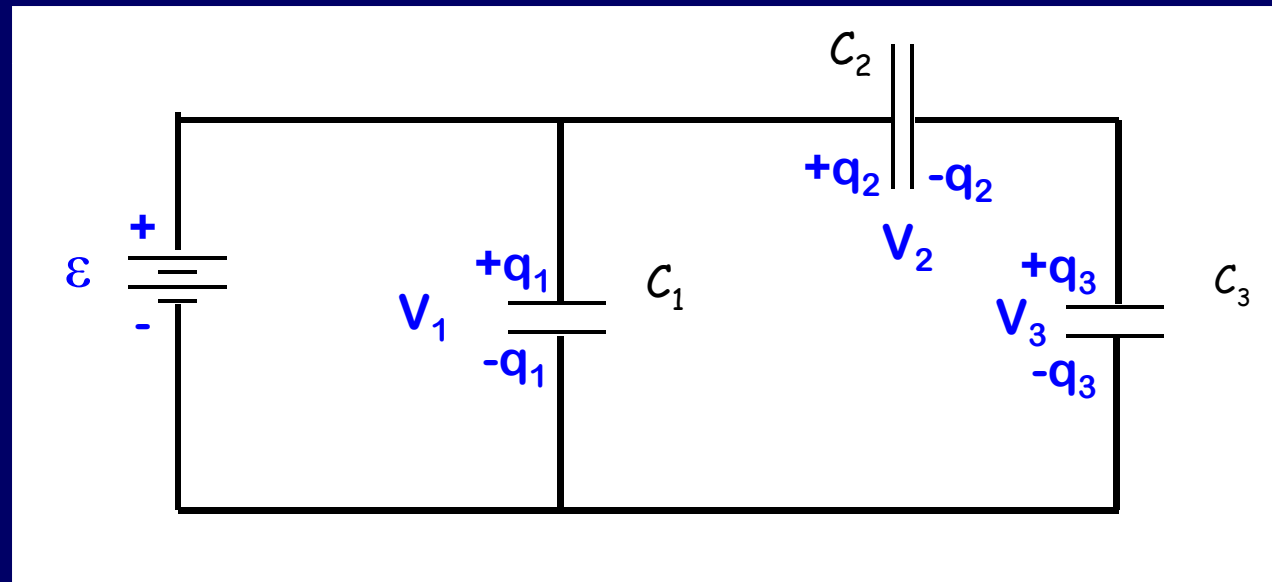
## ACT/CheckPoint 4.4: Which is true?

A circuit consists of three initially uncharged capacitors  $C_1$ ,  $C_2$ , and  $C_3$ , which are then connected to a battery of emf  $\varepsilon$ . The capacitors obtain charges  $q_1$ ,  $q_2$ ,  $q_3$ , and have voltages across their plates  $V_1$ ,  $V_2$ , and  $V_3$ .  $C_{eq}$  is the equivalent capacitance of the circuit.



1)  $q_1 = q_2$  Not necessarily.  $C_1$  and  $C_2$  are NOT in series.


2)  $q_2 = q_3$  Yes!  $C_2$  and  $C_3$  are in series.




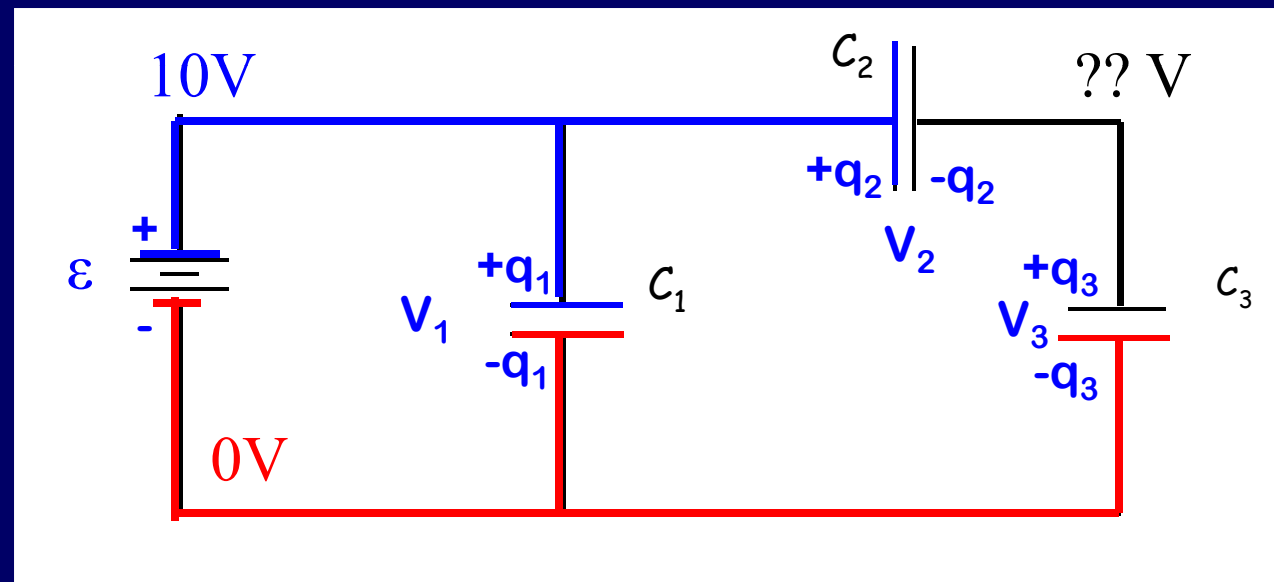
## ACT/CheckPoint 4.4: Which is true?

A circuit consists of three initially uncharged capacitors  $C_1$ ,  $C_2$ , and  $C_3$ , which are then connected to a battery of emf  $\varepsilon$ . The capacitors obtain charges  $q_1$ ,  $q_2$ ,  $q_3$ , and have voltages across their plates  $V_1$ ,  $V_2$ , and  $V_3$ .  $C_{eq}$  is the equivalent capacitance of the circuit.



1)  $V_2 = V_3$  Not necessarily, only if  $C_2 = C_3$

2)  $\varepsilon = V_1$  Yes! Both ends are connected by wires

# Recap of Today's Lecture

- Capacitance  $C = Q/V$
- Parallel Plate:  $C = \epsilon_0 A/d$
- Capacitors in parallel:  $C_{\text{eq}} = C_1 + C_2$
- Capacitors in series:  $1/C_{\text{eq}} = 1/C_1 + 1/C_2$
- Batteries provide fixed potential difference