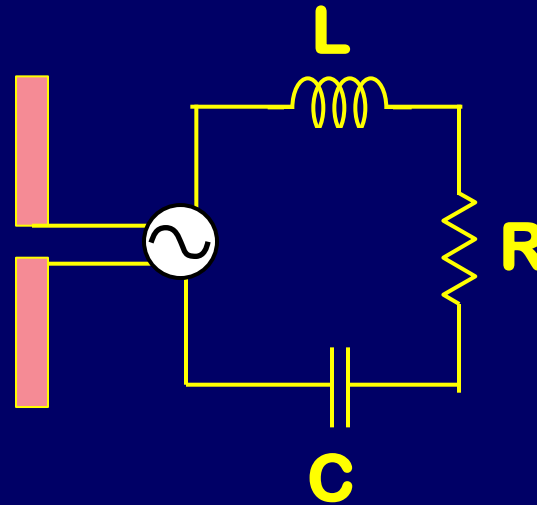




Physics 102: Lecture 13

RLC circuits & Resonance




Review: AC Circuit

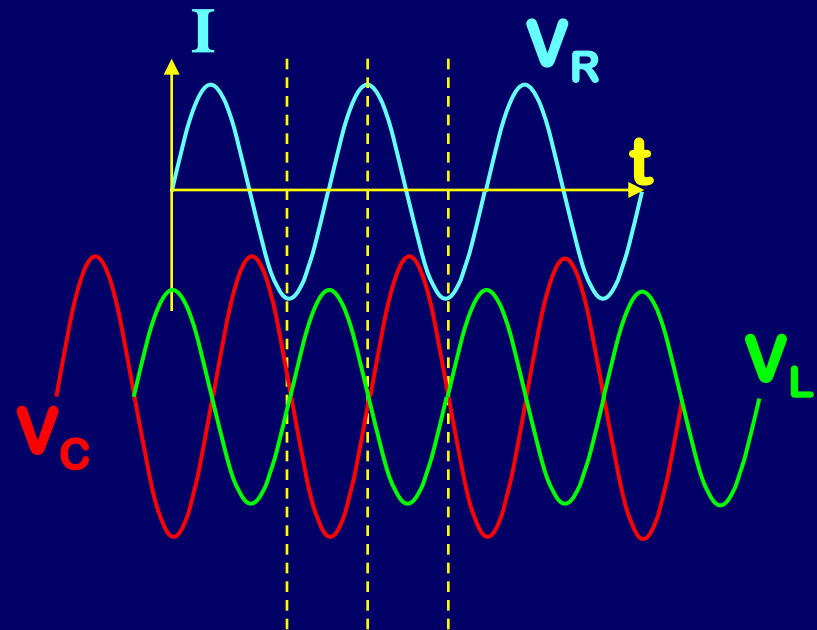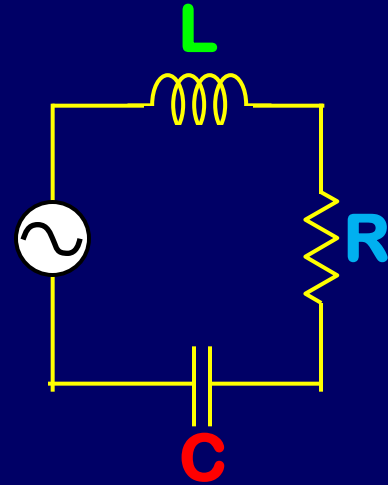- $I = I_{\max} \sin(2\pi ft)$
- $V_R = I_{\max} R \sin(2\pi ft)$
 - V_R in phase with I
- $V_C = I_{\max} X_C \sin(2\pi ft - \pi/2)$
 - V_C lags I “ICE”
- $V_L = I_{\max} X_L \sin(2\pi ft + \pi/2)$
 - V_L leads I “ELI”



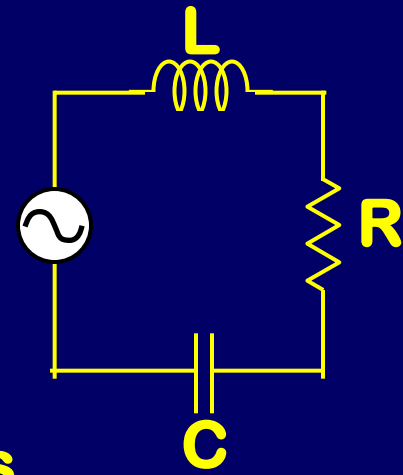Peak & RMS values in AC Circuits (REVIEW)



**When asking about RMS or Maximum values
relatively simple expressions**

$$V_{R,\max} = I_{\max}R$$


$$V_{C,\max} = I_{\max}X_C \quad X_C = \frac{1}{2\pi fC} = \frac{1}{\omega C}$$

$$V_{L,\max} = I_{\max}X_L \quad X_L = 2\pi fL = \omega L$$

Kirchhoff: generator voltage




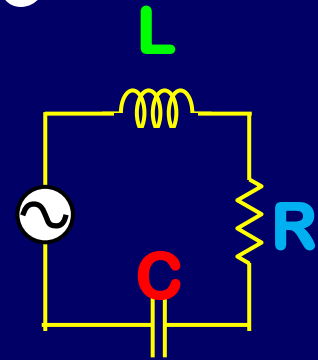- **Instantaneous** voltage across generator (V_{gen}) must equal sum of voltage across all of the elements at all times:



$$V_{\text{gen}}(t) = V_R(t) + V_C(t) + V_L(t)$$
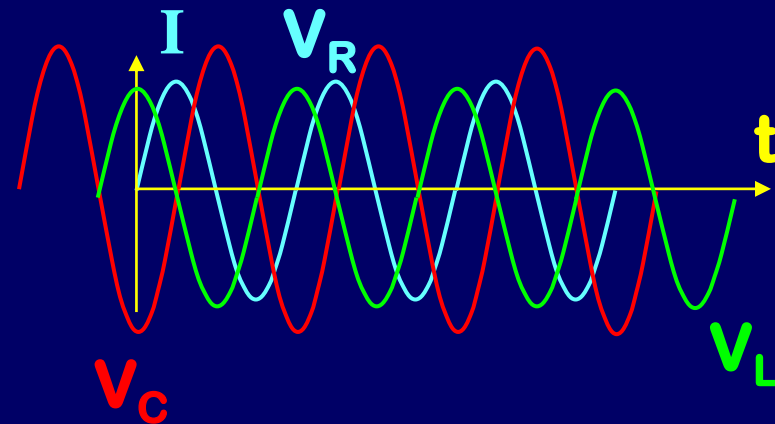
$$V_{\text{gen,max}} \neq V_{L,\text{max}} + V_{R,\text{max}} + V_{C,\text{max}}$$



What is $V_{\text{gen,max}}$?

Define impedance Z : $V_{\text{gen,max}} \equiv I_{\text{max}} Z$

Like: $V=IR$


$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

One last ingredient: is the generator voltage leading or lagging the current?

$$I = I_{max} \sin(2\pi ft)$$

$$V_{gen} = I_{max} Z \sin(2\pi ft + \phi)$$

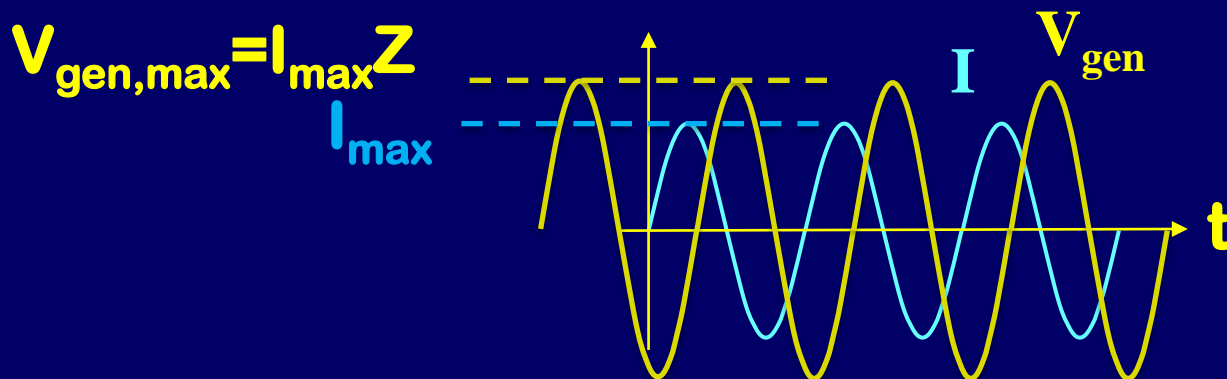Phase angle: $\tan(\phi) = \frac{(X_L - X_C)}{R}$



$\phi < 0$, voltage is lagging

Power in AC circuits

- The voltage generator supplies power.
 - Only resistor dissipates power.
 - Capacitor and Inductor store and release energy.
- $P(t) = I(t)V_R(t)$ oscillates so sometimes power loss is large, sometimes small.
- Average power dissipated by resistor:

$$\begin{aligned}\bar{P} &= \frac{1}{2} I_{\max} V_{R,\max} \\ &= \frac{1}{2} I_{\max} V_{\text{gen},\max} \cos(\phi) \\ &= I_{\text{rms}} V_{\text{gen},\text{rms}} \cos(\phi)\end{aligned}$$

If there is only a resistor, $\phi = 0$



Example

Problem Time!

An AC circuit with $R = 2 \Omega$, $C = 15 \text{ mF}$, and $L = 30 \text{ mH}$ is driven by a generator with voltage $V(t) = 2.5 \sin(8\pi t)$ Volts. Calculate the maximum current in the circuit, and the phase angle.

$$I_{\max} = V_{\text{gen,max}} / Z$$


$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$Z =$$

$$I_{\max} = \quad = \quad \text{Amps}$$

$$\tan(\phi) = \frac{X_L - X_C}{R} =$$

$$\phi =$$

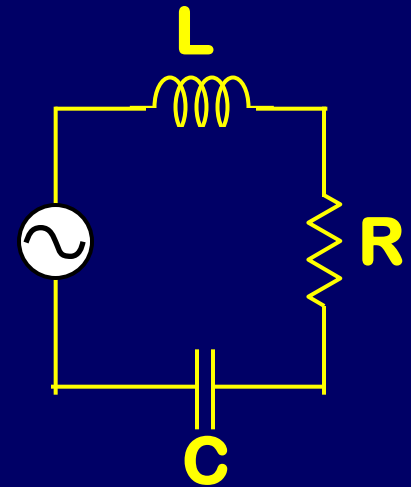





ACT: Power dissipation

Which one of these circuits dissipates the most power?


$$V_{\text{gen,max}} = 10 \text{ V}$$

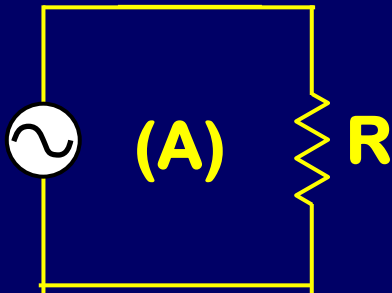


$$V_{\text{gen,max}} = 100 \text{ V}$$

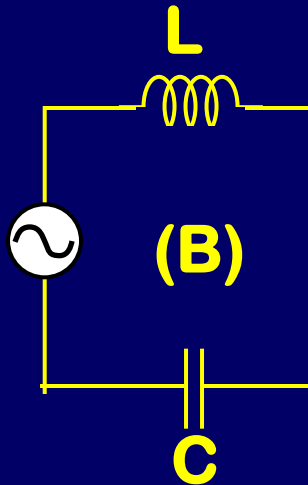

$$\varepsilon = 1 \text{ V}$$

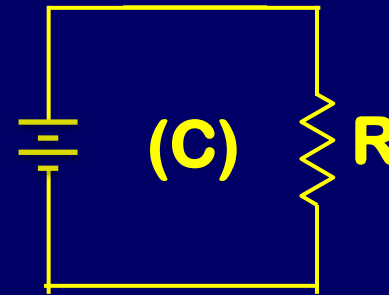

Kirchhoff: generator voltage

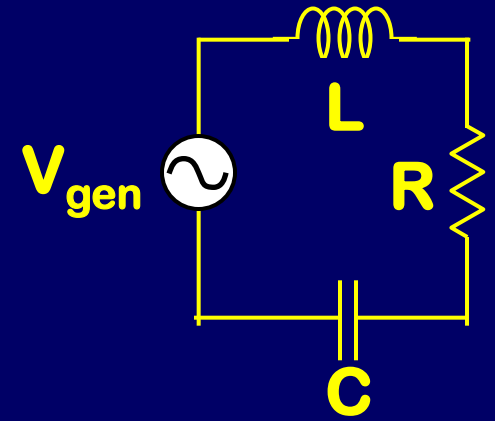


Write down Kirchhoff's Loop Equation:

$$V_{\text{gen}}(t) = \cancel{V_L(t)} + V_R(t) + \cancel{V_C(t)} \text{ at every instant of time}$$


If the frequency is just right...

$$V_{\text{gen}}(t) = V_R(t)$$

Resonance!

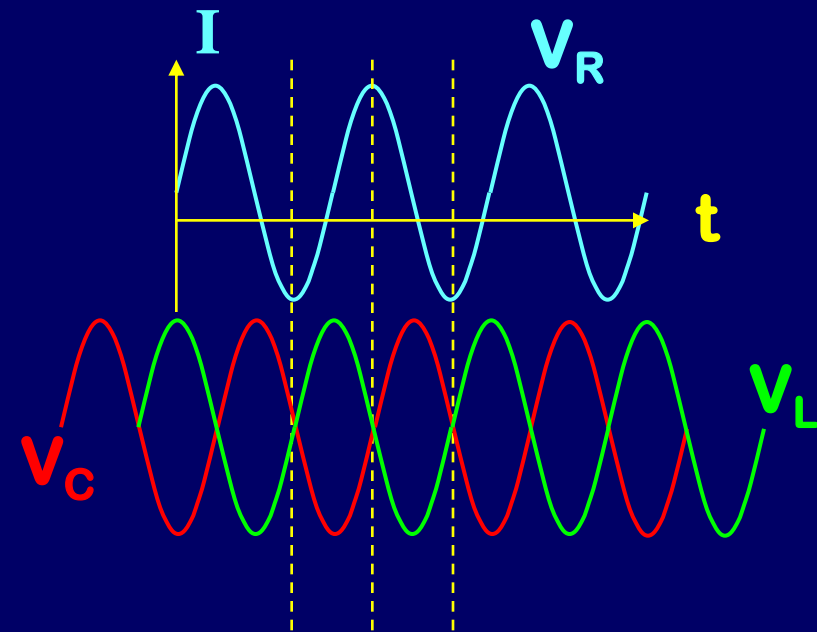


Examples of mechanical resonance

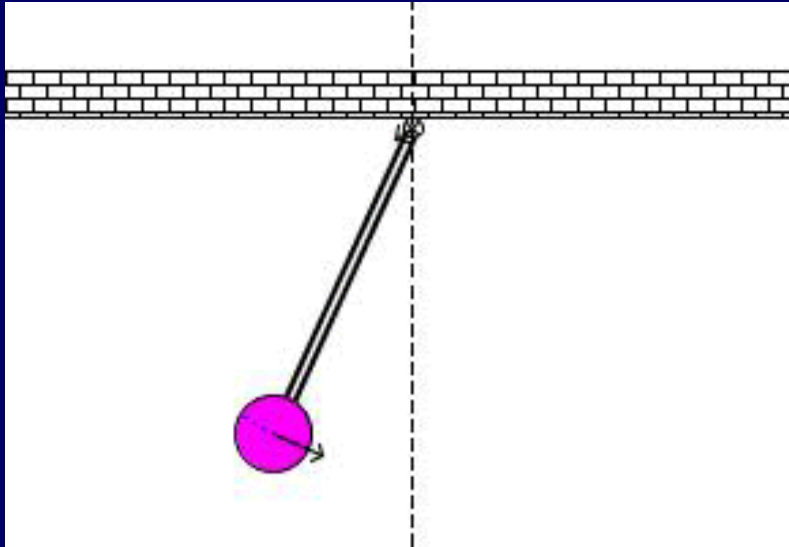

Pendulum:

$$\omega_0 = \sqrt{g/l}$$

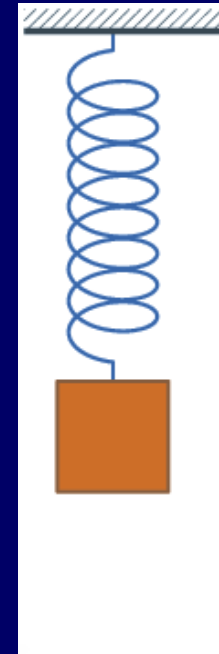

Mass on a spring:

$$\omega_0 = \sqrt{k/m}$$

Common features:

- **Energy converts between two forms (kinetic & potential)**
- **Weak input leads to a big response!**

Resonance!





Tacoma Narrows Bridge




Millennium Bridge


Electric energy

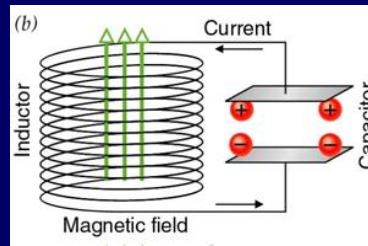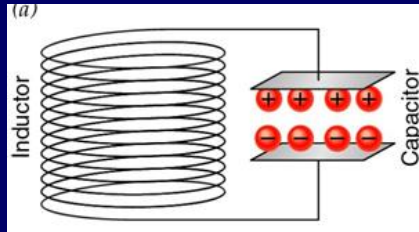


Magnetic energy

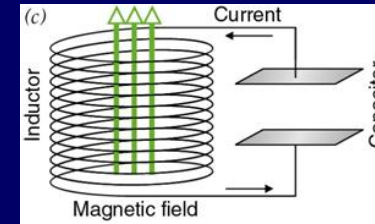


**RLC circuit:
Electrical
resonance**

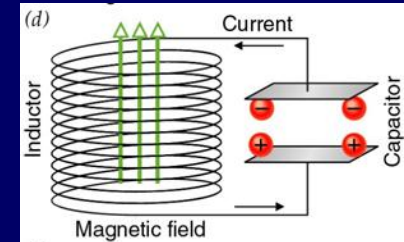

Electric energy

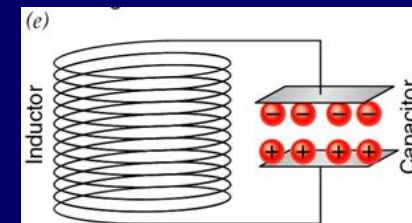

Magnetic energy

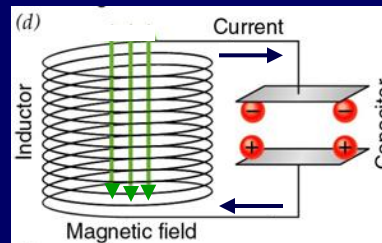



Resonance

R is independent of **f**

X_L increases with **f**

$$X_L = 2\pi fL$$

X_C decreases with **f**


$$X_C = 1/(2\pi fC)$$

Z: **X_L** and **X_C** subtract

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

Resonance: X_L = X_C

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

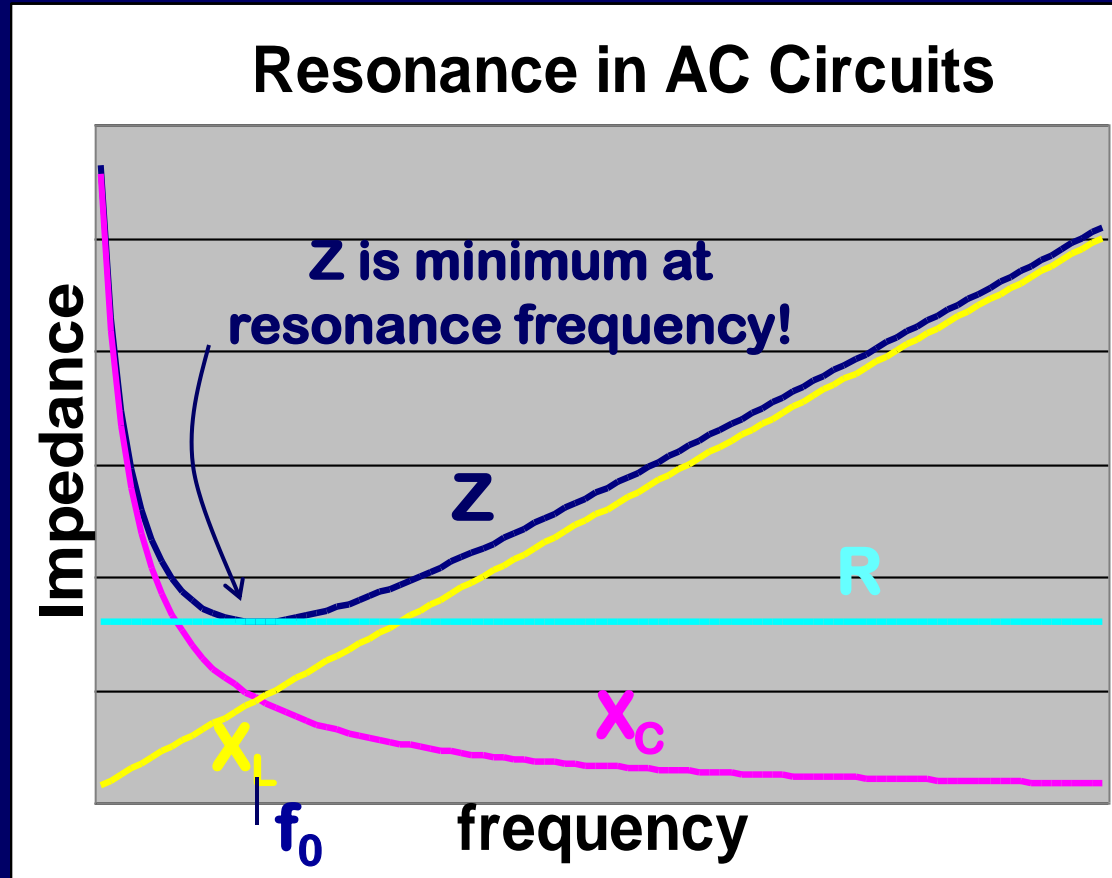



Resonance

R is independent of **f**

X_L increases with **f**

$$X_L = 2\pi fL$$

X_C decreases with **f**


$$X_C = 1/(2\pi fC)$$

Z: **X_L** and **X_C** subtract

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$


Resonance: X_L = X_C

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

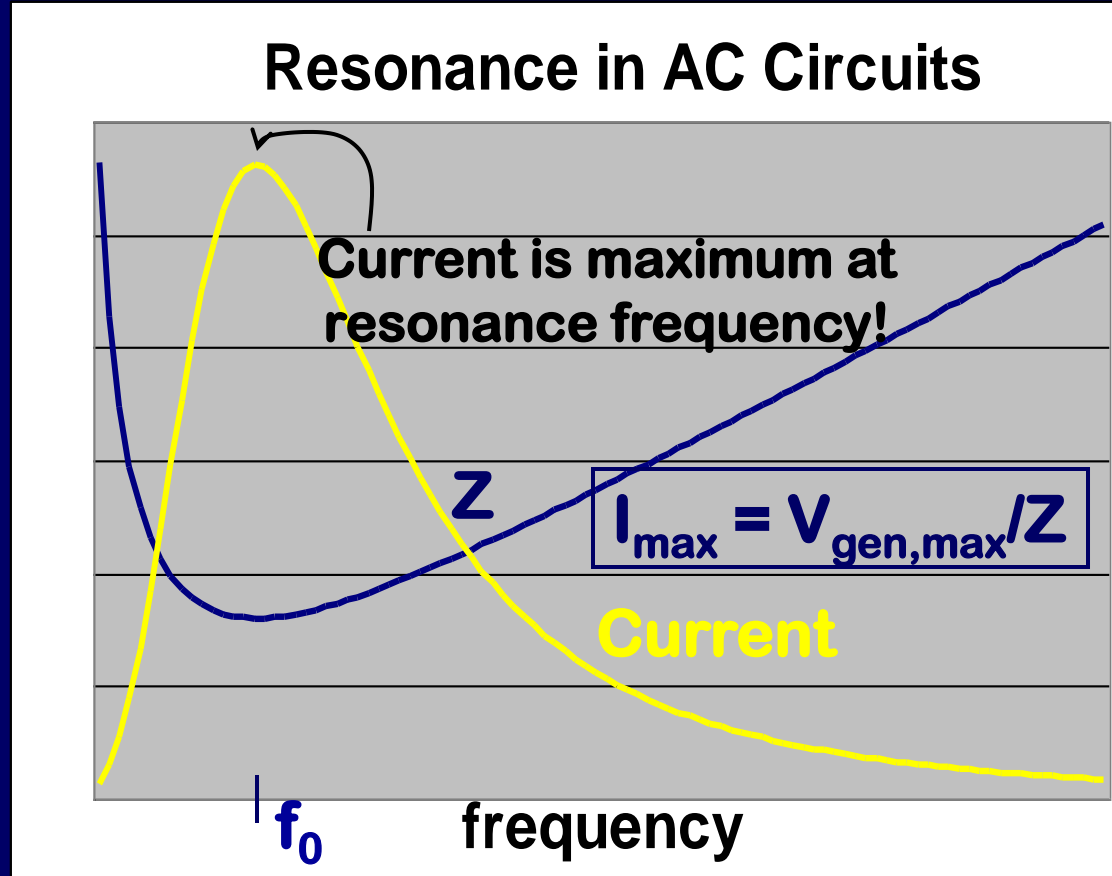



ACT: Resonance

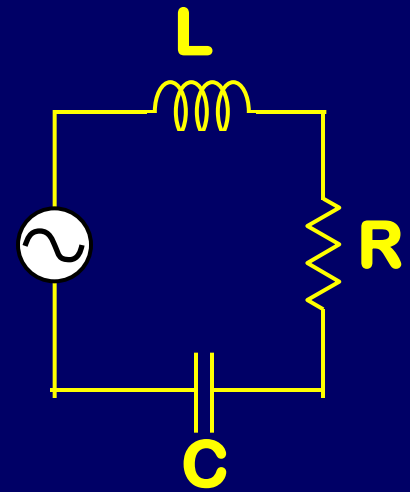


The AC circuit to the right is being driven at its resonance frequency. Compare the maximum voltage across the capacitor with the maximum voltage across the inductor.

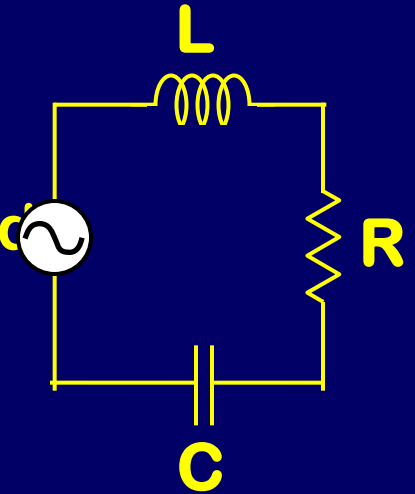- 1) $V_{C,\max} > V_{L,\max}$
- 2) $V_{C,\max} = V_{L,\max}$
- 3) $V_{C,\max} < V_{L,\max}$
- 4) **Depends on R**

CheckPoint 14.1

As the frequency of the circuit is either raised above or lowered below the resonant frequency, the impedance of the circuit:




Always increases

Only increases for lowering the frequency

Only increases for raising the frequency

What is it good for?

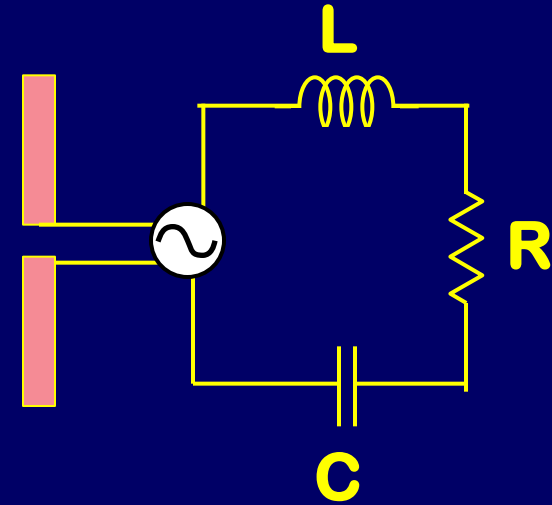


- Current through circuit depends on frequency (maximum at resonance frequency f_0)
 - Radio receiver
 - Stereo equalizer
 - NMR/MRI
 - Picks out radio station freq f_0
 - Picks out music freq f_0
 - Picks out signal from protons at f_0

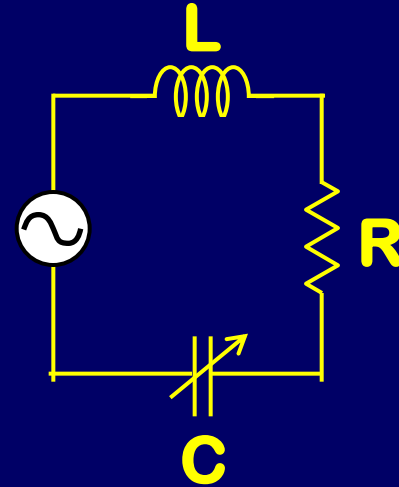Example

Resonance in Radios



An AC circuit with $R = 2 \Omega$, $L = 0.30 \mu\text{H}$ and variable capacitance is connected to an antenna to receive radio signals at the resonance frequency. If you want to listen to music broadcasted at 96.1 MHz, what value of C should be used?



$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

$$C = \quad = \quad = \quad = \quad F$$





ACT: Radios

Your radio is tuned to FM 96.1 MHz and want to change it to FM 105.9 MHz, which of the following will work.

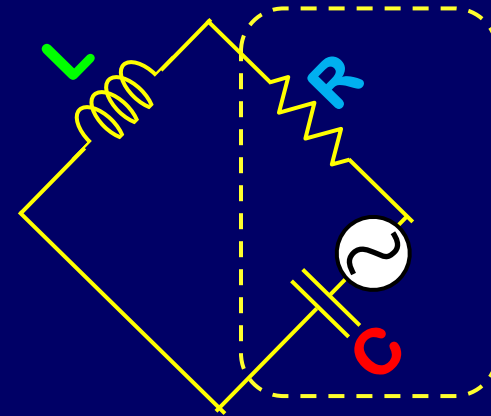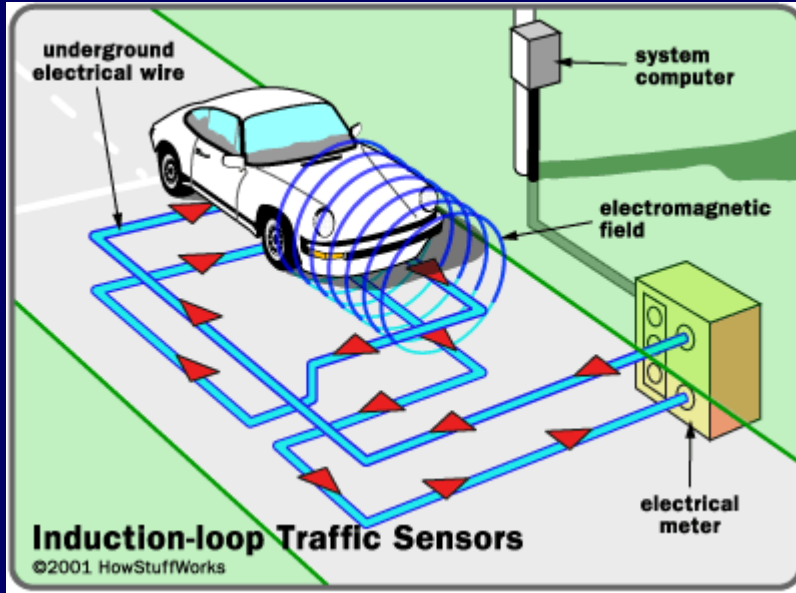1. Increase Capacitance
2. Decrease Capacitance
3. Neither, you need to change R

Another use for RLC circuits: traffic sensors



AC Summary

Resistors: $V_{R,\max} = I_{\max} R$

In phase with I

Capacitors: $V_{C,\max} = I_{\max} X_C$ $X_C = 1/(2\pi f C)$

Lags I

Inductors: $V_{L,\max} = I_{\max} X_L$ $X_L = 2\pi f L$

Leads I

Generator: $V_{\text{gen},\max} = I_{\max} Z$ $Z = \sqrt{R^2 + (X_L - X_C)^2}$

Can lead or lag I

$$\tan(\phi) = (X_L - X_C)/R$$

Power is only dissipated in resistor:

$$\bar{P} = \frac{1}{2} I_{\max} V_{\text{gen},\max} \cos(\phi)$$