






# Phys 102 – Lecture 8


Circuit analysis and Kirchhoff's rules
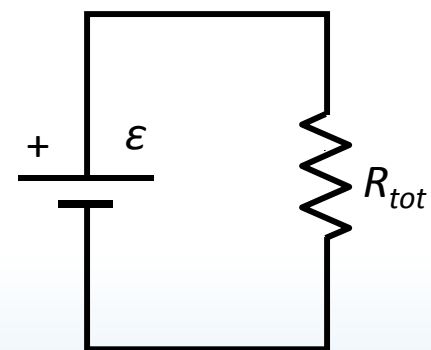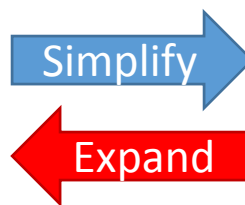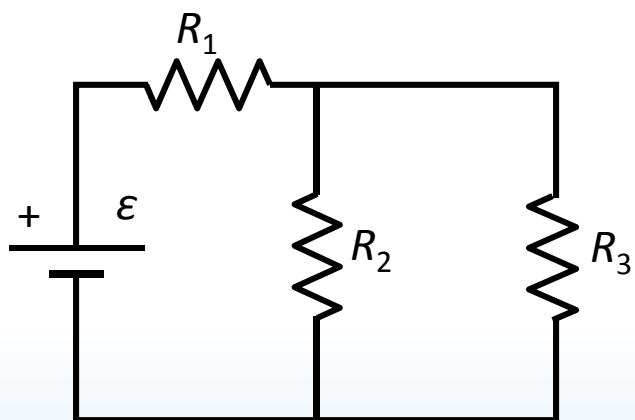
# Recall from last time...

We solved circuits like... by combining series & parallel components




What about a circuit like...

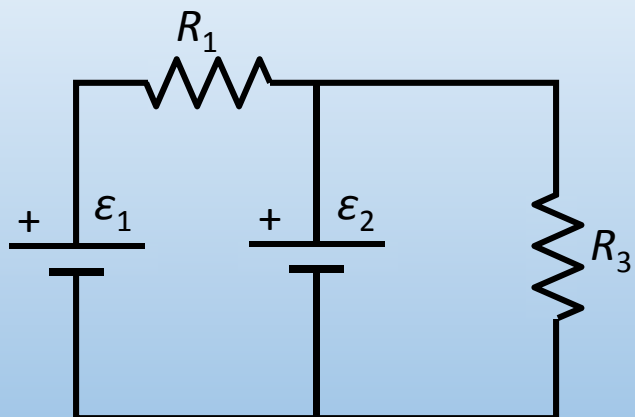


# Kirchhoff's loop rule

Voltages around a loop sum to zero

$$\sum \Delta V = 0$$

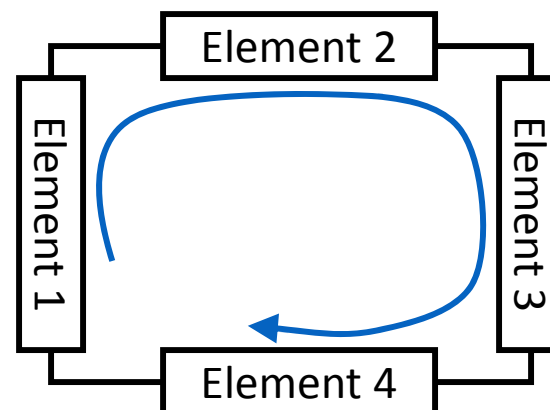


Is voltage positive or negative?

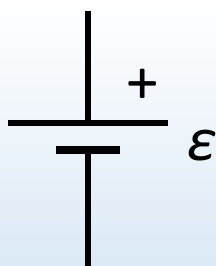

Batteries: + end is always at higher potential



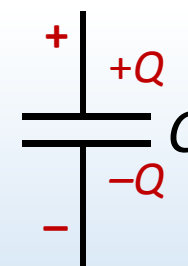Resistors: higher/lower potential depends on current direction




Capacitors: higher/lower potential depends on which plate has +Q/-Q

Label +/- for higher/lower electric potential

Go around loop and write  $+V_{element}$  if electric potential increases  $-V_{element}$  if it decreases

# Calculation: single loop practice

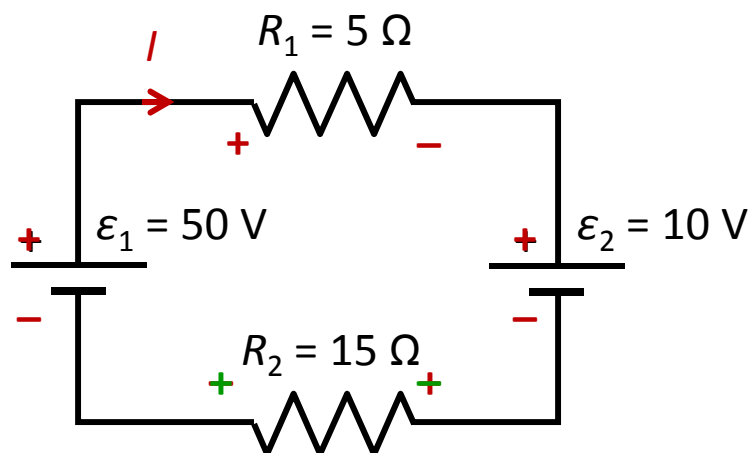

Calculate the current  $I$  in the circuit



What if we go around the loop the “wrong” way?

What if we’re not given the current direction?

What if we pick the “wrong” direction?
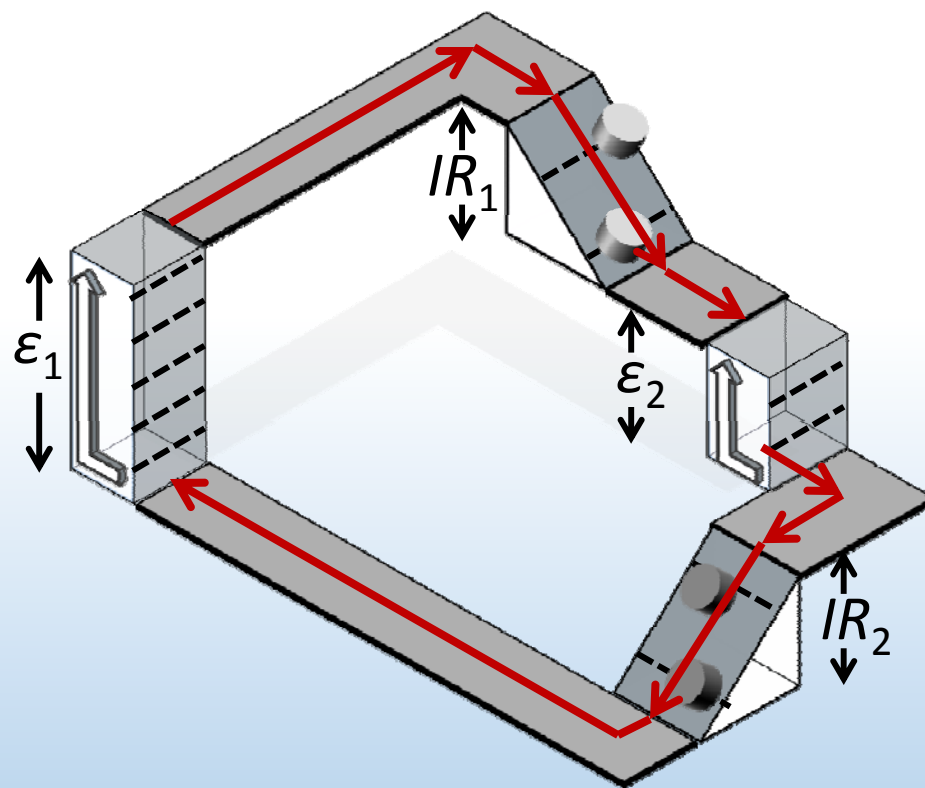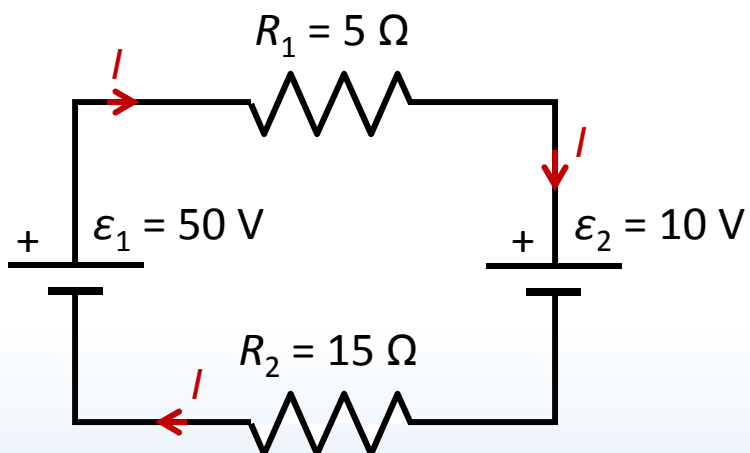
# Calculation: single loop practice

How can the current be driven opposite battery 2?






# ACT: Checkpoint 1.1

Calculate the current through  $R_1$ .

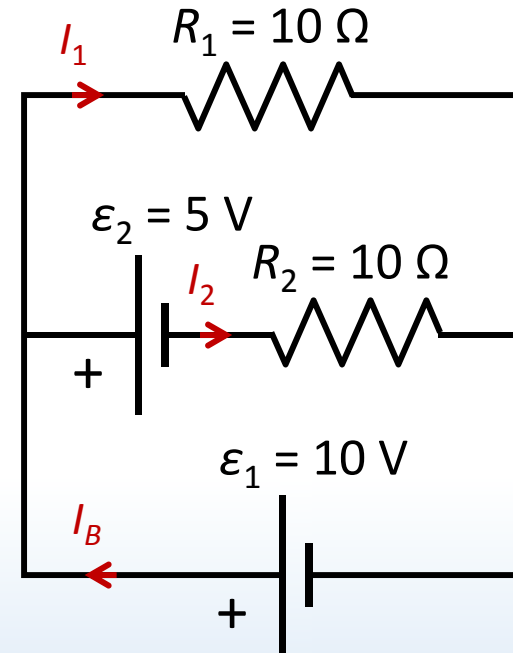- A.  $I_1 = 0.5 \text{ A}$
- B.  $I_1 = 1.0 \text{ A}$
- C.  $I_1 = 1.5 \text{ A}$






## ACT: Checkpoint 1.2



Calculate the current through  $R_2$ .

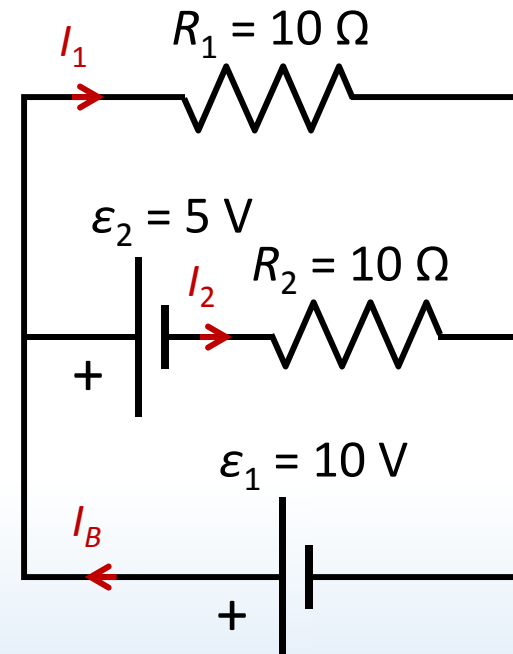- A.  $I_2 = 0.5 \text{ A}$
- B.  $I_2 = 1.0 \text{ A}$
- C.  $I_2 = 1.5 \text{ A}$


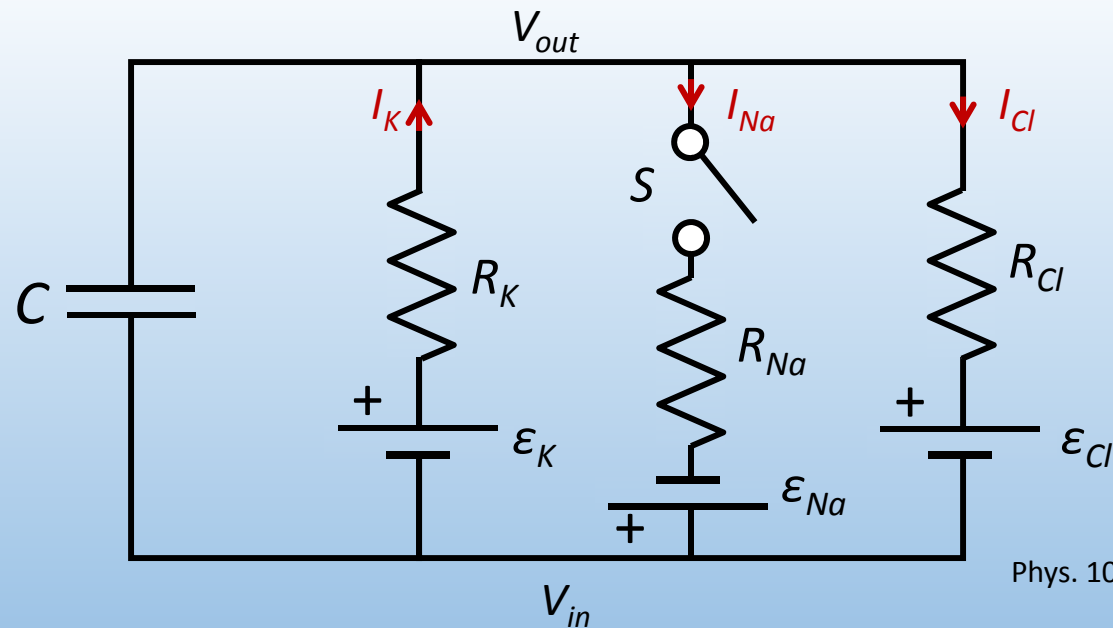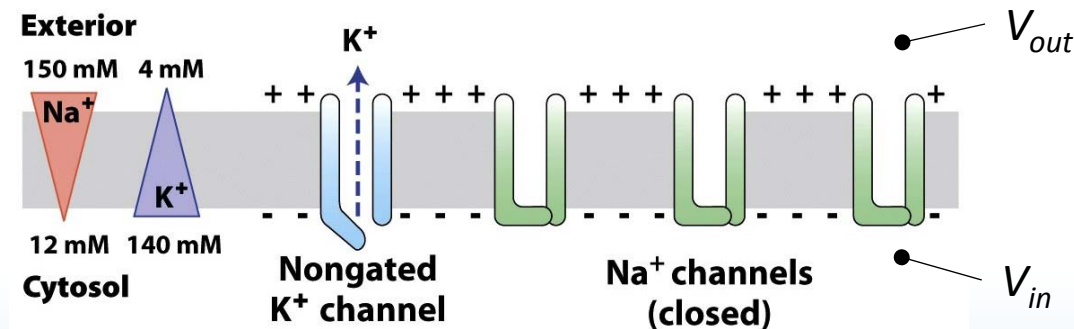
# Nerve cell equivalent circuit

Neurons have different types of ion channels ( $K^+$ ,  $Na^+$ , and  $Cl^-$ ) that pump current into and out of cell – act like batteries!







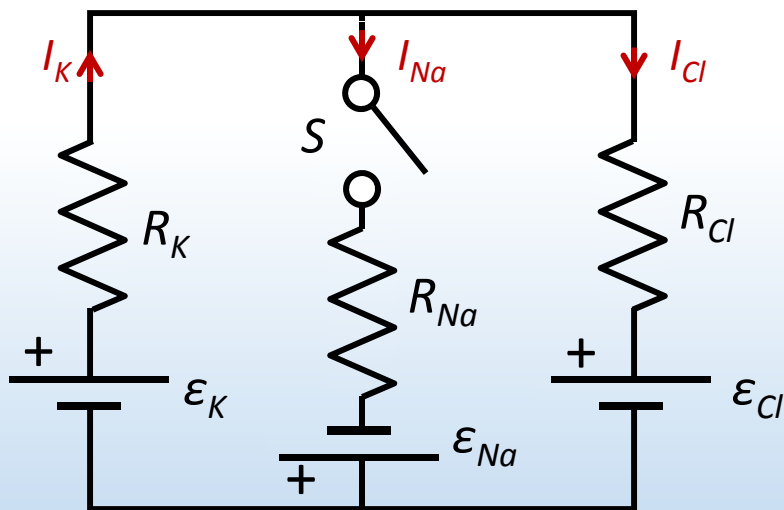
# ACT: loop

Na<sup>+</sup> channels have a “gate” (represented by the switch  $S$ ) that allows or blocks ion flow. In its resting state, a Na<sup>+</sup> channel is shut (i.e. switch  $S$  is open). Which equation is correct?




- A.  $+\epsilon_K - I_K R_K - I_{Cl} R_{Cl} - \epsilon_{Cl} = 0$
- B.  $+\epsilon_K - I_K R_K - I_{Na} R_{Na} - \epsilon_{Na} = 0$
- C.  $+\epsilon_K + I_K R_K - I_{Cl} R_{Cl} - \epsilon_{Cl} = 0$
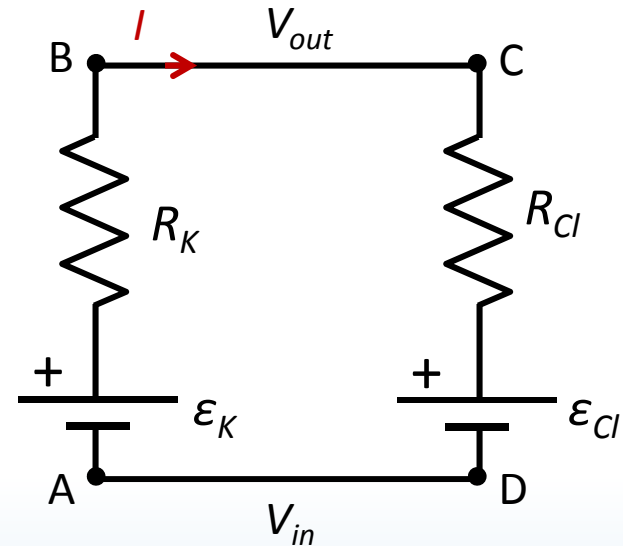
# Calculation: electric potential

Find the electric potential difference across the cell  $V_{in} - V_{out}$   
(Assume  $V_{out} = 0$  for reference)


$$\begin{aligned} \varepsilon_K &= 80 \text{ mV}, \varepsilon_{Na} = 60 \text{ mV}, \varepsilon_{Cl} = 50 \text{ mV} \\ R_K &= 2 \text{ M}\Omega, R_{Na} = 0.2 \text{ M}\Omega, R_{Cl} = 5 \text{ M}\Omega \end{aligned}$$



$$\varepsilon_K - IR_K - IR_{Cl} - \varepsilon_{Cl} = 0$$

$$V_{in} + \varepsilon_K - IR_K = V_{out}$$
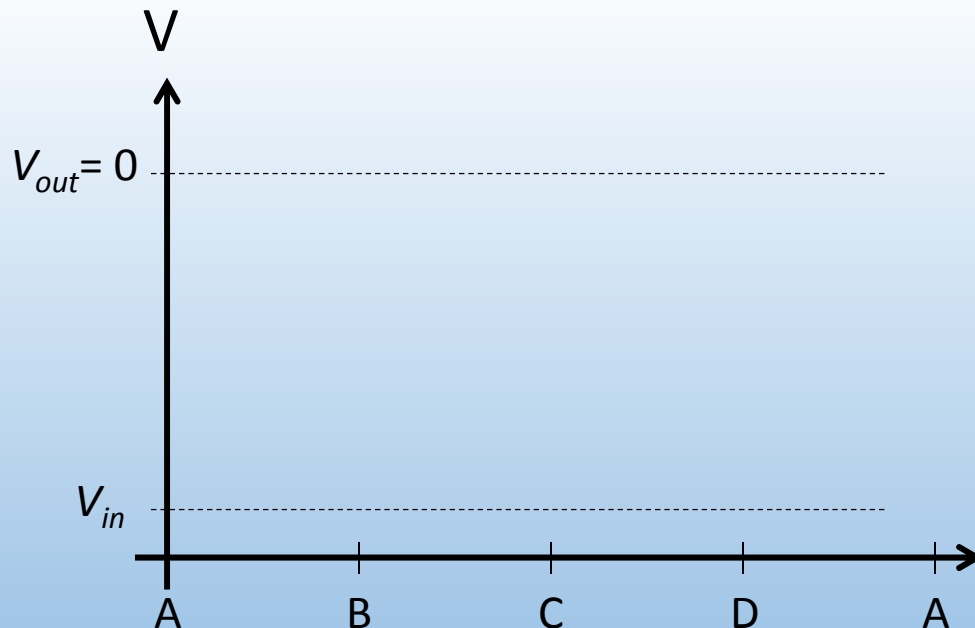
$$\text{or: } V_{out} - IR_{Cl} - \varepsilon_{Cl} = V_{in}$$




# Kirchhoff's junction rule

The sum of currents into a junction equals the sum of currents out of a junction

$$\sum I_{in} = \sum I_{out}$$

Example:

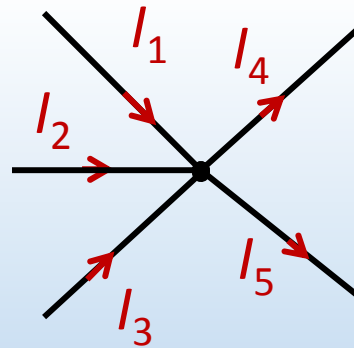


$$I_1 + I_2 + I_3 = I_4 + I_5$$



## ACT: Checkpoint 1.3


Calculate the current through the battery  $I_B$ .

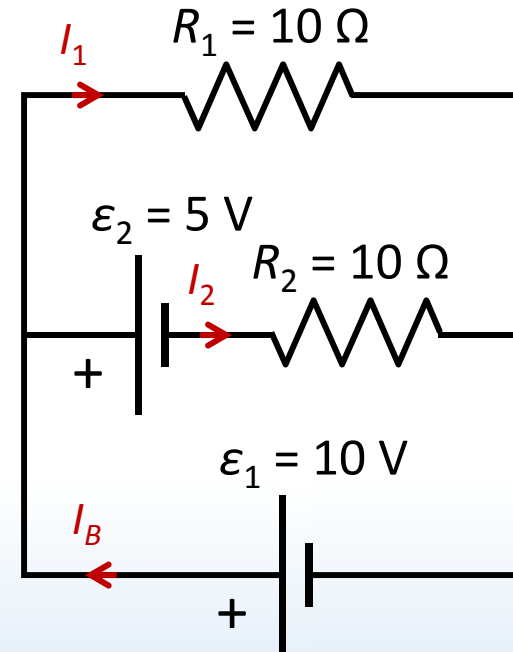- A.  $I_B = 0.5 \text{ A}$
- B.  $I_B = 1.0 \text{ A}$
- C.  $I_B = 1.5 \text{ A}$


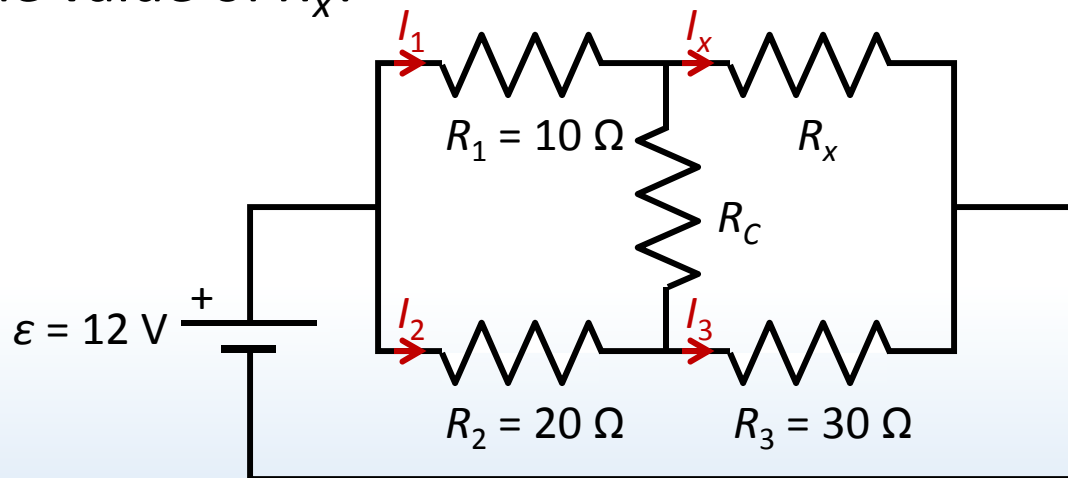
# Calculation: Kirchhoff's laws

In the circuit, the current through  $R_C$  is 0. What is the current through  $R_3$  and the value of  $R_x$ ?





From EX1 FA13

No current flows through  $R_C$  so  $I_2 = I_3$  and  $I_1 = I_x$

No current flows through  $R_C$  so  $V_C = 0$
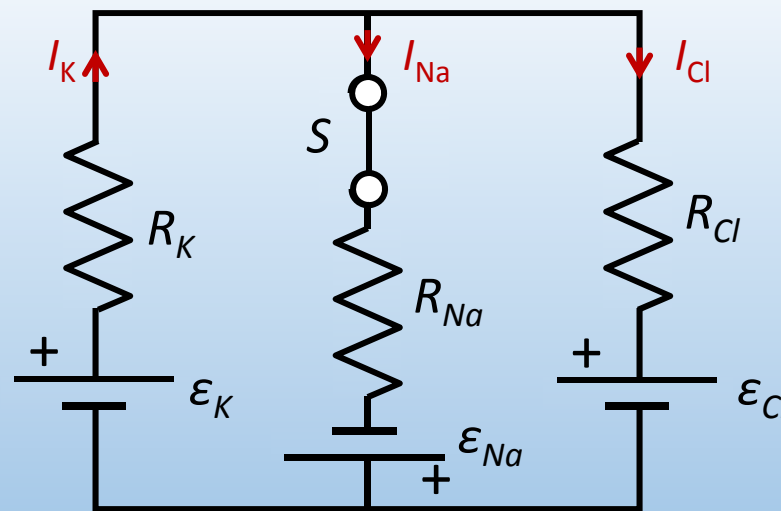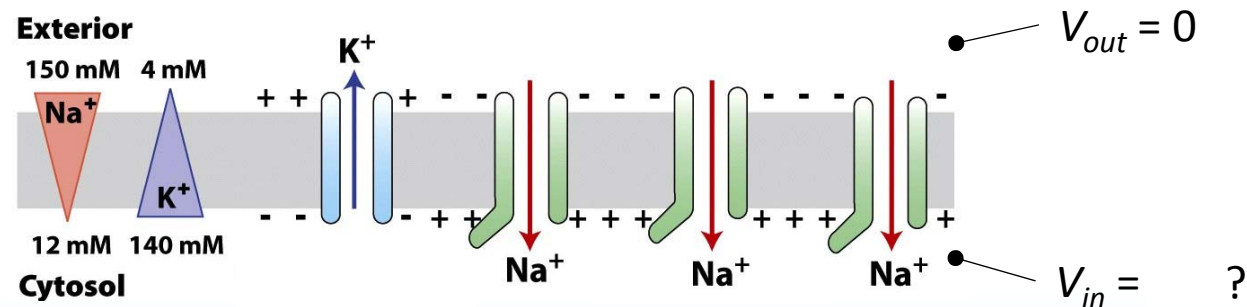
# Nerve cell equivalent circuit

During nerve impulse,  $\text{Na}^+$  channels open (i.e. switch  $S$  closes) and allow  $\text{Na}^+$  to enter the cell




What happens to the currents through the channels and the potential in the cell?
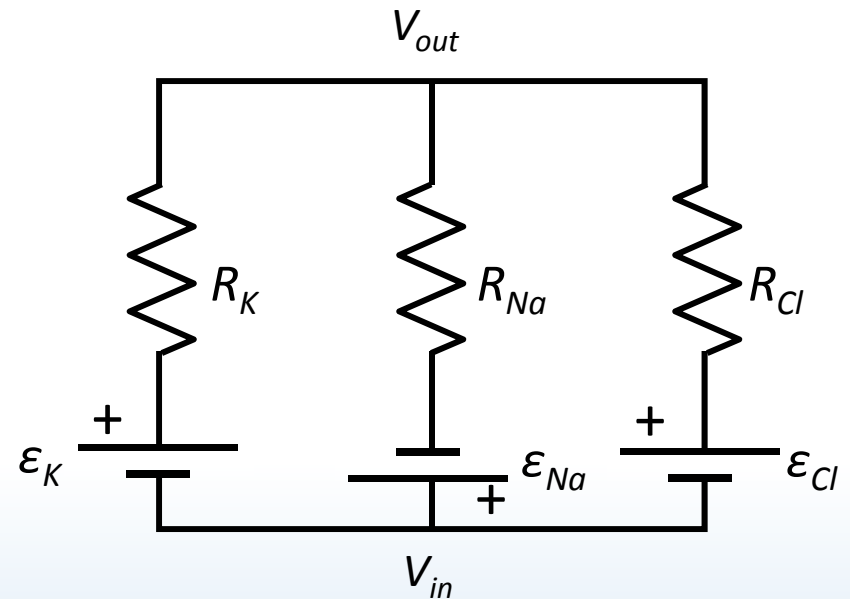
# Calculation: two loop circuit

Given the circuit to the right,  
find  $I_K$ ,  $I_{Na}$  and  $I_{Cl}$  and  $V_{in} - V_{out}$ .

$$\begin{aligned}\epsilon_K &= 80 \text{ mV}, \epsilon_{Na} = 60 \text{ mV}, \epsilon_{Cl} = 50 \text{ mV} \\ R_K &= 2 \text{ M}\Omega, R_{Na} = 0.2 \text{ M}\Omega, R_{Cl} = 5 \text{ M}\Omega\end{aligned}$$




1. Label all currents
2. Label +/– for all elements
3. Choose loop and direction
4. Write down voltage differences


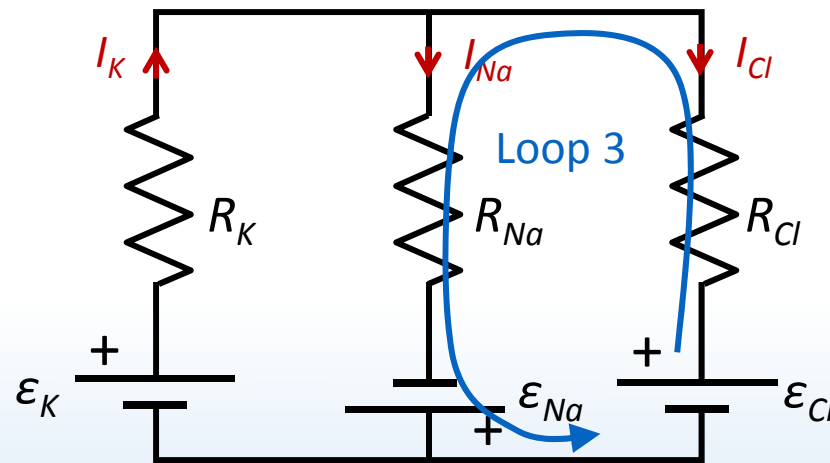
# ACT: Kirchhoff loop rule

What is the correct expression for “Loop 3” in the circuit below?



A.  $+\varepsilon_{Cl} - I_{Cl}R_{Cl} - I_{Na}R_{Na} + \varepsilon_{Na} = 0$

B.  $+\varepsilon_{Cl} - I_{Cl}R_{Cl} + I_{Na}R_{Na} + \varepsilon_{Na} = 0$

C.  $+\varepsilon_{Cl} + I_{Cl}R_{Cl} - I_{Na}R_{Na} + \varepsilon_{Na} = 0$



# Calculation: two loop circuit

Given the circuit to the right,  
find  $I_K$ ,  $I_{Na}$  and  $I_{Cl}$  and  $V_{in} - V_{out}$ .

$$\begin{aligned}\epsilon_K &= 80 \text{ mV}, \epsilon_{Na} = 60 \text{ mV}, \epsilon_{Cl} = 50 \text{ mV} \\ R_K &= 2 \text{ M}\Omega, R_{Na} = 0.2 \text{ M}\Omega, R_{Cl} = 5 \text{ M}\Omega\end{aligned}$$


We have 3 unknowns, need 3 equations

Loop 1:

Loop 2:

Loop 3:


5. Write down junction rule

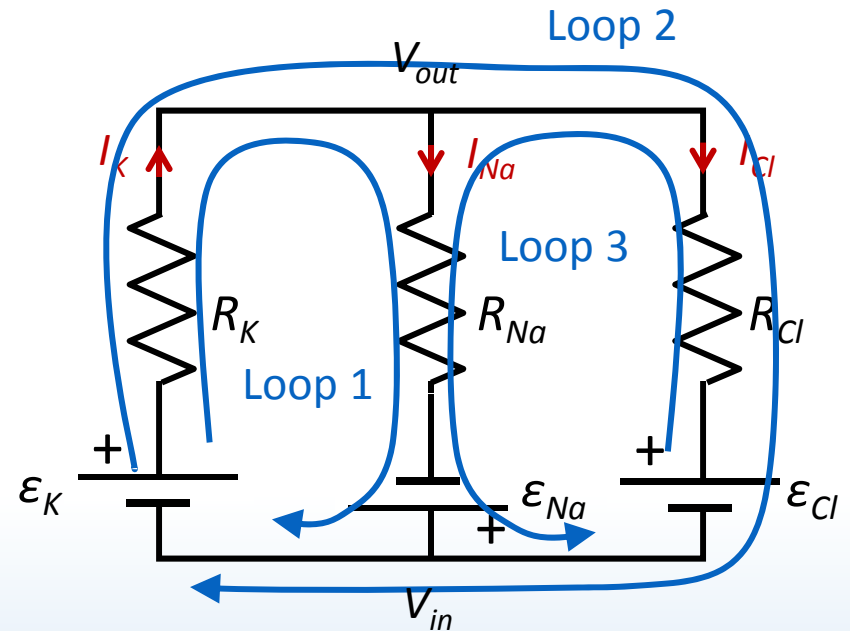


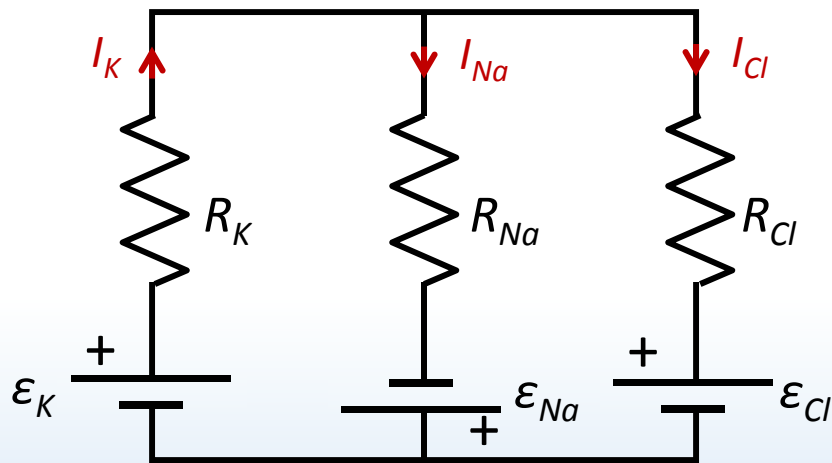
# ACT: Kirchhoff junction rule

What is the correct expression for junction in the circuit?




- A.  $I_K + I_{Na} = I_{Cl}$
- B.  $I_{Na} + I_{Cl} = I_K$
- C.  $I_{Cl} + I_K = I_{Na}$

# Calculation: two loop circuit

Given the circuit to the right,  
find  $I_K$ ,  $I_{Na}$  and  $I_{Cl}$  and  $V_{in} - V_{out}$ .

$$\begin{aligned}\varepsilon_K &= 80 \text{ mV}, \varepsilon_{Na} = 60 \text{ mV}, \varepsilon_{Cl} = 50 \text{ mV} \\ R_K &= 2 \text{ M}\Omega, R_{Na} = 0.2 \text{ M}\Omega, R_{Cl} = 5 \text{ M}\Omega\end{aligned}$$

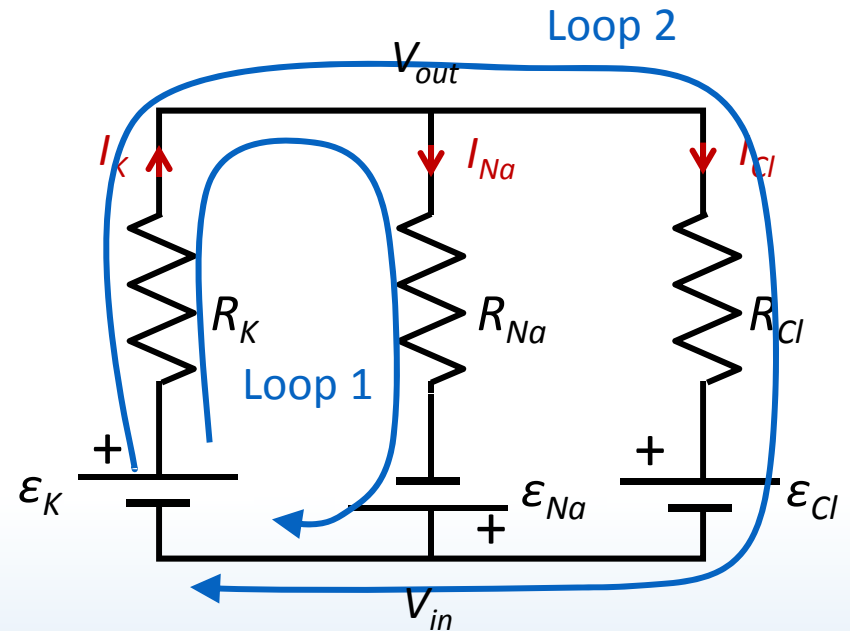3 equations, 3 unknowns,  
the rest is algebra!



$$\begin{aligned}(1) \quad +\varepsilon_K - I_K R_K - I_{Na} R_{Na} + \varepsilon_{Na} &= 0 & +80 - 2I_K - 0.2I_{Na} + 60 &= 0 \\ (2) \quad +\varepsilon_K - I_K R_K - I_{Cl} R_{Cl} - \varepsilon_{Cl} &= 0 & +80 - 2I_K - 5I_{Cl} - 50 &= 0 \\ (3) \quad I_{Na} + I_{Cl} &= I_K & +80 - 2I_K - 5(I_K - I_{Na}) - 50 &= 0\end{aligned}$$

Substitute Eq. (3) into Eq. (2) and rearrange

$$(2') \quad +30 - 7I_K + 5I_{Na} = 0$$

# Calculation: two loop circuits

Now 2 equations (1 and 2'), 2 unknowns ( $I_K$  and  $I_{Na}$ )

$$(1) \quad +70 - I_K - 0.1I_{Na} = 0$$

$$I_K = 70 - 0.1I_{Na}$$

$$(2') \quad +30 - 7I_K + 5I_{Na} = 0$$

$$+30 - 7(70 - 0.1I_{Na}) + 5I_{Na} = 0$$

Substitute  $I_K$  in Eq. (1) into Eq. (2') and rearrange

$$-460 + 5.7I_{Na} = 0 \quad I_{Na} = \frac{460 \text{ mV}}{5.7 \text{ M}\Omega} = 81 \text{ nA}$$

Plug solution into Eq. (2') to get  $I_K$

$$+30 - 7I_K + 5 \cdot 81 = 0 \quad I_K = \frac{435 \text{ mV}}{7 \text{ M}\Omega} = 62 \text{ nA}$$


Use junction Eq. (3) to get  $I_{Cl}$

$$I_{Cl} = 62 - 81 = -19 \text{ nA}$$


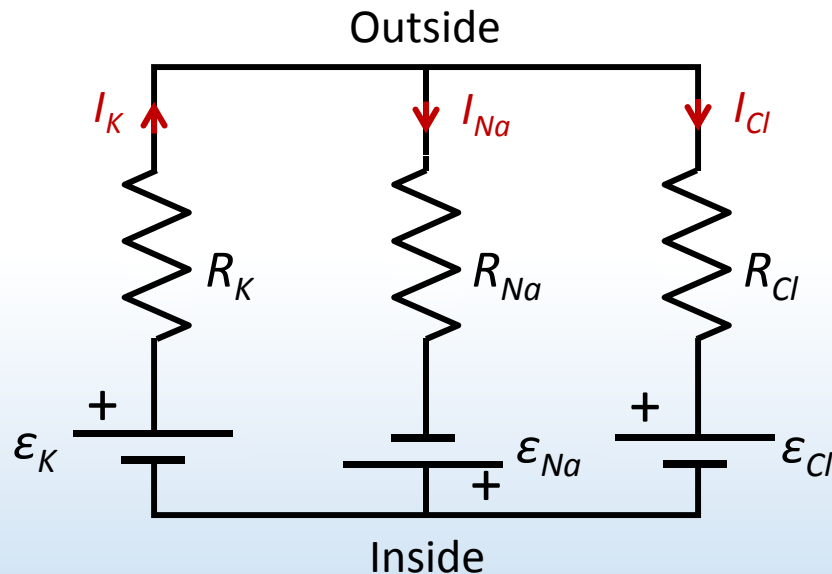
# ACT: Kirchhoff junction rule



We found that  $I_K = 62 \text{ nA}$ ,  $I_{Na} = 81 \text{ nA}$  and  $I_{Cl} = -19 \text{ nA}$ . Which of the following statements is FALSE?



- A.  $I_K$  is out of the cell
- B.  $I_{Na}$  is into the cell
- C.  $I_{Cl}$  is into the cell

# Calculation: two loop circuit

Find the new  $V_{in} - V_{out}$ :

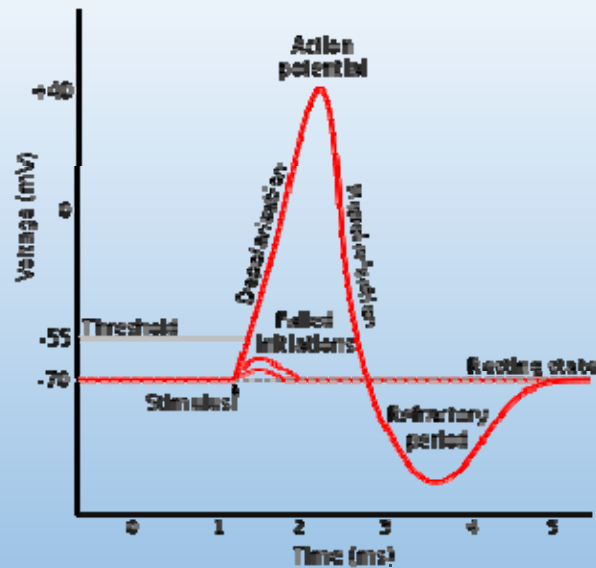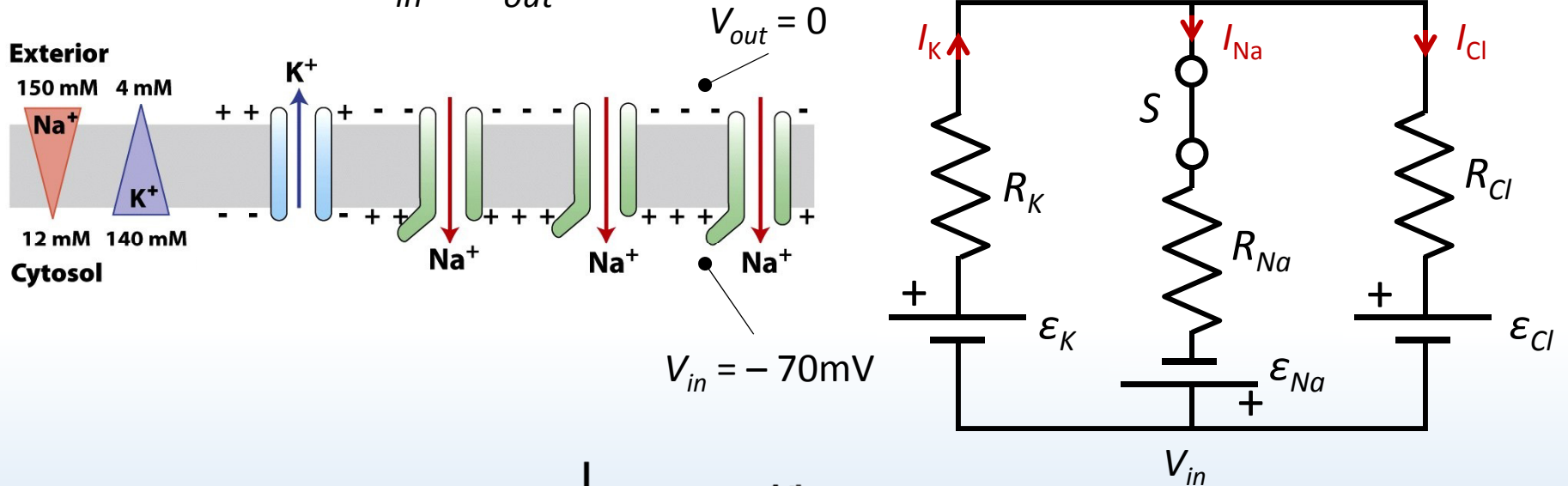

# *Summary of today's lecture*

- Two basic principles:

- Kirchhoff loop rule

Voltages around circuit loop sum to zero (based on conservation of energy)

$$\sum \Delta V = 0$$

- Kirchhoff junction rule

Currents into a circuit branch equal currents out (based on conservation of charge)

$$\sum I_{in} = \sum I_{out}$$

# *Summary of today's lecture*

- Basic approach to solving complex circuits:
  1. Label all currents
  2. Label +/– for all elements
  3. Choose loop(s) and direction(s)
  4. Write down voltage differences
  5. Write down junction ruleThe rest is algebra!