

Physics 212

Lecture 11

Today's Concept:

RC Circuits

Your Comments

The moment I saw Kirchhoff's Rule for charging a capacitor and a resistor was a first order forced differential equation, I got really excited.

I just pretty much failed my test and it is my major after doing good on the quizzes and homework and then you throw this at me and I don' know what is happening. I can kiss my A good bye.

Holly Hell!!! First, please go over EVERYTHING TOMOROW!!! Secondly, why is the university letting us take this course without having done intro to differential equations yet!!!

So let's strip these equations down to more intuitive forms.


Hi Mom!

Hi professor stelzer, could we please have a grade estimator so i can calculate my grade in this class. I didn't do too well on exam 1 and i am freaking out.

I know that a lot of times in prelecture there are extra things told to us to help us get a better understanding (which is very good) but in this prelecture, I couldn't really tell what all we actually had to be responsible for exactly.

This lecture was pretty straight forward. Hopefully we won't have to memorize these equations because they're all complicated and they all look pretty similar. Also, the two batteries and 6 resistors question from the last homework was pretty ridiculous.

Hour Exam 1 Results

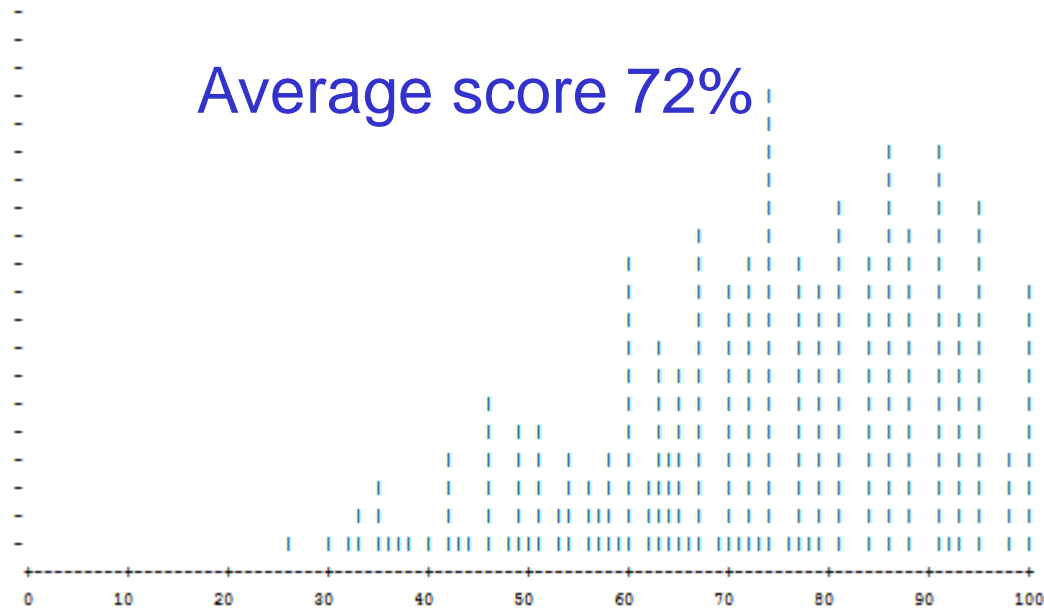

Check under course description for grading policy

(e.g. if you got a 60% on this exam, then you missed 40/1000 course points. That does not mean you will get a D in the course! But, that you should have a strategy to do better on the remaining exams.)

The 212 Differential Equations

We describe the world (electrical circuits, problems in heat transfer, control systems, financial markets, etc.) using differential equations

You only need to know the solutions of two basic differential equations

$$\frac{dq}{dt} + \frac{1}{\tau} q = 0 \quad q = q_{const} e^{-t/\tau}$$

$$\frac{d^2 q}{dt^2} + \omega^2 q = 0 \quad q = q_{const} \sin(\omega t + \phi)$$

Capacitors in RC Circuits

Solve by applying Kirchhoff's Rules to circuit.

Need to understand some key phrases.

IMMEDIATELY After === Charge on capacitor is same as immediately before

After a LONG TIME === Current through capacitor = 0


After xx seconds === Exponentially more difficult!

RC Circuit (Charging)

Capacitor uncharged, Switch is moved to position “a”

Kirchoff's Voltage Rule

$$-V_{battery} + \frac{q}{C} + IR = 0$$

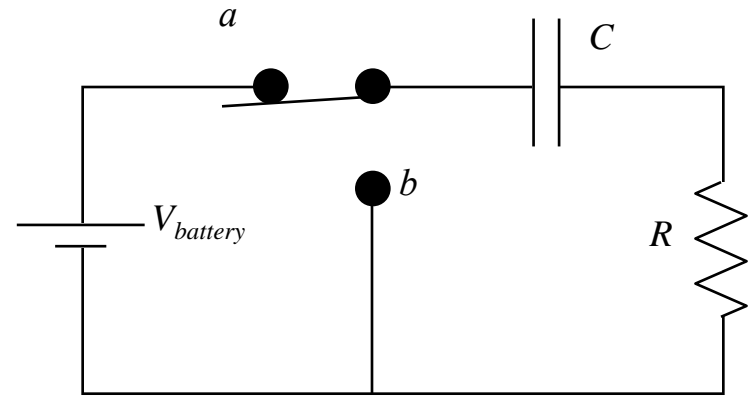

Short Term ($q = q_0 = 0$)

$$-V_{battery} + 0 + I_0 R = 0$$

$$I_0 = \frac{V_{battery}}{R}$$

Long Term ($I_c = 0$)

$$-V_{battery} + \frac{q_\infty}{C} + 0 \cdot R = 0$$



$$q_\infty = CV_{battery}$$

Intermediate

$$-V_{battery} + \frac{q}{C} + \frac{dq}{dt} R = 0$$

$$q(t) = q_\infty (1 - e^{-t/RC})$$


$$I(t) = \frac{dq}{dt} = I_0 e^{-t/RC}$$

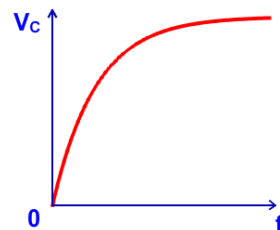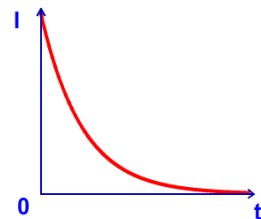

Checkpoint 1



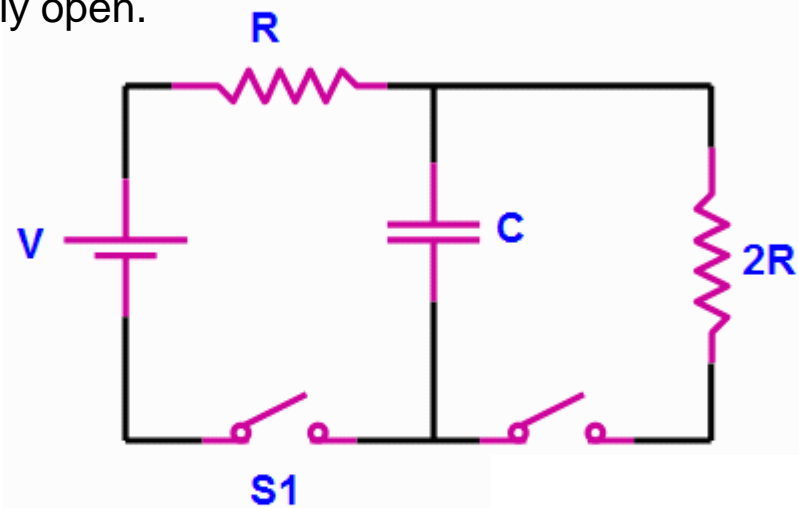A circuit is wired up as shown below. The capacitor is initially uncharged and switches S_1 and S_2 are initially open.



Close S_1 ,

V_1 = voltage across C immediately after

V_2 = voltage across C a long time after

Immediately after the
switch S_1 is closed:

A) $V_1 = V$ $V_2 = V$

B) $V_1 = 0$ $V_2 = V$





C) $V_1 = 0$ $V_2 = 0$

D) $V_1 = V$ $V_2 = 0$

After the switch S_1 has been
closed for a long time

Q is same as immediately before


$$I_C = 0$$

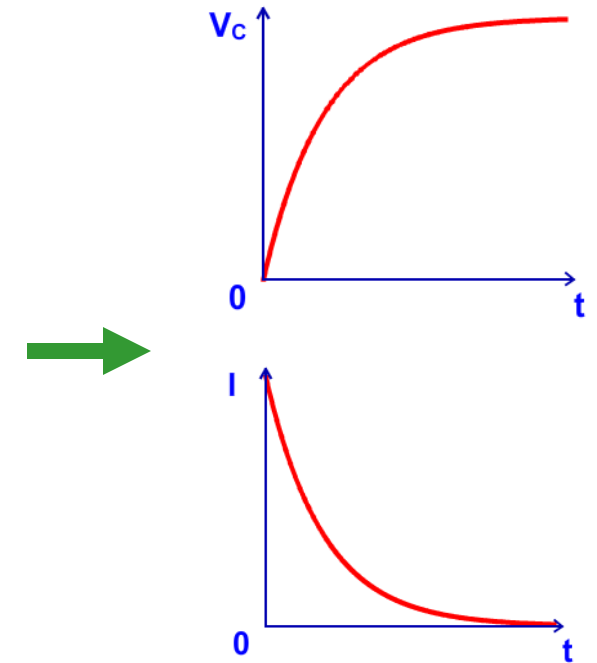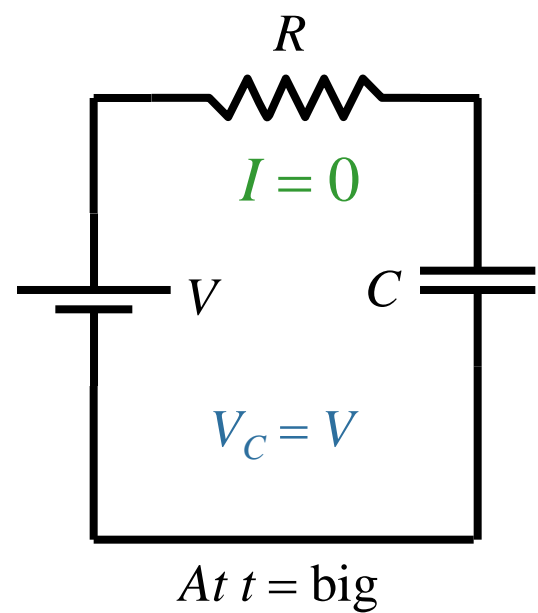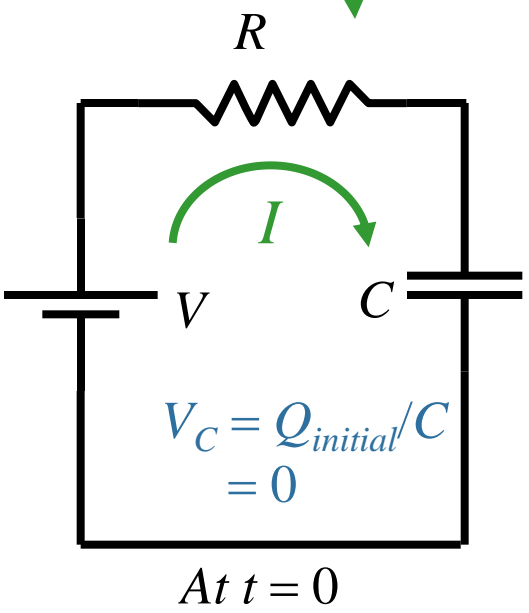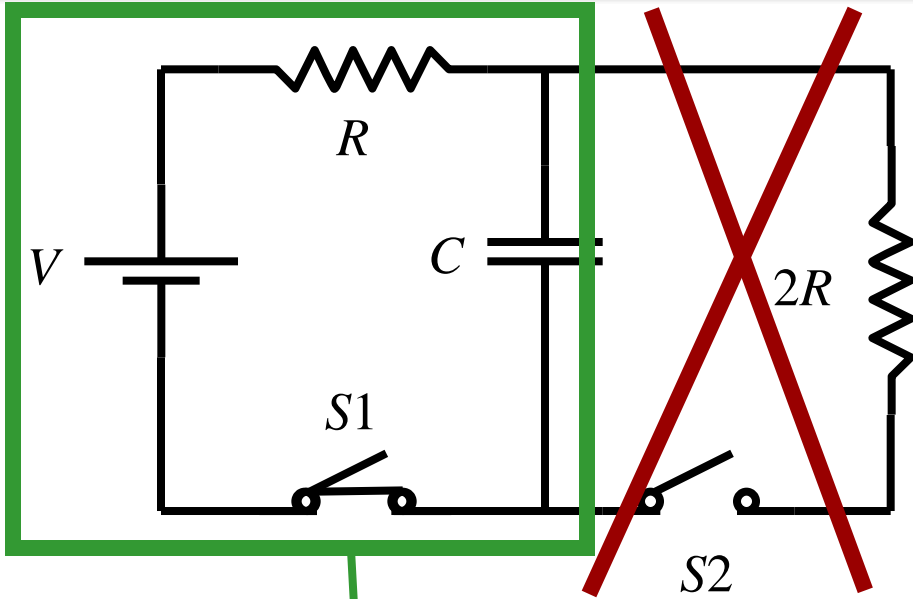

Checkpoint 1



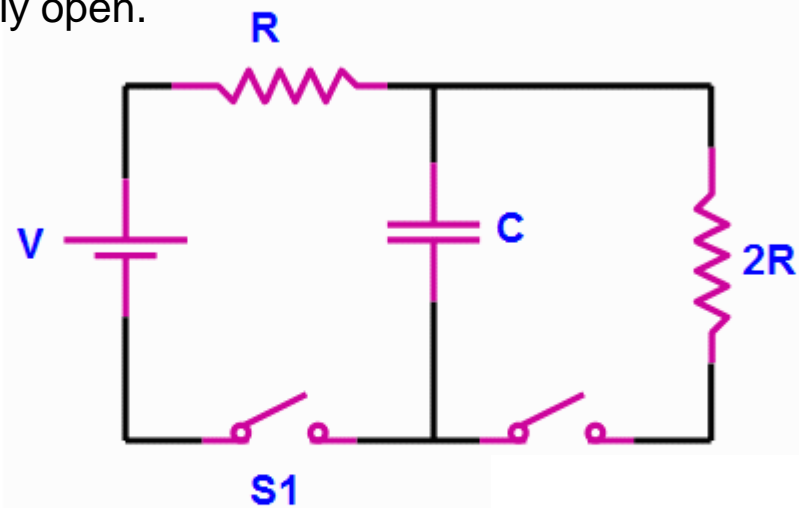A circuit is wired up as shown below. The capacitor is initially uncharged and switches S_1 and S_2 are initially open.



Close S_1 ,

V_1 = voltage across C immediately after

V_2 = voltage across C a long time after

Immediately after the
switch S_1 is closed:

Q is same as immediately before

A) $V_1 = V$ $V_2 = V$

B) $V_1 = 0$ $V_2 = V$

C) $V_1 = 0$ $V_2 = 0$

D) $V_1 = V$ $V_2 = 0$

After the switch S_1 has been
closed for a long time

$$I_C = 0$$

RC Circuit (Discharging)

Capacitor has $q_0 = CV_{battery}$, Switch is moved to position

Kirchoff's Voltage Rule

$$+\frac{q}{C} + IR = 0$$

Short Term ($q = q_0$)


$$V_{battery} + IR = 0$$

$$I_0 = \frac{-V_{battery}}{R}$$

Long Term ($I_c = 0$)

$$\frac{q_\infty}{C} + 0 \cdot R = 0$$

$$q_\infty = 0$$


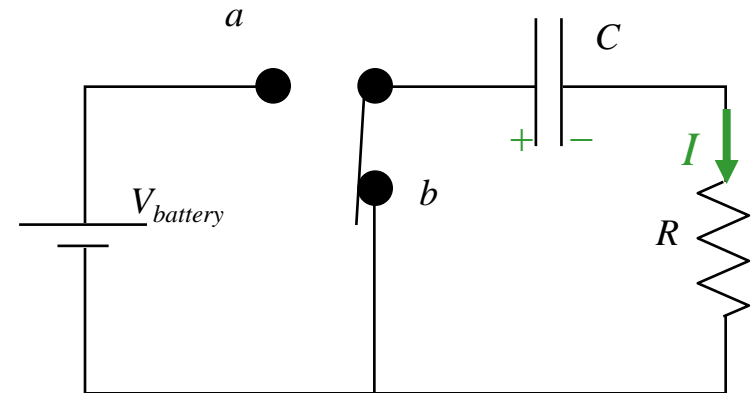


Intermediate

$$+\frac{q}{C} + \frac{dq}{dt} R = 0$$

$$q(t) = q_0 e^{-t/RC}$$


$$I(t) = I_0 e^{-t/RC}$$

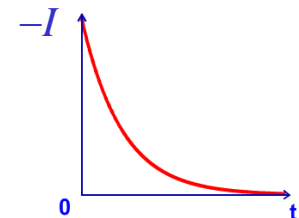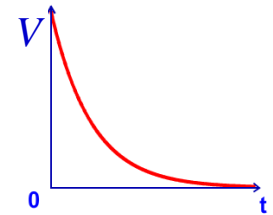

CheckPoint 1c






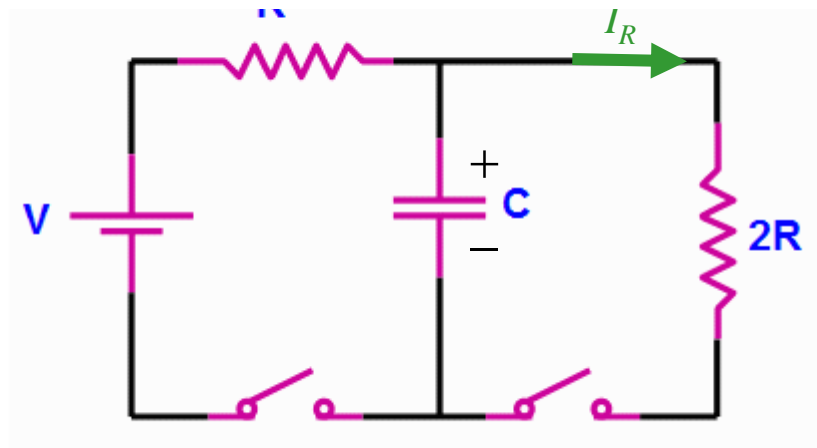A circuit is wired up as shown below. The capacitor is initially uncharged and switches S1 and S2 are initially open.




After being closed a long time, switch 1 is opened and switch 2 is closed. What is the current through the right resistor immediately after switch 2 is closed?

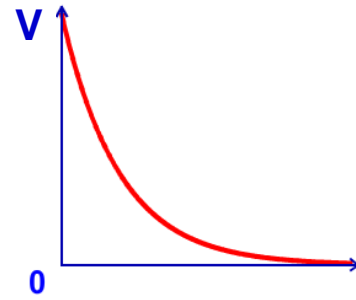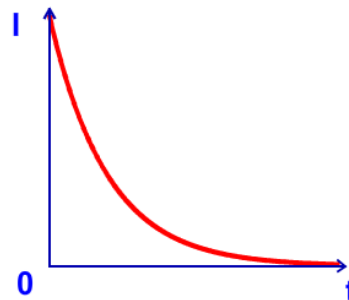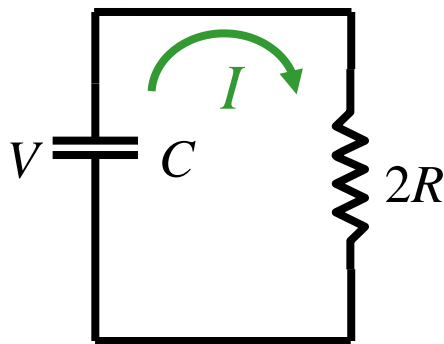
- A.** $I_R = 0$
 B. $I_R = V/3R$
 C. $I_R = V/2R$
 D. $I_R = V/R$



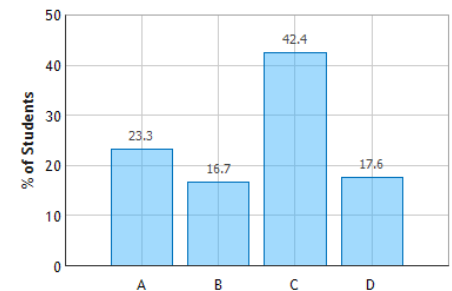Two Loop RC Circuit: Question 5 (N = 825)



CheckPoint 1 d

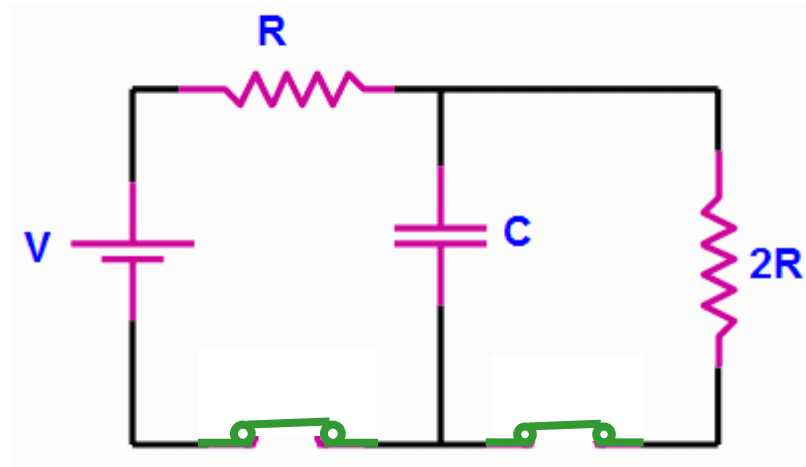

Now suppose both switches are closed. What is the voltage across the capacitor after a very long time?

A. $V_C = 0$


B. $V_C = V$

C. $V_C = 2V/3$


A) The capacitor would discharge completely as t approaches infinity

B) The capacitor will become fully charged after a long time.

C) Current through capacitor is zero

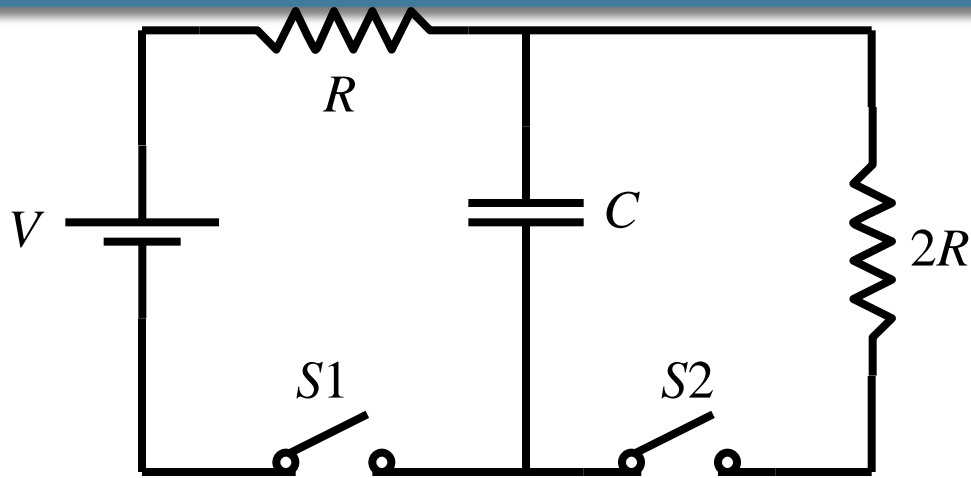

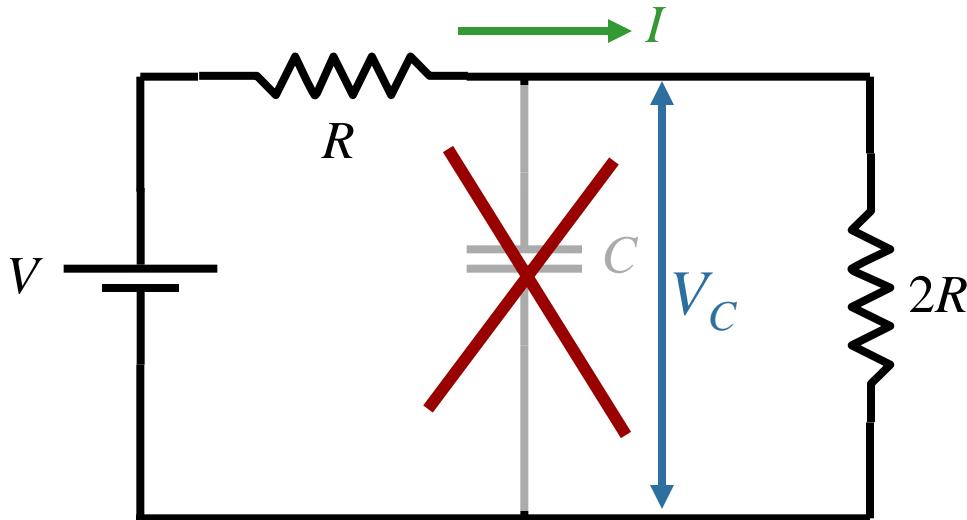Close both $S1$ and $S2$ and wait a long time...




No current flows through the capacitor after a long time. **This will always be the case in any static circuit!!**

$$\begin{aligned} \text{Outer Loop} \\ IR + 2IR - V &= 0 \\ I &= V/(3R) \end{aligned}$$

$$\begin{aligned} \text{Right Loop} \\ +V_C - 2IR &= 0 \\ V_C &= 2IR \end{aligned}$$

→ $V_C = (2/3)V$

CheckPoint 1 d

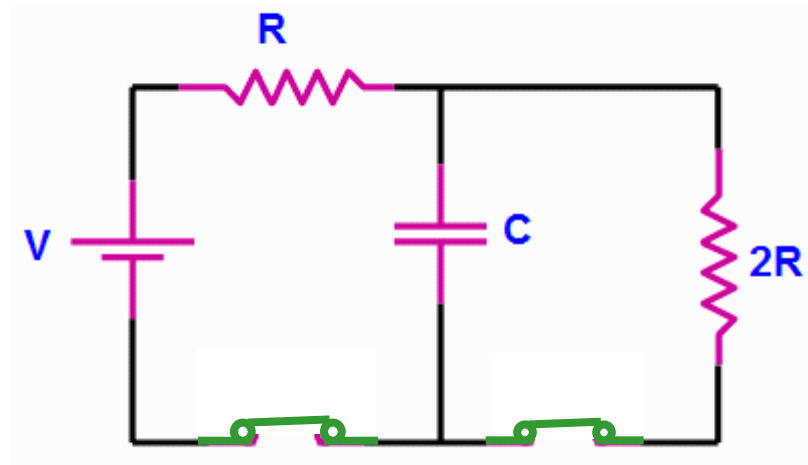

Now suppose both switches are closed. What is the voltage across the capacitor after a very long time?

A. $V_C = 0$

B. $V_C = V$


C. $V_C = 2V/3$

a) The capacitor would discharge completely as t approaches infinity


b) The capacitor will become fully charged after a long time.

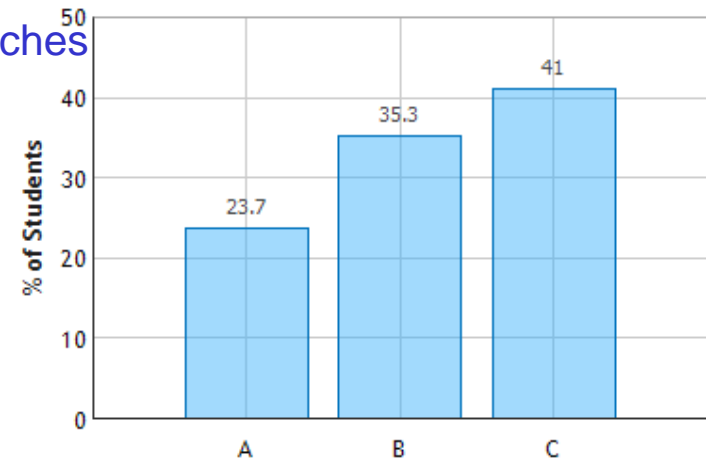c) Current through capacitor is zero

Two Loop RC Circuit: Question 7 (N = 824)



DEMO - Clicker Question 1

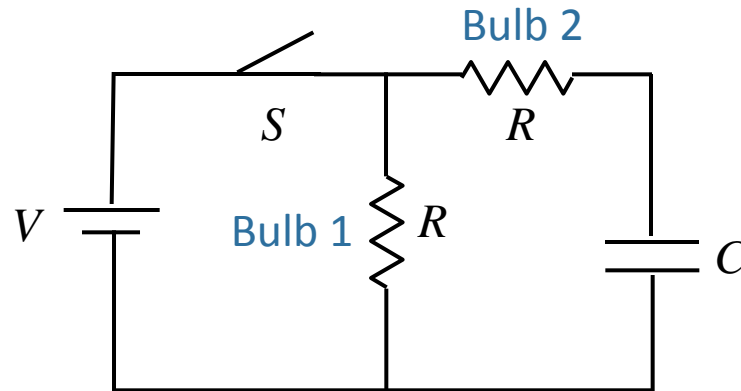

What will happen after I close the switch?

- A) Both bulbs come on and stay on.
- B) Both bulbs come on but then bulb 2 fades out.**
- C) Both bulbs come on but then bulb 1 fades out.
- D) Both bulbs come on and then both fade out.

No initial charge
on capacitor



$$V(\text{bulb 1}) = V(\text{bulb 2}) = V$$




Both bulbs light

No final current
through capacitor



$$V(\text{bulb 2}) = 0$$

DEMO Clicker Question 2

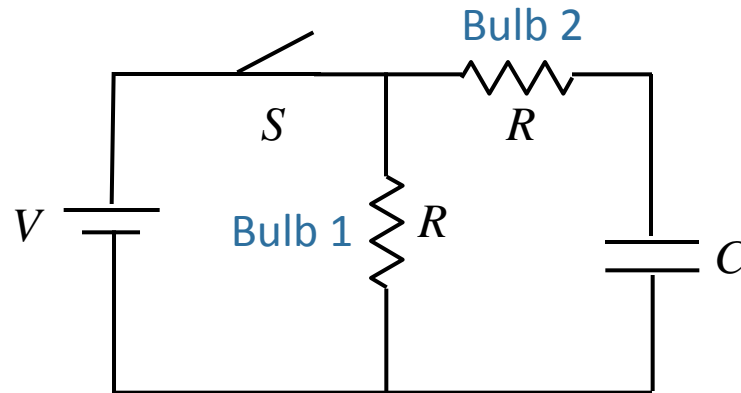


Suppose the switch has been closed a long time.
Now what will happen after open the switch?

- A) Both bulbs come on and stay on.
- B) Both bulbs come on but then bulb 2 fades out.
- C) Both bulbs come on but then bulb 1 fades out.
- D) Both bulbs come on and then both fade out.

Capacitor has charge ($=CV$)  Capacitor discharges through both resistors

Calculation

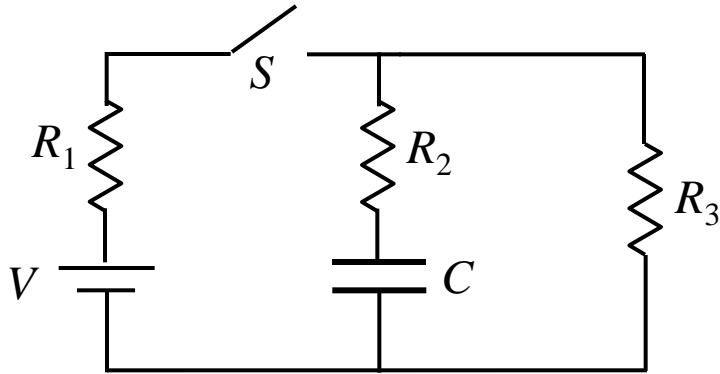

In this circuit, assume V , C , and R_i are known.
 C initially uncharged and then switch S is closed.

What is the voltage across the capacitor after a long time ?

Conceptual Analysis:

Circuit behavior described by Kirchhoff's Rules:

$$\Sigma V_{drops} = 0$$


$$\Sigma I_{in} = \Sigma I_{out}$$

S closed and C charges to some voltage with some time constant

Strategic Analysis

Determine currents and voltages in circuit a long time after S closed

Calculation

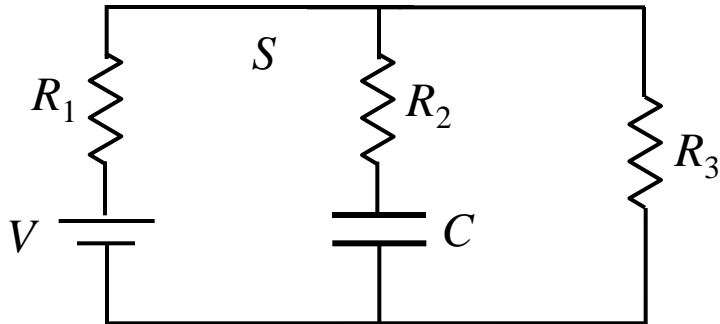

In this circuit, assume V , C , and R_i are known.
 C initially uncharged and then switch S is closed.

What is the voltage across the capacitor after a long time ?

Immediately after S is closed:

what is I_2 , the current through C

what is V_C , the voltage across C ?


- A) Only $I_2 = 0$ **B) Only $V_C = 0$** C) Both I_2 and $V_C = 0$ D) Neither I_2 nor $V_C = 0$

Why?

We are told that C is initially uncharged ($V = Q/C$)

I_2 cannot be zero because charge must flow in order to charge C

Calculation

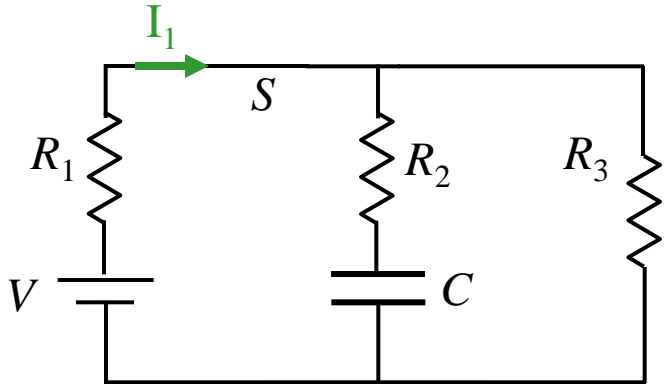

In this circuit, assume V , C , and R_i are known.
 C initially uncharged and then switch S is closed.

What is the voltage across the capacitor after a long time ?

Immediately after S is closed, what is I_1 , the current through R_1 ?

$$\frac{V}{R_1}$$

A

$$\frac{V}{R_1 + R_3}$$

B

$$\frac{V}{R_1 + R_2 + R_3}$$

C

$$\frac{V}{R_1 + \frac{R_2 R_3}{R_2 + R_3}}$$

D


$$V \frac{R_1 + R_2 + R_3}{R_1 R_2 + R_2 R_3 + R_1 R_3}$$

E


Why?

Draw circuit just after S closed (knowing $V_C = 0$)

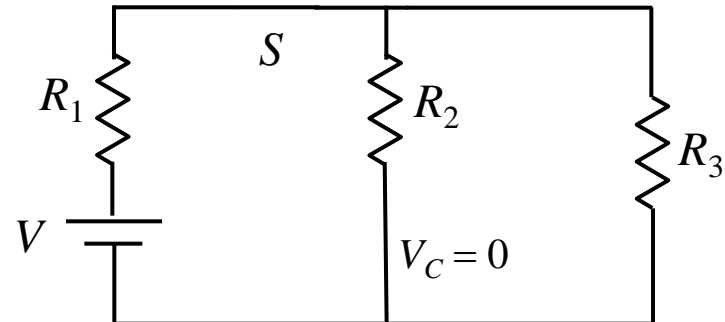R_1 is in series with the parallel combination of R_2 and R_3



Calculation

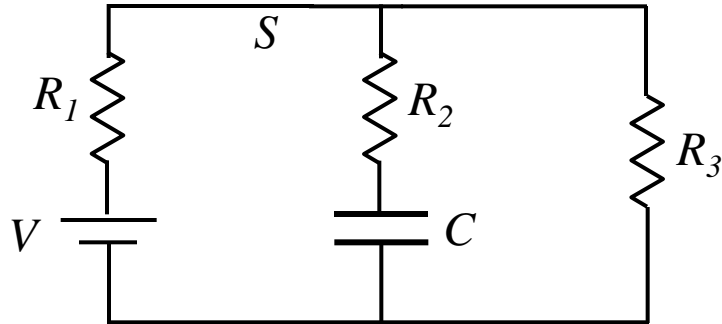

In this circuit, assume V , C , and R_i are known.
 C initially uncharged and then switch S is closed.

What is the voltage across the capacitor after a long time ?

After S has been closed “for a long time”, what is I_2 , the current through R_2 ?

$$\frac{V}{R_2}$$

A

$$\frac{V}{R_1}$$


B

0
C


Why?

After a long time in a static circuit, the current through any capacitor approaches 0 !

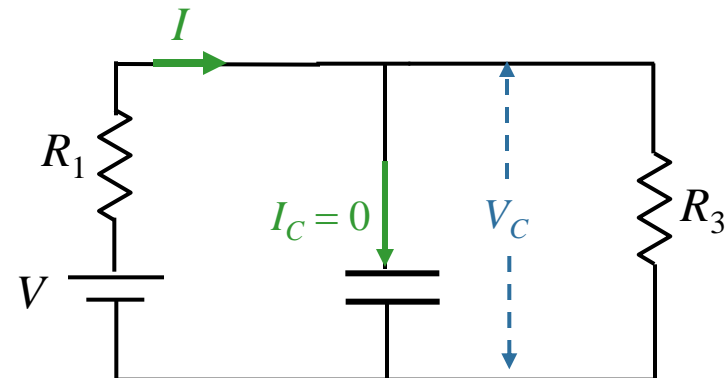This means we Redraw circuit with open circuit in middle leg



Calculation

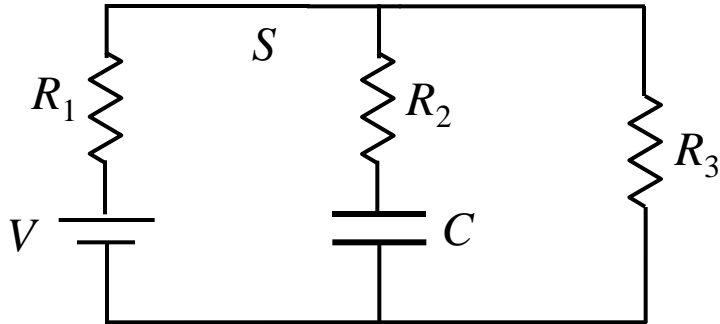

In this circuit, assume V , C , and R_i are known.
 C initially uncharged and then switch S is closed.

What is the voltage across the capacitor after a long time ?

After S has been closed “for a long time”, what is V_C , the voltage across C ?

$$V \frac{R_3}{R_1 + R_3}$$

A

$$V \frac{R_2}{R_1 + R_2}$$

B

$$V$$

C

$$V \frac{R_2}{R_1 + \frac{R_2 R_3}{R_2 + R_3}}$$


D

$$0$$


E

Why?
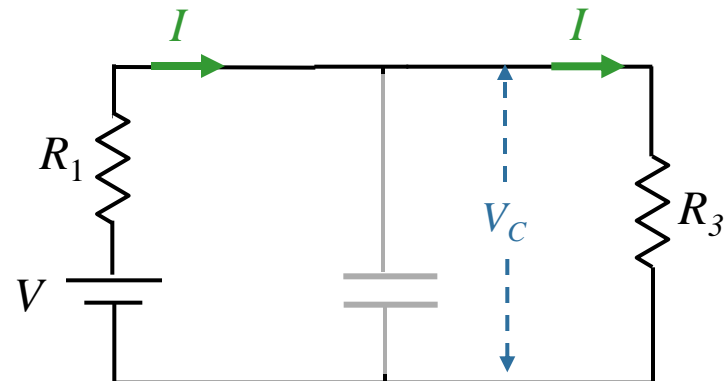
$$- V_C = V_3 = IR_3 = (V/(R_1 + R_3))R_3$$



Challenge (like homework problem)

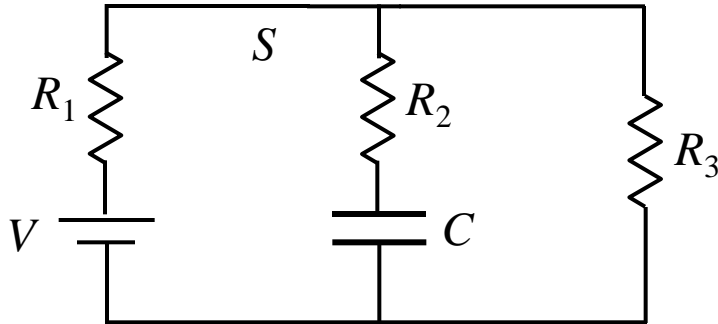

In this circuit, assume V , C , and R_i are known. C initially uncharged and then switch S is closed.

What is τ_c , the charging time constant?

Strategy

Write down KVR and KCR for the circuit when S is closed

2 loop equations and 1 node equation

Use $I_2 = dQ_2/dt$ to obtain one equation that looks like simple charging RC circuit

($(Q/C) + R(dQ/dt) - V = 0$)


Make correspondence: " R " = ?, and " C " = ?, then $\tau = R \times C$

I got:
$$\tau_c = \left(R_2 + \frac{R_1 R_3}{R_1 + R_3} \right) C$$


Checkpoint 2



The two circuits shown below contain identical capacitors that hold the same charge at $t = 0$. Circuit 2 has twice as much resistance as circuit 1.

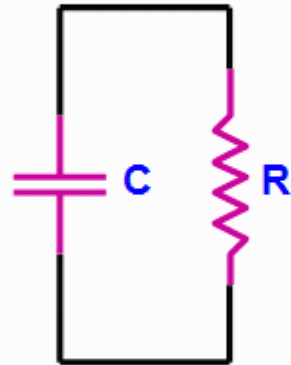

Circuit 1


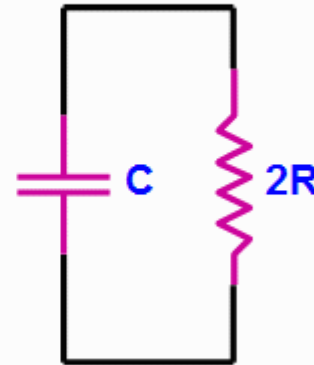


Circuit 2

Which circuit has the largest time constant?

- A) Circuit 1
- B) Circuit 2**
- C) Same



$$\tau = R_{equiv}/C$$

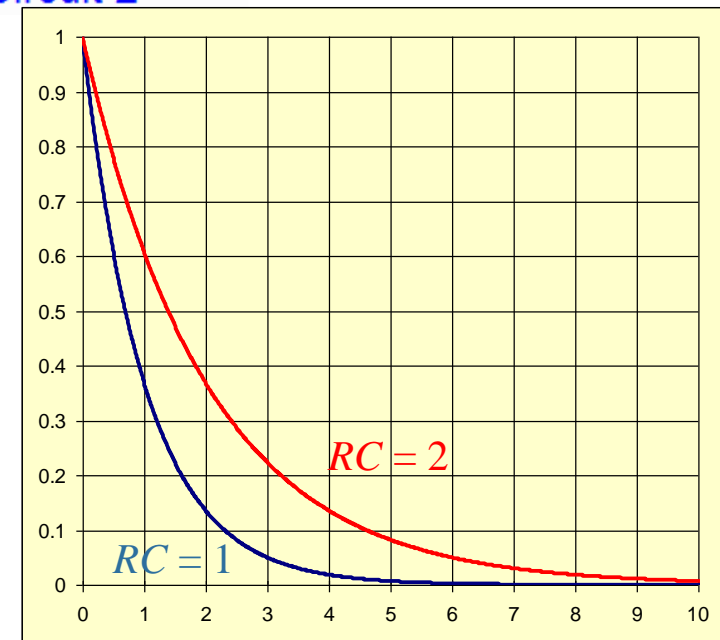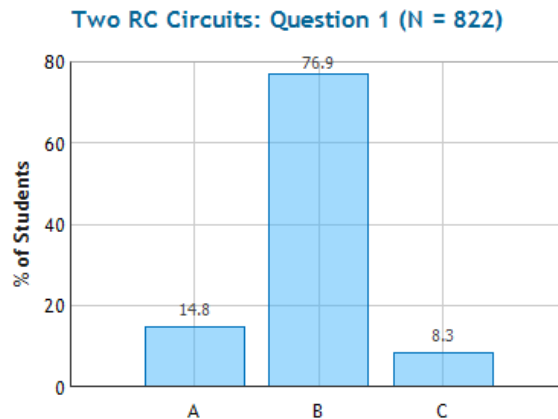


Checkpoint 2



The two circuits shown below contain identical capacitors that hold the same charge at $t = 0$. Circuit 2 has twice as much resistance as circuit 1.

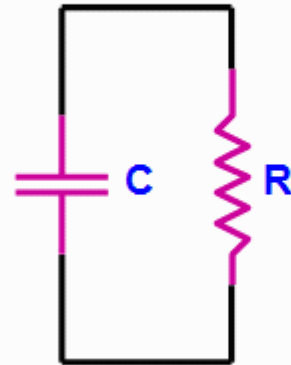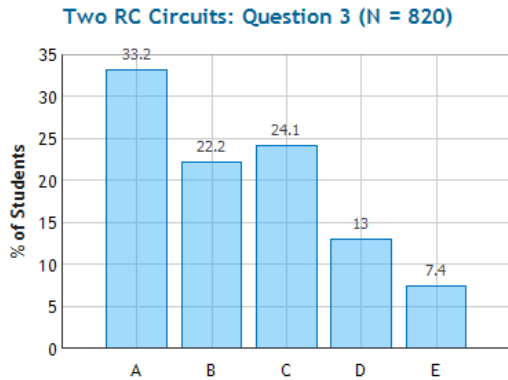

Circuit 1

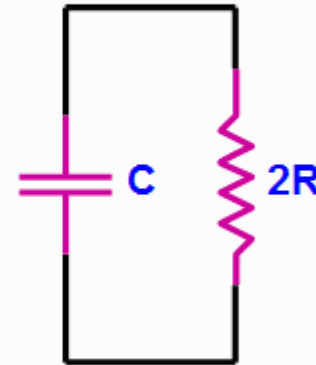

Circuit 2

Which of the following statements best describes the charge remaining on each of the the two capacitors for for any time after $t = 0$?

- $Q_1 < Q_2$
- $Q_1 > Q_2$
- $Q_1 = Q_2$
- $Q_1 < Q_2$ at first and then $Q_1 > Q_2$ after a long time
- $Q_1 > Q_2$ at first and then $Q_1 < Q_2$ after a long time

$$Q = Q_0 e^{-t/RC}$$

Look at plot!

