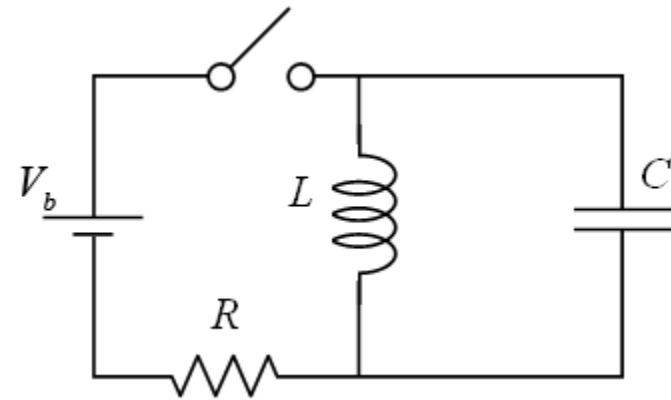


Your Comments

I am not feeling great about this midterm...some of this stuff is really confusing still and I don't know if I can shove everything into my brain in time, especially after spring break. Can you go over which topics will be on the exam Wednesday?

This was a very confusing prelecture. Do you think you could go over thoroughly how the LC circuits work qualitatively?

I may have missed something simple, but in question 1 during the prelecture why does the charge on the capacitor have to be 0 at $t=0$? I feel like that bit of knowledge will help me with the test wednesday



I remember you mentioning several weeks ago that there was one equation you were going to add to the 2013 [equation sheet](#)... which formula was that? Thanks!

Some Exam Stuff

Exam Wed. night (March 27th) at 7:00

- Covers material in Lectures 9 – 18
- Bring your ID: Rooms determined by discussion section (see link)

Don't forget:

- Worked examples in homeworks (the optional questions)
- Other old exams

For most people, taking old exams is most beneficial

Final Exam dates are now posted

The Big Ideas L9-18

Kirchoff's Rules

- Sum of voltages around a loop is zero
- Sum of currents into a node is zero
- Kirchoff's rules with capacitors and inductors
 - In RC and RL circuits: charge and current involve exponential functions with time constant: "charging and discharging"
 - E.g. $IR + \frac{Q}{C} = R \frac{dQ}{dt} + \frac{Q}{C} = V$
- Capacitors and inductors store energy


Magnetic fields

- Generated by electric currents (no magnetic charges)
- Magnetic forces only on charges in motion $\vec{F}_{mag} = q\vec{v} \times \vec{B}$
- Easiest to calculate with Ampere's Law $\oint \vec{B} \cdot d\vec{\ell} = \mu_0 I_{enclosed}$
- Changing magnetic fields can generate electric fields! FARADAY'S LAW

$$\int \vec{E} \cdot d\vec{\ell} = EMF = \Delta V = -\frac{d}{dt} \int \vec{B} \cdot d\vec{A} = -\frac{d\phi_{mag}}{dt}$$




Physics 212

Lecture 19

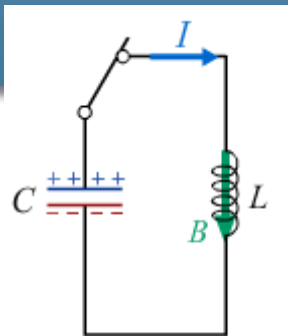


Today's Concepts:

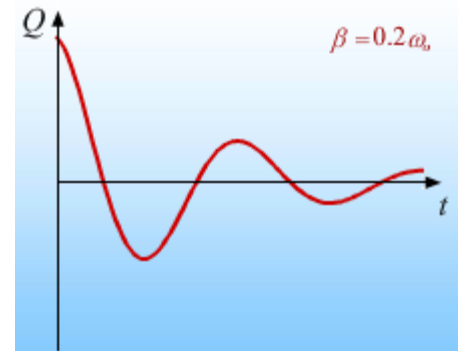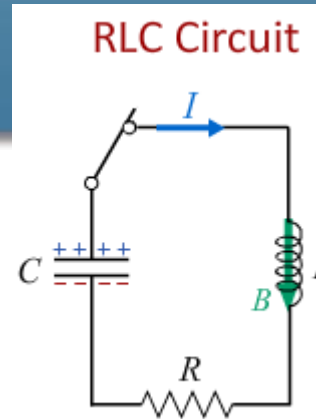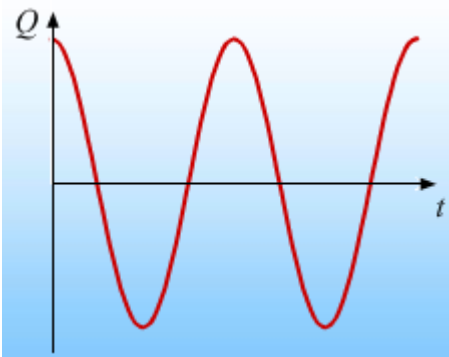- A) Oscillation Frequency
- B) Energy
- C) Damping



LC Circuit

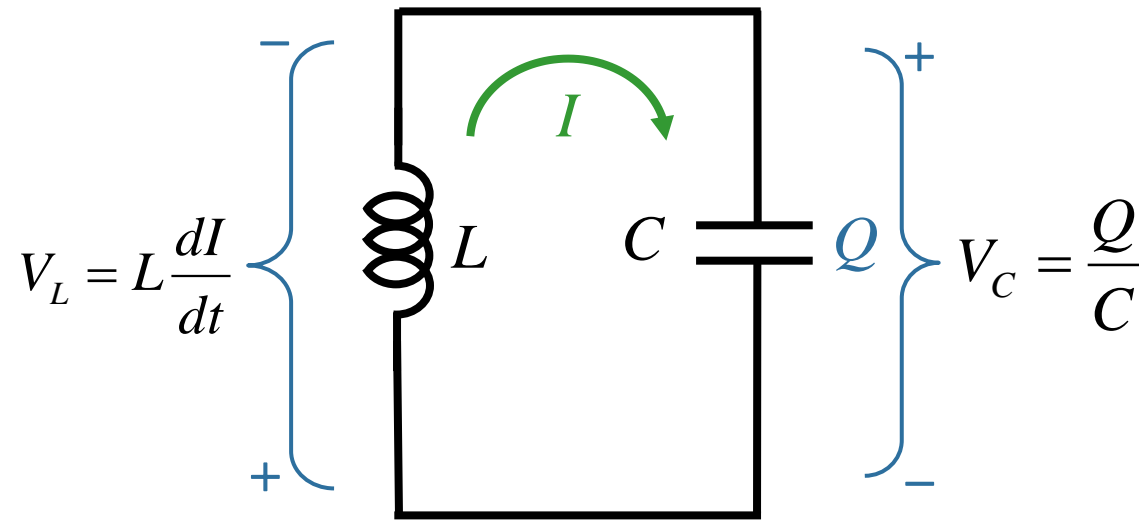

Circuit Equation: $\frac{Q}{C} + L \frac{dI}{dt} = 0$

$$I = \frac{dQ}{dt} \longrightarrow \frac{d^2Q}{dt^2} = -\frac{Q}{LC} \longrightarrow \frac{d^2Q}{dt^2} = -\omega^2 Q$$


where

$$\omega = \frac{1}{\sqrt{LC}}$$

CheckPoint 1a



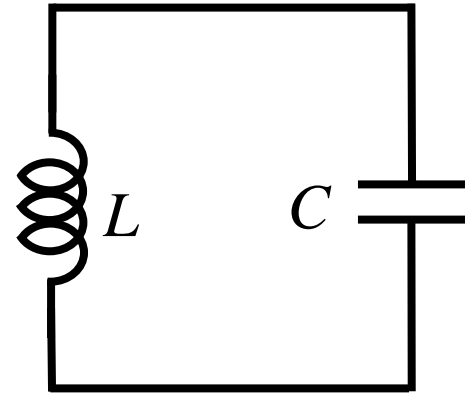At time $t = 0$ the capacitor is fully charged with Q_{max} and the current through the circuit is 0.



What is the potential difference across the inductor at $t = 0$?

A) $V_L = 0$

B) $V_L = Q_{max}/C$


C) $V_L = Q_{max}/2C$

since $V_L = V_C$

The voltage across the capacitor is Q_{max}/C . Kirchhoff's Voltage Rule implies that must also be equal to the voltage across the inductor

Pendulum.


LC Circuit: Question 1 (N = 749)

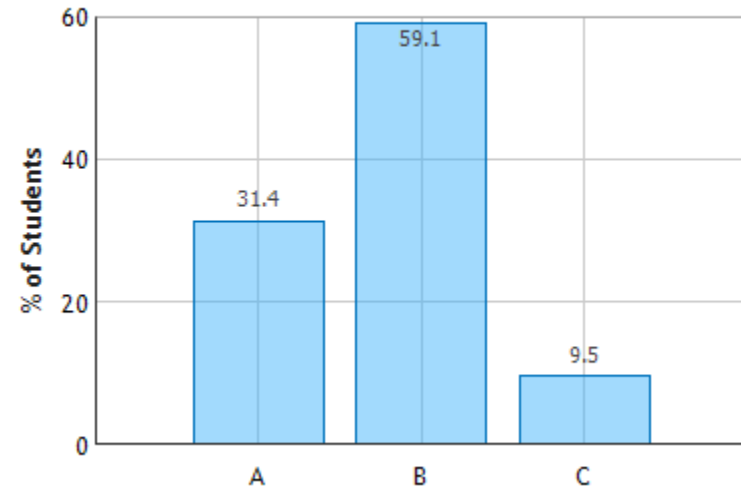

LC Circuits analogous to mass on spring


$$\frac{d^2Q}{dt^2} = -\omega^2 Q$$

$$\omega = \frac{1}{\sqrt{LC}}$$

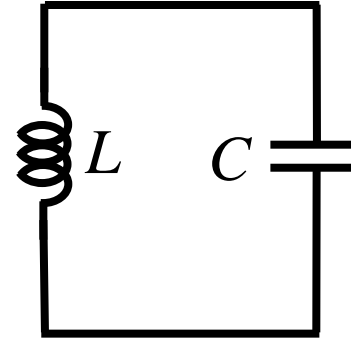

$$\frac{d^2x}{dt^2} = -\omega^2 x$$

$$\omega = \sqrt{\frac{k}{m}}$$

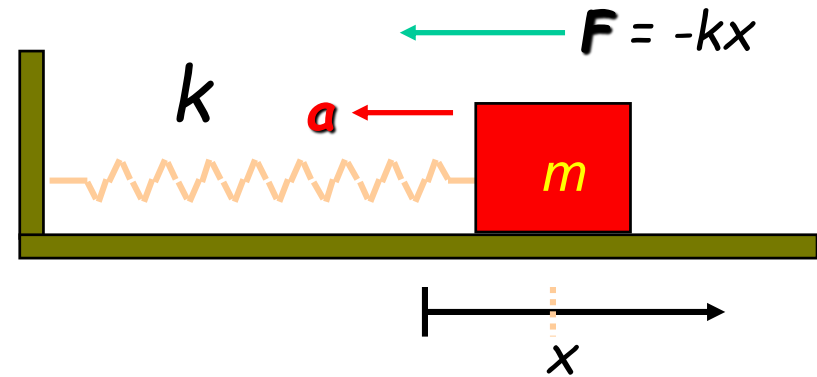



Same thing if we notice that

$$k \leftrightarrow \frac{1}{C}$$

and

$$m \leftrightarrow L$$


Time Dependence

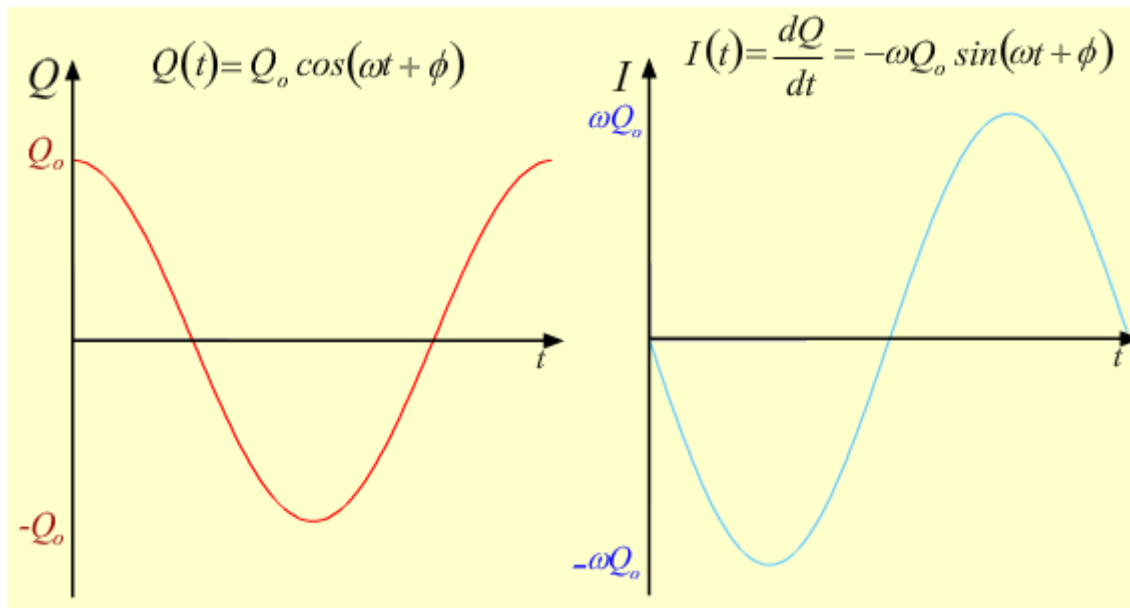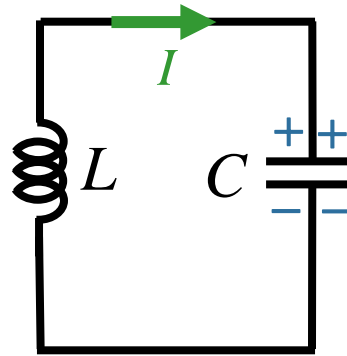

CheckPoint 1b



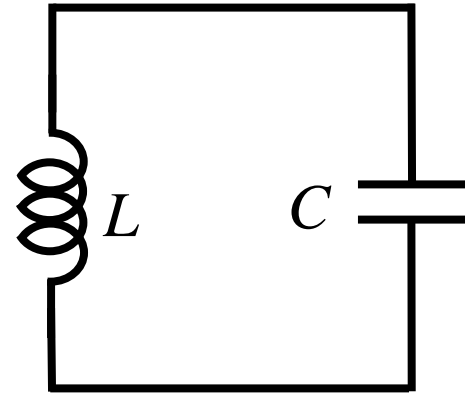At time $t = 0$ the capacitor is fully charged with Q_{max} and the current through the circuit is 0.



What is the potential difference across the inductor at when the current is maximum?


A) $V_L = 0$

B) $V_L = Q_{max}/C$

C) $V_L = Q_{max}/2C$

dI/dt is zero when current is maximum


LC Circuit: Question 3 (N = 748)

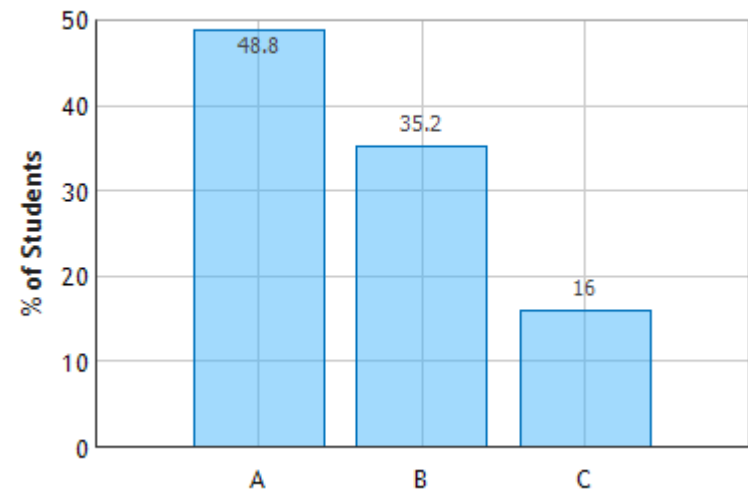

CheckPoint 1c



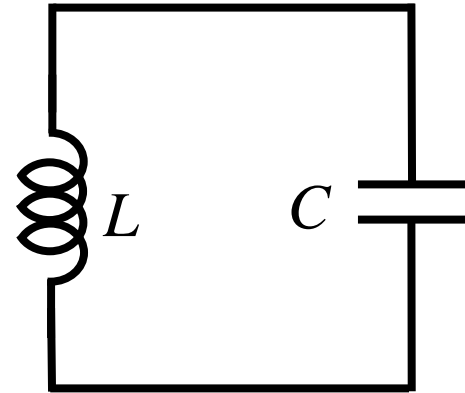At time $t = 0$ the capacitor is fully charged with Q_{max} and the current through the circuit is 0.



How much energy is stored in the capacitor when the current is a maximum ?

A) $U = Q_{max}^2 / (2C)$

B) $U = Q_{max}^2 / (4C)$

C) $U = 0$


Total Energy is constant!

$$U_{Lmax} = \frac{1}{2} L I_{max}^2$$

$$U_{Cmax} = \frac{Q_{max}^2}{2C}$$

$I = max$ when $Q = 0$


LC Circuit: Question 5 (N = 748)

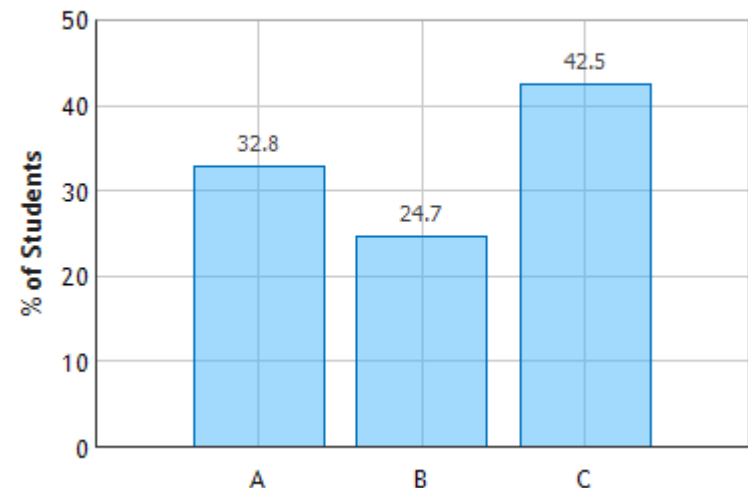

CheckPoint 2a



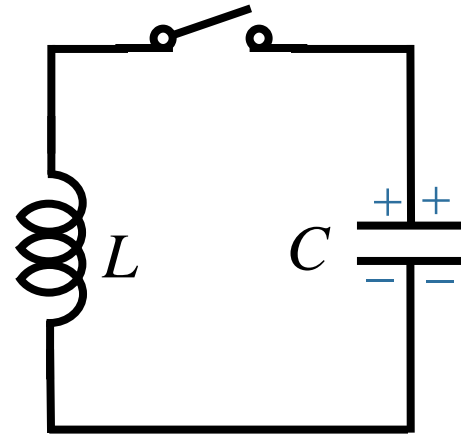The capacitor is charged such that the top plate has a charge $+Q_0$ and the bottom plate $-Q_0$. At time $t = 0$, the switch is closed and the circuit oscillates with frequency $\omega = 500$ radians/s.



$$L = 4 \times 10^{-3} \text{ H}$$
$$\omega = 500 \text{ rad/s}$$

What is the value of the capacitor C ?


A) $C = 1 \times 10^{-3} \text{ F}$

B) $C = 2 \times 10^{-3} \text{ F}$







C) $C = 4 \times 10^{-3} \text{ F}$

$$\omega = \frac{1}{\sqrt{LC}} \longrightarrow C = \frac{1}{\omega^2 L} = \frac{1}{(25 \times 10^4)(4 \times 10^{-3})} = 10^{-3}$$

LC Circuit 2: Question 1 (N = 747)

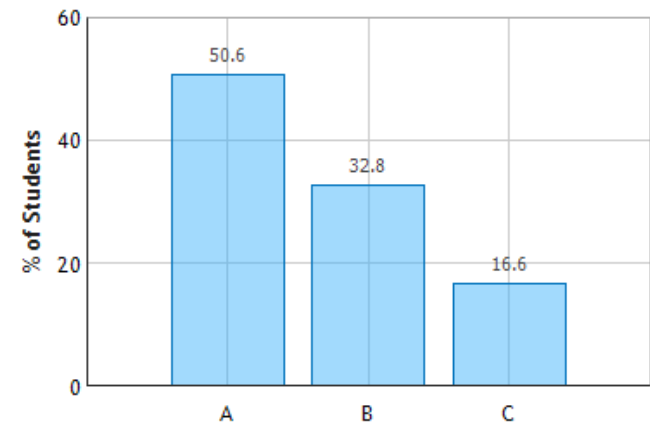

CheckPoint 2b

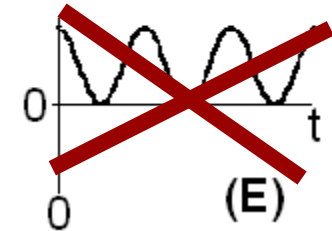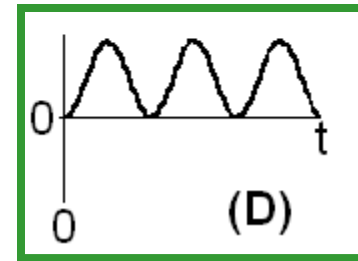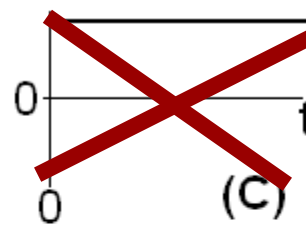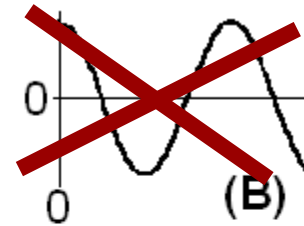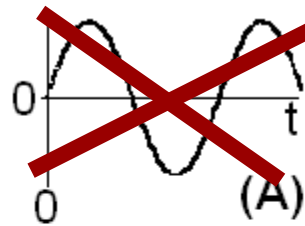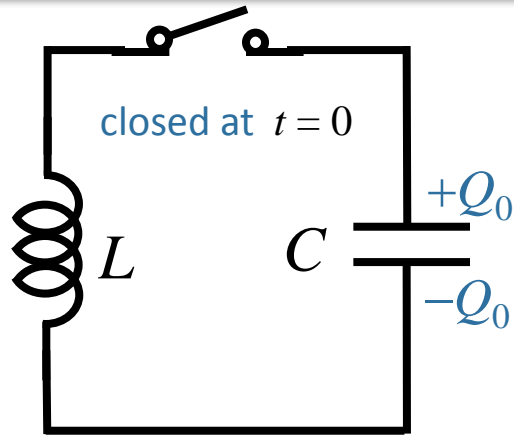

Which plot best represents the energy in the inductor as a function of time starting just after the switch is closed?


$$U_L = \frac{1}{2} LI^2$$

Energy proportional to $I^2 \Rightarrow C$ cannot be negative

Current is changing $\Rightarrow U_L$ is not constant

Initial current is zero


LC Circuit 2: Question 3 (N = 747)

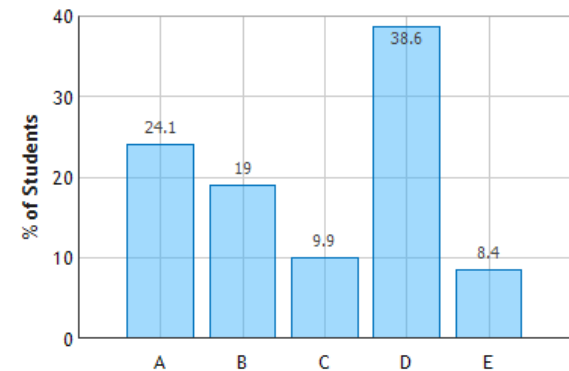


CheckPoint 2c



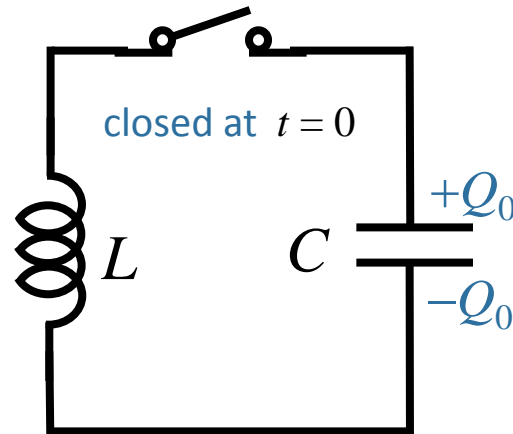When the energy stored in the capacitor reaches its maximum again for the **first time after $t = 0$** , how much charge is stored on the top plate of the capacitor?



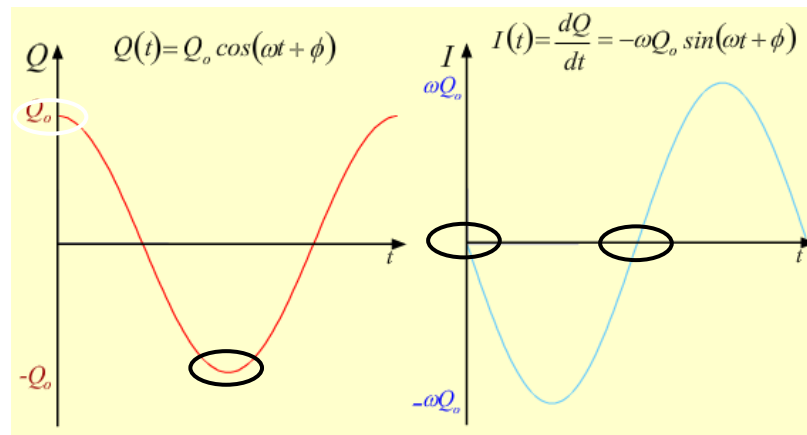- A) $+Q_0$
- B) $+Q_0/2$
- C) 0
- D) $-Q_0/2$
- E) $-Q_0$**




Q is maximum when current goes to zero

$$I = \frac{dQ}{dt}$$


Current goes to zero twice during one cycle

LC Circuit 2: Question 5 (N = 746)

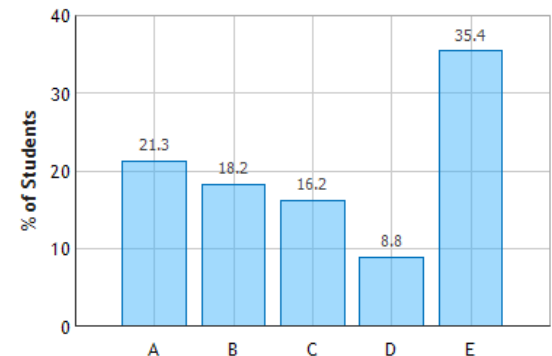

Add R: Damping

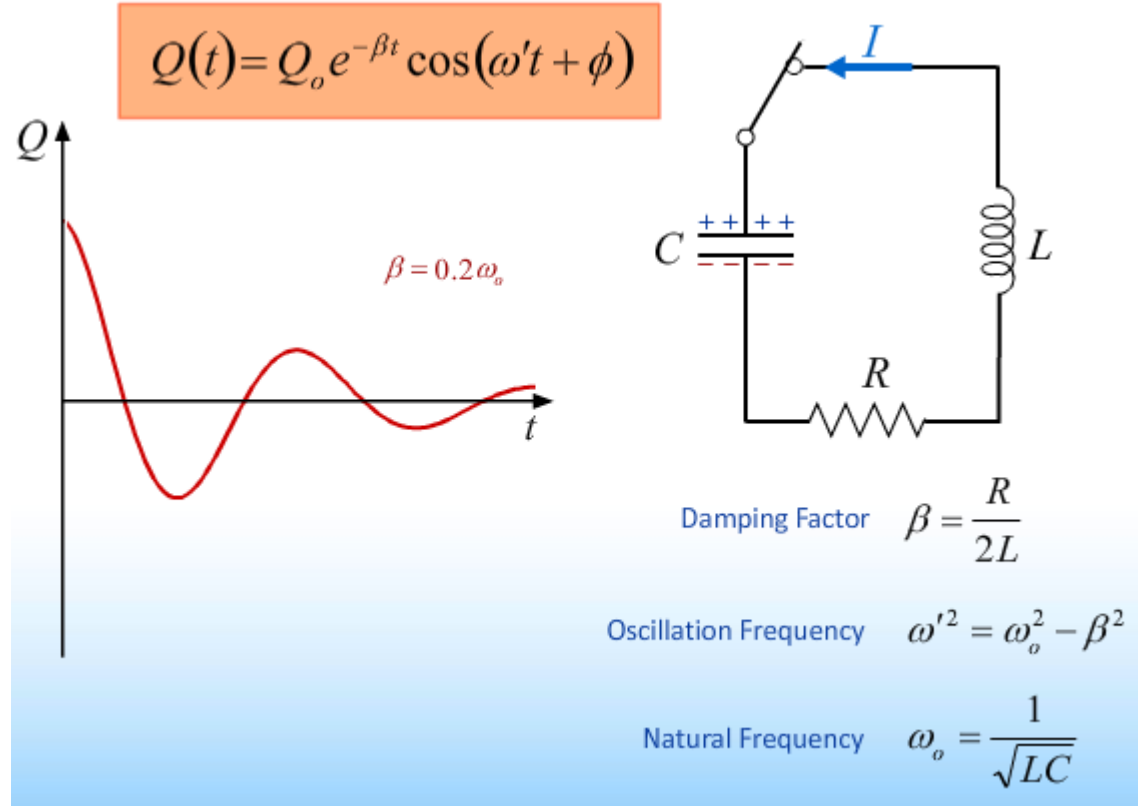Just like LC circuit but energy but the oscillations get smaller because of R



Concept makes sense...

...but answer looks kind of complicated

Physics Truth #1:

Even though the answer sometimes looks complicated...


$$Q(t) = Q_0 \cos(\omega t - \phi)$$

the physics under the hood is still very simple!

$$\frac{d^2 Q}{dt^2} = -\omega^2 Q$$

The elements of a circuit are very simple:

$$V_L = L \frac{dI}{dt}$$

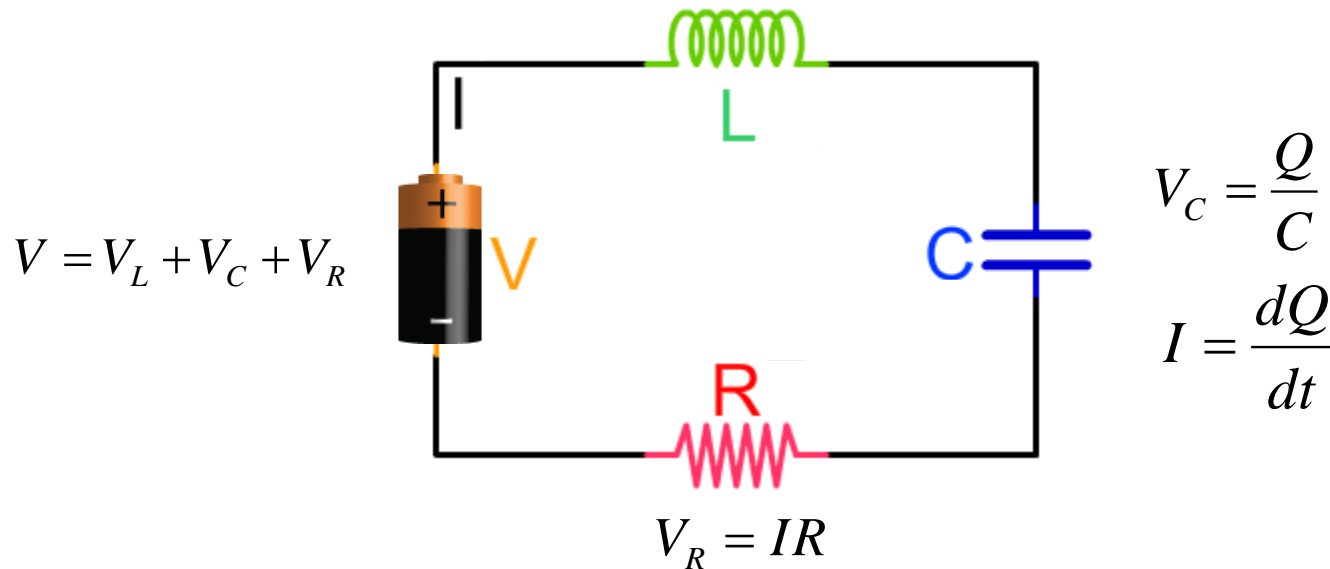


This is all we need to know to solve for anything!

Calculation

The switch in the circuit shown has been closed for a long time. At $t = 0$, the switch is opened.

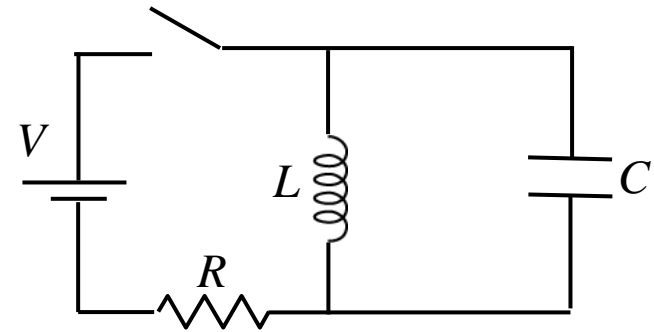What is Q_{MAX} , the maximum charge on the capacitor?



Conceptual Analysis


Once switch is opened, we have an LC circuit
Current will oscillate with natural frequency ω_0

Strategic Analysis

- Determine initial current
- Determine oscillation frequency ω_0
- Find maximum charge on capacitor

Calculation

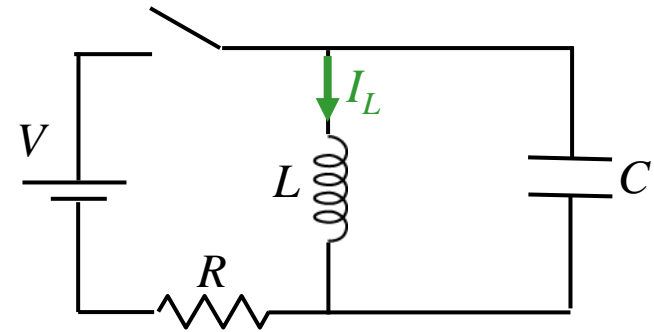The switch in the circuit shown has been closed for a long time. At $t = 0$, the switch is opened.



What is I_L , the current in the inductor, immediately **after** the switch is opened? Take positive direction as shown.

A) $I_L < 0$

B) $I_L = 0$

C) $I_L > 0$


Current through inductor immediately **after** switch is opened
is the same as
the current through inductor immediately **before** switch is opened

before switch is opened:

all current goes through inductor in direction shown

Calculation

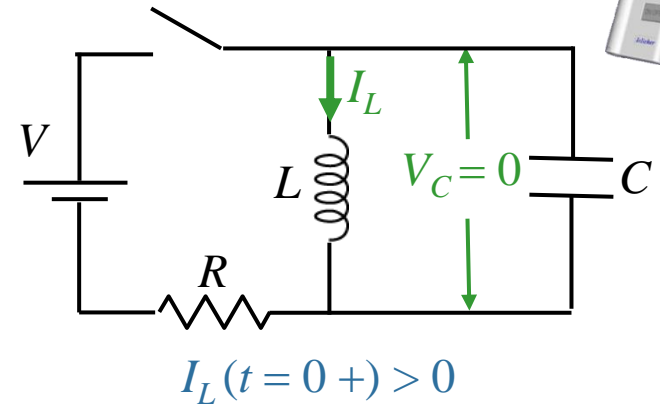The switch in the circuit shown has been closed for a long time. At $t = 0$, the switch is opened.



The energy stored in the capacitor immediately after the switch is opened is zero.

A) TRUE

B) FALSE

before switch is opened:

$$dI_L/dt \sim 0 \Rightarrow V_L = 0$$

BUT: $V_L = V_C$

since they are in parallel

→ $V_C = 0$

after switch is opened:

V_C cannot change abruptly

→ $V_C = 0$

→ $U_C = \frac{1}{2} CV_C^2 = 0!$

IMPORTANT: NOTE DIFFERENT CONSTRAINTS AFTER SWITCH OPENED


CURRENT through INDUCTOR cannot change abruptly

VOLTAGE across CAPACITOR cannot change abruptly

Calculation



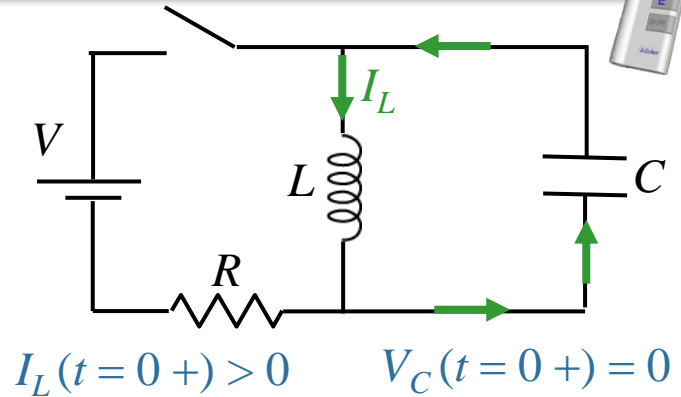The switch in the circuit shown has been closed for a long time. At $t = 0$, the switch is opened.



What is the direction of the current immediately after the switch is opened?

A) clockwise

B) counterclockwise

Current through inductor immediately **after** switch is opened
is the same as
the current through inductor immediately **before** switch is opened


Before switch is opened: Current moves down through L

After switch is opened: Current continues to move down through L

Calculation



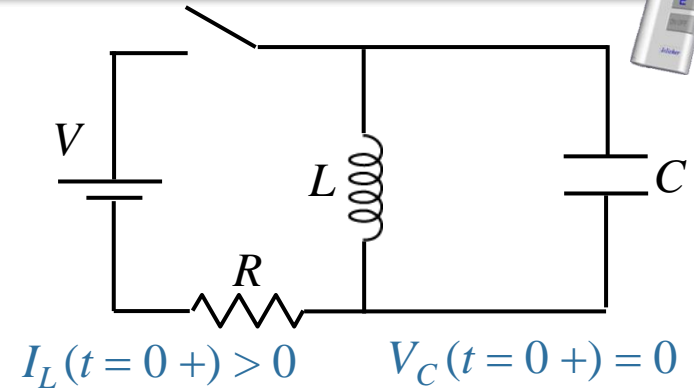The switch in the circuit shown has been closed for a long time. At $t = 0$, the switch is opened.



What is the magnitude of the current right after the switch is opened?

A) $I_o = V \sqrt{\frac{C}{L}}$


B) $I_o = \frac{V}{R^2} \sqrt{\frac{L}{C}}$

C) $I_o = \frac{V}{R}$

D) $I_o = \frac{V}{2R}$

Current through inductor immediately **after** switch is opened
is the same as
the current through inductor immediately **before** switch is opened

Before switch is opened:

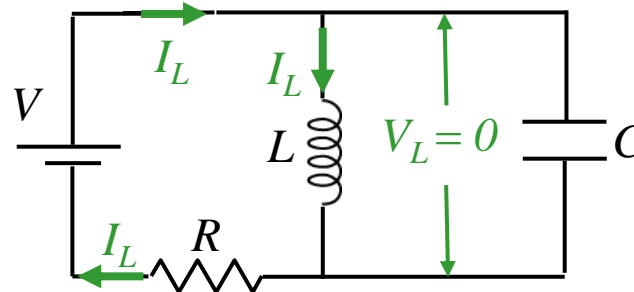


$V_L = 0$
↓
 $V = I_L R$

Calculation

The switch in the circuit shown has been closed for a long time. At $t = 0$, the switch is opened.

Hint: Energy is conserved

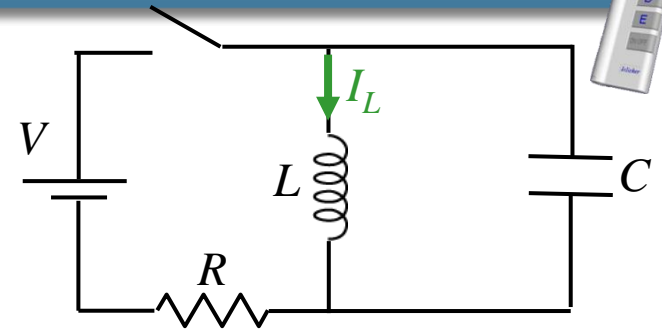

$$I_L(t = 0+) = V/R \quad V_C(t = 0+) = 0$$


What is Q_{\max} , the maximum charge on the capacitor during the oscillations?

$$\text{A) } Q_{\max} = \frac{V}{R} \sqrt{LC}$$

$$\text{B) } Q_{\max} = \frac{1}{2} CV$$


$$\text{C) } Q_{\max} = CV$$
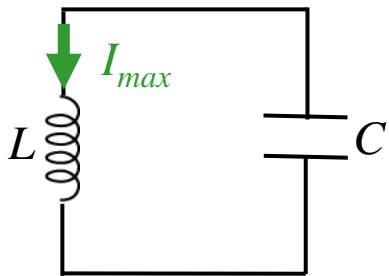
$$\text{D) } Q_{\max} = \frac{V}{R\sqrt{LC}}$$



When I is *max*
(and Q is 0)

$$U = \frac{1}{2} LI^2$$

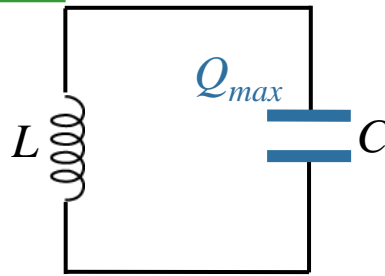

When Q is *max*
(and I is 0)

$$U = \frac{1}{2} \frac{Q_{\max}^2}{C}$$




$$\frac{1}{2} LI^2 = \frac{1}{2} \frac{Q_{\max}^2}{C}$$

$$Q_{\max} = I_{\max} \sqrt{LC} = \frac{V}{R} \sqrt{LC}$$

Follow-Up



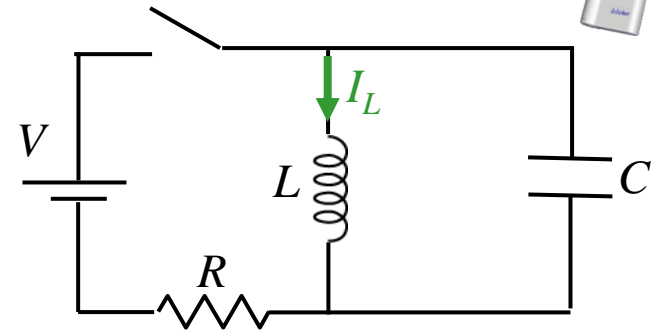The switch in the circuit shown has been closed for a long time. At $t = 0$, the switch is opened.



Is it possible for the maximum voltage on the capacitor to be greater than V ?

A) YES

B) NO

$$I_{\max} = V/R$$

$$Q_{\max} = \frac{V}{R} \sqrt{LC}$$

$$Q_{\max} = \frac{V}{R} \sqrt{LC} \rightarrow V_{\max} = \frac{V}{R} \sqrt{\frac{L}{C}} \rightarrow V_{\max} \text{ can be greater than } V \text{ IF: } \sqrt{\frac{L}{C}} > R$$

We can rewrite this condition in terms of the resonant frequency:

$$\omega_0 L > R \quad \text{OR} \quad \frac{1}{\omega_0 C} > R$$

We will see these forms again when we study **AC** circuits!