

Your Comments

This seemed very graphical and diagram based. What kind of problems would we see from this topic?

This was one of the most confusing things I've ever seen. I did AP C in high school but I don't think we did this topic? Or am I forgetting something?

What is reactance?

Can we discuss qualitatively why the current and voltage are out of phase for capacitors and inductors? It's difficult to remember which is which without understanding why it works the way it does.

I don't like having to do these prelectures the day of an exam...

This is the first time I didn't understand the prelecture at all. Please explain this!! What does the phasor diagram do??


always wanted to learn about AC. Speaking of AC, can you play "Epic Rap Battles of History: Thomas Edison vs Nikola Tesla" before class?

<http://www.youtube.com/watch?v=gJ1Mz7kGVf0>. Tesla is awesome!

THIS IS UNREAL @@.. who came up with the idea of a phasor diagram?

Set phasors to stun!

Physics 212 Lecture 20

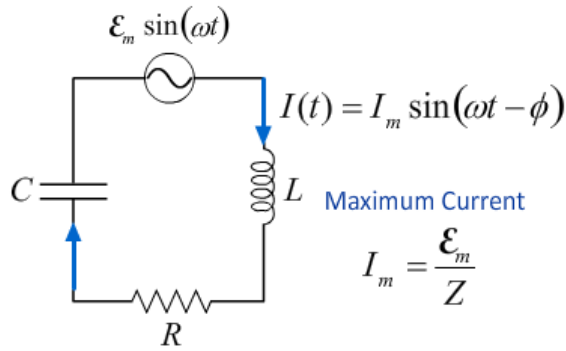


Today's Concept:

AC Circuits

Maximum currents & voltages

Phasors: A Simple Tool

Voltage Phasor Diagram

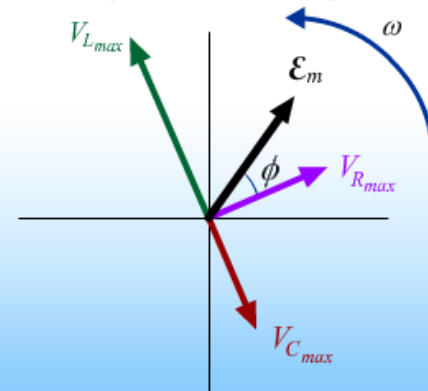

Big Idea

KVR

$$L \frac{d^2 Q}{dt^2} + R \frac{dQ}{dt} + \frac{Q}{C} - \mathcal{E}_m \sin(\omega t) = 0$$

Maximum Values (easy $V=IR$)



$$I_{max} = \mathcal{E}_{max} / Z$$
$$V_{Rmax} = I_{max} R$$
$$V_{Lmax} = I_{max} X_L$$
$$V_{Cmax} = I_{max} X_C$$

Value at specific time (phasors)



y component gives voltage

$V_{\text{-Inductor}}$ Leads current

$V_{\text{-Capacitor}}$ Lags current

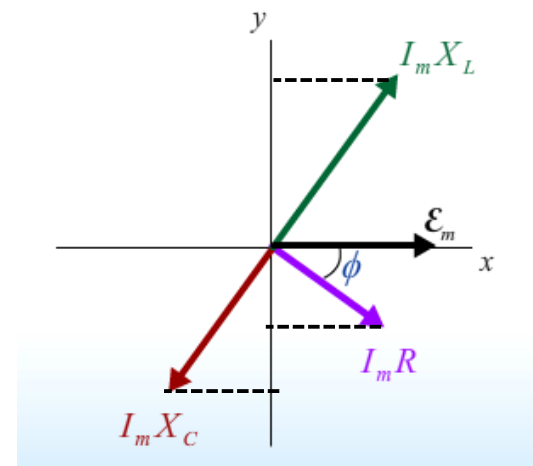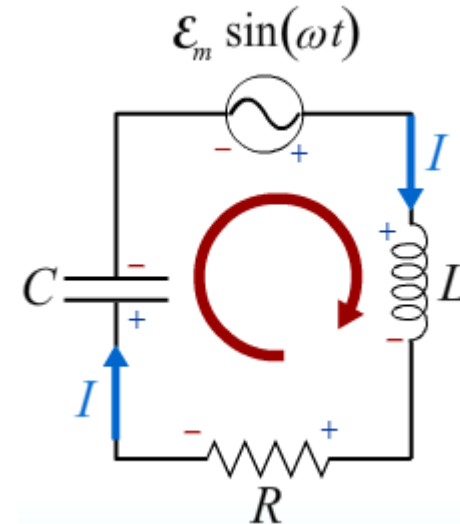


Resistors

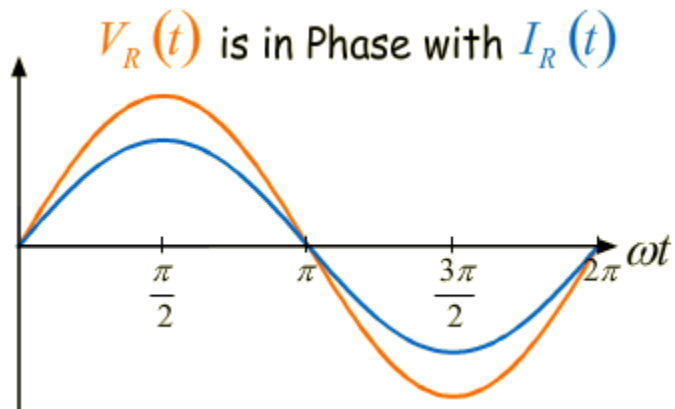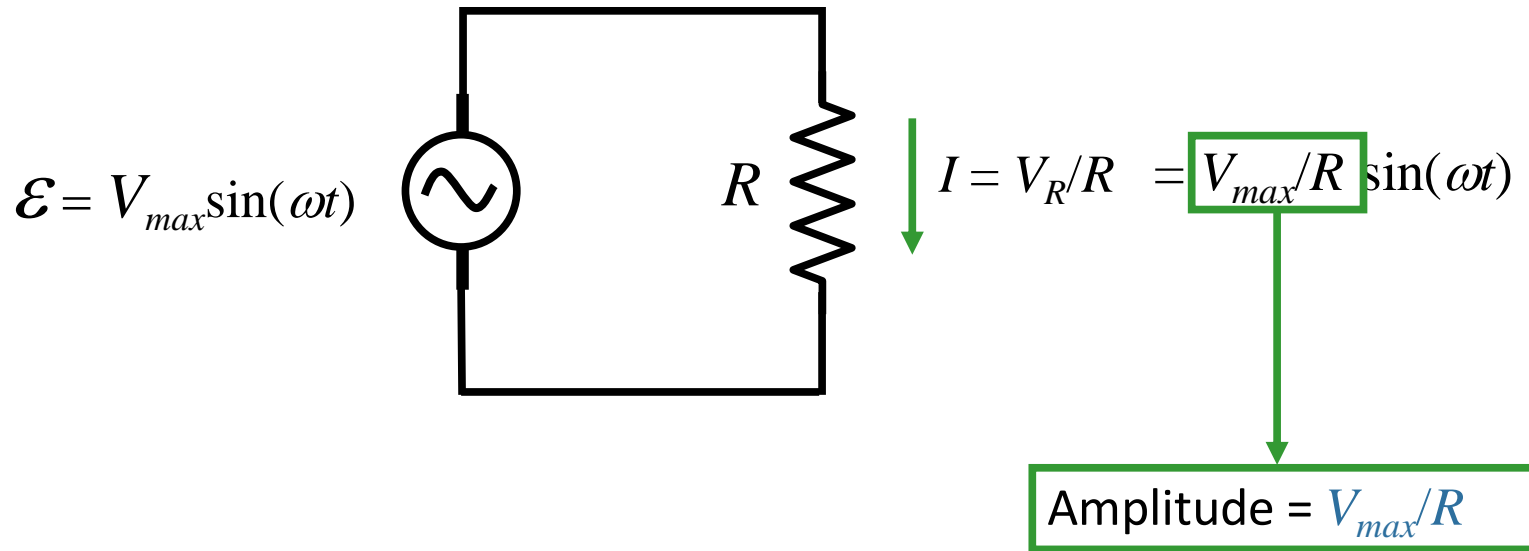

Capacitors

$$\mathcal{E} = V_{max} \sin(\omega t)$$

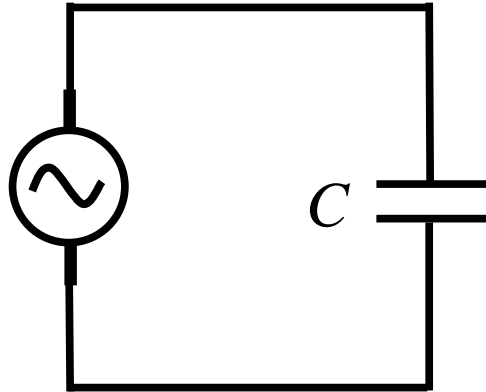

$$Q = CV = CV_{max} \sin(\omega t)$$


$$I = dQ/dt$$

$$I = V_{max} \omega C \cos(\omega t)$$

$$\text{Amplitude} = V_{max} / X_C$$


where $X_C = 1/\omega C$
is like the “resistance”
of the capacitor
 X_C depends on ω

$V_C(t)$ lags $I_C(t)$ by 90°

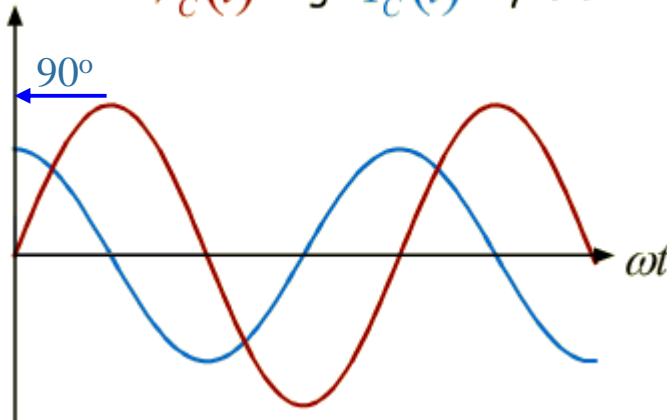

Inductors

$$\mathcal{E} = V_{max} \sin(\omega t)$$

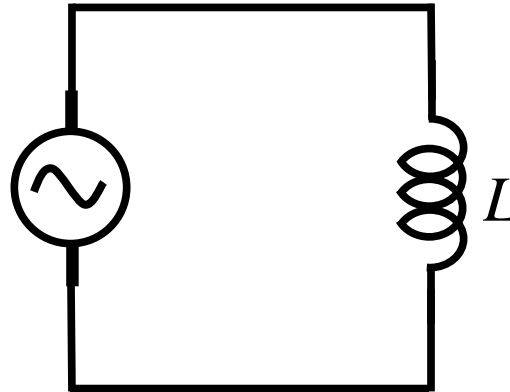


$$L \, dI/dt = V_L = V_{max} \sin(\omega t)$$

$$I = -V_{max}/\omega L \cos(\omega t)$$

$$\text{Amplitude} = V_{max}/X_L$$

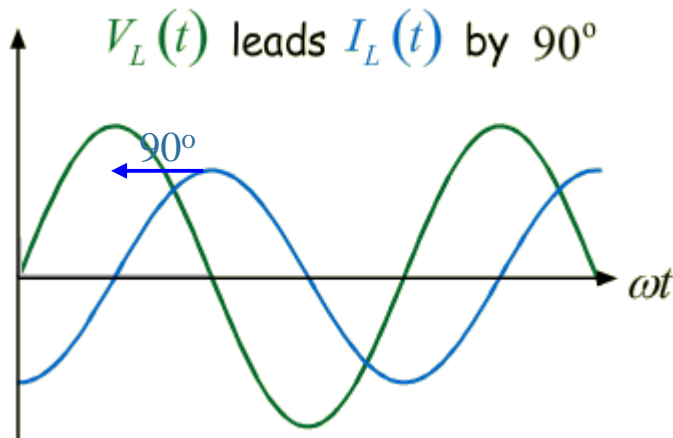
where $X_L = \omega L$
is like the “resistance”
of the inductor
 X_L depends on ω



RL Clicker Question



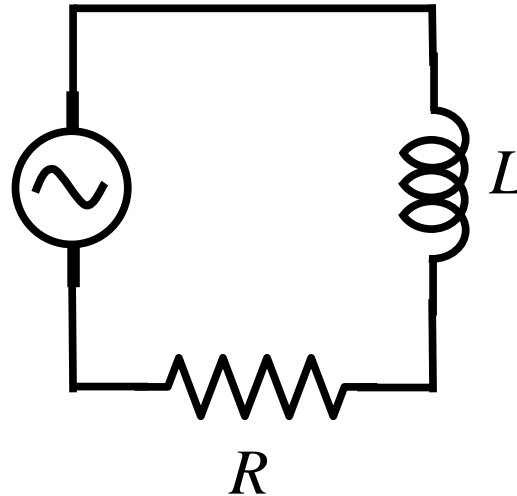An RL circuit is driven by an *AC* generator as shown in the figure.



$$X_L = \omega L$$

As $\omega \rightarrow 0$, so does X_L




As $\omega \rightarrow 0$,
resistance of circuit R
current gets bigger

For what driving frequency ω of the generator will the current through the resistor be largest

- A) ω large
- B) Current through R doesn't depend on ω
- C) ω small


Summary

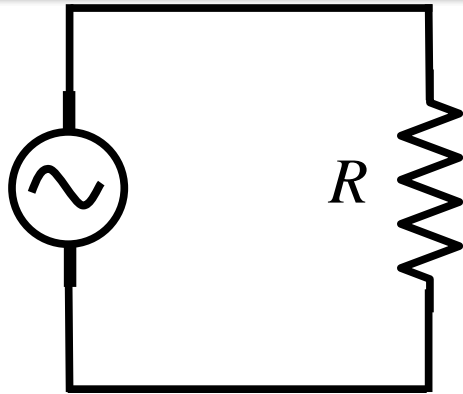

$$I_{max} = V_{max}/R$$

V_R in phase with I

Because resistors are simple

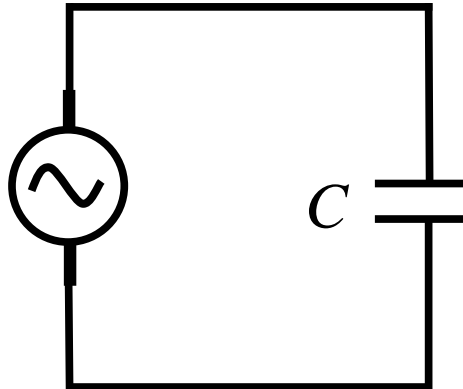


$$I_{max} = V_{max}/X_C$$

$$X_C = 1/\omega C$$

V_C 90° behind I

Current comes first since it charges capacitor

Like a wire at high ω

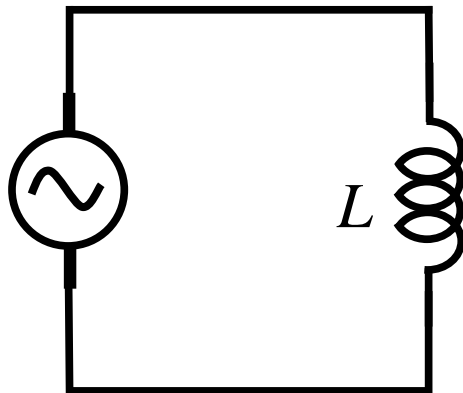

$$I_{max} = V_{max}/X_L$$

$$X_L = \omega L$$

V_L 90° ahead of I



Opposite of capacitor

Like a wire at low ω

CheckPoint 1c



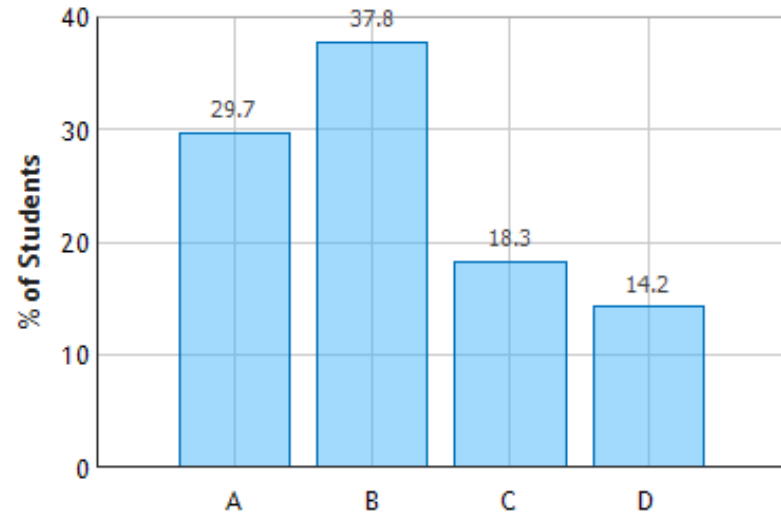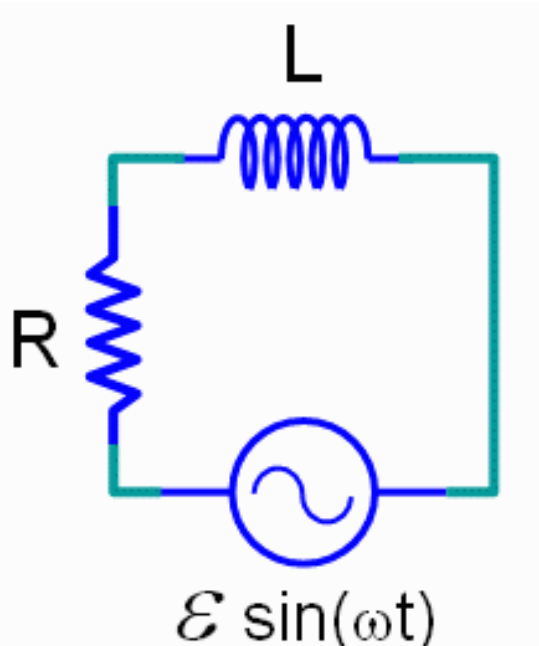A RL circuit is driven by an AC generator as shown in the figure.



The phase difference between the CURRENT through the resistor and inductor

- A)** Is always zero
- B)** Is always 90°
- C)** Depends on the value of L and R
- D)** Depends on L, R and the generator voltage


The CURRENT is THE CURRENT
There is only 1 current in this circuit
Same everywhere in circuit

Driven RLC Circuit

Makes sense to write everything in terms of I since this is the same everywhere in a one-loop circuit:

$$V_{max} = I_{max} X_C$$

V 90° behind I

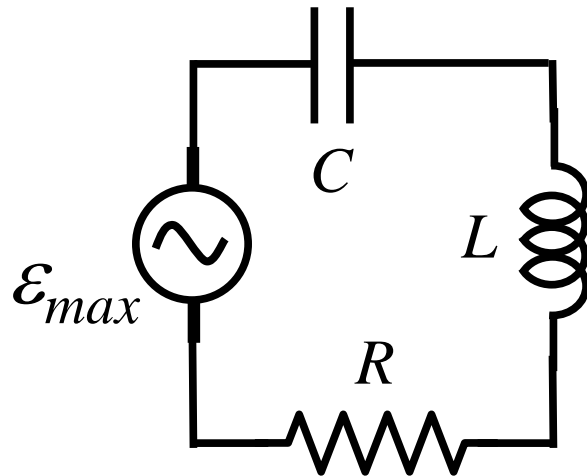


$$V_{max} = I_{max} X_L$$

V 90° ahead of I

$$V_{max} = I_{max} R$$

V in phase with I




Phasors make this simple to see

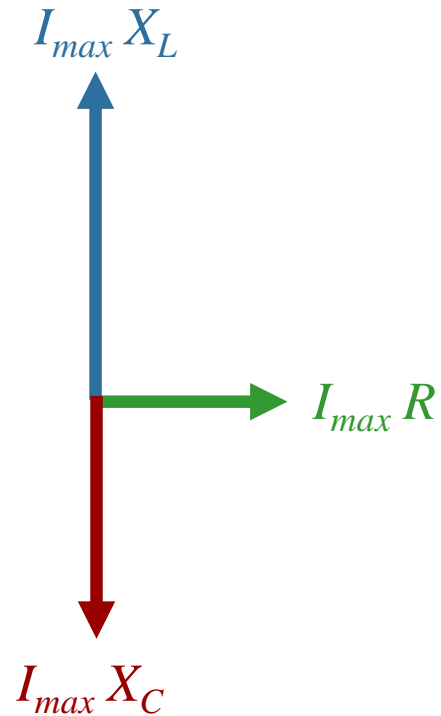




Always looks the same.
Only the lengths will change

The Voltages still Add Up



But now we are adding vectors:

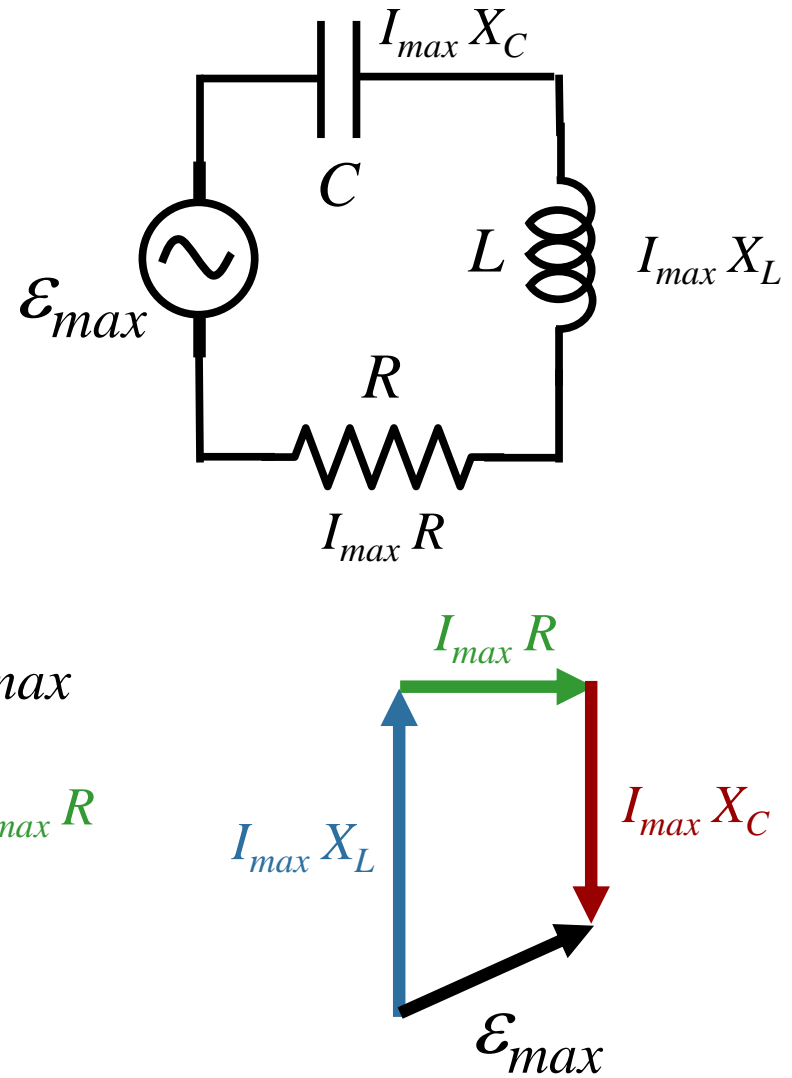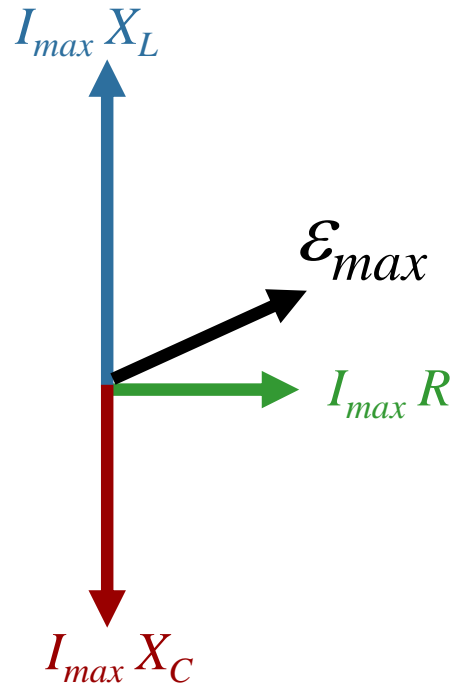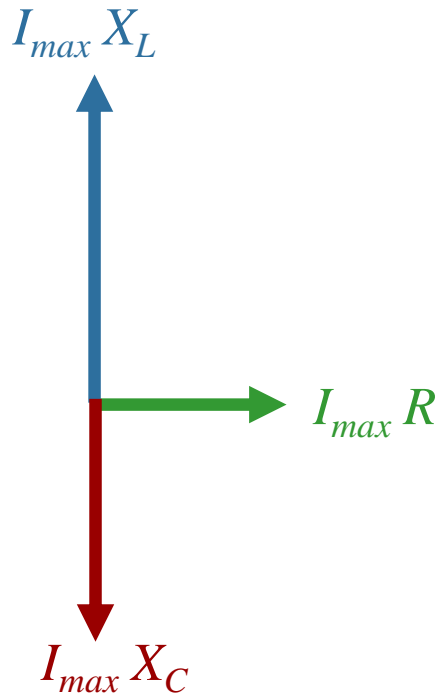

Make this Simpler

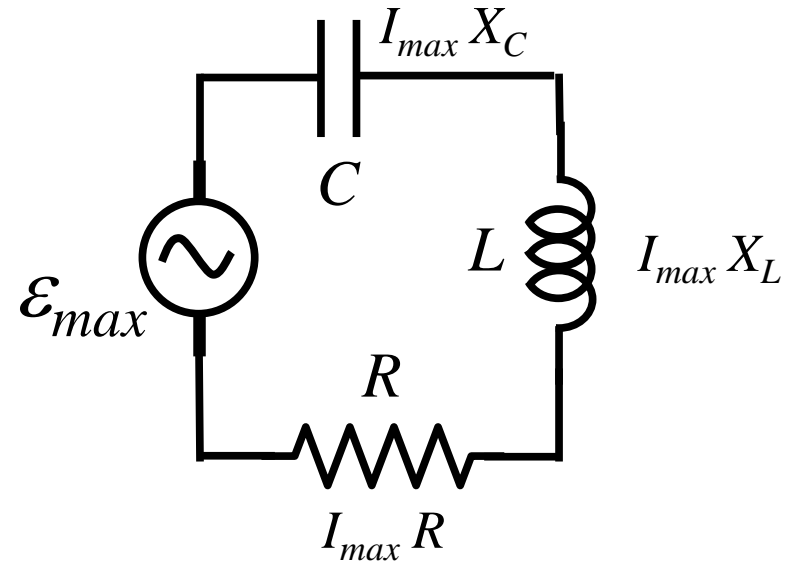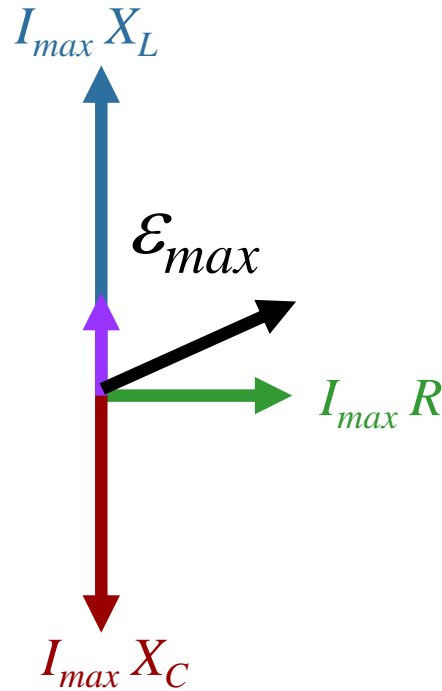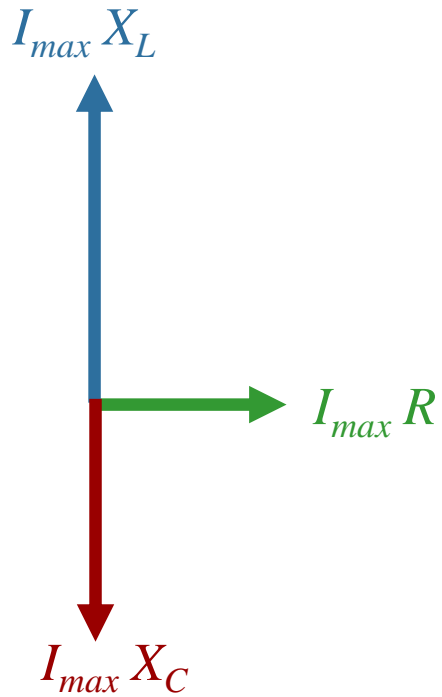



Make this Simpler

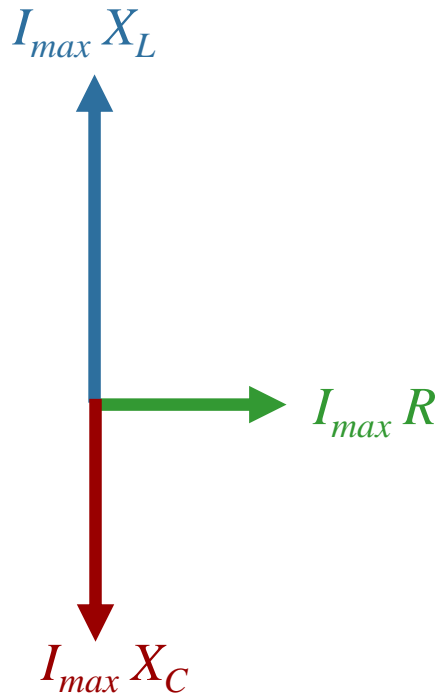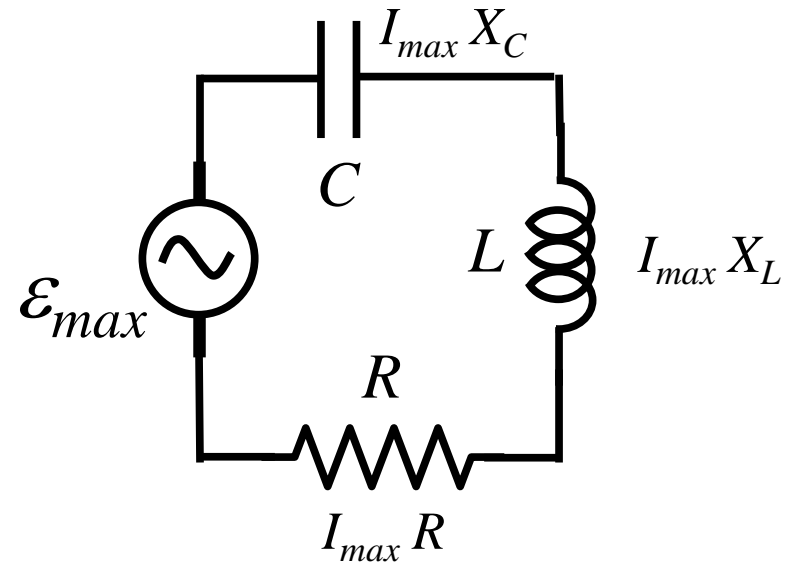




$$\mathcal{E}_{max} = I_{max} Z$$

A phasor diagram showing a black vector representing the total EMF \mathcal{E}_{max} . It is the vector sum of a green vector $I_{max} R$ pointing to the right and a purple vector $I_{max}(X_L - X_C)$ pointing upwards.

Make this Simpler

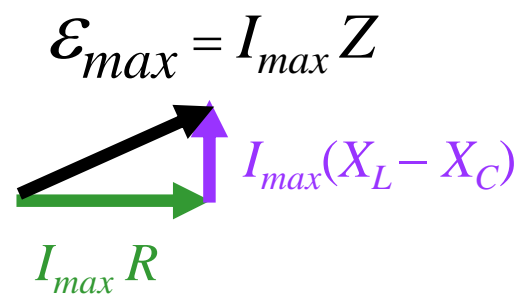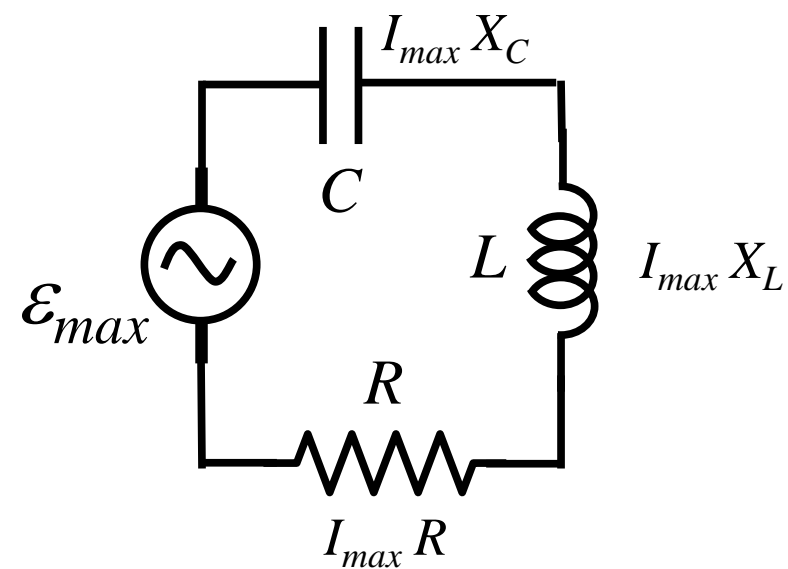

Make this Simpler

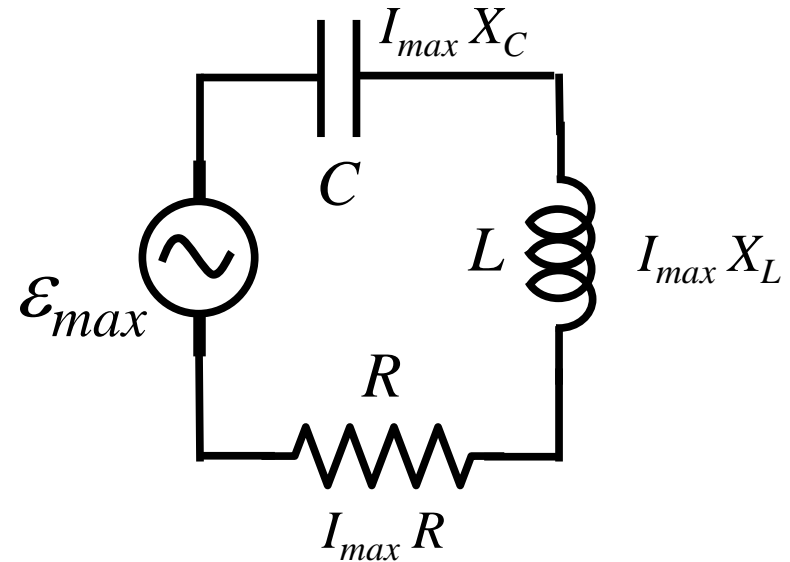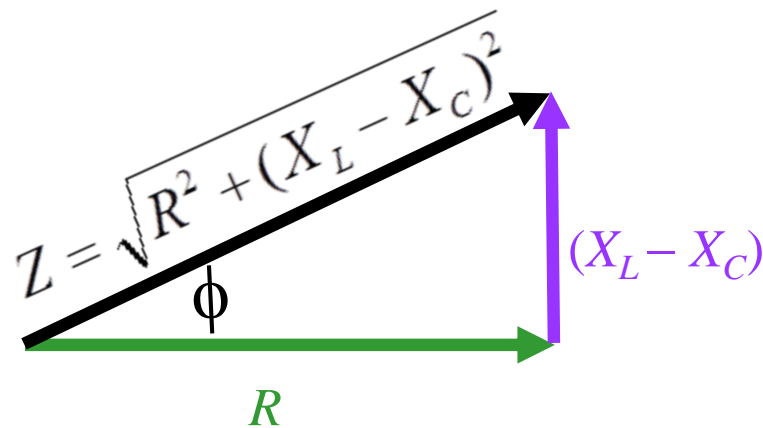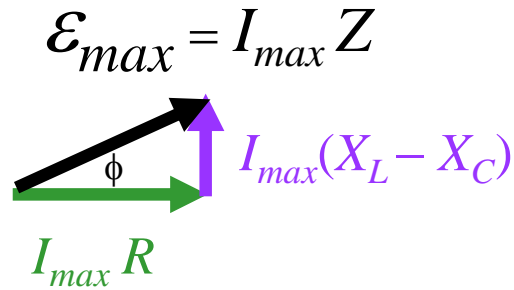

Impedance Triangle

$$\tan(\phi) = \frac{X_L - X_C}{R}$$

Summary

$$V_{Cmax} = I_{max} X_C$$

$$V_{Lmax} = I_{max} X_L$$



$$V_{Rmax} = I_{max} R$$

$$\mathcal{E}_{max} = I_{max} Z$$



$$I_{max} = \mathcal{E}_{max} / Z$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$\tan(\phi) = \frac{X_L - X_C}{R}$$

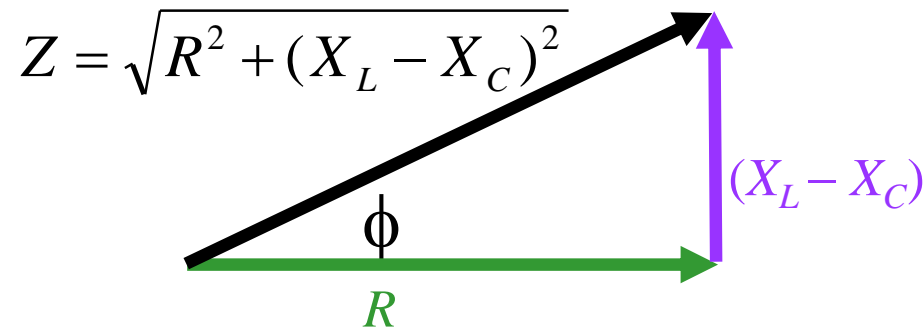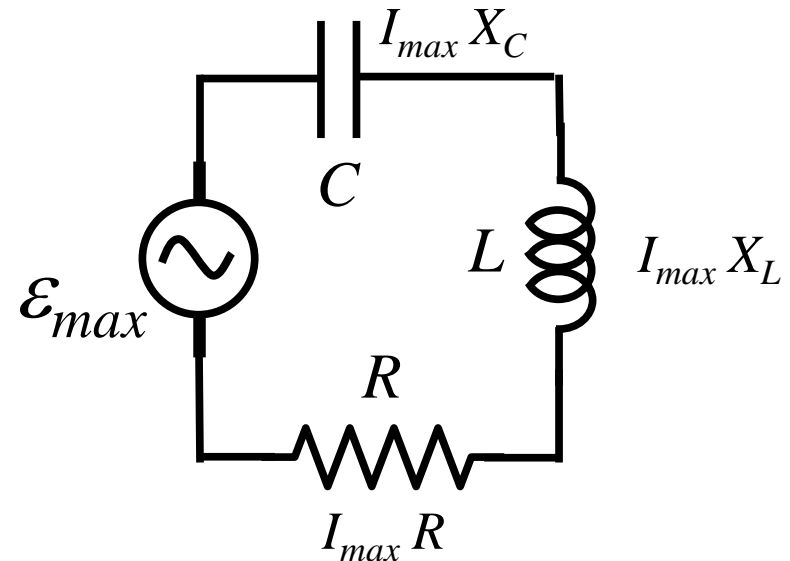


Example: RL Circuit $X_c = 0$

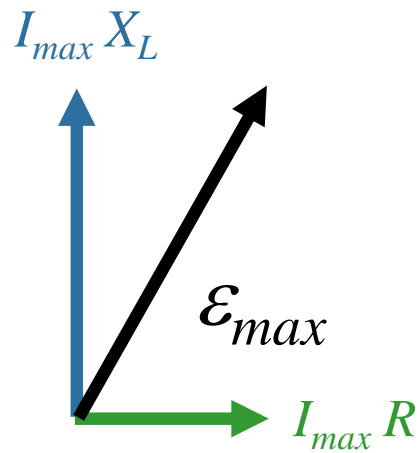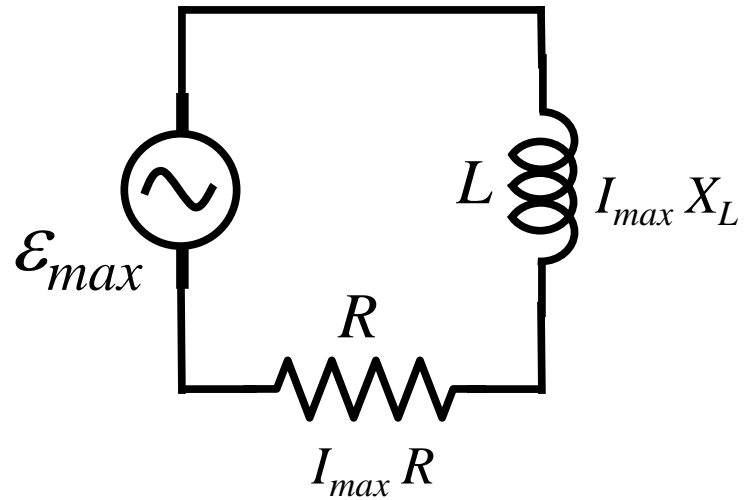


CheckPoint 1a



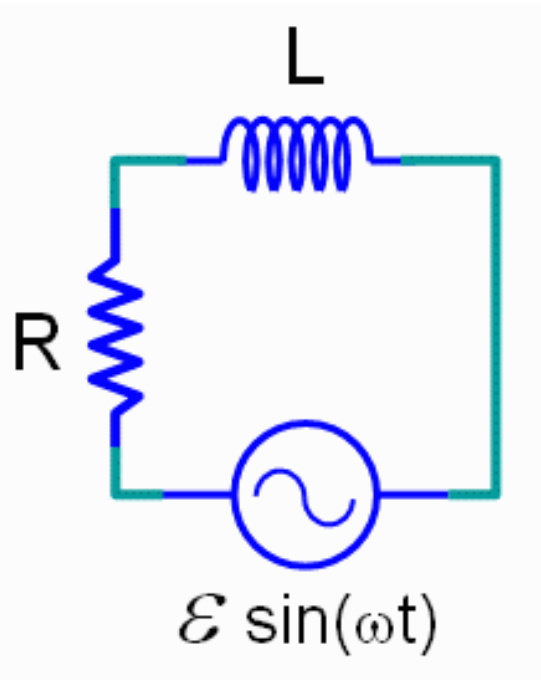2) A RL circuit is driven by an AC generator as shown in the figure.




Draw Voltage Phasors

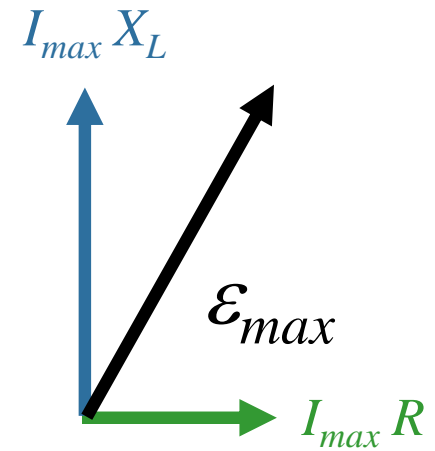

The voltages across the resistor and generator are


- A)** Always out of phase
- B)** Always in phase
- C)** Sometimes in and sometimes out of phase

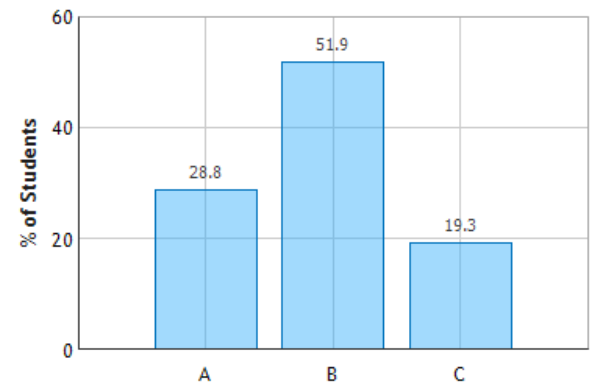


CheckPoint 1b



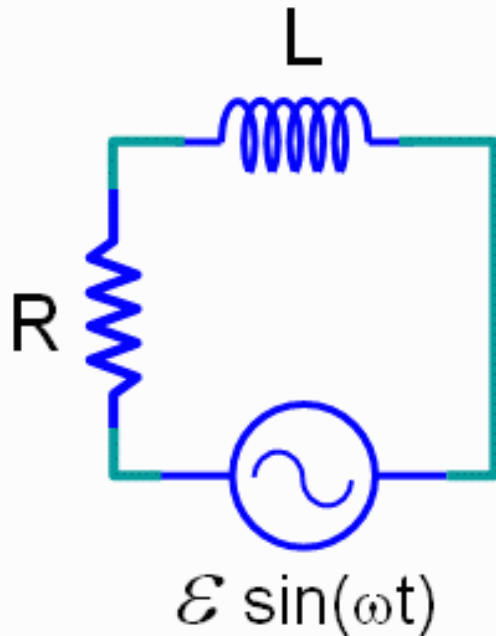A RL circuit is driven by an AC generator as shown in the figure.




Draw Voltage Phasors

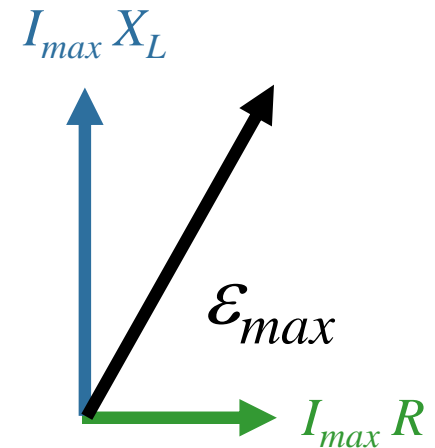

The voltages across the resistor and inductor are




- A)** Always out of phase
- B)** Always in phase
- C)** Sometimes in and sometimes out of phase

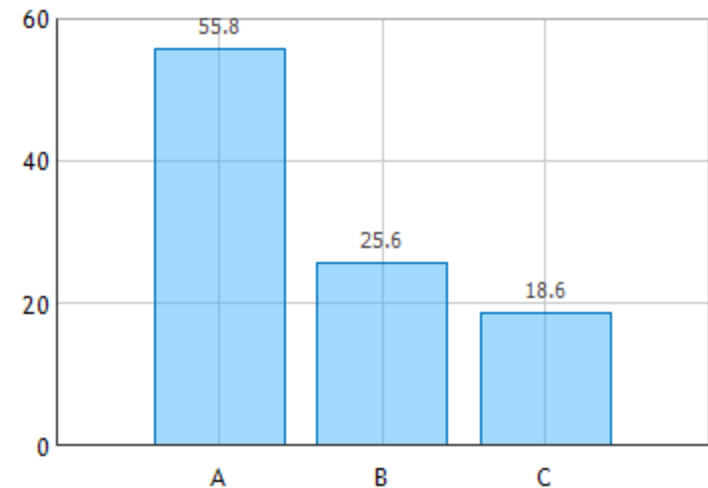

CheckPoint 2a



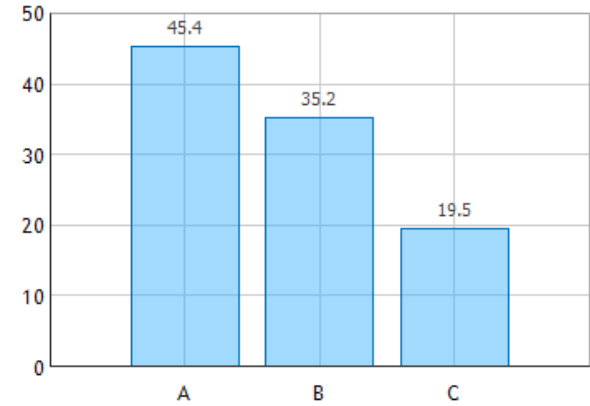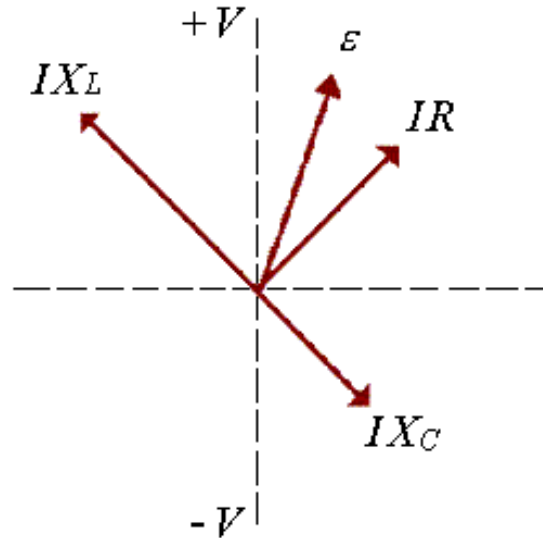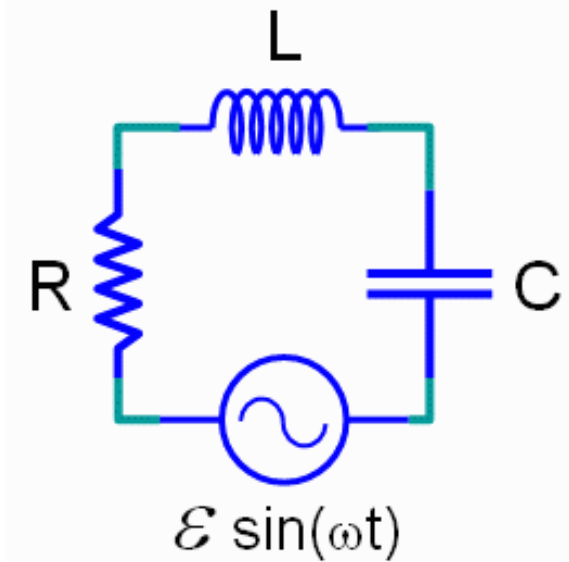A driven RLC circuit is represented by the phasor diagram below.




The vertical axis of the phasor diagram represents voltage. When the current through the circuit is maximum, what is the potential difference across the inductor?

A) $V_L = 0$

B) $V_L = V_{L,max}/2$

C) $V_L = V_{L,max}$




What does the voltage phasor diagram look like when the current is a maximum?

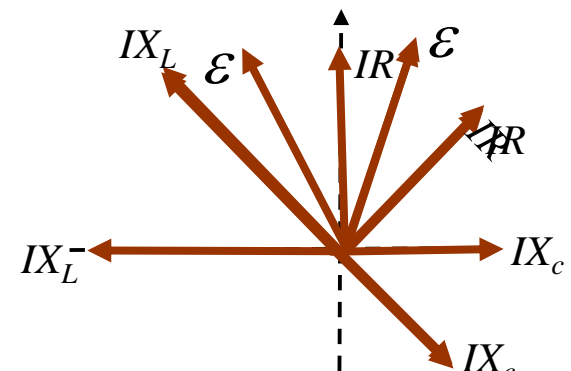

CheckPoint 2b



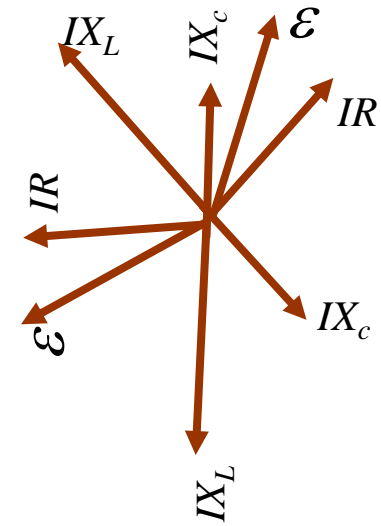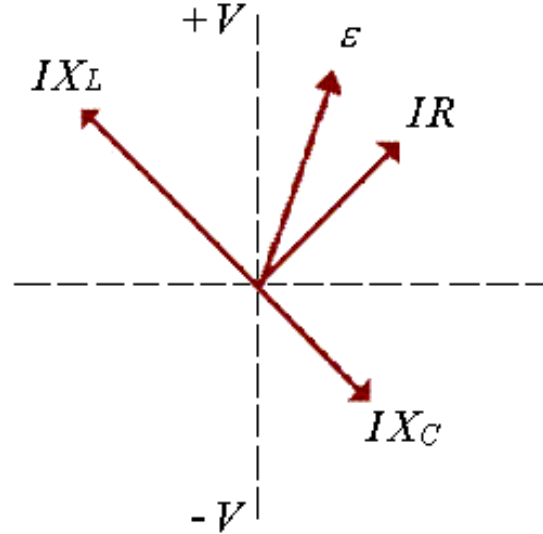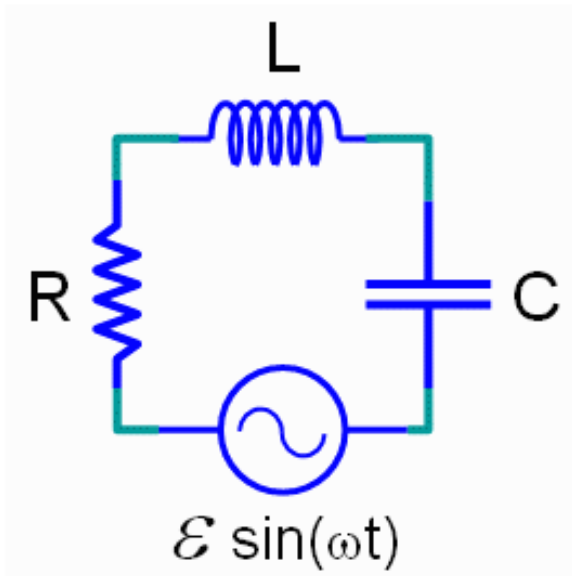A driven RLC circuit is represented by the phasor diagram below.




When the capacitor is fully charged, what is the magnitude of the voltage across the inductor?

A) $V_L = 0$

B) $V_L = V_{L,max}/2$




C) $V_L = V_{L,max}$

What does the voltage phasor diagram look like when the capacitor is fully charged?

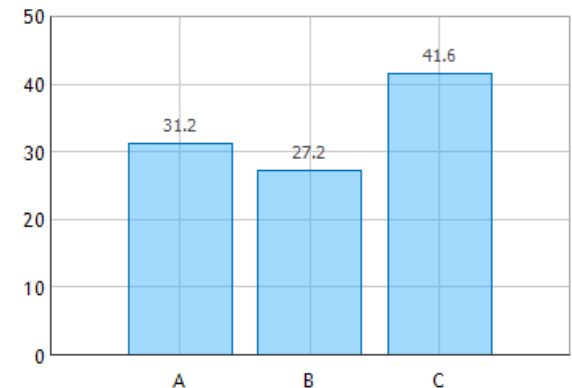

CheckPoint 2C

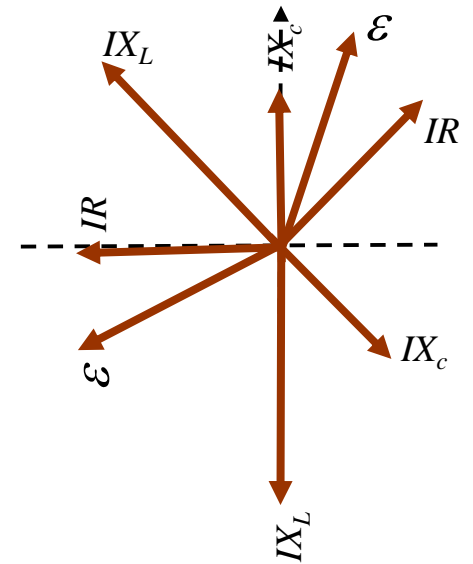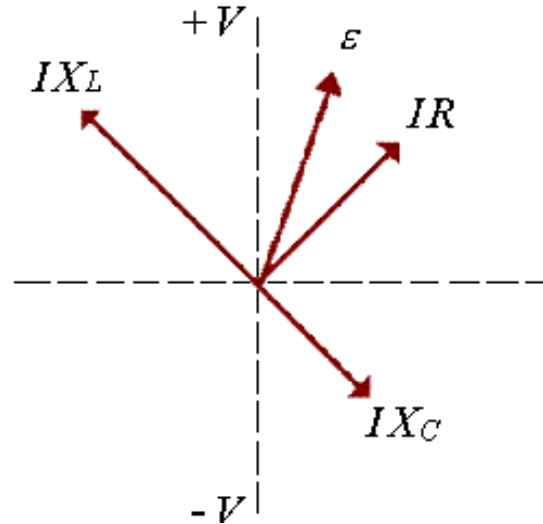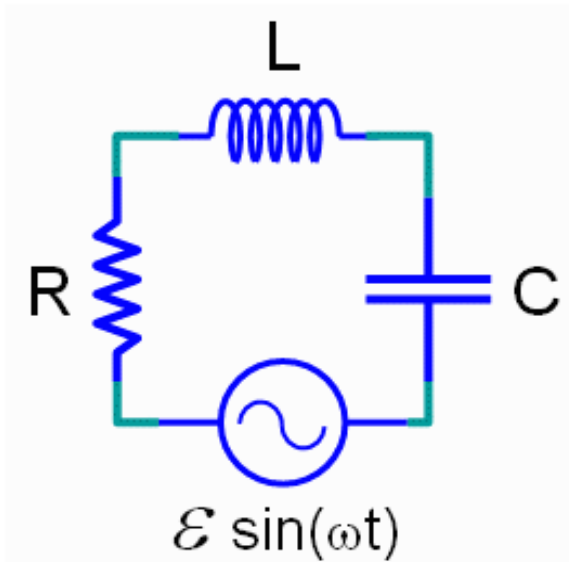A driven RLC circuit is represented by the phasor diagram below.




When the voltage across the capacitor is at its positive maximum, $V_C = +V_{C,max}$, what is the voltage across the inductor?

A) $V_L = 0$

B) $V_L = V_{L,max}$

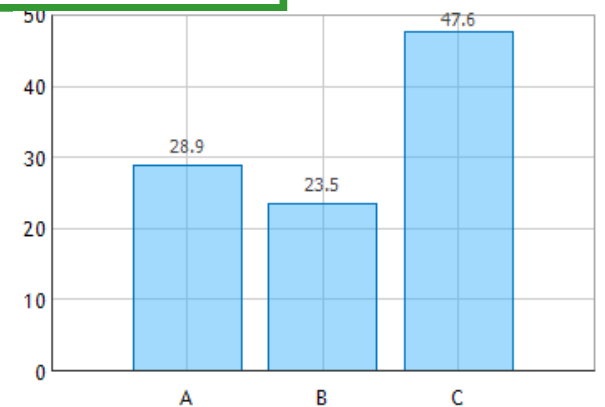C) $V_L = -V_{L,max}$

What does the voltage phasor diagram look like when the voltage across capacitor is at its positive maximum?



Calculation

Consider the harmonically driven series *LCR* circuit shown.

$$V_{max} = 100 \text{ V}$$


$$I_{max} = 2 \text{ mA}$$

$$V_{Cmax} = 113 \text{ V}$$

The current leads generator voltage by 45°

L and *R* are unknown.

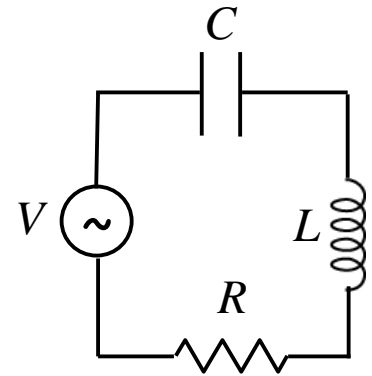What is X_L , the reactance of the inductor, at this frequency?



Conceptual Analysis

The maximum voltage for each component is related to its reactance and to the maximum current.

The impedance triangle determines the relationship between the maximum voltages for the components

Strategic Analysis

Use V_{max} and I_{max} to determine Z

Use impedance triangle to determine R

Use V_{Cmax} and impedance triangle to determine X_L

Calculation



Consider the harmonically driven series *LCR* circuit shown.


$$V_{max} = 100 \text{ V}$$

$$I_{max} = 2 \text{ mA}$$

$$V_{Cmax} = 113 \text{ V}$$

The current leads generator voltage by 45°

L and *R* are unknown.

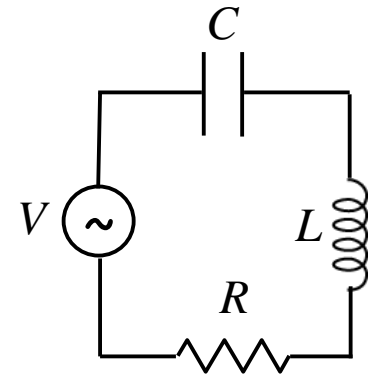

What is X_L , the reactance of the inductor, at this frequency?

Compare X_L and X_C at this frequency:

A) $X_L < X_C$



B) $X_L = X_C$

C) $X_L > X_C$

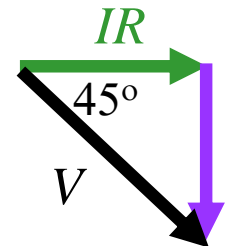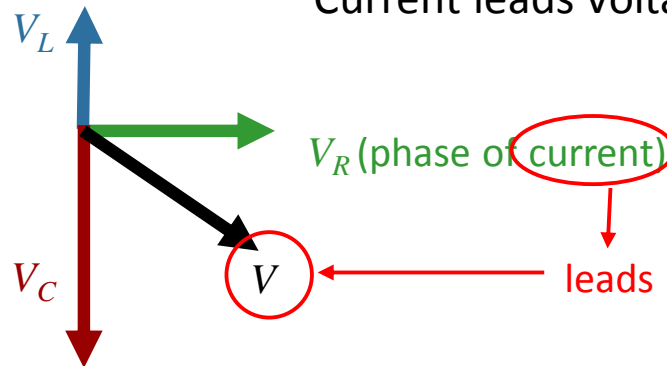D) Not enough information

This information is determined from the phase
Current leads voltage

$$V_L = I_{max} X_L$$
$$V_C = I_{max} X_C$$



Calculation



Consider the harmonically driven series *LCR* circuit shown.

$$V_{max} = 100 \text{ V}$$

$$I_{max} = 2 \text{ mA}$$

$$V_{Cmax} = 113 \text{ V}$$

The current leads generator voltage by 45°

L and *R* are unknown.

What is X_L , the reactance of the inductor, at this frequency?


What is *Z*, the total impedance of the circuit?

A) 70.7 k Ω

B) 50 k Ω

C) 35.4 k Ω

D) 21.1 k Ω

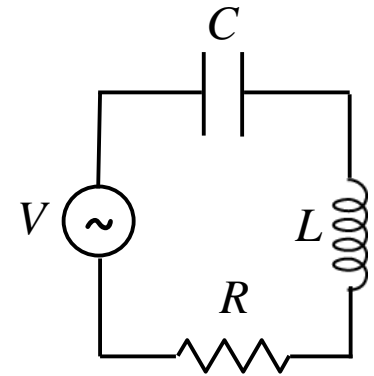

$$Z = \frac{V_{max}}{I_{max}} = \frac{100V}{2mA} = 50k\Omega$$

Calculation



Consider the harmonically driven series *LCR* circuit shown.

$$V_{max} = 100 \text{ V}$$


$$I_{max} = 2 \text{ mA}$$

$$V_{Cmax} = 113 \text{ V}$$

The current leads generator voltage by 45°

L and *R* are unknown.

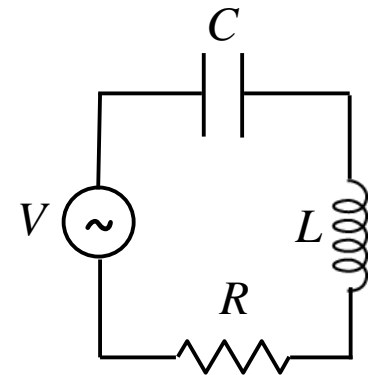What is X_L , the reactance of the inductor, at this frequency?



$$Z = 50 \text{ k}\Omega$$

$$\sin(45) = .707$$

$$\cos(45) = .707$$

What is *R*?


A) $70.7 \text{ k}\Omega$

B) $50 \text{ k}\Omega$

C) $35.4 \text{ k}\Omega$

D) $21.1 \text{ k}\Omega$

Determined from impedance triangle

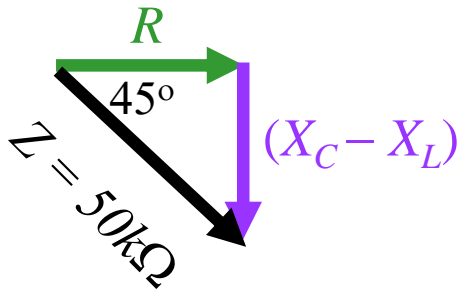

$$\cos(45) = \frac{R}{Z}$$



$$R = Z \cos(45^\circ)$$

$$= 50 \text{ k}\Omega \times 0.707$$

$$= 35.4 \text{ k}\Omega$$

Calculation



Consider the harmonically driven series *LCR* circuit shown.

$$V_{max} = 100 \text{ V}$$


$$I_{max} = 2 \text{ mA}$$

$$V_{Cmax} = 113 \text{ V}$$

The current leads generator voltage by 45°

L and *R* are unknown.

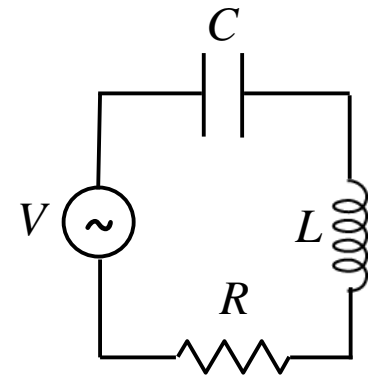What is X_L , the reactance of the inductor, at this frequency?



$$Z = 50 \text{ k}\Omega$$

$$R = 35.4 \text{ k}\Omega$$


A) $70.7 \text{ k}\Omega$

B) $50 \text{ k}\Omega$

C) $35.4 \text{ k}\Omega$

D) $21.1 \text{ k}\Omega$

We start with the impedance triangle:

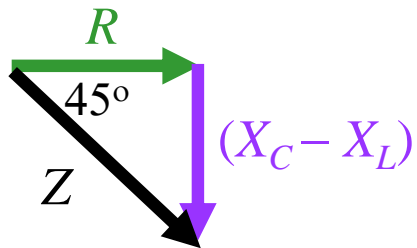

$$\frac{X_C - X_L}{R} = \tan 45^\circ = 1 \quad \rightarrow$$

$$X_L = X_C - R$$

What is X_C ?

$$V_{Cmax} = I_{max} X_C$$

$$X_C = \frac{113}{2} = 56.5 \text{ k}\Omega$$

$$X_L = 56.5 \text{ k}\Omega - 35.4 \text{ k}\Omega$$