

# Your Comments

THIS IS SOOOO HARD. I get the concept and mathematical expression. But I do not get links among everything.

Very confusing prelecture especially what happens when switches are closed/opened and what happens during long periods of time.

My brain just fell on the ground. Please help me pick it back up.

It's been a while since I have been this lost after watching a prelecture. I cannot visualize these concepts as well.

I understood what was used in the questions, but are the differential equations that they used going to be on exams? They were derived very quickly and if they're very important I would like to go over them a little more.

This lecture was not too bad. My only concern is for the challenging circuits I am sure will appear on the homework. I would like to do more problems like the those in class if that's possible.

It is difficult relating all these relationships together. Also I'm having trouble determining when something is being charged and when it is being discharged.

# *Physics 212*

## *Lecture 11*

Today's Concept:

RC Circuits

# *The 212 Differential Equations*

We describe the world (electrical circuits, problems in heat transfer, control systems, financial markets, etc.) using differential equations

You only need to know the solutions of two basic differential equations

$$\frac{dq}{dt} + \frac{1}{\tau} q = 0 \qquad q = q_{\text{const}} e^{-t/\tau}$$

---

$$\frac{d^2 q}{dt^2} + \omega^2 q = 0 \qquad q = q_{\text{const}} \sin(\omega t + \phi)$$

# Capacitors in RC Circuits

Solve by applying Kirchhoff's Rules to circuit.

Need to understand some key phrases.

**IMMEDIATELY After** === Charge on capacitor is same as immediately before

**After a LONG TIME** === Current through capacitor = 0


**After xx seconds** === *Exponentially* more difficult!

# RC Circuit (Charging)

Capacitor uncharged, Switch is moved to position “a”

## Kirchoff's Voltage Rule

$$-V_{battery} + \frac{q}{C} + IR = 0$$

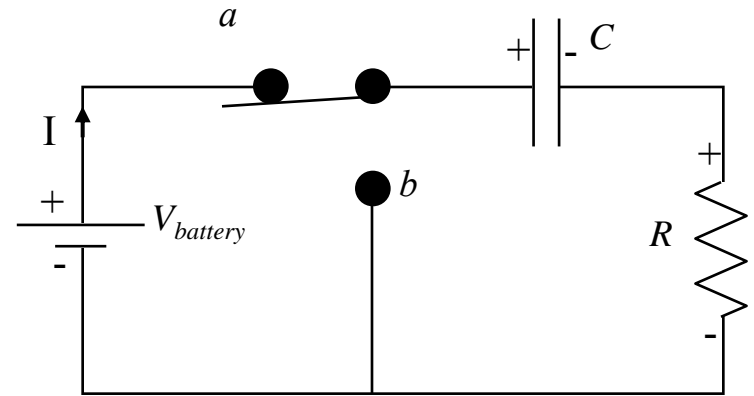

## Short Term ( $q = q_0 = 0$ )

$$-V_{battery} + 0 + I_0 R = 0$$

$$I_0 = \frac{V_{battery}}{R}$$

## Long Term ( $I_c = 0$ )

$$-V_{battery} + \frac{q_\infty}{C} + 0 \cdot R = 0$$



$$q_\infty = CV_{battery}$$

## Intermediate

$$-V_{battery} + \frac{q}{C} + \frac{dq}{dt} R = 0$$

$$q(t) = q_\infty (1 - e^{-t/RC})$$


$$I(t) = \frac{dq}{dt} = I_0 e^{-t/RC}$$

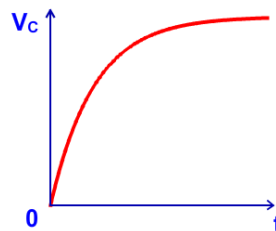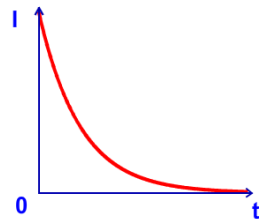
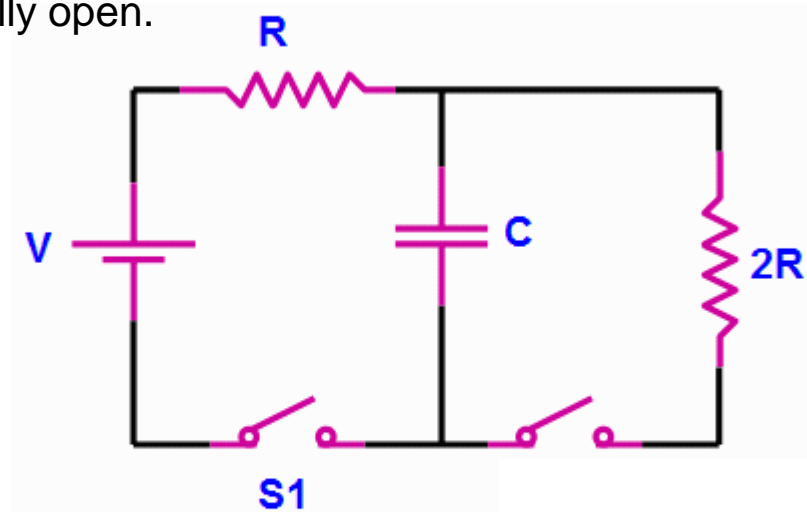
# CheckPoint 1



A circuit is wired up as shown below. The capacitor is initially uncharged and switches  $S_1$  and  $S_2$  are initially open.



Close  $S_1$ ,

$V_1$  = voltage across  $C$  immediately after

$V_2$  = voltage across  $C$  a long time after

Immediately after the  
switch  $S_1$  is closed:

A)  $V_1 = V$        $V_2 = V$

B)  $V_1 = 0$        $V_2 = V$


C)  $V_1 = 0$        $V_2 = 0$

D)  $V_1 = V$        $V_2 = 0$


After the switch  $S_1$  has been  
closed for a long time

$Q$  is same as immediately before


$$I_C = 0$$

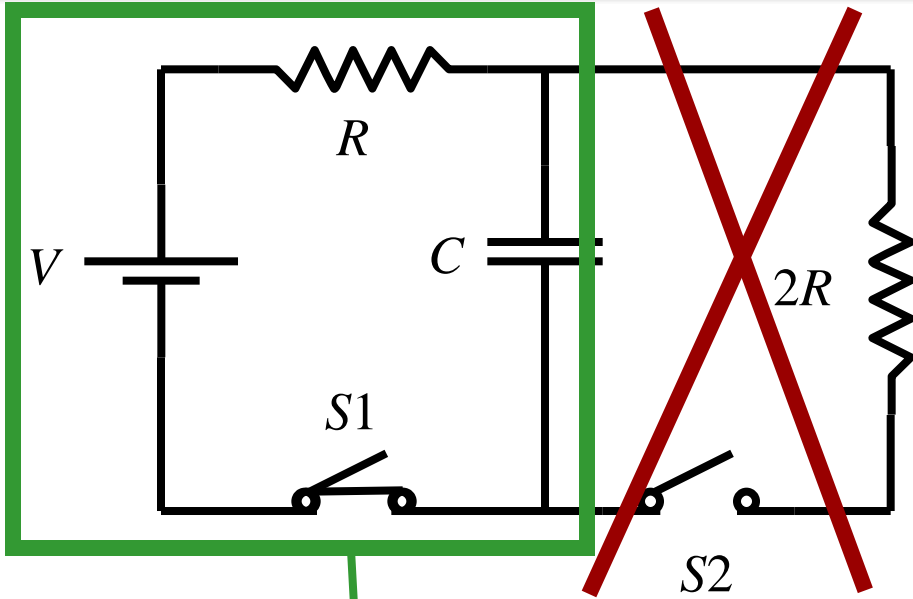

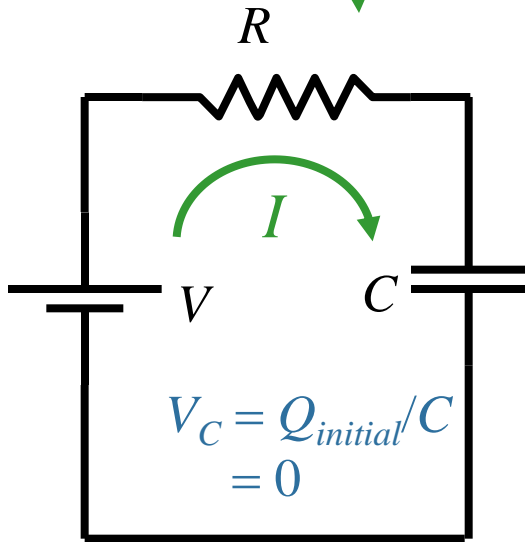
Close  $S_1$  at  $t = 0$   
(leave  $S_2$  open)



At  $t = 0$

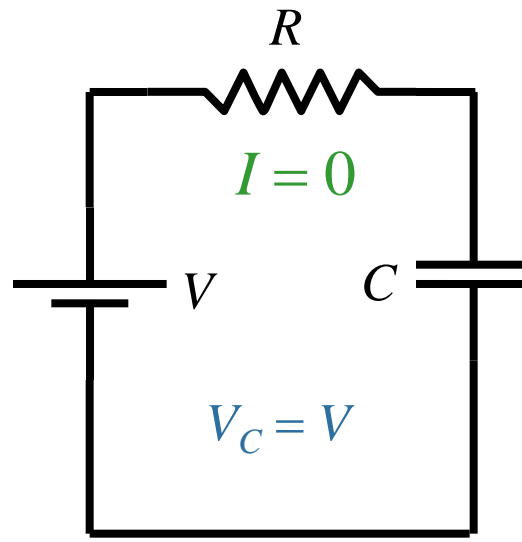


At  $t = \text{big}$

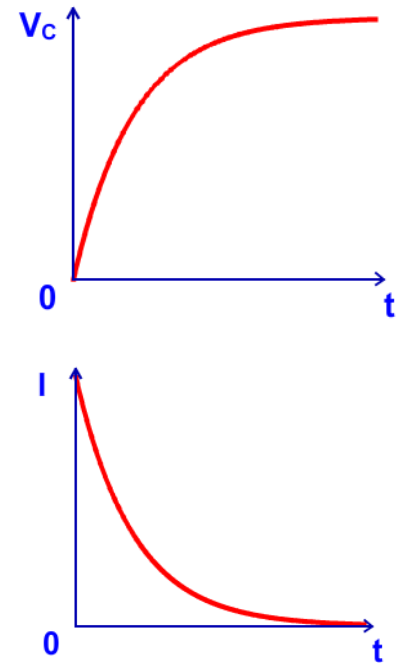
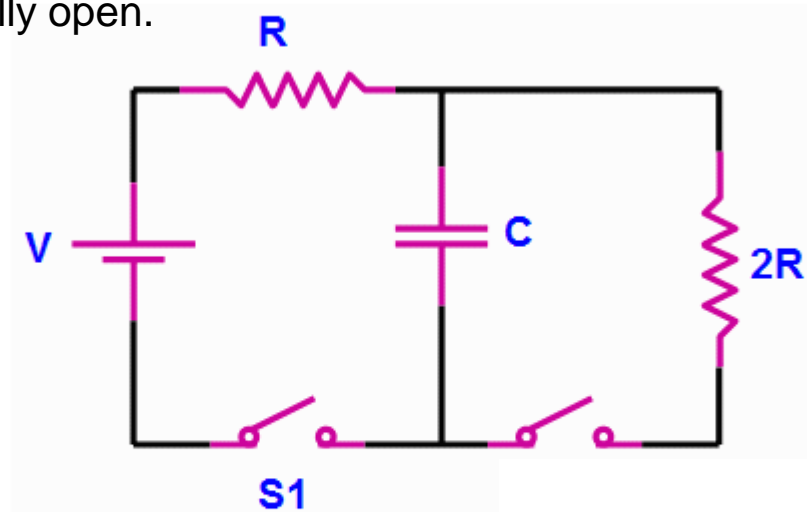
# CheckPoint 1



A circuit is wired up as shown below. The capacitor is initially uncharged and switches  $S_1$  and  $S_2$  are initially open.



Close  $S_1$ ,

$V_1$  = voltage across  $C$  immediately after

$V_2$  = voltage across  $C$  a long time after

Immediately after the  
switch  $S_1$  is closed:

$Q$  is same as immediately before

A)  $V_1 = V$        $V_2 = V$

B)  $V_1 = 0$        $V_2 = V$

C)  $V_1 = 0$        $V_2 = 0$

D)  $V_1 = V$        $V_2 = 0$

After the switch  $S_1$  has been  
closed for a long time

$$I_C = 0$$



# RC Circuit (Discharging)

Capacitor has  $q_0 = CV_{battery}$ , Switch is moved to position “b”

## Kirchoff's Voltage Rule

$$+\frac{q}{C} + IR = 0$$


## Short Term ( $q = q_0$ )

$$V_{battery} + IR = 0$$

$$I_0 = \frac{-V_{battery}}{R}$$
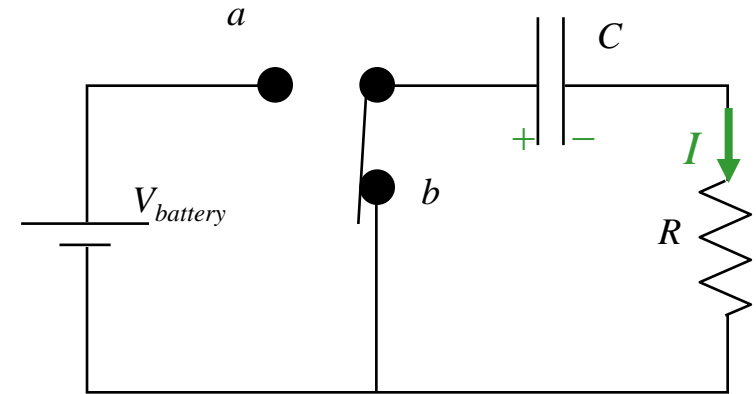
## Long Term ( $I_c = 0$ )

$$\frac{q_\infty}{C} + 0 \cdot R = 0$$
$$q_\infty = 0$$





## Intermediate

$$+\frac{q}{C} + \frac{dq}{dt} R = 0$$

$$q(t) = q_0 e^{-t/RC}$$


$$I(t) = I_0 e^{-t/RC}$$

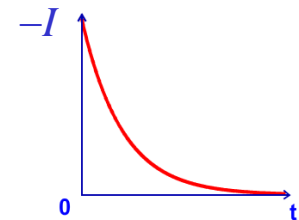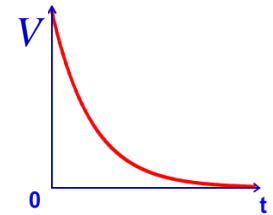
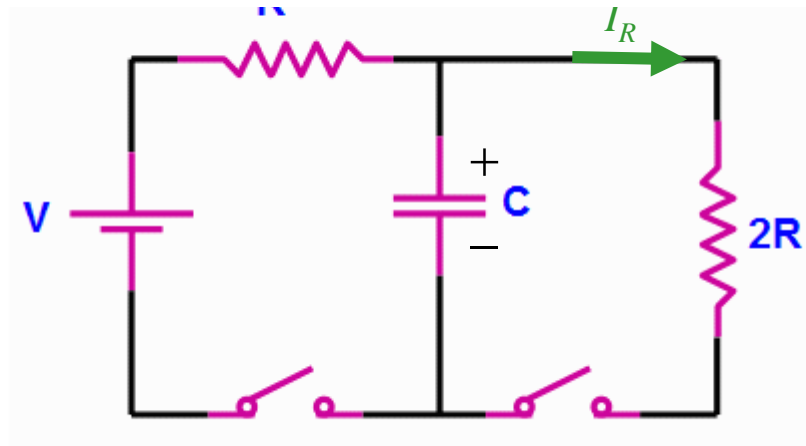
# CheckPoint 1c



A circuit is wired up as shown below. The capacitor is initially uncharged and switches S1 and S2 are initially open.






After being closed a long time, switch 1 is opened and switch 2 is closed. What is the current through the right resistor immediately after switch 2 is closed?

**A.**  $I_R = 0$


**B.**  $I_R = V/3R$

**C.**  $I_R = V/2R$


**D.**  $I_R = V/R$

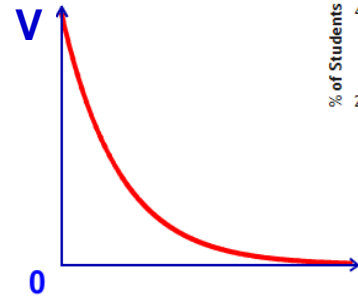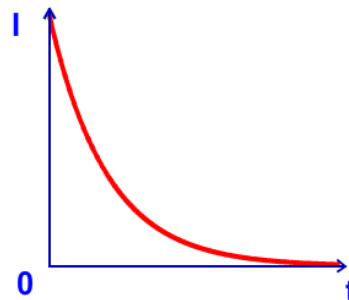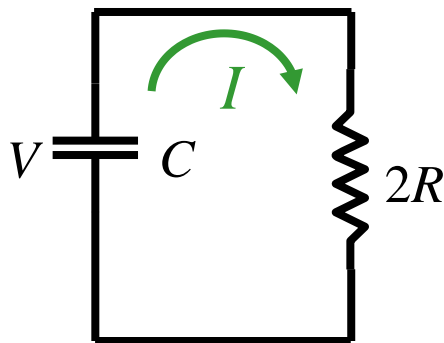

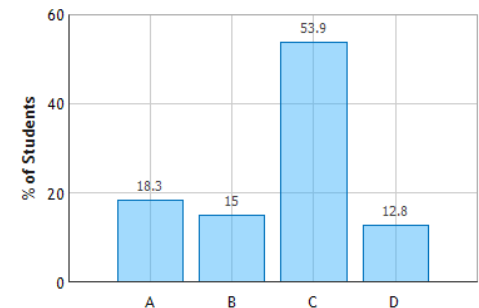Two Loop RC Circuit: Question 5 (N = 859)




# CheckPoint 1 d

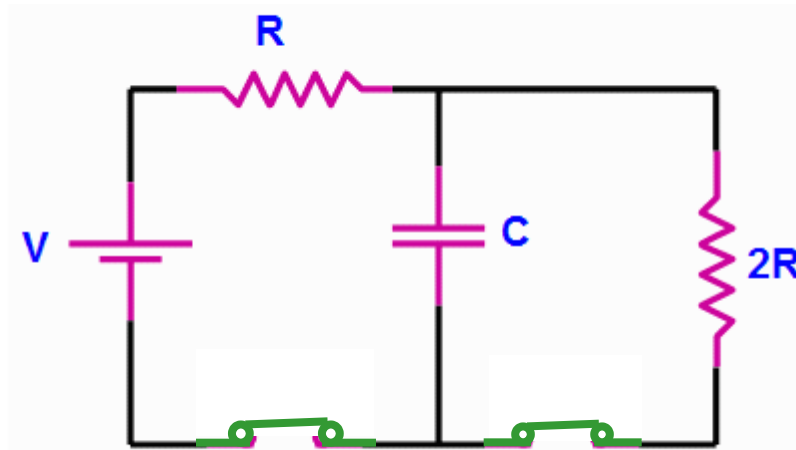


Now suppose both switches are closed. What is the voltage across the capacitor after a very long time?

- A.**  $V_C = 0$       **B.**  $V_C = V$       **C.**  $V_C = 2V/3$

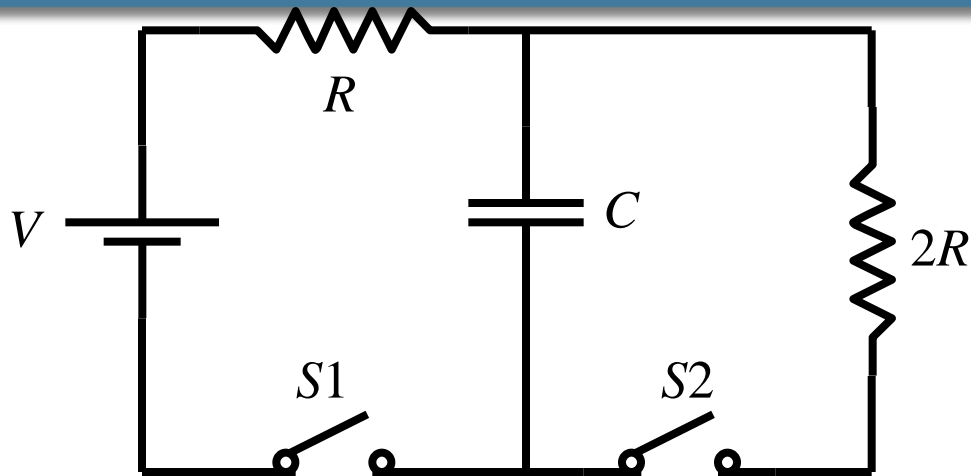- A) The capacitor would discharge completely as  $t$  approaches infinity  
B) The capacitor will become fully charged after a long time.  
C) Current through capacitor is zero



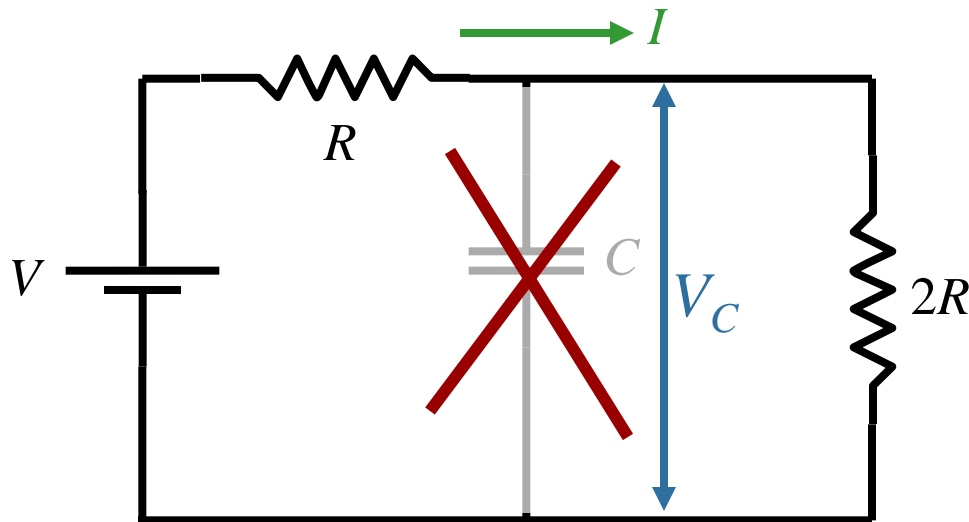Close both  $S1$  and  $S2$  and wait a long time...




No current flows through the capacitor after a long time. **This will always be the case in any static circuit!!**

Outer Loop  
 $IR + 2IR - V = 0$   
 $I = V/(3R)$

Right Loop  
 $+V_C - 2IR = 0$   
 $V_C = 2IR$

→  $V_C = (2/3)V$

# CheckPoint 1 d

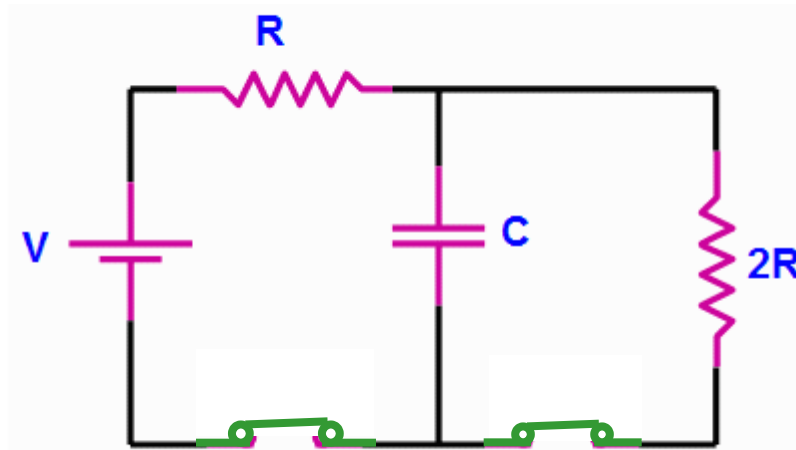

Now suppose both switches are closed. What is the voltage across the capacitor after a very long time?

**A.**  $V_C = 0$

**B.**  $V_C = V$


**C.**  $V_C = 2V/3$

a) The capacitor would discharge completely as  $t$  approaches infinity


b) The capacitor will become fully charged after a long time.

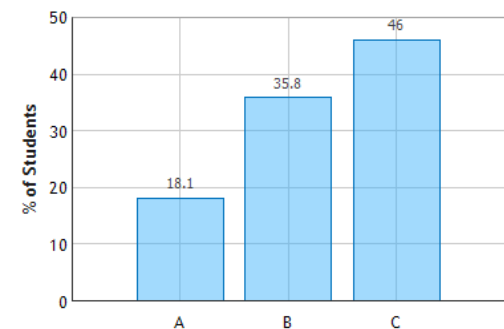c) Current through capacitor is zero

Two Loop RC Circuit: Question 7 (N = 860)



# DEMO - Clicker Question 1

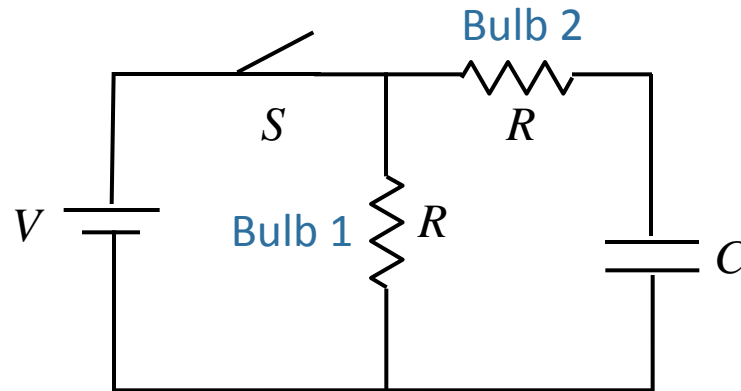

What will happen after I close the switch?

- A) Both bulbs come on and stay on.
- B) Both bulbs come on but then bulb 2 fades out.**
- C) Both bulbs come on but then bulb 1 fades out.
- D) Both bulbs come on and then both fade out.

No initial charge  
on capacitor



$$V(\text{bulb 1}) = V(\text{bulb 2}) = V$$




Both bulbs light

No final current  
through capacitor



$$V(\text{bulb 2}) = 0$$

# DEMO Clicker Question 2

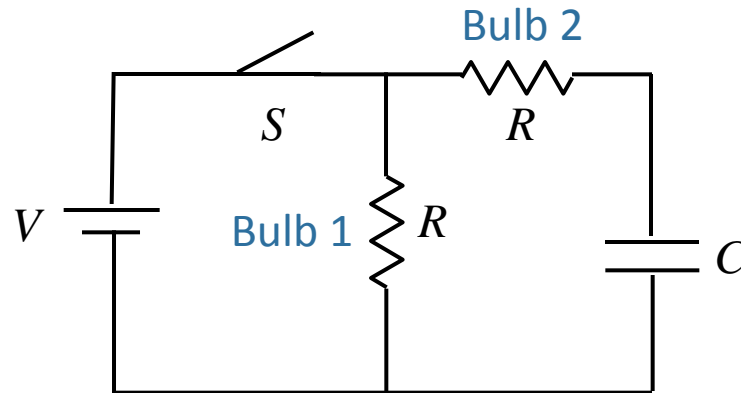


Suppose the switch has been closed a long time.  
Now what will happen after open the switch?

- A) Both bulbs come on and stay on.
- B) Both bulbs come on but then bulb 2 fades out.
- C) Both bulbs come on but then bulb 1 fades out.
- D) Both bulbs come on and then both fade out.

Capacitor has charge ( $=CV$ )  Capacitor discharges through both resistors

# Calculation

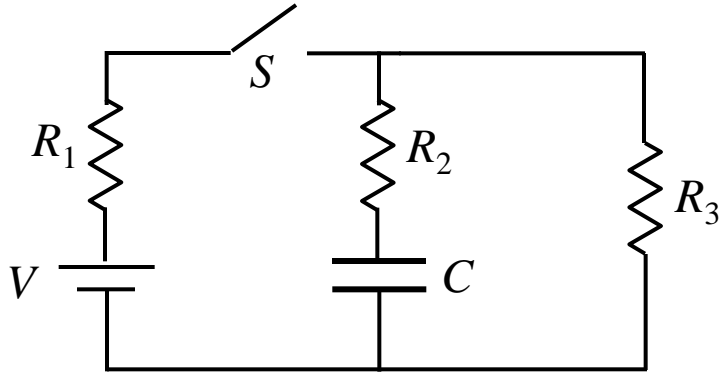

In this circuit, assume  $V$ ,  $C$ , and  $R_i$  are known.  
 $C$  initially uncharged and then switch  $S$  is closed.

What is the voltage across the capacitor after a long time ?

## Conceptual Analysis:

Circuit behavior described by Kirchhoff's Rules:

$$\sum V_{drops} = 0$$

$$\sum I_{in} = \sum I_{out}$$


$S$  closed and  $C$  charges to some voltage with some time constant

## Strategic Analysis

Determine currents and voltages in circuit a long time after  $S$  closed



# Calculation

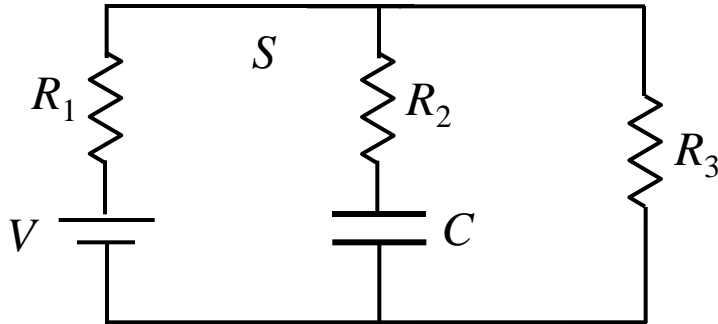

In this circuit, assume  $V$ ,  $C$ , and  $R_i$  are known.  
 $C$  initially uncharged and then switch  $S$  is closed.

What is the voltage across the capacitor after a long time ?

Immediately after  $S$  is closed:

what is  $I_2$ , the current through  $C$

what is  $V_C$ , the voltage across  $C$ ?


- A) Only  $I_2 = 0$    **B) Only  $V_C = 0$**    C) Both  $I_2$  and  $V_C = 0$    D) Neither  $I_2$  nor  $V_C = 0$

Why?

We are told that  $C$  is initially uncharged ( $V = Q/C$ )

$I_2$  cannot be zero because charge must flow in order to charge  $C$

# Calculation

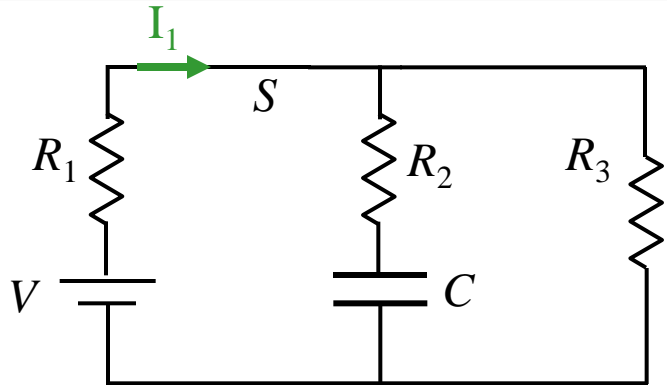

In this circuit, assume  $V$ ,  $C$ , and  $R_i$  are known.  
 $C$  initially uncharged and then switch  $S$  is closed.

What is the voltage across the capacitor after a long time ?

Immediately after  $S$  is closed, what is  $I_1$ , the current through  $R_1$  ?

$$\frac{V}{R_1}$$

A

$$\frac{V}{R_1 + R_3}$$

B

$$\frac{V}{R_1 + R_2 + R_3}$$

C

$$\frac{V}{R_1 + \frac{R_2 R_3}{R_2 + R_3}}$$

D


$$V \frac{R_1 + R_2 + R_3}{R_1 R_2 + R_2 R_3 + R_1 R_3}$$

E


Why?

Draw circuit just after  $S$  closed (knowing  $V_C = 0$ )

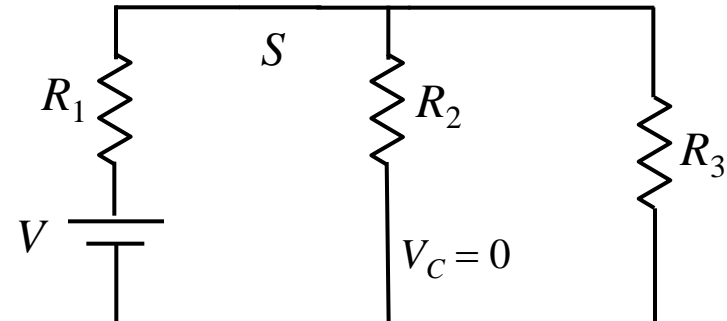$R_1$  is in series with the parallel combination of  $R_2$  and  $R_3$



# Calculation

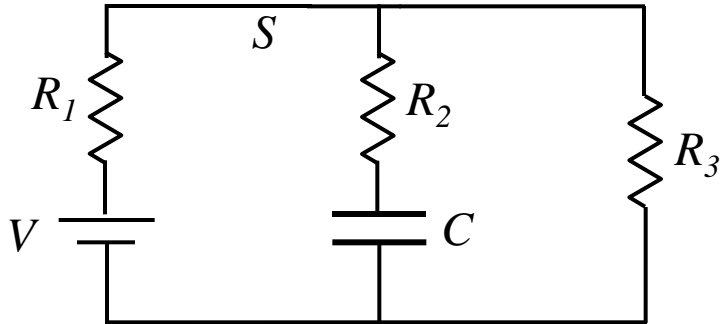

In this circuit, assume  $V$ ,  $C$ , and  $R_i$  are known.  
 $C$  initially uncharged and then switch  $S$  is closed.

What is the voltage across the capacitor after a long time ?

After  $S$  has been closed “for a long time”, what is  $I_2$ , the current through  $R_2$  ?

$$\frac{V}{R_2}$$

A

$$\frac{V}{R_1}$$

B


$$0$$

C


Why?

After a long time in a static circuit, the current through any capacitor approaches 0 !

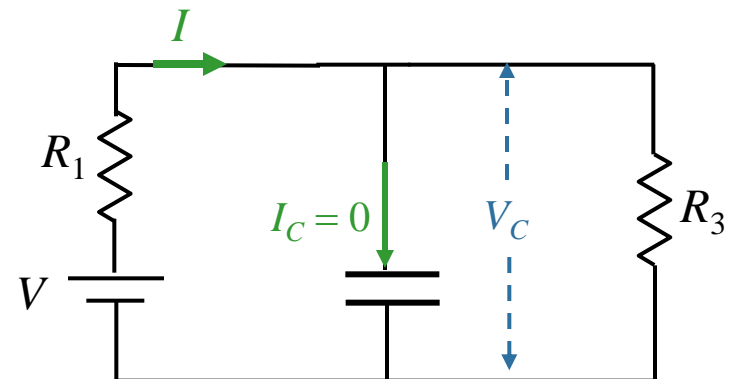This means we Redraw circuit with open circuit in middle leg



# Calculation

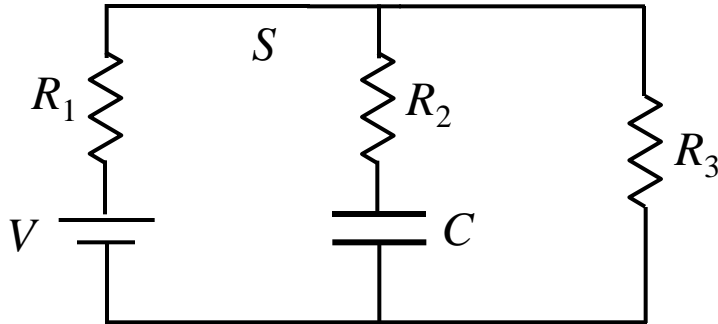

In this circuit, assume  $V$ ,  $C$ , and  $R_i$  are known.  
 $C$  initially uncharged and then switch  $S$  is closed.

What is the voltage across the capacitor after a long time ?

After  $S$  has been closed “for a long time”, what is  $V_C$ , the voltage across  $C$  ?

$$V \frac{R_3}{R_1 + R_3}$$

A

$$V \frac{R_2}{R_1 + R_2}$$

B

$$V$$

C

$$V \frac{R_2}{R_1 + \frac{R_2 R_3}{R_2 + R_3}}$$


D

$$0$$

E

Why?

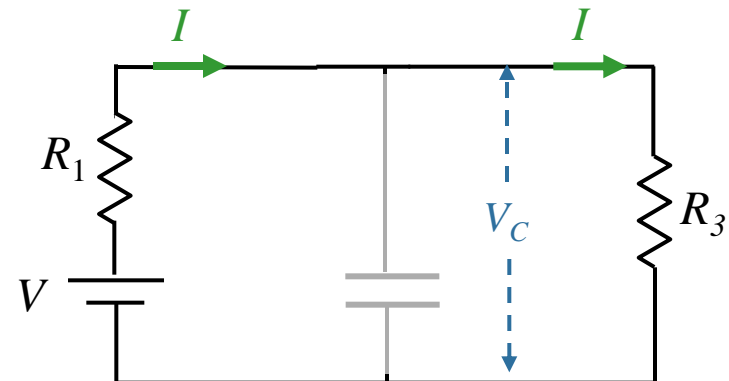
$$- V_C = V_3 = IR_3 = (V/(R_1 + R_3))R_3$$




# CheckPoint 2



The two circuits shown below contain identical capacitors that hold the same charge at  $t = 0$ . Circuit 2 has twice as much resistance as circuit 1.

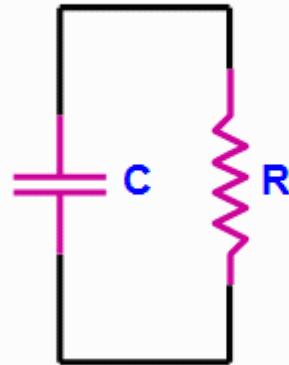

Circuit 1

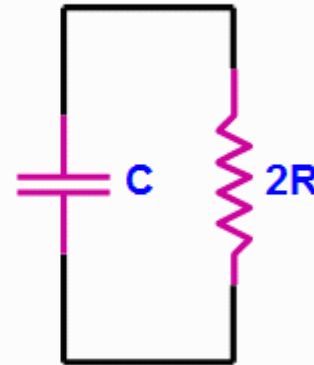

Circuit 2



Which circuit has the largest time constant?

A) Circuit 1

B) Circuit 2

C) Same

$$\tau = R_{equiv} C$$

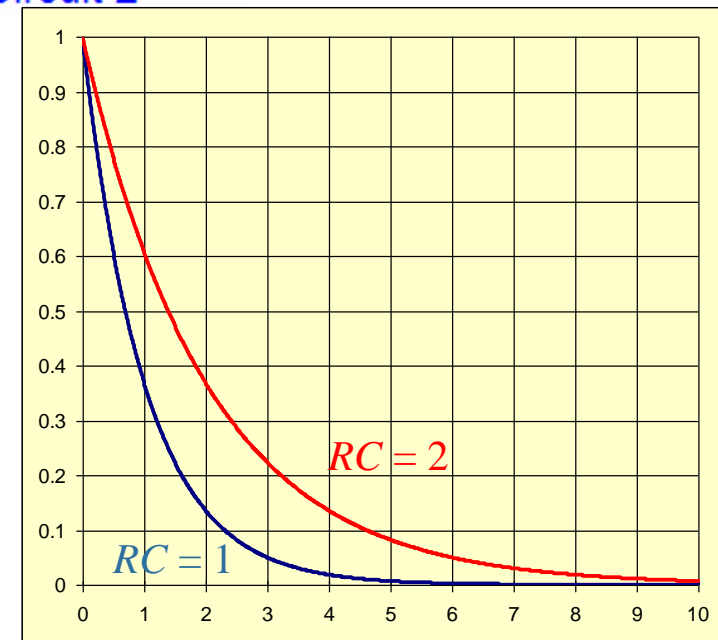
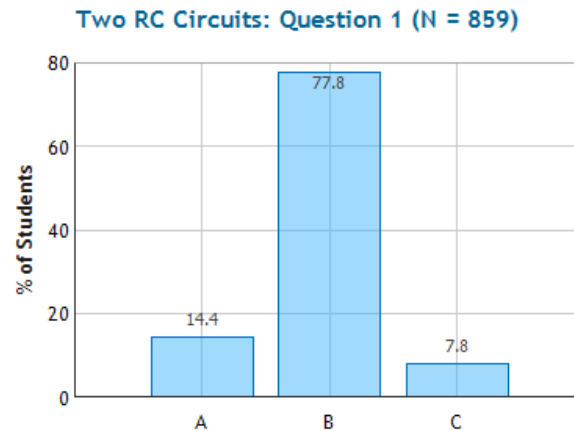


# CheckPoint 2




The two circuits shown below contain identical capacitors that hold the same charge at  $t = 0$ . Circuit 2 has twice as much resistance as circuit 1.

Two RC Circuits: Question 3 (N = 858)

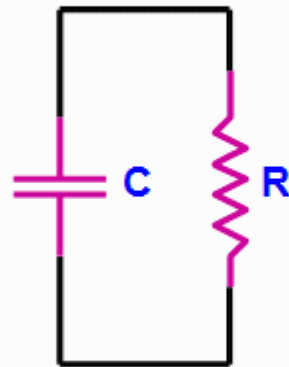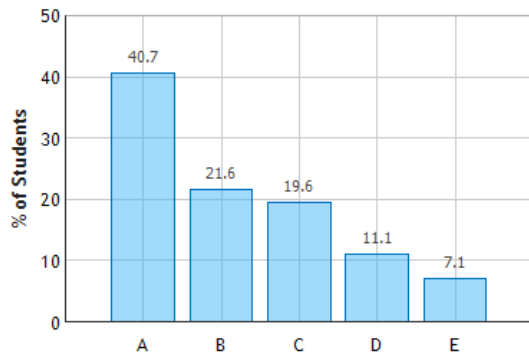

Circuit 1

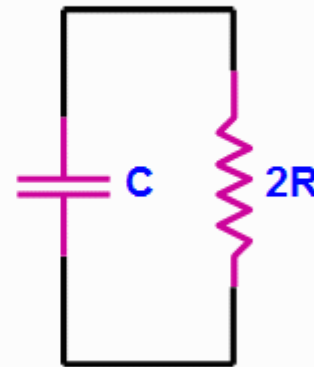

Circuit 2

Which of the following statements best describes the charge remaining on each of the two capacitors for any time after  $t = 0$ ?

- ☒  $Q_1 < Q_2$
- ☐  $Q_1 > Q_2$
- ☐  $Q_1 = Q_2$
- ☐  $Q_1 < Q_2$  at first and then  $Q_1 > Q_2$  after a long time
- ☐  $Q_1 > Q_2$  at first and then  $Q_1 < Q_2$  after a long time

$$Q = Q_0 e^{-t/RC}$$

Look at plot!

