

Your Comments

Pretty straightforward! The analogy to spring motion really helped. Is there any false comparison with it that we should watch out for?

I think I got a lot of this, the pre-lecture confused me a little bit though with the phase angle and when it called ω the oscillation frequency $= 1/\sqrt{LC}$ and then later it called that same ω the natural frequency and gave us a different equation for the oscillation frequency

Seems interesting, but my mind is on the test right now.

As soon as I heard the word "damping" my mind switched to Diff Equ. I love it when the things that I learn in one class matches up to what I learn in another class :)

Can we please have a review session tomorrow???? Spring break took a toll on all of us and it would mean so much to the student body if you guys pushed back lecture which you guys can and do a review session. Obviously you guys want everyone to do good, this review session will help everyone so much AND I can guarantee it will improve the test average. It's just one lecture and we would love you guys for doing it. If you say no to this, post this comment so you guys can see how upset the student body will be if you choose not to. Once more please!!!!!!!!!!!!!!

Come on, teacher!! Give me a break!!! Oscillations just after my amazing vacation? My brain hurts ever since the oscillatory frequency started popping into and out of the screen.

Some Exam Stuff

Exam Wed. night (April 2nd) at 7:00

- Covers material in Lectures 9 – 18
- Bring your ID: Rooms determined by discussion section (see link)

Don't forget:

- Worked examples in homeworks (the optional questions)
- Other old exams

For most people, taking old exams is most beneficial

- » Take them like real exam (calculator and formula sheet)
- » Complete full exam, then grade (harshly)
- » Review problems got wrong (why did you get it wrong)
- » Repeat

The Big Ideas L9-18

Kirchoff's Rules

- Sum of voltages around a loop is zero
- Sum of currents into a node is zero
- Kirchoff's rules with capacitors and inductors
 - In RC and RL circuits: charge and current involve exponential functions with time constant: “charging and discharging”
 - E.g. $IR + \frac{Q}{C} = V$
- Capacitors and inductors store energy

Magnetic fields

- Generated by electric currents (no magnetic charges)
- Magnetic forces only on charges in motion $\vec{F}_{mag} = q\vec{v} \times \vec{B}$
- Easiest to calculate with Ampere's Law $\oint \vec{B} \cdot d\vec{\ell} = \mu_0 I_{enclosed}$
- Changing magnetic fields can generate electric fields! FARADAY'S LAW

$$\int \vec{E} \cdot d\vec{\ell} = EMF = \Delta V = -\frac{d}{dt} \int \vec{B} \cdot d\vec{A} = -\frac{d\phi_{mag}}{dt}$$


Physics 212

Lecture 19


Today's Concepts:

- A) Oscillation Frequency
- B) Energy
- C) Damping


RLC Circuit

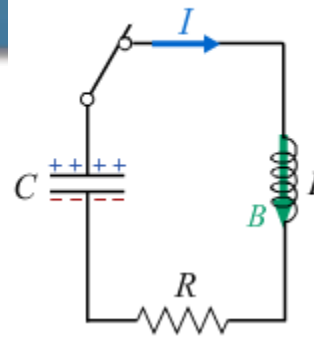

$$\beta = 0.2\omega_0$$

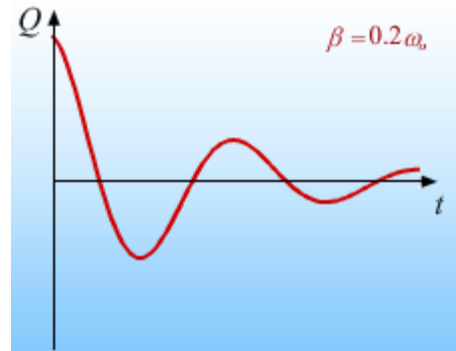

LC Circuit

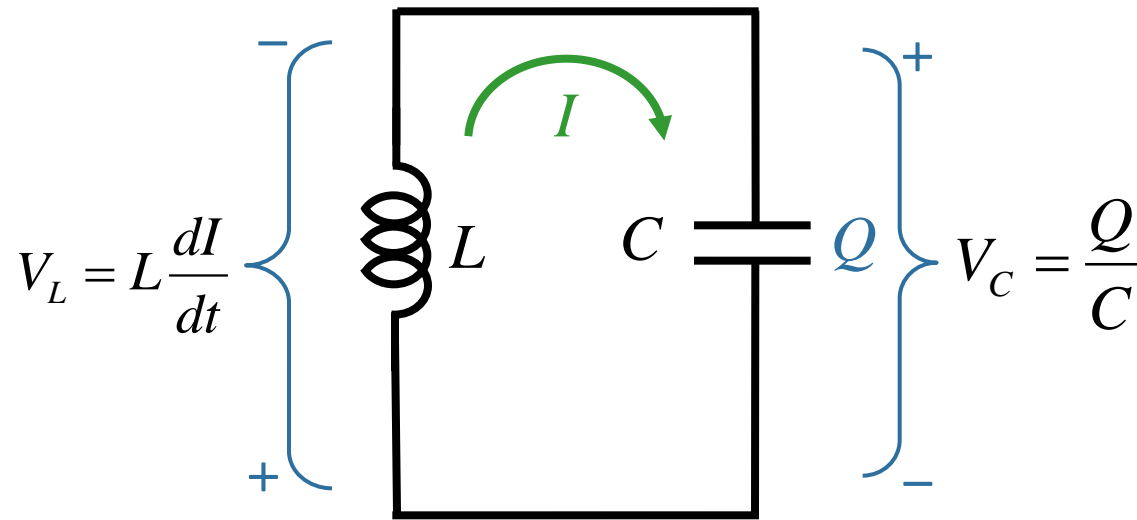

Circuit Equation: $\frac{Q}{C} + L \frac{dI}{dt} = 0$

$$I = \frac{dQ}{dt} \longrightarrow \frac{d^2Q}{dt^2} = -\frac{Q}{LC} \longrightarrow \frac{d^2Q}{dt^2} = -\omega^2 Q$$


where

$$\omega = \frac{1}{\sqrt{LC}}$$

CheckPoint 1a



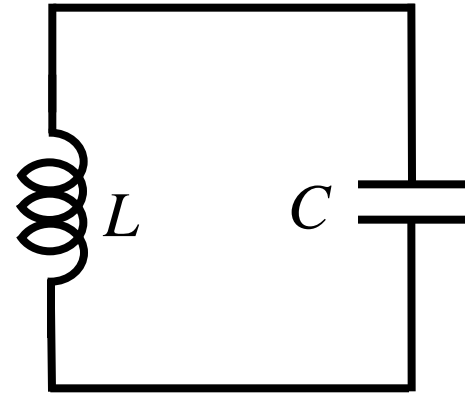At time $t = 0$ the capacitor is fully charged with Q_{max} and the current through the circuit is 0.



What is the potential difference across the inductor at $t = 0$?

A) $V_L = 0$

B) $V_L = Q_{max}/C$


C) $V_L = Q_{max}/2C$

since $V_L = V_C$

The two elements are in parallel,
so $V_L = V_C = Q/C$

Pendulum.


LC Circuit: Question 1 (N = 815)

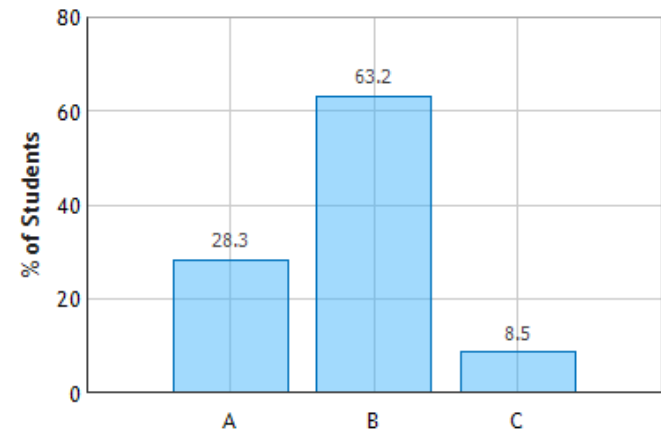

LC Circuits analogous to mass on spring


$$\frac{d^2 Q}{dt^2} = -\omega^2 Q$$

$$\omega = \frac{1}{\sqrt{LC}}$$

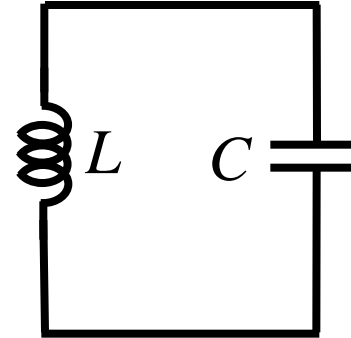

$$\frac{d^2 x}{dt^2} = -\omega^2 x$$

$$\omega = \sqrt{\frac{k}{m}}$$

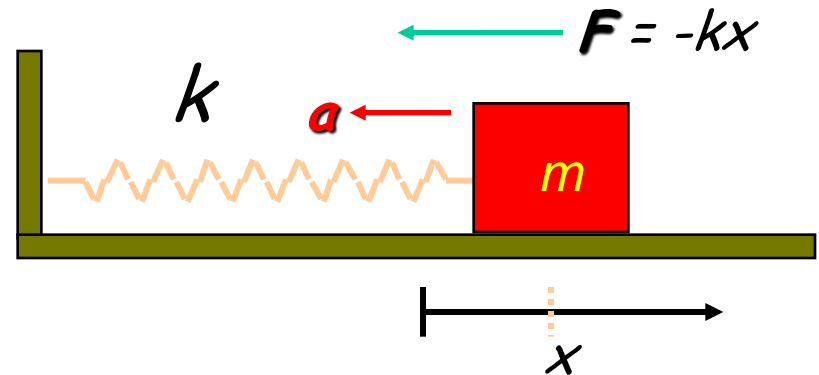



Same thing if we notice that

$$k \leftrightarrow \frac{1}{C}$$

and

$$m \leftrightarrow L$$


Time Dependence

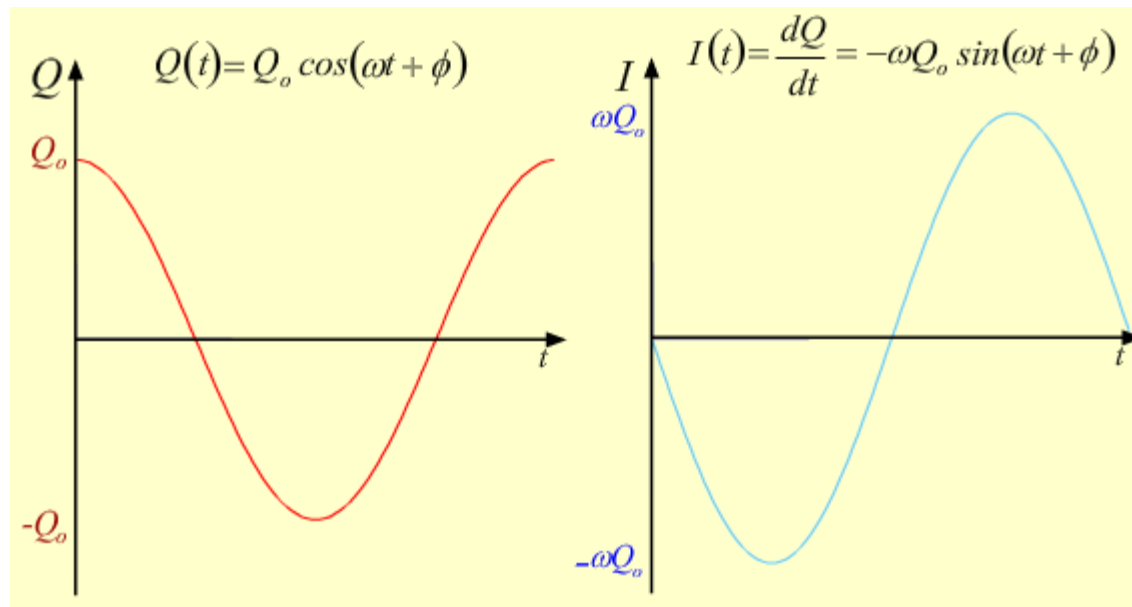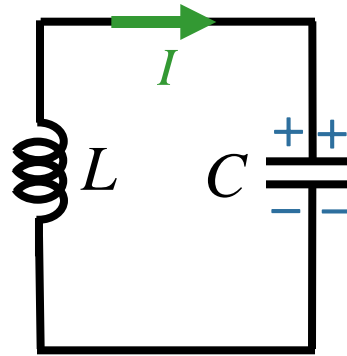

Checkpoint 1b



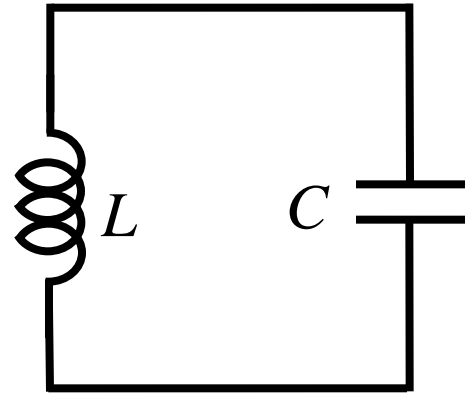At time $t = 0$ the capacitor is fully charged with Q_{max} and the current through the circuit is 0.




What is the potential difference across the inductor at when the current is maximum?

- A) $V_L = 0$
- B) $V_L = Q_{max}/C$
- C) $V_L = Q_{max}/2C$

dI/dt is zero when current is maximum


LC Circuit: Question 3 (N = 815)

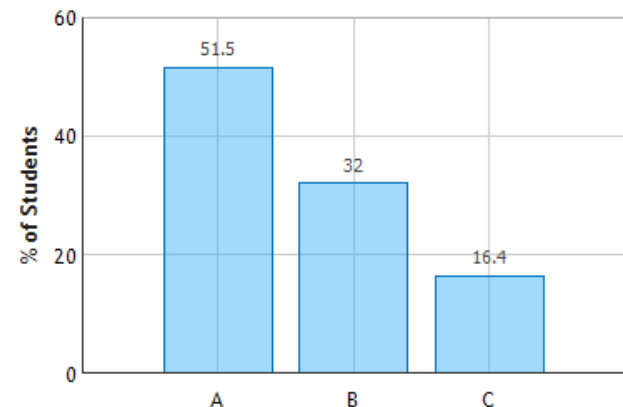

CheckPoint 1c



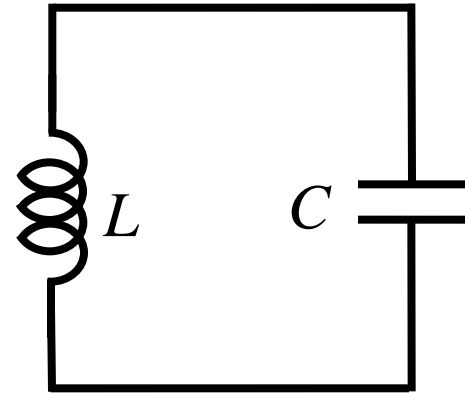At time $t = 0$ the capacitor is fully charged with Q_{max} and the current through the circuit is 0.



How much energy is stored in the capacitor when the current is a maximum ?

A) $U = Q_{max}^2 / (2C)$

B) $U = Q_{max}^2 / (4C)$

C) $U = 0$


Total Energy is constant!

$$U_{Lmax} = \frac{1}{2} L I_{max}^2$$

$$U_{Cmax} = Q_{max}^2 / 2C$$

$I = max$ when $Q = 0$


LC Circuit: Question 5 (N = 815)

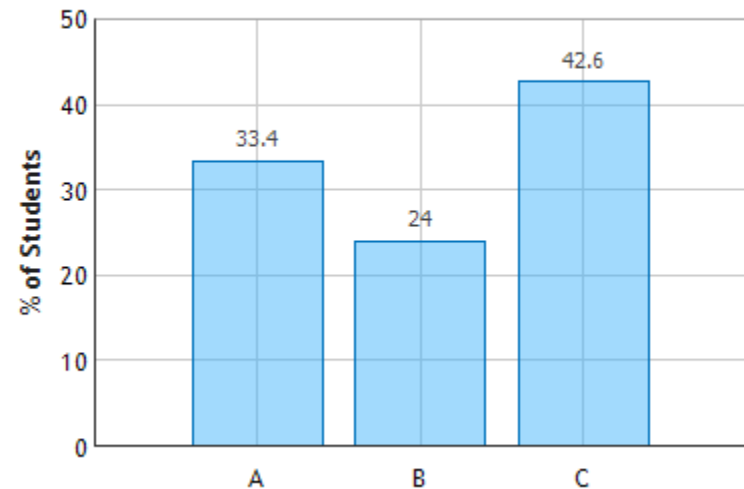

CheckPoint 2a



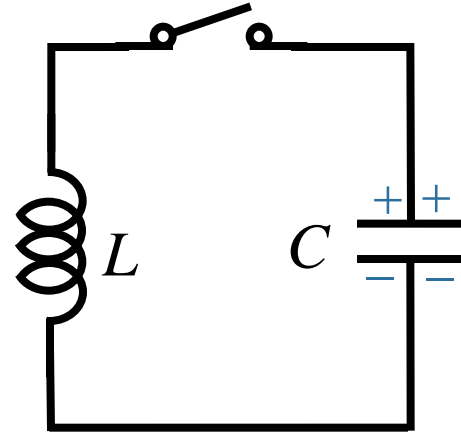The capacitor is charged such that the top plate has a charge $+Q_0$ and the bottom plate $-Q_0$. At time $t = 0$, the switch is closed and the circuit oscillates with frequency $\omega = 500$ radians/s.




$$L = 4 \times 10^{-3} \text{ H}$$
$$\omega = 500 \text{ rad/s}$$

What is the value of the capacitor C ?







- A) $C = 1 \times 10^{-3} \text{ F}$
- B) $C = 2 \times 10^{-3} \text{ F}$
- C) $C = 4 \times 10^{-3} \text{ F}$

$$\omega = \frac{1}{\sqrt{LC}} \longrightarrow C = \frac{1}{\omega^2 L} = \frac{1}{(25 \times 10^4)(4 \times 10^{-3})} = 10^{-3}$$

LC Circuit 2: Question 1 (N = 811)

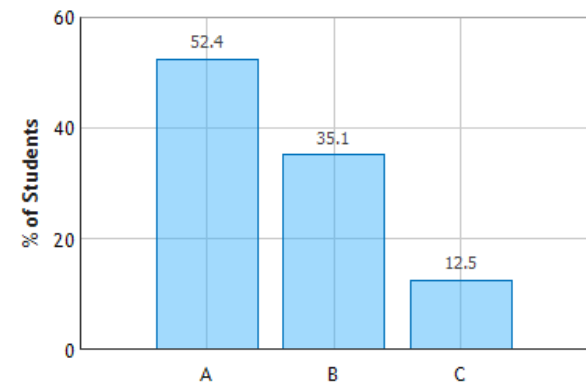

CheckPoint 2b

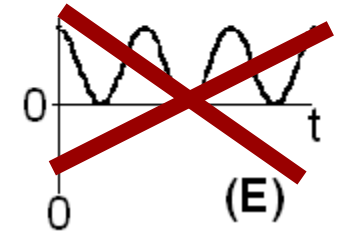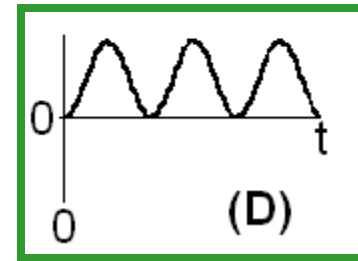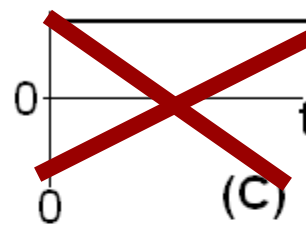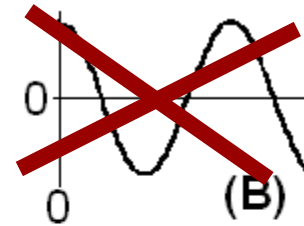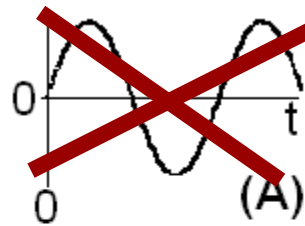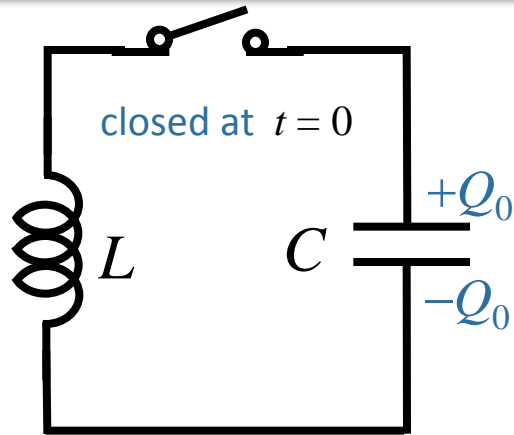


Which plot best represents the energy in the inductor as a function of time starting just after the switch is closed?

$$U_L = \frac{1}{2} L I^2$$

Energy proportional to $I^2 \Rightarrow U_L$ cannot be negative

Current is changing $\Rightarrow U_L$ is not constant


Initial current is zero

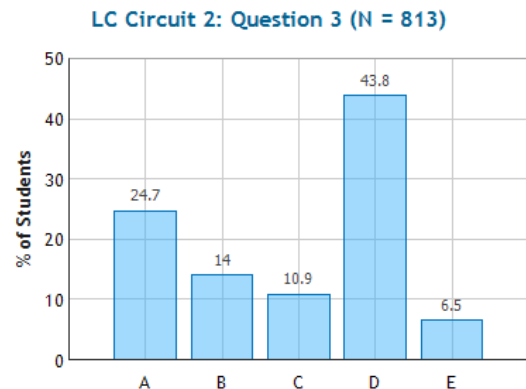


CheckPoint 2c



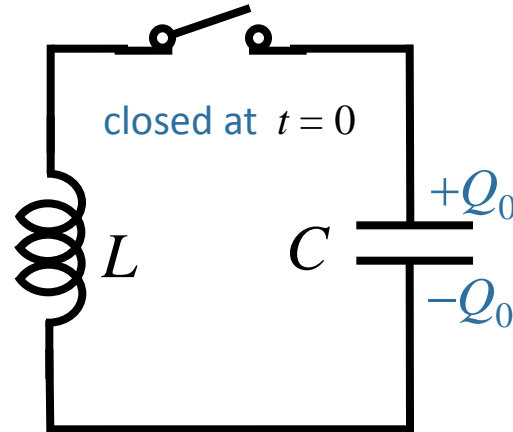When the energy stored in the capacitor reaches its maximum again for the **first time after $t = 0$** , how much charge is stored on the top plate of the capacitor?



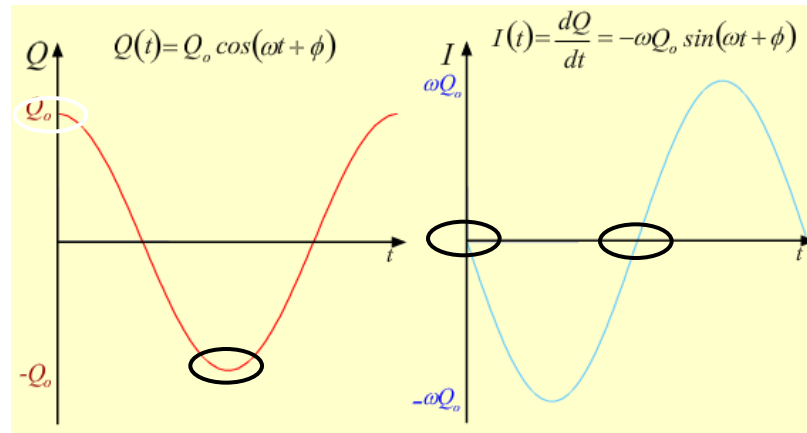- A) $+Q_0$
- B) $+Q_0/2$
- C) 0
- D) $-Q_0/2$
- E) $-Q_0$**




Q is maximum when current goes to zero

$$I = \frac{dQ}{dt}$$


Current goes to zero twice during one cycle

LC Circuit 2: Question 5 (N = 811)

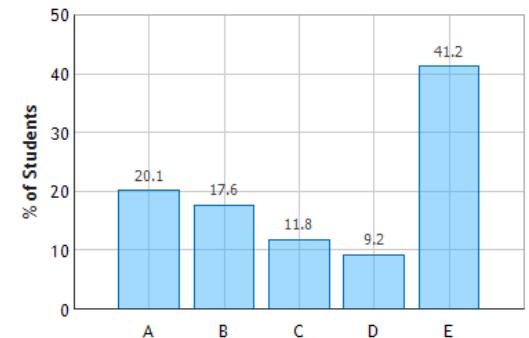

Add R: Damping

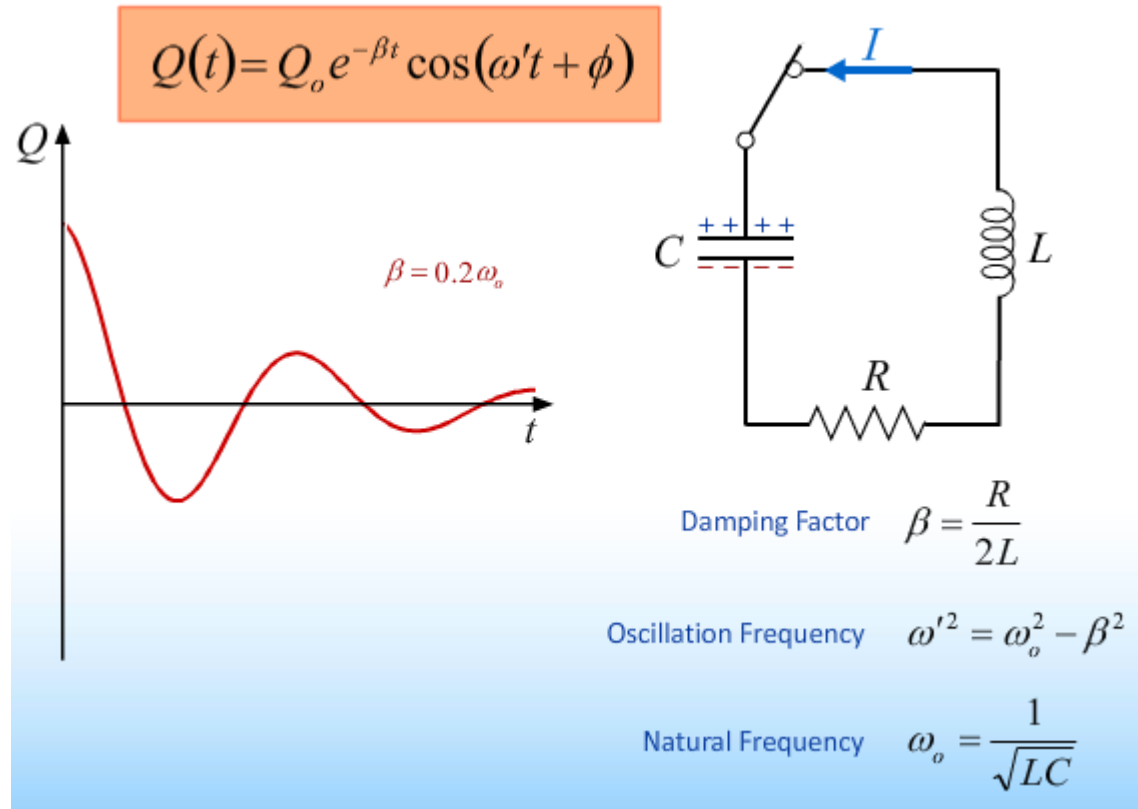Just like LC circuit but energy but the oscillations get smaller because of R



Concept makes sense...

...but answer looks kind of complicated

Physics Truth #1:

Even though the answer sometimes looks complicated...


$$Q(t) = Q_o \cos(\omega t - \phi)$$

the physics under the hood is still very simple!

$$\frac{d^2 Q}{dt^2} = -\omega^2 Q$$

The elements of a circuit are very simple:

$$V_L = L \frac{dI}{dt}$$

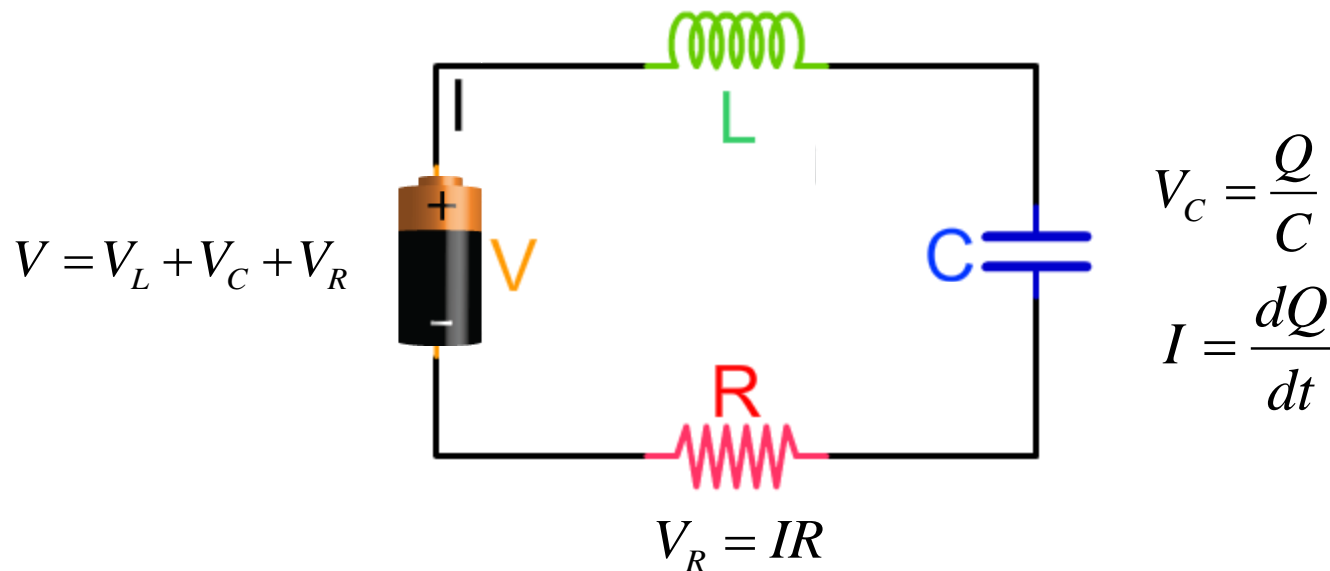


This is all we need to know to solve for anything!

Calculation

The switch in the circuit shown has been closed for a long time. At $t = 0$, the switch is opened.

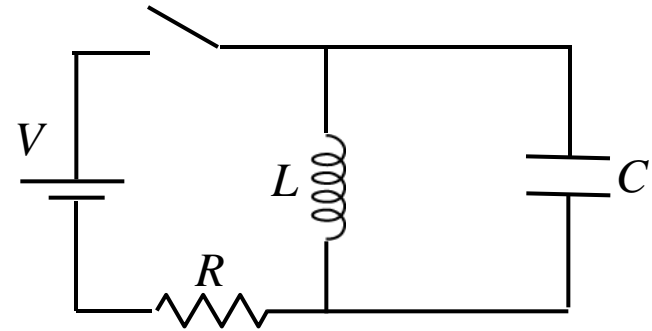What is Q_{MAX} , the maximum charge on the capacitor?



Conceptual Analysis


Once switch is opened, we have an LC circuit
Current will oscillate with natural frequency ω_0

Strategic Analysis

Determine initial current
Determine oscillation frequency ω_0
Find maximum charge on capacitor

Calculation

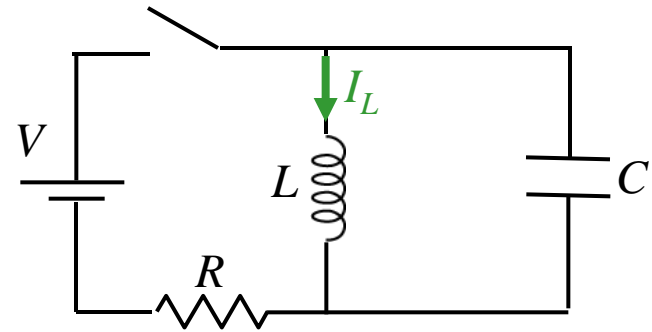The switch in the circuit shown has been closed for a long time. At $t = 0$, the switch is opened.



What is I_L , the current in the inductor, immediately **after** the switch is opened? Take positive direction as shown.

A) $I_L < 0$

B) $I_L = 0$

C) $I_L > 0$


Current through inductor immediately **after** switch is opened
is the same as
the current through inductor immediately **before** switch is opened

before switch is opened:

all current goes through inductor in direction shown

Calculation

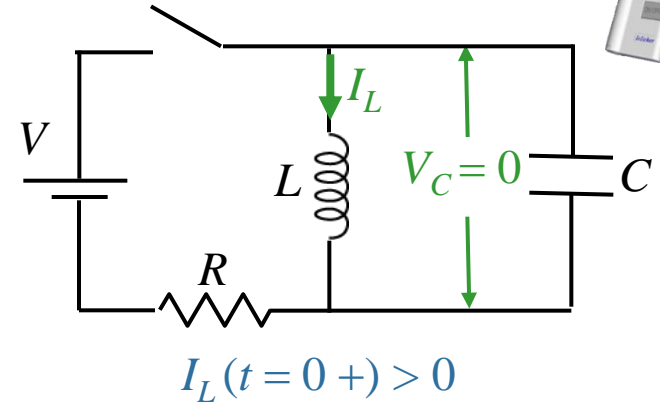The switch in the circuit shown has been closed for a long time. At $t = 0$, the switch is opened.



The energy stored in the capacitor immediately after the switch is opened is zero.

A) TRUE

B) FALSE

before switch is opened:

$$dI_L/dt \sim 0 \Rightarrow V_L = 0$$

BUT: $V_L = V_C$
since they are in parallel

$$\longrightarrow V_C = 0$$

after switch is opened:

V_C cannot change abruptly

$$\longrightarrow V_C = 0$$

$$\longrightarrow U_C = \frac{1}{2} CV_C^2 = 0 !$$


IMPORTANT: NOTE DIFFERENT CONSTRAINTS AFTER SWITCH OPENED

CURRENT through INDUCTOR cannot change abruptly

VOLTAGE across CAPACITOR cannot change abruptly

Calculation

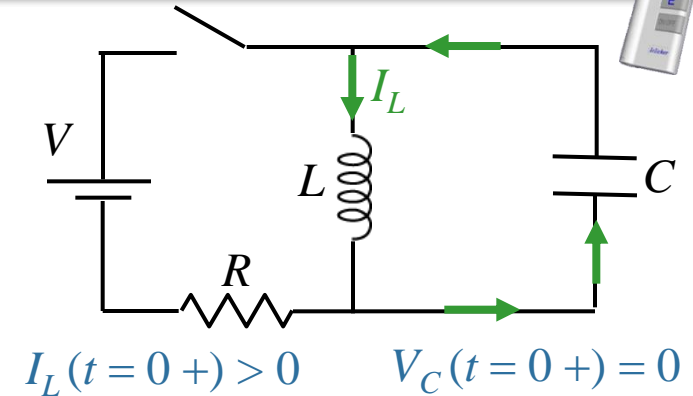The switch in the circuit shown has been closed for a long time. At $t = 0$, the switch is opened.



What is the direction of the current immediately after the switch is opened?

A) clockwise

B) counterclockwise


Current through inductor immediately **after** switch is opened
is the same as
the current through inductor immediately **before** switch is opened

Before switch is opened: Current moves down through L

After switch is opened: Current continues to move down through L

Calculation

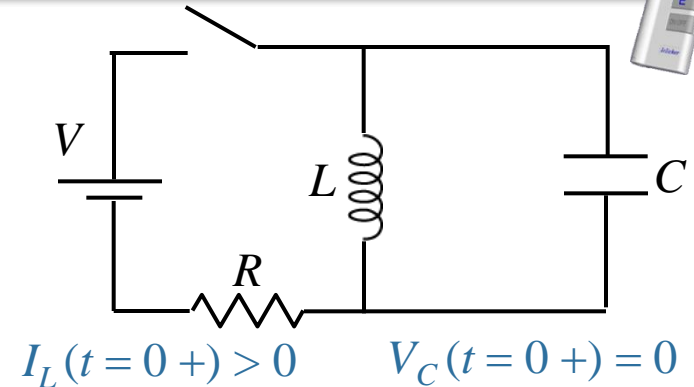The switch in the circuit shown has been closed for a long time. At $t = 0$, the switch is opened.



What is the magnitude of the current right after the switch is opened?

A) $I_o = V \sqrt{\frac{C}{L}}$


B) $I_o = \frac{V}{R^2} \sqrt{\frac{L}{C}}$

C) $I_o = \frac{V}{R}$

D) $I_o = \frac{V}{2R}$

Current through inductor immediately **after** switch is opened
is the same as
the current through inductor immediately **before** switch is opened


Before switch is opened:

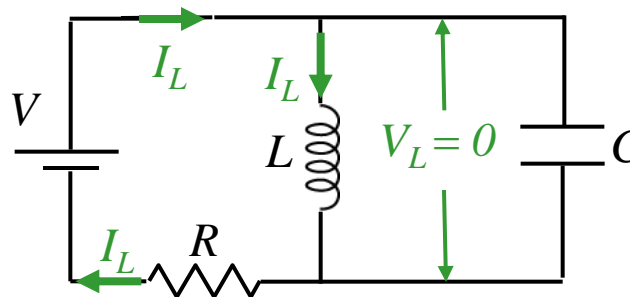

Calculation

The switch in the circuit shown has been closed for a long time. At $t = 0$, the switch is opened.

Hint: Energy is conserved

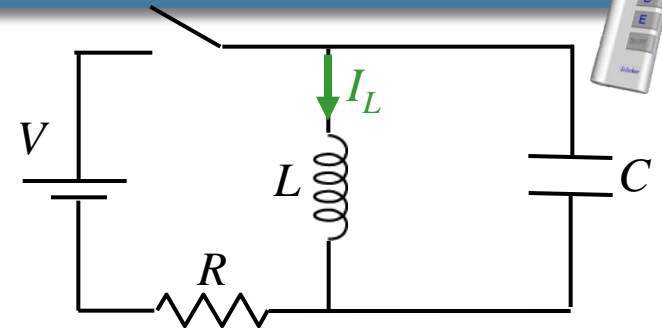

$$I_L(t = 0+) = V/R \quad V_C(t = 0+) = 0$$


What is Q_{\max} , the maximum charge on the capacitor during the oscillations?

A) $Q_{\max} = \frac{V}{R} \sqrt{LC}$

B) $Q_{\max} = \frac{1}{2} CV$


C) $Q_{\max} = CV$

D) $Q_{\max} = \frac{V}{R\sqrt{LC}}$

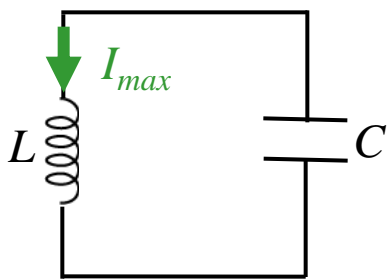

When I is *max*
(and Q is 0)

$$U = \frac{1}{2} LI_{\max}^2$$

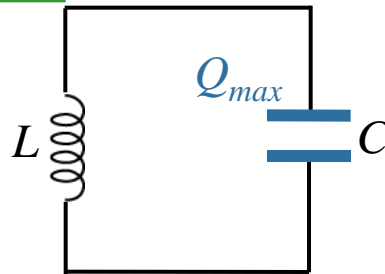

When Q is *max*
(and I is 0)

$$U = \frac{1}{2} \frac{Q_{\max}^2}{C}$$



$$\frac{1}{2} LI_{\max}^2 = \frac{1}{2} \frac{Q_{\max}^2}{C}$$

$$Q_{\max} = I_{\max} \sqrt{LC}$$


$$= \frac{V}{R} \sqrt{LC}$$

Follow-Up



The switch in the circuit shown has been closed for a long time. At $t = 0$, the switch is opened.

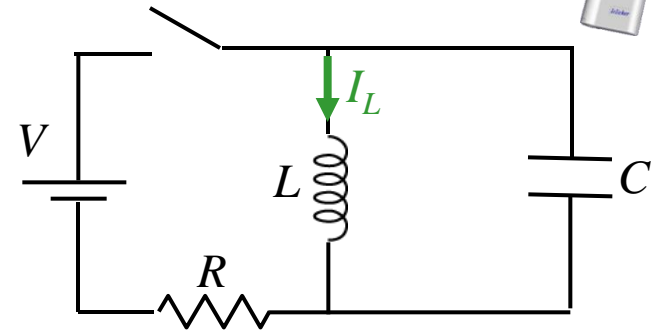Is it possible for the maximum voltage on the capacitor to be greater than V ?



A) YES

B) NO

$$I_{\max} = V/R \qquad Q_{\max} = \frac{V}{R} \sqrt{LC}$$

$$Q_{\max} = \frac{V}{R} \sqrt{LC} \rightarrow V_{\max} = \frac{V}{R} \sqrt{\frac{L}{C}} \rightarrow V_{\max} \text{ can be greater than } V \text{ IF: } \sqrt{\frac{L}{C}} > R$$

We can rewrite this condition in terms of the resonant frequency:

$$\omega_0 L > R \quad \text{OR} \quad \frac{1}{\omega_0 C} > R$$

We will see these forms again when we study AC circuits!