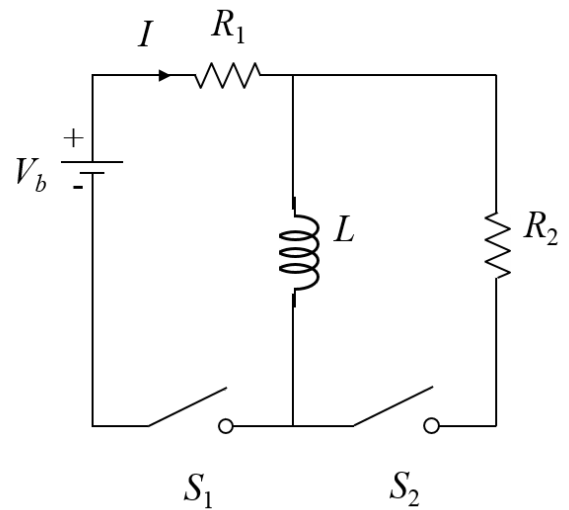


The next three questions pertain to the situation described below.

The circuit below consists of a battery with voltage, $V_b = 24$ V, two resistors, $R_1 = 20 \Omega$ and $R_2 = 30 \Omega$, an inductor, $L = 22$ mH and two switches, S_1 and S_2 . S_1 and S_2 have been open for a long time. At $t = 0$, S_1 is closed.



1) What is the rate of change of current through the inductor immediately after switch S_1 is closed (e.g. $t = 0$)?

- a. $dI/dt = 1090$ A/s
- b. $dI/dt = 1.2$ A/s
- c. $dI/dt = 0.48$ A/s
- d. $dI/dt = 0.8$ A/s
- e. $dI/dt = 0$ A/s

2) What is the magnitude of the current through resistor R_1 at time $t = 1.4$ ms after switch S_1 is closed?


- a. $|I_{R1}| = 0.864$ A
- b. $|I_{R1}| = 0.336$ A
- c. $|I_{R1}| = 1.02$ A

3) After S_1 has been closed for a long time, S_2 is closed, and then S_1 is opened. What is the magnitude of the voltage across resistor R_2 , immediately after switch S_1 is opened?

- a. $|V_{R2}| = 24$ V
- b. $|V_{R2}| = 36$ V
- c. $|V_{R2}| = 16$ V

The next three questions pertain to the situation described below.

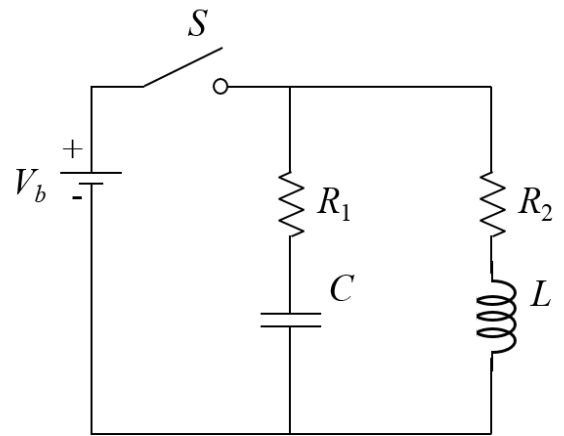
A circuit is composed of a battery with voltage $V_b = 6\text{ V}$, two resistors $R_1 = 40\ \Omega$ and $R_2 = 24\ \Omega$, a capacitor $C = 17\text{ nF}$, an inductor $L = 28\text{ mH}$ and a switch S . The switch has been open for a long time; at $t = 0$, it is closed.



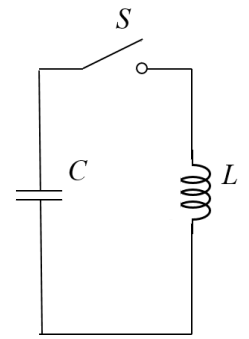- 4) What is the current through the battery at $t = 0$, just after the switch is closed?
- $I_b = 0.0938\text{ A}$
 - $I_b = 0.15\text{ A}$
 - $I_b = 0.4\text{ A}$
 - $I_b = 0\text{ A}$
 - $I_b = 0.25\text{ A}$
- 5) What is V_C , the voltage across the capacitor, after the switch has been closed for a long time?
- $V_C = 3.75\text{ V}$
 - $V_C = 0\text{ V}$
 - $V_C = 6\text{ V}$
- 6) How much energy is stored in the inductor after the switch has been closed for a long time?
- $U_L = 0.315\text{ mJ}$
 - $U_L = 51\text{ mJ}$
 - $U_L = 0.875\text{ mJ}$
 - $U_L = 0\text{ mJ}$
 - $U_L = 1.5\text{ mJ}$

The next three questions pertain to the situation described below.

The circuit shown consists of a capacitor, $C = 4 \mu\text{F}$ that has an initial charge $Q_i = 24 \mu\text{C}$, an unknown inductor, L , and an open switch, S . At time $t = 0$ the switch is closed.



7) At $t = 0$, the total energy, E_{tot} , stored in the circuit is

- a. $E_{\text{tot}} = 0.072 \text{ mJ}$
- b. $E_{\text{tot}} = 0.144 \text{ mJ}$
- c. $E_{\text{tot}} = 0 \text{ mJ}$

8) At the instants in time when the current through the inductor is not changing ($dI/dt = 0$), what is V_C , the voltage across the capacitor?


- a. $V_C = 12 \text{ V}$
- b. $V_C = 0 \text{ V}$
- c. $V_C = 6 \text{ V}$

9) After the switch is closed, the frequency of the oscillations in the circuit is measured to be $f = 40 \text{ kHz}$. At $t = 107 \mu\text{s}$, what is the magnitude of the voltage across the inductor?

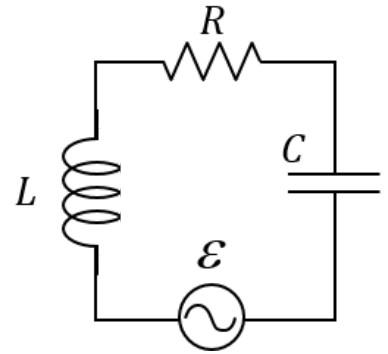- a. $V_L = 1.12 \text{ V}$
- b. $V_L = 6 \text{ V}$
- c. $V_L = 0 \text{ V}$
- d. $V_L = 3 \text{ V}$
- e. $V_L = 5.89 \text{ V}$

The next four questions pertain to the situation described below.

Consider the electrical AC circuit shown. It consists of a variable frequency AC generator providing a voltage $V(t) = 28 \sin(\omega t)$ Volts, a 10Ω resistor, a $1.5 \mu\text{F}$ capacitor, and a 2.4 mH inductor.



- 10) At resonance, which of the following components has the largest peak voltage across it?
- a. Generator
 - b. Capacitor
 - c. Resistor
- 11) What is the peak current through the circuit when the generator is running at $\omega = 2 \times 10^4 \text{ rad/s}$?
- a. $I_{\text{max}} = 0.583 \text{ A}$
 - b. $I_{\text{max}} = 1.58 \text{ A}$
 - c. $I_{\text{max}} = 2.8 \text{ A}$
- 12) What is the magnitude of the phase angle between the voltage across generator, and the current through the generator when the generator is running at $\omega = 2 \times 10^4 \text{ rad/s}$?
- a. $|\phi| = 16.7^\circ$
 - b. $|\phi| = 0^\circ$
 - c. $|\phi| = 55.7^\circ$
- 13) With the generator frequency still set to $2 \times 10^4 \text{ rad/s}$, what is the first time after $t=0$, that the magnitude of the voltage across the resistor is a maximum?
- a. $t = 7.85 \times 10^{-5} \text{ s}$
 - b. $t = 1.27 \times 10^{-4} \text{ s}$
 - c. $t = 4.86 \times 10^{-5} \text{ s}$

The next four questions pertain to the situation described below.

The electric field in an electromagnetic wave traveling through the vacuum is given by

$$\vec{E} = \frac{E_0}{\sqrt{2}} [\hat{x} \cos(kz + \omega t) + \hat{y} \sin(kz + \omega t)], \text{ where } \omega > 0 \text{ and } k > 0. \text{ The wavelength is } \lambda = 0.5 \text{ cm.}$$

14) What is the angular frequency ω of this wave?

- a. $\omega = 1.88 \times 10^{11} \text{ rad/s}$
- b. $\omega = 3.77 \times 10^{11} \text{ rad/s}$
- c. $\omega = 1.33 \times 10^{11} \text{ rad/s}$

15) The electromagnetic wave is

- a. unpolarized.
- b. linearly polarized.
- c. circularly polarized.

16) Which equation describes the magnetic field of this wave?


- a. $\vec{B} = \frac{E_0}{\sqrt{2}c} [\hat{x} \sin(kz + \omega t) - \hat{y} \sin(kz + \omega t)]$
- b. $\vec{B} = \frac{E_0}{\sqrt{2}c} [\hat{x} \sin(kz + \omega t) + \hat{y} \cos(kz + \omega t)]$
- c. $\vec{B} = \frac{E_0}{\sqrt{2}c} [\hat{x} \sin(kz + \omega t) - \hat{y} \cos(kz + \omega t)]$
- d. $\vec{B} = \frac{E_0}{\sqrt{2}c} [\hat{x} \cos(kz + \omega t) - \hat{y} \sin(kz + \omega t)]$
- e. $\vec{B} = \frac{E_0}{\sqrt{2}c} [\hat{x} \cos(kz + \omega t) + \hat{y} \sin(kz + \omega t)]$

17) Which of the following statements about the magnitude of the Poynting vector $|\vec{S}|$ for this wave is correct?

- a. $|\vec{S}|$ varies as a function of t but is independent of z .
- b. $|\vec{S}|$ varies as a function of both z and t .
- c. $|\vec{S}|$ is independent of both z and t .

The next four questions pertain to the situation described below.

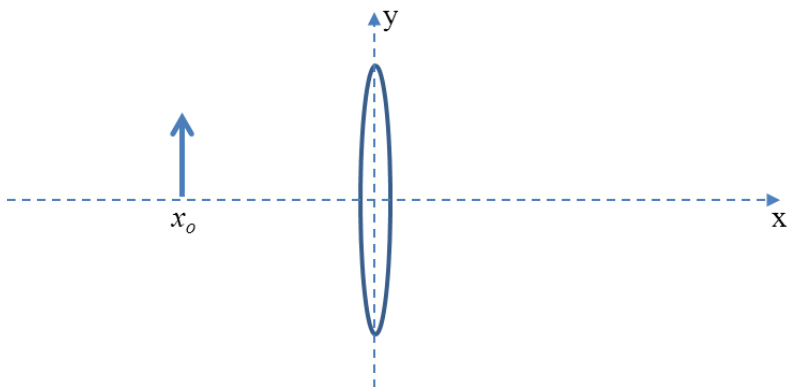A converging lens, made of glass with index of refraction $n = 1.5$, has a focal length $f = 0.25$ m. The lens is positioned at $x = 0$, as shown below.



18) At what position, x_0 , to the left of the lens should an object be placed so that the resulting image has a magnification $M = -2.5$?

- a. $x_0 = -0.35$ m
- b. $x_0 = -0.25$ m
- c. $x_0 = -0.15$ m
- d. $x_0 = -0.1$ m
- e. $x_0 = -0.625$ m

19) The resulting image is

- a. real
- b. virtual


20) The resulting image is

- a. upright
- b. inverted

21) If the entire apparatus was placed inside an aquarium filled with water ($n=1.3$), in order to produce an image with the same magnification $M = -2.5$, the object should be moved

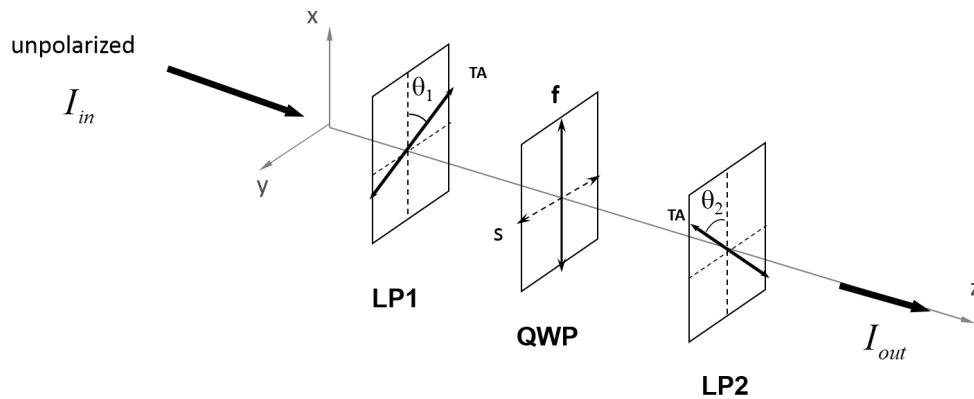- a. closer to the lens.
- b. at the same location as when the system was in air.
- c. further from the lens.

The next three questions pertain to the situation described below.



Consider a beam of unpolarized light with initial intensity I_{in} traveling in the $+z$ direction that goes through an arrangement of two linear polarizers (LP1 and LP2) and a quarter wave plate (QWP) as shown in the figure. The surfaces of the polarizers and QWP are parallel to the xy plane. The transmission axes of the polarizers are at $\theta_1 = 45^\circ$ one way and $\theta_2 = 60^\circ$ the opposite way with respect to the x -axis, as shown in the diagram. The fast axis of the QWP is parallel to the x axis.

22) What is the polarization of the light immediately after it passes through the quarter wave plate (QWP)?

- a. linearly polarized at 60° relative to the x axis.
- b. left circularly polarized
- c. right circularly polarized
- d. linearly polarized at 45° relative to the x axis.
- e. unpolarized

23) What is the intensity of the transmitted light?


- a. $I_{out} = 0.5 * I_{in}$
- b. $I_{out} = 0.25 * I_{in}$
- c. $I_{out} = I_{in}$
- d. $I_{out} = 0.066 * I_{in}$
- e. $I_{out} = 0.033 * I_{in}$

24) If the first polarizer is rotated such that $\theta_1 = 0^\circ$, what would happen to the intensity of the transmitted light I_{out} ?

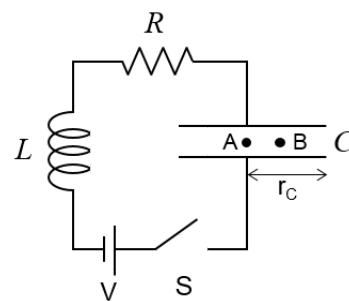- a. I_{out} would decrease
- b. I_{out} would not change
- c. I_{out} would increase

The next two questions pertain to the situation described below.

A series RLC circuit is connected to a battery. The capacitor consists of two parallel, circular plates of radius $r_C = 0.045$ m. At time $t = 0$, the switch is closed.



25) **Immediately** after the switch is closed (e.g. $t=0$), which of the following correctly describes the magnitude of the magnetic field at points **A** and **B**


- a. $|B_A| < |B_B|$
- b. $|B_A| > |B_B|$
- c. $|B_A| = |B_B|$

26) At the instant in time when the current through the resistor is 0.4 A, what is the magnitude of the magnetic field at point **B**, a distance $r = 0.015$ m from the center of the capacitor?

- a. $|B| = 0$ T
- b. $|B| = 5.34 \times 10^{-6}$ T
- c. $|B| = 1.98 \times 10^{-7}$ T
- d. $|B| = 5.93 \times 10^{-7}$ T
- e. $|B| = 1.78 \times 10^{-6}$ T

The next two questions pertain to the situation described below.

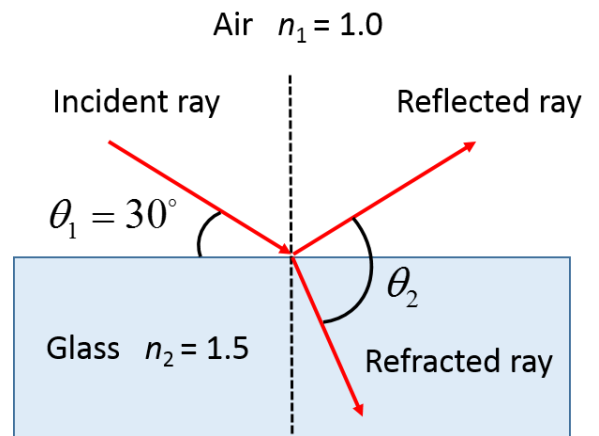A light ray is incident from the air into a glass of index of refraction $n_2 = 1.5$ at an angle $\theta_1 = 30^\circ$. The angle between the reflected ray and the refracted ray is θ_2 as shown in the figure.



27) What is the value of θ_2 ?

- a. $\theta_2 = 90.0^\circ$
- b. $\theta_2 = 19.5^\circ$
- c. $\theta_2 = 84.7^\circ$

28) if θ_1 decreases to 25° , how would θ_2 change?

- a. θ_2 would not change
- b. θ_2 would increase
- c. θ_2 would decrease