

UNIVERSITY OF ILLINOIS  
AT URBANA-CHAMPAIGN

# Frequency Domain Analysis of Linear Circuits Using Synchronous Detection

Physics 401, Fall 2016.

*Eugene V. Colla*





in 1822, Jean Baptiste Fourier developed the theory that shows that any real waveform can be represented by the sum of sinusoidal waves.

Let us try to create the square wave as a sum of sine waves of different frequencies




**Jean Baptiste Joseph  
Fourier  
(1768 – 1830)**

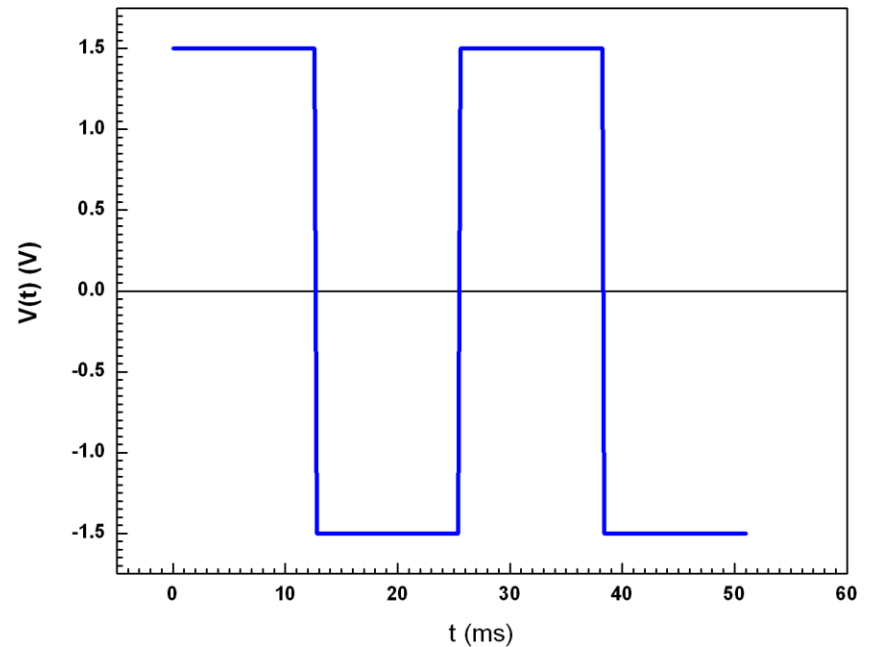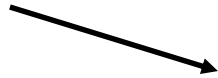
**Square wave.  
 $F=40\text{Hz}$ ,  $A=1.5\text{V}$**




$$A_1 \sin(2\pi\omega t)$$

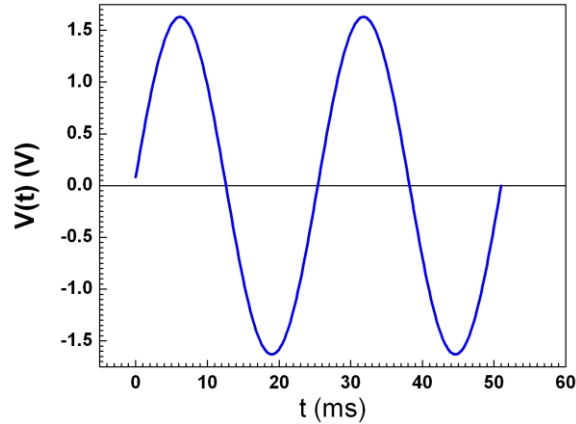

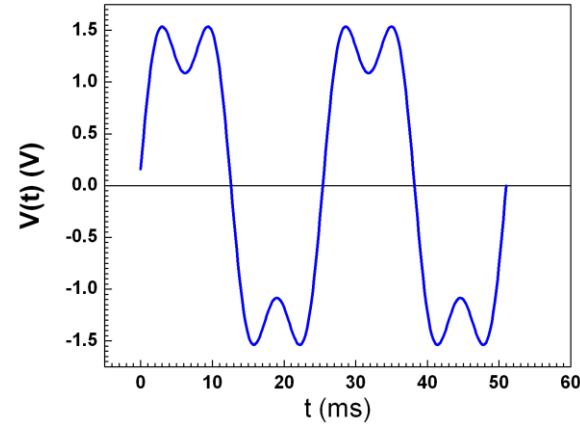
$$A_1 \sin(2\pi\omega t) + A_3 \sin(2\pi 3\omega t + \varphi_3)$$


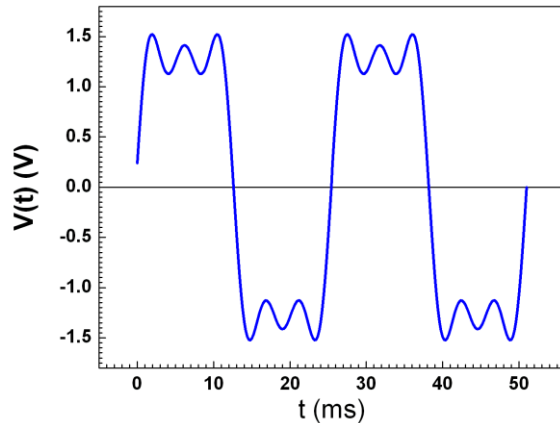
$$A_1 \sin(2\pi\omega t) + A_3 \sin(2\pi 3\omega t + \varphi_3) + A_5 \sin(2\pi 5\omega t + \varphi_5)$$


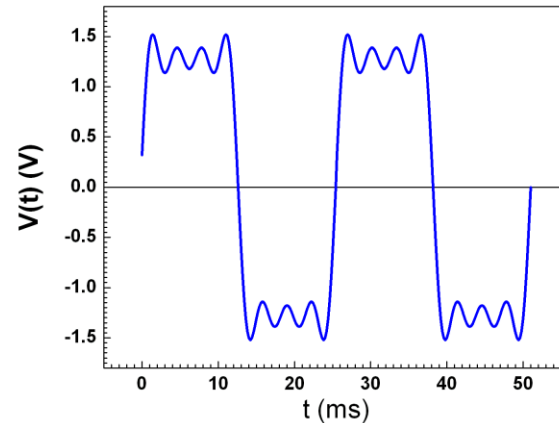
$$A_1 \sin(2\pi\omega t) + A_3 \sin(2\pi 3\omega t + \varphi_3) + A_5 \sin(2\pi 5\omega t + \varphi_5) + A_7 \sin(2\pi 7\omega t + \varphi_7)$$



# Fourier Transform

The continuous Fourier transformation of the signal  $h(t)$  can be written as:

$$H(f) = \int_{-\infty}^{+\infty} h(t) e^{2\pi jft} dt; \quad j = \sqrt{-1}$$

$H(f)$  represents in frequency domain mode the time domain signal  $h(t)$

Equation for inverse Fourier transform gives the correspondence of the infinite continuous frequency spectra to the corresponding time domain signal.

$$h(t) = \int_{-\infty}^{+\infty} H(f) e^{-2\pi jft} df$$

In real life we working with discrete representation of the time domain signal recorded during a finite time.




# Discrete Fourier Transform


It comes out that in practice more useful is the representation the frequency domain pattern of the time domain signal  $h_k$  as sum of the frequency harmonic calculated as:

$$H_n = H(f_n) = \frac{1}{N} \sum_{k=0}^{N-1} h_k e^{2\pi kn/N}$$

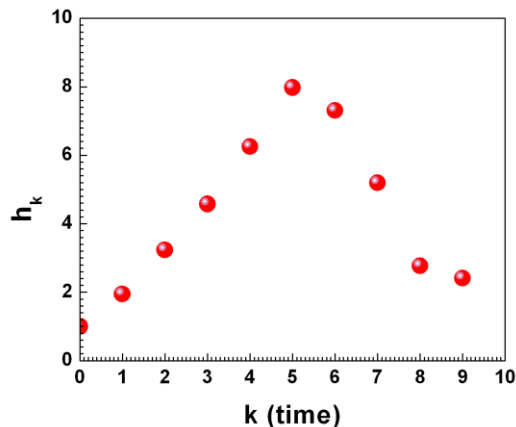$\Delta$  is the sampling interval,  $N$  – number of collected points



Time domain

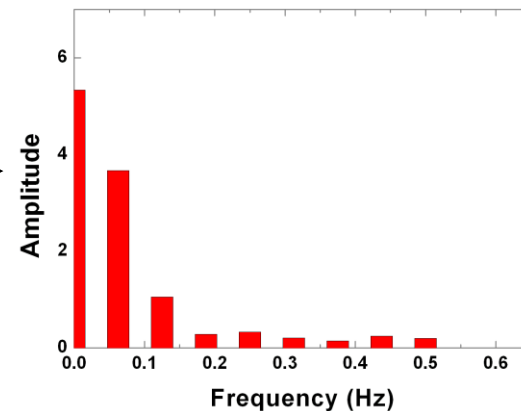

Frequency domain



# Discrete Fourier Transform

For periodic signals with period  $T_0$ :

$$F(t) = \frac{a_0}{2} + \sum_{n=1}^{\infty} a_n \cos\left(\frac{2\pi nt}{T_0}\right) + \sum_{n=1}^{\infty} b_n \sin\left(\frac{2\pi nt}{T_0}\right)$$

$$a_n = \frac{2}{T_0} \int_0^{T_0} F(t) \cos\left(\frac{2\pi nt}{T_0}\right) dt; \quad b_n = \frac{2}{T_0} \int_0^{T_0} F(t) \sin\left(\frac{2\pi nt}{T_0}\right) dt;$$


$$a_0 = \frac{2}{T_0} \int_0^{T_0} F(t) dt;$$



# Discrete Fourier Transform

Now how I found the amplitudes of the harmonics to compose the square wave signal from sine waves of different frequencies.

## Time domain signal

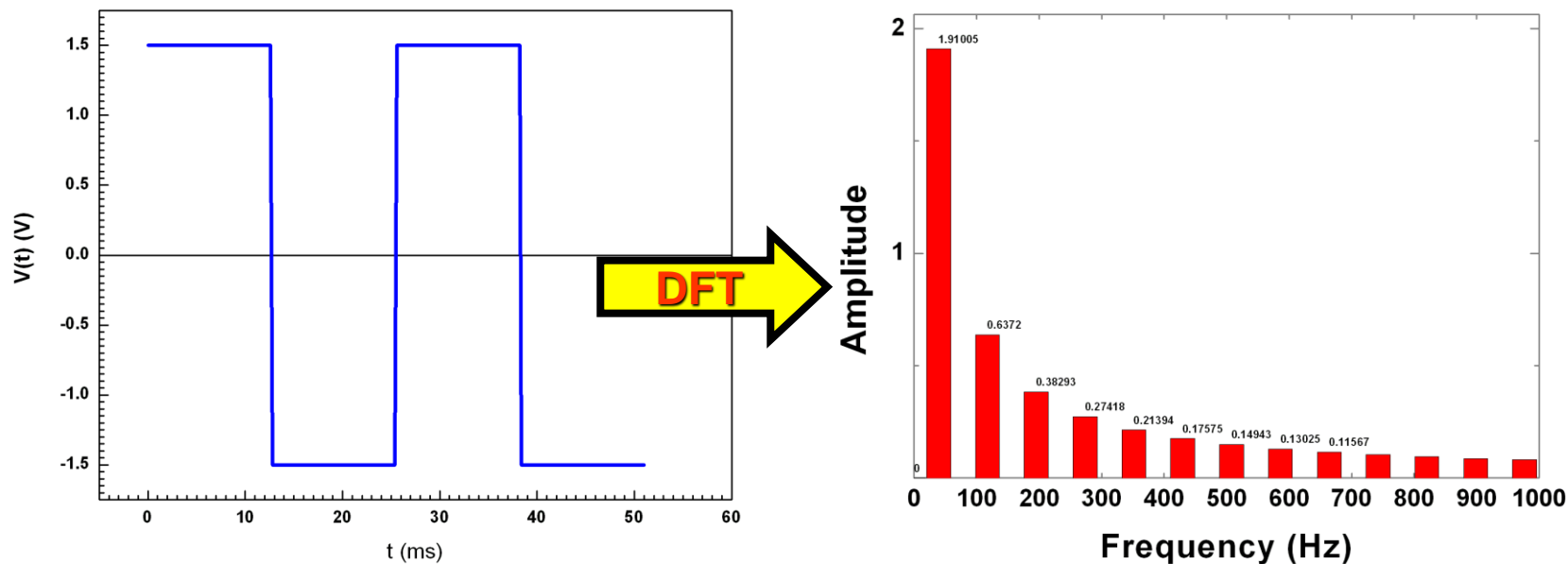



Decomposition the signal into the sine wave harmonics. The only modulus's of the harmonics amplitudes are presented in this picture.




# Frequency Domain Spectroscopy

(linear system)

Applied test signal

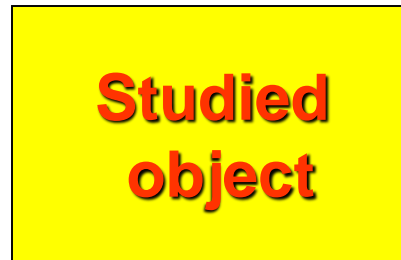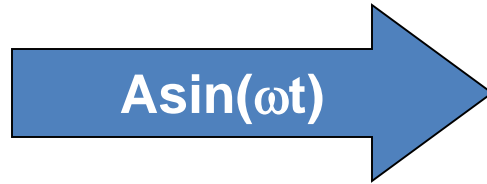

Response of the studied system

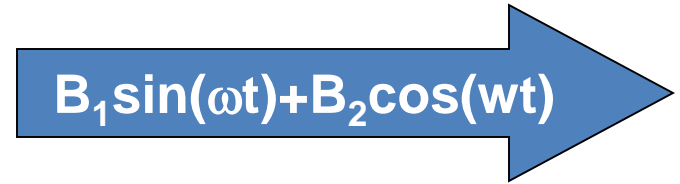


We applying the sine wave signal to the tested object and measuring the response. Varying the frequency we can study the frequency properties of the system.




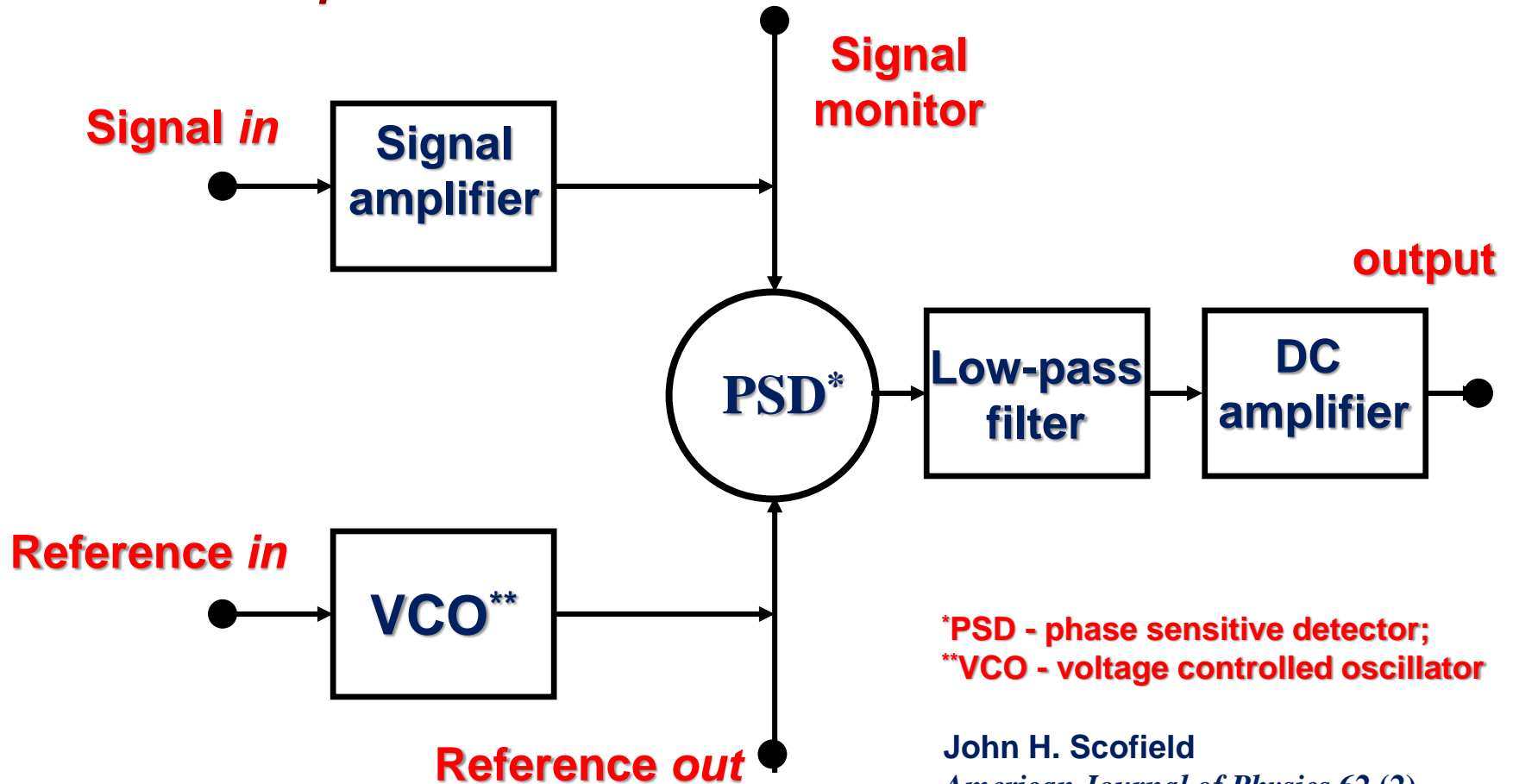
# Lock-in amplifier

*Now about the most powerful tool which can be used in frequency domain technique.*




\*PSD - phase sensitive detector;  
\*\*VCO - voltage controlled oscillator

John H. Scofield  
*American Journal of Physics* 62 (2)  
129-133 (Feb. 1994).







# Lock-in amplifier. How it works.

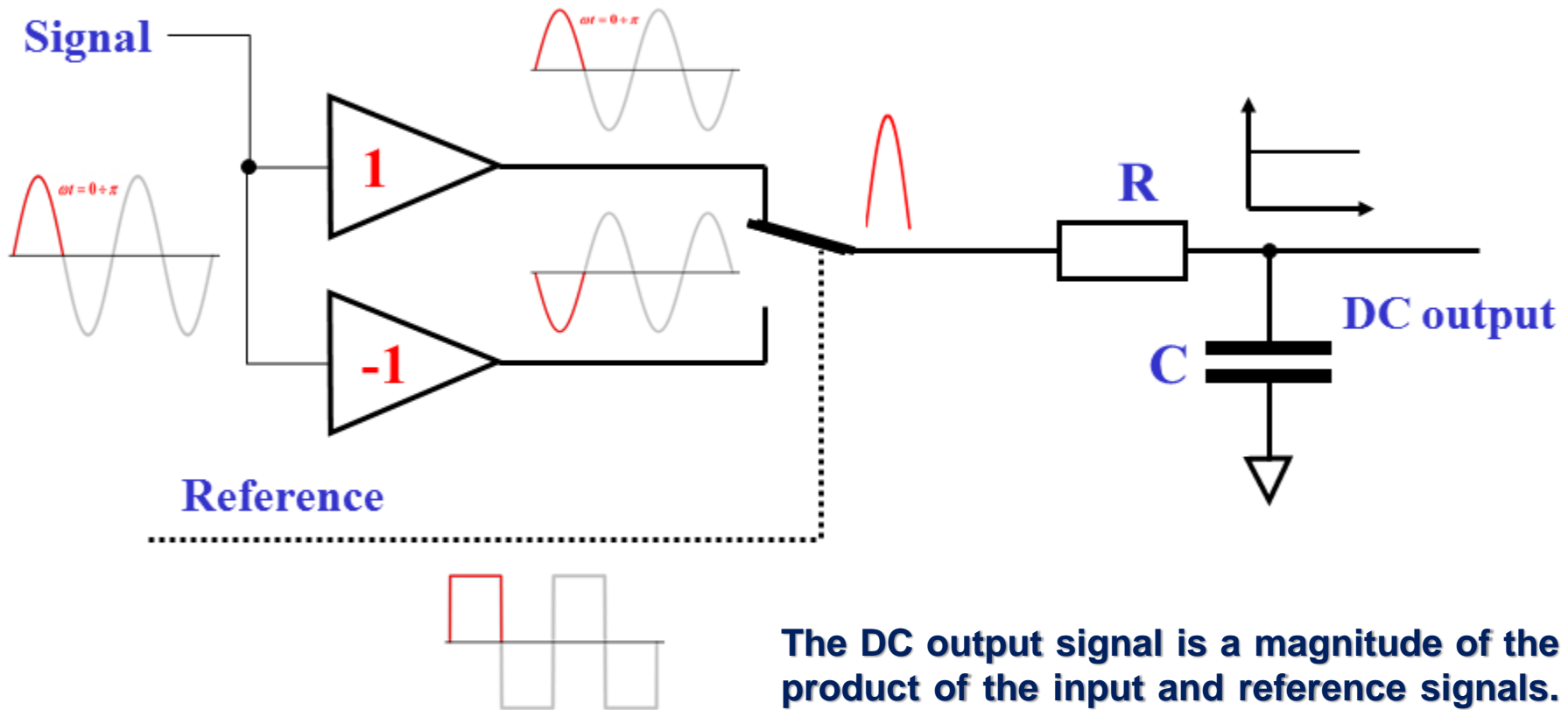

The DC output signal is a magnitude of the product of the input and reference signals. AC components of output signal are filtered out by the low-pass filter with time constant  $\tau$  (her  $\tau=RC$ )

# Lock-in Amplifier. What is the Advantage of Using Synchronous Detecting?





**DMM, lock-in etc.**

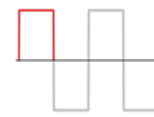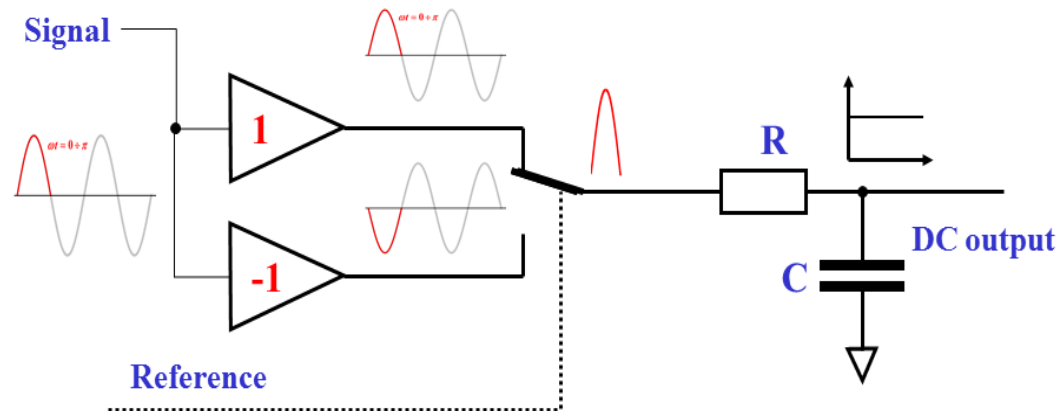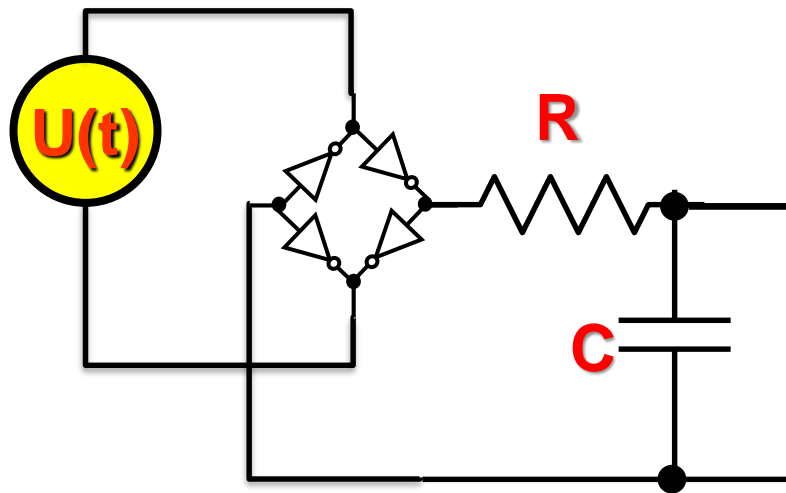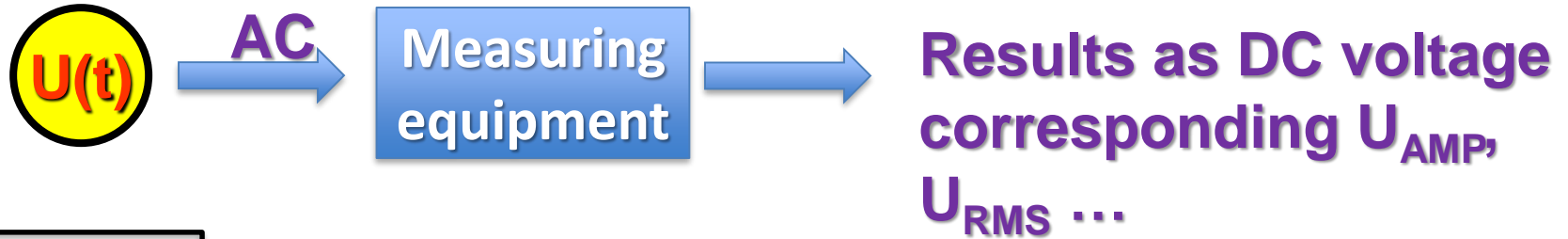

# Lock-in Amplifier. What is the Advantage of Using Synchronous Detecting?

1

Clean sine wave – no “noise”

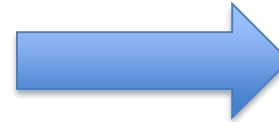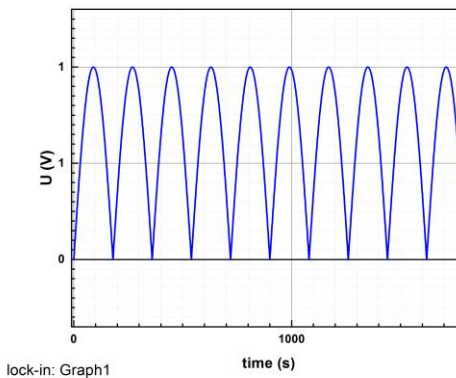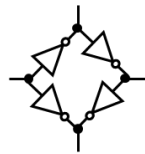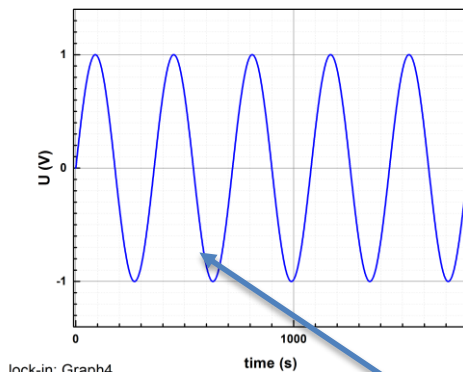

$$U_{DC} = 0.63643V$$





We need to measure the amplitude/rms value of the sine wave



# Lock-in Amplifier. What is the Advantage of Using Synchronous Detecting?

1

“Noisy” sine wave

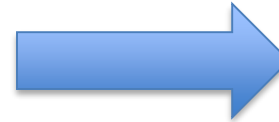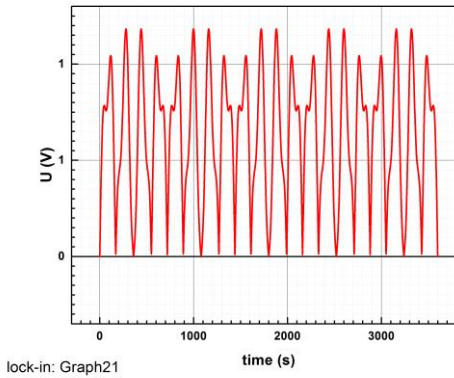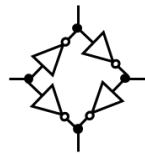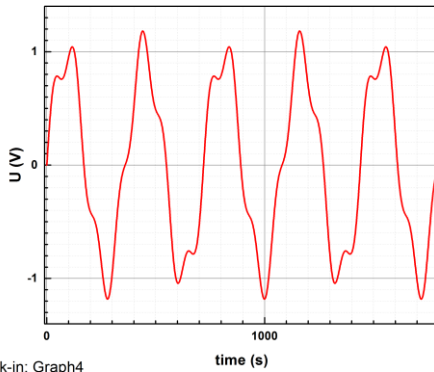

$U_{DC} = 0.64208V$   
compare to


$U_{DC} = 0.63643V$




# Lock-in Amplifier. What is the Advantage of Using Synchronous Detecting?

2


Clear sine wave – no “noise”

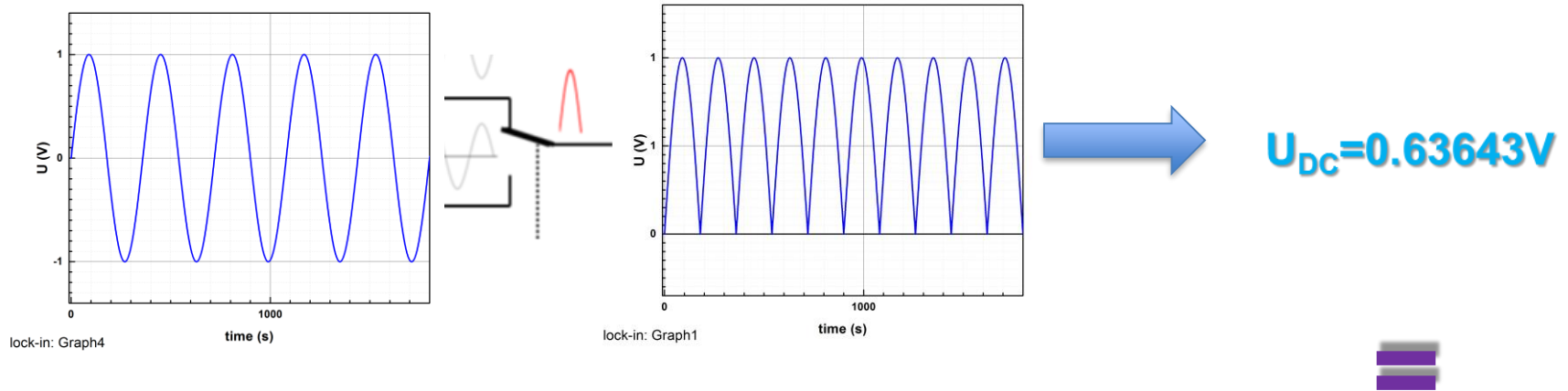

“Noisy” sine wave

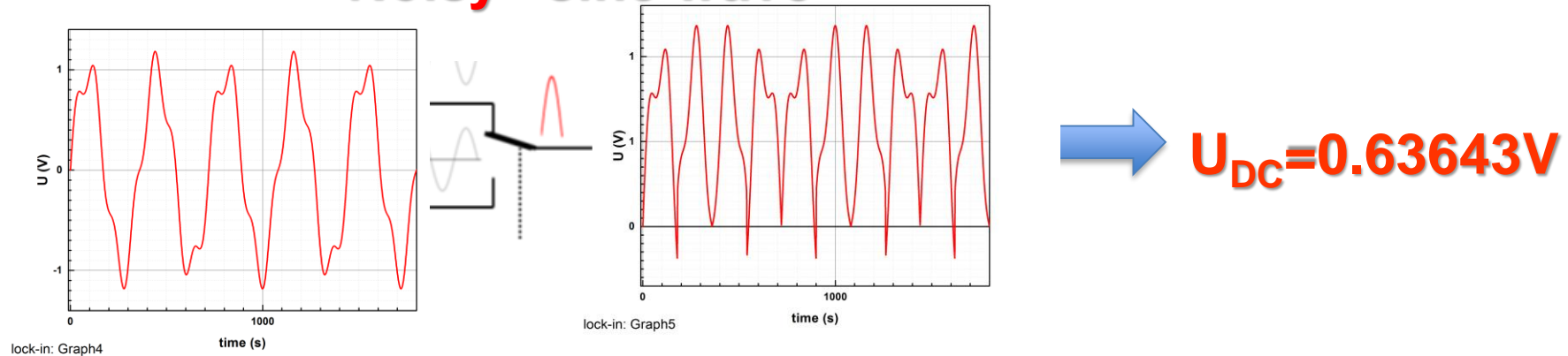


# Lock-in Amplifier. Phase shift.

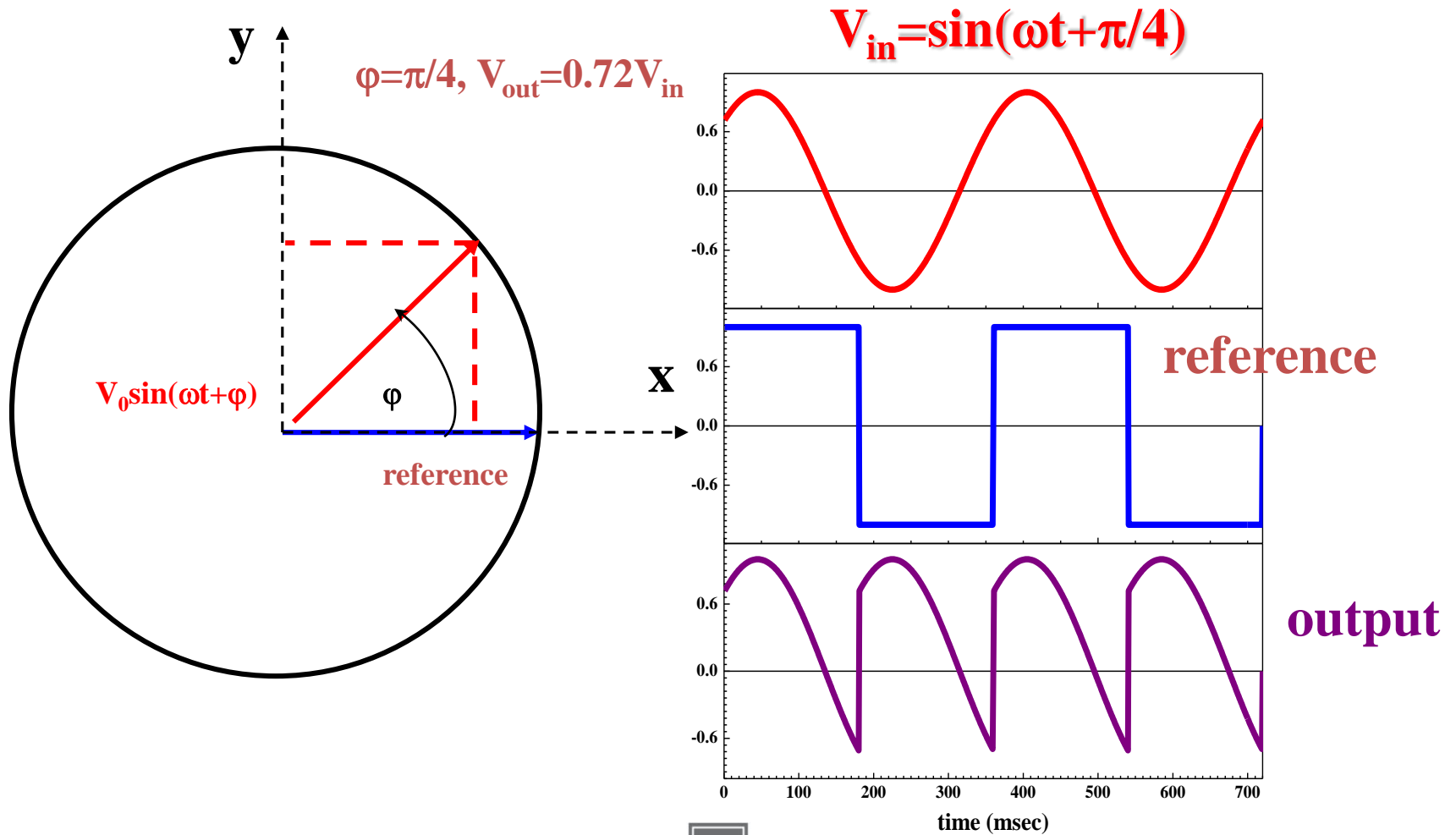

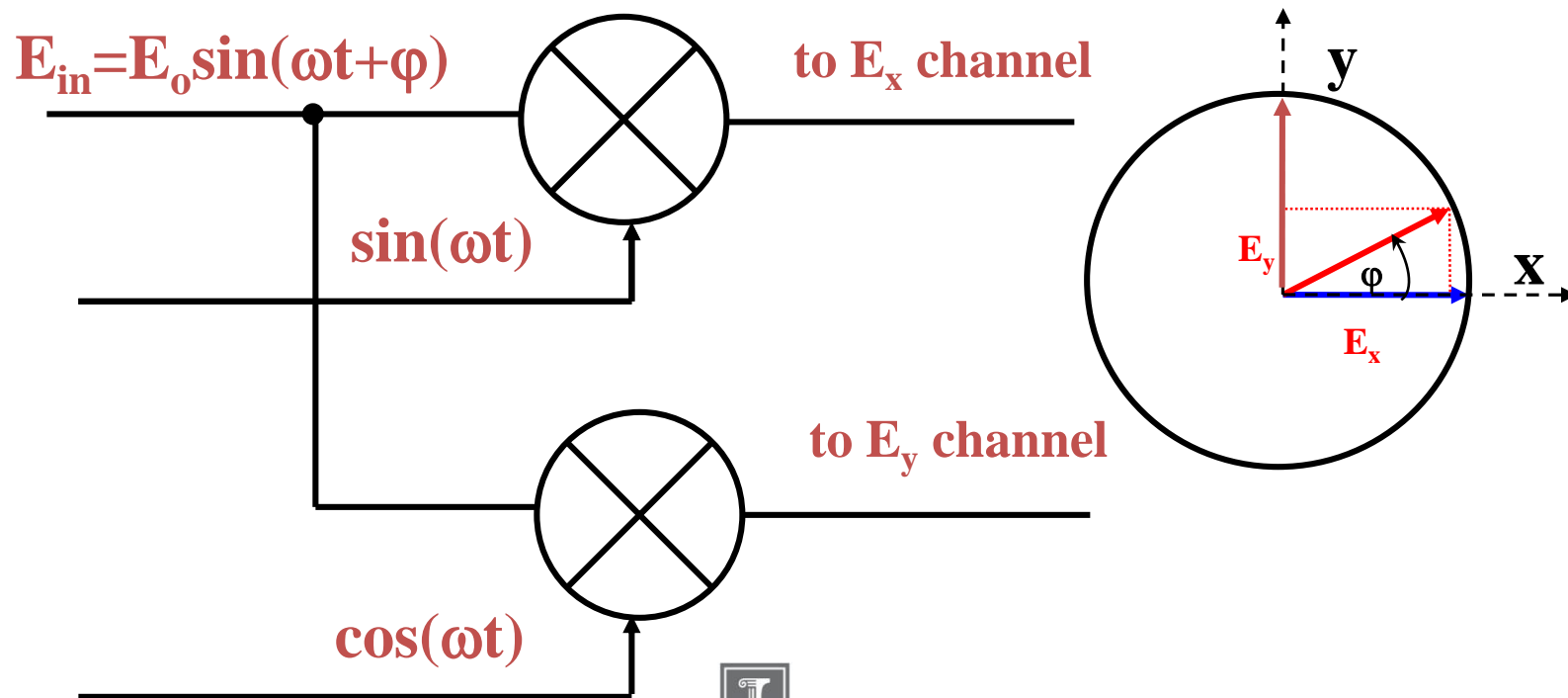
# Lock-in Amplifier. Two Channels Demodulation.

In many scientific applications it is a great advantage to measure both components ( $E_x$ ,  $E_y$ ) of the input signal. We can use two lock-ins to do this or we can measure these value in two steps providing the phase shift of reference signal  $0$  and  $\pi/2$ . Much better solution is to use the lock-in amplifier equipped by two demodulators.





# Digital Lock-in Amplifier

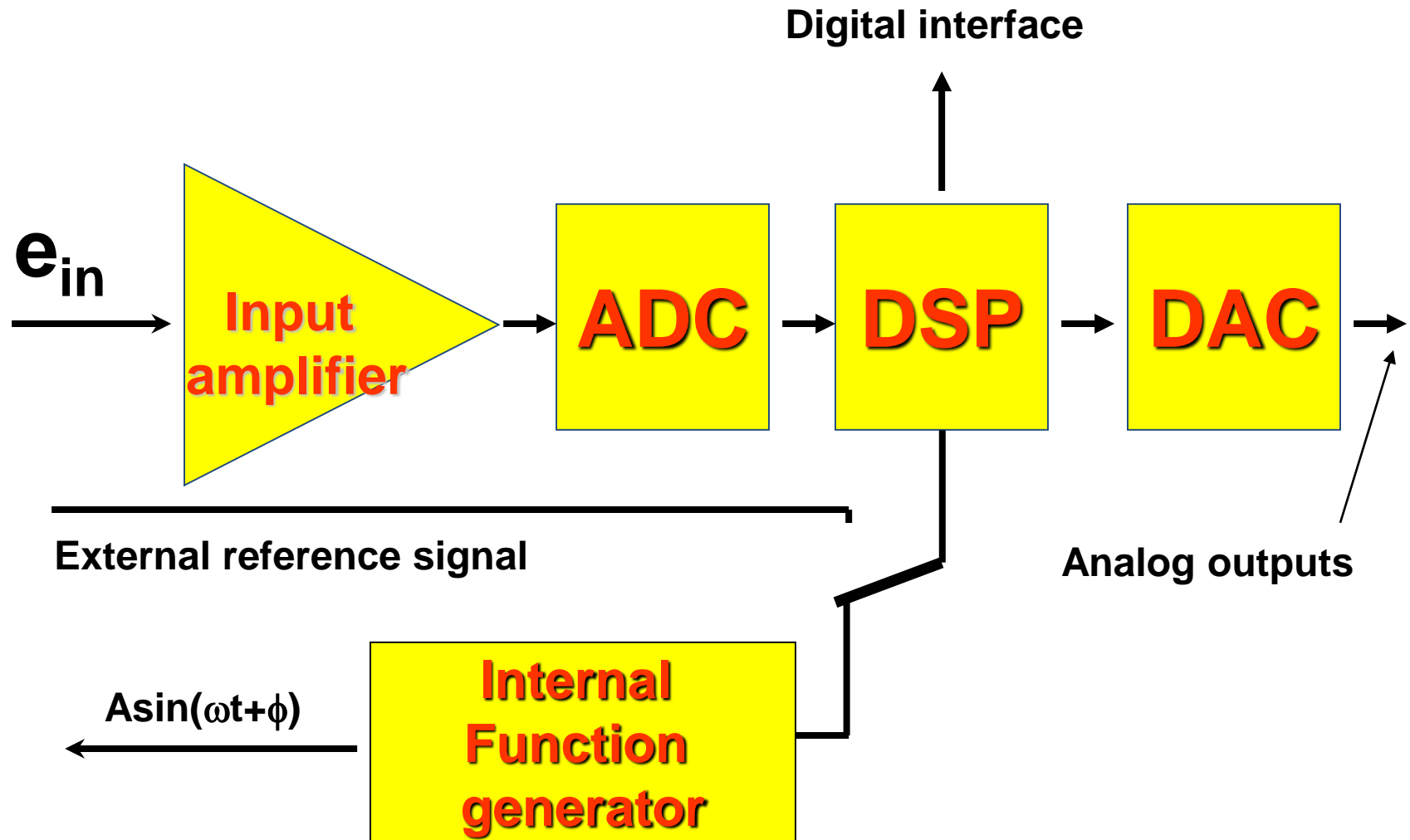

# SR830. Digital Lock-in Amplifier



In SR830 manual you can find the chapter dedicated to general description of the lock-in amplifier idea

## SR830 BASICS

### WHAT IS A LOCK-IN AMPLIFIER?

Lock-in amplifiers are used to detect and measure very small AC signals - all the way down to a few nanovolts! Accurate measurements may be made even when the small signal is obscured by noise

experiment at the reference frequency. In the diagram below, the reference signal is a square wave at frequency  $\omega_r$ . This might be the sync output from a function generator. If the sine output from

<\\engr-file-03\PHYINST\APL Courses\PHYCS401\Common\EquipmentManuals>



# Digital Lock-in amplifier. SR830

Time constant

And output filter sensitivity

Auto functions

Channel#1

Channel#2



Inputs

Notch filter settings


Analog outputs

Interface settings

Function generator


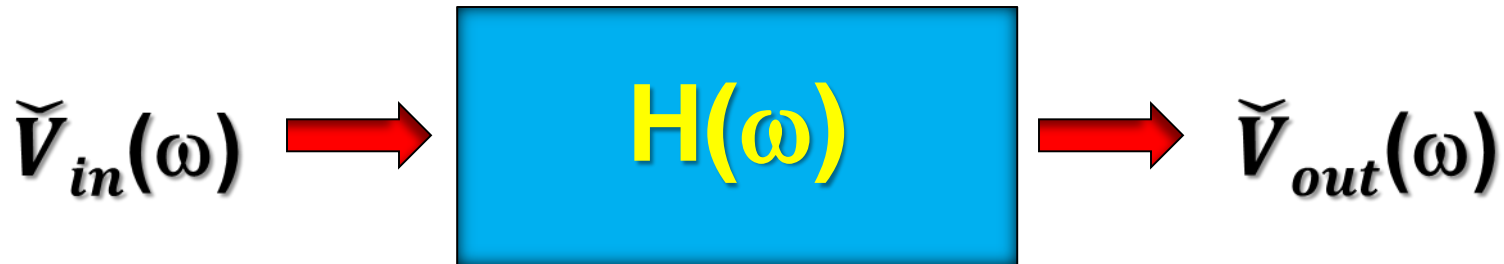
# Experiments. Main idea. Investigating the frequency response of circuit.




Frequency domain representation of the system

Response function  $\rightarrow \check{H}(\omega) = \frac{\check{V}_{out}(\omega)}{\check{V}_{in}(\omega)}$

Linear systems are those that can be modeled by linear differential equations.



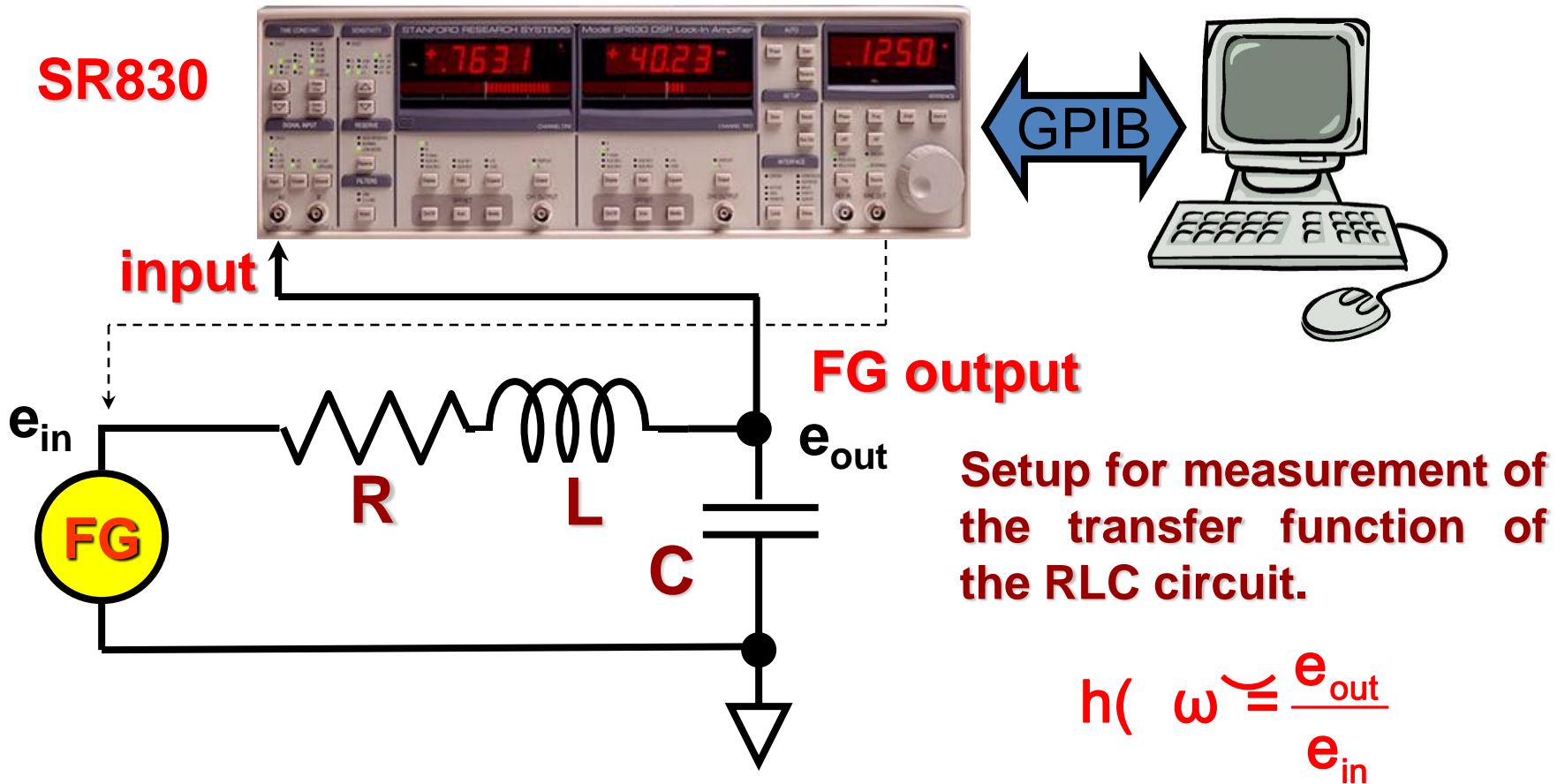
# Application of the Lock-in Amplifier for Study of the Transfer Function of the RLC Circuit



# Experiments. Main Idea.

## Calculation of the Response Function in Frequency Domain Mode.

### Example 1. High-pass filter.

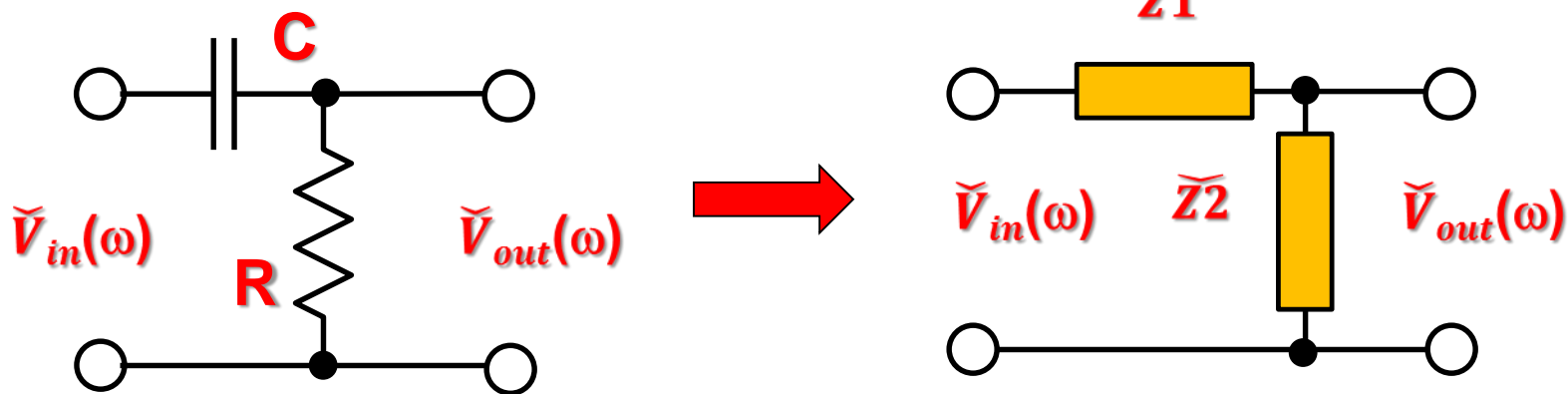


Applying the Kirchhoff Law to this simple network

$$\tilde{V}_{out}(\omega) = \tilde{H}(\omega) * \tilde{V}_{in}(\omega) = \tilde{V}_{in}(\omega) \frac{\tilde{Z}_2(\omega)}{\tilde{Z}_1(\omega) + \tilde{Z}_2(\omega)}$$


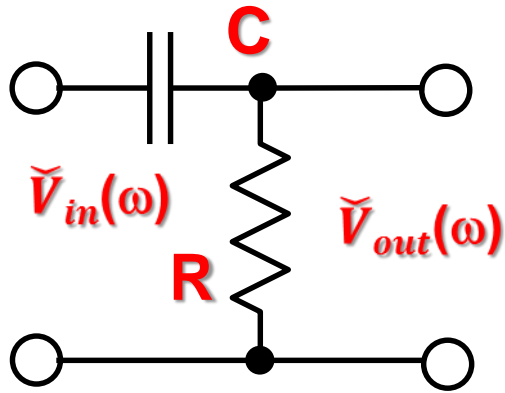
# Experiments. Calculation of the Response Function in Frequency Domain Mode. High-pass Filter



## Ideal case

$$\tilde{Z}_R = R$$

$$\tilde{Z}_L = j\omega L$$

$$\tilde{Z}_C = \frac{1}{j\omega C} = -\frac{j}{\omega C}$$

## More realistic

$$\tilde{Z}_R = R + \dots$$


$$\tilde{Z}_L = j\omega L + R_L$$

$$\tilde{Z}_C = \frac{1}{j\omega C} = \frac{1}{j\omega C + R_C^{-1}}$$

$$\tilde{V}_{out}(\omega) = \tilde{H}(\omega) * \tilde{V}_{in}(\omega) = \tilde{V}_{in}(\omega) \frac{\tilde{Z}_2(\omega)}{\tilde{Z}_1(\omega) + \tilde{Z}_2(\omega)}$$


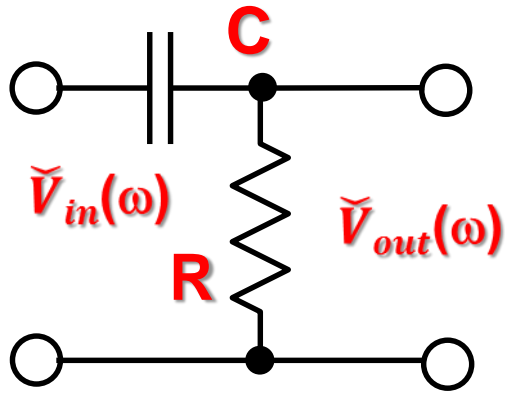
# Experiments. Calculation of the Response Function in Frequency Domain Mode. High-pass Filter



$\tau$  – time constant of the filter

$\omega_c$  - cutoff frequency

$$\tilde{H}(\omega) = H_R(\omega) + jH_I(\omega) = \frac{R}{R + \frac{1}{j\omega C}} = \frac{j\omega RC}{1 + j\omega RC} = \frac{j\omega\tau}{1 + j\omega\tau} = \frac{\omega\tau}{(1 + \omega^2\tau^2)}(\omega\tau + j);$$



where  $\tau = RC = \omega_c^{-1}$ ;

$$|\tilde{H}(\omega)| = \sqrt{H_R^2 + H_I^2} = \frac{\omega\tau}{\sqrt{1 + (\omega\tau)^2}}; \quad \theta(\omega) = \arctan\left(\frac{H_I(\omega)}{H_R(\omega)}\right) = \arctan\left(\frac{1}{\omega\tau}\right)$$





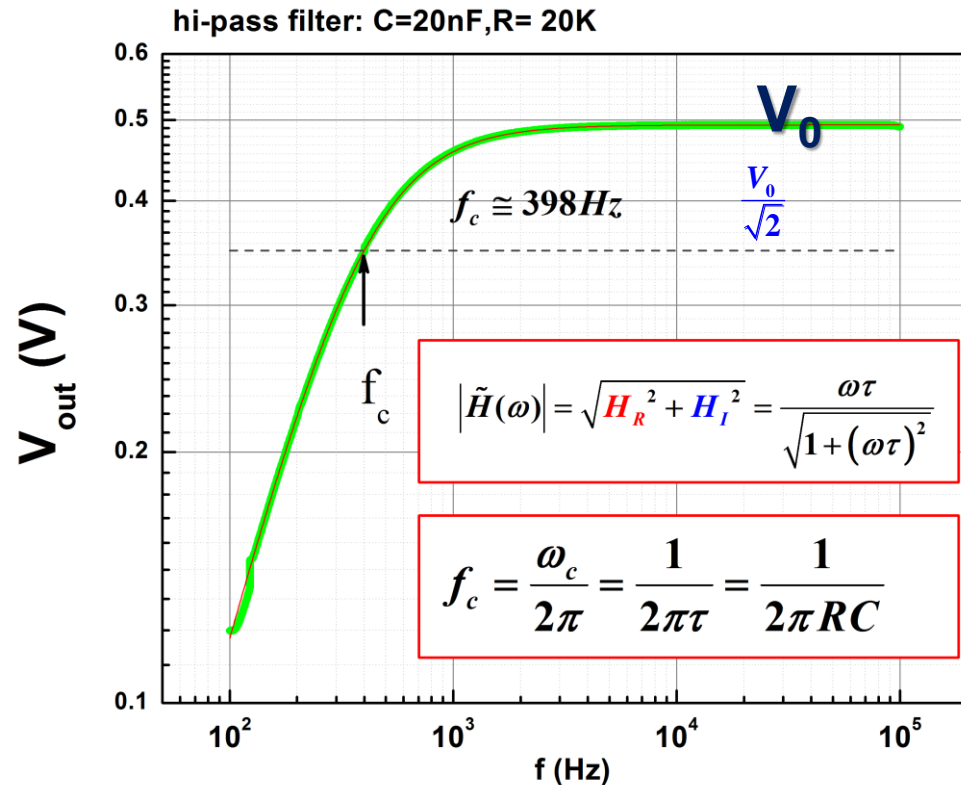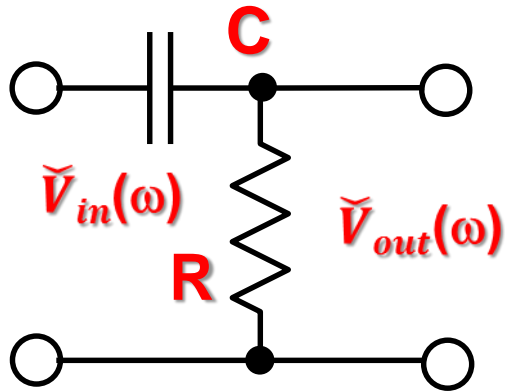
# Experiments. Calculation of the Response Function in Frequency Domain Mode. High-pass Filter



# High-pass Filter. Fitting.

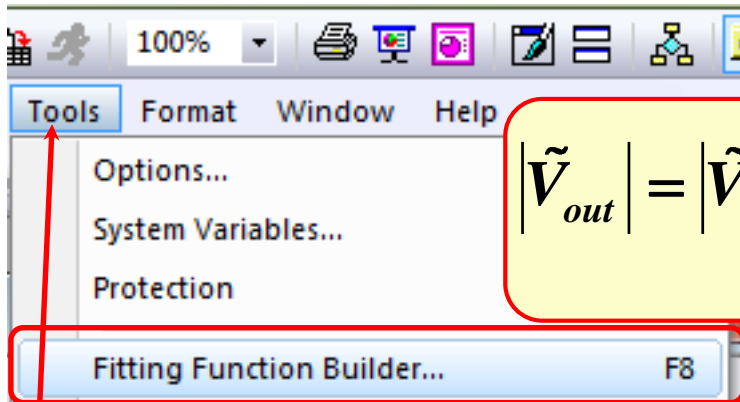

$$|\tilde{V}_{out}| = |\tilde{V}_{in}| * |\tilde{H}(\omega)| = V_0 * \frac{\omega\tau}{\sqrt{1 + (\omega\tau)^2}}; \quad \tau = RC$$

**Fitting parameters:  $V_0$ ,  $\tau$ ,  $V_{off}$**

V0,tau,Voff

| Param | Unit | Meaning | Fixed                    | Initial Value | Significant Digits |
|-------|------|---------|--------------------------|---------------|--------------------|
| V0    |      | ?       | <input type="checkbox"/> | 1             | System             |
| tau   |      | ?       | <input type="checkbox"/> | 1             | System             |
| Voff  |      | ?       | <input type="checkbox"/> | 1             | System             |



Function Body (Dependent Variables : y)

$$y = V_0 * 2 * \pi * x * \tau / \sqrt{1 + (2 * \pi * \tau)^2} + V_{off}$$




**Fitting function** →


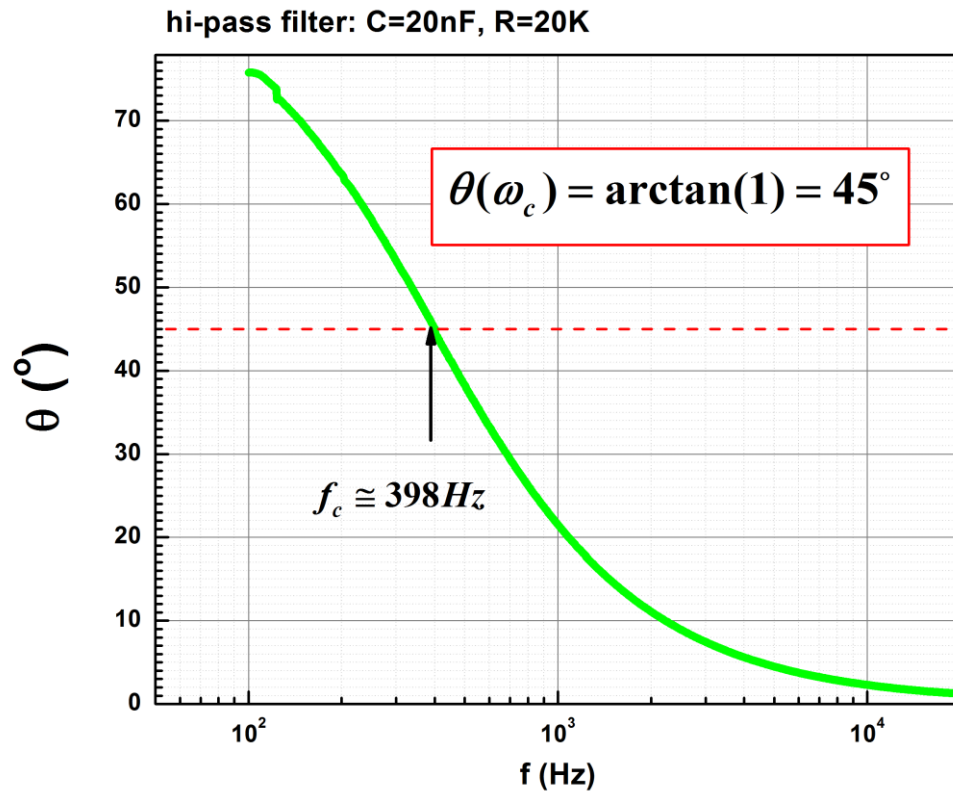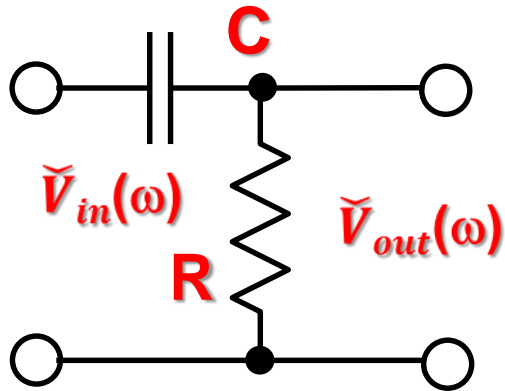
# Experiments. Calculation of the Response Function in Frequency Domain Mode. High-pass Filter.


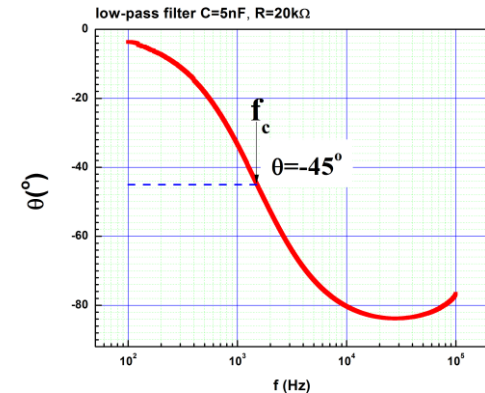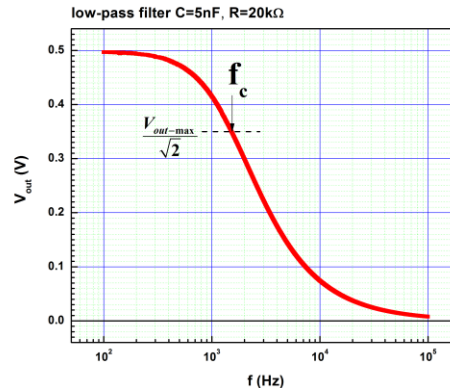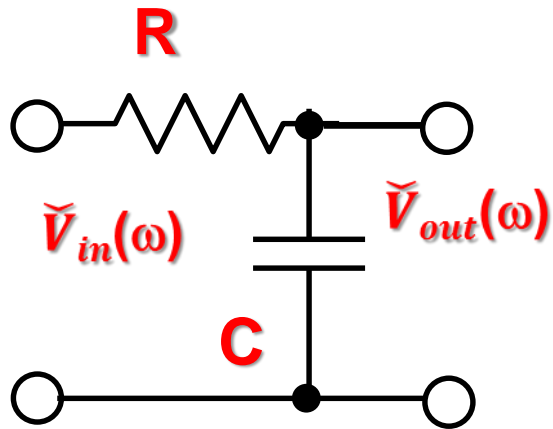
# Experiments. Calculation of the Response Function in Frequency Domain Mode. Low-pass Filter




$$\tilde{H}(\omega) = H_R(\omega) + jH_I(\omega) = \frac{1}{R + \frac{1}{j\omega C}} = \frac{1}{1 + j\omega RC} = \frac{1}{1 + j\omega\tau} = \frac{(1 - j\omega\tau)}{(1 + \omega^2\tau^2)};$$

where  $\tau = RC = \omega_c^{-1}$ ;

$$|\tilde{H}(\omega)| = \sqrt{H_R^2 + H_I^2} = \frac{1}{\sqrt{1 + (\omega\tau)^2}}; \quad \theta(\omega) = \arctan\left(\frac{H_I(\omega)}{H_R(\omega)}\right) = -\arctan(\omega\tau)$$


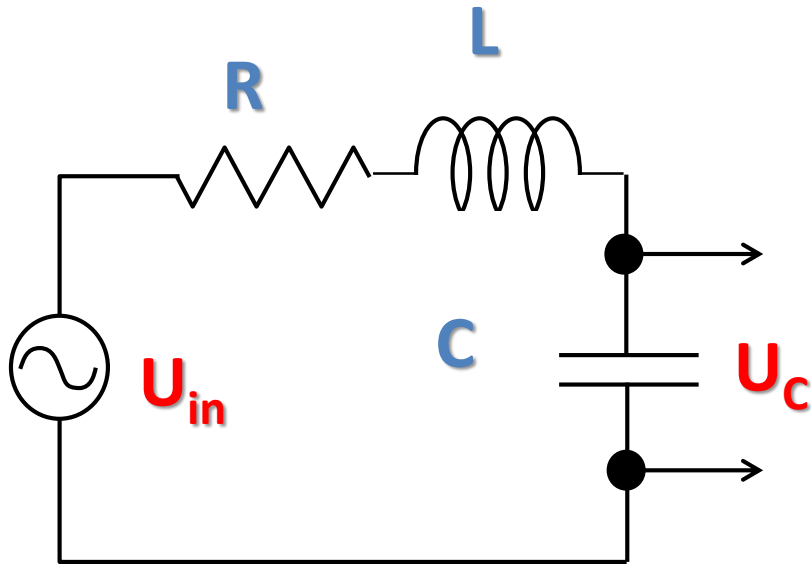
# Application of the Lock-in Amplifier for Study of the Transfer Function of the RLC Circuit .



$$U_C = U_{in} \cdot \frac{Z_C}{Z_C + Z_L + R} =$$
$$= \frac{1}{j\omega C} \frac{1}{\frac{1}{j\omega C} + j\omega L + R}$$



# Application of the Lock-in Amplifier for Study of the Transfer Function of the RLC Circuit .


$$H = \frac{U_c}{U_{in}} = \frac{1}{(1 - \omega^2 LC) + j\omega CR} = \frac{\left(1 - \left(\frac{\omega}{\omega_0}\right)^2\right) - j\omega CR}{\left(1 - \left(\frac{\omega}{\omega_0}\right)^2\right)^2 + \omega^2 C^2 R^2} \times;$$

$$\omega_0 = \frac{1}{\sqrt{LC}}; \nu \equiv \frac{\omega}{\omega_0}; Q = \frac{1}{R} \sqrt{\frac{L}{C}};$$

$$H = \frac{(1 - \nu^2) - j\frac{\nu}{Q}}{(1 - \nu^2)^2 + \frac{\nu^2}{Q^2}}; \theta = -\tan^{-1}\left(\frac{\nu}{Q(1 - \nu^2)}\right)$$



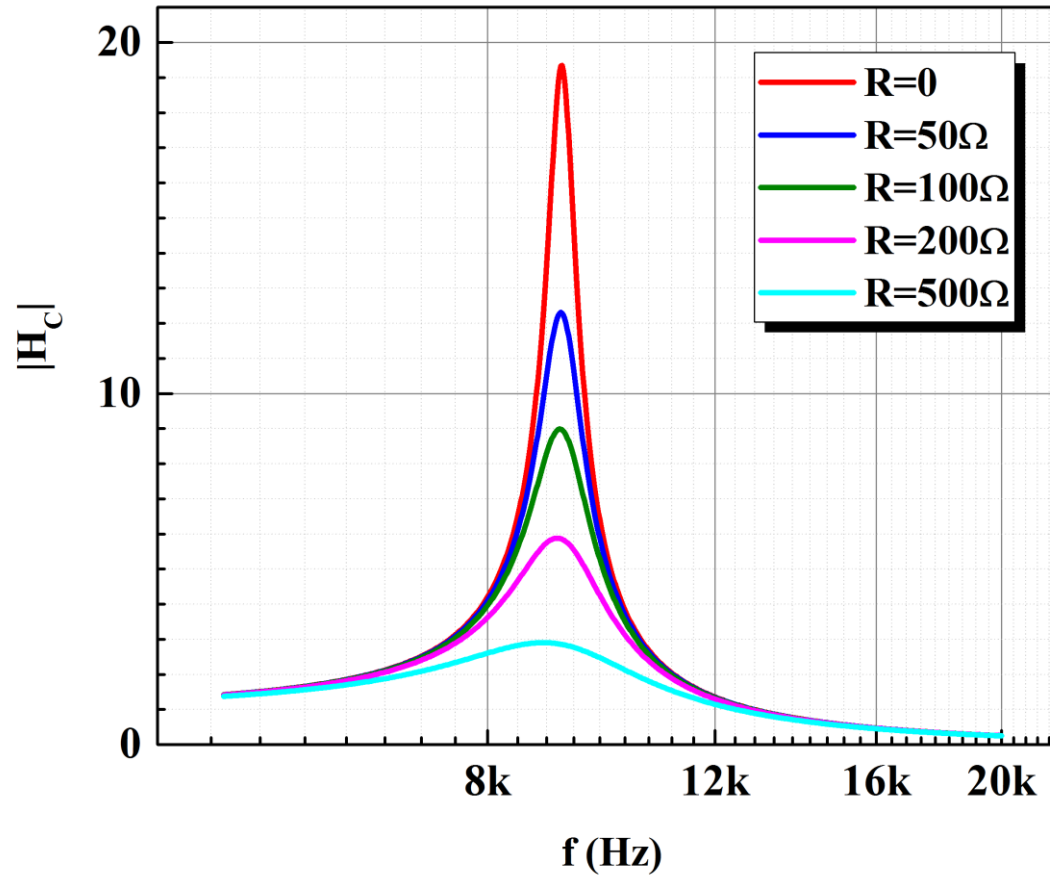
# Application of the Lock-in Amplifier for Study of the Transfer Function of the RLC Circuit .



The resonance curves obtained on RLC circuits with different damping resistors.


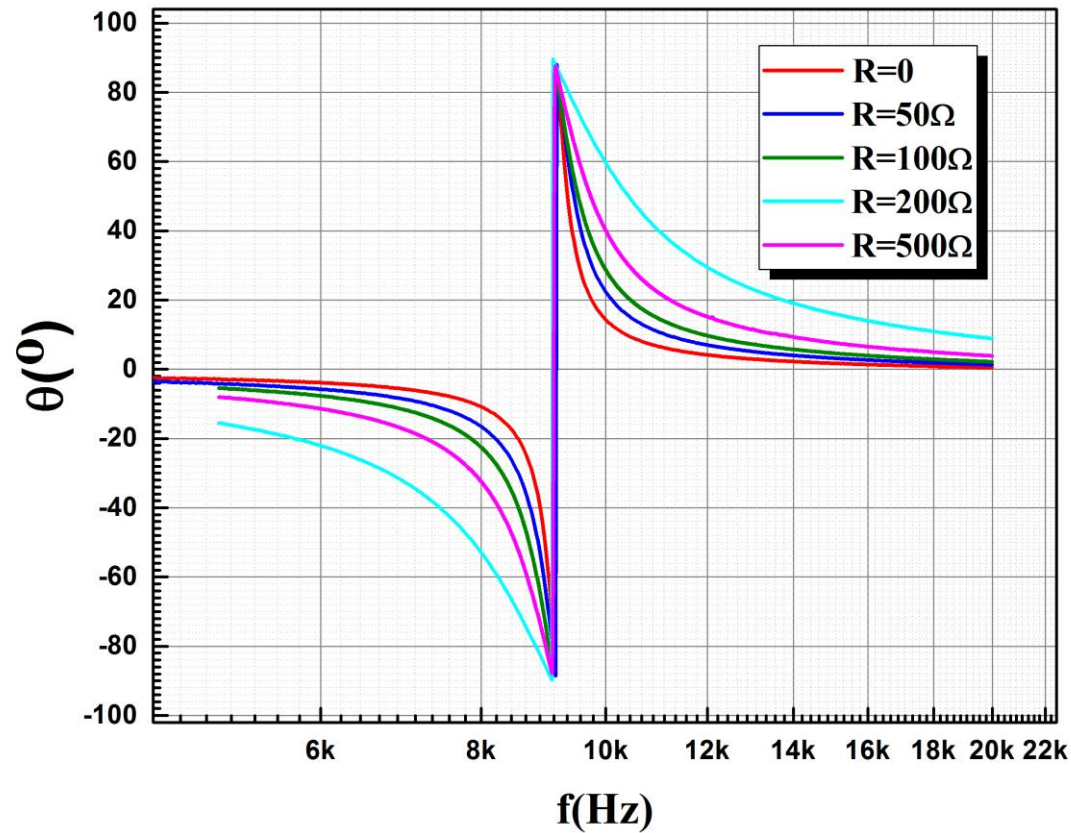
# Application of the Lock-in Amplifier for Study of the Transfer Function of the RLC Circuit




**The resonance curves obtained on RLC circuits with different damping resistors**





# Fitting. RLC Resonance Circuit.

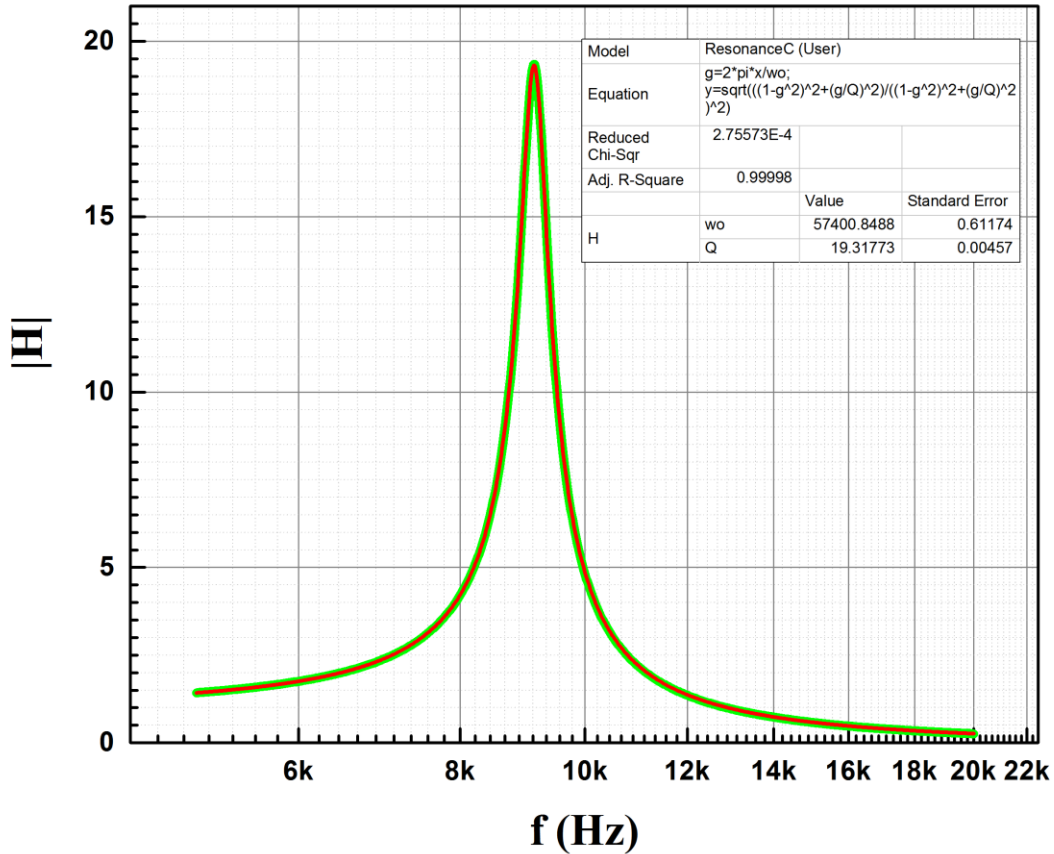


$$|H| = \frac{\sqrt{(1-\gamma^2)^2 + \left(\frac{\gamma}{Q}\right)^2}}{(1-\gamma^2)^2 + \left(\frac{\gamma}{Q}\right)^2}; \gamma = \frac{\omega}{\omega_0}$$

**fitting function for |H|**

**variable parameters:  
 $\omega_0$  and Q**


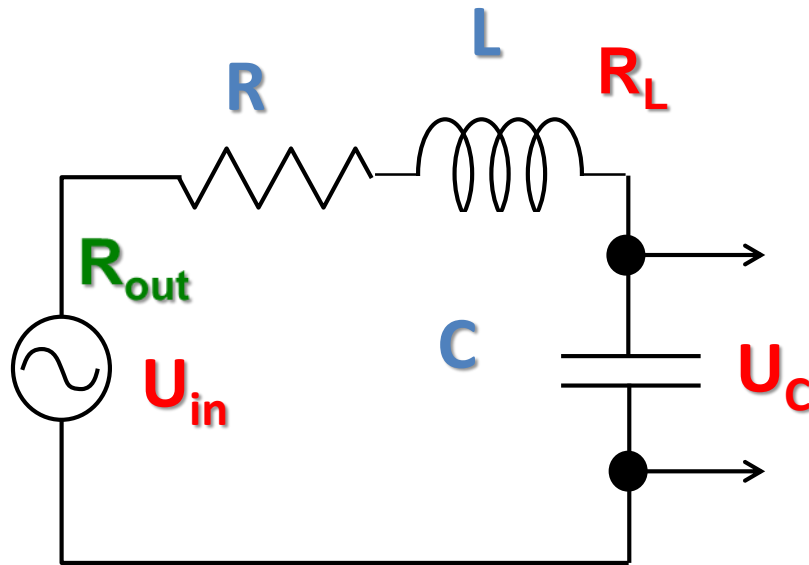
# Application of the Lock-in Amplifier for Study of the Transfer Function of the RLC Circuit




$$R=0; R_L=35.8\Omega; R_{out}=50\Omega$$

Actual damping resistance is a sum of  $R$ ,  $R_L$  (resistance of the coil) and  $R_{out}$  (output resistance of the function generator)

Actual  $R$  calculated from fitting pars is  $\sim 88.8\Omega$  what is reasonable close to  $85.8\Omega$



# Fitting. RLC Resonance Circuit.

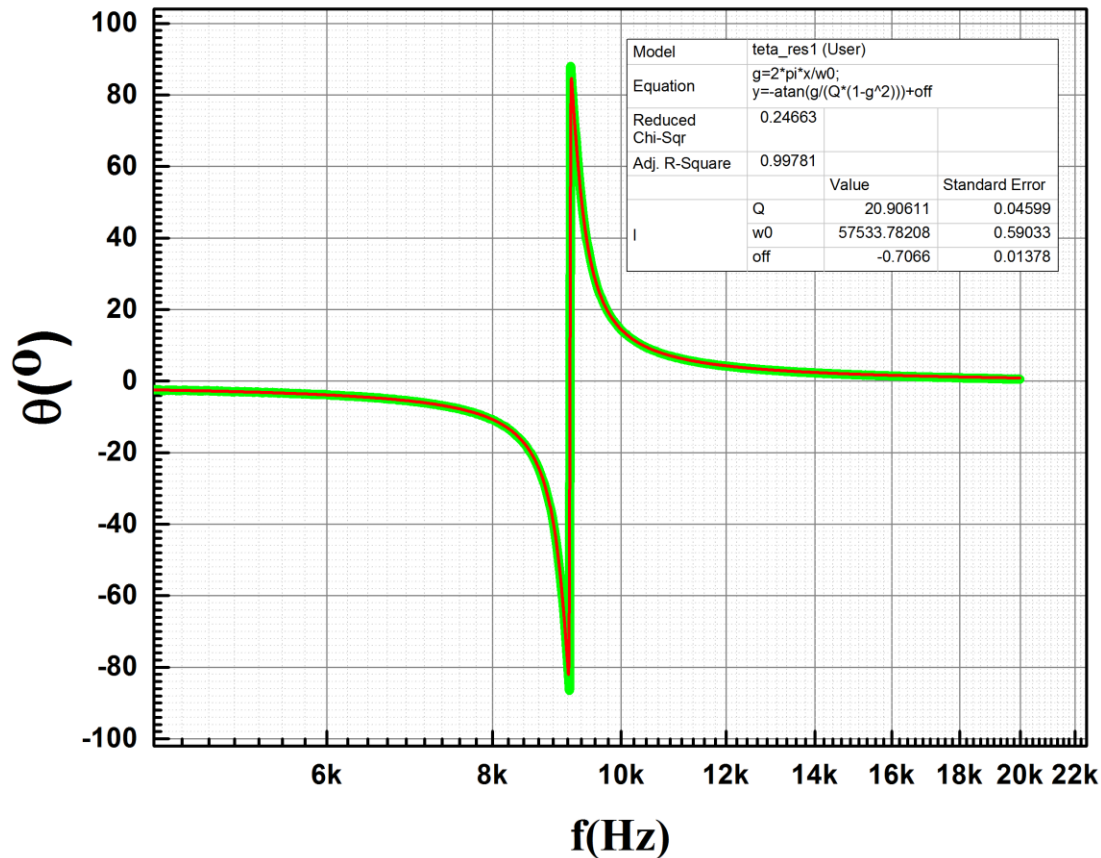

$$\theta = \tan^{-1} \left( \frac{Y}{X} \right)$$

measured


$$\theta = -\tan^{-1} \left( \frac{\gamma}{Q(1-\gamma^2)} \right); \gamma = \frac{\omega}{\omega_0}$$

fitting function

variable parameters:  
 $\omega_0$  and  $Q$




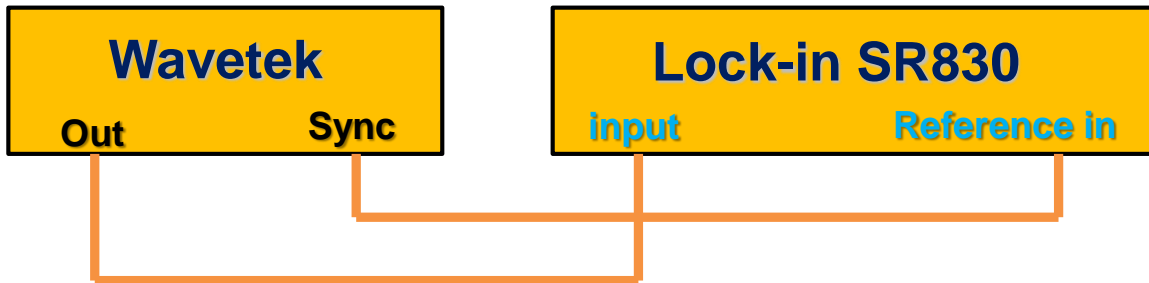
# From Time Domain to Frequency Domain. Experiment.



$$V = V_0 \left( 0 < t \leq \frac{T_0}{2} \right);$$

$$-V_0 \left( \frac{T_0}{2} < t \leq T_0 \right)$$

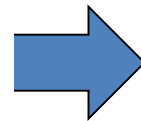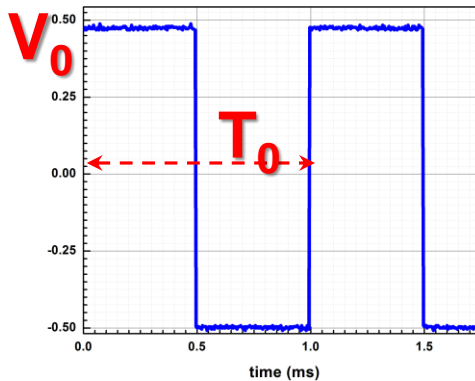$F(t)$  – periodic function  $F(t)=F(t+T_0)$ :



Frequency  
domain ?

$$a_n = \frac{2}{T_0} \int_0^{T_0} F(t) \cos\left(\frac{2\pi nt}{T_0}\right) dt;$$


$$b_n = \frac{2}{T_0} \int_0^{T_0} F(t) \sin\left(\frac{2\pi nt}{T_0}\right) dt;$$

$$a_0 = \frac{2}{T_0} \int_0^{T_0} F(t) dt$$

Time domain pattern



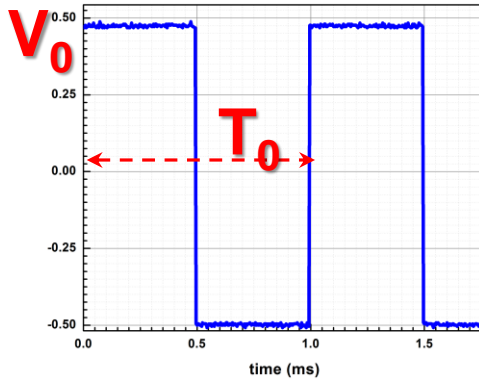
# From Time Domain to Frequency Domain. Experiment with SR830. Results.



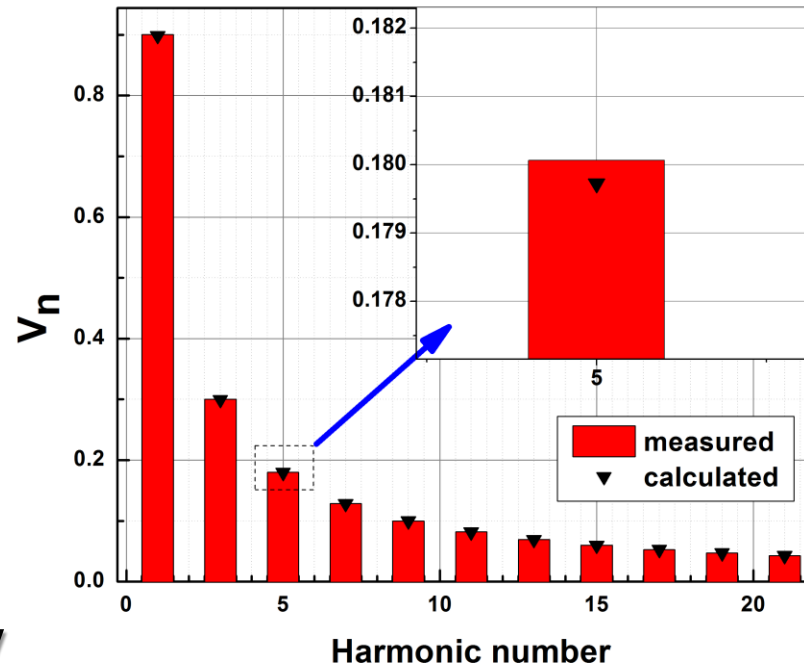**Time domain**


**Spectrum measured by  
SR 830 lock-in amplifier**



**Frequency domain**



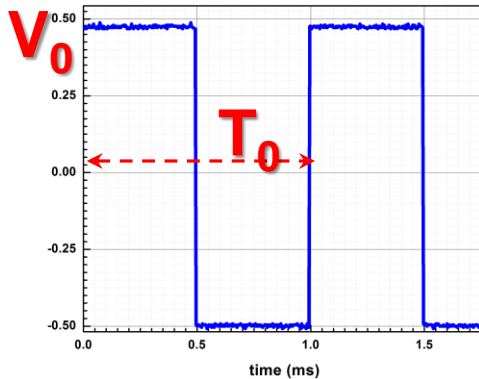
# From Time Domain To Frequency Domain. FFT using Origin. Results.




**Data file can be used to convert time domain to frequency domain**


**Time domain taken by Tektronix scope**

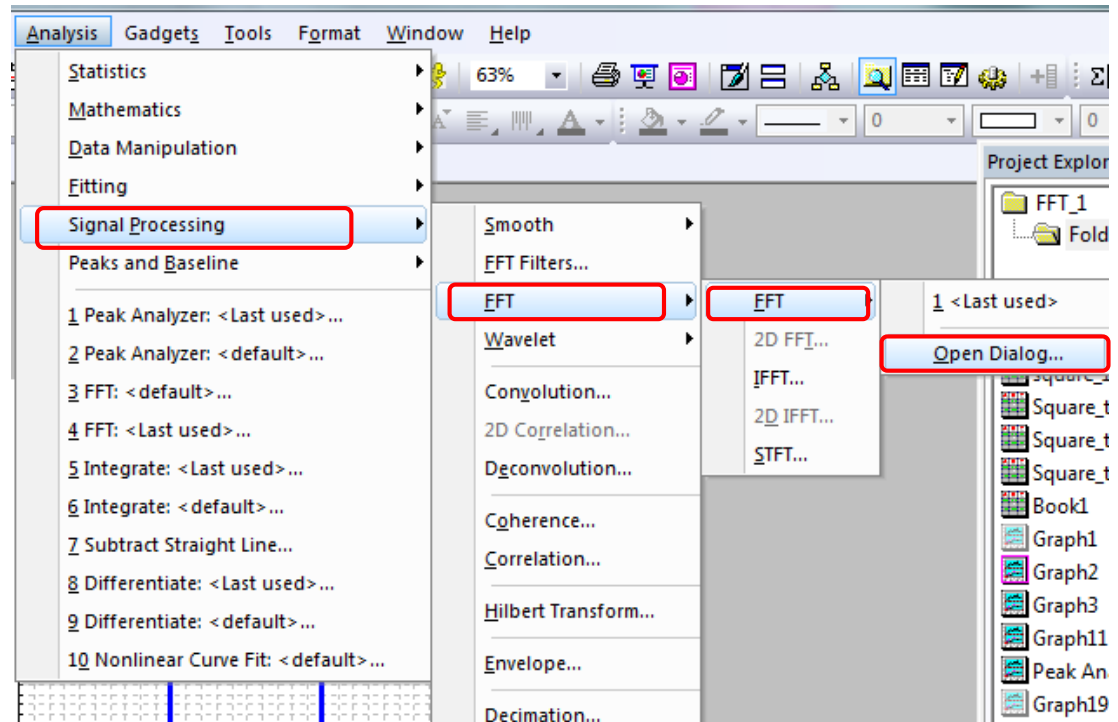
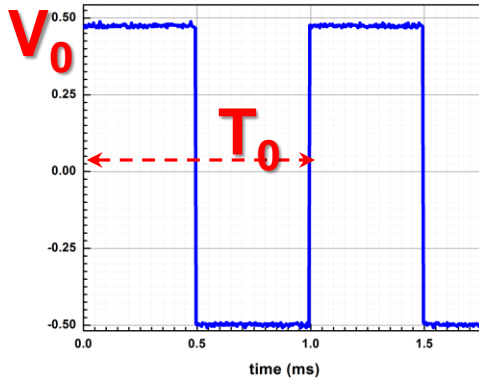
# From Time Domain to Frequency Domain. FFT using Origin. Results.



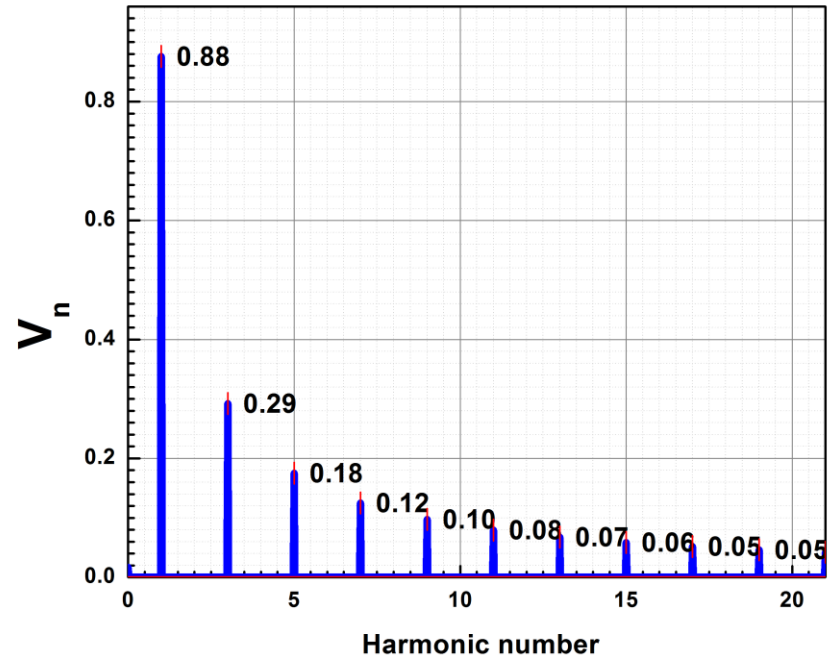
**Time domain taken by  
Tektronix scope**




**Spectrum calculated by Origin. Accuracy is  
limited because of the limited resolution of  
the scope**


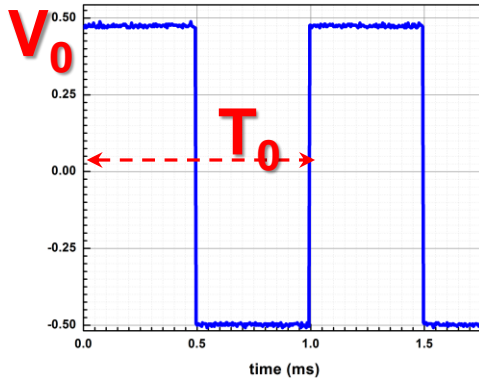
# From Time Domain to Frequency Domain. Using of the Math Option of the Scope.



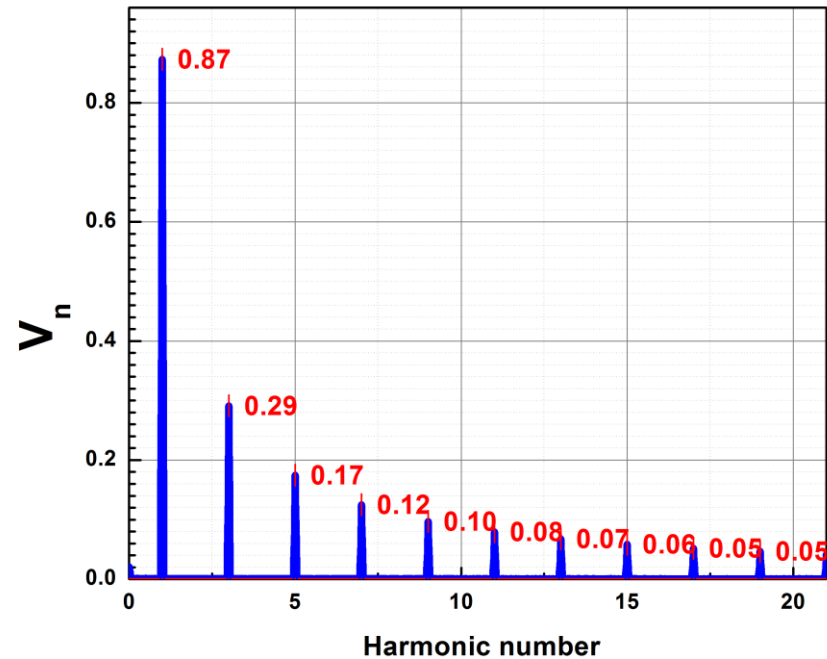**Time domain taken by  
Tektronix scope**




**Spectrum calculated by  
Tektronix scope.**

**Accuracy is limited because of the  
limited resolution of the scope**





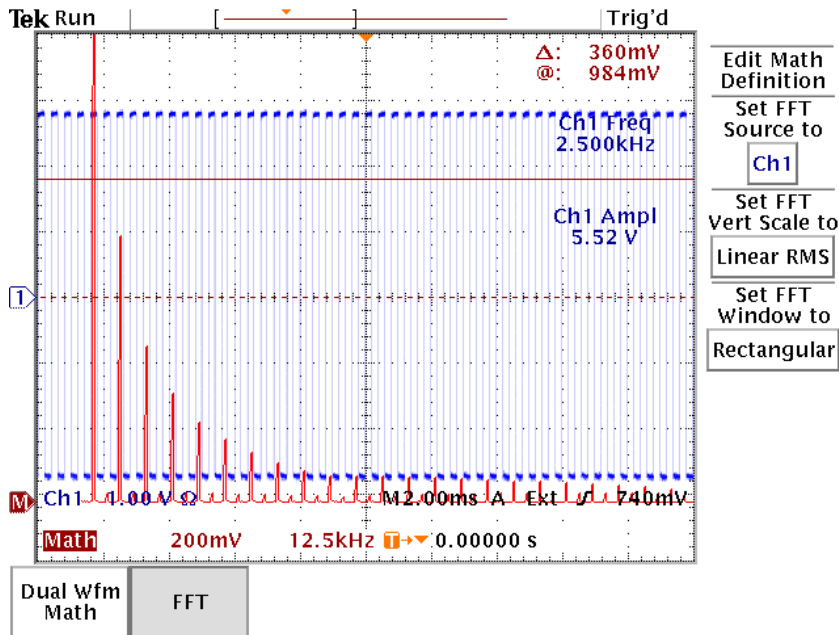
# From Time Domain to Frequency Domain. Using of the Math Option of the Scope.




**Spectrum of the square wave signal**

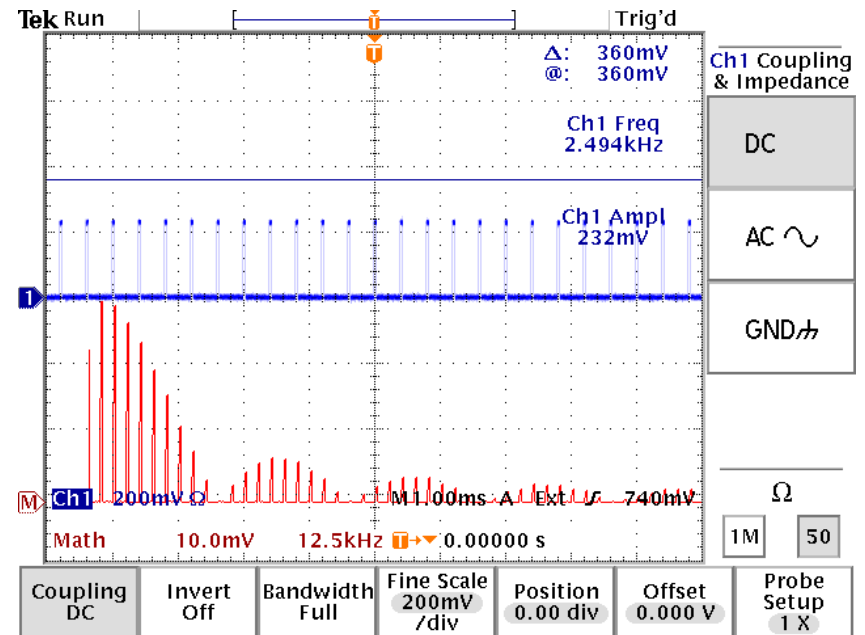




**Spectrum of the pulse signal**




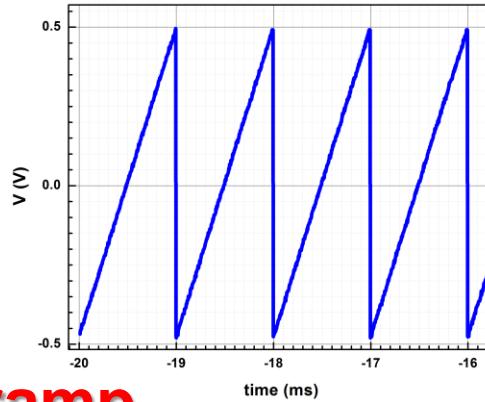
# From Time Domain to Frequency Domain. Different Waveforms. Using Lock-in.



**ramp**

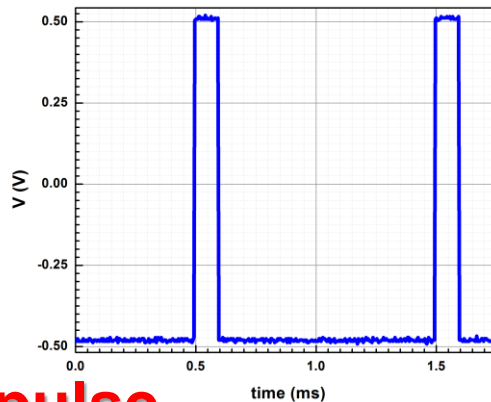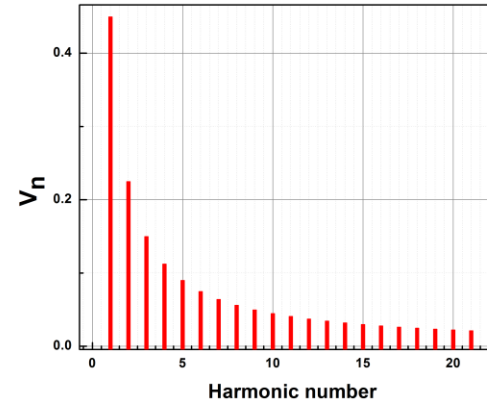
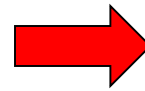


**pulse**

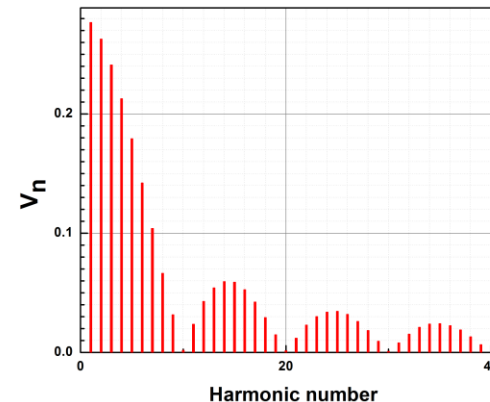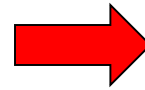

# Appendix #1

## Origin templates for the this week Lab:

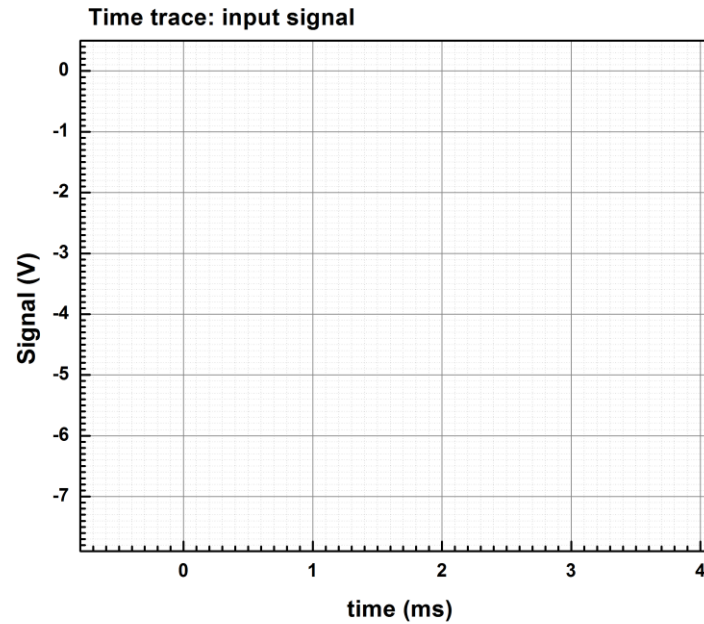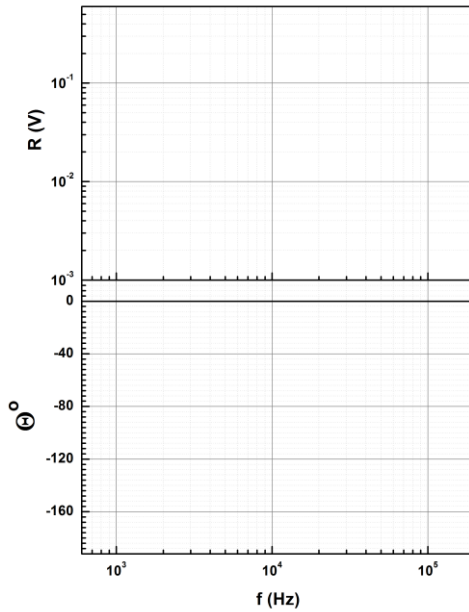

Physics401



# References:

1. John H. Scofield, “A Frequency-Domain Description of a Lock-in Amplifier” *American Journal of Physics* 62 (2) 129-133 (Feb. 1994).
  2. *Steve Smith* “The Scientist and Engineer's Guide to Digital Signal Processing” copyright ©1997-1998 by Steven W. Smith. For more information visit the book's website at: [www.DSPguide.com](http://www.DSPguide.com)”\*
- You can find a soft copy of this book in:
  - [llengr-file-03\phyinst\APL Courses\PHYCS401\Experiments](file:///lengr-file-03/phyinst/APL%20Courses/PHYCS401/Experiments)

