



AC Circuits
using complex impedances

Lecture Outline

- **Special Lecture on Complex Impedance:**
 - $V_{ac} = \epsilon_0 e^{i\omega t}$ $Z_R = R$, $Z_L = i\omega L$, $Z_C = 1/i\omega C$
- **Introduction:**
 - resistor networks, equivalent R_{eff} , Kirchhoff's Laws
 - purpose of lecture: same at ac for R, C, and L elements
- **Complex Numbers and Functions:**
 - $e^{i\omega t}$ is a rotating 2D *unit* vector in complex plane
 - complex impedances relate current & voltage for Resistors, Capacitors, and (L)inductors.
- **Application to Any Driven LCR Circuit:**
 - series RLC circuit (like in last/next lecture)
 - parallel RLC circuit
 - any network with RLC at any freq.
 - low pass filter

Introduction

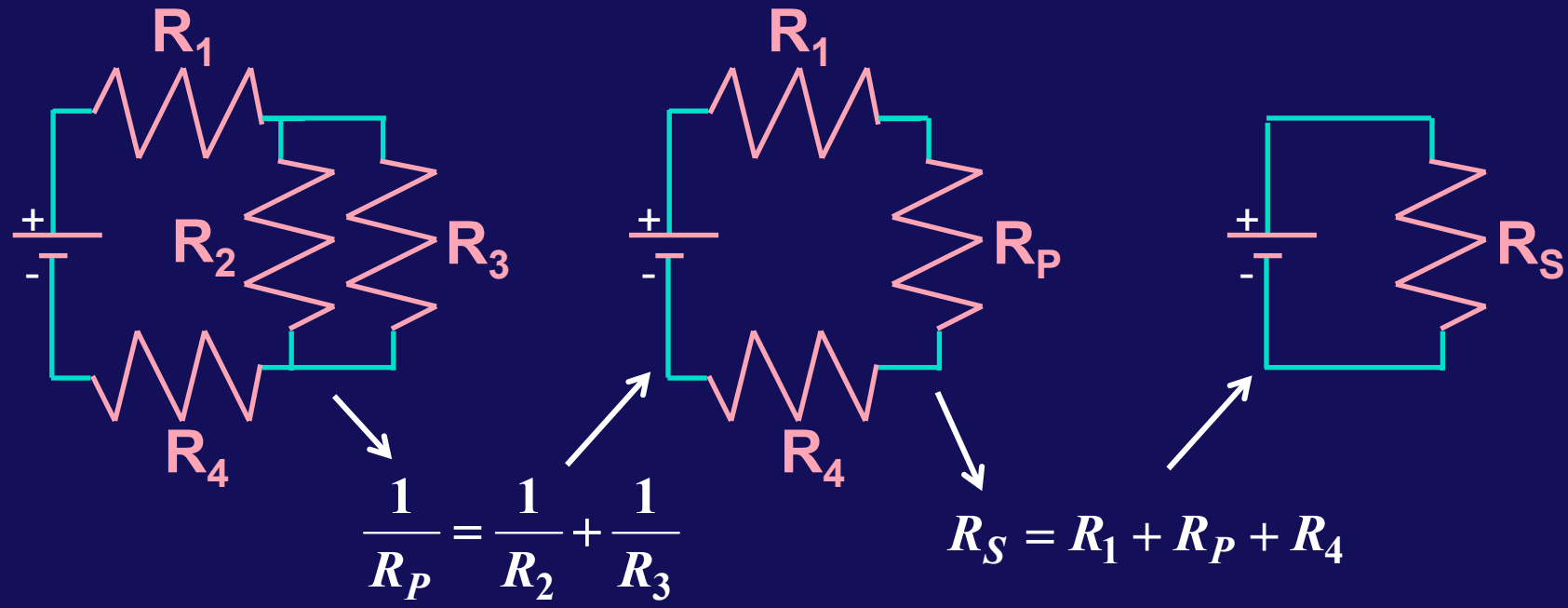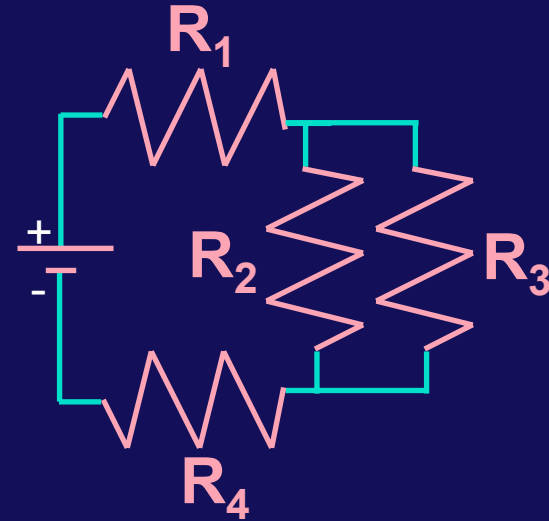- Remember good old dc circuits involving only batteries and resistors?
 - All branch currents proportional to voltage across branch
 - solve this with Kirchoff's voltage & current laws
 - resistor networks expressed as equivalent resistances



Introduction

- Problem extending this idea to ac circuits with R, L and C:
 - current through R is proportional to voltage across R
 - current through L and C not proportional to voltage (using real numbers/functions)
 - phase between I and V
 - for series RLC circuit phasor algebra gives a clumsy answer
- New Idea:
 - represent currents and voltages in circuits as complex functions of time
 - measured value of voltage or current is **real part** of complex value you get at the end of the calculation
 - current through L or C is proportional to voltage across L or C
 - **complex impedance** plays role of resistance as in dc circuits but *automatically* contain phase shift of voltage *vis a vis* current
 - how does this happen -> via rules of complex number algebra!

complex number algebra

- **definition:** $i = \sqrt{-1}$


- **so that** $i^2 = -1$ $i^3 = -i$ $i^4 = 1$

- **definition:** $z = x + iy$

- **looks like a 2-D vector space (x,y)**

- **provides a natural description of phasors**


- **length or modulus** $|z| = \sqrt{x^2 + y^2} = \sqrt{(\operatorname{Re} z)^2 + (\operatorname{Im} z)^2}$

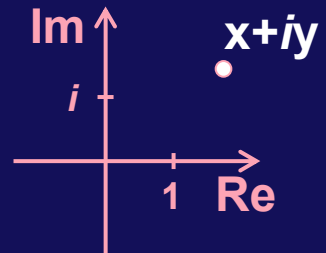

- **complex numbers** provide solution to algebraic equations that have none with only real numbers

$$z^2 - 2z + 5 = 0$$
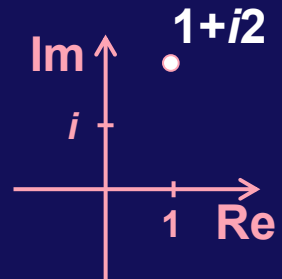
$$z = 1 \pm \frac{1}{2} \sqrt{4 - 20} = 1 \pm \sqrt{-4} = 1 \pm i2$$




- **Next:**

- **including trig functions in complex functions -> $\cos(\omega t)$**

complex number algebra

- **addition:** $(a+ib) + (c+id) = (a+c) + i(b+d)$

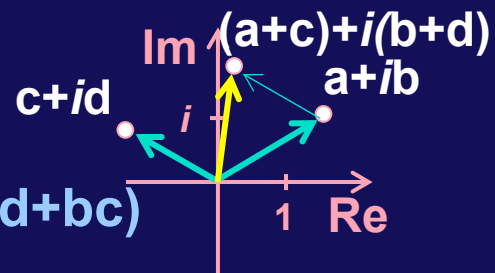- **so that addition is component-wise or vectorial**



- **multiplication:** $(a+ib) \times (c+id) = (ac-bd) + i(ad+bc)$

- **remember $i^2 = -1$**


- **Trigonometric functions, the unit circle:**

- **if $z = \cos\theta + i\sin\theta$, then length is 1 - unit circle**

- **exponential representation:**

prove using expansion formulae for exp, sin and cos functions.
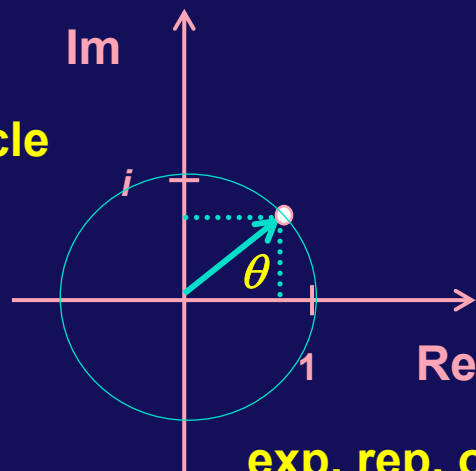
$$e^{i\theta} = \cos\theta + i\sin\theta$$



exp. rep. of any point

they multiply like exponents:

$$e^{i\theta} \cdot e^{i\phi} = (\cos\theta + i\sin\theta) \cdot (\cos\phi + i\sin\phi)$$

$$= (\cos\theta\cos\phi - \sin\theta\sin\phi) + i(\sin\theta\cos\phi + \cos\theta\sin\phi)$$

$$= \cos(\theta + \phi) + i\sin(\theta + \phi)$$

$$= e^{i(\theta+\phi)}$$

$$\theta = \tan^{-1}\left(\frac{\text{Im}z}{\text{Re}z}\right)$$

$$z = re^{i\theta} = r(\cos\theta + i\sin\theta)$$

Expanding exponential and sin & cos functions

- Write $e^{i\theta}$ and $\cos\theta + i \sin\theta$ in power series expansion and show they are equal

$$e^x = 1 + x + \frac{1}{2!}x^2 + \frac{1}{3!}x^3 + \frac{1}{4!}x^4 + \dots + \frac{1}{n!}x^n + \dots$$

$$e^{i\theta} = 1 + i\theta - \frac{1}{2!}\theta^2 - i\frac{1}{3!}\theta^3 + \frac{1}{4!}\theta^4 + \dots + \frac{i^n}{n!}\theta^n + \dots$$


$$e^{i\theta} = 1 - \frac{1}{2!}\theta^2 + \frac{1}{4!}\theta^4 + i\left(\theta - \frac{1}{3!}\theta^3\right) + \dots$$

$$e^{i\theta} = \cos\theta + i\sin\theta$$


complex number algebra/circuit application

- Our sinusoidal phasor voltage and current functions have convenient exponential representations:
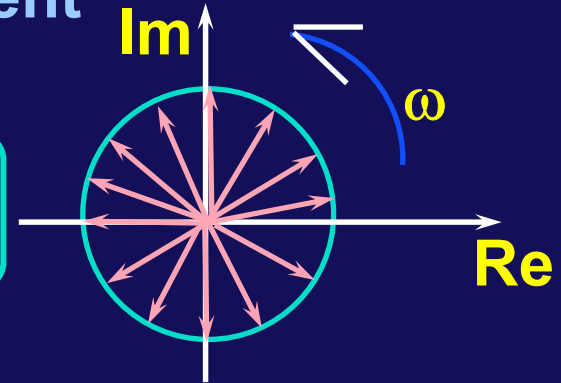
$$V(t) = V_o e^{i\omega t} = V_o (\cos \omega t + i \sin \omega t)$$



Use this in a circuit, first a resistor:

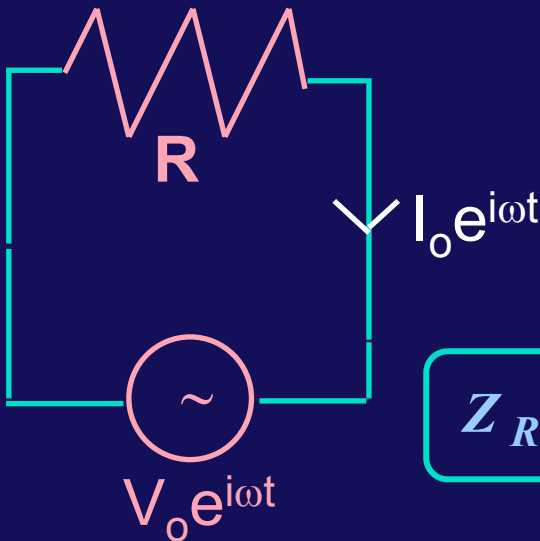

$$Z_R = R$$

In general case, I_o is complex with a magnitude and phase


Here, I_o is real with phase = 0, and magnitude = V_o/R

Capacitor and inductor are much more interesting....

Impedances of capacitors and inductors

$$V(t) = V_o e^{i\omega t} = V_o (\cos \omega t + i \sin \omega t)$$

- Consider a capacitor driven by $V(t)$:

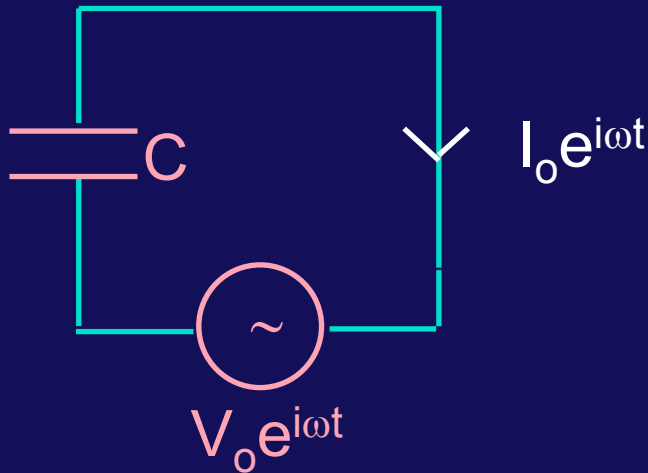

Looks like “resistor”:
current proportional to
voltage, but....

$$Z_C = \frac{1}{i\omega C}$$

In this case, I_o is complex
with a magnitude and phase

Recall that $Q(t) = CV(t)$. Since
 $I(t) = dQ/dt$, we must differentiate
 $V(t)$ to get current.

$$I_o e^{i\omega t} \equiv I(t)$$

$$= \frac{d}{dt} C V_o e^{i\omega t} = i\omega C V_o e^{i\omega t}$$


$$\cancel{I_o e^{i\omega t}} = i\omega C V_o \cancel{e^{i\omega t}}$$

$$V_o = I_o \frac{1}{i\omega C} \quad \leftarrow \text{voltage lags current}$$

Impedances of capacitors and inductors

$$V(t) = V_o e^{i\omega t} = V_o (\cos \omega t + i \sin \omega t)$$

- Consider an inductor driven by $V(t)$:

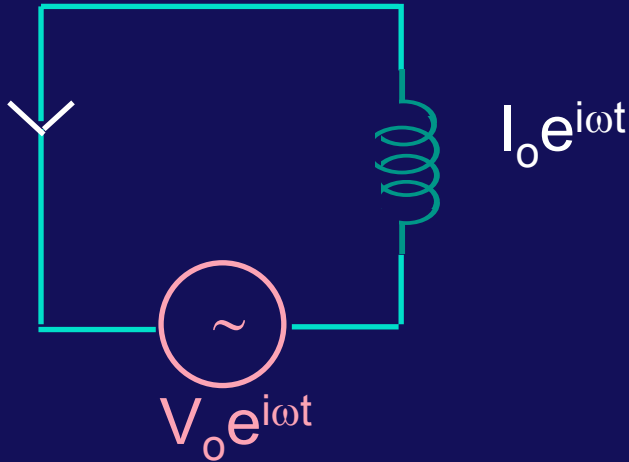

Looks like resistor:
current proportional to
voltage

$$Z_L = i\omega L$$

In this case, too, I_o is complex
with a magnitude and phase

Recall that $V(t) = L di/dt$. Now we
must differentiate $I(t)$ to get voltage.

$$V_o e^{i\omega t} = L \frac{d}{dt} I_o e^{i\omega t}$$


$$\cancel{V_o e^{i\omega t}} = i\omega L I_o \cancel{e^{i\omega t}}$$

$$V_o = i\omega L I_o$$

↖ voltage leads current

Complex impedances

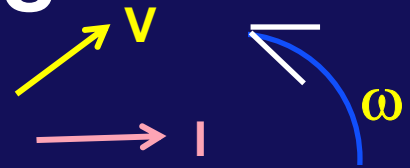- Make a table to show impedance for different circuit elements:




circuit element	complex impedance, Z	If $I = I_o e^{i\omega t}$ what is V_o	math	phasor picture
R	$Z_R = R$	$V_o = I_o R$		
L	$Z_L = i\omega L$	$V_o = I_o i\omega L$	$i = e^{i\frac{\pi}{2}}$ $V_L \propto e^{i\left(\omega t + \frac{\pi}{2}\right)}$	
C	$Z_C = \frac{1}{i\omega C}$	$V_o = I_o \frac{1}{i\omega C}$	$-i = e^{-i\frac{\pi}{2}}$ $V_C \propto e^{i\left(\omega t - \frac{\pi}{2}\right)}$	

Series LCR Circuit

- Back to the original problem: the loop equation gave us before:
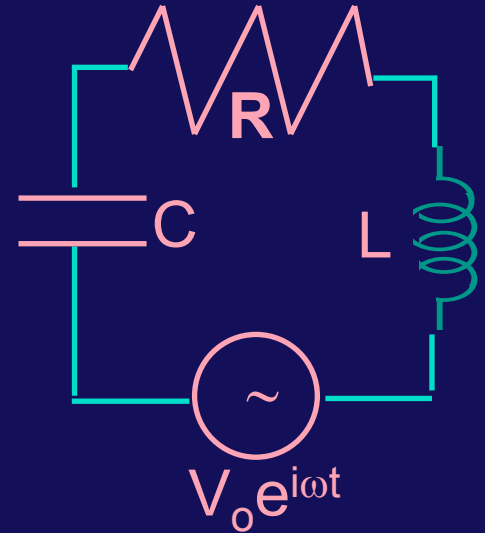
$$L \frac{d^2 Q}{dt^2} + \frac{Q}{C} + R \frac{dQ}{dt} = V_o \sin \omega t$$



- Now use complex impedances and assume an ac current of the form $I(t) = I_o e^{i\omega t}$

- KVL gives us: $V_o = I_o \left(R + \frac{1}{i\omega C} + i\omega L \right)$

$$V_o = I_o \left(R + iL \left(-\frac{1}{\omega LC} + \omega \right) \right)$$

$$V_o = I_o \left(R + i \frac{L}{\omega} (\omega^2 - \omega_o^2) \right)$$

$$\omega_o^2 = \frac{1}{LC}$$

Series LCR AC Circuit

- using complex impedances and assuming an ac current of the form $I(t) = I_o e^{i\omega t}$

- KVL gave us: $V_o = I_o \left(R - i \frac{1 - \omega^2 LC}{\omega C} \right)$



$$\phi = \tan^{-1} \left(\frac{\omega^2 LC - 1}{\omega RC} \right)$$

Impedance $Z(\omega)$
is a complex number


$$Z_{series} = Z \cdot e^{i\phi}$$

$$Z = \sqrt{R^2 + \left(\frac{1 - \omega^2 LC}{\omega C} \right)^2}$$

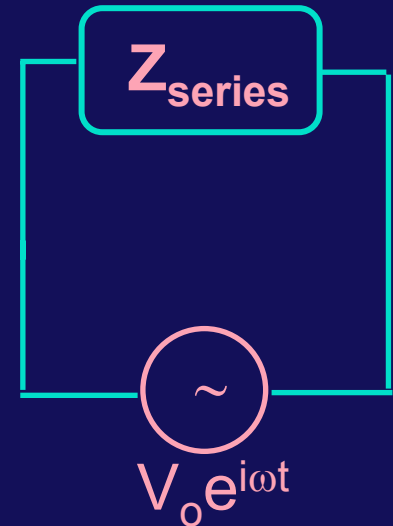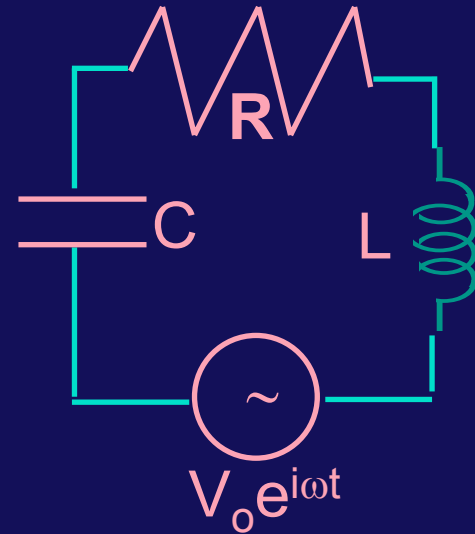
resonance when
the numerator $\rightarrow 0$



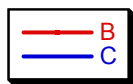- On resonance, the current is a maximum.
- If R is very small, the current will tend to go to infinity on resonance




current through series RLC network

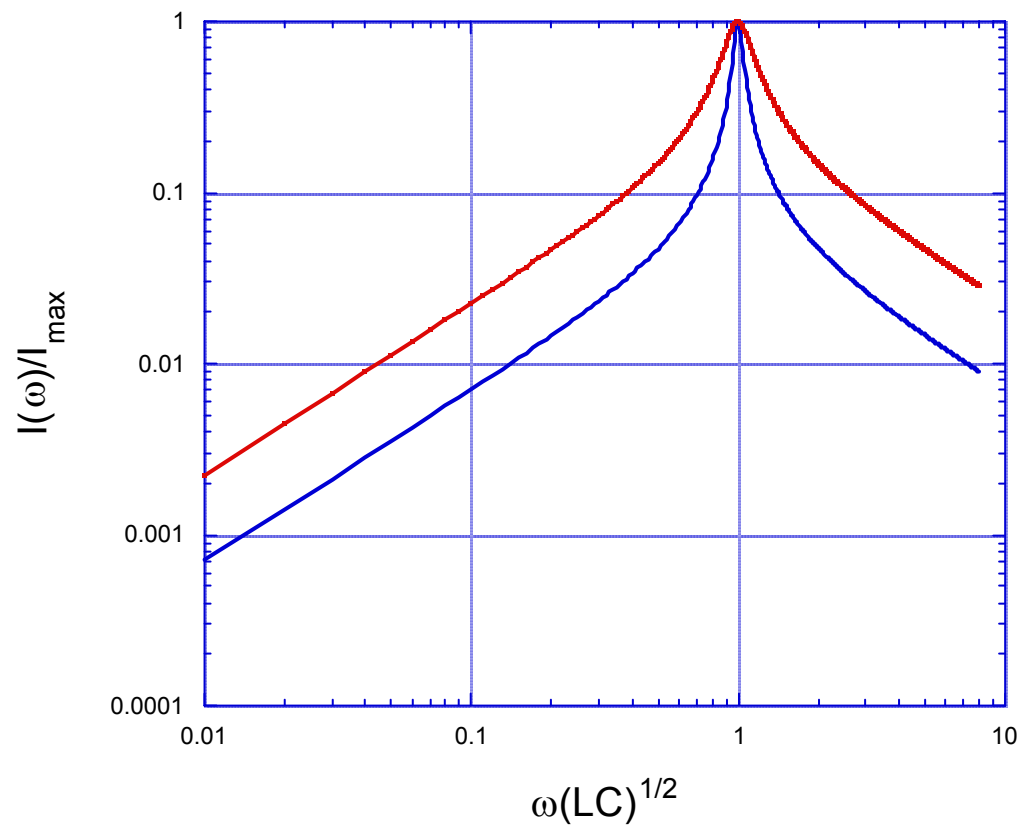

Parallel LCR AC Circuit

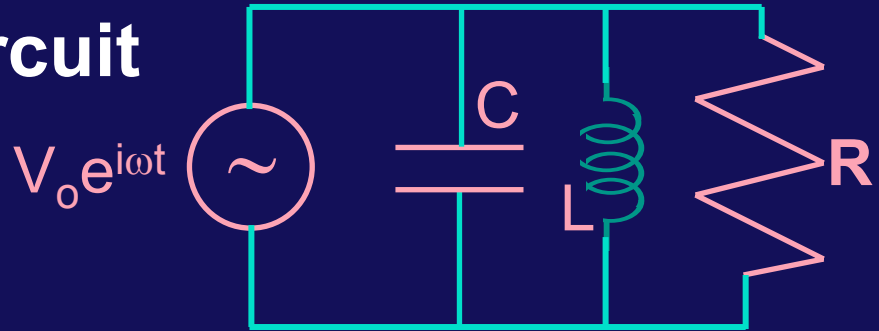- Now, let's use complex impedances to solve a new problem:




- This time figure out an equivalent impedance from the parallel combination of the capacitor, inductor and resistor

$$\frac{1}{Z_P} = \frac{1}{R} + \frac{1}{i\omega L} + i\omega C$$

$$I_o = \frac{V_o}{Z_P} = V_o \left(\frac{1}{R} + i \left(\omega C - \frac{1}{\omega L} \right) \right)$$

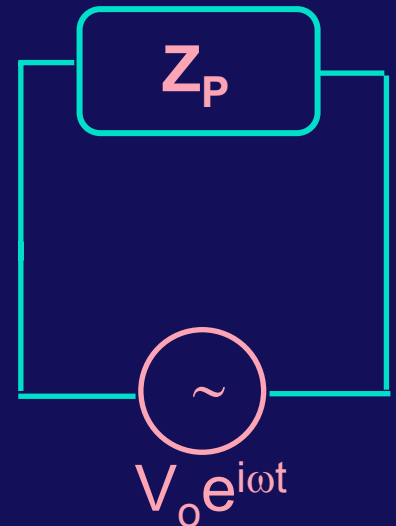
←→
Inverse impedance $1/Z(\omega)$
is a complex number



Inverse impedance shows how current and voltage are related in this problem


Parallel LCR AC Circuit

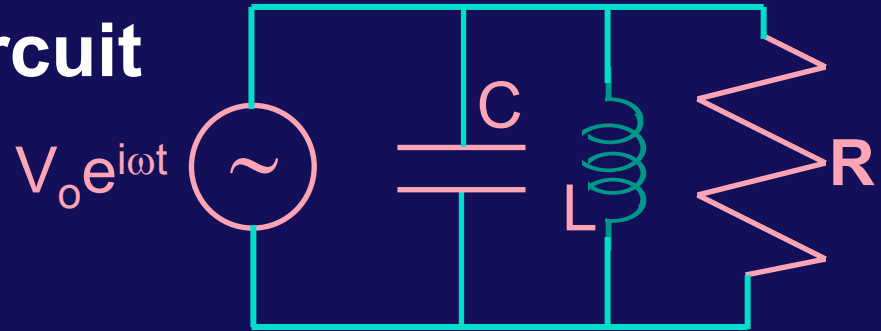- Let's examine the solution from previous slide:




$$I_o = \frac{V_o}{Z_P} = V_o \left(\frac{1}{R} + i \left(\omega C - \frac{1}{\omega L} \right) \right)$$
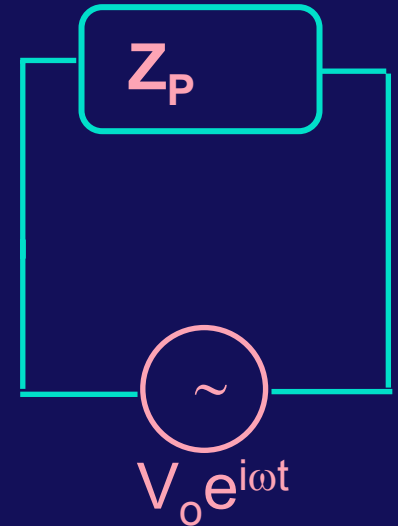
$$I_o = \frac{V_o}{Z_P} = V_o \left(\frac{1}{R} + i \left(\frac{\omega^2 LC - 1}{\omega L} \right) \right)$$



- As in the series case, there is a resonance at $\omega = 1/\sqrt{LC}$
- On resonance, the current is a minimum.
- If R is very large, the current will tend to go to zero on resonance


Parallel LCR AC Circuit

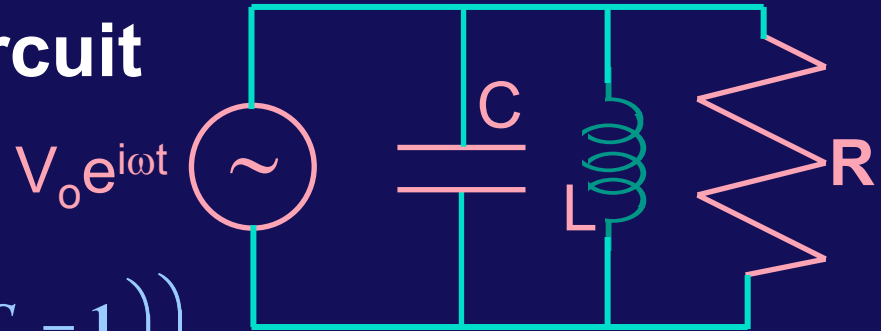


$$I_o = \frac{V_o}{Z_P} = V_o \left(\frac{1}{R} + i \left(\frac{\omega^2 LC - 1}{\omega L} \right) \right)$$

← this is $1/Z$, a complex function of ω →

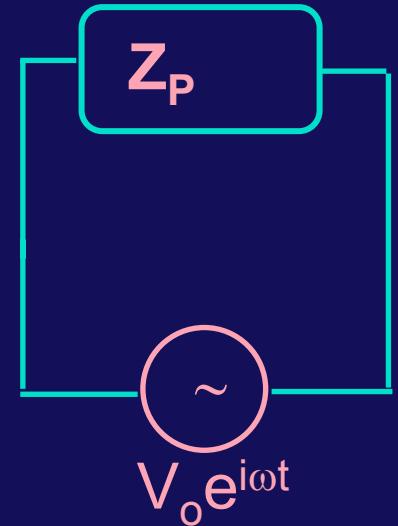
- On resonance, the current is a minimum.
- Magnitude of current is proportional to magnitude of $1/Z$


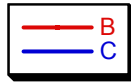
$$\text{mod} \left(\frac{1}{Z} \right) = \frac{1}{R} \sqrt{1 + \frac{(\omega^2 LC - 1)^2}{\left(\omega \frac{L}{R} \right)^2}}$$



current through parallel RLC network

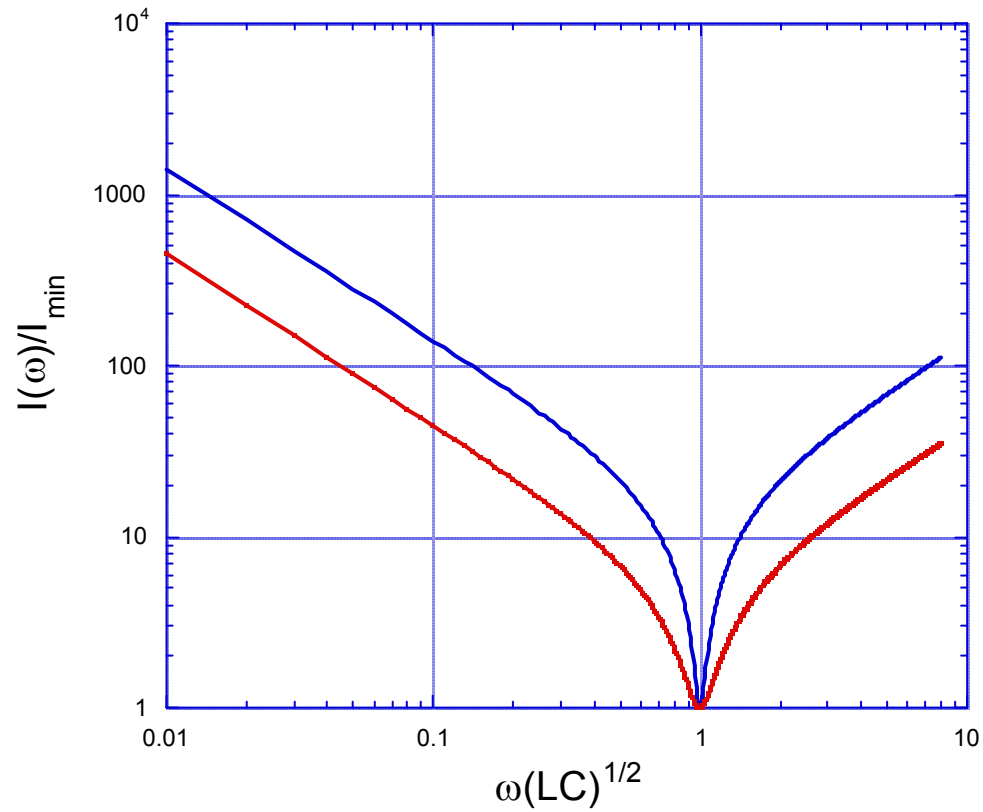


Low pass filter AC Circuit

- Suppose we want to limit the current to be at “low frequency” into a resistor from an ac “current source”

- Design a low pass filter

- Current at low ω should go through R
- Current at high ω should not go through R

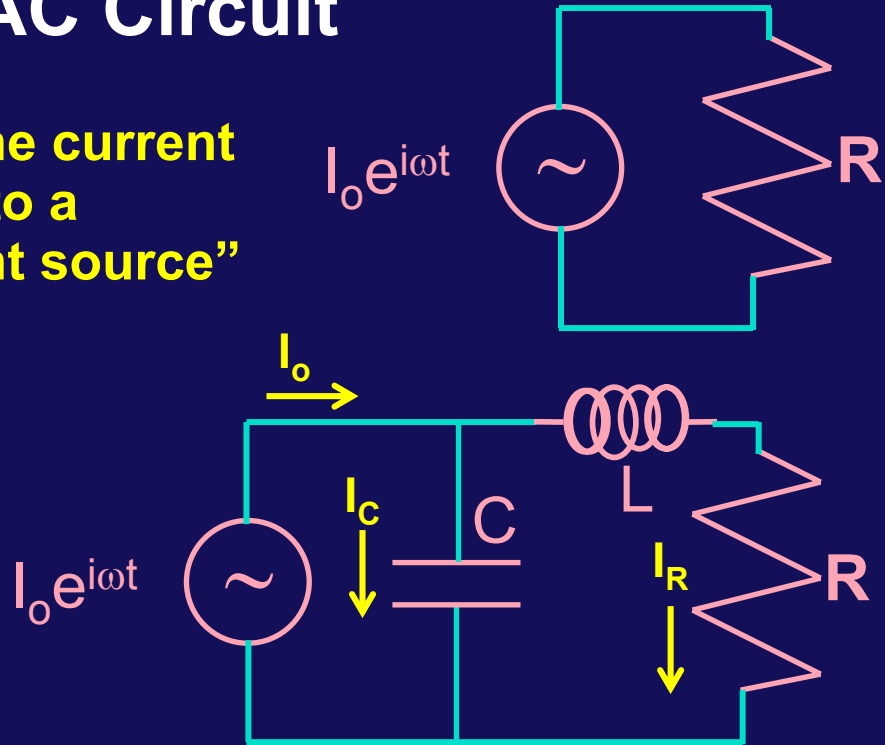- At high frequencies, the inductor will block current: $Z_L = i\omega L$
- At low frequencies, the capacitor will block current: $Z_C = 1/i\omega C$
- Maximize I_R/I_o at low freq. and minimize it at high freq.



Low pass filter AC Circuit

- Voltage across C must equal voltage across L+R


$$I_C \frac{1}{i\omega C} = I_R (i\omega L + R)$$

- And current through cap. is total current minus current through R

$$I_o \frac{1}{i\omega C} = I_R \left(i\omega L + R + \frac{1}{i\omega C} \right)$$

- Solve for magnitude of I_R/I_o
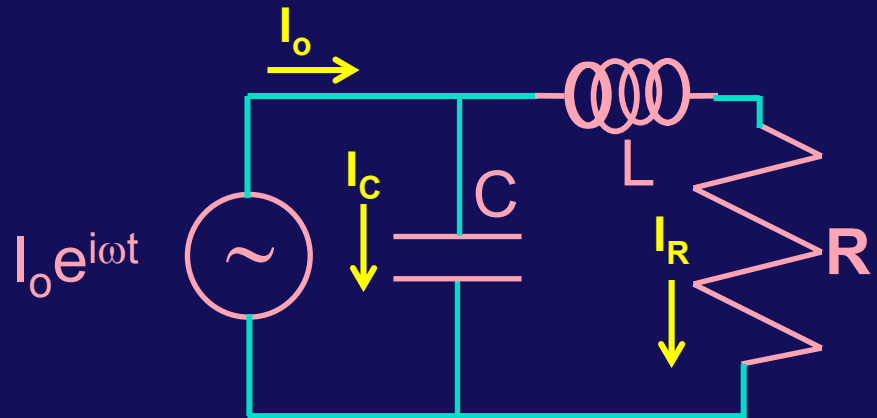
$$\text{mag} \frac{I_R}{I_o} = \frac{1}{\sqrt{(1 - \omega^2 LC)^2 + (\omega RC)^2}}$$



$$I_o e^{i\omega t}$$

$$I_C = I_o - I_R$$

$$I_o = I_R (1 - \omega^2 LC + i\omega RC)$$

- Choose $C = 2L/R^2$

$$\text{mag} \frac{I_R}{I_o} = \frac{1}{\sqrt{1 + (\omega\tau)^4}} \quad \tau = \sqrt{2} \frac{L}{R}$$

—•— filter response

matched low pass filter response

