

UNIVERSITY OF ILLINOIS
AT URBANA-CHAMPAIGN

Transients and Oscillations in RLC Circuits

Physics 401, Spring 2013.

Eugene V. Colla



Transients and Oscillations in RLC Circuits. Outline

Transients. Definition.

- Transients in RLC
- Resonance in RLC

Data analysis. Origin. Fitting.


Some complimentary but very important stuff:
Voltage source, current source,
Input resistance, output resistance
Two probe, four probe measuring technique



Transients. Definition.

transient (physics) a short-lived oscillation in a system caused by a sudden change of voltage or current or load

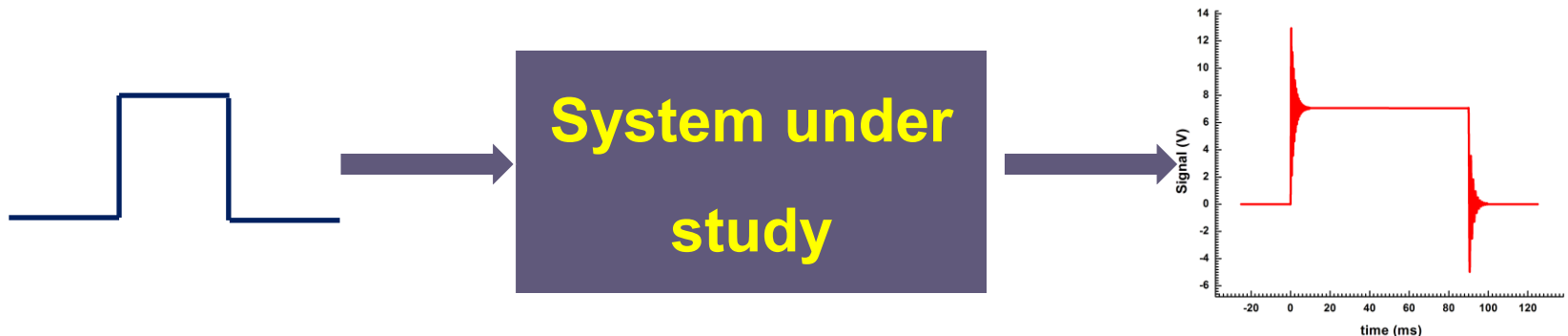a transient response or natural response is the response of a system to a change from equilibrium.





Transients in RLC circuit.

Resistance R [Ohm]

Capacitance C [μF] (10^{-6}F)

Inductance L [mH] (10^{-3}H)

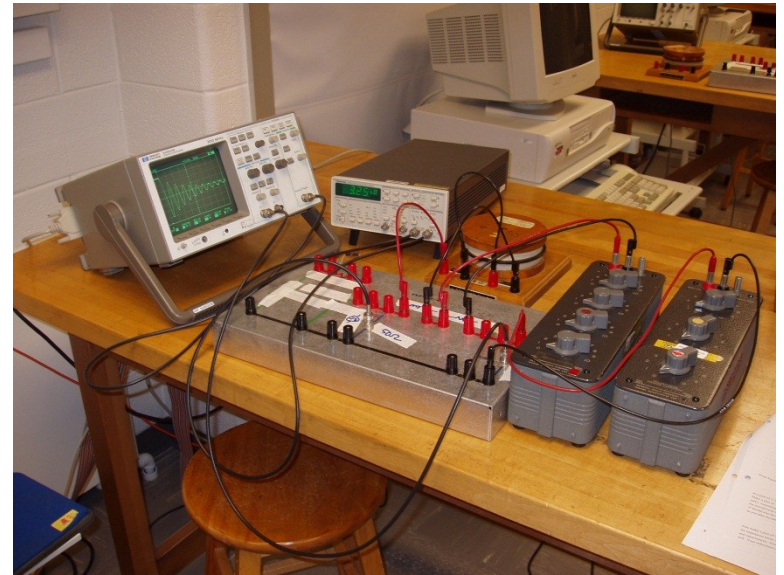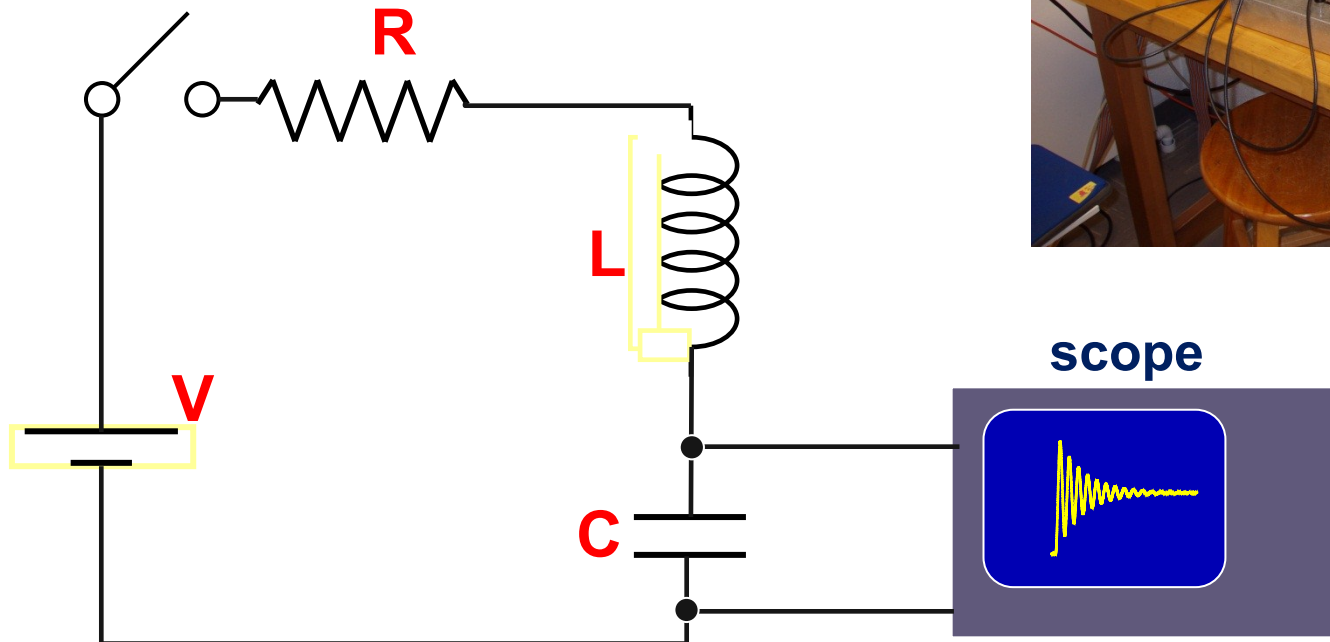



Transients in RLC circuit.

According to Kirchhoff's law

$$V_R + V_L + V_C = V(t)$$

$$L \frac{d^2 q(t)}{dt^2} + R \frac{dq(t)}{dt} + \frac{q(t)}{C} = 0, \quad \frac{q(t)}{C} = V_0 \quad (1)$$

*See Lab write-up for details

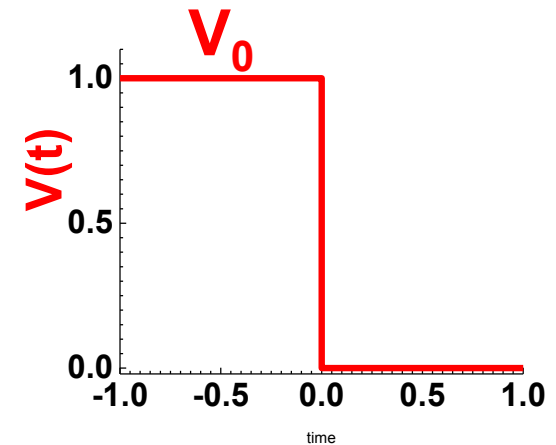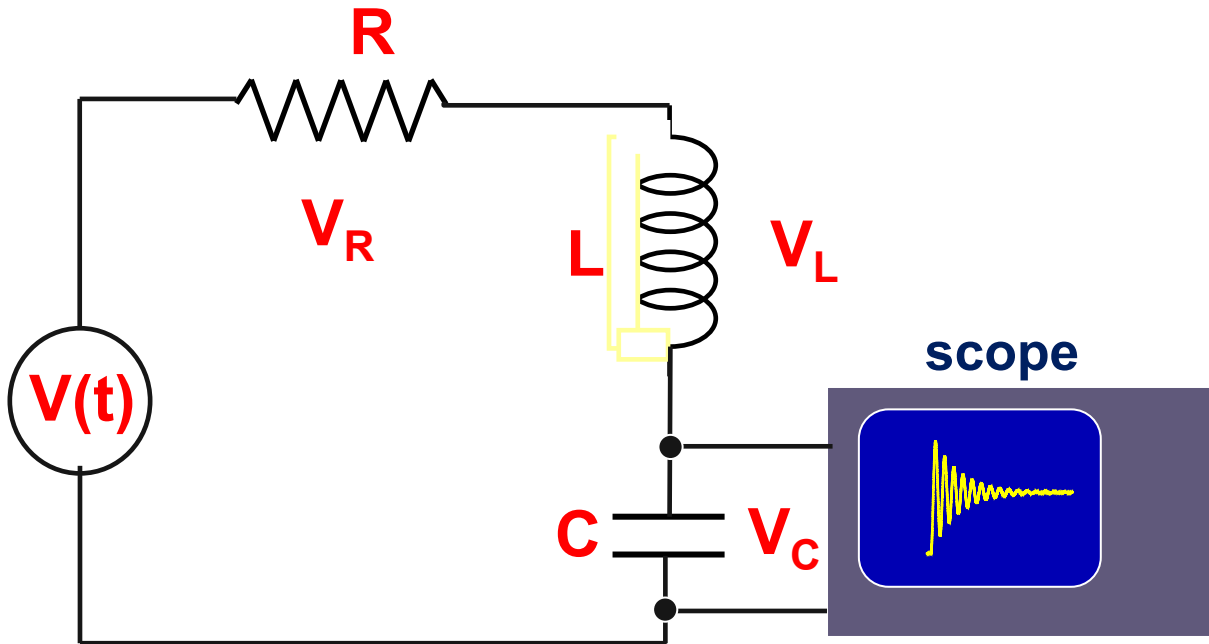

Transients in RLC circuit. Three solutions

The solution of this differential equation can be found in the form

$$q(t) = Ae^{st}$$

This will convert (1) in quadratic equation

$$s^2 + \left(\frac{R}{L}\right)s + \frac{1}{LC} = 0$$

with solutions:

$$s_{1,2} = -\frac{R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \left(\frac{1}{LC}\right)} \equiv -a \pm b$$

$$a = \frac{R}{2L}, \quad b = \sqrt{\left(\frac{R}{2L}\right)^2 - \left(\frac{1}{LC}\right)}$$

$b^2 > 0$ over-damped solution

$b^2 = 0$ critically damped solution

$b^2 < 0$ under-damped solution



Transients in RLC circuit. Over-damped solution: $b^2 > 0$

In this case the solution will be aperiodic
exponential decay function with no
oscillations:

$$q(t) = e^{-at} (A_1 e^{bt} + B_1 e^{-bt})$$

$$i(t) = \frac{dq}{dt} = -ae^{-at} (A_1 e^{bt} + B_1 e^{-bt}) + be^{-at} (A_1 e^{bt} - B_1 e^{-bt})$$



Transients in RLC circuit. Over-damped solution: $b^2 > 0$

Taken in account the initial conditions: $q(0)=q_0$ and $i(0)=0$

$$q(t) = q_0 e^{-at} \left(\cosh bt + \frac{a}{b} \sinh bt \right)$$

$$\xrightarrow{(a-b)t \gg 1} \frac{q_0}{2} \left(1 + \frac{a}{b} \right) e^{-(a-b)t}$$

$$i(t) = -\frac{q_0}{2} \left(\frac{a^2 - b^2}{b} \right) e^{-(a-b)t}$$

This is exponential decay function



Transients in RLC circuit. Critically-damped solution

$$b^2=0$$

For this case the general solution can be found as

$q(t)=(A_2+B_2t)e^{-at}$. Applying the same initial condition


the current can be written as $i=-a^2q_0te^{-at}$

Critical damped case shows the fastest decay with no oscillations



Transients in RLC circuit. Critically-damped solution. Real data analysis.

$$b^2=0$$

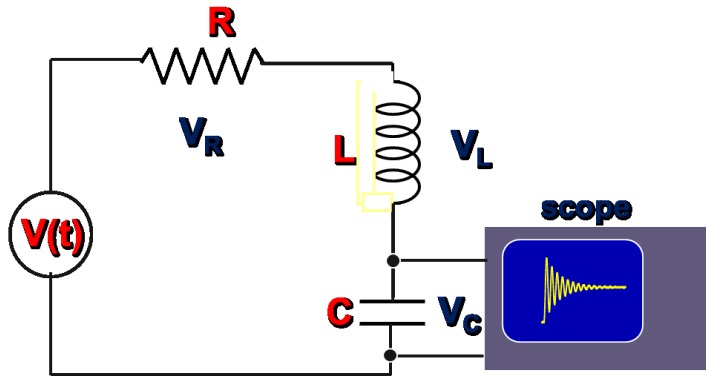

In this experiment $R=300$ ohms,
 $C=1\mu\text{F}$, $L=33.43\text{mH}$.

The output resistance of Wavetek is 50 ohms and resistance of coil was measured as 8.7 ohms, so actual resistance of the network is $R_a=300+50+8.7=358.7$


Decay coefficient
$$a = \frac{R}{2L} = \frac{358.7}{2 * 33.43E-3} \approx 5365$$



Transients in RLC circuit. Critically-damped solution. Real data analysis.

$$b^2=0$$
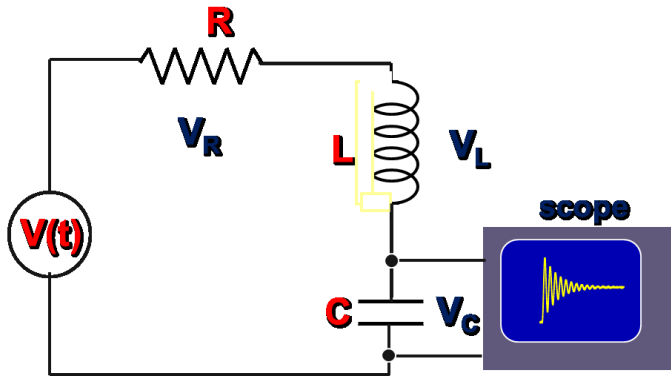
$$V_C \sim q, \text{ fitting function: } V_C = V_{co}(1+at)e^{-at}$$




Calculated decay coefficient ~ 5385 ,

Obtained from fitting - ~ 5820 .

Possible reason – it is still slightly over damped

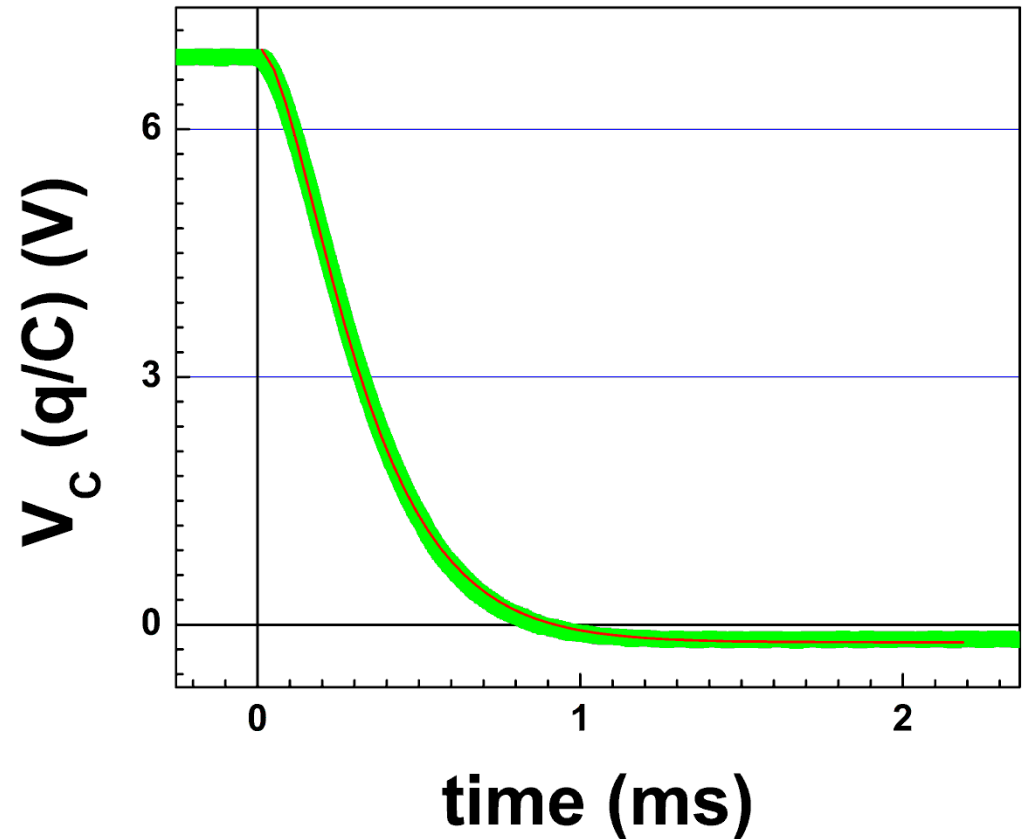Calculated b^2 is $b^2 = 2.99e7 - 2.90e7 > 0$



Transients in RLC circuit. Under-damped solution.

If $b^2 < 0$ we will have oscillating solution. Omitting the details (see Lab write-up) we have the equations for charge and current as:

$$q(t) = q_0 e^{-at} \left(\cos bt + \frac{a}{b} \sin bt \right) = q_0 e^{-at} \sqrt{1 + \frac{a^2}{b^2}} \sin(bt + \varphi)$$

$$i(t) = q_0 e^{-at} \left(\frac{a^2 + b^2}{b} \right) \sin bt$$

$$a = \frac{R}{2L}, \quad b = \sqrt{\left(\frac{R}{2L}\right)^2 - \left(\frac{1}{LC}\right)}; \quad f = \frac{1}{2\pi} \sqrt{\left(\frac{1}{LC}\right) - \left(\frac{R}{2L}\right)^2}$$




Transients in RLC circuit. Under-damped solution. Log decrement. Quality factor.

Log decrement can be defined as $\delta = \ln \left(\frac{q(t_{max})}{q(t_{max}+T_1)} \right) = \ln \left(\frac{e^{-at_{max}}}{e^{-at_{max}+T_1}} \right) = aT_1$, where $T_1=1/f_1$


Quality factor can be defined as $Q = 2\pi \frac{E}{\Delta E}$,

For RLC $Q = \frac{\omega_1 L}{R} = \frac{\pi}{\delta}$

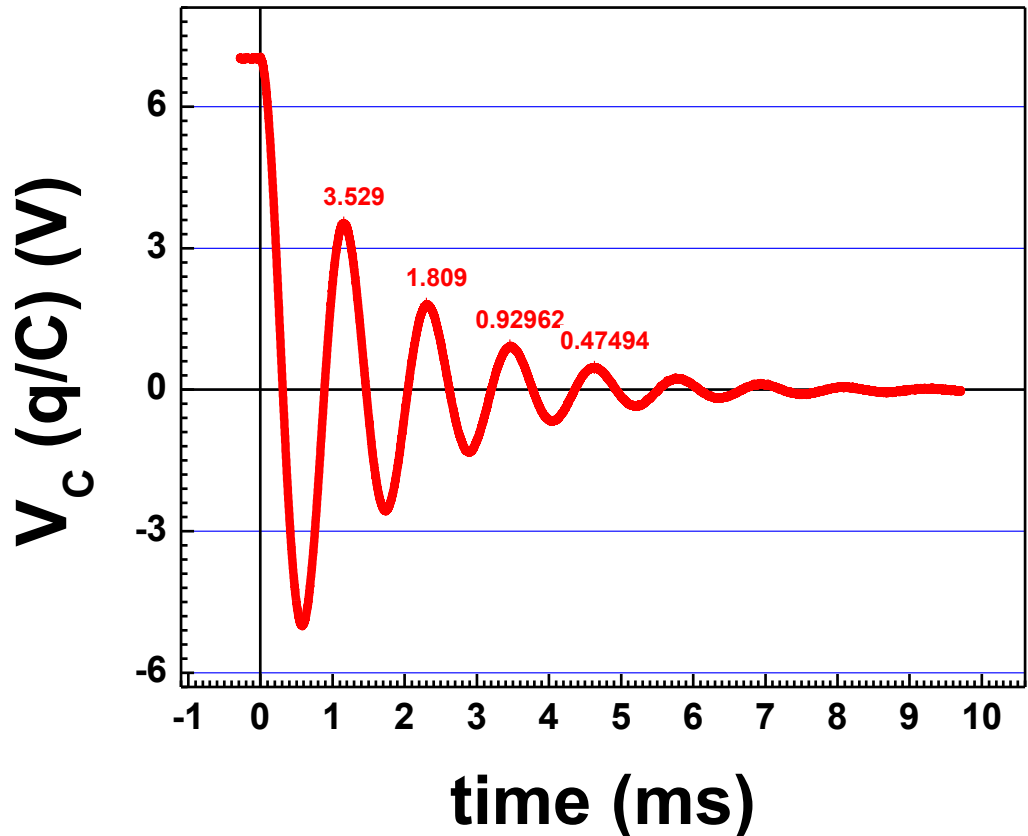
From this plot $\delta \approx 0.67$
 $Q \approx 4.7$



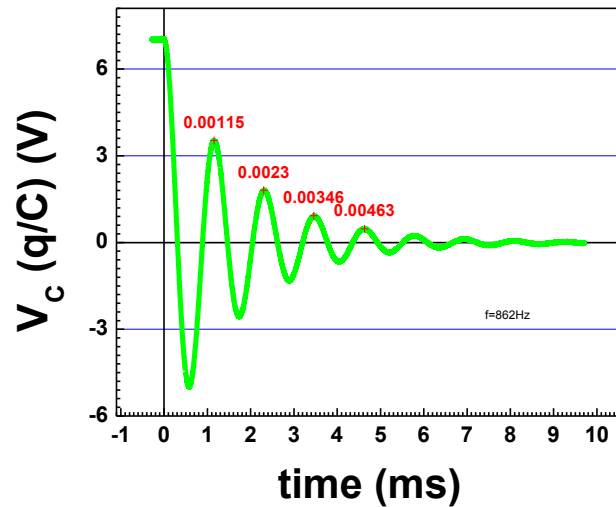
Transients in RLC circuit. Data analysis. Using Origin software.



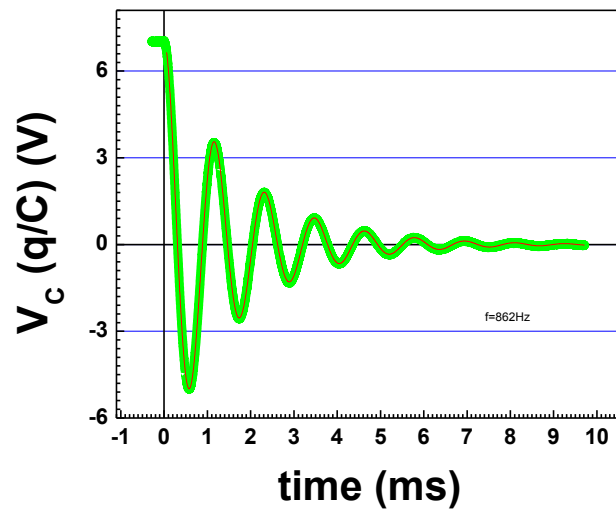
1. Pick peaks
2. Envelope
3. Exponential term
4. Nonlinear fitting




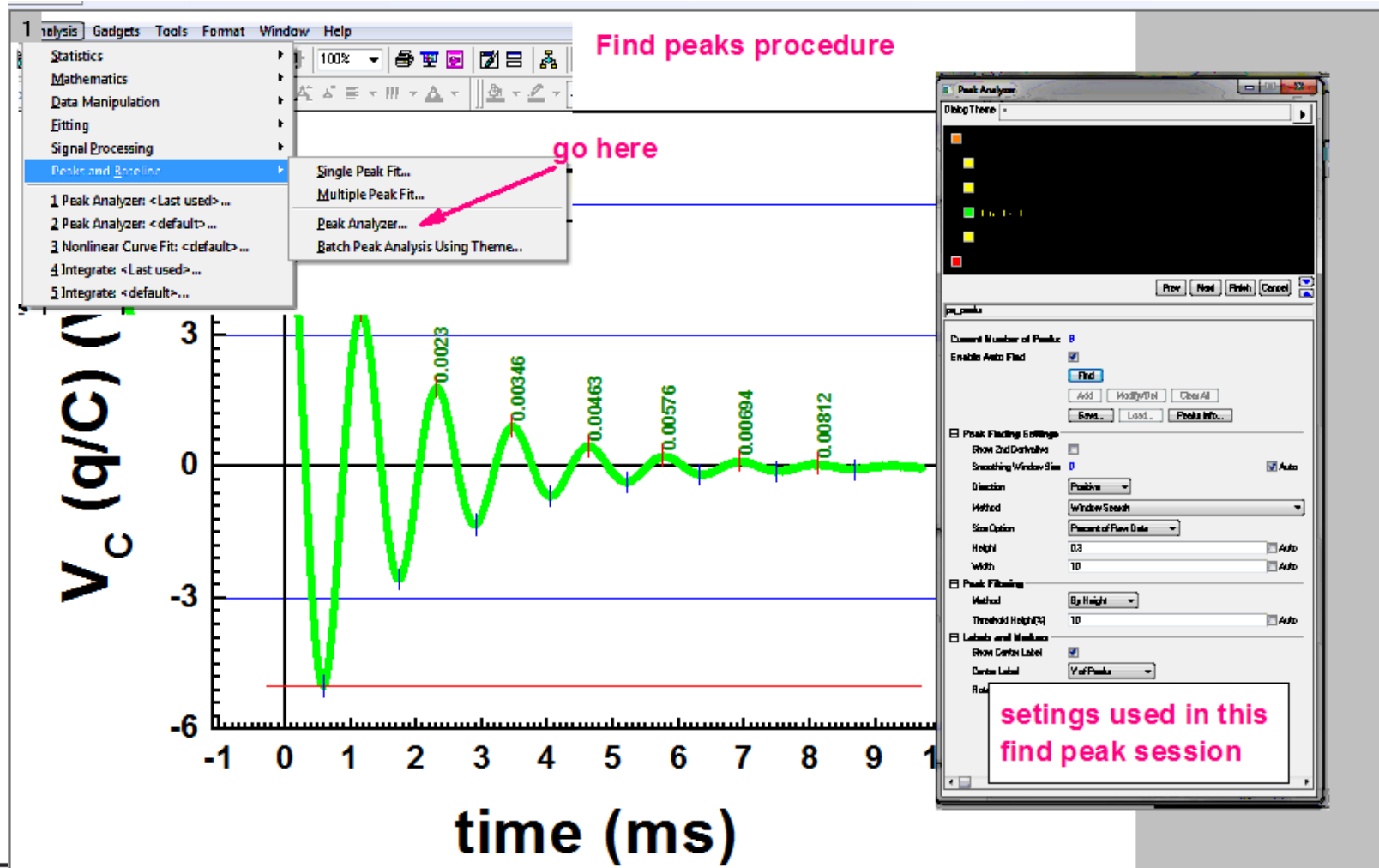
Transients in RLC circuit. Under-damped solution. Log decrement. Quality factor.



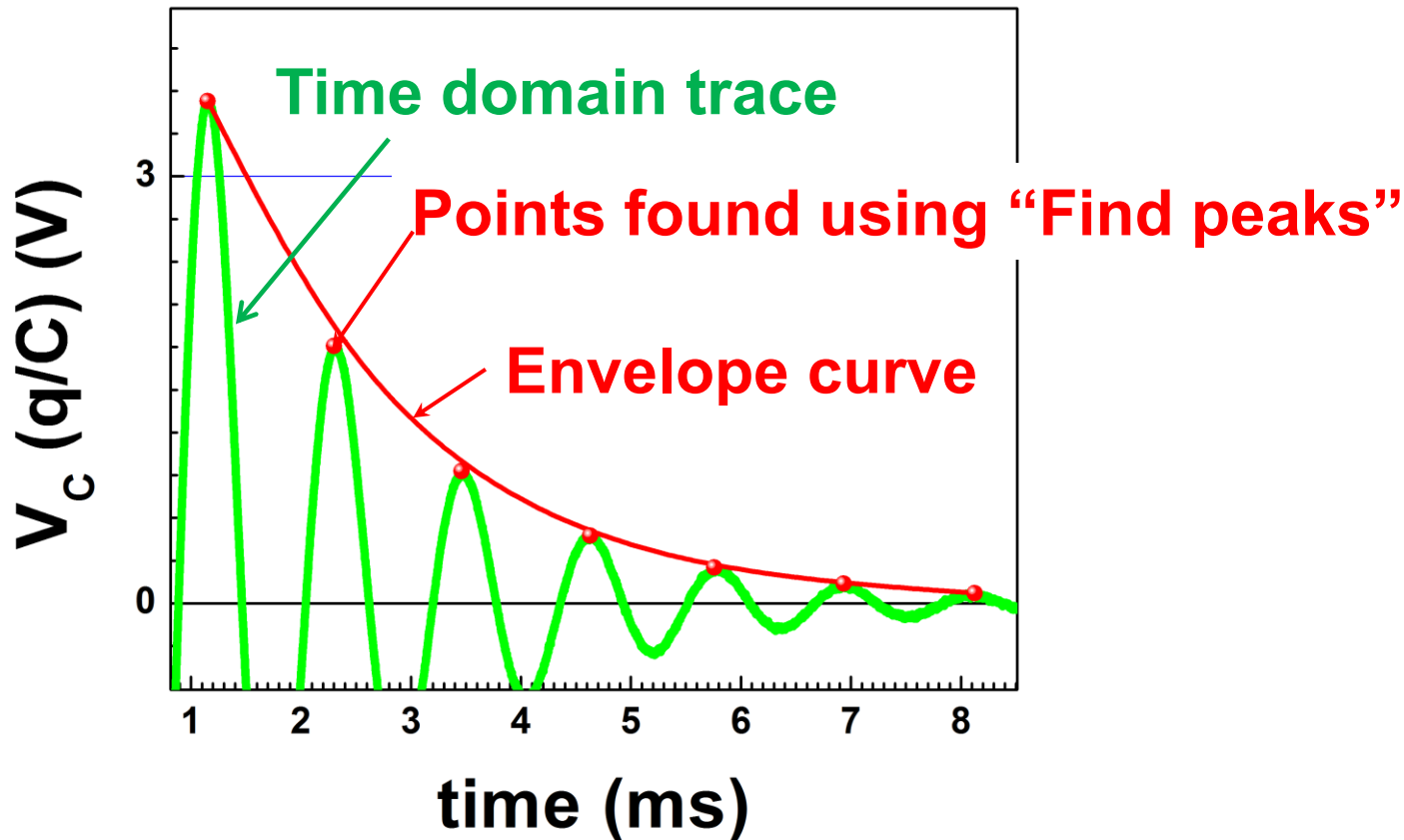Transients in RLC circuit. Data analysis. Log decrement. Using Origin software. Results.



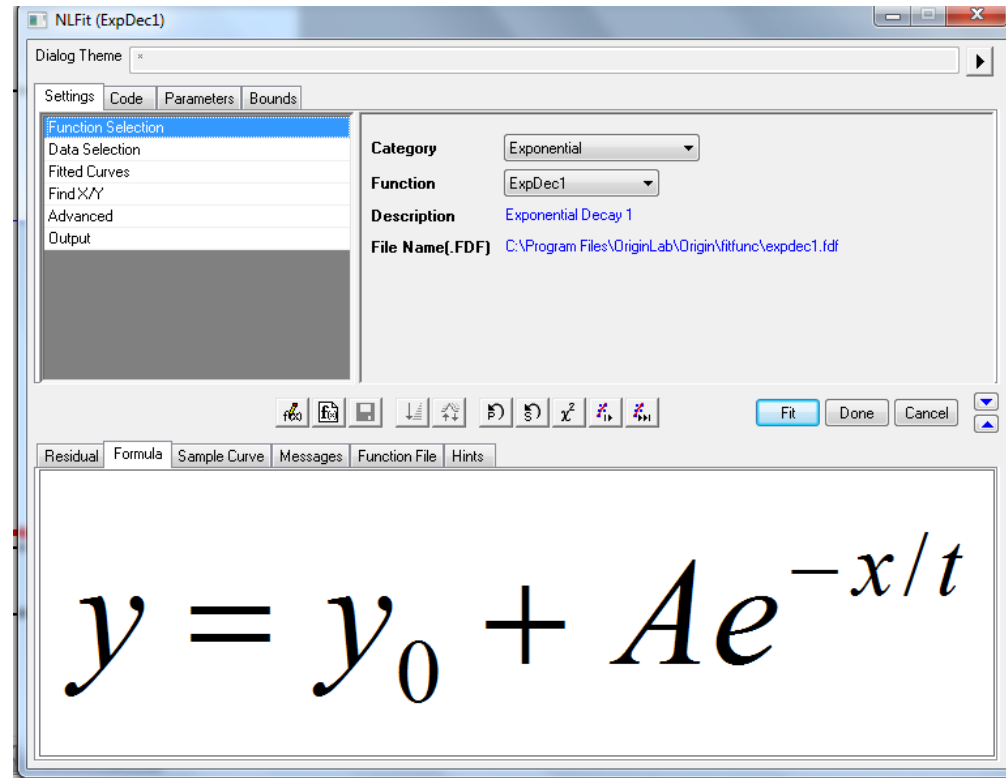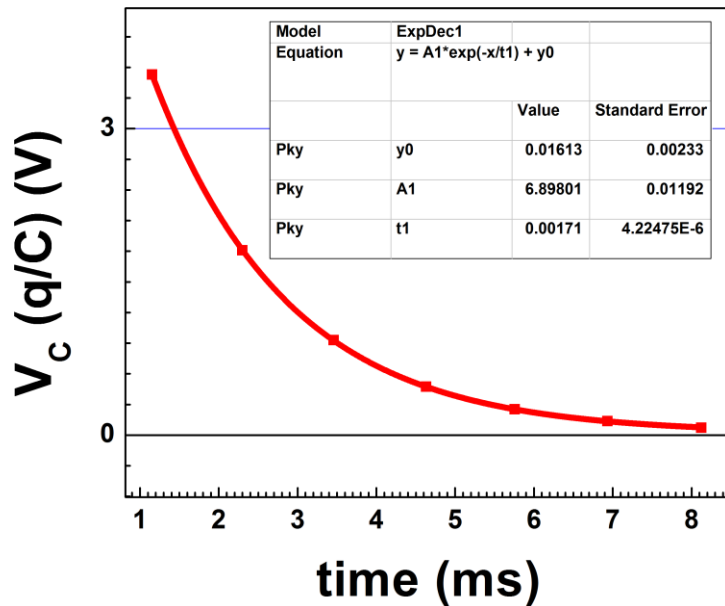Transients in RLC circuit. Data analysis. Log decrement. Using Origin software. Results.




Fitting the “envelope data” to exponential decay function



Transients in RLC circuit. Data analysis. (1/T)² vs 1/C experiment.
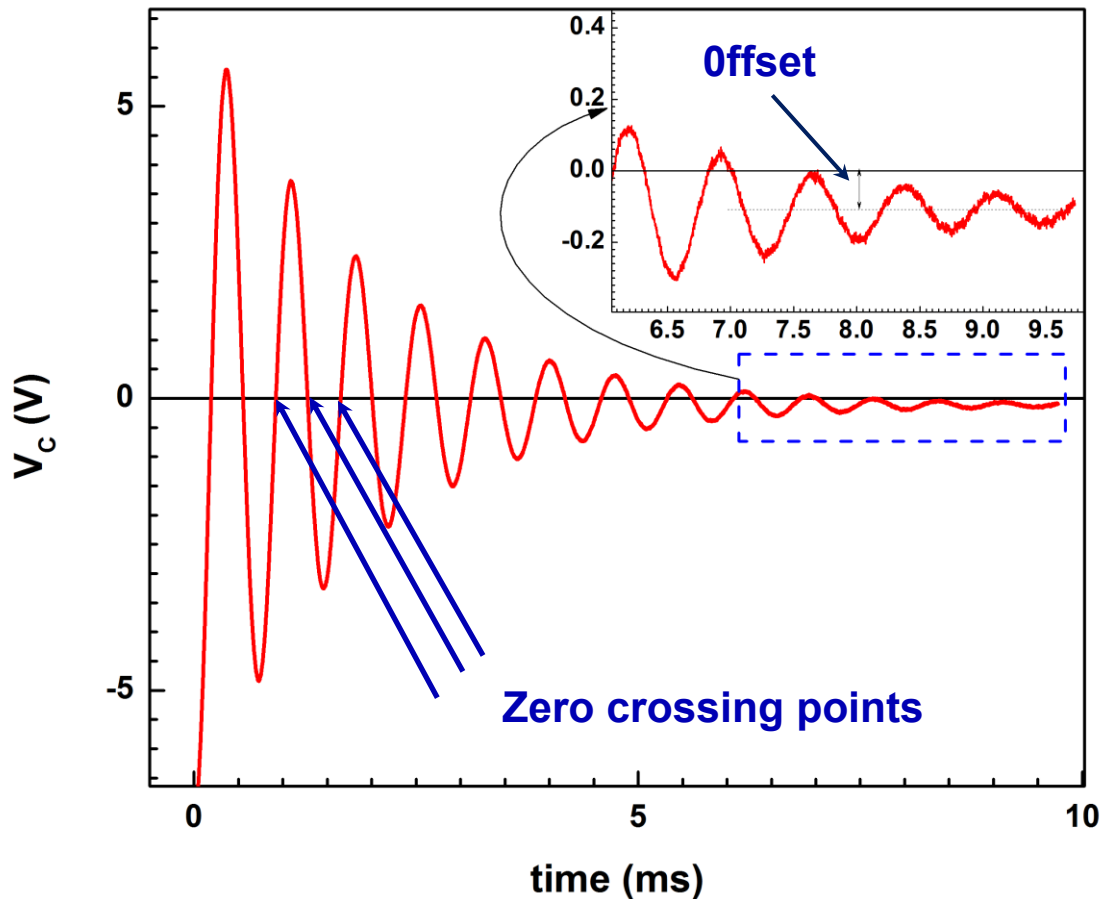
$$q(t) = Ae^{-at} \sin(\omega t + \varphi) + \text{offset}$$




Manual evaluation of the period of the oscillations

Limited accuracy

Results can be effected by DC offset



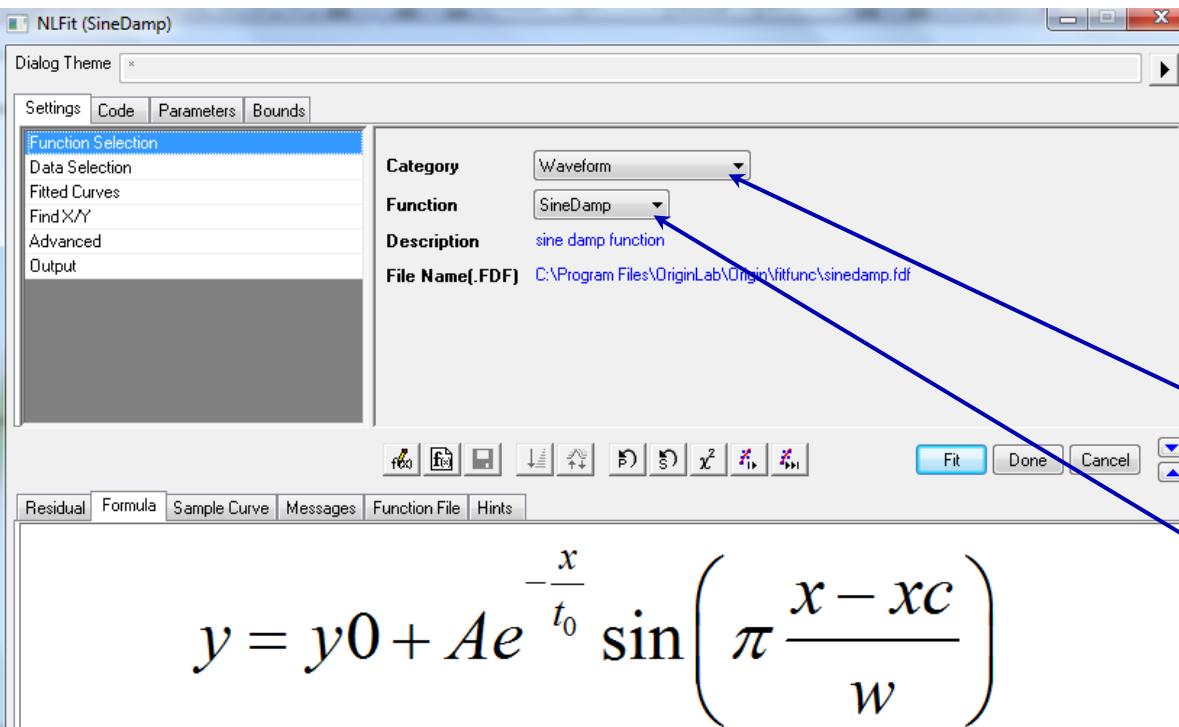Transients in RLC circuit. Data analysis. (1/T)² vs 1/C experiment. Using Origin software.



$$q(t) = Ae^{-at} \sin(\omega t + \varphi)$$

Use Origin standard function

Category: Waveform



Function: SineDamp

Fitting function ; y_0, A, t_0, x_c, w – fitting parameters




Transients in RLC circuit. Data analysis. (1/T)² vs 1/C experiment. Using Origin software.
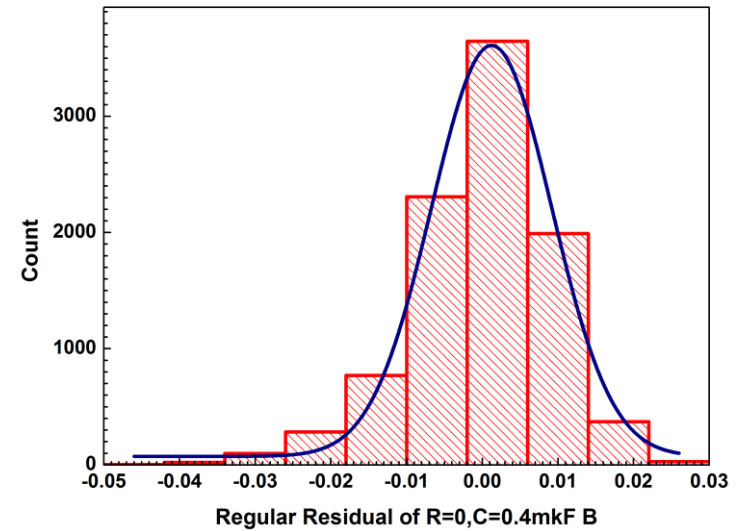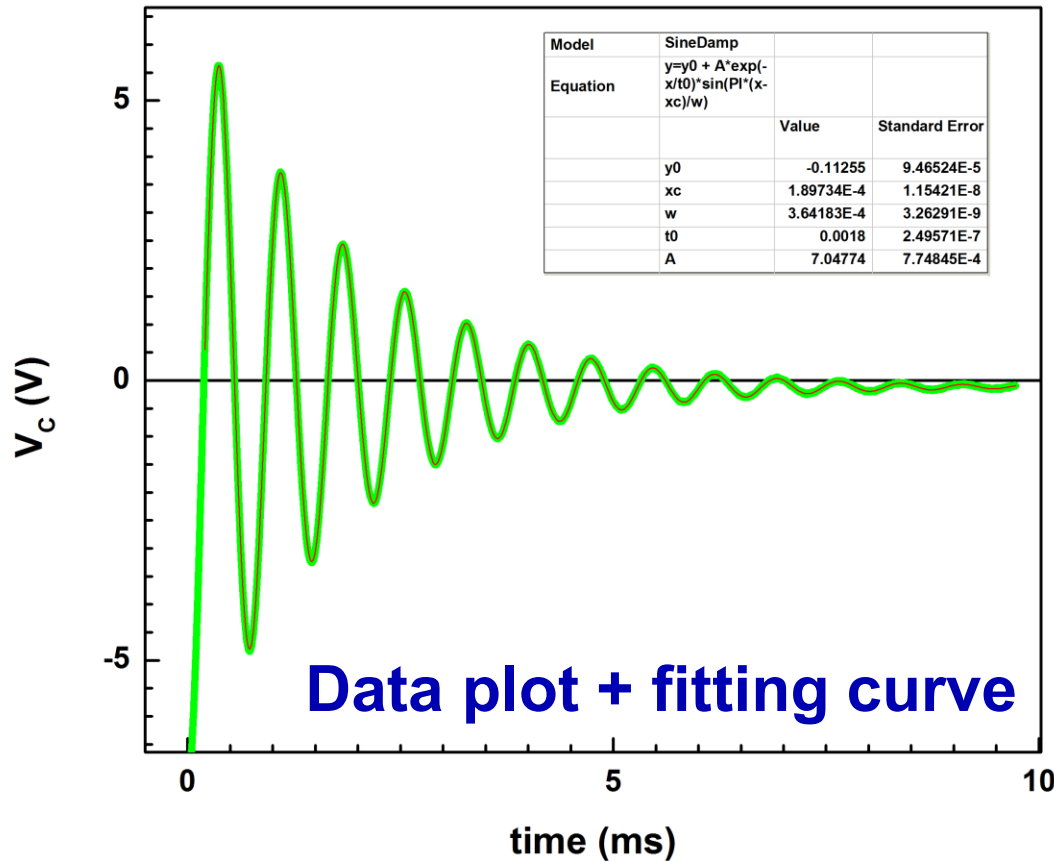
$$q(t) = Ae^{-at} \sin(\omega t + \varphi)$$



Transients in RLC circuit. Data analysis. $(1/T)^2$ vs $1/C$ experiment. Using Origin software.
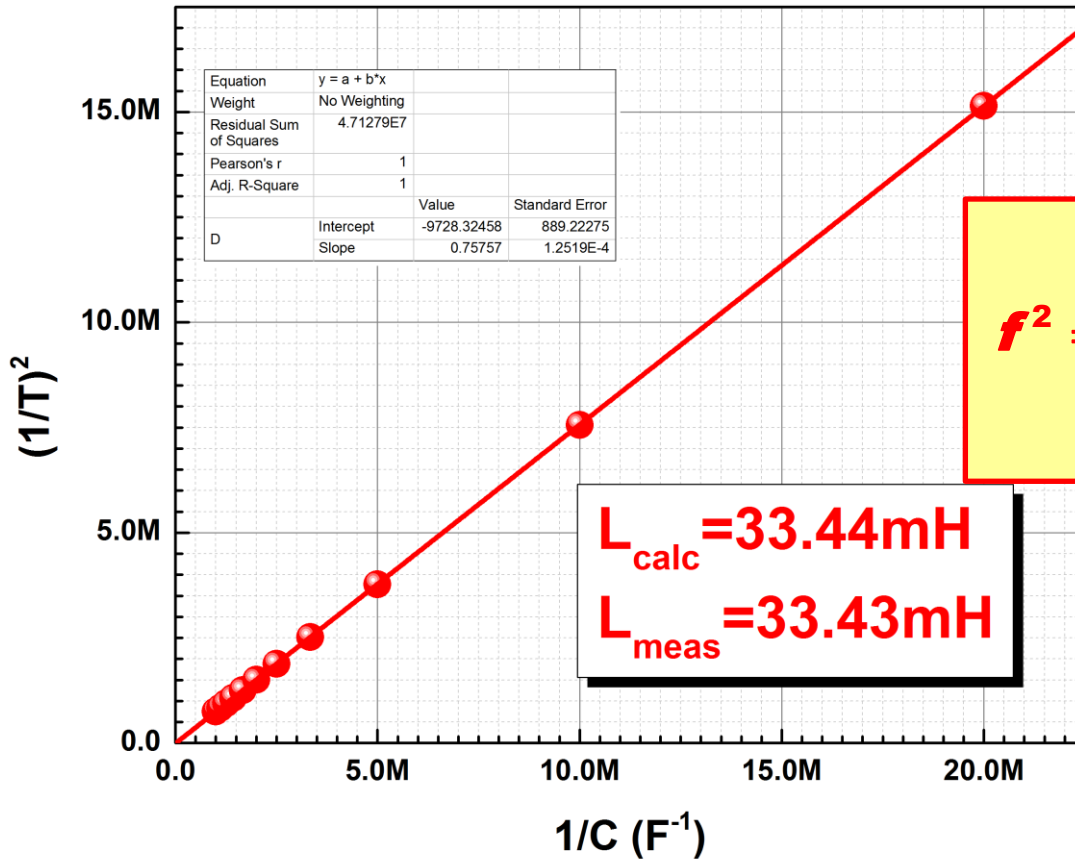
$$q(t) = Ae^{-at} \sin(\omega t + \varphi)$$





$$f^2 = \left(\frac{1}{T}\right)^2 = \frac{1}{2\pi} \left(\left(\frac{1}{LC}\right) - \left(\frac{R}{2L}\right)^2 \right)$$

Final results



Resonance in RLC circuit.

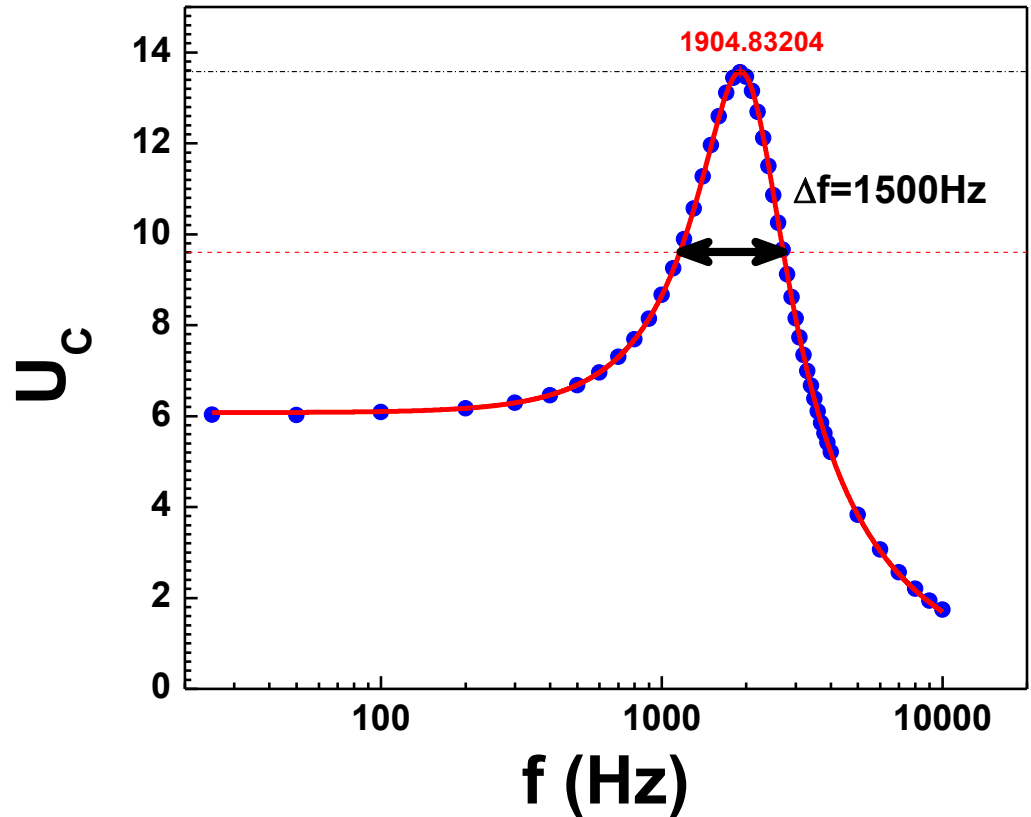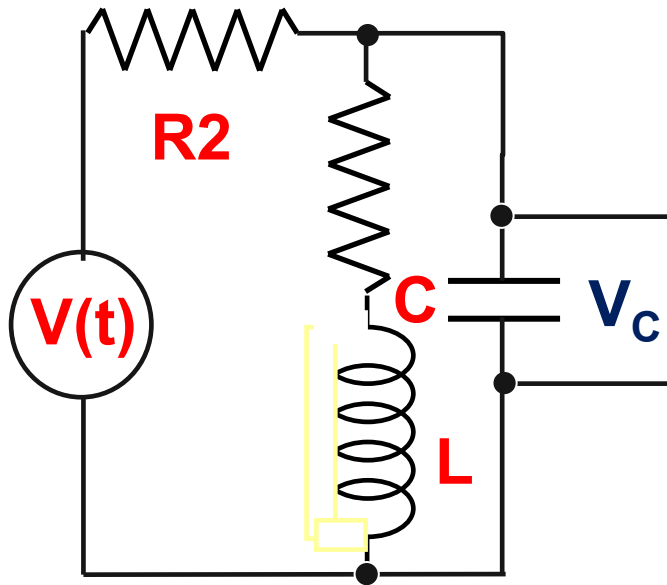


$$Q = \frac{f}{\Delta f} = \frac{1904}{1500} = 1.26$$



Input resistance. Measuring the voltage.

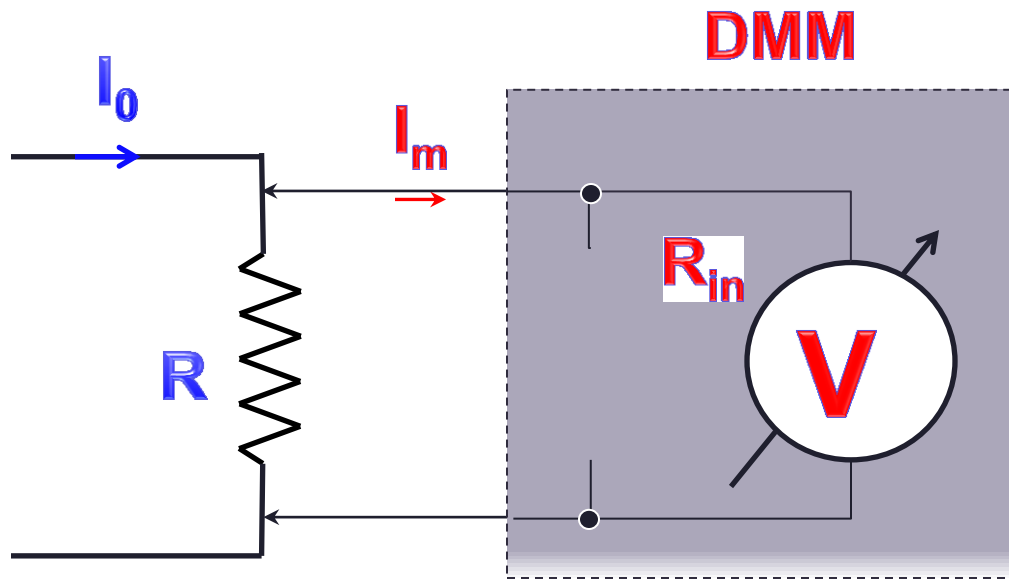One important parameter for any electrical measuring equipment (DMM, scope, amplifier) is its input resistance



Ideal case:

$$R_{in} = \infty;$$

$$I_m = 0;$$

$$V = R \cdot I_0$$

Real situation:

$$R_{in} \neq \infty;$$

$$I_m = I_0 \left(\frac{\frac{R}{R_{in}}}{1 + \frac{R}{R_{in}}} \right);$$


$$V = I_0 \left(\frac{R}{1 + \frac{R}{R_{in}}} \right)$$

For correct voltage measurements it necessary to have $R_{in} \gg R$



Input resistance. Measuring the current.

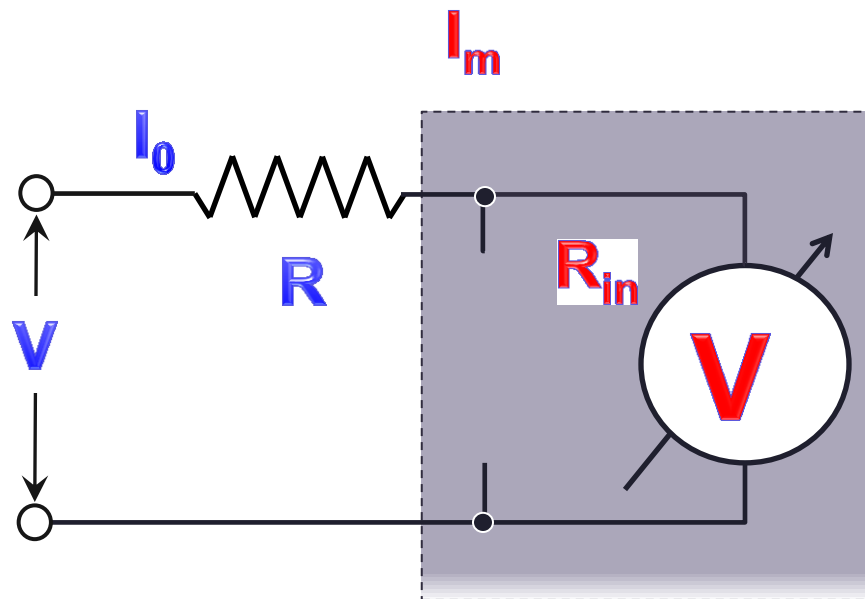The same about current measurement, but for ampere meter the requirement for R_{in} is much different.



Ideal case:

$$I_0 = \frac{V}{R} \text{ (expected value)}$$

Real situation:

$$I = \frac{V}{R + R_{in}}$$


$$I \approx I_0 \text{ if } R_{in} \rightarrow 0$$

For correct current measurements it necessary to have $R_{in} \ll R$



Measuring of the input resistance of the voltmeter.

Why?

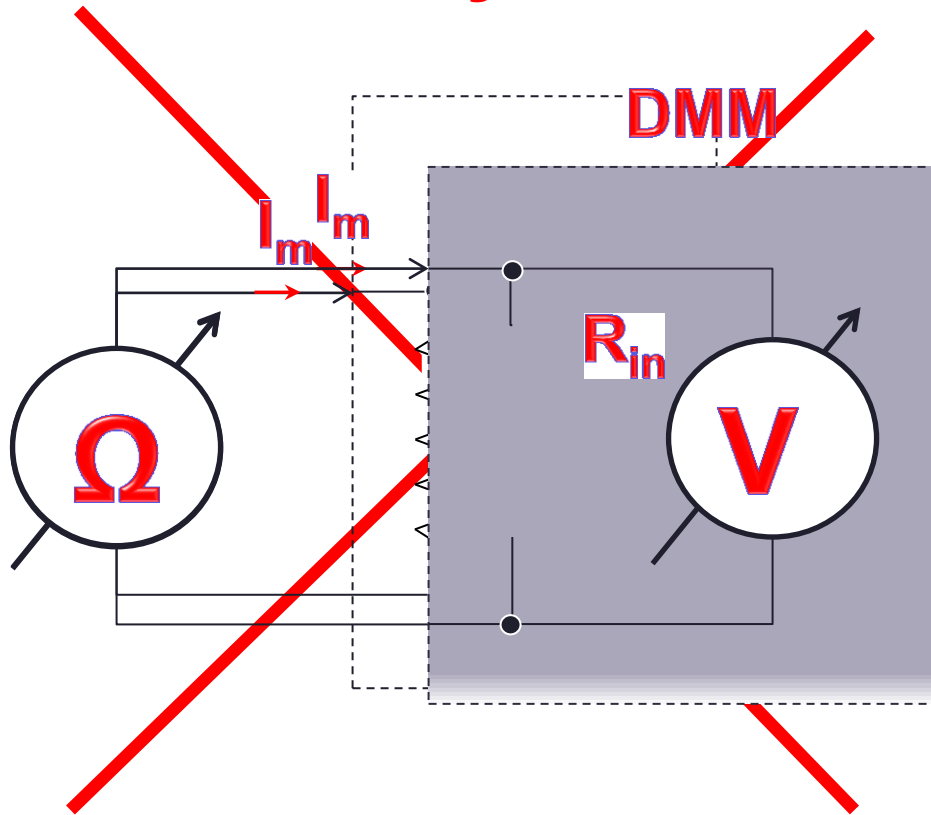


The current applied by ohmmeter to the input of amplifier or DMM can destroy the electronics



Measuring the input resistance of voltmeter.

Correct idea

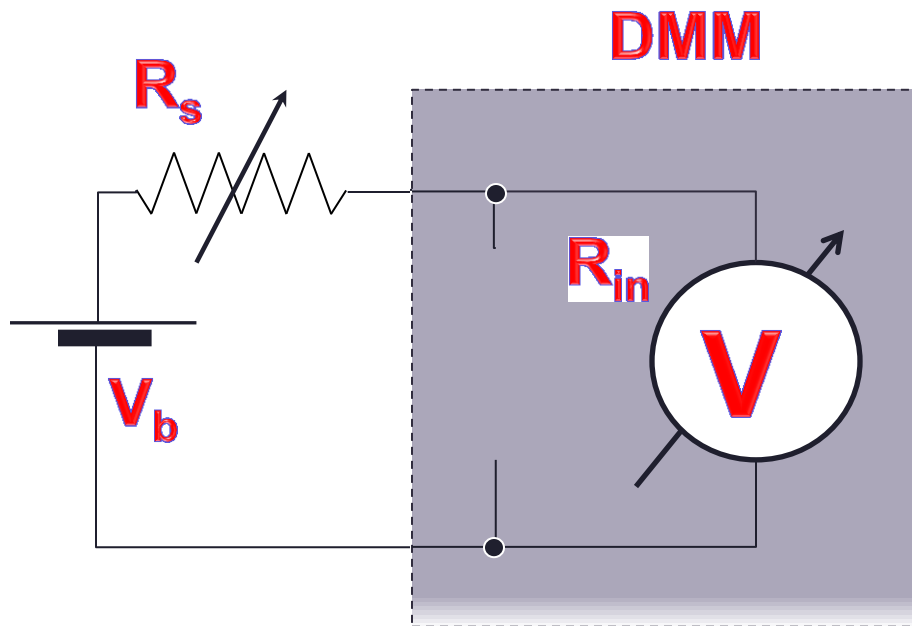

Ignoring battery output resistance V_b we can measure if $R_s=0$. Next we have to vary R_s until DMM reading becomes equal $0.5 V_b$



$$V = 0.5V_b = \frac{R_{in}}{R_s + R_{in}} V_b$$

$$\rightarrow R_s = R_{in}$$



Output resistance. Voltage source.

Equivalent circuit of voltage source

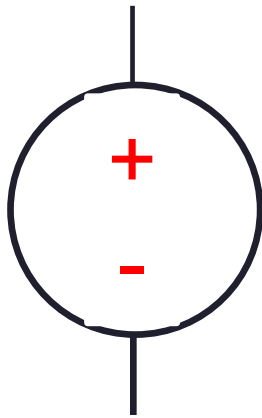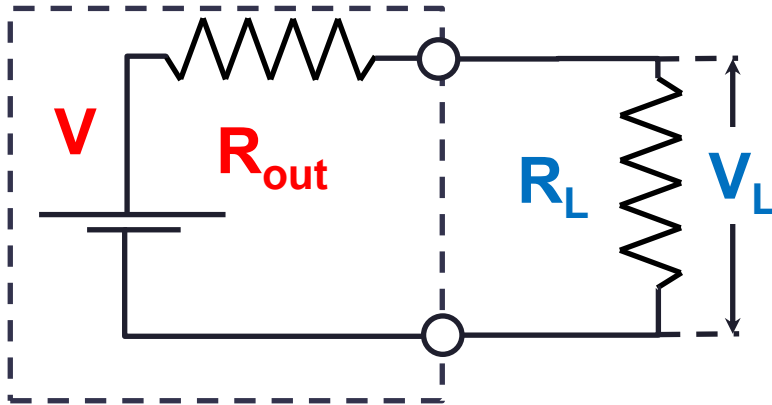

Voltage source circuit diagram symbol

Voltage on the load:

$$V_L = V \times \frac{R_L}{R_L + R_{out}}$$

$$V_L \approx V \text{ if } R_{out} \ll R_L$$

Power on the load:



$$P = \frac{V_L^2}{R_L} = \frac{V^2 R_L}{(R_L + R_{out})^2}$$

$$P = P_{max} = \frac{V^2}{4R_{out}} \text{ if } R_L = R_{out}$$



Output resistance. Current Source.

Equivalent circuit of current source

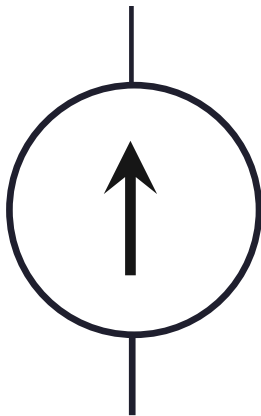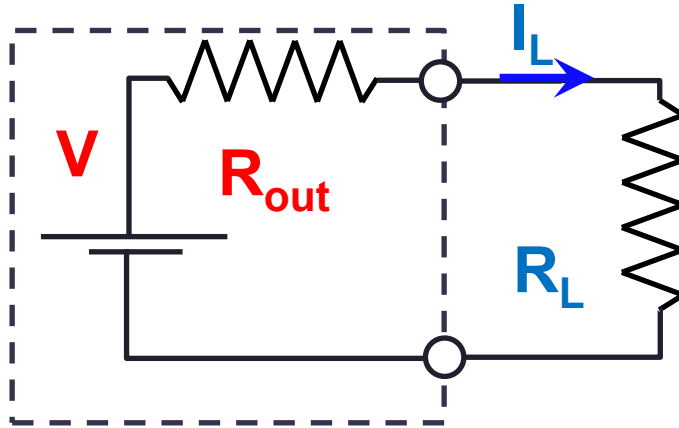

Current source circuit diagram symbol

Ideal current source – current in the load should not depend on the load resistance.

$$I_L = \frac{V}{R_L + R_{out}} = \frac{I_0}{1 + \frac{R_L}{R_{out}}}$$


where

$$I_0 = \frac{V}{R_{out}}$$

So, for ideal current source $R_{out} \rightarrow \infty$



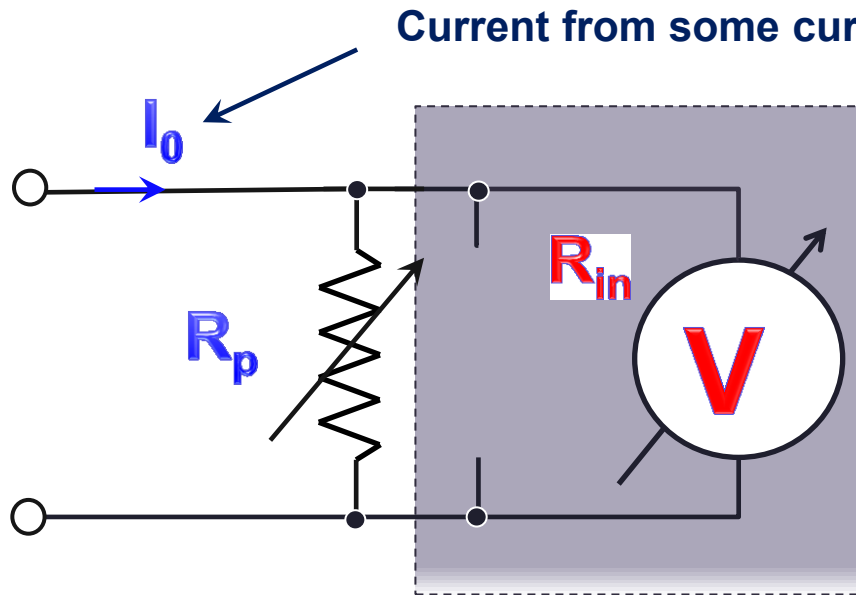Measuring of the Input resistance of the current meter.




For measurement of the input resistance of the current meter we can use the current divider .

Varying the resistance of the parallel resistor R_p we have to find the value of R_p corresponding the reading of current equal $I_0/2$. In this case

$$R_{in} = R_p$$



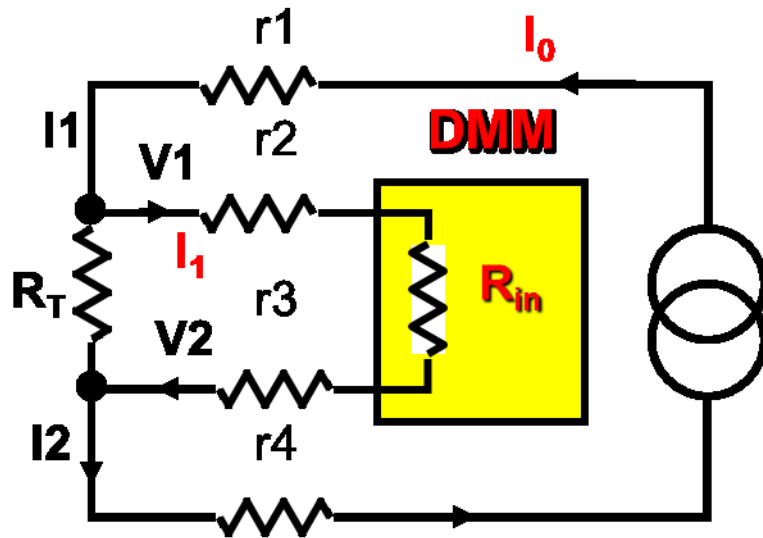Measuring of voltage, resistance. Four probe technique



Most of DMM's have four probe option for resistance measurements.


If the sensor is mounted in cryostat the overall leads resistance could reach a couple of ohms. This will in case of RTD100 the resistance at 0°C is 100Ω give an error of a couple percent!

$$I_1 = I_0 * R_T / (r_2 + r_3 + R_{in}) \sim 0$$




$$R_{in} \sim 10^{10} \Omega$$



Origin templates for this week Lab.

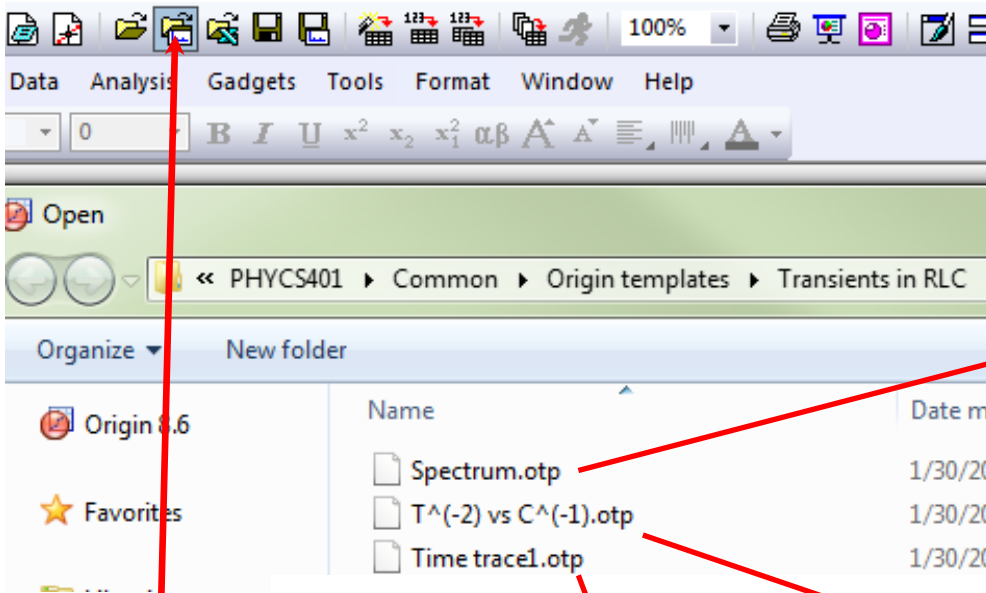

**Open template
button**

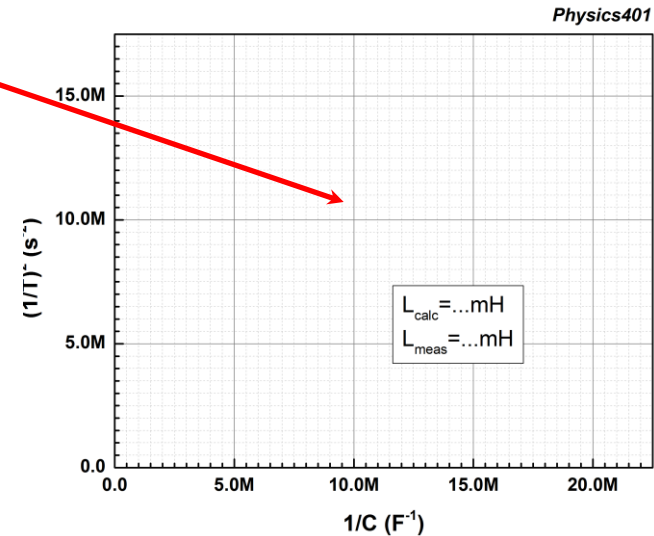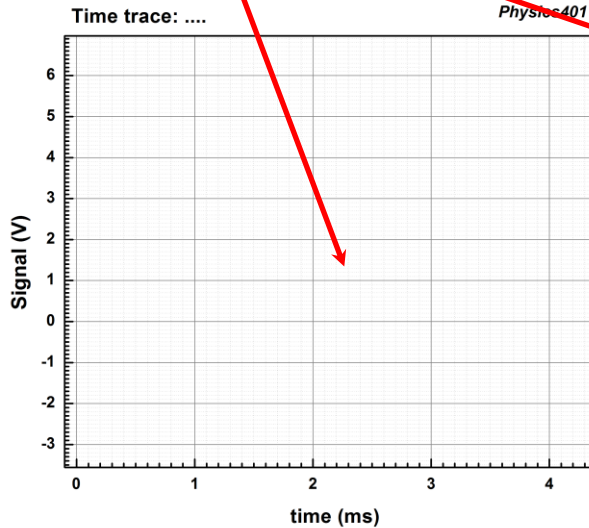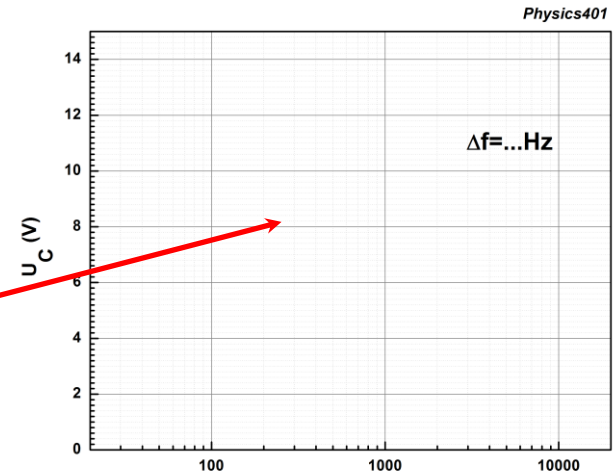


Origin manuals



Working with Origin 8.6.

Step1. Importing data

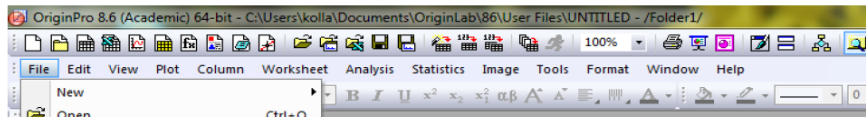


Very short and simple manual which covers only main general operations with Origin. Document located on server (\\Phyap\portal\PHYCS401\Comm on\Origin manuals) and there is a link from P401 WEB page

There are (\\Phyap\portal\PHYCS401\Common\Origin manuals) also manuals from OriginLab.

Do not forget about Origin Help

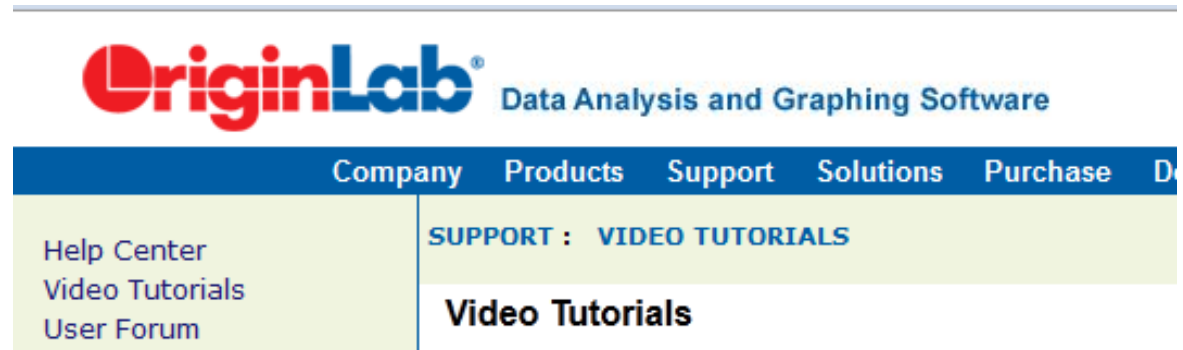Video Tutorials at the site of the company



<http://www.originlab.com/index.aspx?go=SUPPORT/VideoTutorials>

