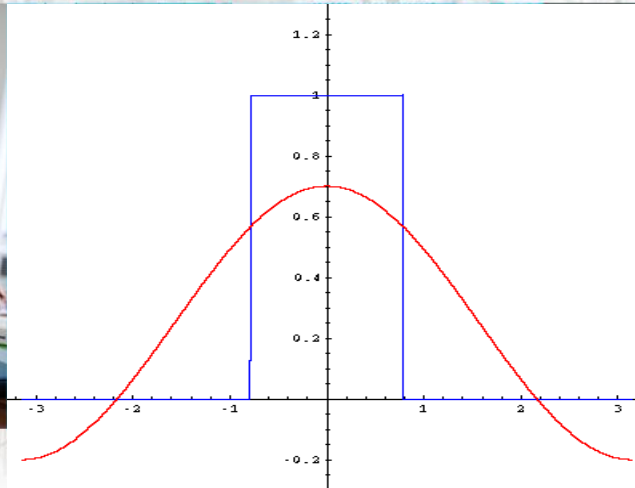


Frequency domain analysis of linear circuits using synchronous detection

Physics 401, Spring 2014.

Eugene V. Colla



Frequency domain analysis of linear circuits using synchronous detection

Outline

1. Fourier transform,. Discrete Fourier transform. Some properties.
2. Time domain and Frequency domain representation of the data.
3. Frequency domain spectroscopy (FDS)
4. Lock-in amplifiers
5. Practical application of lock-in's in FDS
6. Taking data and simple data analysis using OriginPro.




in 1822, Jean Baptiste Fourier developed the theory that shows that any real waveform can be represented by the sum of sinusoidal waves.




**Jean Baptiste Joseph
Fourier
(1768 – 1830)**

Let us try to create the square wave as a sum of sine waves of different frequencies

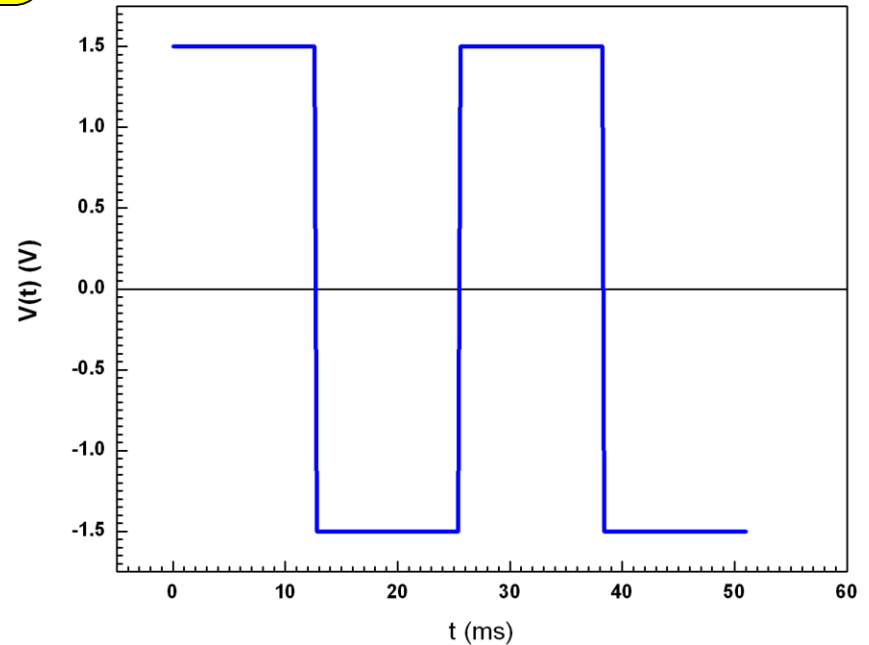
**Square wave.
 $F=40\text{Hz}$, $A=1.5\text{V}$**




$$A_1 \sin(2\pi\omega t)$$

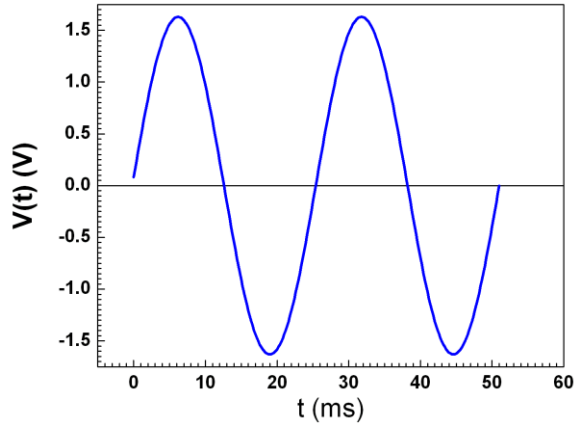

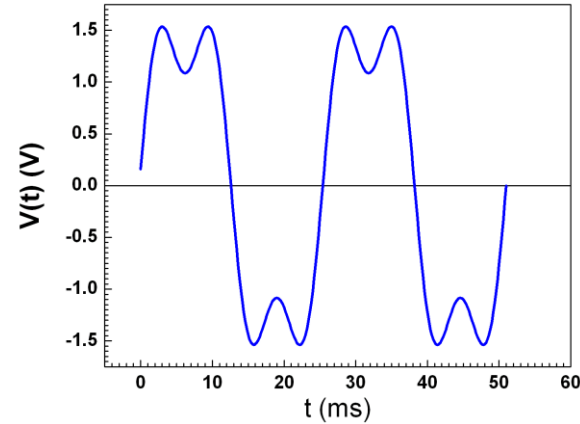
$$A_1 \sin(2\pi\omega t) + A_3 \sin(2\pi 3\omega t + \varphi_3)$$


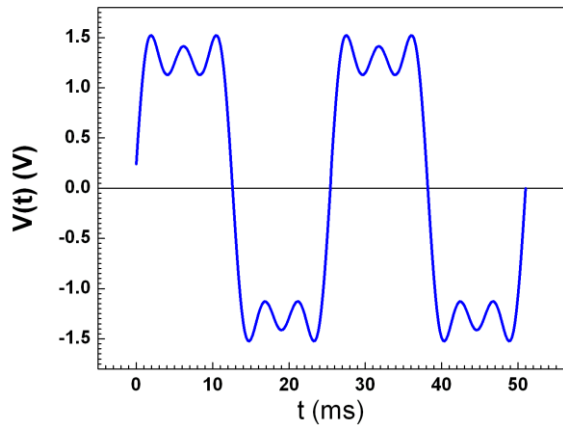
$$A_1 \sin(2\pi\omega t) + A_3 \sin(2\pi 3\omega t + \varphi_3) + A_5 \sin(2\pi 5\omega t + \varphi_5)$$


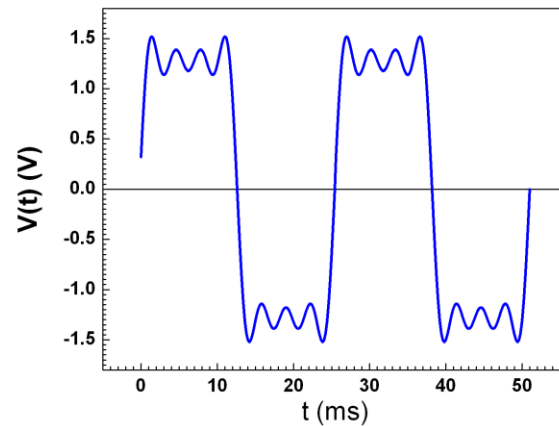
$$A_1 \sin(2\pi\omega t) + A_3 \sin(2\pi 3\omega t + \varphi_3) + A_5 \sin(2\pi 5\omega t + \varphi_5) + A_7 \sin(2\pi 7\omega t + \varphi_7)$$



Fourier Transform

The continuous Fourier transformation of the signal $h(t)$ can be written as:

$$H(f) = \int_{-\infty}^{+\infty} h(t) e^{2\pi jft} dt; \quad j = \sqrt{-1}$$

$H(f)$ represents in frequency domain mode the time domain signal $h(t)$

Equation for inverse Fourier transform gives the correspondence of the infinite continuous frequency spectra to the corresponding time domain signal.

$$h(t) = \int_{-\infty}^{+\infty} H(f) e^{-2\pi jft} df$$


In real life we working with discrete representation of the time domain signal recorded during a finite time.

Discrete Fourier Transform


It comes out that in practice more useful is the representation the frequency domain pattern of the time domain signal h_k as sum of the frequency harmonic calculated as:

$$H_n = H(f_n) = \frac{1}{N} \sum_{k=0}^{N-1} h_k e^{2\pi kn/N}$$

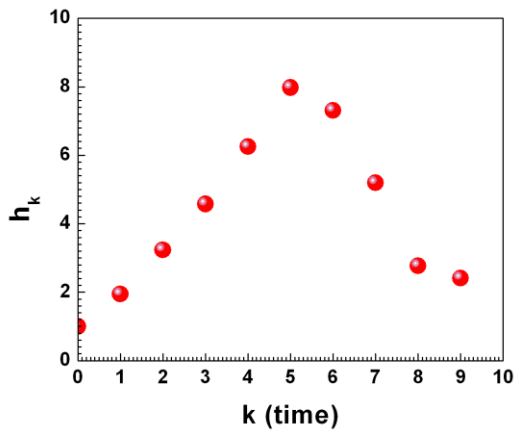Δ is the sampling interval, N – number of collected points



Time domain

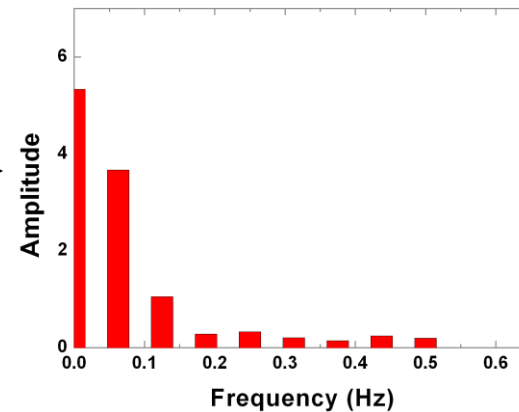

Frequency domain

Discrete Fourier Transform

For periodic signals with period T_0 :

$$F(t) = \frac{a_0}{2} + \sum_{n=1}^{\infty} a_n \cos\left(\frac{2\pi nt}{T_0}\right) + \sum_{n=1}^{\infty} b_n \sin\left(\frac{2\pi nt}{T_0}\right)$$




$$a_n = \frac{2}{T_0} \int_0^{T_0} F(t) \cos\left(\frac{2\pi nt}{T_0}\right) dt; \quad b_n = \frac{2}{T_0} \int_0^{T_0} F(t) \sin\left(\frac{2\pi nt}{T_0}\right) dt;$$

$$a_0 = \frac{2}{T_0} \int_0^{T_0} F(t) dt;$$

Discrete Fourier Transform

Now how I found the amplitudes of the harmonics to compose the square wave signal from sine waves of different frequencies.


Time domain signal

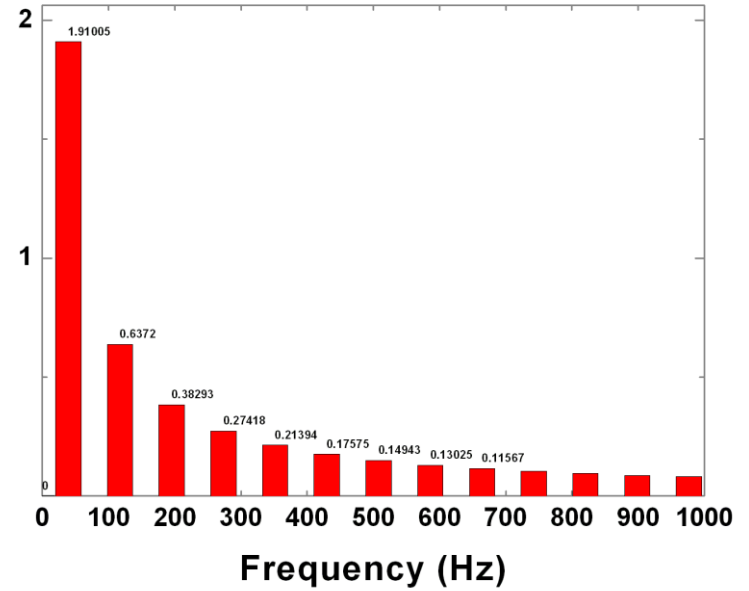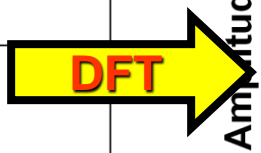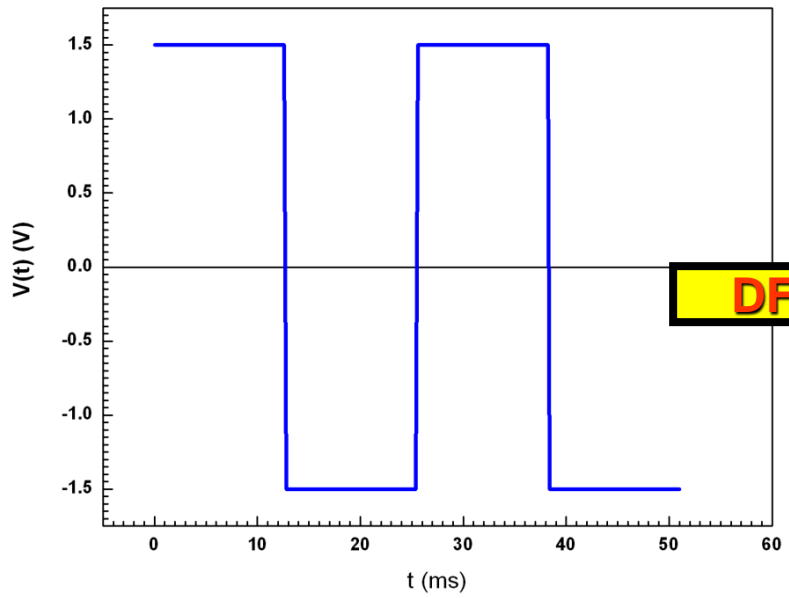

Decomposition the signal into the sine wave harmonics. The only modulus's of the harmonics amplitudes are presented in this picture.

Frequency Domain Spectroscopy


(linear system)

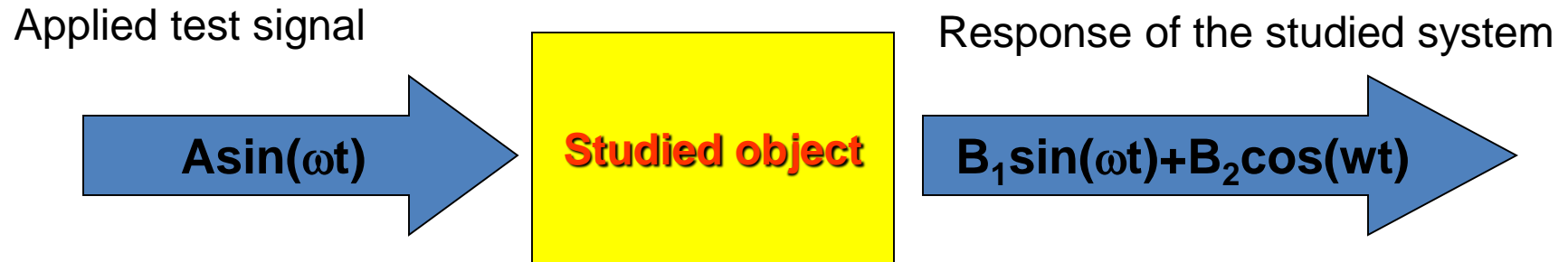

We applying the sine wave signal to tested object and measuring the response. Varying the frequency we can study the frequency properties of the system

Lock-in amplifier

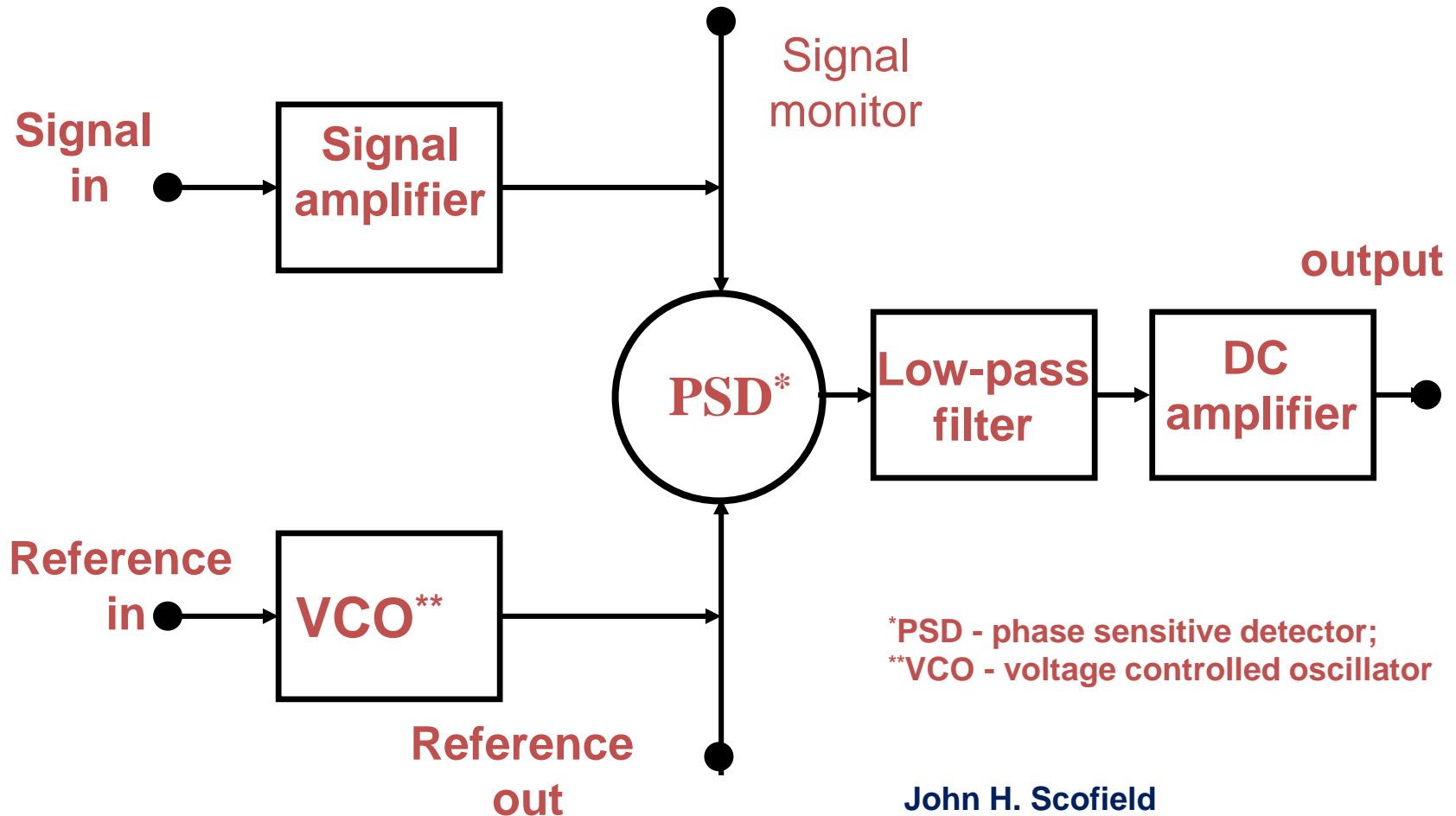
Now about the most powerful tool which can be used in frequency domain technique.



*PSD - phase sensitive detector;
**VCO - voltage controlled oscillator


John H. Scofield
American Journal of Physics 62 (2)
129-133 (Feb. 1994).

Lock-in amplifier. How it works.

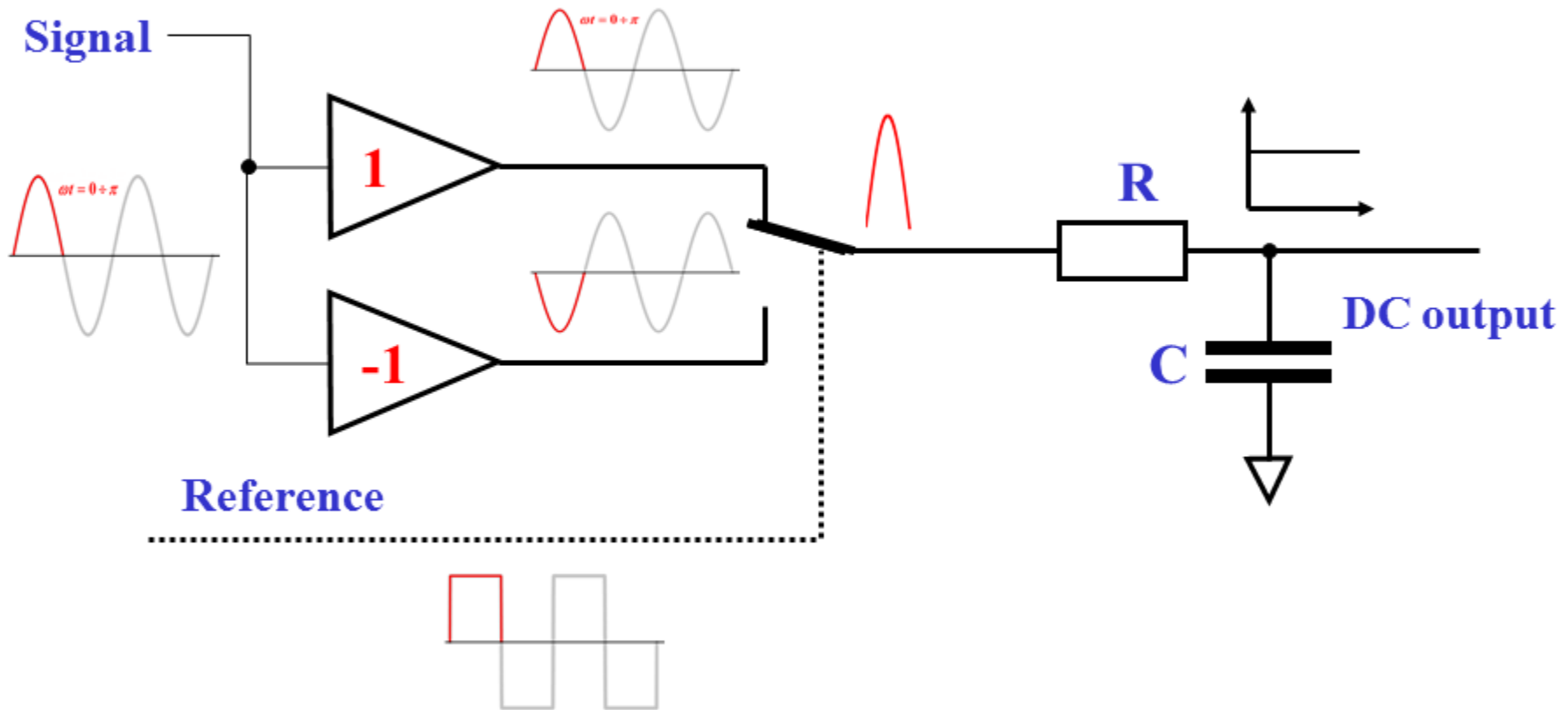


The DC output signal is a magnitude of the product of the input and reference signals. AC components of output signal are filtered out by the low-pass filter with time constant τ (her $\tau=RC$)

Lock-in amplifier. Phase shift.

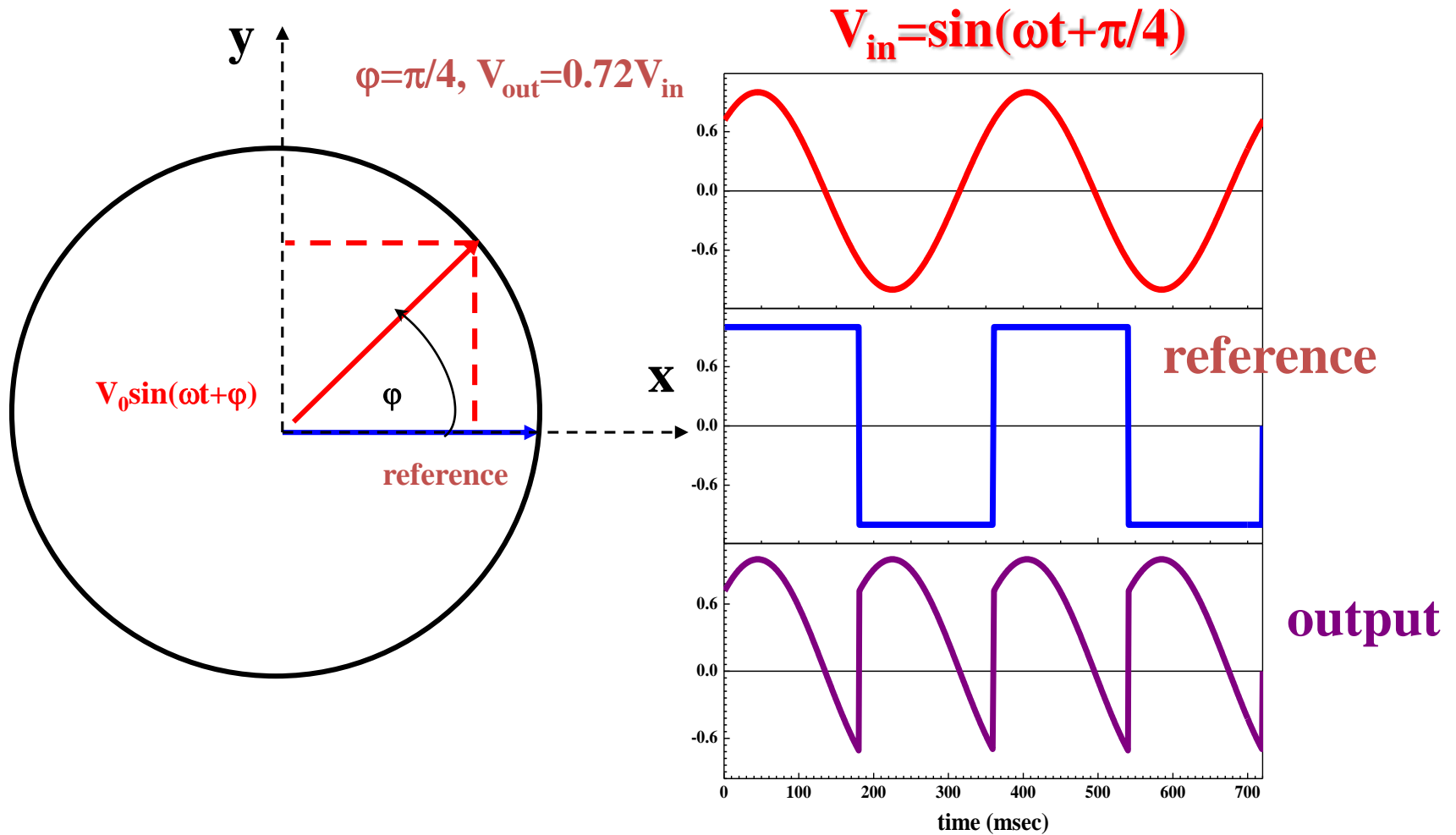


Lock-in amplifier. Two channels demodulation.

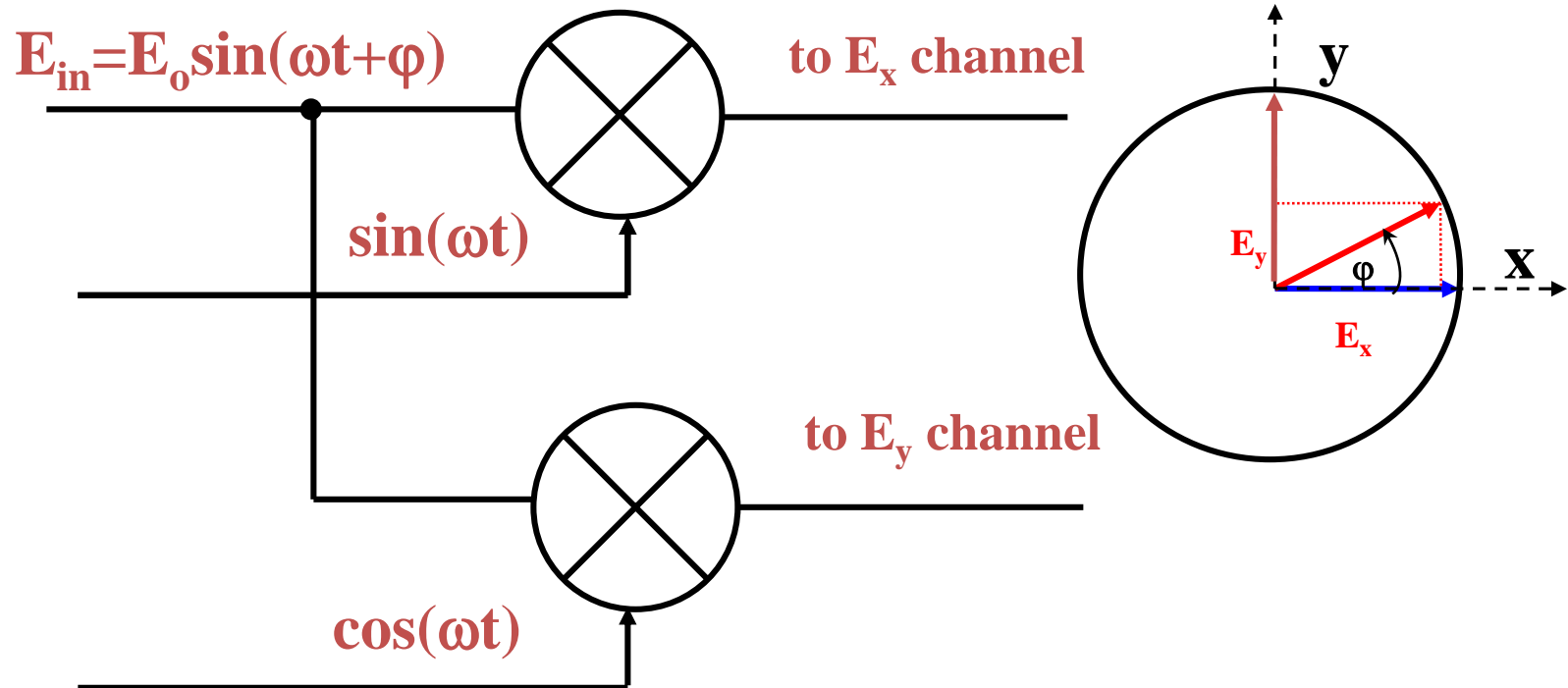In many scientific applications it is a great advantage to measure both components (E_x , E_y) of the input signal. We can use two lock-ins to do this or we can measure these value in two steps providing the phase shift of reference signal 0 and $\pi/4$. Much better solution is to use the lock-in amplifier equipped by two demodulators.



Digital Lock-in amplifier

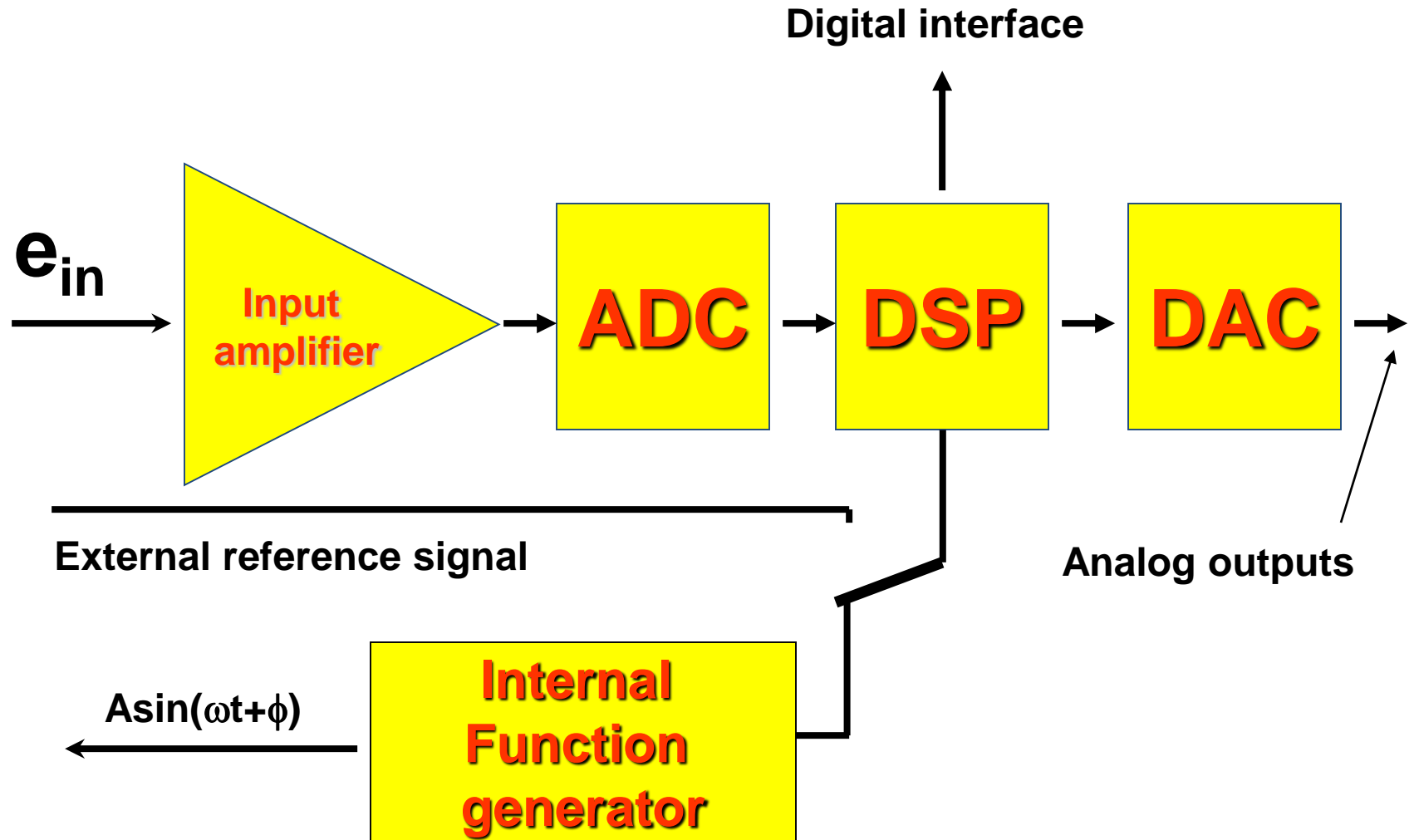


Digital Lock-in amplifier




Digital lock-in SR830

[Lock-in demo](#)

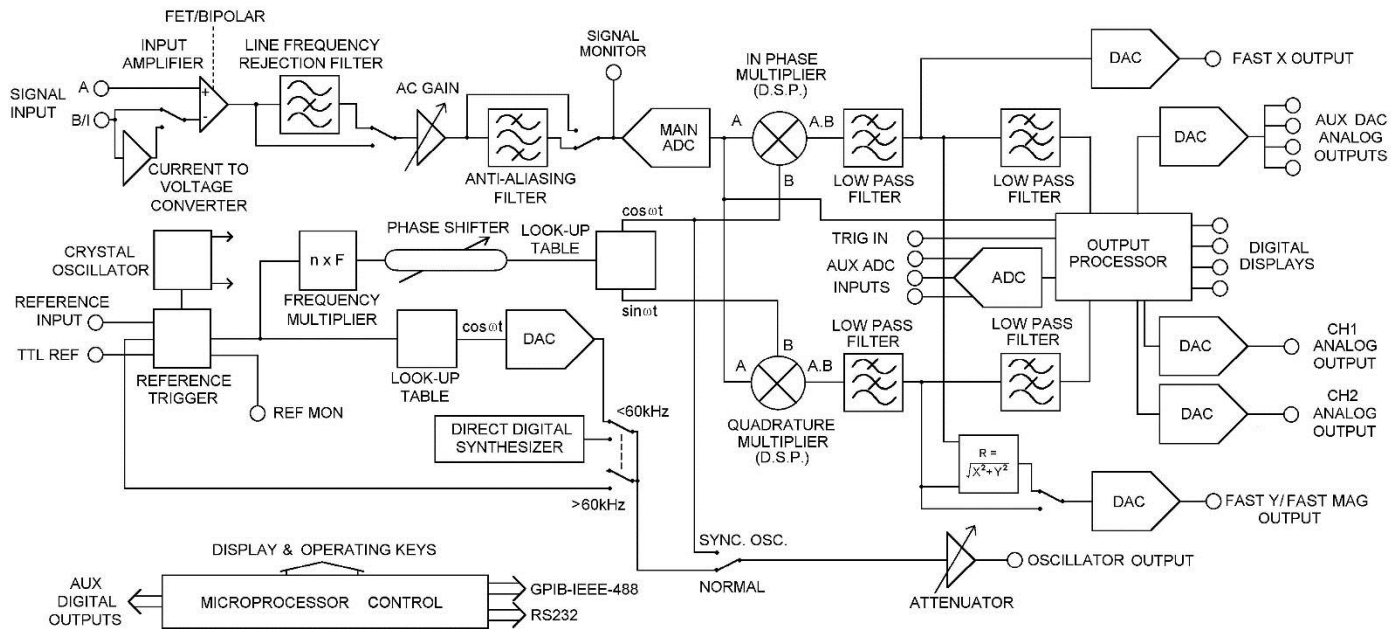


Digital Lock-in amplifier. SR830

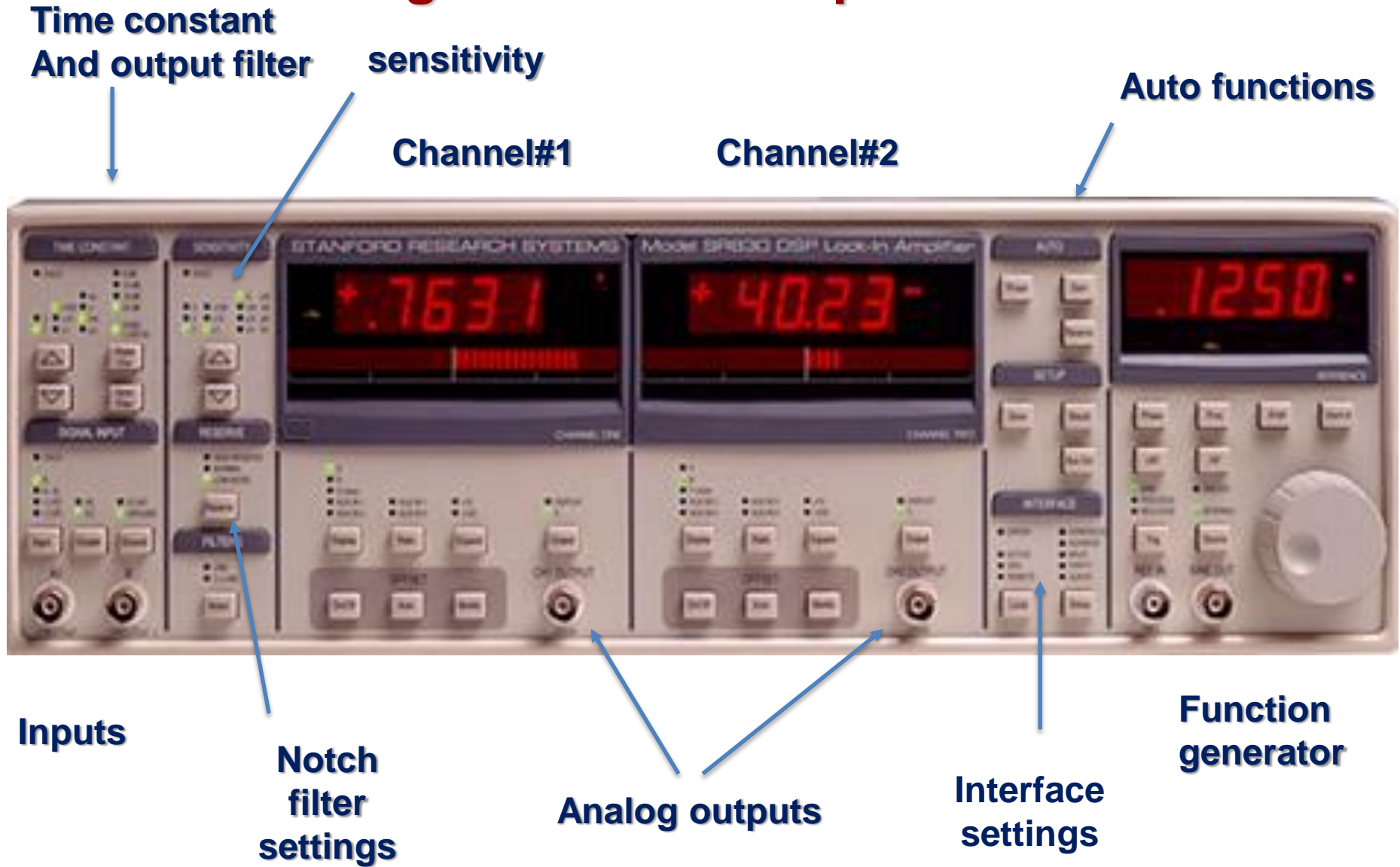

Experiments. Main idea.

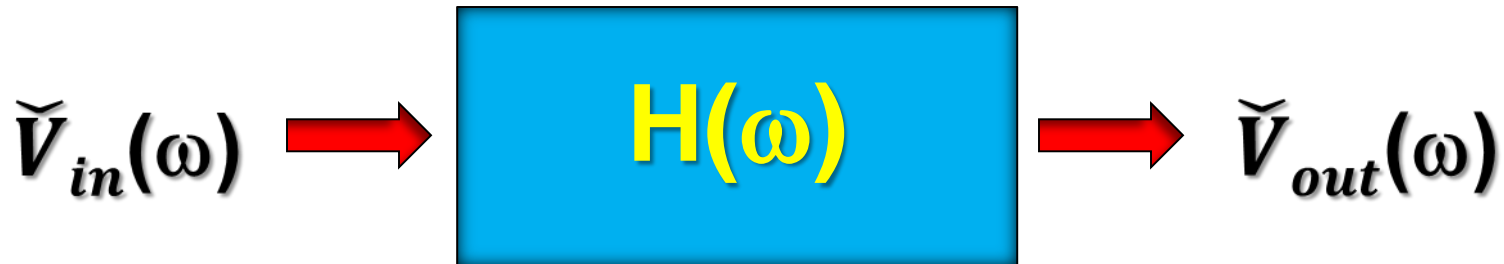Investigating the frequency response of circuit.



Frequency domain representation of the system


Response function $\rightarrow \check{H}(\omega) = \frac{\check{V}_{out}}{\check{V}_{in}}$

Linear systems are those that can be modeled by linear differential equations.


Typical application of the lock-in amplifier



Receiver

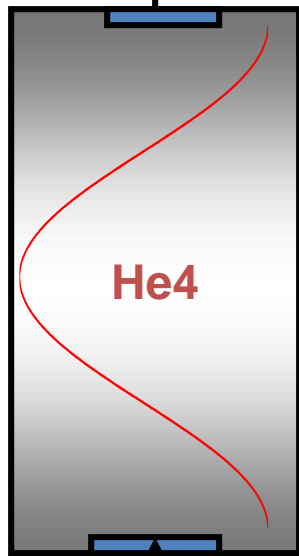

He4

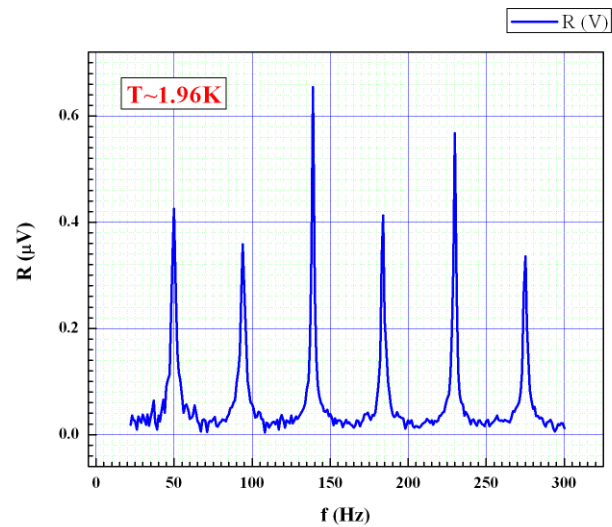

AC drive signal


Transmitter (heater)



Experiments. Main idea.

Calculation of the response function in frequency domain mode.


Example 1. High-pass filter.

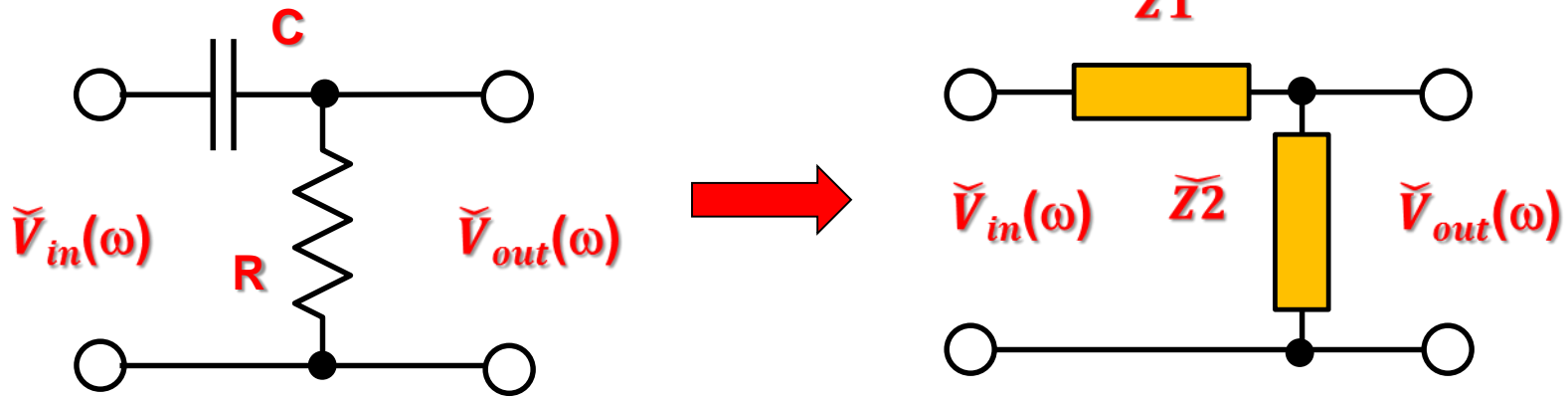

Applying the Kirchhoff Law to this simple network

$$\tilde{V}_{out}(\omega) = \tilde{H}(\omega) * \tilde{V}_{in}(\omega) = \tilde{V}_{in}(\omega) \frac{\tilde{Z}_2(\omega)}{\tilde{Z}_1(\omega) + \tilde{Z}_2(\omega)}$$

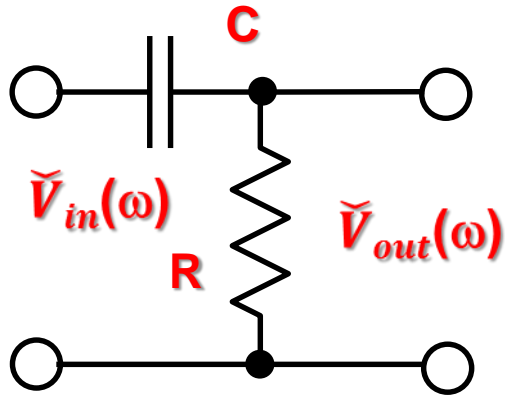Experiments. Calculation of the response function in frequency domain mode. High-pass filter



Ideal case

$$\tilde{Z}_R = R$$

$$\tilde{Z}_L = j\omega L$$

$$\tilde{Z}_C = \frac{1}{j\omega C} = -\frac{j}{\omega C}$$

More realistic


$$\tilde{Z}_R = R + \dots$$

$$\tilde{Z}_L = j\omega L + R_L$$

$$\tilde{Z}_C = \frac{1}{j\omega C} = \frac{1}{j\omega C + R_C^{-1}}$$

$$\tilde{V}_{out}(\omega) = \tilde{H}(\omega) * \tilde{V}_{in}(\omega) = \tilde{V}_{in}(\omega) \frac{\tilde{Z}_2(\omega)}{\tilde{Z}_1(\omega) + \tilde{Z}_2(\omega)}$$

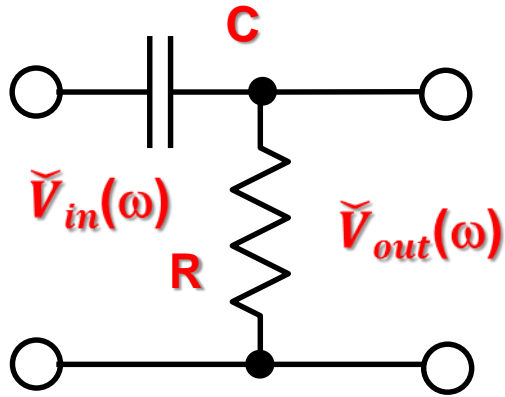Experiments. Calculation of the response function in frequency domain mode. High-pass filter



τ – time constant of the filter



ω_c - cutoff frequency

$$\tilde{H}(\omega) = H_R(\omega) + jH_I(\omega) = \frac{R}{R + \frac{1}{j\omega C}} = \frac{j\omega RC}{1 + j\omega RC} = \frac{j\omega\tau}{1 + j\omega\tau} = \frac{\omega\tau}{(1 + \omega^2\tau^2)}(\omega\tau + j);$$


where $\tau = RC = \omega_c^{-1}$;

$$|\tilde{H}(\omega)| = \sqrt{H_R^2 + H_I^2} = \frac{\omega\tau}{\sqrt{1 + (\omega\tau)^2}}; \quad \theta(\omega) = \arctan\left(\frac{H_I(\omega)}{H_R(\omega)}\right) = \arctan\left(\frac{1}{\omega\tau}\right)$$

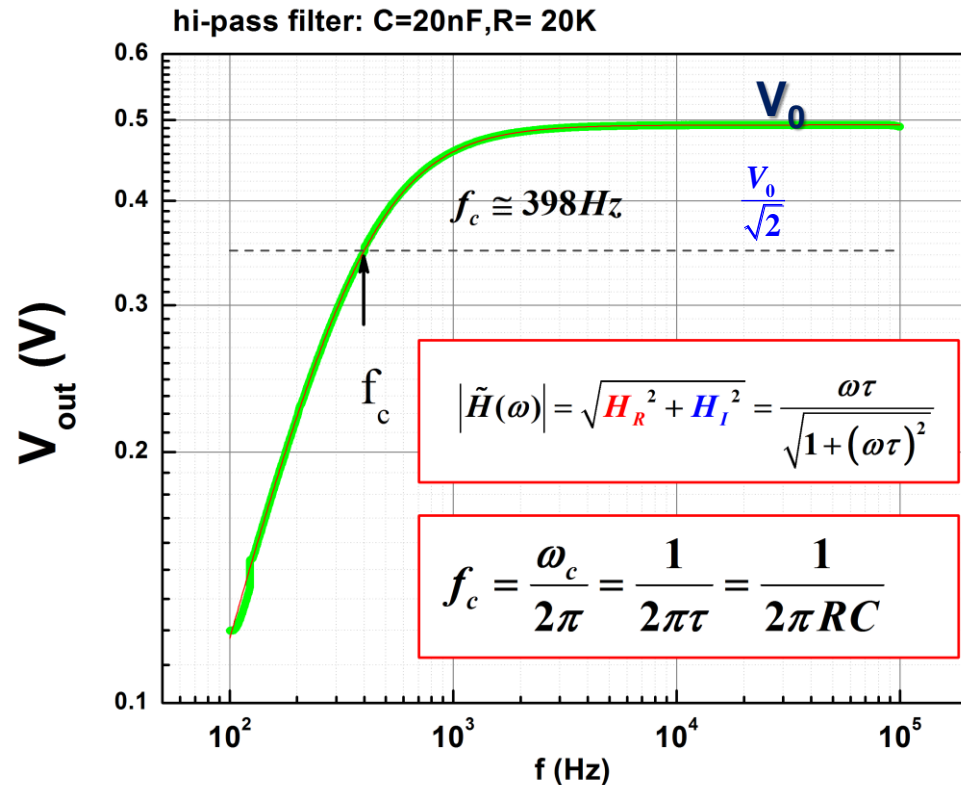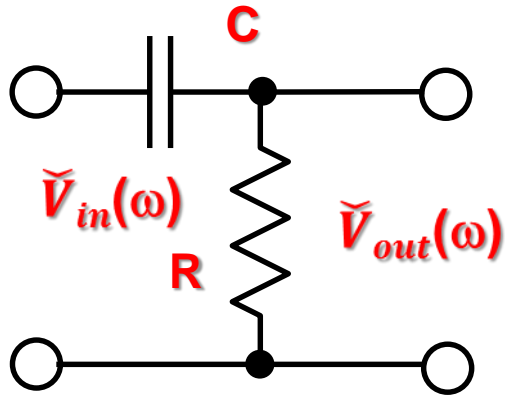Experiments. Calculation of the response function in frequency domain mode. High-pass filter



High-pass filter. Fitting

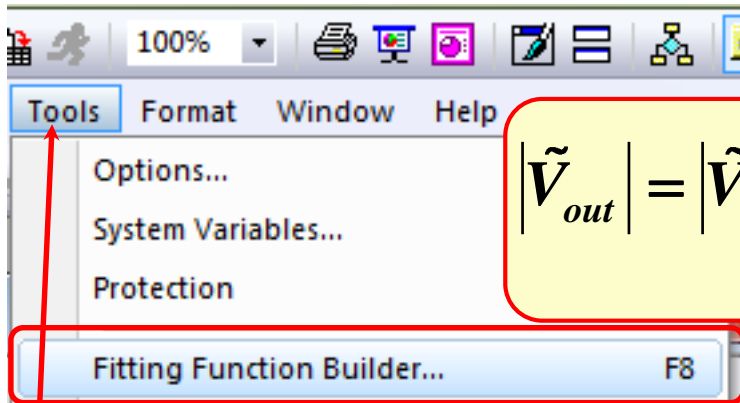

$$|\tilde{V}_{out}| = |\tilde{V}_{in}| * |\tilde{H}(\omega)| = V_0 * \frac{\omega\tau}{\sqrt{1 + (\omega\tau)^2}}; \quad \tau = RC$$

Fitting parameters: V_0 , τ , V_{off}

Parameters

Parameters

Constants



Param	Unit	Meaning	Fixed	Initial Value	Significant Digits
V0		?	<input type="checkbox"/>	1	System <input type="button" value="v"/>
tau		?	<input type="checkbox"/>	1	System <input type="button" value="v"/>
Voff		?	<input type="checkbox"/>	1	System <input type="button" value="v"/>

Function Body (Dependent Variables : y)




$$y = V_0 * 2 * \pi * x * \tau / \sqrt{1 + (2 * \pi * \tau * x)^2} + V_{off}$$

Fitting function 

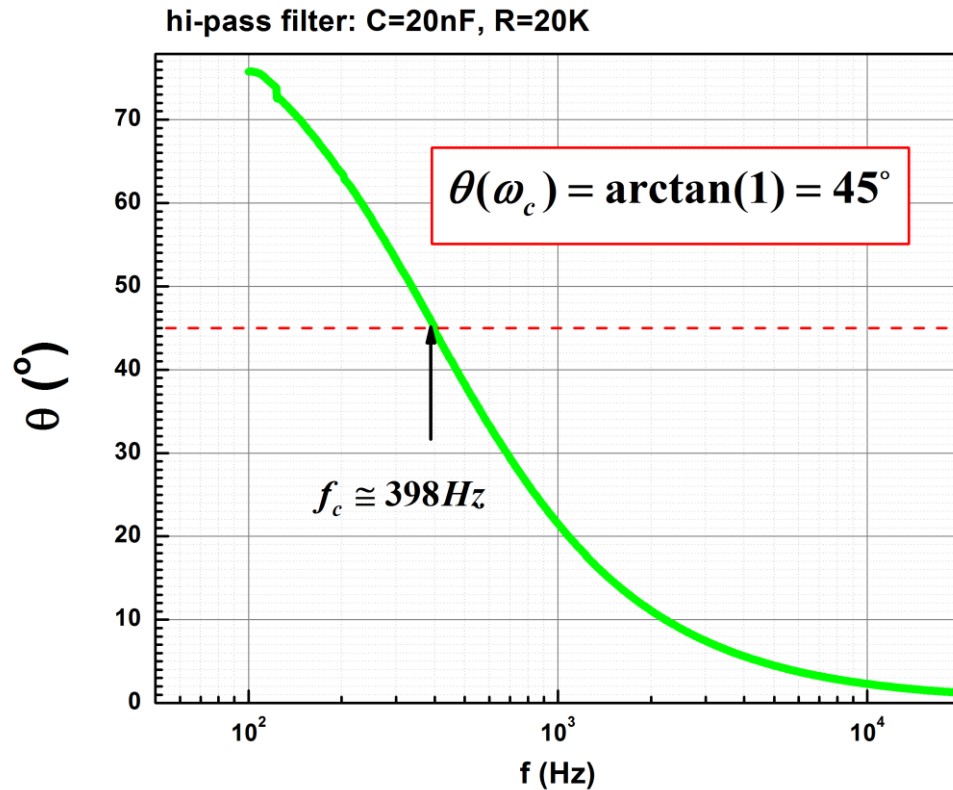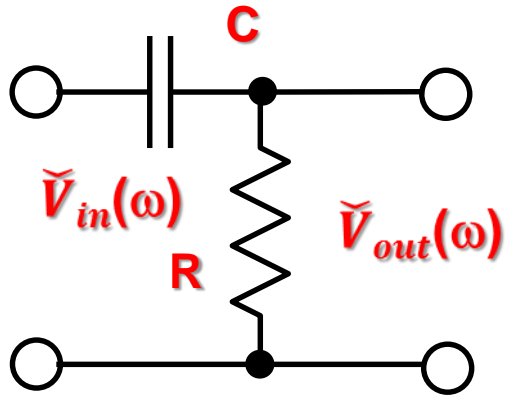Experiments. Calculation of the response function in frequency domain mode. High-pass filter



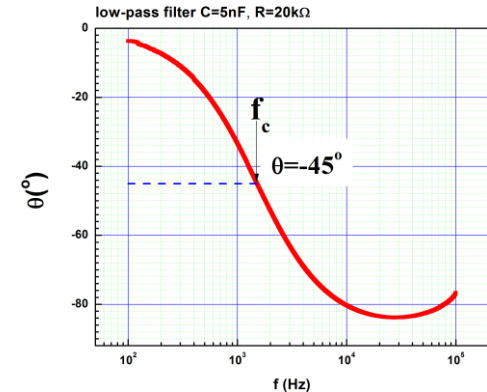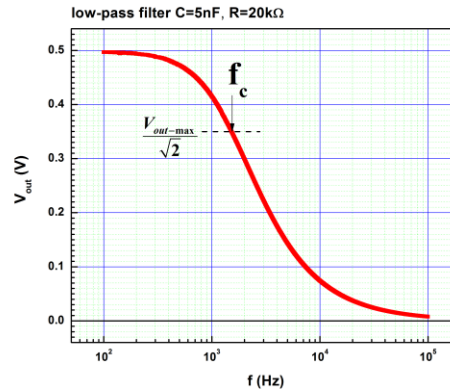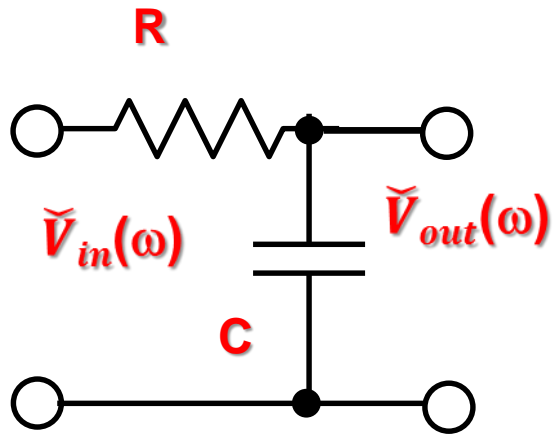Experiments. Calculation of the response function in frequency domain mode. Low-pass filter




$$\tilde{H}(\omega) = H_R(\omega) + jH_I(\omega) = \frac{1}{R + \frac{1}{j\omega C}} = \frac{1}{1 + j\omega RC} = \frac{1}{1 + j\omega\tau} = \frac{(1 - j\omega\tau)}{(1 + \omega^2\tau^2)};$$

where $\tau = RC = \omega_c^{-1}$;

$$|\tilde{H}(\omega)| = \sqrt{H_R^2 + H_I^2} = \frac{1}{\sqrt{1 + (\omega\tau)^2}}; \quad \theta(\omega) = \arctan\left(\frac{H_I(\omega)}{H_R(\omega)}\right) = -\arctan(\omega\tau)$$

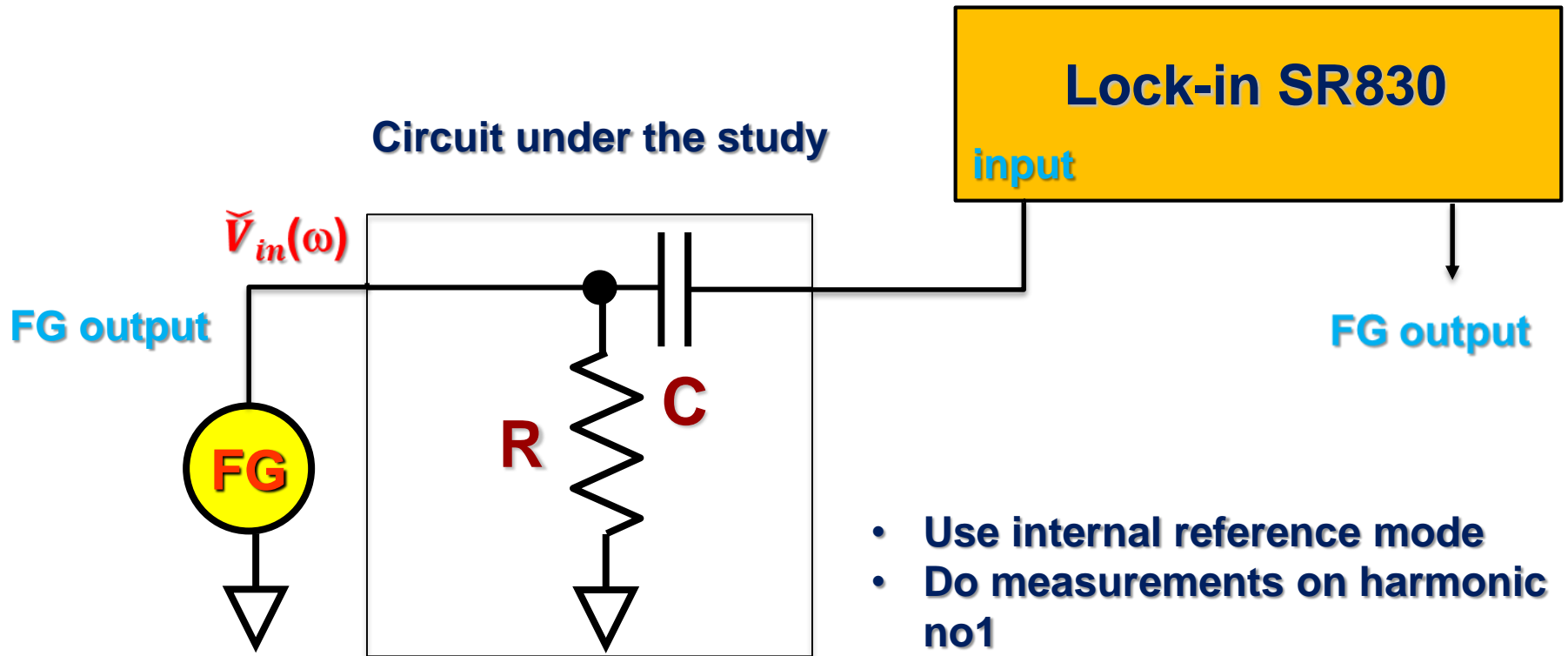
Application of the lock-in amplifier for study of the transfer function of the RLC circuit




Setup for measuring of the response function of the Hi-pass filter

- Use internal reference mode
- Do measurements on harmonic no1
- Take care about time constant – should be at least ~10 times larger than period of measuring frequency
- Avoid overloading of the lock-in

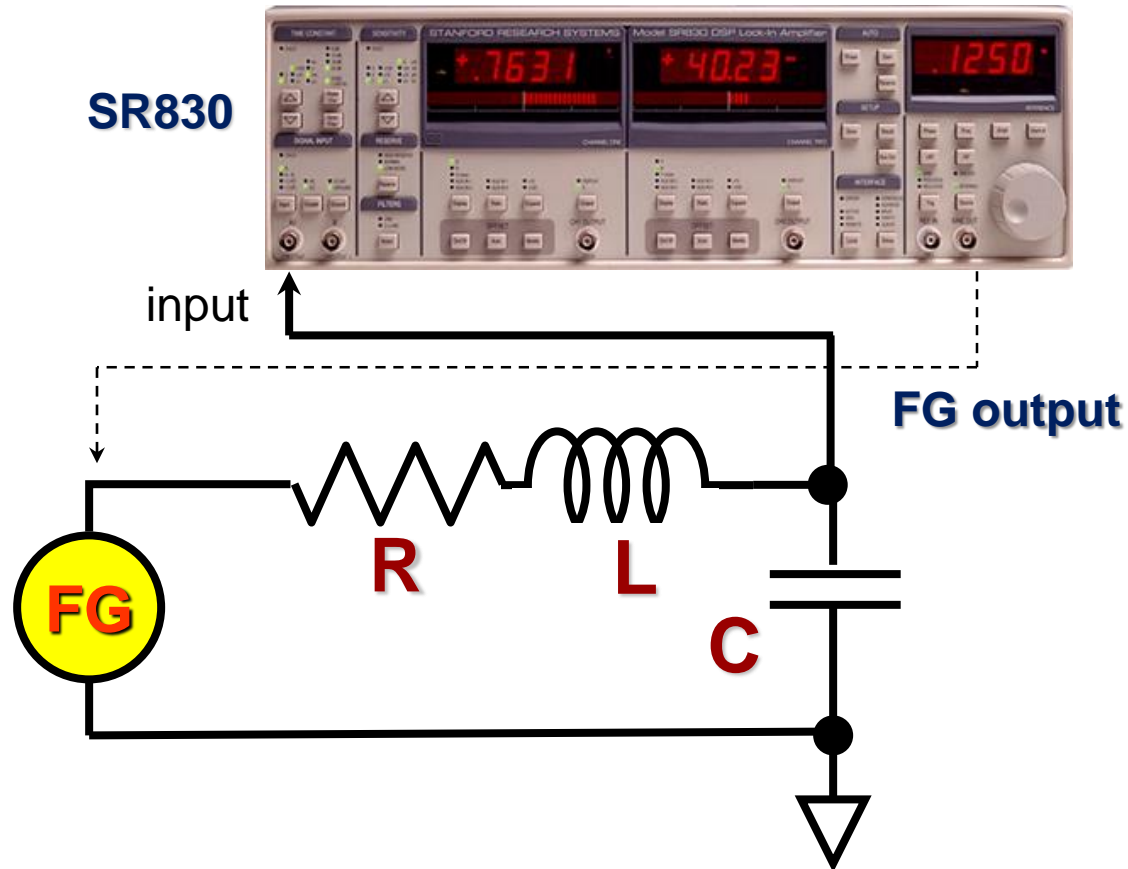Setup for measurement of the transfer function of the RLC circuit.



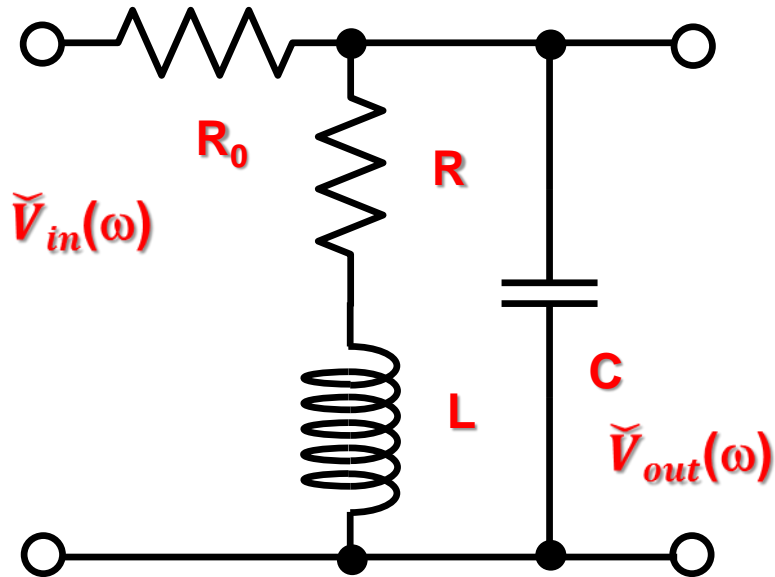Application of the lock-in amplifier for study of the transfer function of the RLC circuit



$$\tilde{H} = \left(\frac{1}{R_0} \right) \frac{R + j\omega L}{1 - \omega^2 LC + j\omega RC} =$$

$$\left(\frac{1}{R_0} \right) \frac{R + j\omega L}{\left(1 - \frac{\omega^2}{\omega_0^2} \right) + j\omega RC}$$

$$R_0 \gg |Z_{RLC}|$$

$$\omega_0 = 2\pi f = \frac{1}{\sqrt{LC}}; \quad Q = \frac{1}{\omega_0 RC} = \frac{1}{R} \sqrt{\frac{L}{C}}$$

Application of the lock-in amplifier for study of the transfer function of the RLC circuit

$$\begin{aligned}\tilde{H} &= \left(\frac{1}{R_0}\right) \frac{R + j\omega L}{\left(1 - \frac{\omega^2}{\omega_0^2}\right) + j\omega RC} = \left(\frac{R}{R_0}\right) \frac{1 + j\frac{\omega}{\omega_0}Q}{\left(1 - \frac{\omega^2}{\omega_0^2}\right) + j\frac{\omega}{\omega_0}\frac{1}{Q}} \\ &= \left(\frac{R}{R_0}\right) \frac{1 - j\frac{\omega}{\omega_0}\left(\frac{1}{Q} - Q\left(1 - \frac{\omega^2}{\omega_0^2}\right)\right)}{\left(1 - \frac{\omega^2}{\omega_0^2}\right)^2 + \left(\frac{\omega}{\omega_0}\right)^2 \frac{1}{Q^2}}\end{aligned}$$

$$\omega_0 = 2\pi f = \frac{1}{\sqrt{LC}}; \quad Q = \frac{1}{\omega_0 RC} = \frac{1}{R} \sqrt{\frac{L}{C}}$$

Another style of the transfer function expressions

$$V_{out} = \frac{\omega_0^2 L}{R_0} \times \frac{\delta \omega_0^2 + j\omega(\omega_0^2 - \omega^2 - \omega\delta)}{(\omega_0^2 - \omega^2)^2 + \omega^2 \delta^2};$$


$$X_{out} = \frac{\omega_0^2 L}{R_0} \times \frac{\delta \omega_0^2}{(\omega_0^2 - \omega^2)^2 + \omega^2 \delta^2};$$

$$Y_{out} = \frac{\omega_0^2 L}{R_0} \times \frac{j\omega(\omega_0^2 - \omega^2 - \omega\delta)}{(\omega_0^2 - \omega^2)^2 + \omega^2 \delta^2};$$

$$\omega_0 = \frac{1}{\sqrt{LC}}; \quad \delta = \frac{R}{L}; \quad Q = \frac{\omega_0}{\delta}$$


Fitting parameters: $\frac{\omega_0^2 L}{R_0}$ - scaling coefficient ω_0 and δ

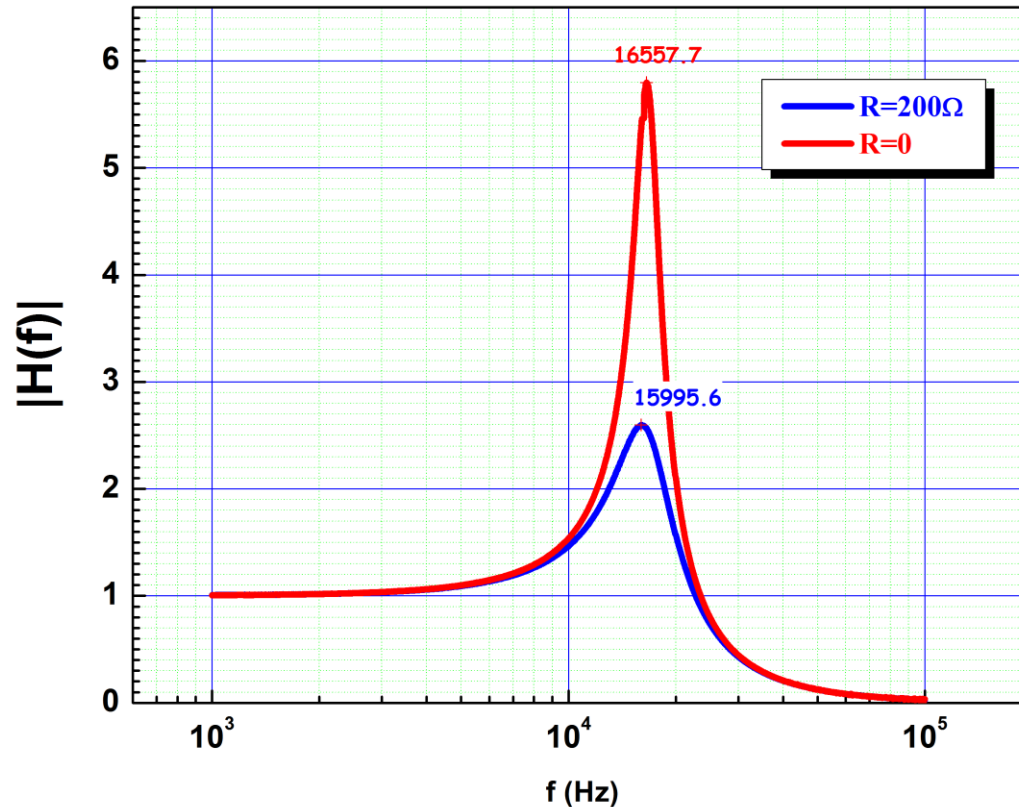Application of the lock-in amplifier for study of the transfer function of the RLC circuit



The resonance curves obtained on RLC circuits with two different damping resistors

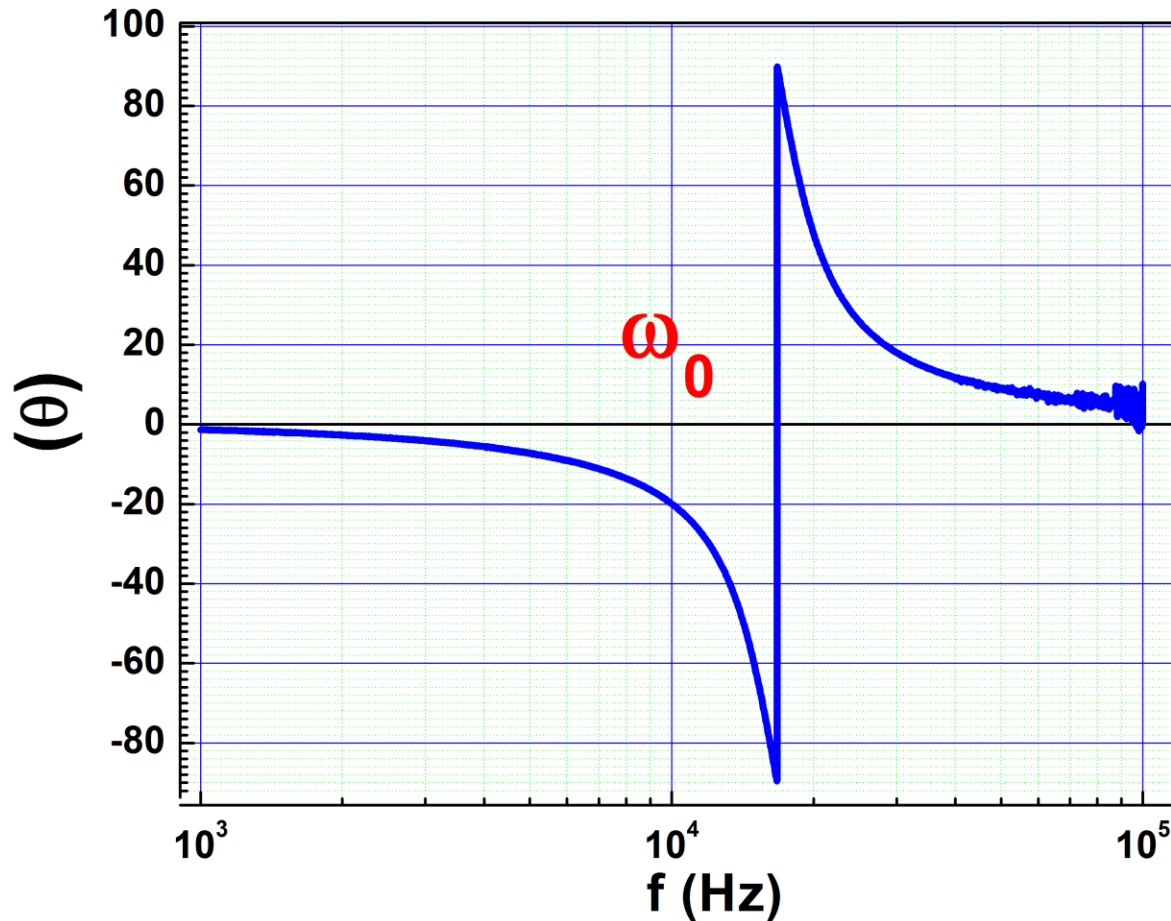
Application of the lock-in amplifier for study of the transfer function of the RLC circuit



The example of fitting of the RLC circuit data to the analytical expression could be found in:


\\engr-file-03\PHYINST\APL Courses\PHYCS401\Common\Simple Examples\Lab 3 Frequency Domain Analysis_example.opj\

Fitting function

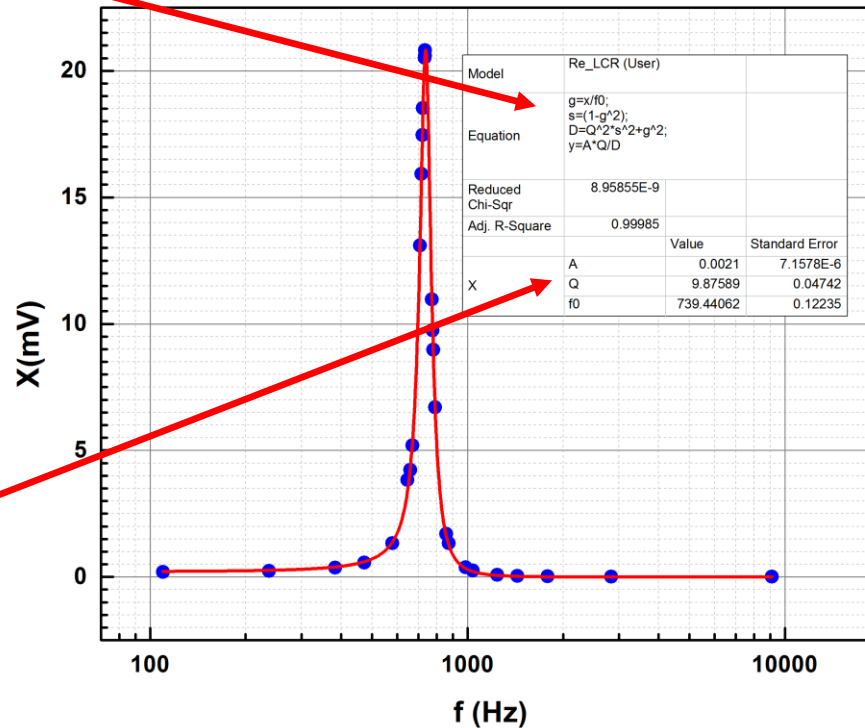

Fitting parameters

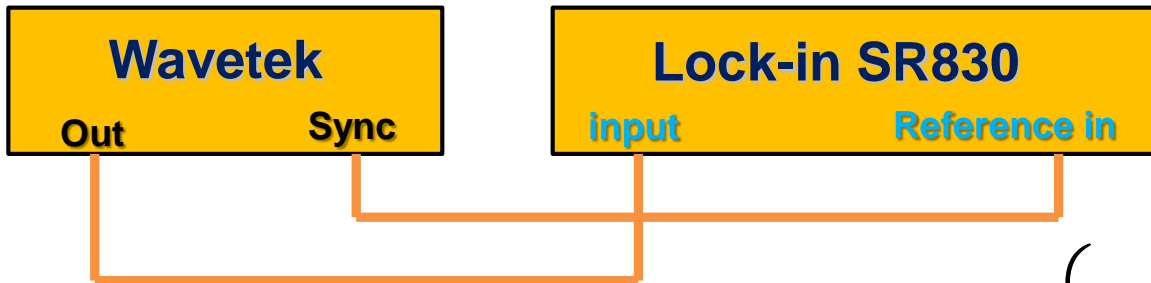
From time domain to frequency domain. Experiment.




$F(t)$ – periodic function $F(t)=F(t+T_0)$:

$$V = V_0 \left(0 < t \leq \frac{T_0}{2} \right);$$
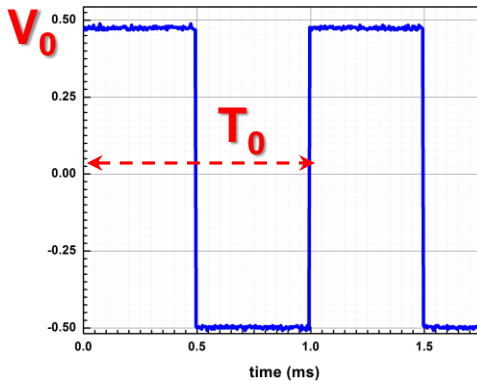
$$-V_0 \left(\frac{T_0}{2} < t \leq T_0 \right)$$



Time domain pattern

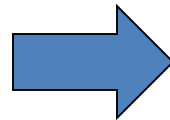


Frequency
domain ?

$$a_n = \frac{2}{T_0} \int_0^{T_0} F(t) \cos\left(\frac{2\pi n t}{T_0}\right) dt;$$

$$b_n = \frac{2}{T_0} \int_0^{T_0} F(t) \sin\left(\frac{2\pi n t}{T_0}\right) dt;$$


$$a_0 = \frac{2}{T_0} \int_0^{T_0} F(t) dt$$

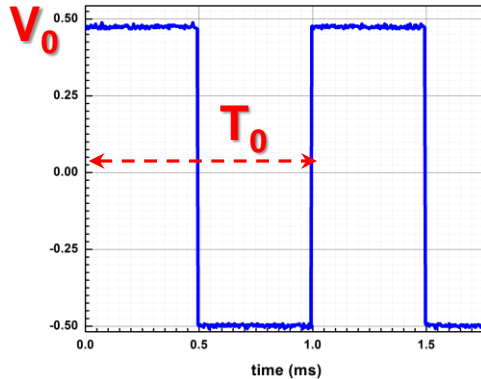From time domain to frequency domain. Experiment with SR830. Results.



Time domain

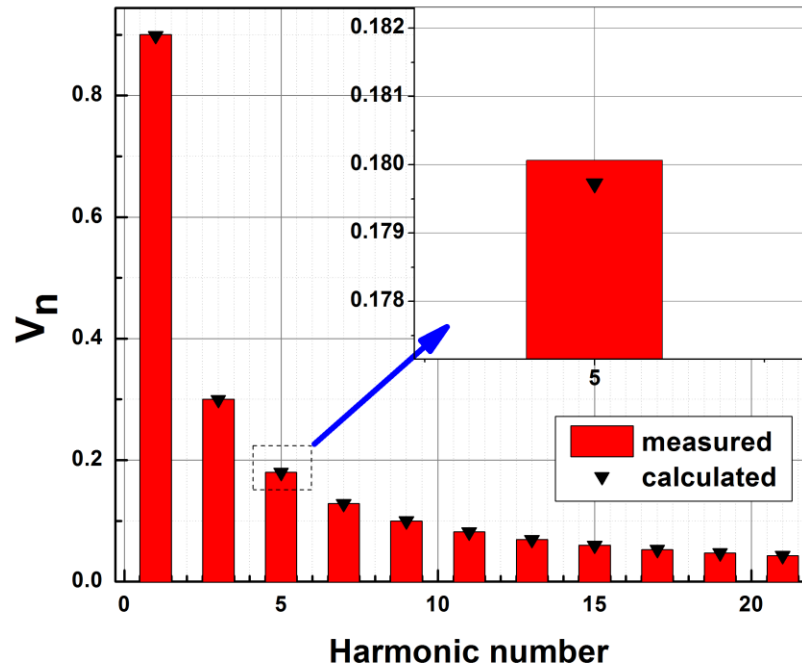
Spectrum measured by
SR 830 lock-in amplifier



Frequency domain


Time domain pattern

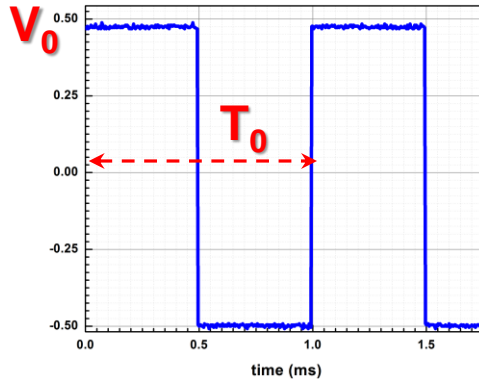From time domain to frequency domain. FFT using Origin. Results.




Time domain taken
by Tektronix scope

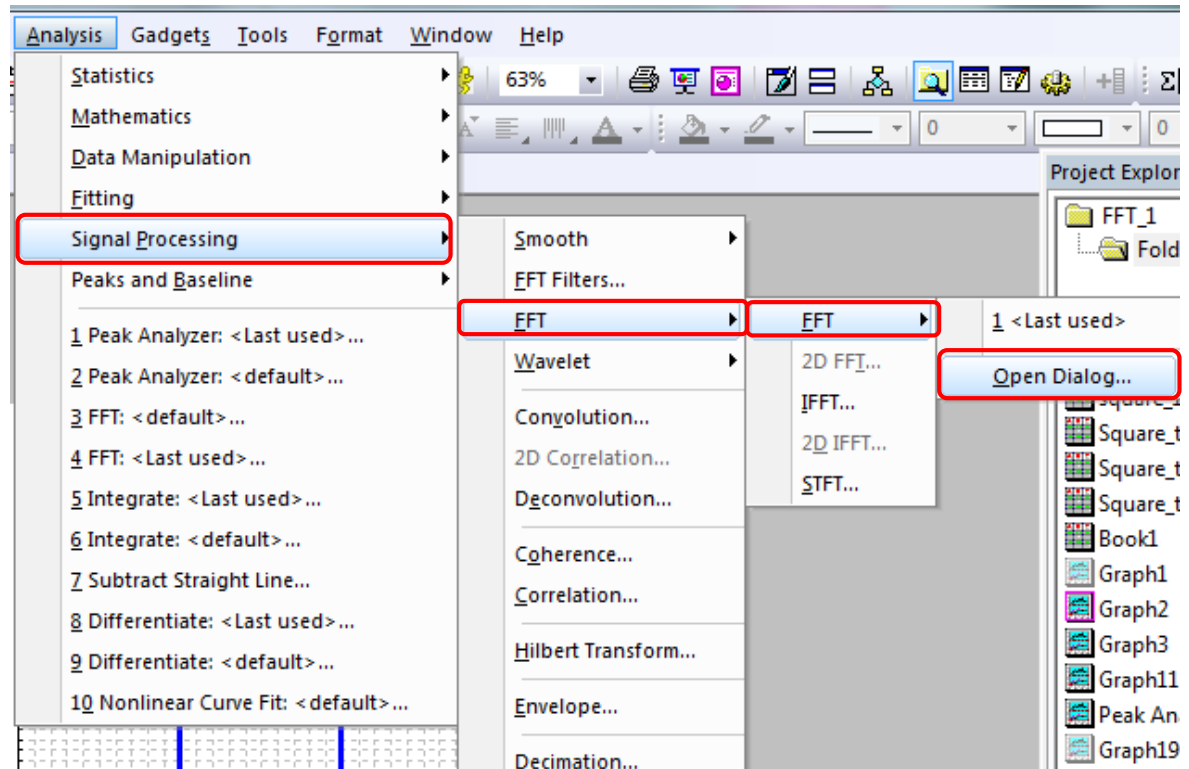Data file can be used to convert
time domain to frequency domain



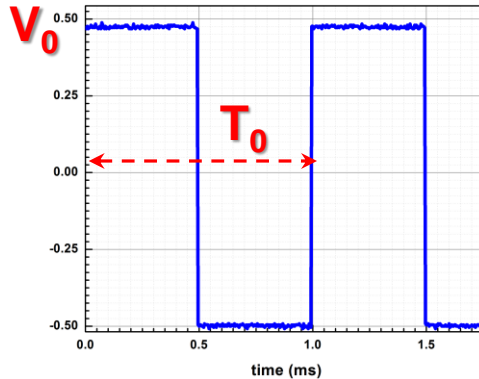From time domain to frequency domain. FFT using Origin. Results.




Time domain taken
by Tektronix scope


Spectrum calculated by
Origin.

Accuracy is limited because
of the limited resolution of
the scope

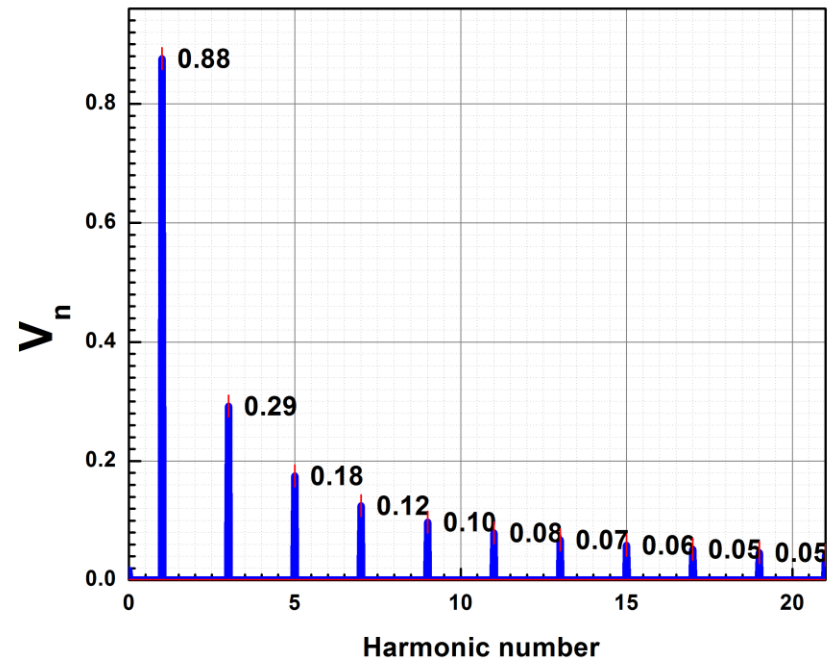Data file can be used to convert
time domain to frequency domain



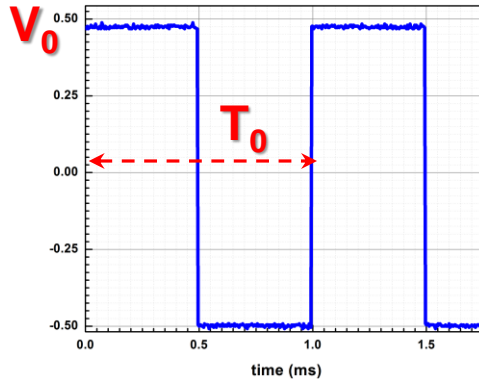
From time domain to frequency domain. Using of the Math option of the scope.




Time domain taken
by Tektronix scope

Spectrum calculated by
Tektronix scope.

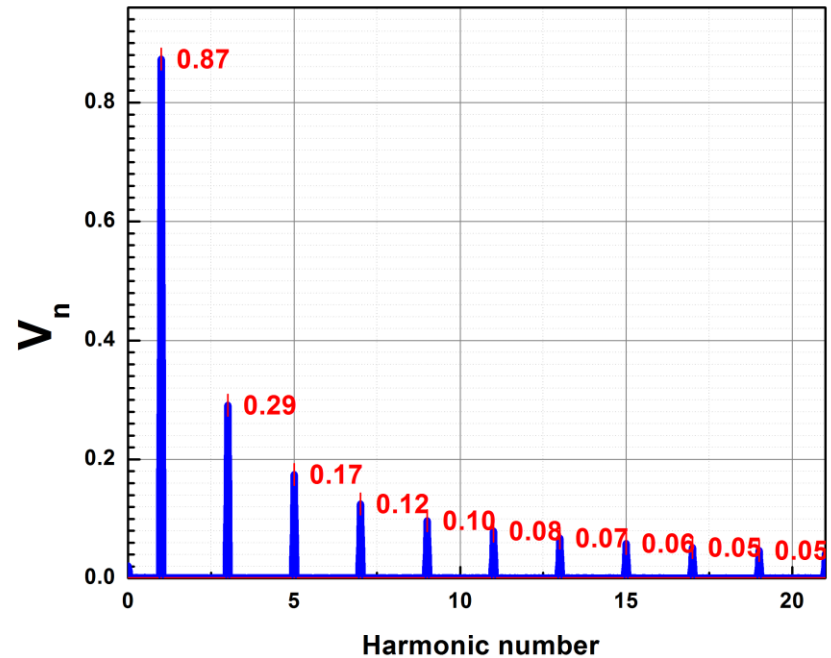
Accuracy is limited because
of the limited resolution of
the scope



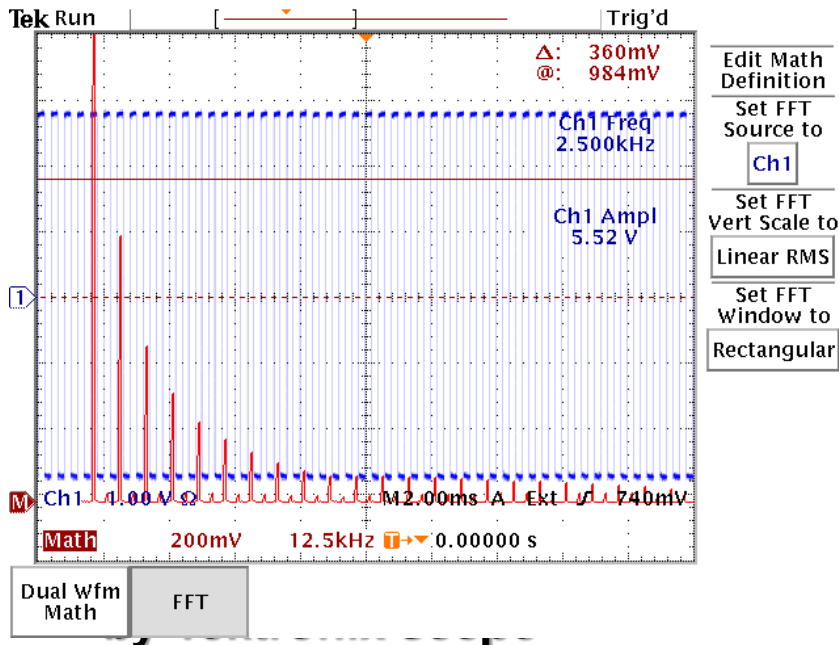From time domain to frequency domain. Using of the Math option of the scope.









Spectrum of the square wave signal

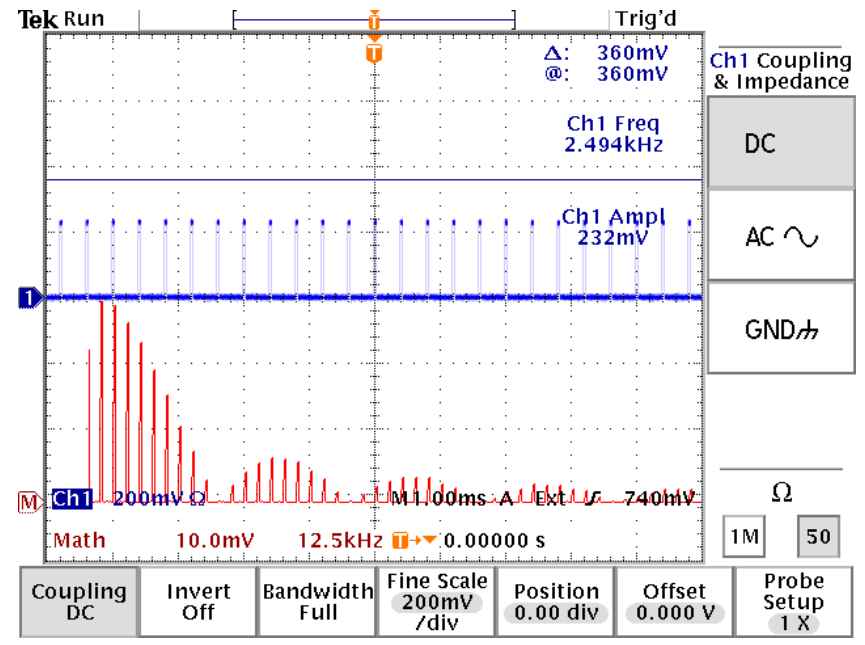

Spectrum of the pulse signal

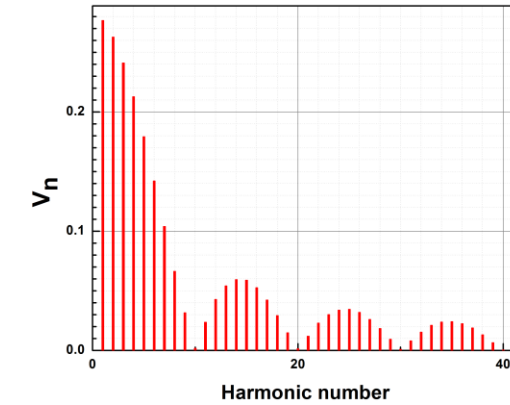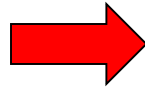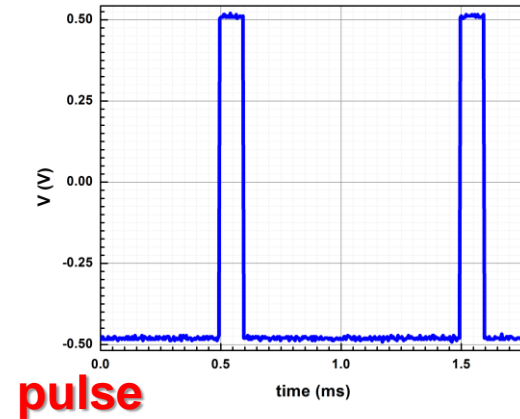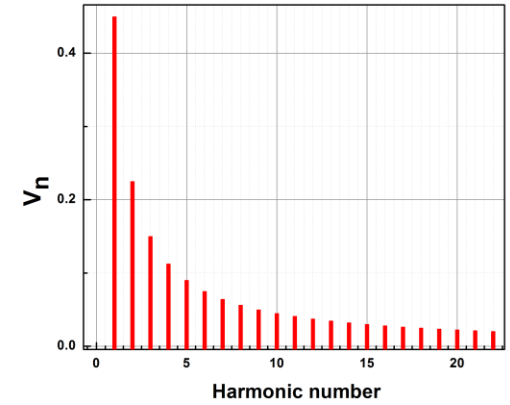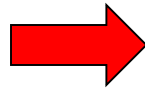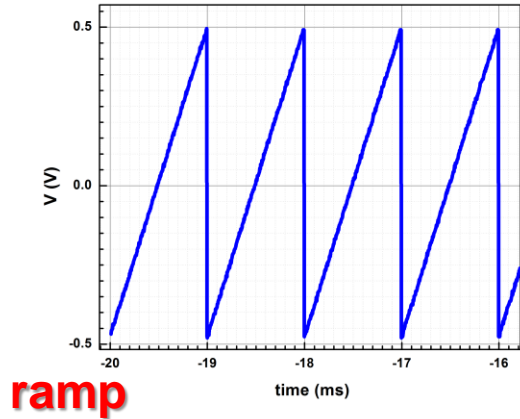From time domain to frequency domain. Different waveforms. Lock-in.



Appendix #1

**Reminder: please submit the reports by e-mail in MsWord or pdf format.
Strongly recommend the file name structure as:**



L1_lab2_student1

The diagram illustrates the file naming convention. The text **L1_lab2_student1** is centered. Below it, three labels are positioned: **Lab section** on the left, **Lab number** in the middle, and **Your name** on the right. Three arrows point from these labels to the corresponding parts of the file name: one from **Lab section** to **L1**, one from **Lab number** to **lab2**, and one from **Your name** to **student1**.

Appendix #2

Origin templates for the Lab are available in:
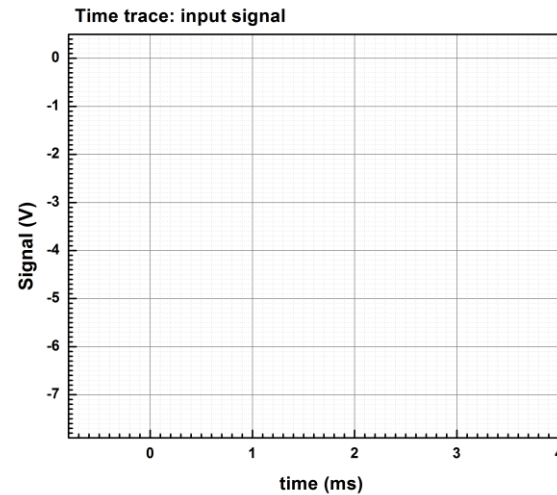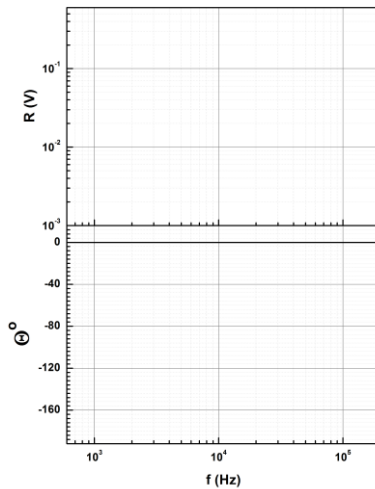
`\\engr-file-03\PHYINST\APL Courses\PHYCS401\Common\Origin templates\frequency domain analysis`



Appendix #3

Lab Server access

\\engr-file-03\PHYINST\APL Courses\PHYCS401

<http://it.engineering.illinois.edu/user-guides/remote-access/how-do-i-connect-network-drive-or-file-share>

If still there are questions – send the question to the help desk: engrit-help@illinois.edu



The screenshot shows the Engineering IT Shared Services website. The header includes the logo and navigation links for MY.ENGR and CONTACT US. The main navigation bar has links for INFORMATION FOR..., SERVICES, ABOUT US, EWS LABS, and USER GUIDES AND FAQ'S. The left sidebar contains a menu with 'User Guides and FAQ's' selected, listing items like 'Connecting to the Network', 'Email and Phones', 'Remote Access', 'Using Linux Apps Remotely with X-Forwarding', 'Accessing the Linux Terminals remotely with SSH', 'Connecting to Citrix from a Mac', 'Connecting to Citrix from a Windows Computer', and 'Connecting to Citrix from an iPhone or iPad'. The main content area shows the breadcrumb 'Home » User Guides and FAQ's » Remote Access' and the title 'How do I connect to a network drive or file share?'. The text below the title states: '10/23/2013 NOTE: Because of file server restructuring, there is now a server for linux files and a server for windows files. The old guide still applies to accessing your Windows files, but will not work for accessing the Linux files, which needs to connect to a linux server. Updated Guide Can Be Found Here: <http://it.engineering.illinois.edu/user-guides/engineering-workstation-s...>'. Below this is the section 'Connecting to Linux File Servers' with the text: 'Any scp, sftp, ssh client should be able to connect to your account and access your linux files. Connect as you would SSH (netid and password for credentials, remlnx.ews.illinois as host, port 22): netidname@remlnx.ews.illinois.edu??'.

References:

1. John H. Scofield, "A Frequency-Domain Description of a Lock-in Amplifier" *American Journal of Physics* 62 (2) 129-133 (Feb. 1994).
2. *Steve Smith* "The Scientist and Engineer's Guide to Digital Signal Processing" copyright ©1997-1998 by Steven W. Smith. For more information visit the book's website at: www.DSPguide.com *
 - You can find a soft copy of this book in:
 - `\\engr-file-03\phyinst\APL Courses\PHYCS401\Experiments`