

Transients and Oscillations in RLC Circuits

Professor Jeff Filippini

Physics 401

Spring 2020




Goals of this Lab

- Concepts: Oscillators in the time domain
 - Transients
 - Resonances
 - Damping regimes
- Implementation: RLC electrical circuits
- Data analysis using Origin

Driven Systems and Transients



- Consider a **system** that takes an input $x(t)$ and yields output $y(t)$
 - We'll focus mostly on (approx.) **linear time-invariant (LTI)** systems, governed by constant-coefficient linear homogeneous differential equations
- The **transient response** of such a system is its (“short-lived”) response to a change in input from an **equilibrium** state
 - Commonly discuss **impulse response** and **step response**

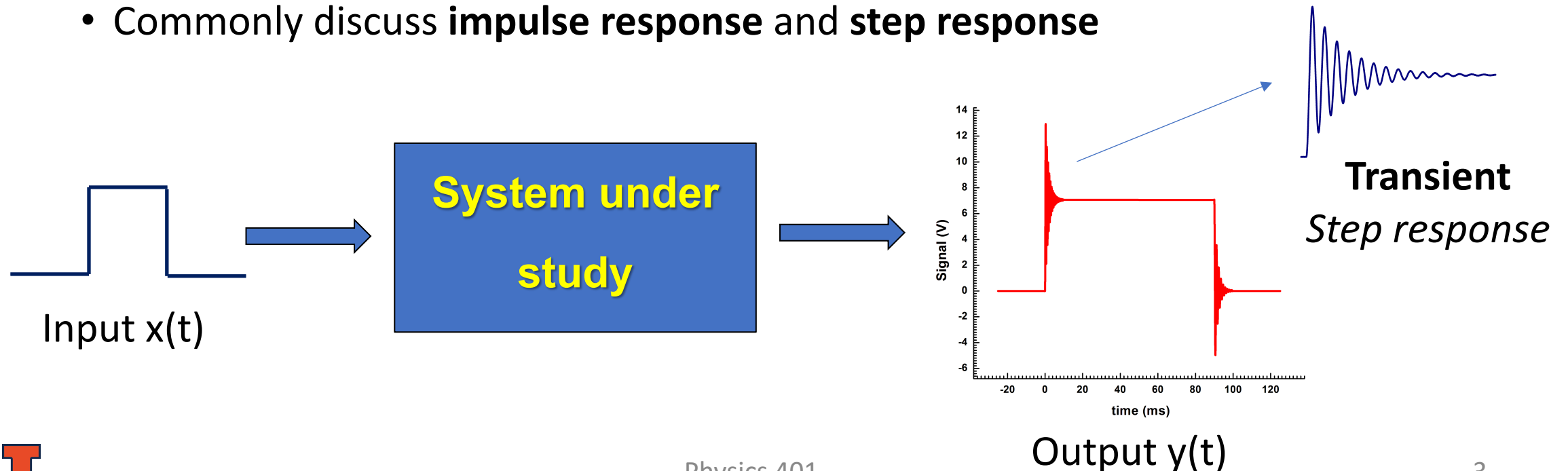


From Harmonic Oscillator to RLC Circuit

- A good reference LTI system is a **driven damped harmonic oscillator**
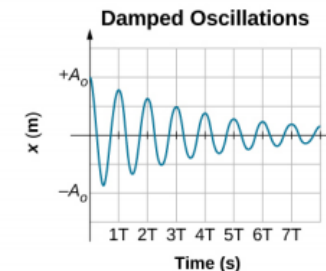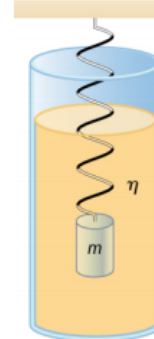
$$\text{Inertia } m \frac{d^2 x}{dt^2} + \text{Damping force } c \frac{dx}{dt} + \text{Restoring force } kx = \text{Driving force } F(t)$$



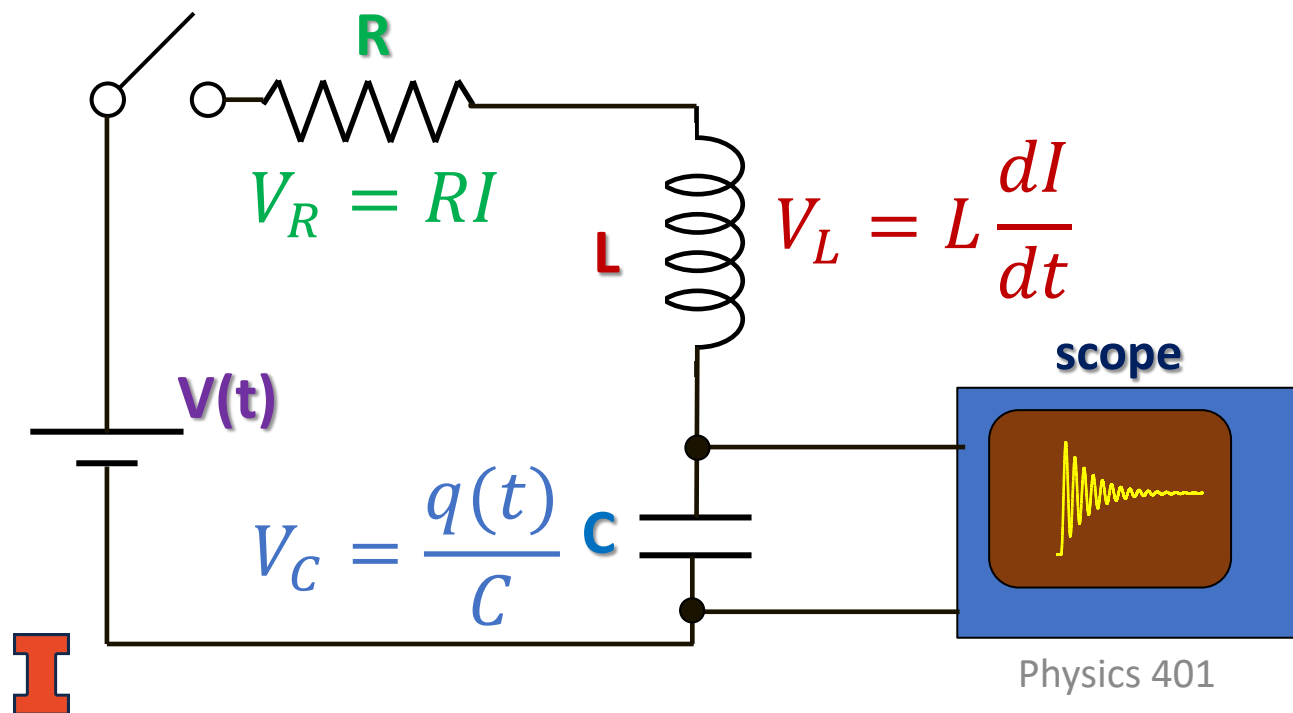- A useful implementation of this is an **RLC circuit**



$$V_R + V_L + V_C = V(t)$$



$$L \frac{d^2 q}{dt^2} + R \frac{dq}{dt} + \frac{1}{C} q = V(t)$$

Where...

- $q(t)$ is the charge on the capacitor
- The scope measures $V_C(t) = \frac{q(t)}{C}$

RLCs in the 401 Lab

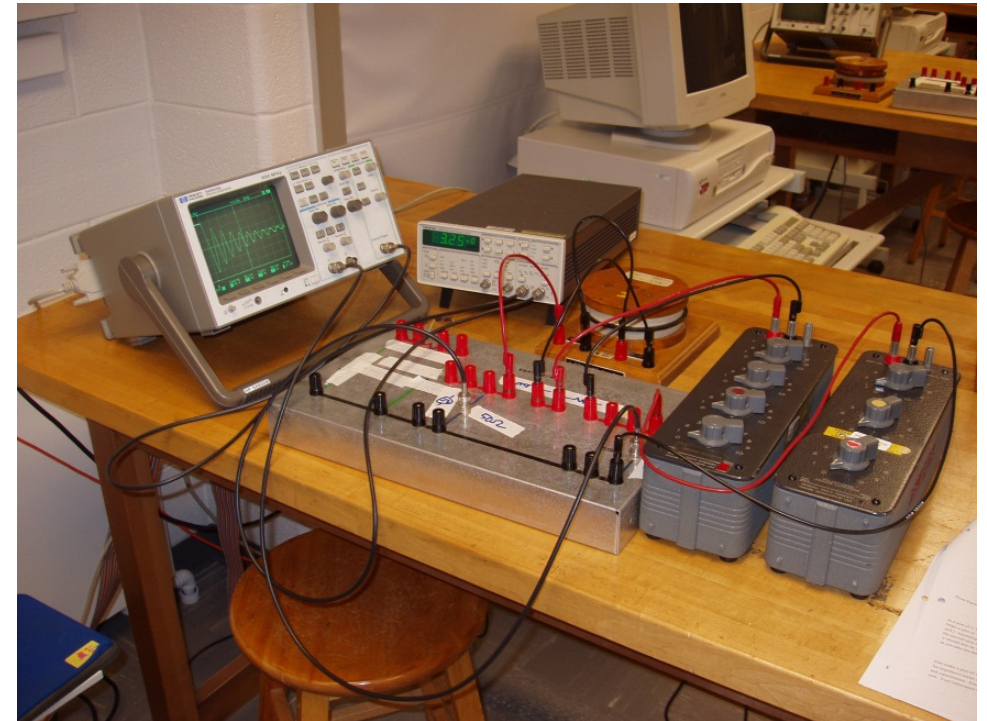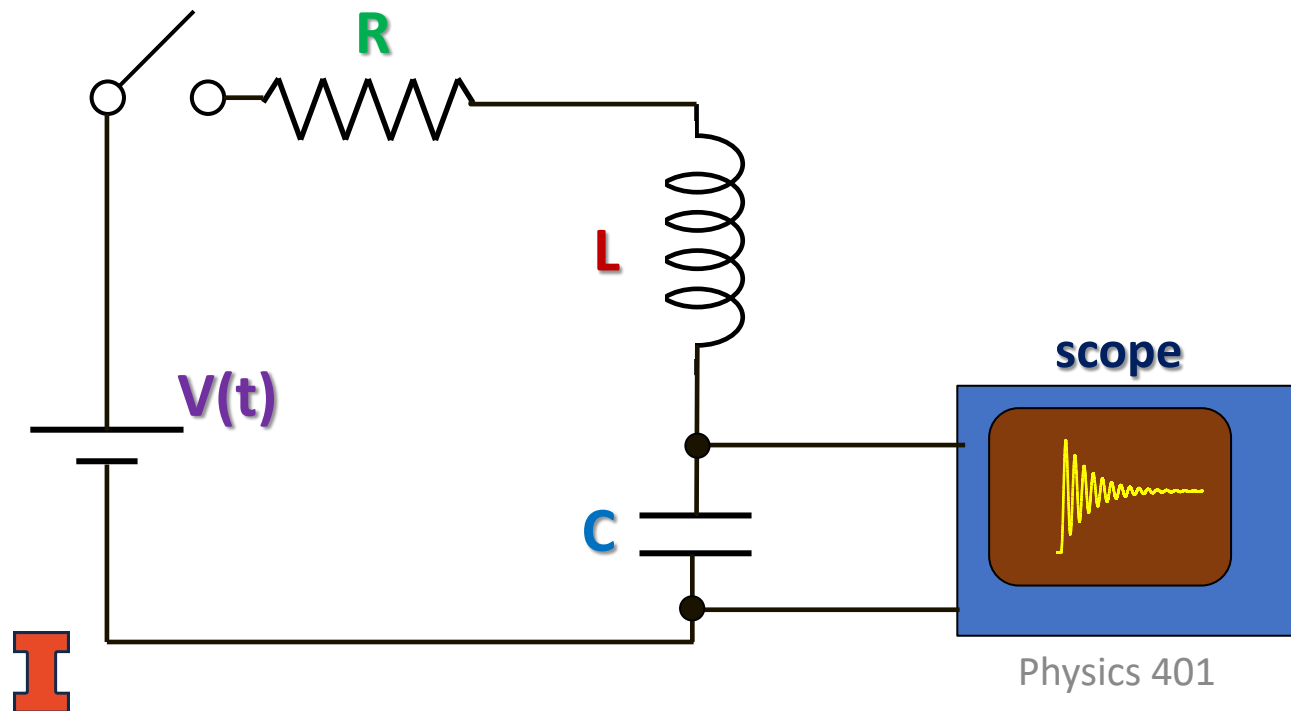- Voltage V V (Volt)
- Resistance R Ω (Ohm)
- Inductance L mH (10^{-3} Henry)
- Capacitance C μF (10^{-6} Farad)



$$L \frac{d^2 q}{dt^2} + R \frac{dq}{dt} + \frac{1}{C} q = V(t)$$

RLC Transients: Three Solutions


- What happens after input voltage drops to zero?
- Solutions have the form: $q(t) = Ae^{st}$
- This turns our diff. eq. into a quadratic equation:

$$s^2 + \left(\frac{R}{L}\right)s + \frac{1}{LC} = 0$$

- ... with solutions:

$$s_{\pm} = -\underbrace{\frac{R}{2L}}_a \pm \underbrace{\sqrt{\left(\frac{R}{2L}\right)^2 - \left(\frac{1}{LC}\right)}}_b \equiv -a \pm b$$

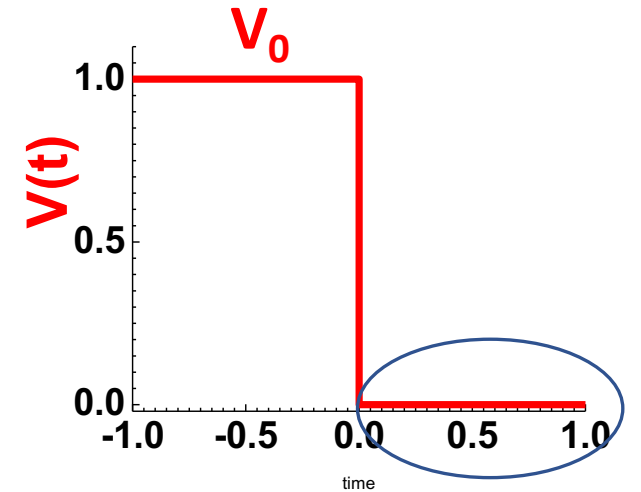- ... and boundary conditions $q(0) = CV_0$, $i(0) = \dot{q}(0) = 0$



$b^2 > 0$: Overdamped
 $b^2 = 0$: Critically damped
Exponential decay
 $b^2 < 0$: Underdamped
Oscillation / ringing

RLC Transients: Over-Damped Solutions

- $b^2 > 0$ ($R^2 > 4L/c$): aperiodic **exponential decay**

- Solutions have the form:

$$q(t) = e^{-at} (A_1 e^{bt} + A_2 e^{-bt})$$
$$i(t) = \dot{q}(t) = -ae^{-at} (A_1 e^{bt} + A_2 e^{-bt}) + be^{-at} (A_1 e^{bt} - A_2 e^{-bt})$$

- Applying boundary conditions $q(0) = CV_0$, $i(0) = \dot{q}(0) = 0$

$$q(t) = q(0)e^{-at} (\cosh bt + \sinh bt)$$

$$q(t) \xrightarrow[(a-b)t \gg 1]{} \frac{q(0)}{2} \left(1 + \frac{a}{b}\right) e^{-(a-b)t}$$

RLC Transients: Critical Damping

- $b^2=0$ ($R^2 = 4L/c$): fastest possible **exponential decay**

- Solutions have the form:

$$q(t) = e^{-at}(A_1 + A_2t)$$
$$i(t) = \dot{q}(t) = -ae^{-at}(A_1 + A_2t) + A_2e^{-at}$$

- Applying boundary conditions $q(0) = CV_0$, $i(0) = \dot{q}(0) = 0$

$$q(t) = q(0)e^{-at}(1 + at)$$
$$i(t) = -a^2q(0)te^{-at}$$


Ex: Real Data Analysis for Critical Damping

In this experiment:

- $R = 300 \text{ ohm}$
- $C = 1 \text{ } \mu\text{F}$
- $L = 33.43 \text{ mH}$

... plus practical reality:

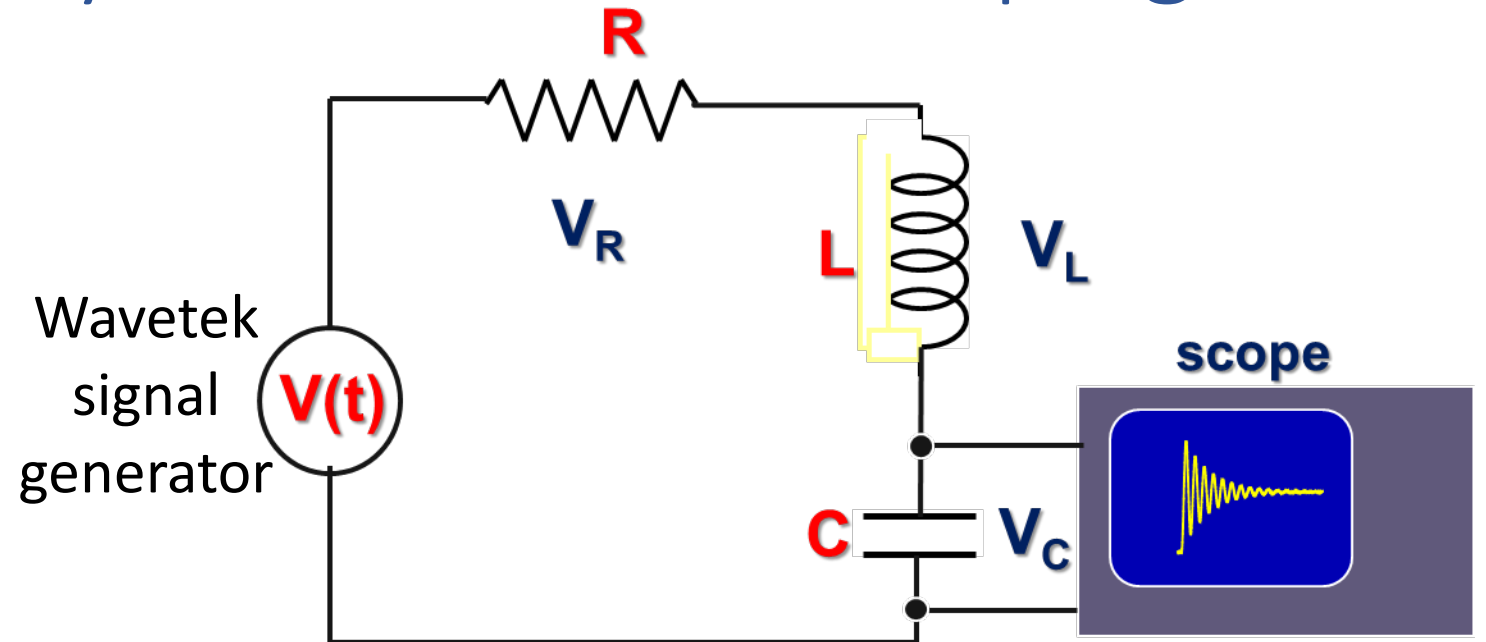
- Wavetek has 50 ohm output resistance
 - Inductor coil has 8.7 ohm measured R
- => Loop $R_{\text{tot}} = 358.7 \text{ ohm}$



Decay coefficient

$$a = \frac{R_{\text{tot}}}{2L} = \frac{358.7}{2 * 33.43 * 10^{-3}} \approx 5365 \text{ s}^{-1} \approx \frac{1}{0.2 \text{ ms}}$$

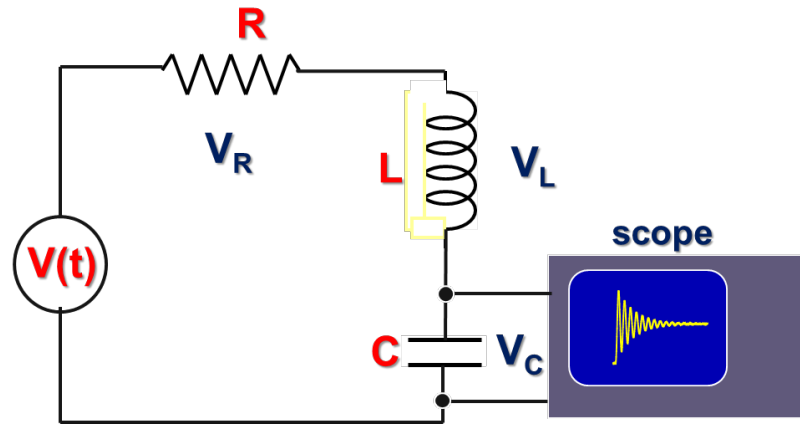Ex: Real Data Analysis for Critical Damping



Fitting function for measured $V_C \propto q$:

$$V_C = V_{c0}(1 + at)e^{-at}$$


Delay coefficient:

- Calculated: $a=5385 \text{ s}^{-1}$
- Fitted: $a= 5820 \text{ s}^{-1} (+8\%)$

Possible cause for discrepancy?

Perhaps slightly overdamped?

Calculated $b^2 = 2.99e7 - 2.90e7 > 0$

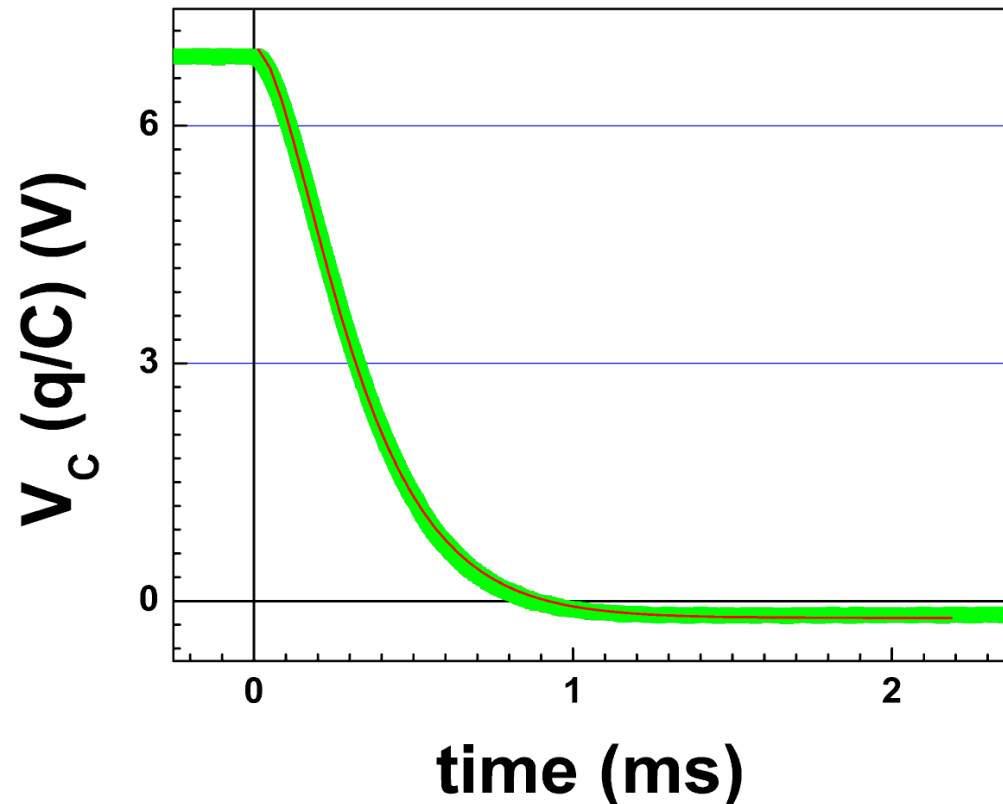

RLC Transients: Underdamped Case

- $b^2 < 0$ ($R^2 < 4L/c$): decaying oscillation

- Solutions (*see write-up!*):

$$q(t) = q(0)e^{-at} \sqrt{1 - \frac{a^2}{\omega^2}} \sin(\omega t + \varphi)$$
$$i(t) = q(0)e^{-at} \left(\frac{a^2 - \omega^2}{\omega} \right) \sin \omega t$$
$$a = \frac{R}{2L}; \quad \omega = 2\pi f = \sqrt{\left(\frac{1}{LC}\right) - \left(\frac{R}{2L}\right)^2}$$

Quantifying Damping

General idea: How many *oscillation periods* ($T \equiv 1/f$) does it take for the *oscillation amplitude* to decay “substantially”?


- **Log-decrement** can be defined as:

$$\delta \equiv \ln \left(\frac{q(t_{max})}{q(t_{max} + T)} \right) = \ln \left(\frac{e^{-at_{max}}}{e^{-a(t_{max}+T)}} \right) = aT$$



- More commonly, define **Quality Factor**

$$Q \equiv 2\pi \frac{E}{\Delta E} = \frac{\pi}{\delta}$$

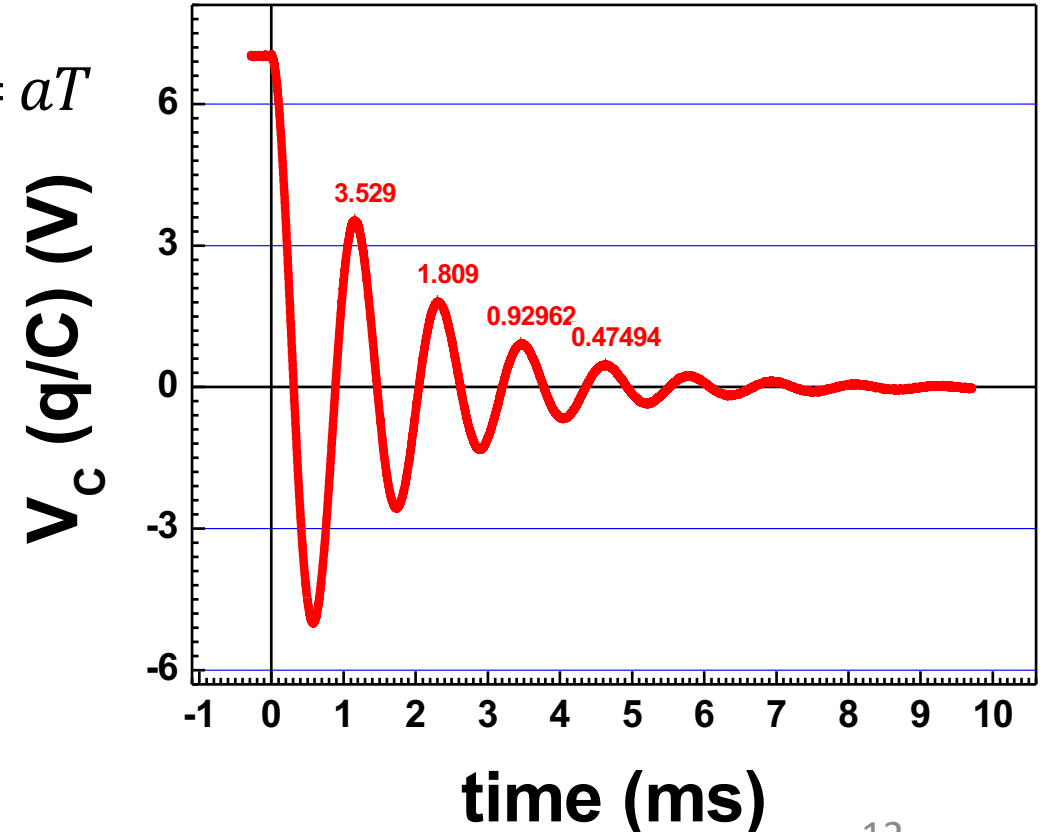- From this plot, $\delta \approx 0.67$, $Q \approx 4.7$



Analysis Using Origin

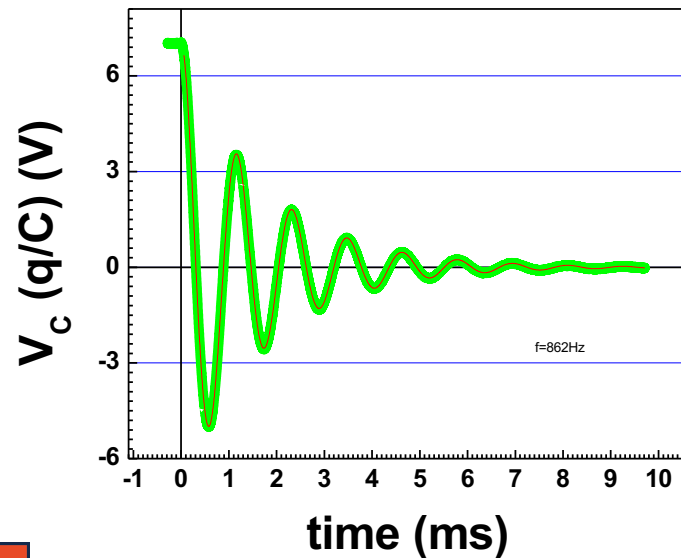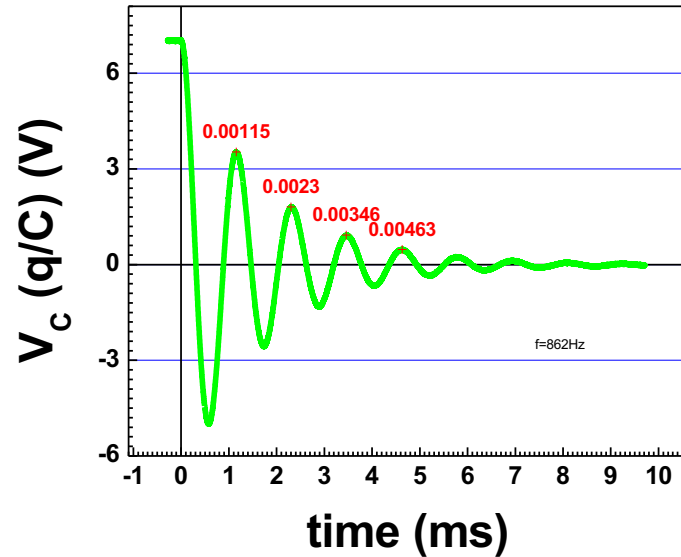


Keep in mind:

- Fitting multi-parameter **linear** models to data is generally pretty robust
- Fitting **non-linear** models to data is all about making **good initial guesses**

Practical procedure:

1. Identify peaks
2. Fit “envelope”
3. Perform nonlinear fit


Analysis Using Origin: Identify Peaks

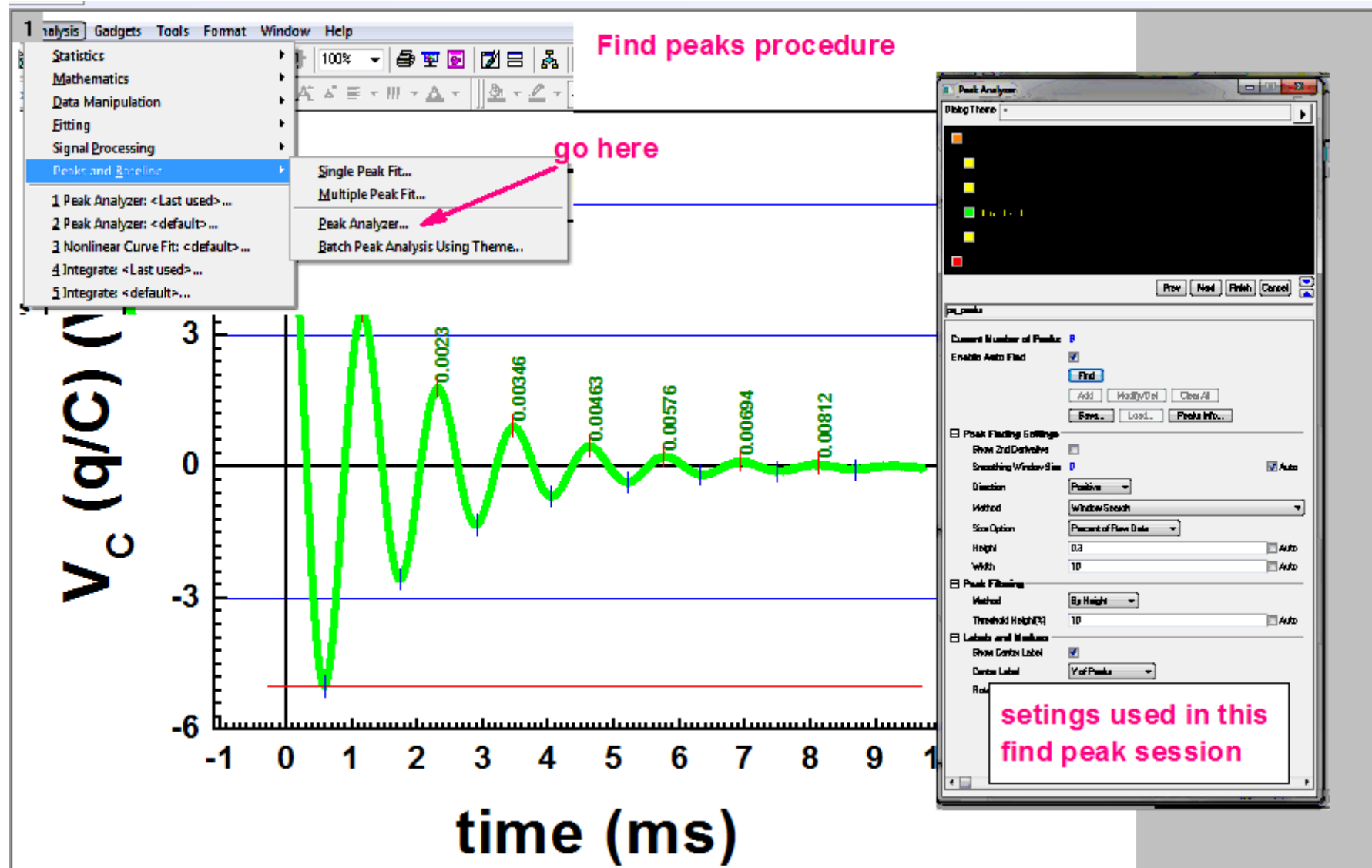


Analysis Using Origin: Fit Decay Envelope

Points found using "Find Peaks"

Time-domain trace

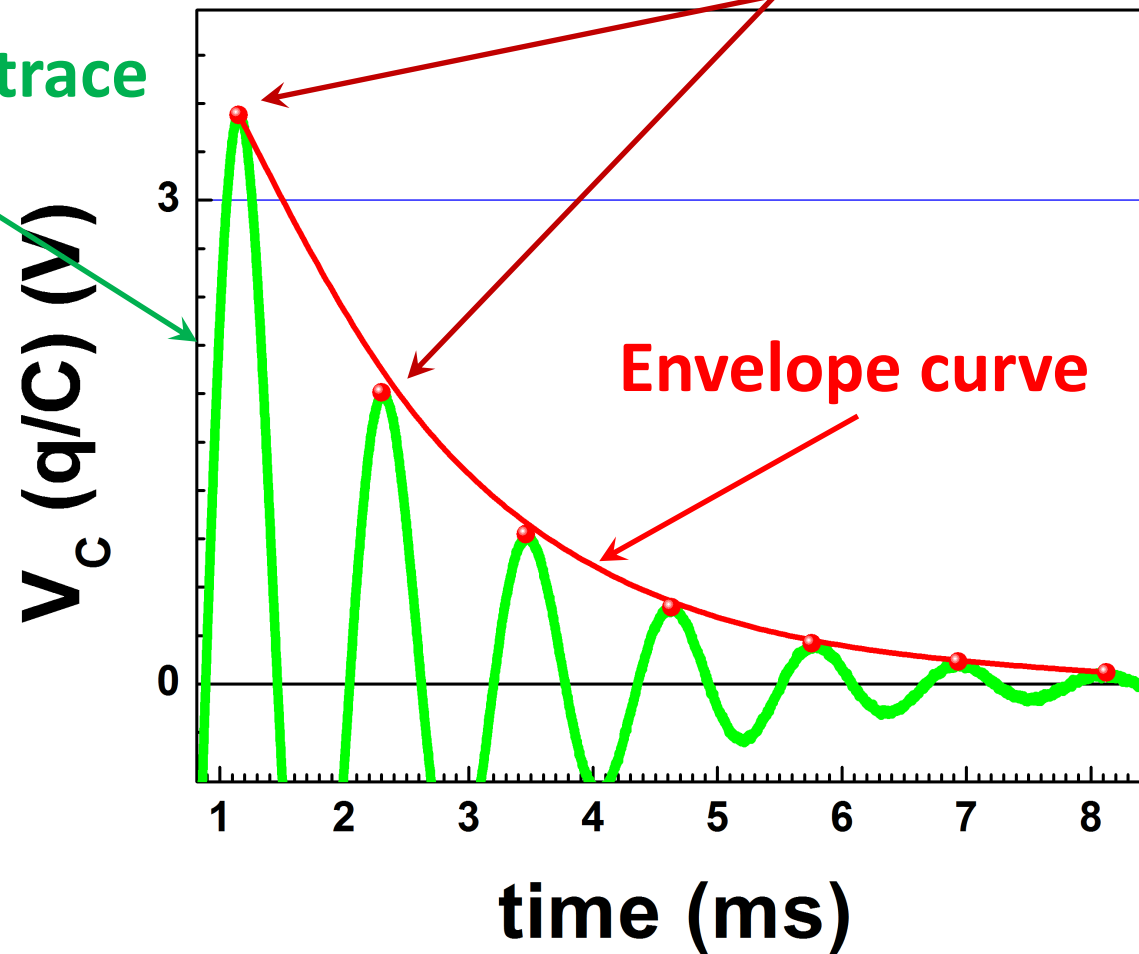

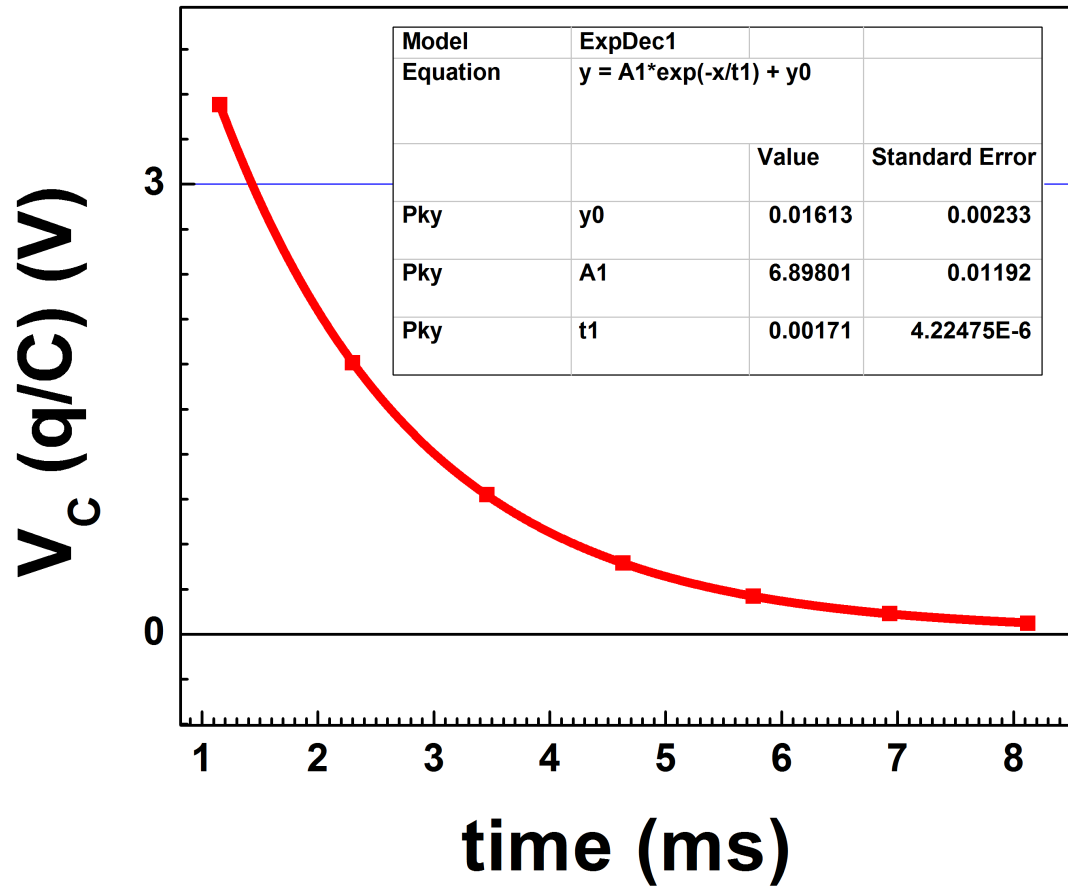Analysis Using Origin: Fit Decay Envelope



Dialog Theme: *

Settings | Code | Parameters | Bounds

Function Selection

Data Selection

Fitted Curves

Find X/Y

Advanced

Output

Category: Exponential

Function: ExpDec1

Description: Exponential Decay 1


File Name(.FDF): C:\Program Files\OriginLab\Origin\fitfunc\expdec1.fdf

Fit Done Cancel

Residual Formula Sample Curve Messages Function File Hints

$$y = y_0 + Ae^{-x/t}$$

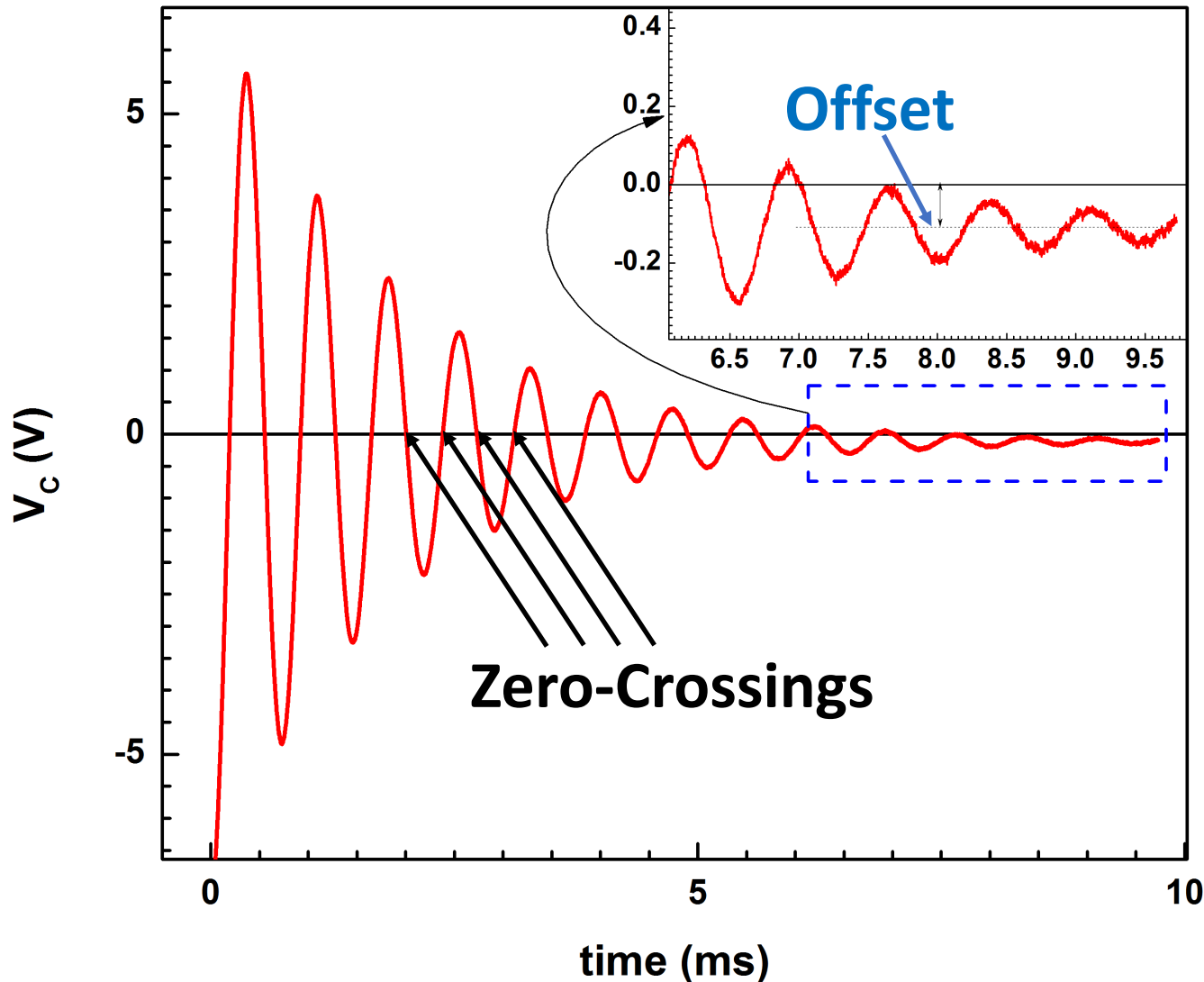Analysis Using Origin: Periods and Offsets



$$q(t) = Ae^{-at} \sin(\omega t + \varphi) + \boxed{K}$$

Offset

- Manually evaluate period of the oscillations
- Limited accuracy!
- Answer can be biased by **DC offset**

Analysis Using Origin: Non-Linear Fit

$$q(t) = Ae^{-at} \sin(\omega t + \varphi)$$

$$U_C(t) = \frac{q(t)}{C}$$

- Use Origin standard function
 - Category: Waveform
 - Function: SineDamp

- Fit parameters: y_0 , A , t_0 , x_c , w


- From fit we can obtain:

$$a = \frac{1}{t_0}; \quad T = \frac{1}{f} = 2w$$


The screenshot shows the Origin software interface for non-linear fitting. The 'NLFit (SineDamp)' dialog box is open, with the 'Function Selection' tab selected. The 'Category' is set to 'Waveform' and the 'Function' is 'SineDamp'. The 'Description' is 'sine damp function' and the 'File Name(.FDF)' is 'C:\Program Files\OriginLab\Origin\fitfunc\sinedamp.fdf'. The 'Formula' tab at the bottom displays the equation: $y = y_0 + Ae^{-\frac{x}{t_0}} \sin\left(\pi \frac{x - x_c}{w}\right)$. The y_0 term is highlighted with a blue box.

Offset

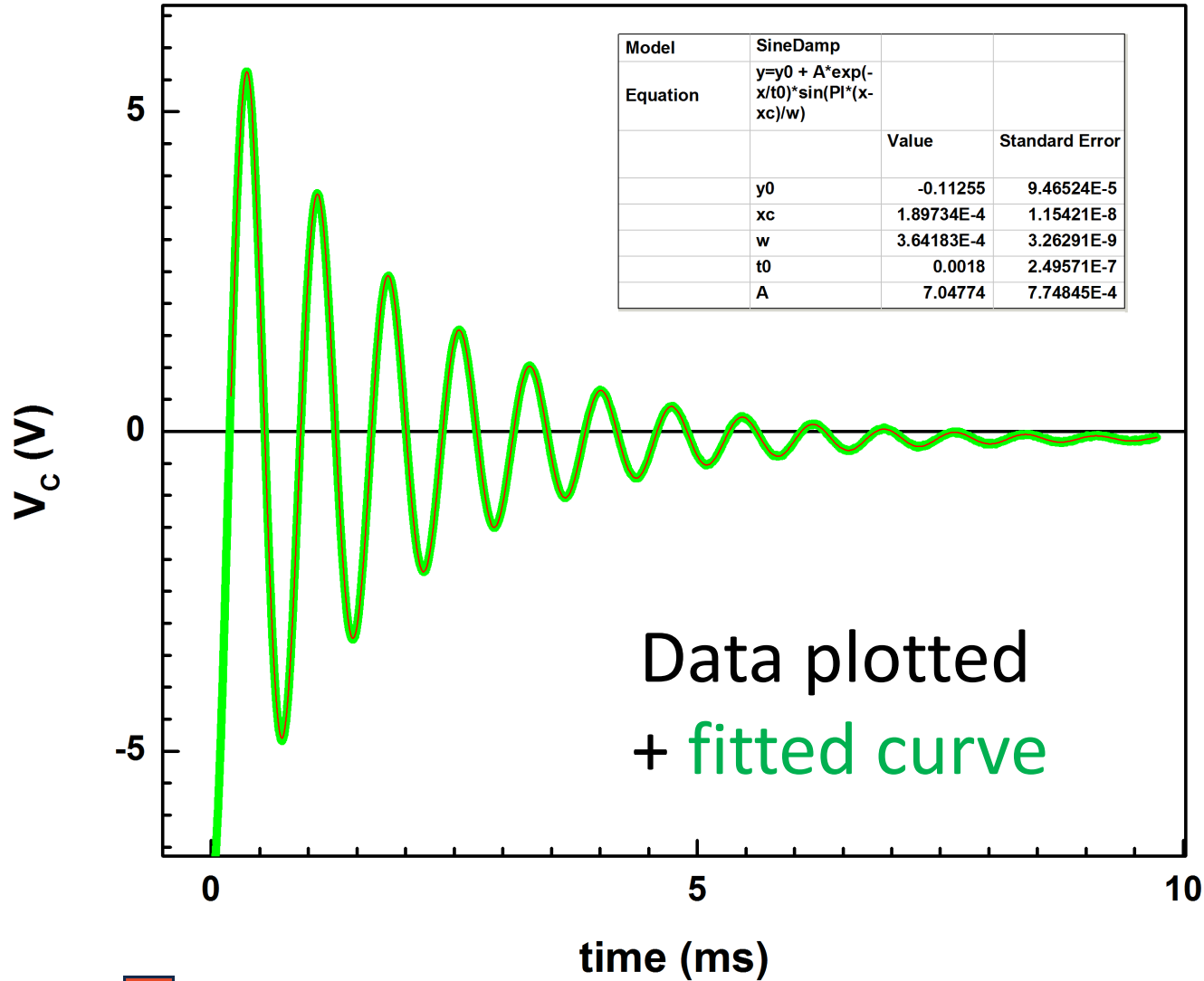Analysis Using Origin: Evaluating the Fit



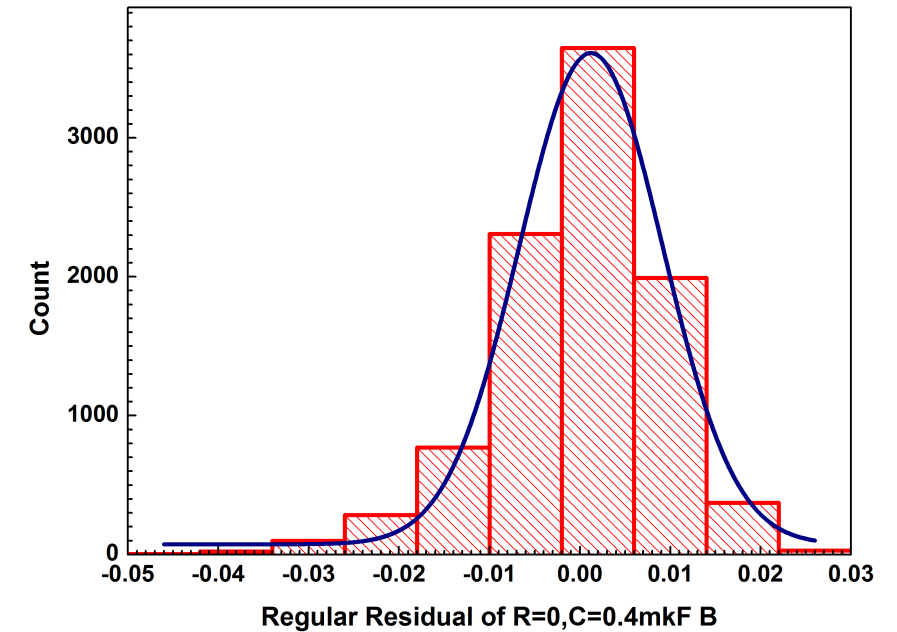
$$q(t) = Ae^{-at} \sin(\omega t + \varphi)$$



Residuals (data – fit): metric for quality of fit

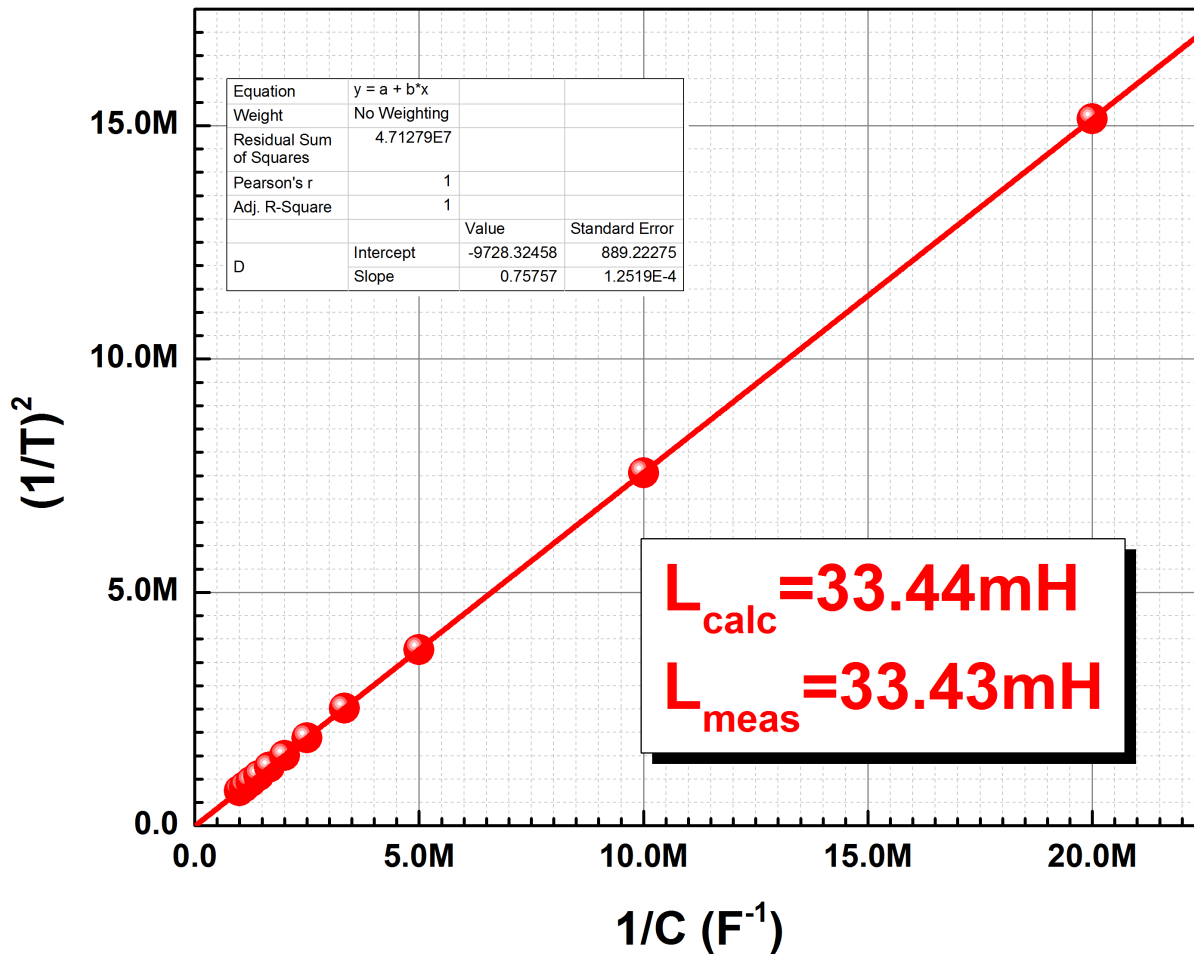Analysis Using Origin: Interpreting Results



$$q(t) = Ae^{-at} \sin(\omega t + \varphi)$$


$$f^2 = \left(\frac{1}{T}\right)^2 = \left(\frac{1}{2\pi}\right)^2 \left(\left(\frac{1}{LC}\right) - \left(\frac{R}{2L}\right)^2 \right)$$

Final Results


Not the fit itself, but constraints on the physical model parameters!

Foreshadowing: Resonance in RLC Circuits

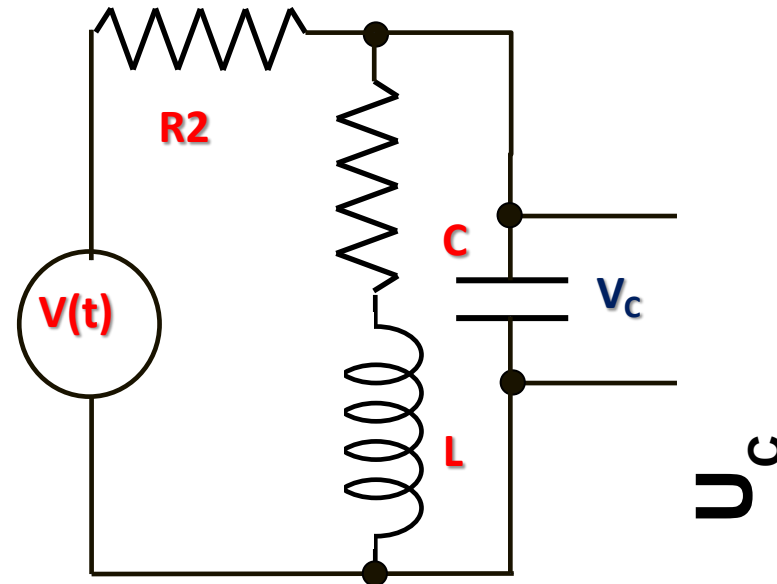
Parallel config:
Energy can
“slosh” from C
to L and back





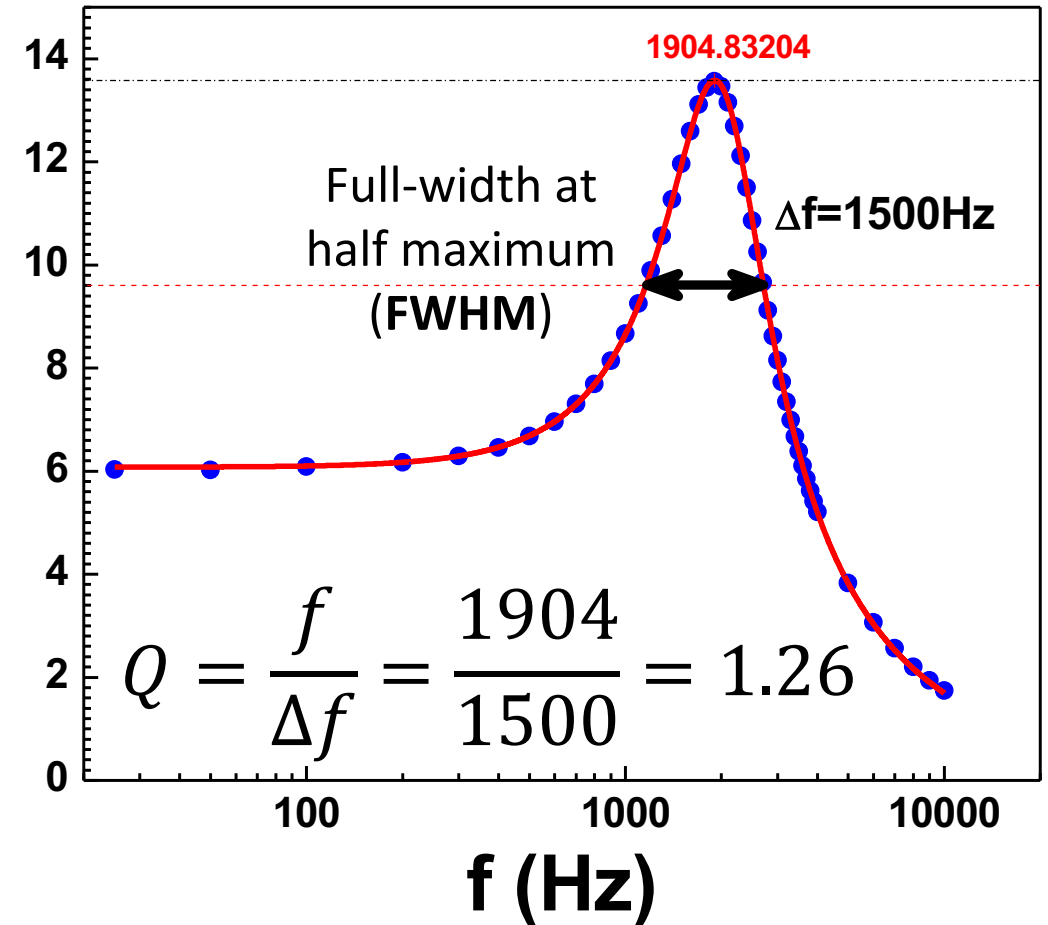
Resonance: Amplified response when a system is driven at (or near) one of its “natural” frequencies



Origin Templates for This Week's Lab

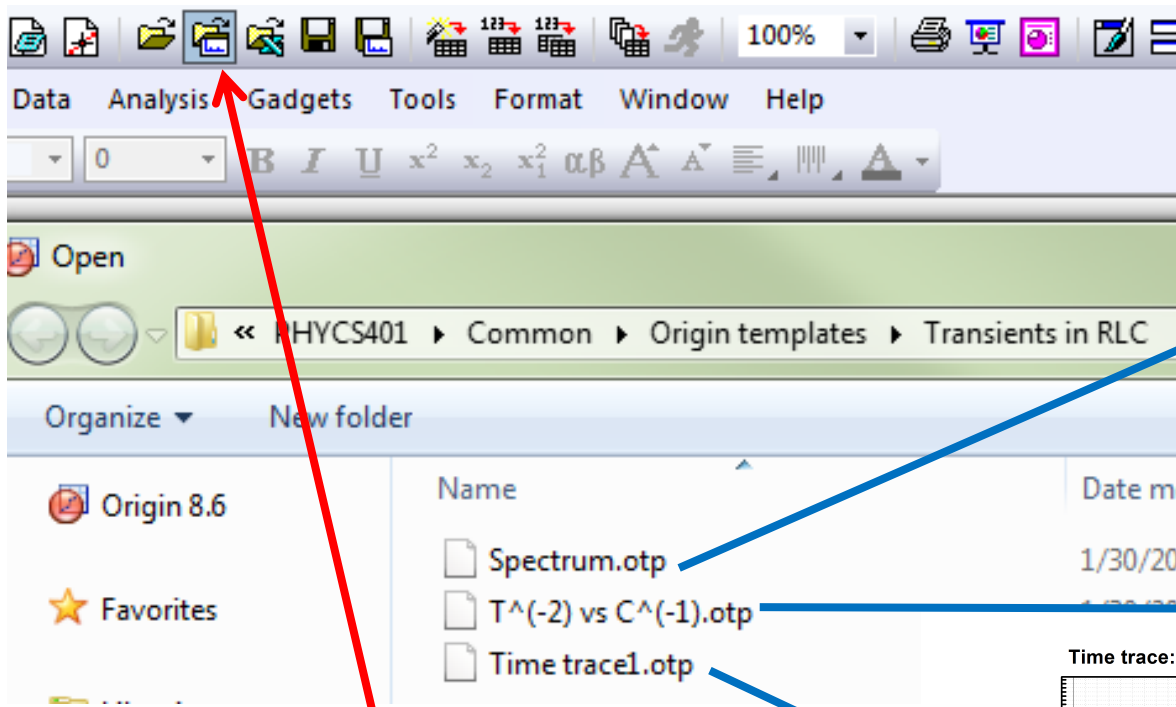

Open Template button

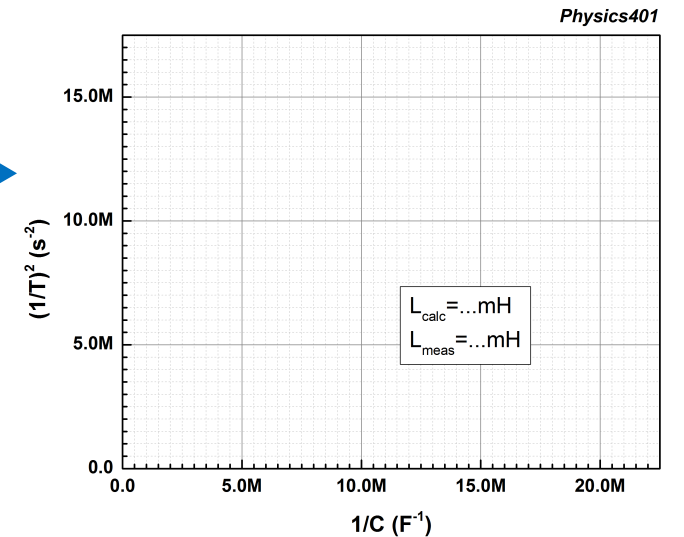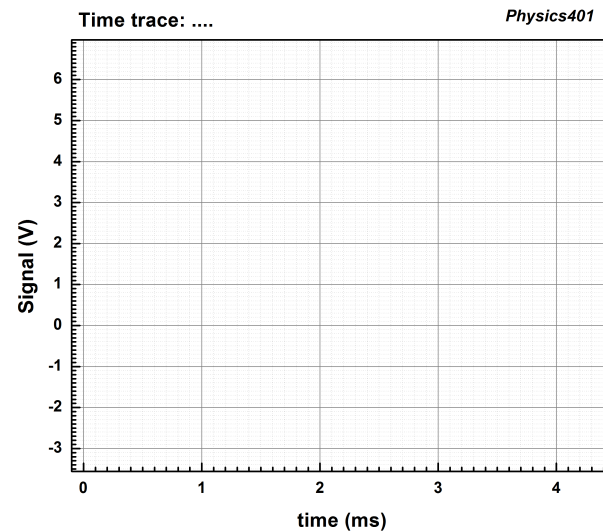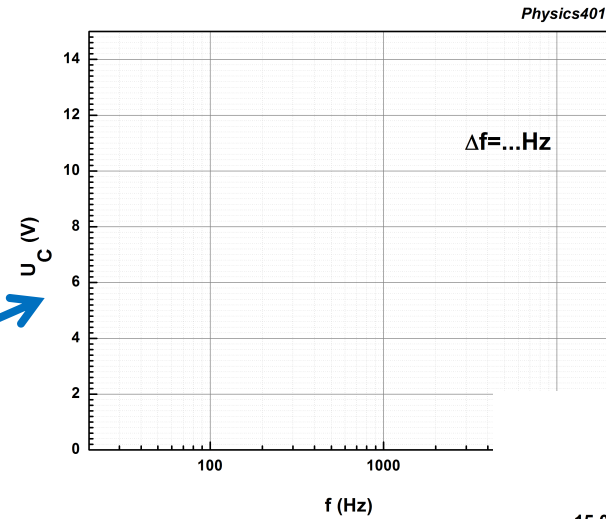


Origin Manuals



Working with Origin 8.6.

Step1. Importing data

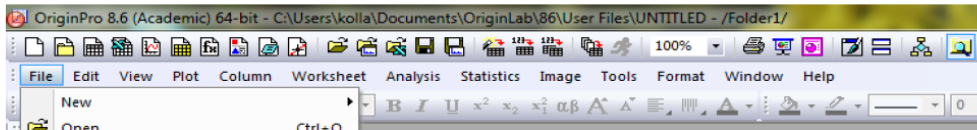

Don't forget about Origin help!

Video tutorial library on company website

Short, simple manual covering only basic operations with Origin
(linked from [P401 webpage](#))



Company	Products	Support	Solutions	Purchase	D
Help Center		SUPPORT : VIDEO TUTORIALS			
Video Tutorials		Video Tutorials			
User Forum					