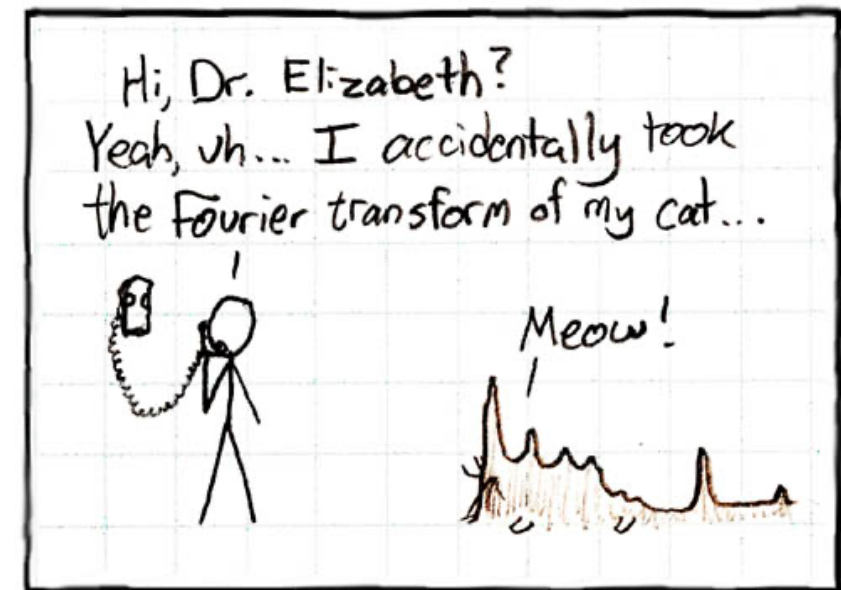


Frequency Domain Analysis of Linear Circuits using Synchronous Detection




Professor Jeff Filippini
Physics 401
Spring 2020




Key Topics of this Lab


1. The Fourier Transform and its Uses

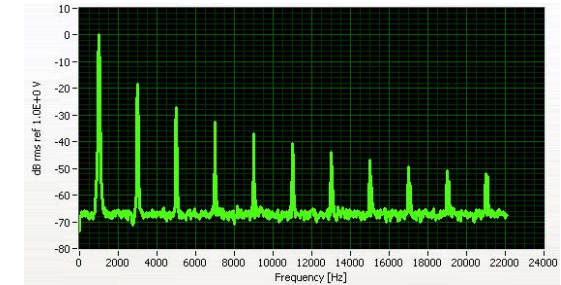

2. Lock-In Amplifiers

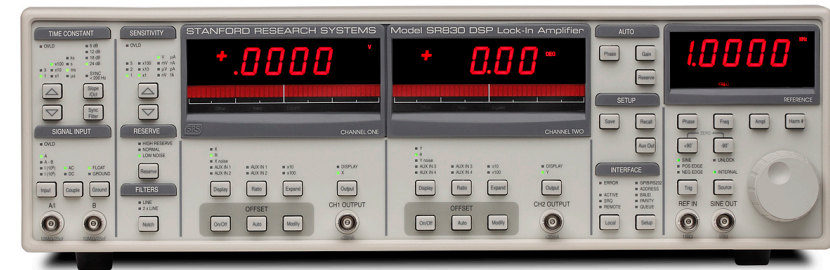


3. Data Analysis

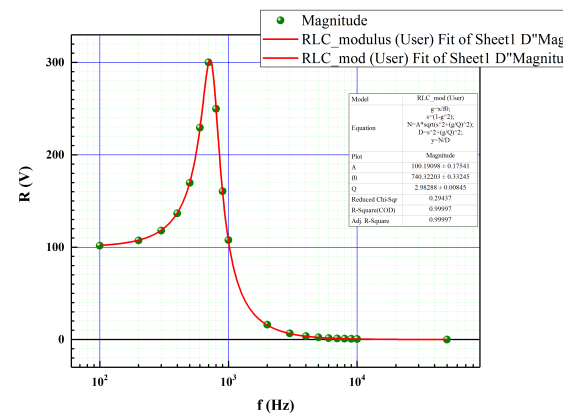


Key Topics of this Lab


1. The Fourier Transform and its Uses

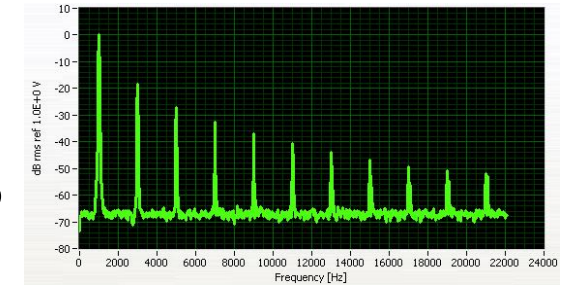

2. Lock-In Amplifiers

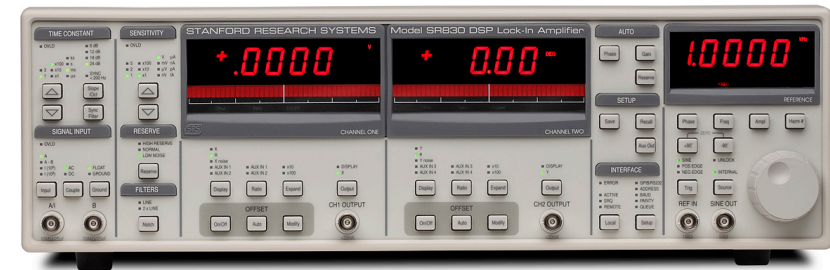

3. Data Analysis

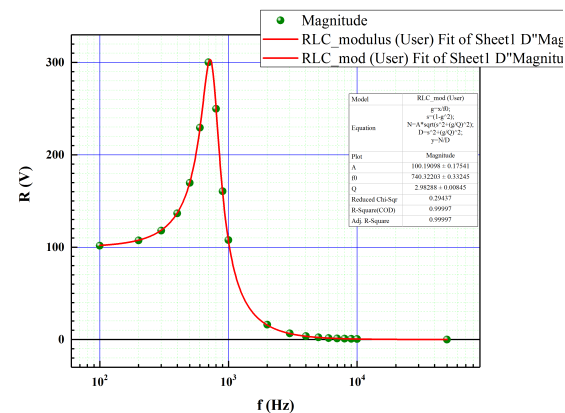


Fourier Series

Circa 1807, while struggling to solve the heat equation, Jean Baptiste Joseph Fourier described how any* real-valued waveform can be described uniquely** as a sum of sinusoidal waves ([web visualization](#))



*Jean Baptiste Joseph
Fourier*

I (1768 – 1830)

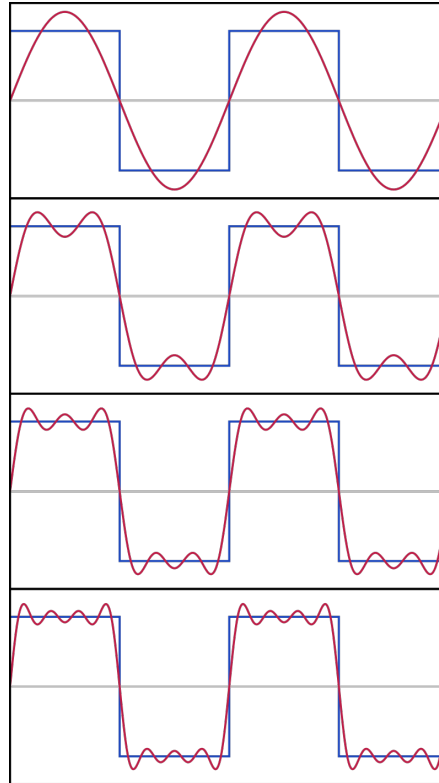

$$A \sin \omega t \quad (\omega \equiv 2\pi f)$$

$$+ \frac{A}{3} \sin 3\omega t$$

$$+ \frac{A}{5} \sin 5\omega t$$

$$+ \frac{A}{7} \sin 7\omega t + \dots$$

* square-integrable, periodic, ...

** *sin, cos* a **basis** for function space 4

Fourier Transform

Extend this scheme elegantly to any* complex function by:

1. Replacing sin and cos with complex exponentials ($e^{i\omega t} = \cos \omega t + i \sin \omega t$)
2. Allow for complex coefficients (incorporates phases)
3. Replacing sums with integrals




The Discrete Fourier Transform

Suppose that our data is a **regularly-sampled** time series, $h_n \equiv h(t_n) = h(n \Delta t)$. Then the right analog of the FT is the Discrete Fourier Transform:


$$H_k = H(f_k) = H(k \delta f) = \sum_{n=0}^{N-1} h_n e^{-2\pi i n k / N} \quad \Delta f = \frac{1}{N \Delta t}$$

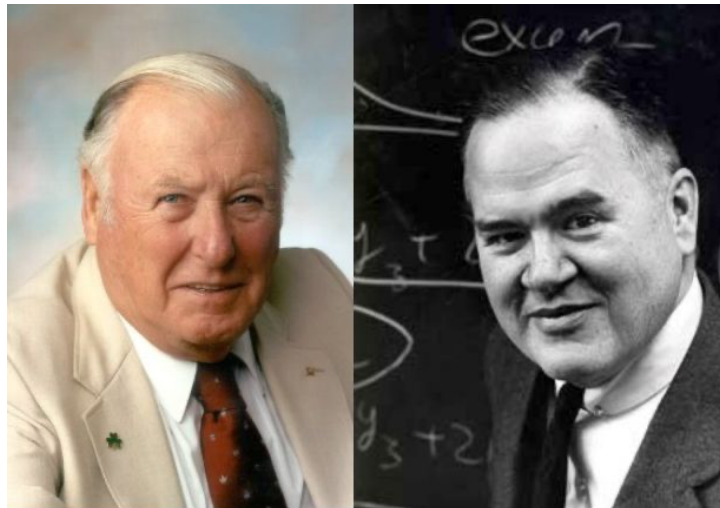In 1965 J.W. Cooley and J. Tukey* showed how to compute this extremely efficiently if N is a power of 2 (or at least has few prime factors). This is the **Fast Fourier Transform (FFT)**, and is approx. the only Fourier transform anyone computes




James William Cooley
(1926-)

John Wilder Tukey
(1915-2000)

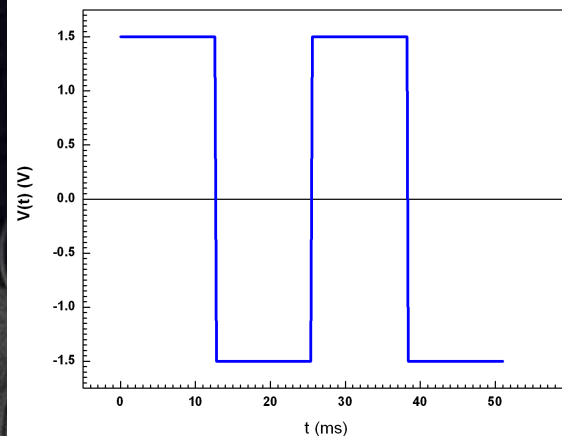

Time domain

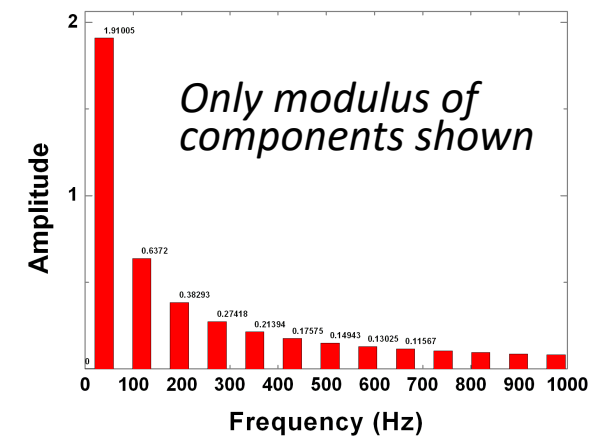


Frequency domain



Fourier Analysis of Signals and Systems

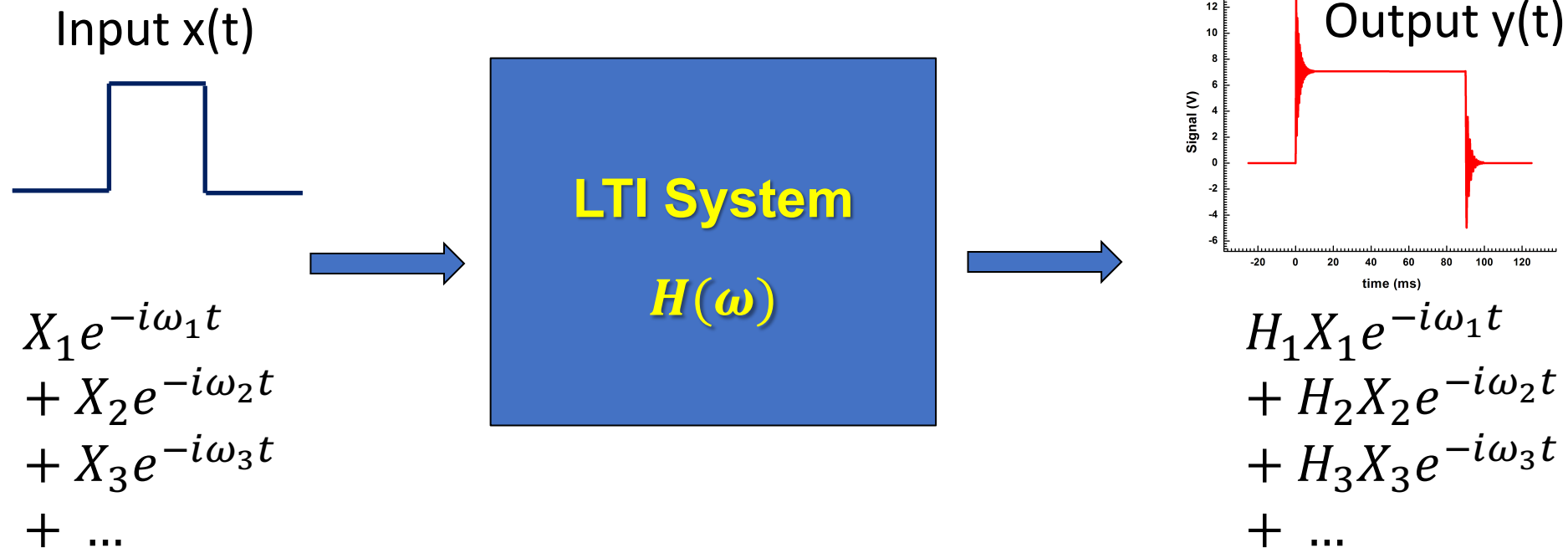
Fourier analysis is very useful for working with Linear Time-Invariant (LTI) systems, because differential equations become algebraic ones



The (complex) **transfer function $H(f)$** fully describes the response of an LTI system, and can be applied (in Fourier space!) to any desired input.

Use for diff. eq., filters, control systems, signal processing, circuits (complex impedance), ...

Frequency Domain Spectroscopy

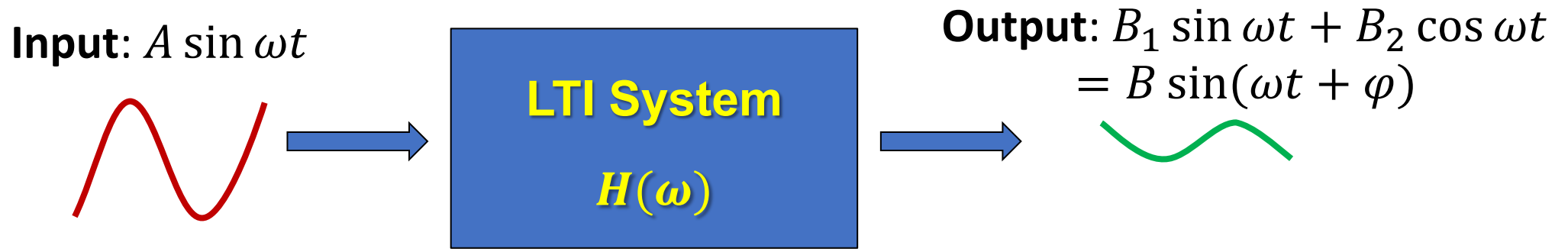


Apply a **sine wave input** to the system under study and measure the response.

For a **linear** system the response will be at the same frequency, but possibly amplified/attenuated (B/A) and phase-shifted (φ).


Vary the driving frequency to measure the **transfer function** $H(\omega)$ directly

Key Topics of this Lab


1. The Fourier Transform and its Uses

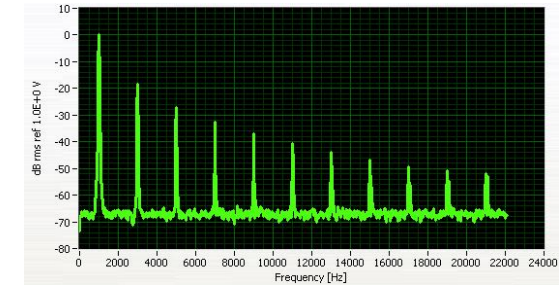

2. Lock-In Amplifiers

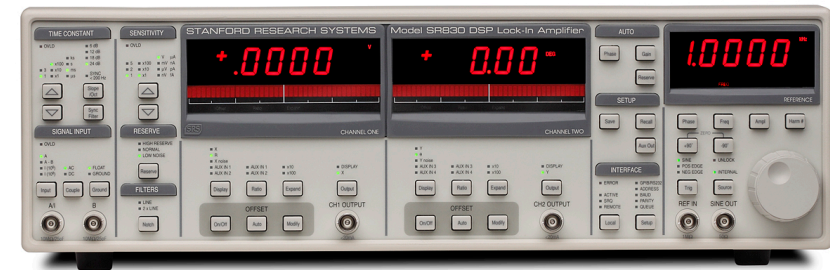

3. Data Analysis

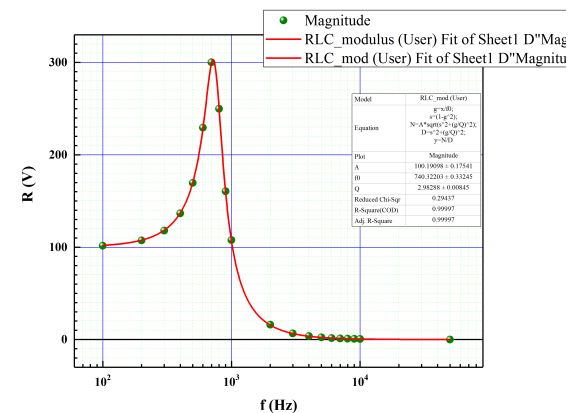


The Lock-In Amplifier

Immensely powerful and widely-applicable tool, implemented in hardware or (increasingly) digital signal processing




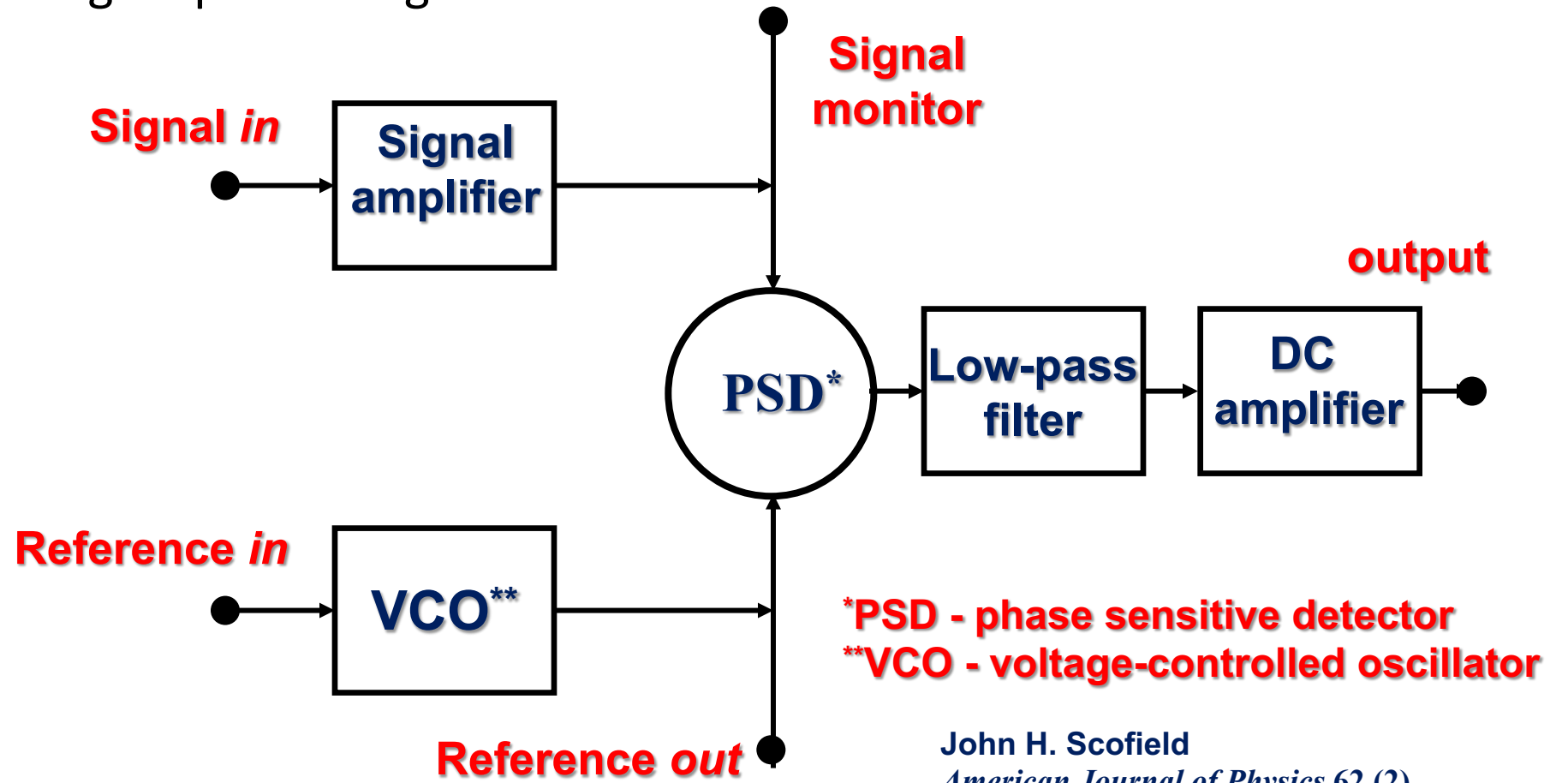Modern lock-in amps credited to **Bob Dicke** (1916-1997) Princeton astronomer




John H. Scofield
American Journal of Physics 62 (2)
129-133 (Feb. 1994).

The Lock-In Amplifier: How It Works

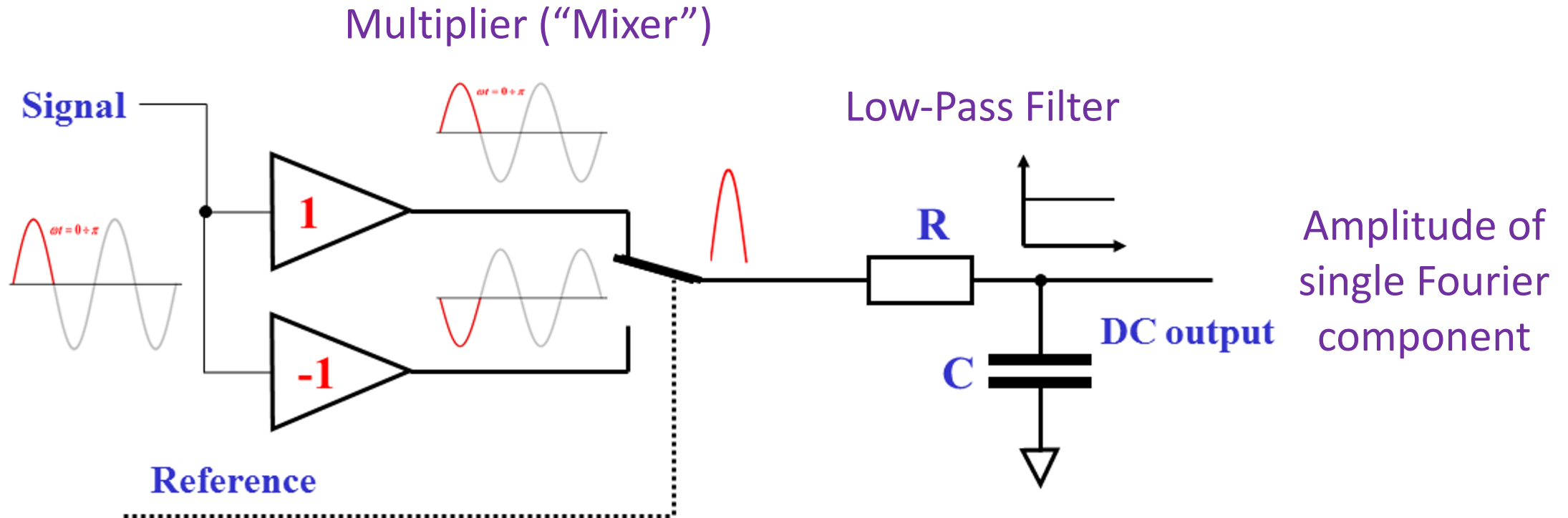


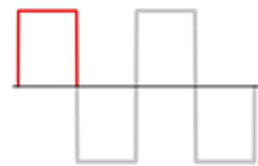Similar to **homodyne demodulation** in AM radio receivers





The DC output signal is the magnitude of the **product** of the input and reference signals. AC components of the output signal are filtered out by the **low-pass filter**, with time constant τ (*here $\tau=RC$*)

The Lock-In Amplifier: How It Works

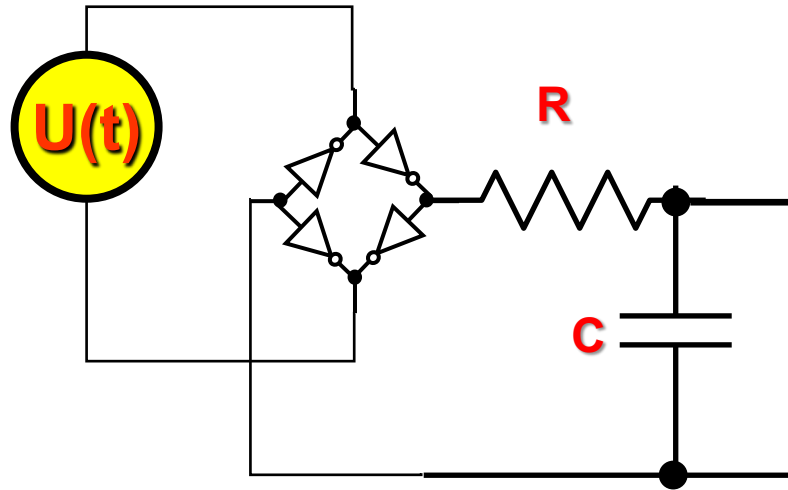

Simple implementation


1

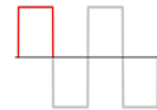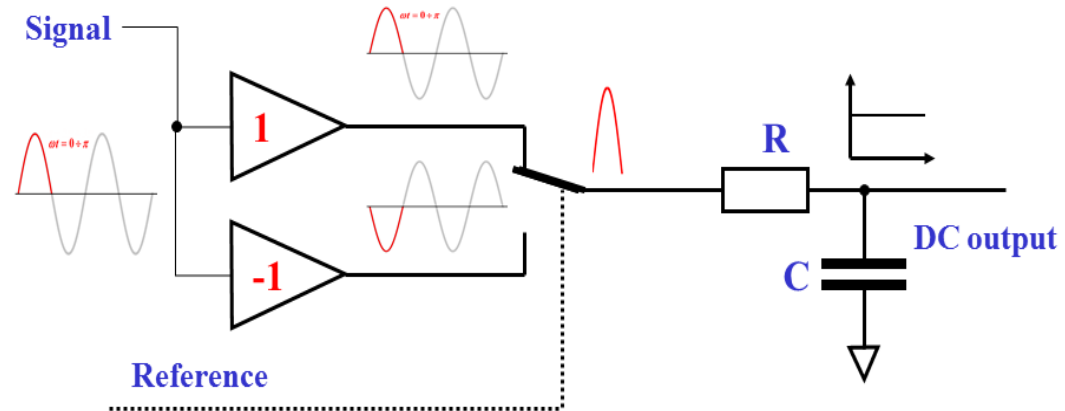

2

Why Synchronous Detection?


“Clean” sine wave – no noise

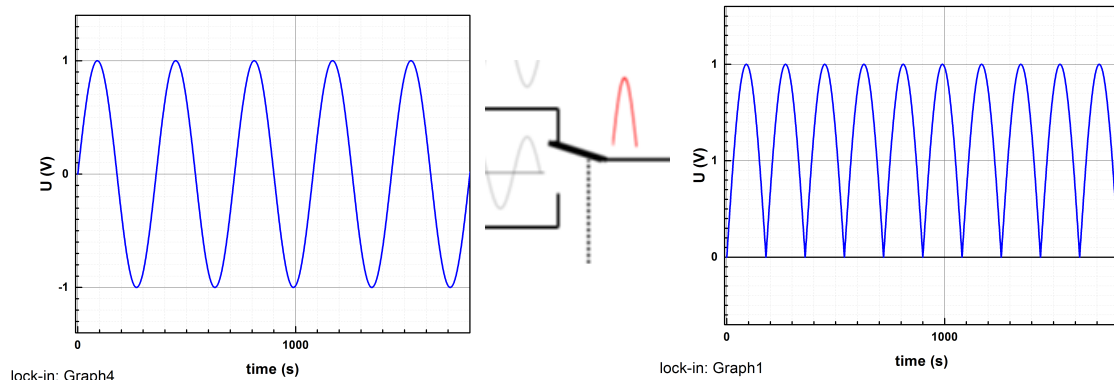

$$U_{DC} = 0.63643 \text{ V}$$

=

“Noisy” sine wave

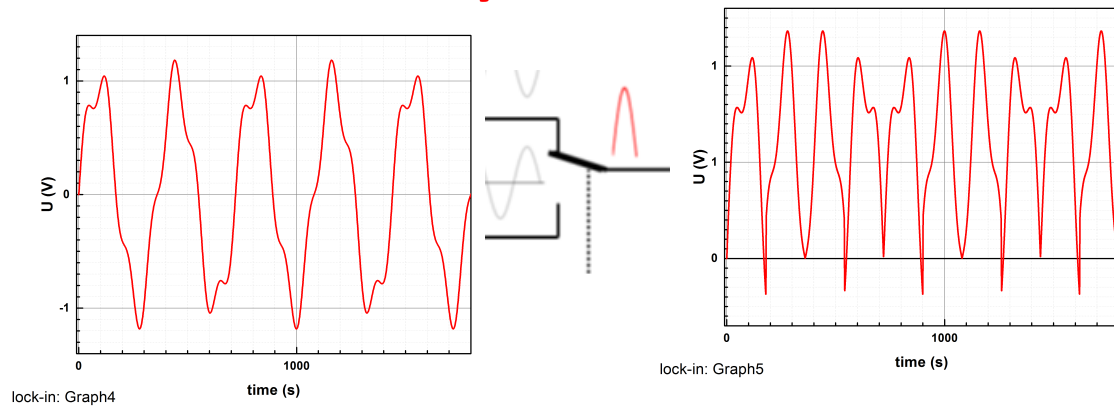

$$U_{DC} = 0.63643 \text{ V}$$


Because sine wave of different frequencies are **orthogonal**

$$\int_0^{2\pi} \sin nx \sin mx dx = \delta_{nm}$$


lock-ins can reject contamination extremely well

How well depends on integration time constant τ

Why Synchronous Detection?

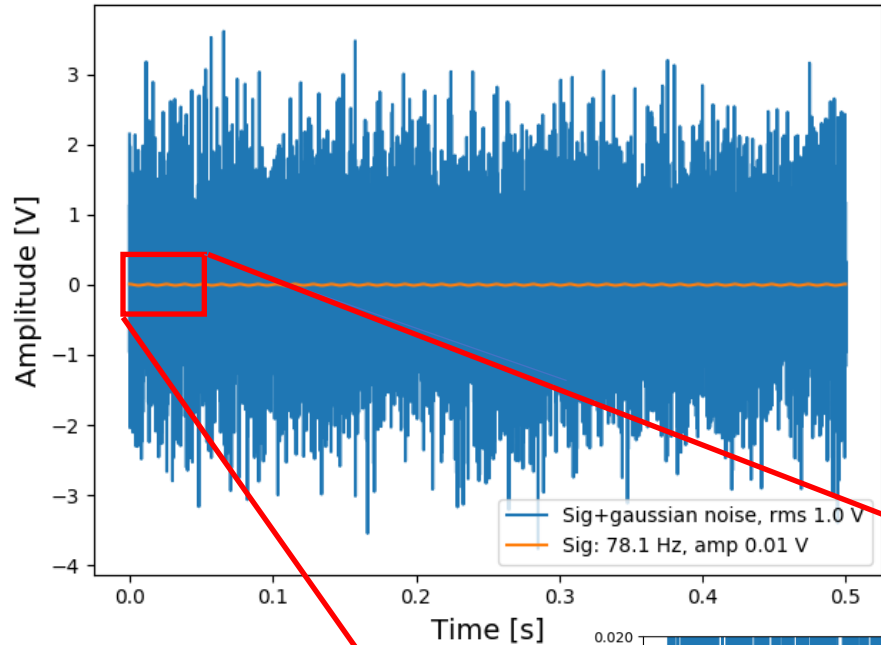


0.5s integration time

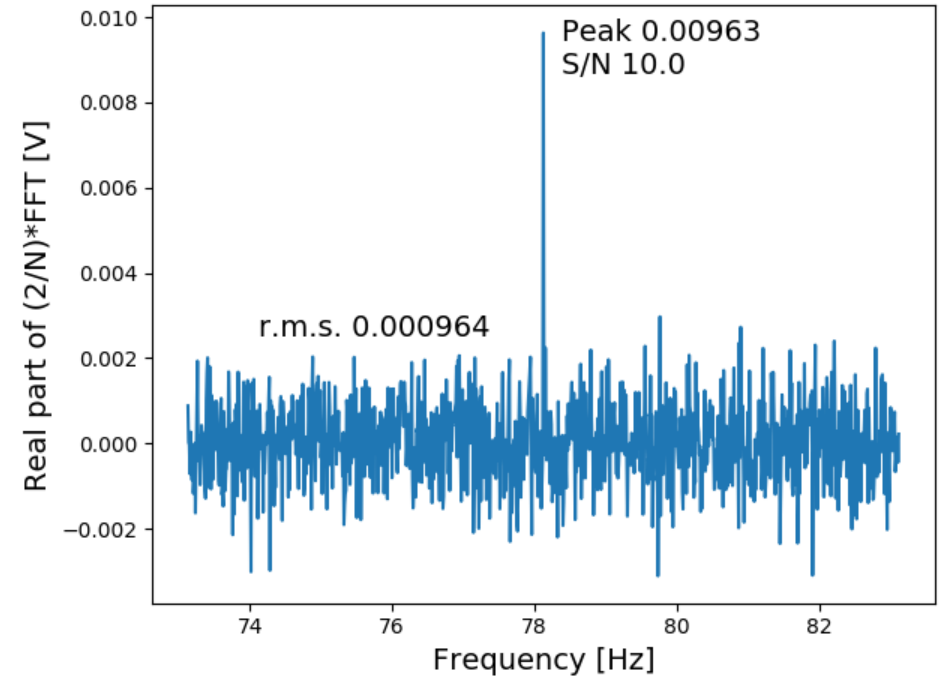

Signal amplitude
 $1/100^{\text{th}}$ of noise rms

20 kHz sampling

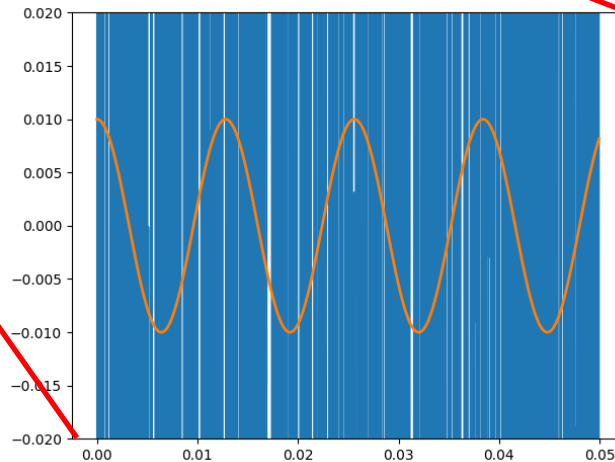


Moral: Synchronous detection can identify faint signals buried in overwhelming noise.

Precision measurements often take this form!




Lock-In Amplifier: Phase Shifts

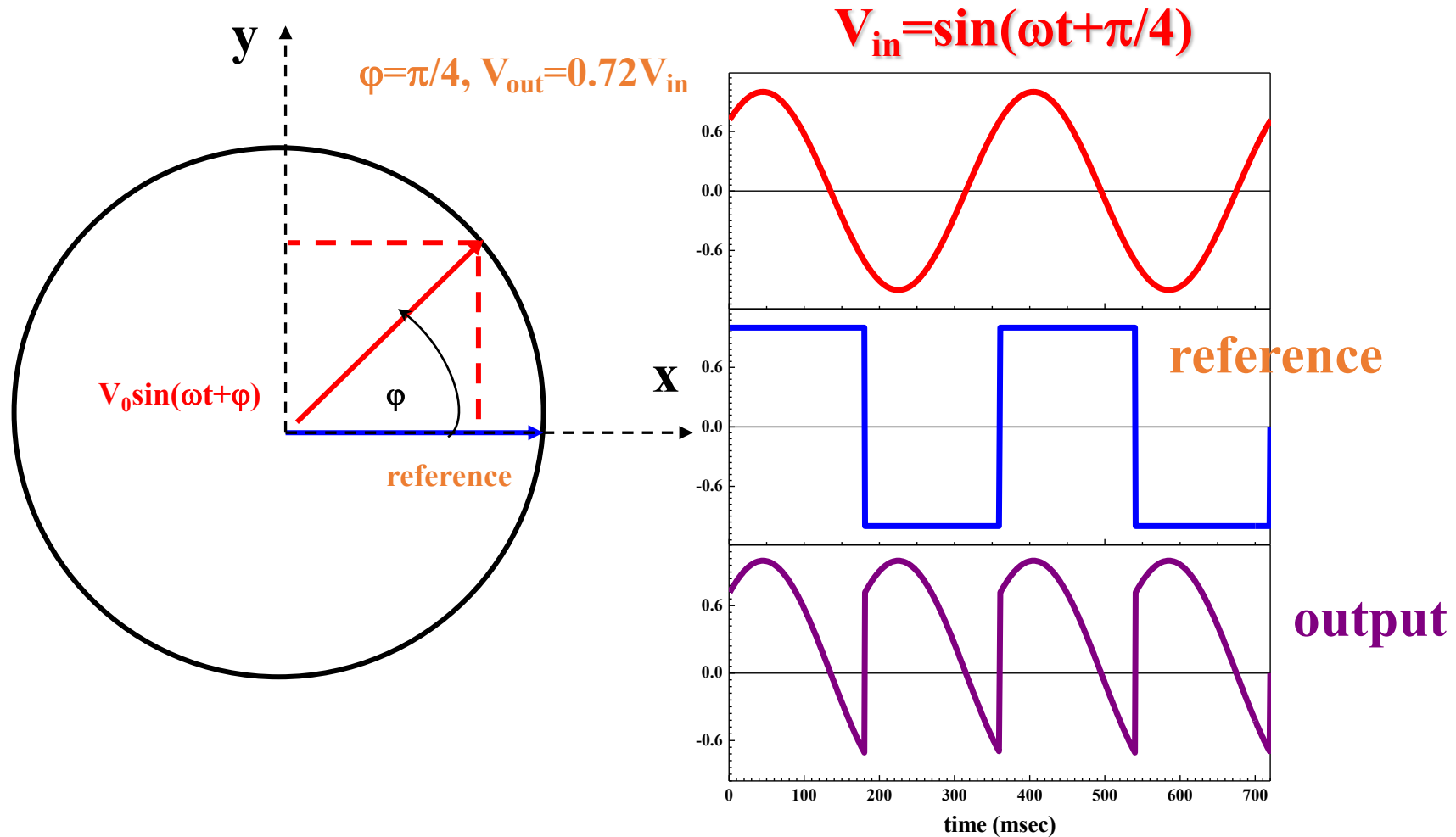

Dual-Channel Lock-In Amplifier

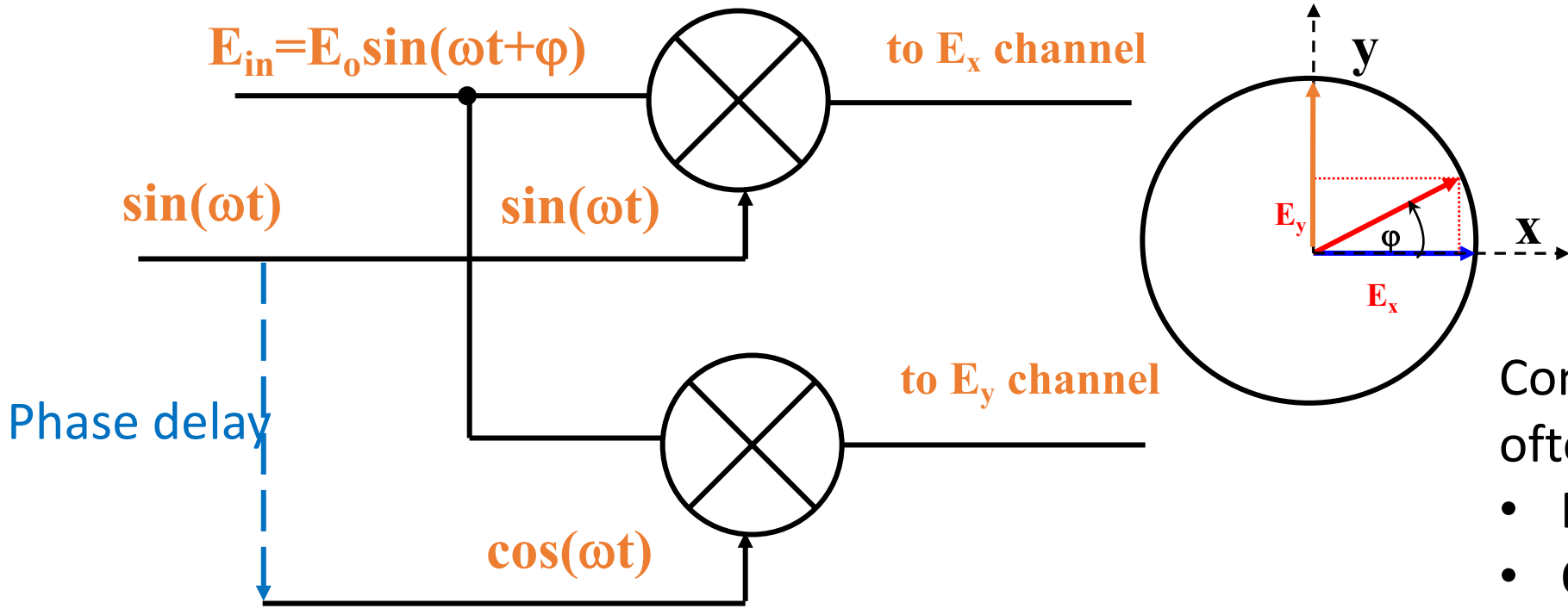We can measure the **phase shift** of the output relative to the reference by demodulating with both the reference and a $\frac{\pi}{2}$ phase-shifted copy of the reference. Yields two amplitudes (E_x/E_y , or I/Q), or equivalently an amplitude and phase shift




Components also often called

- I: in-phase
- Q: quadrature



Digital Lock-In Amplifier

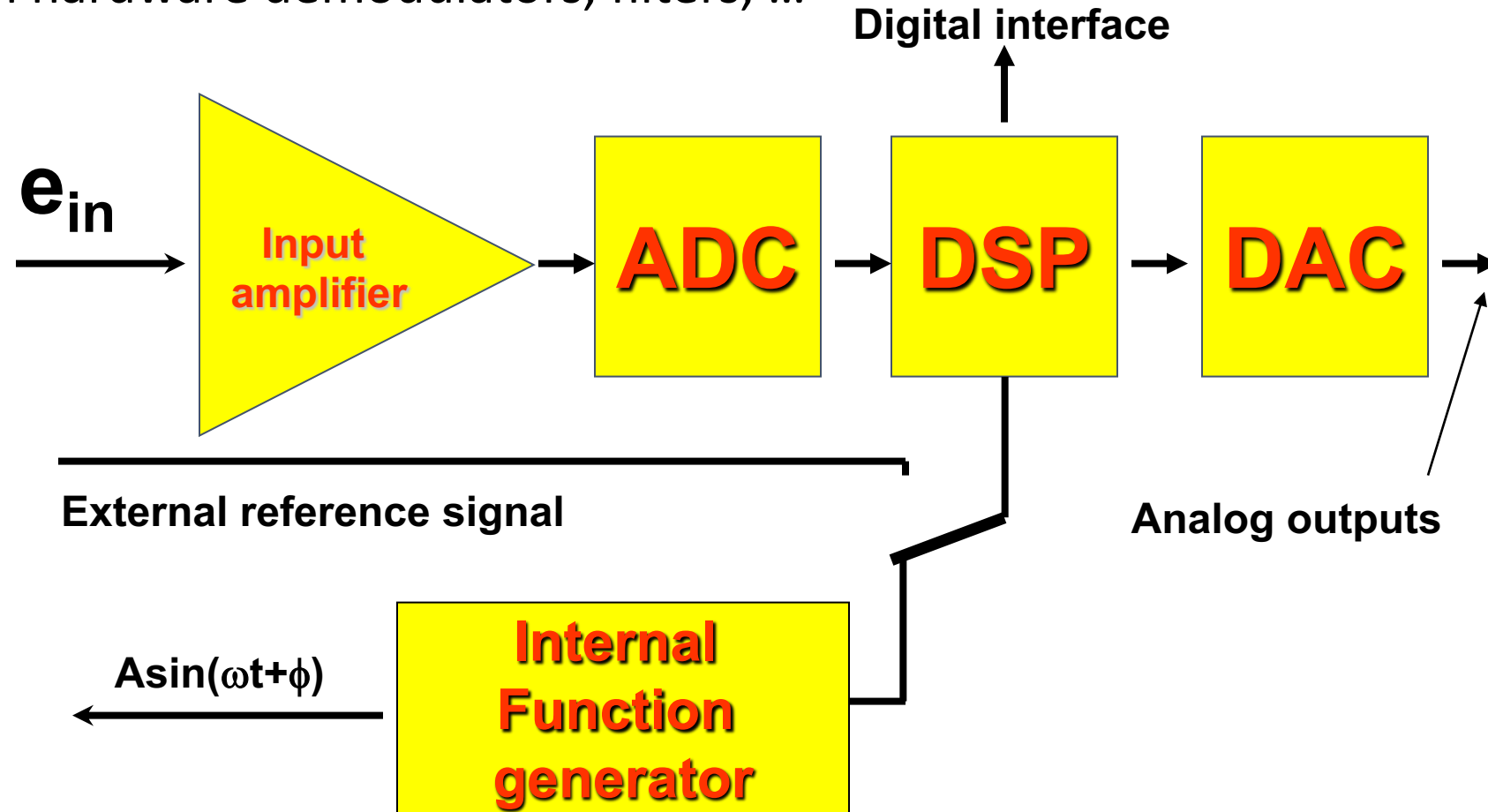Digitize everything and implement the above with **Digital Signal Processing (DSP)** rather than hardware demodulators, filters, ...



SR830 Digital Lock-In Amplifier

Output filter
time constant
& order


Sensitivity
range

Channel #1

Channel #2

Auto
settings

Function
Generator

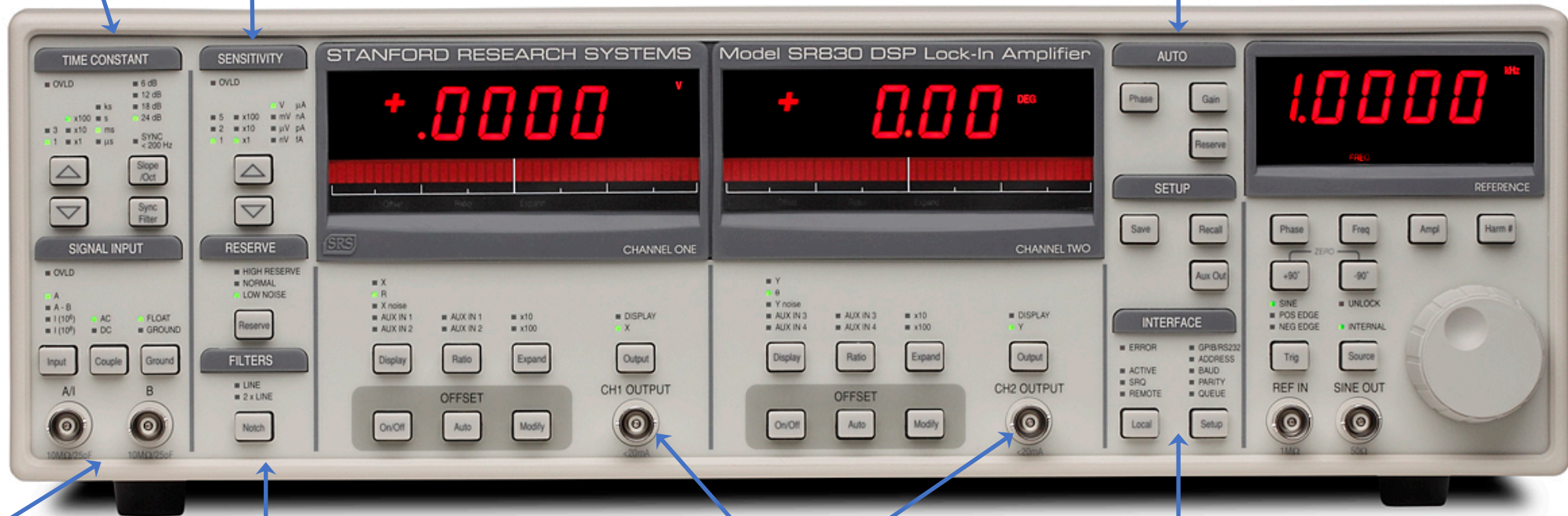

Analog inputs


Power line
notch filter
settings

Analog
outputs

Interface
settings



SR830 Digital Lock-In Amplifier

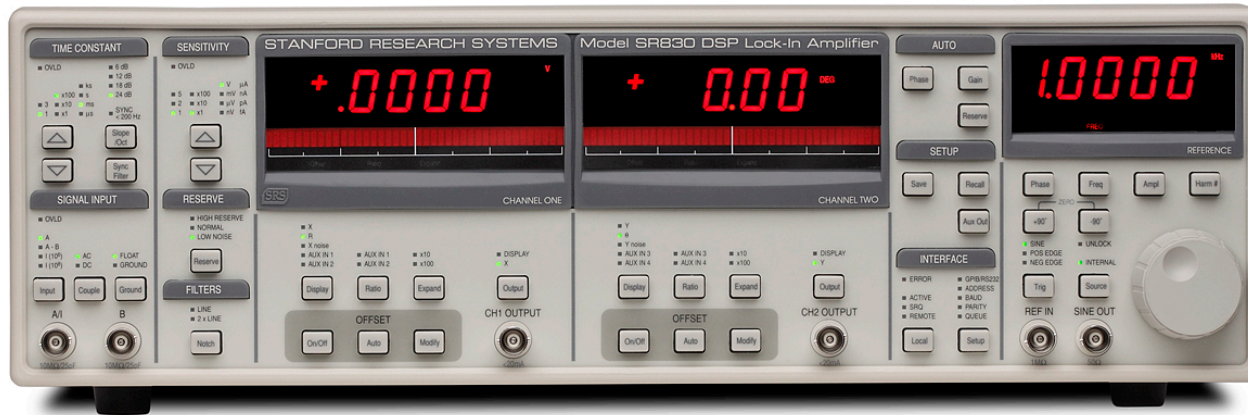

The SR830 manual includes a chapter dedicated to a general description of the lock-in amplifier concept

SR830 BASICS

WHAT IS A LOCK-IN AMPLIFIER?

Lock-in amplifiers are used to detect and measure very small AC signals - all the way down to a few nanovolts! Accurate measurements may be made even when the small signal is obscured by noise


experiment at the reference frequency. In the diagram below, the reference signal is a square wave at frequency ω_r . This might be the sync output from a function generator. If the sine output from

<\\engr-file-03\PHYINST\APL Courses\PHYCS401\Common\EquipmentManuals>




Key Topics of this Lab


1. The Fourier Transform and its Uses

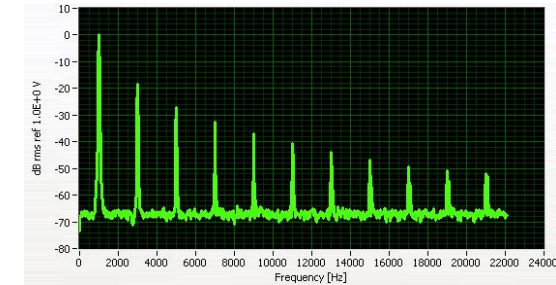


2. Lock-In Amplifiers

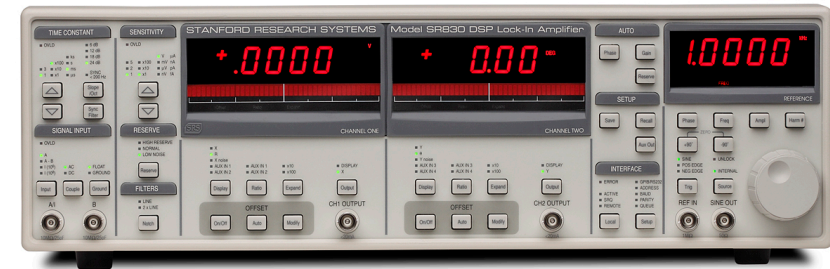

3. Data Analysis

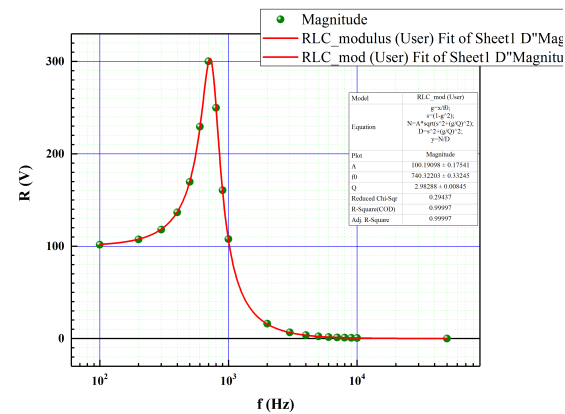

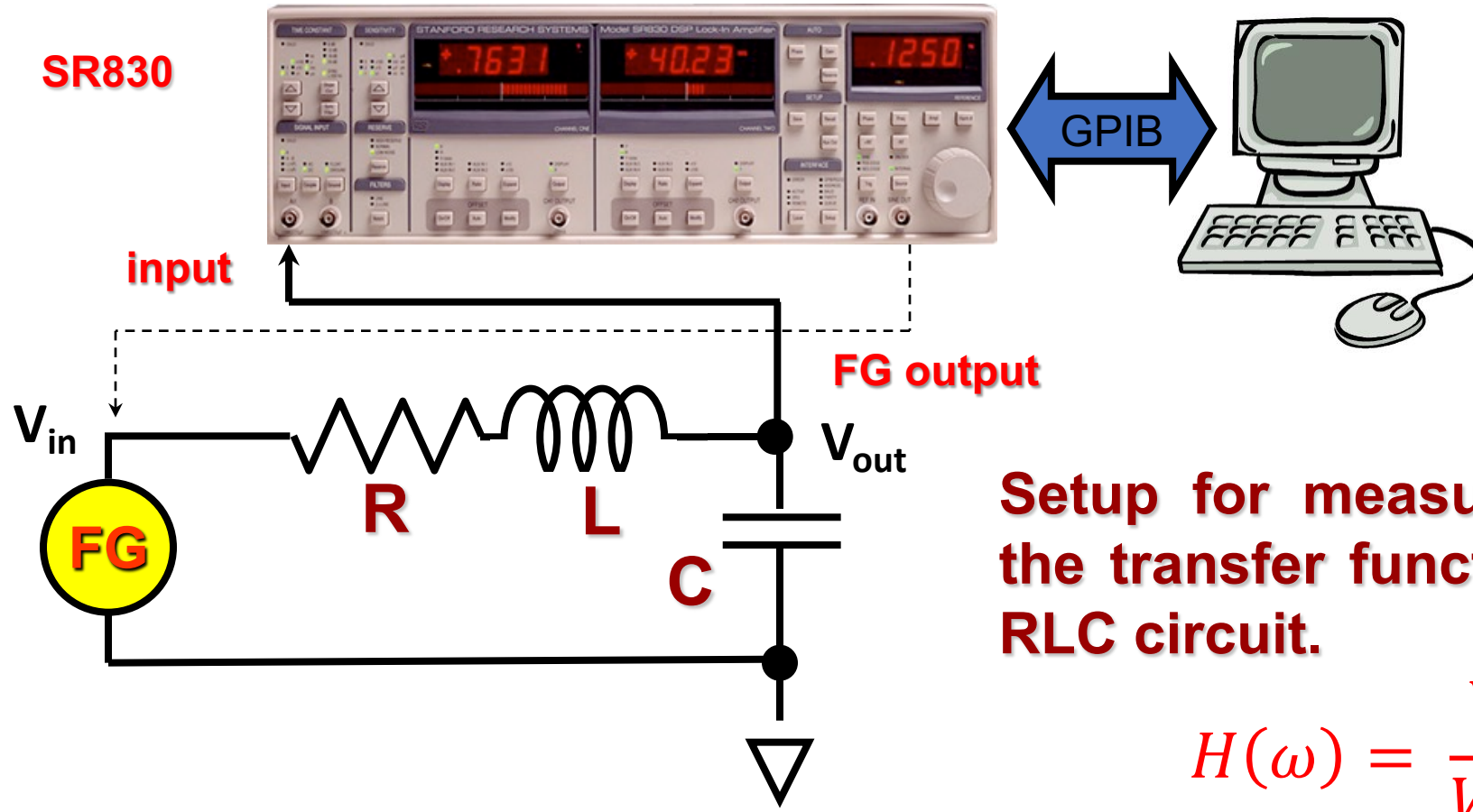Experiment: Lock-In Measurement of the Transfer function of an RLC Circuit




Setup for measurement of the transfer function of the RLC circuit.

$$H(\omega) = \frac{V_{in}}{V_{out}}$$

Calculating Frequency-Domain Response

Example 1. Simple high-pass filter

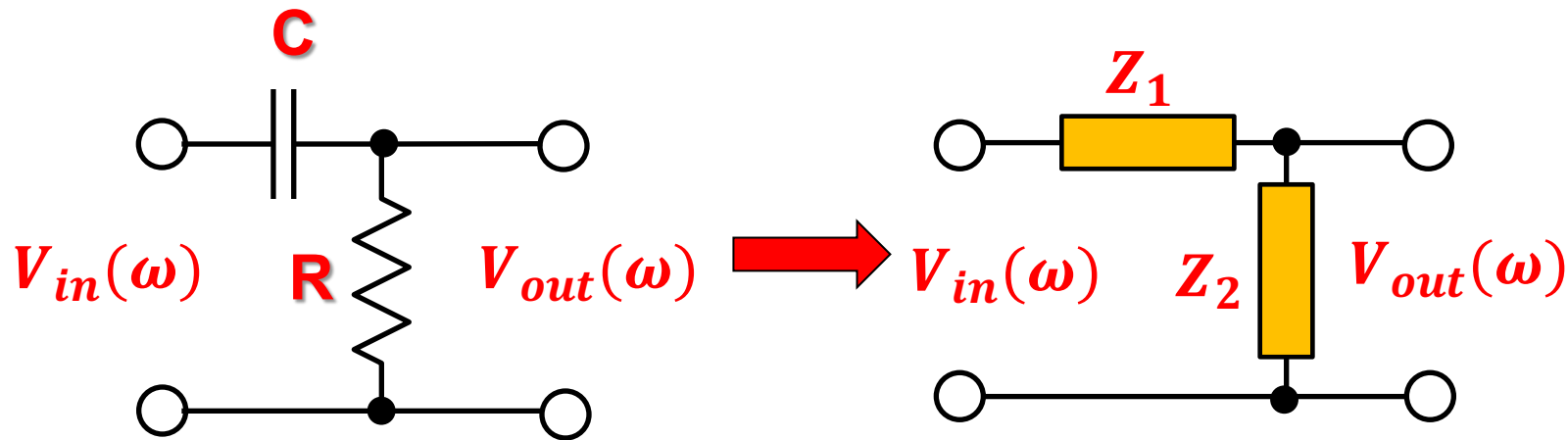

In the frequency domain, each linear component has a (complex) transfer function, called its **impedance**.


$$Z(\omega) \equiv \frac{V(\omega)}{I(\omega)}$$

Makes everything a voltage divider!

Applying Kirchhoff's Law to this simple network...

$$V_{out}(\omega) = H(\omega) * V_{in}(\omega) = \frac{Z_2(\omega)}{Z_1(\omega) + Z_2(\omega)} V_{in}(\omega)$$

Assigning Impedances

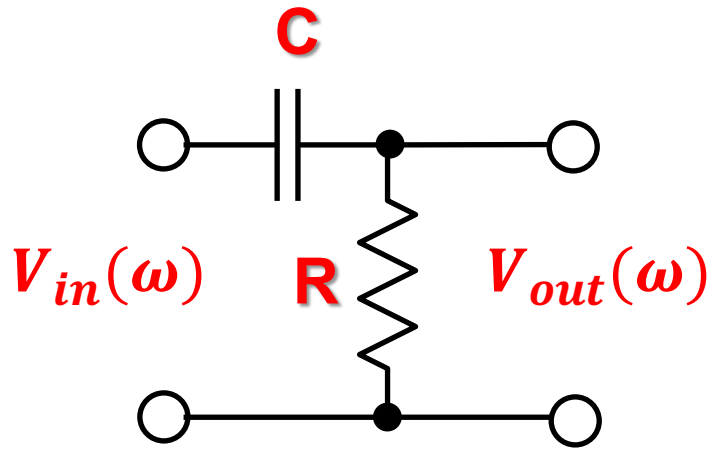

$$Z(\omega) \equiv \frac{V(\omega)}{I(\omega)}$$

Inductor: $V e^{i\omega t} = L \frac{d}{dt} (I e^{i\omega t}) = i\omega L I e^{i\omega t}$

Capacitor: $CV = Q; C \frac{dV}{dt} = \frac{dQ}{dt} = I; i\omega C V e^{i\omega t} = I e^{i\omega t}$

Ideal components

$$Z_R = R$$

$$Z_L = i\omega L$$

$$Z_C = \frac{1}{i\omega C} = -\frac{i}{\omega C}$$

More realistic...


$$Z_R = R + \dots$$

$$Z_L = i\omega L + R_L$$

$$Z_C = \frac{1}{i\omega C + R_C^{-1}}$$

$$V_{out}(\omega) = H(\omega) * V_{in}(\omega) = \frac{Z_2(\omega)}{Z_1(\omega) + Z_2(\omega)} V_{in}(\omega)$$

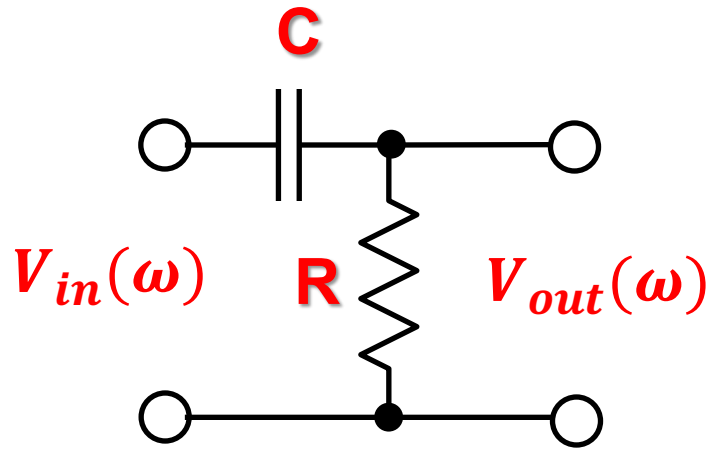High-Pass Filter Frequency-Domain Response





Convenient to define:

- **Time constant** $\tau = RC$ [seconds]
- **Cutoff frequency** $\omega_c = \frac{1}{\tau}$ [rad/s]

$$H(\omega) \equiv \frac{V_{out}(\omega)}{V_{in}(\omega)} = \frac{R}{R + \frac{1}{i\omega C}} = \frac{i\omega RC}{1 + i\omega RC} = \frac{i\omega\tau}{1 + i\omega\tau} = \frac{\omega\tau}{1 + \omega^2\tau^2} (H_R(\omega) + iH_I(\omega))$$

$$|H(\omega)| = \sqrt{H_R^2 + H_I^2} = \frac{\omega\tau}{\sqrt{1 + \omega^2\tau^2}}; \quad \Theta(\omega) = \tan^{-1}\left(\frac{H_I}{H_R}\right) = \tan^{-1}\left(\frac{1}{\omega\tau}\right)$$

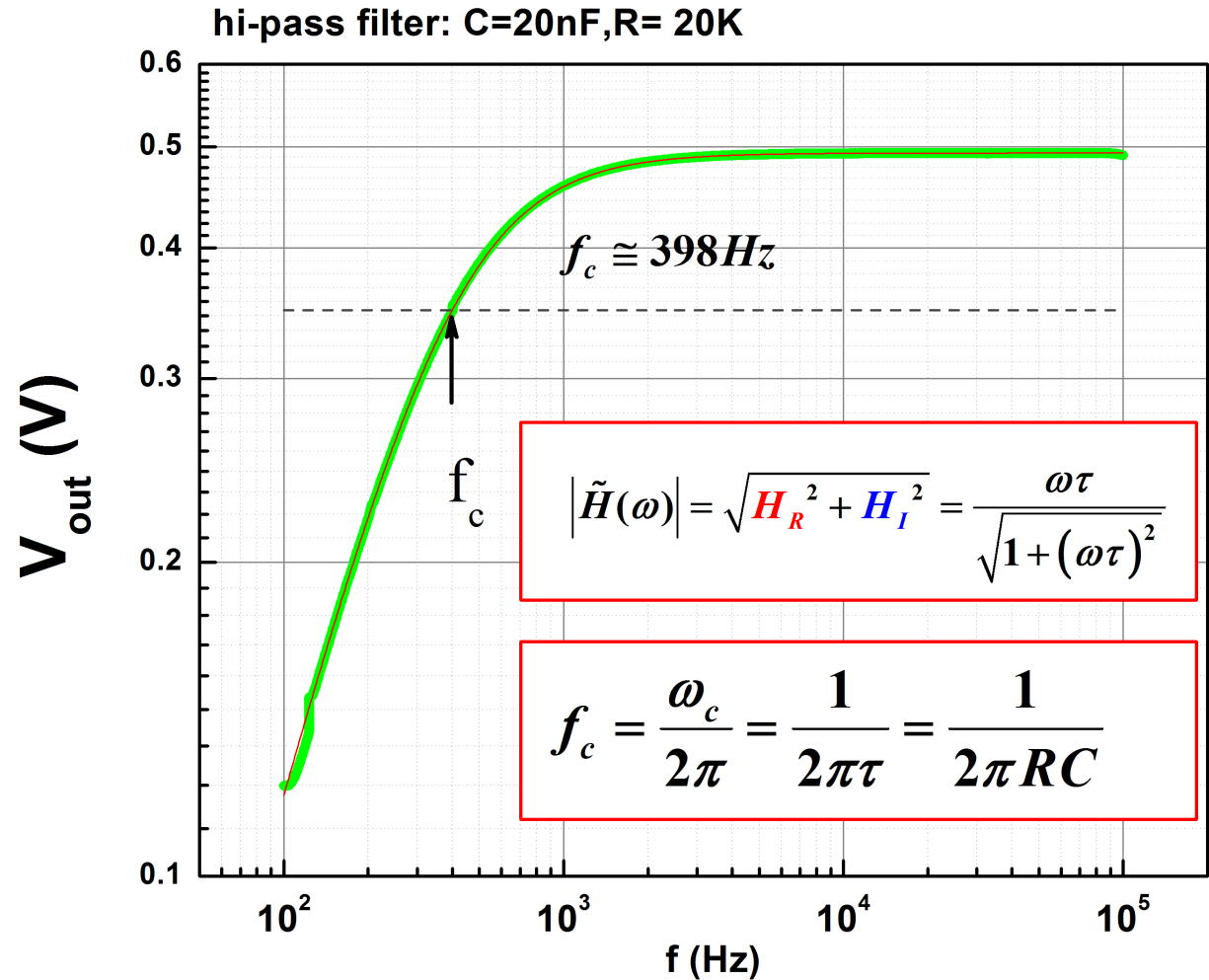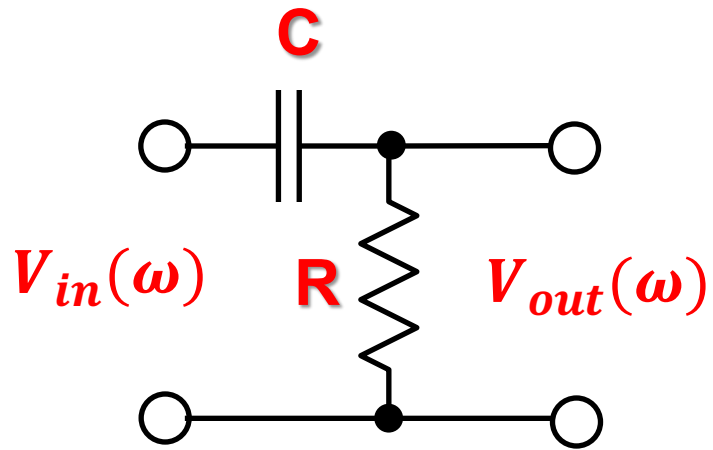High-Pass Filter Frequency-Domain Response



Aside on Frequencies and Time Constants


Be careful of your factors of 2π !

- **Time constant** $\tau = RC$ [seconds]
 - **Cutoff frequency** $\omega_c = \frac{1}{\tau}$ [radians/s]
 - $f_{3dB} = \frac{\omega_c}{2\pi}$ [cycles/s = Hz]
- Your **formulas** will naturally use these
- Your **measurements** will naturally use these

The **cutoff frequency** is when the **power** ($P \propto V^2$) is down by a factor of 2 (*a.k.a.* -3 dB), so the **amplitude** has dropped by a factor of $\sqrt{2}$ (0.707 of peak).


Note to remember: Time constants are the inverses of *omegas* (angular frequencies), not *frequencies*!

High-Pass Filter: Fitting

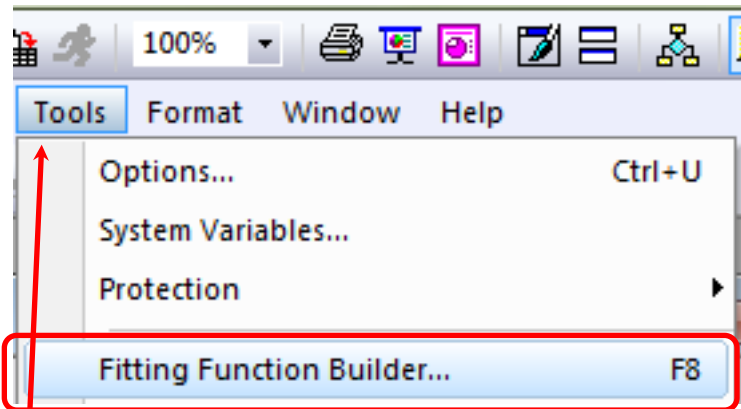

$$|\tilde{V}_{out}| = |\tilde{V}_{in}| * |\tilde{H}(\omega)| = V_0 * \frac{\omega\tau}{\sqrt{1 + (\omega\tau)^2}}; \quad \tau = RC$$

Fitting parameters: V_0 , τ , V_{off}

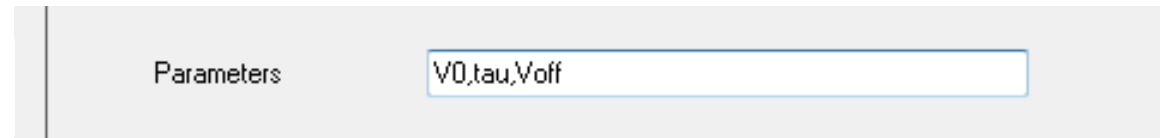



Param	Unit	Meaning	Fixed	Initial Value	Significant Digits
V0		?	<input type="checkbox"/>	1	System
tau		?	<input type="checkbox"/>	1	System
Voff		?	<input type="checkbox"/>	1	System

Fitting function →




Function Body (Dependent Variables : y)

$$y = V_0 * 2 * \pi * x * \tau / \sqrt{1 + (2 * \pi * \tau)^2} + V_{off}$$

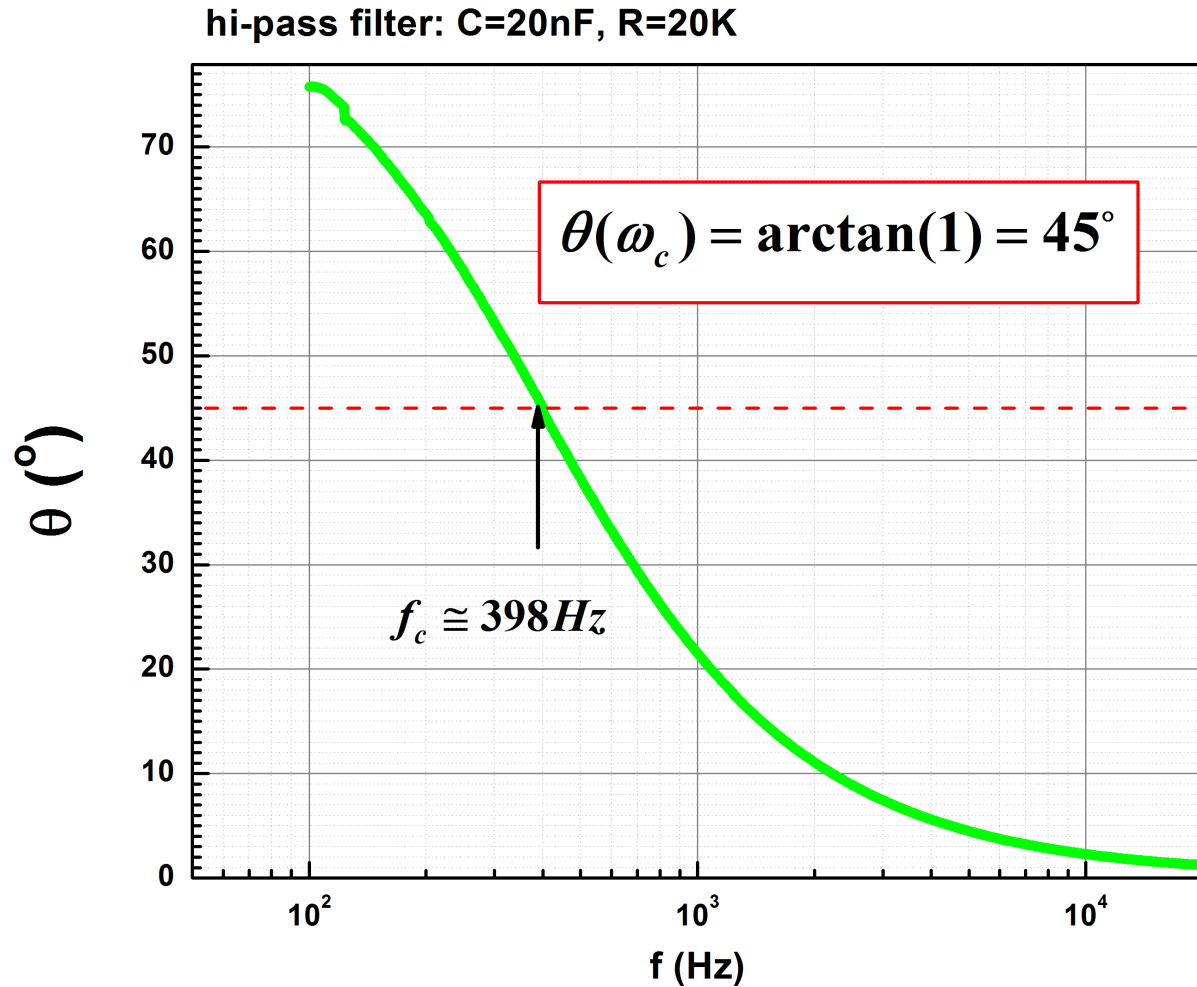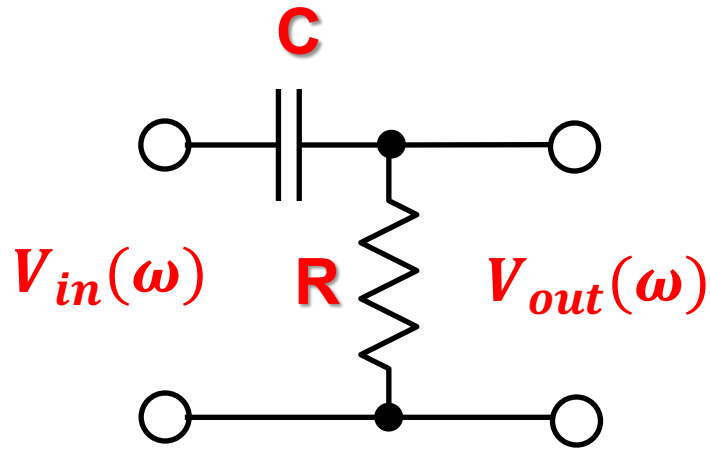High-Pass Filter Frequency-Domain Response



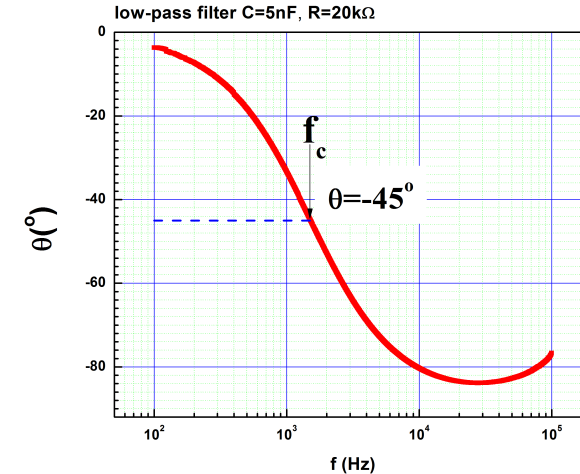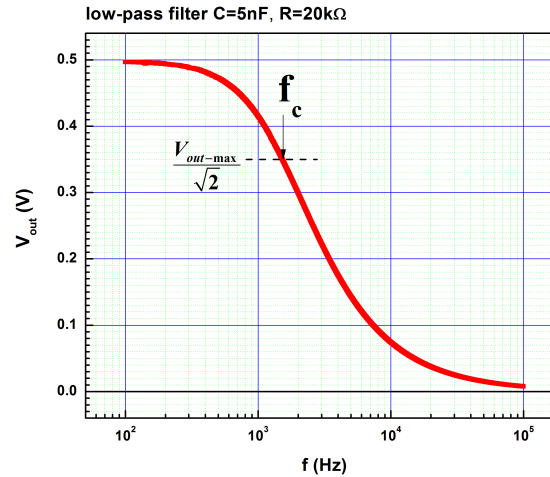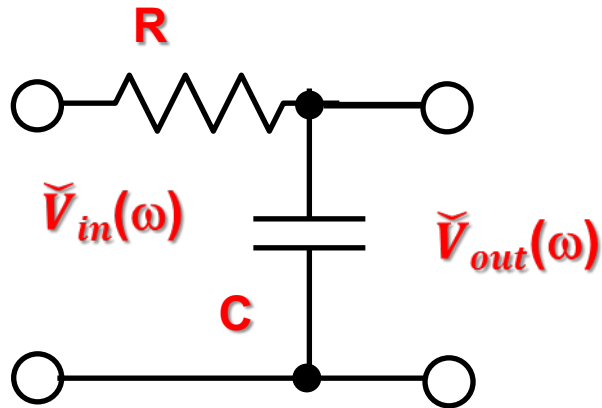
Low-Pass Filter Frequency-Domain Response



$$H(\omega) \equiv \frac{V_{out}(\omega)}{V_{in}(\omega)} = \frac{1}{R + \frac{1}{i\omega C}} = \frac{1}{1 + i\omega RC} = \frac{1}{1 + i\omega\tau} = \frac{H_R(\omega) + iH_I(\omega)}{1 + \omega^2\tau^2} = \frac{1 - i\omega\tau}{1 + \omega^2\tau^2}$$

$$|H(\omega)| = \sqrt{H_R^2 + H_I^2} = \frac{1}{\sqrt{1 + \omega^2\tau^2}}; \quad \Theta(\omega) = \tan^{-1}\left(\frac{H_I}{H_R}\right) = -\tan^{-1}(\omega\tau)$$

RLC Circuit Frequency-Domain Response

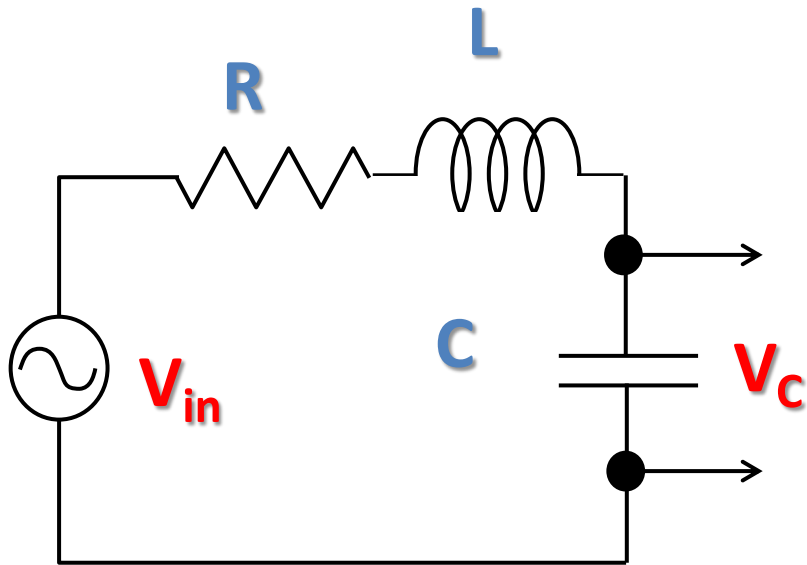

$$H(\omega) = \frac{V_C(\omega)}{V_{in}(\omega)} = \frac{\frac{1}{i\omega C}}{R + i\omega L + \frac{1}{i\omega C}} = \frac{1}{1 + i\omega RC - \omega^2 LC}$$


Defining $\omega_0 \equiv \frac{1}{\sqrt{LC}}$; $\tau \equiv RC$; $Q \equiv \frac{1}{\omega_0 \tau}$ and rearranging...

$$H(\omega) = \frac{\left(1 - \left(\frac{\omega}{\omega_0}\right)^2\right) - i\omega\tau}{\left(1 - \left(\frac{\omega}{\omega_0}\right)^2\right)^2 + (\omega\tau)^2} = \frac{\left(1 - \left(\frac{\omega}{\omega_0}\right)^2\right) - \frac{i}{Q}\left(\frac{\omega}{\omega_0}\right)}{\left(1 - \left(\frac{\omega}{\omega_0}\right)^2\right)^2 + \frac{1}{Q^2}\left(\frac{\omega}{\omega_0}\right)^2}$$

RLC Circuit Frequency-Domain Response

$$\omega_0 \equiv \frac{1}{\sqrt{LC}}; \quad \tau \equiv RC; \quad Q \equiv \frac{1}{\omega_0 \tau}$$

$$|H(\omega)| = \frac{1}{\sqrt{\left(1 - \left(\frac{\omega}{\omega_0}\right)^2\right)^2 + \frac{1}{Q^2} \left(\frac{\omega}{\omega_0}\right)^2}}$$
$$\Theta = \tan^{-1} \left(\frac{\left(\frac{\omega}{\omega_0}\right)}{Q \left(1 - \left(\frac{\omega}{\omega_0}\right)^2\right)} \right)$$

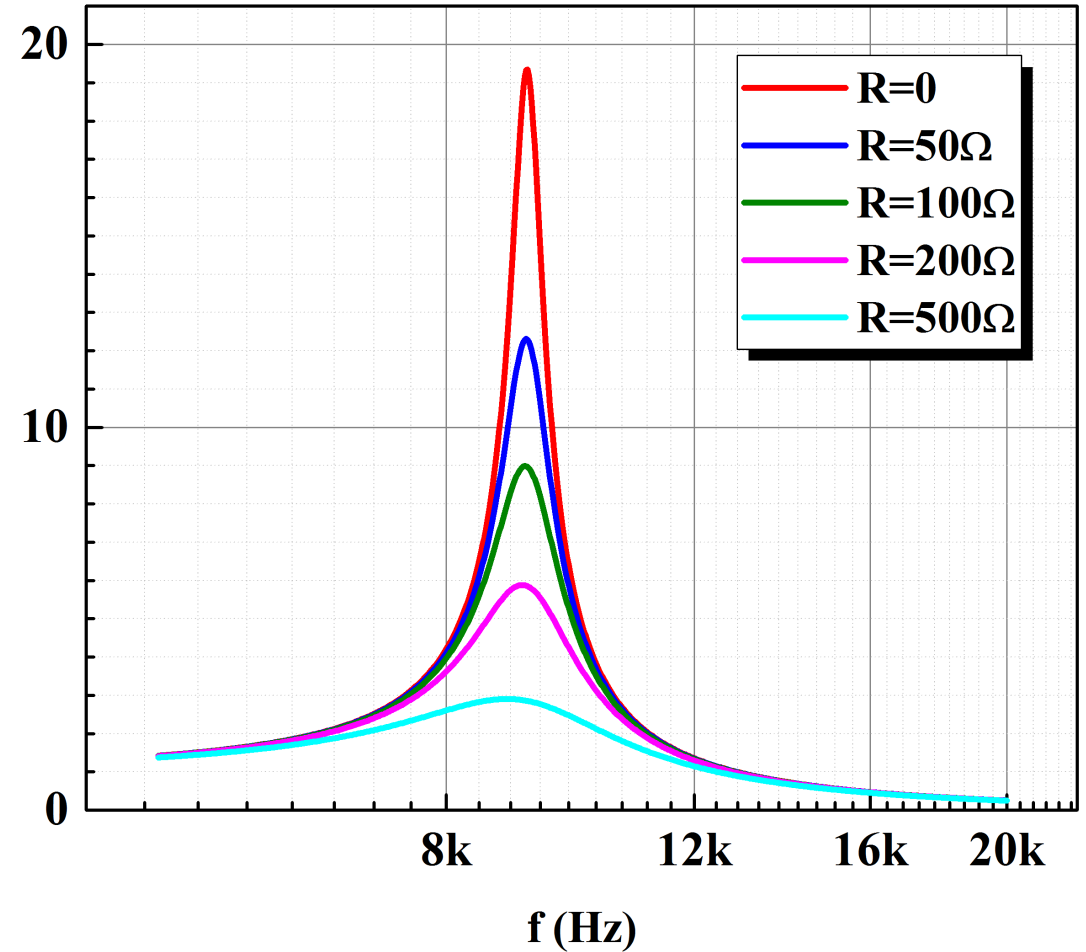


Resonance curves with varying **R** (and thus **Q**)


RLC Circuit Frequency-Domain Response

$$\omega_0 \equiv \frac{1}{\sqrt{LC}}; \quad \tau \equiv RC; \quad Q \equiv \frac{1}{\omega_0 \tau}$$

$$|H(\omega)| = \frac{1}{\sqrt{\left(1 - \left(\frac{\omega}{\omega_0}\right)^2\right)^2 + \frac{1}{Q^2} \left(\frac{\omega}{\omega_0}\right)^2}}$$
$$\Theta = \tan^{-1} \left(\frac{\left(\frac{\omega}{\omega_0}\right)}{Q \left(1 - \left(\frac{\omega}{\omega_0}\right)^2\right)} \right)$$

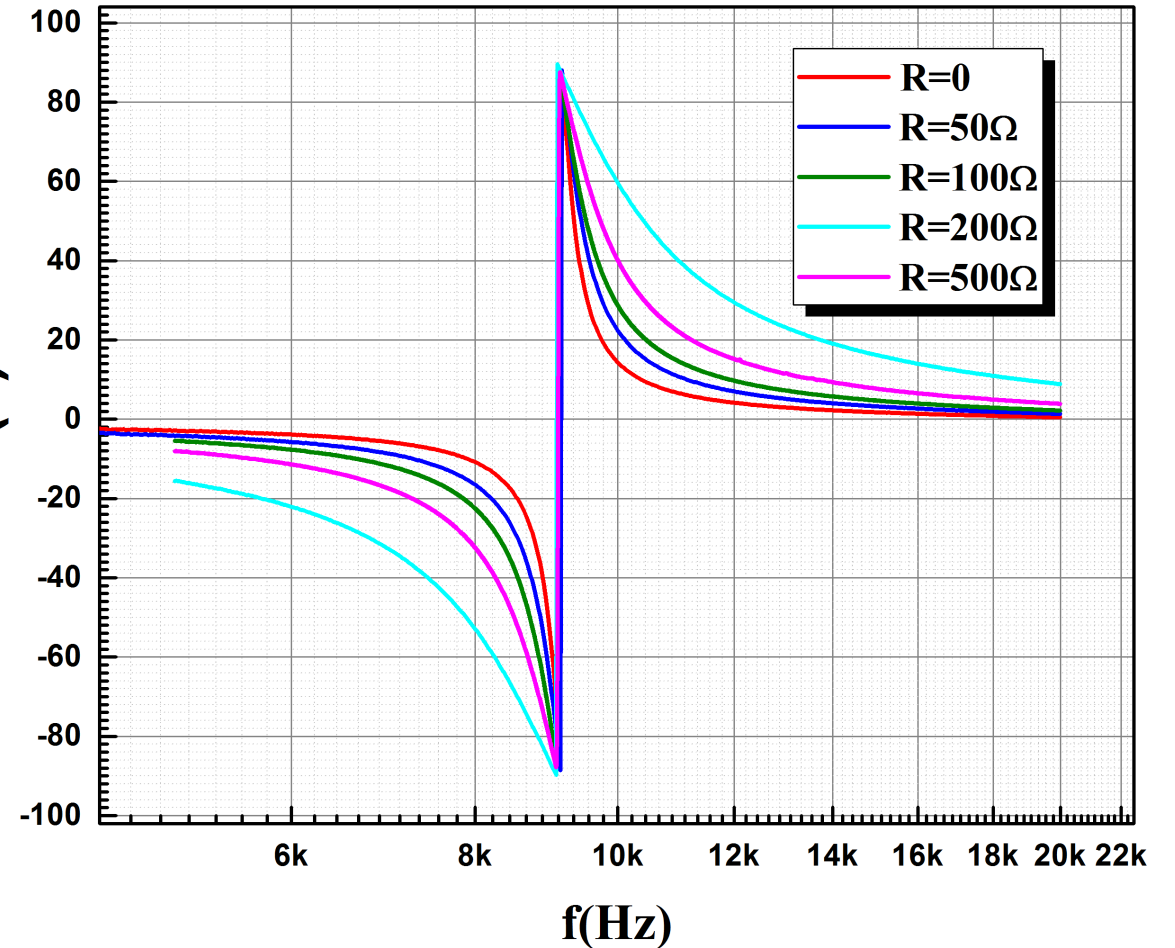

Applying a Lock-In to Study RLC Response

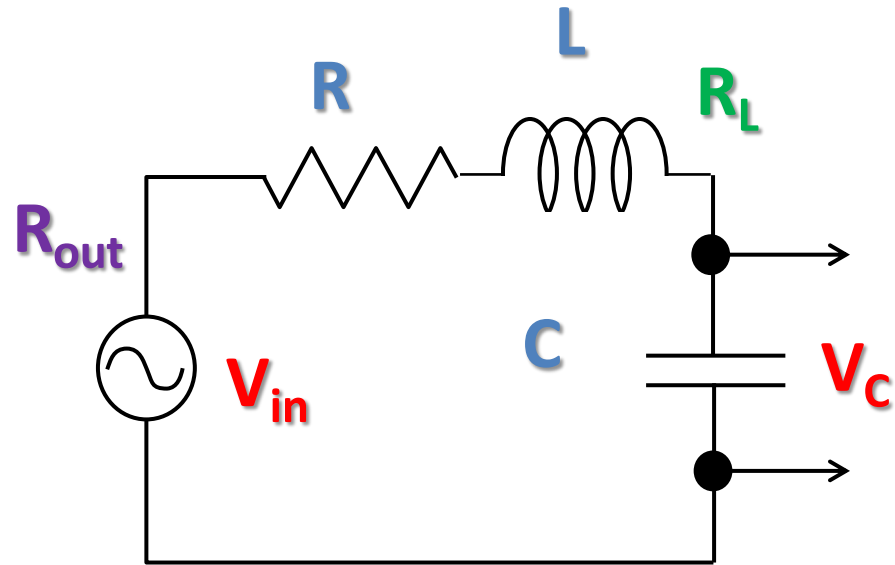


$$R=0; R_{out} = 50 \Omega; R_L = 35.8 \Omega$$

Actual damping resistance R is the sum of:

- R : the explicit resistor
- R_{out} : the function generator output impedance
- R_L : the resistance of the coil

Actual R from fitting parameters is ~ 88.8 ohms, not far from calculated 85.8 ohms

Fitting RLC Circuit Response

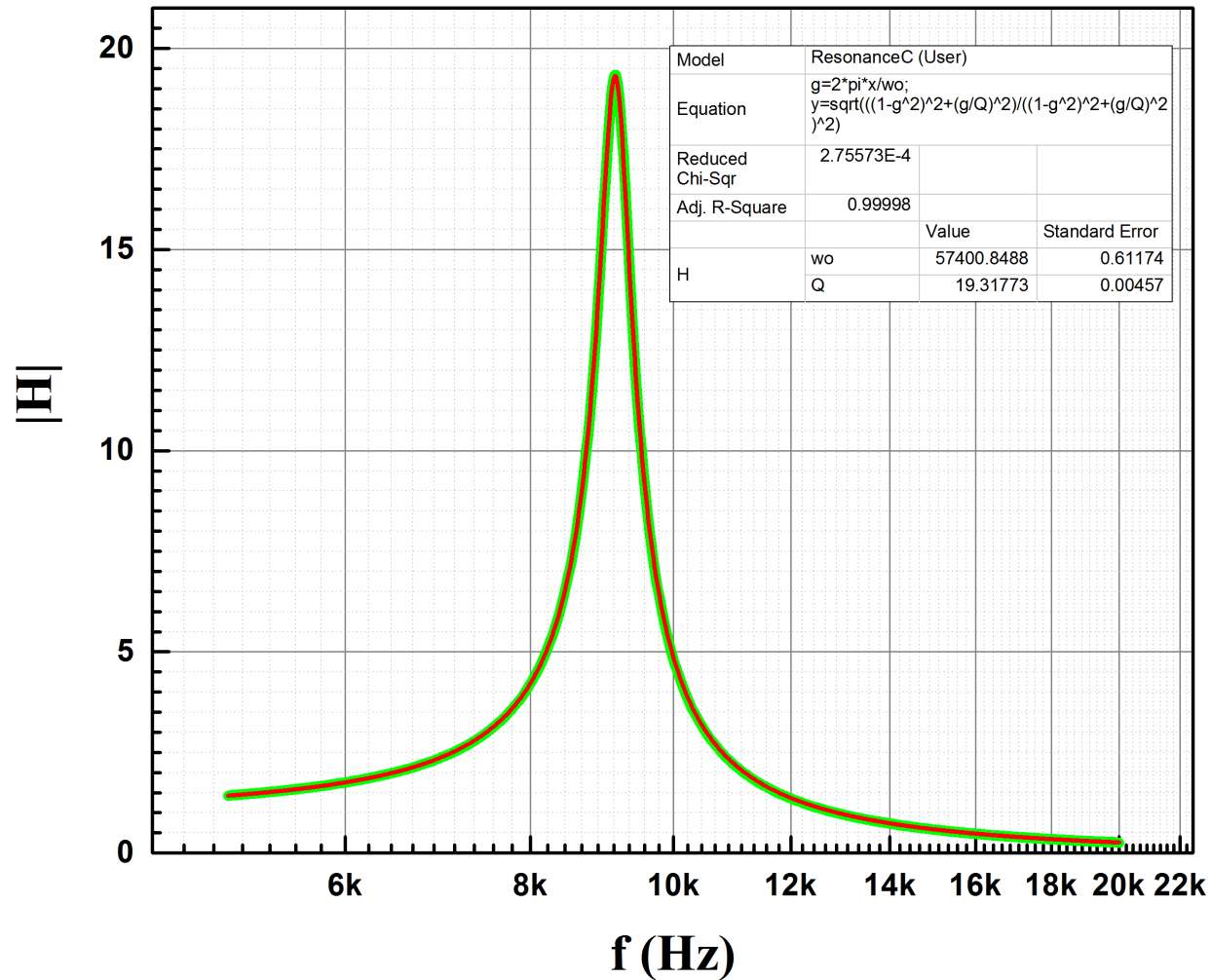


$$\omega_0 \equiv \frac{1}{\sqrt{LC}}; \quad \tau \equiv RC; \quad Q \equiv \frac{1}{\omega_0 \tau}$$

$$|H(\omega)| = \frac{1}{\sqrt{\left(1 - \left(\frac{\omega}{\omega_0}\right)^2\right)^2 + \frac{1}{Q^2} \left(\frac{\omega}{\omega_0}\right)^2}}$$

Fitting for amplitude **|H|**

Fit parameters ω_0 and Q

Fitting RLC Circuit Response

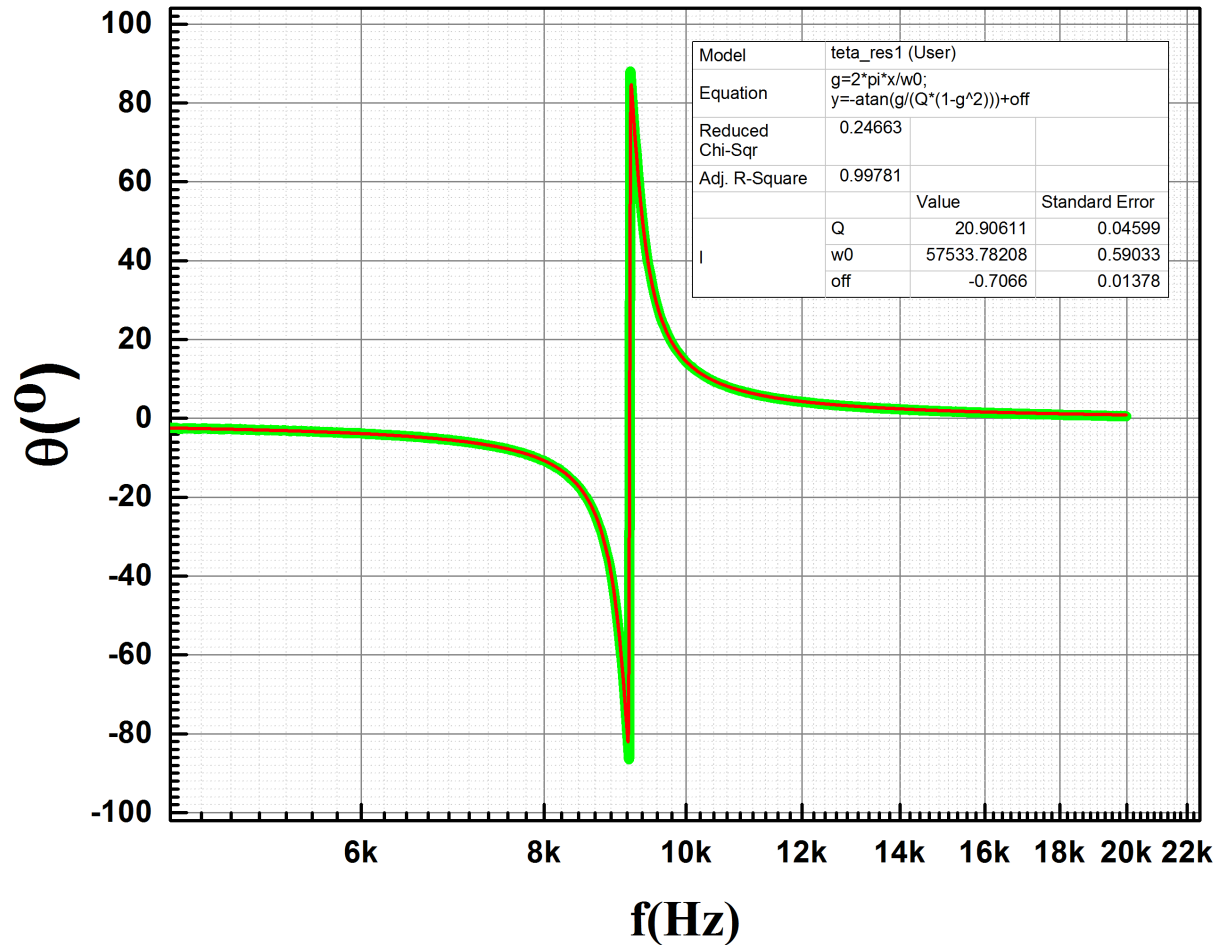


$$\omega_0 \equiv \frac{1}{\sqrt{LC}}; \quad \tau \equiv RC; \quad Q \equiv \frac{1}{\omega_0 \tau}$$

$$\Theta = \tan^{-1} \left(\frac{\left(\frac{\omega}{\omega_0}\right)}{Q \left(1 - \left(\frac{\omega}{\omega_0}\right)^2\right)} \right)$$


Fitting for amplitude **|H|**

Fit parameters ω_0 and Q

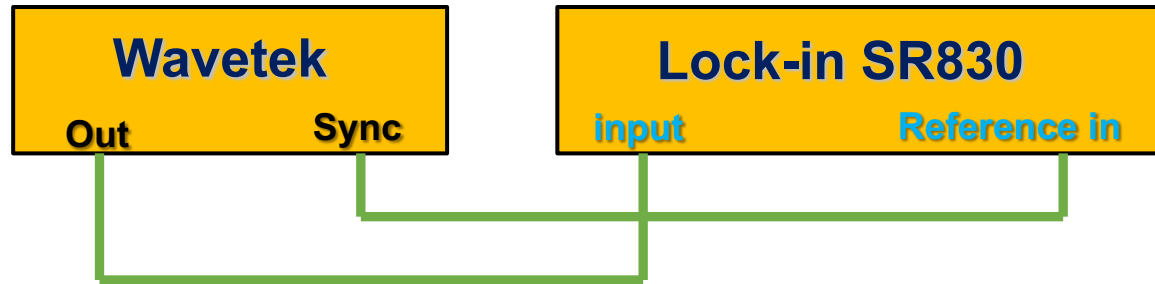From Time Domain to Frequency Domain: Experiment



F(t) – periodic function F(t)=F(t+T₀):

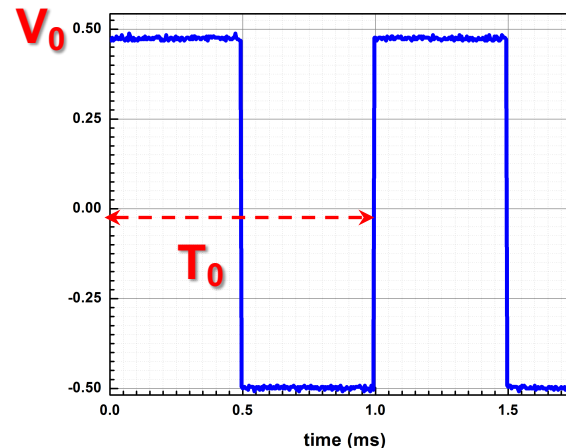

Time domain pattern

➔ **Frequency domain ?**



$$V(t) = \begin{cases} V_0: 0 < t \leq \frac{T_0}{2} \\ -V_0: \frac{T_0}{2} < t \leq T_0 \end{cases}$$

$$a_n = \frac{2}{T_0} \int_0^{T_0} F(t) \cos\left(\frac{2\pi n t}{T_0}\right) dt$$

$$b_n = \frac{2}{T_0} \int_0^{T_0} F(t) \sin\left(\frac{2\pi n t}{T_0}\right) dt$$


$$a_0 = \frac{2}{T_0} \int_0^{T_0} F(t) dt$$

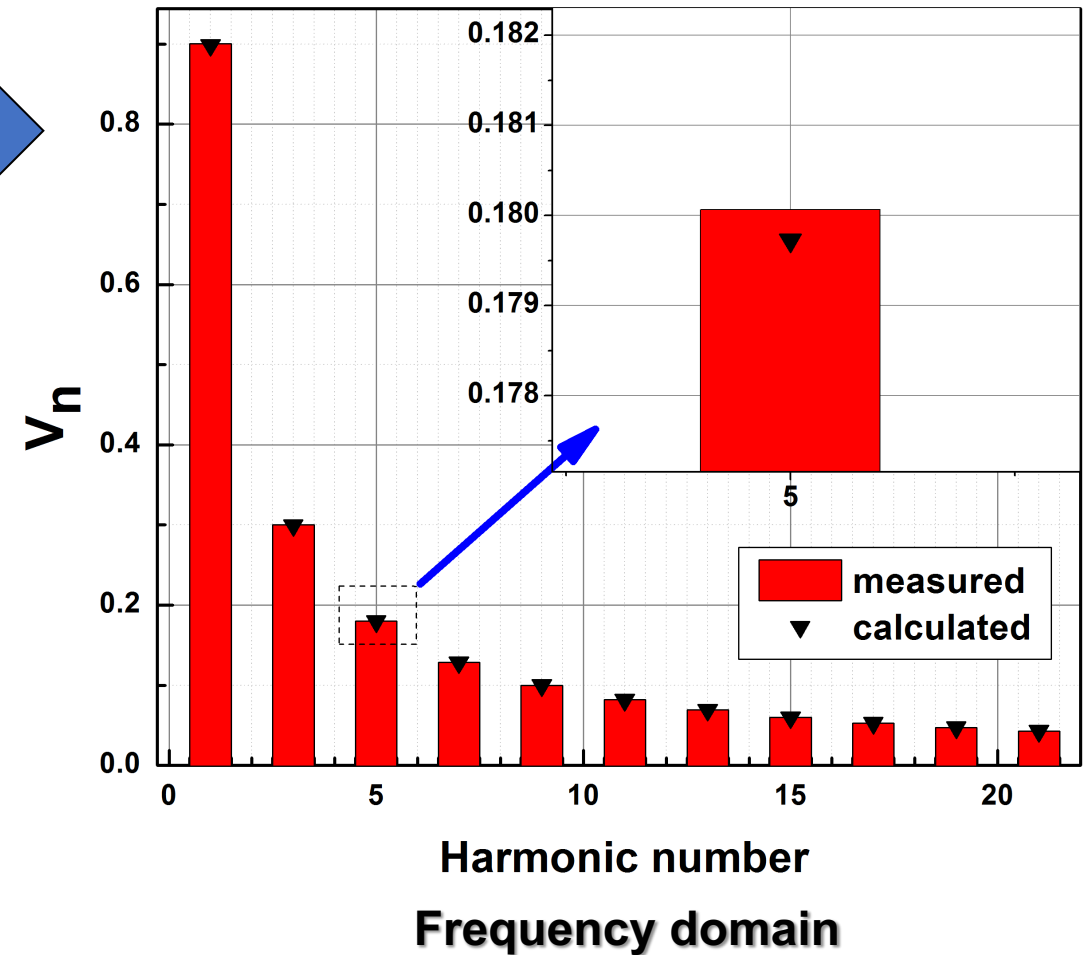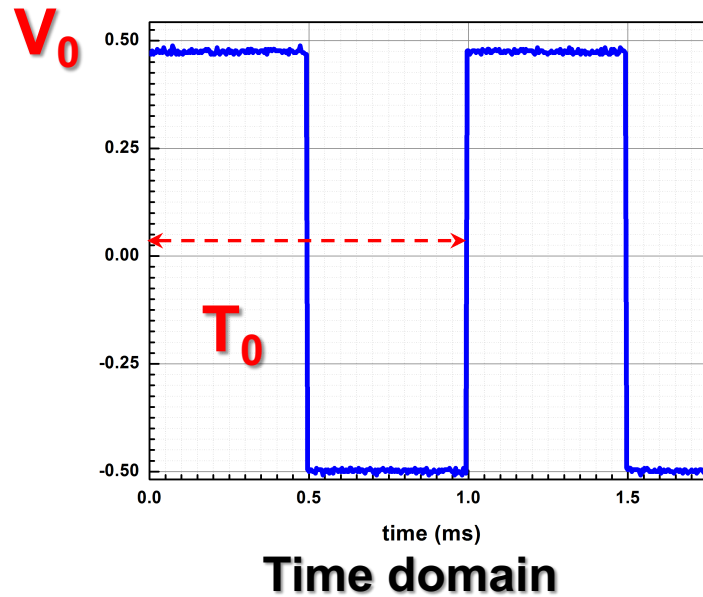From Time Domain to Frequency Domain: Lock-In




Spectrum measured by
SR830 lock-in amplifier

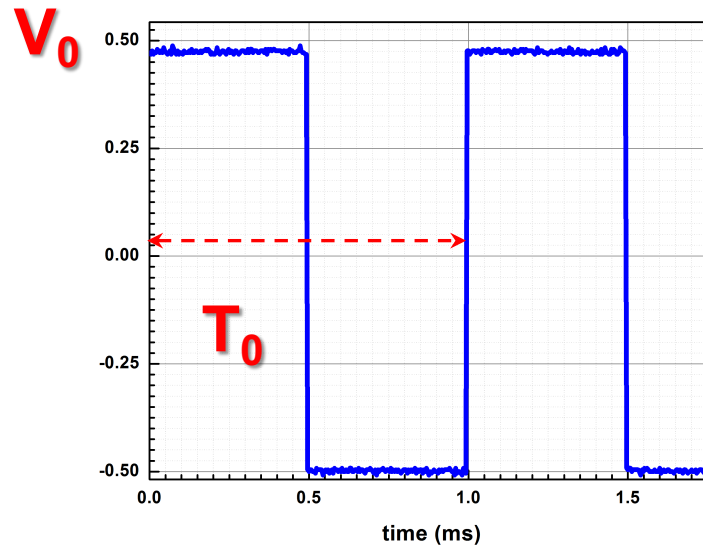From Time Domain to Frequency Domain: Origins




Time domain trace acquired using Tektronix scope

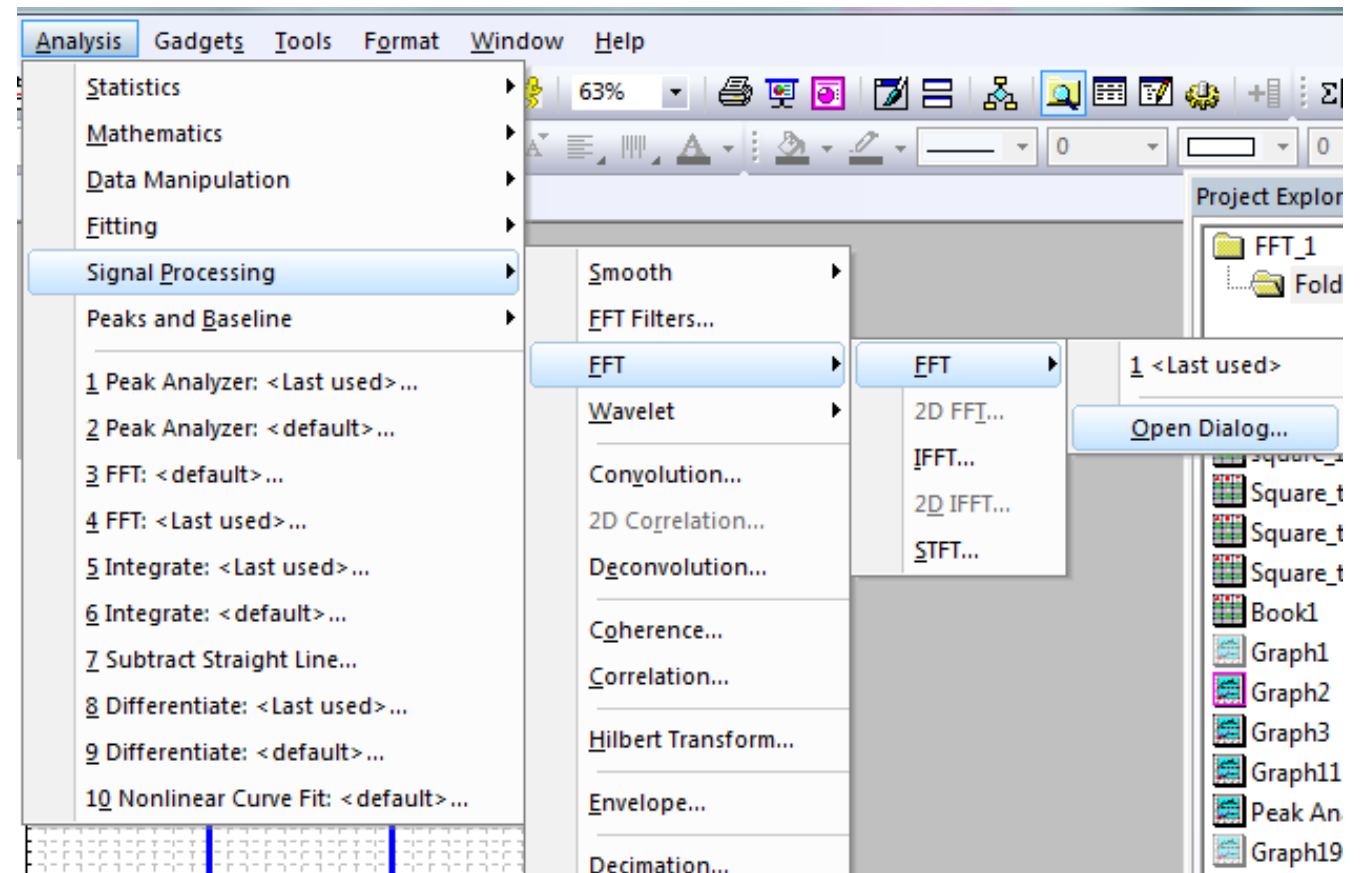
Origins can convert saved data file to frequency domain



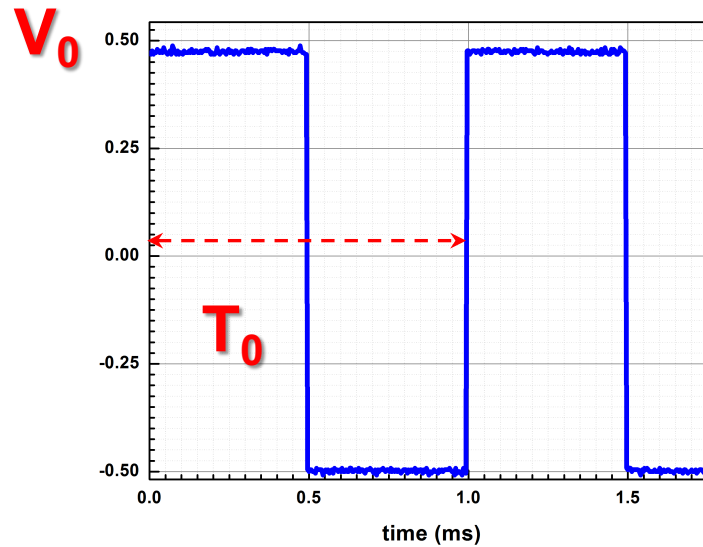From Time Domain to Frequency Domain: Origins



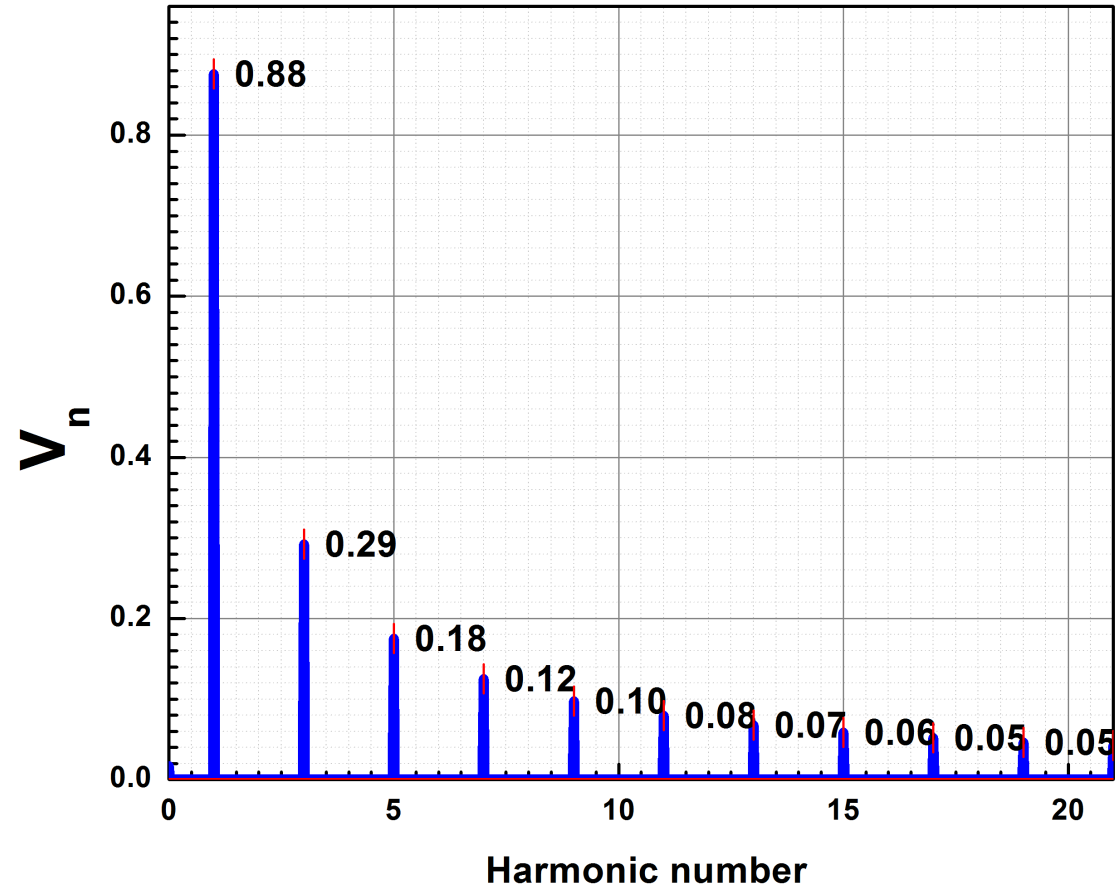
Time domain trace acquired using Tektronix scope




Spectrum calculated by **Origin**. Accuracy is limited by the modest resolution of the scope.



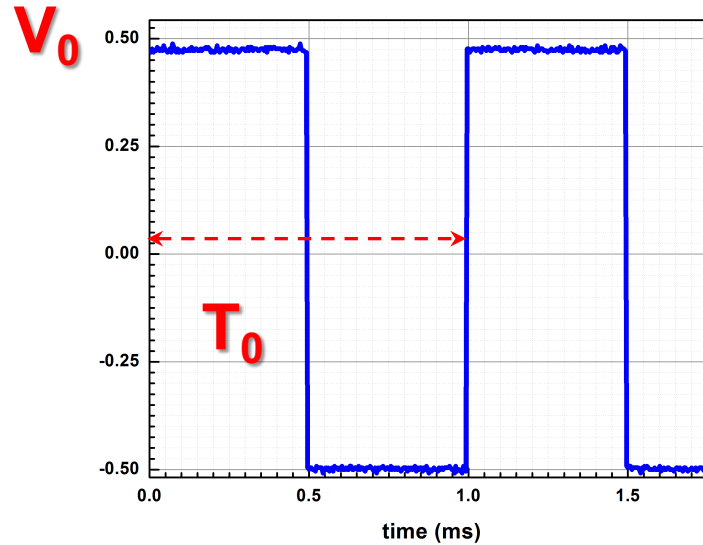From Time Domain to Frequency Domain: Scope




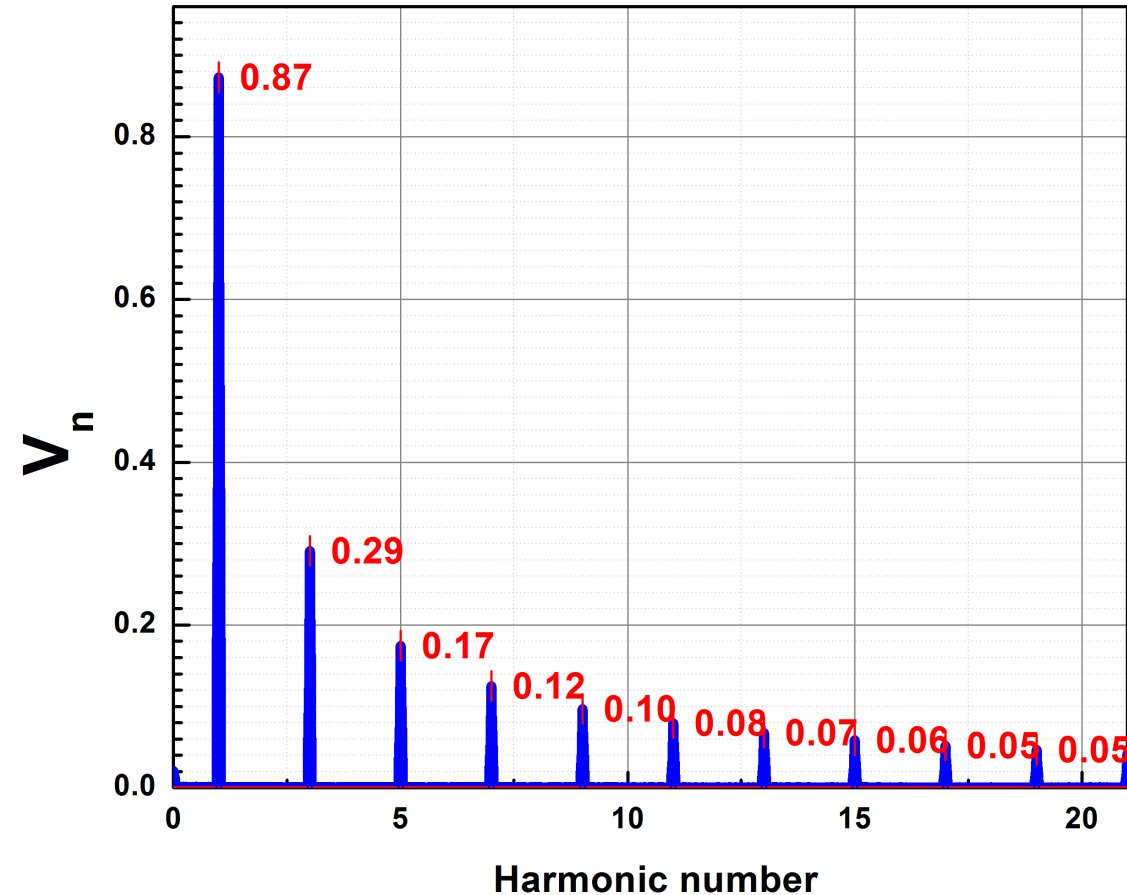Time domain trace acquired using Tektronix scope




Spectrum calculated by the **Math options** of the **Tektronix scope**. Accuracy is limited by the modest resolution of the scope.

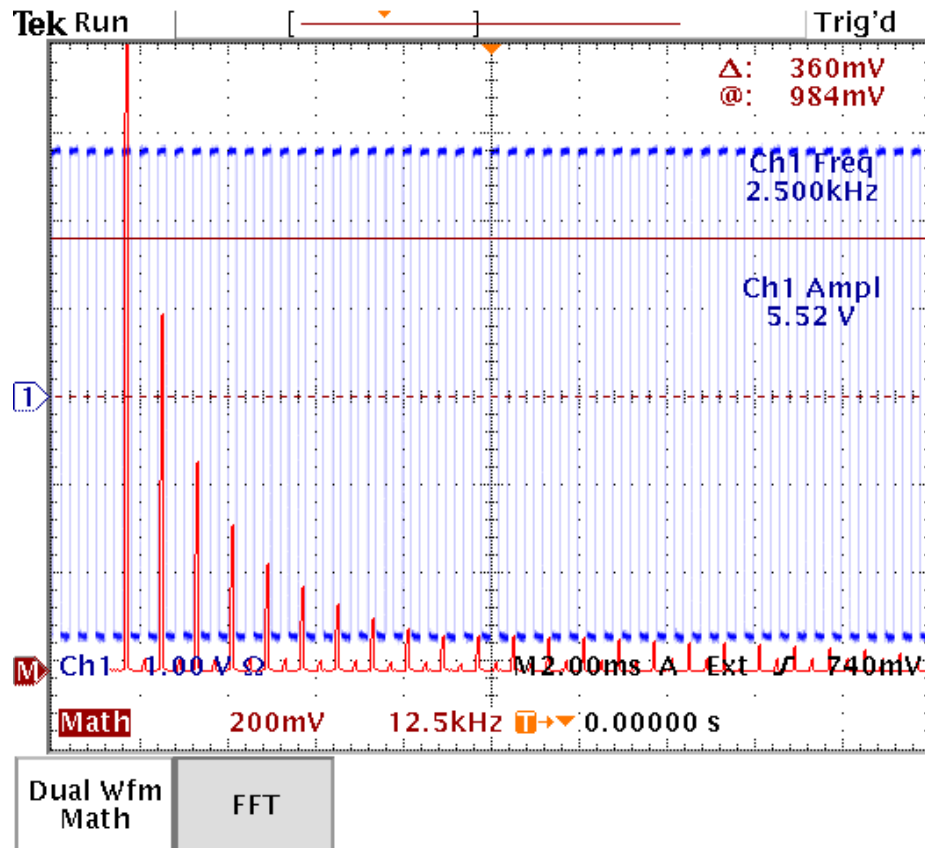From Time Domain to Frequency Domain: Scope



Spectrum of **square wave** from signal generator

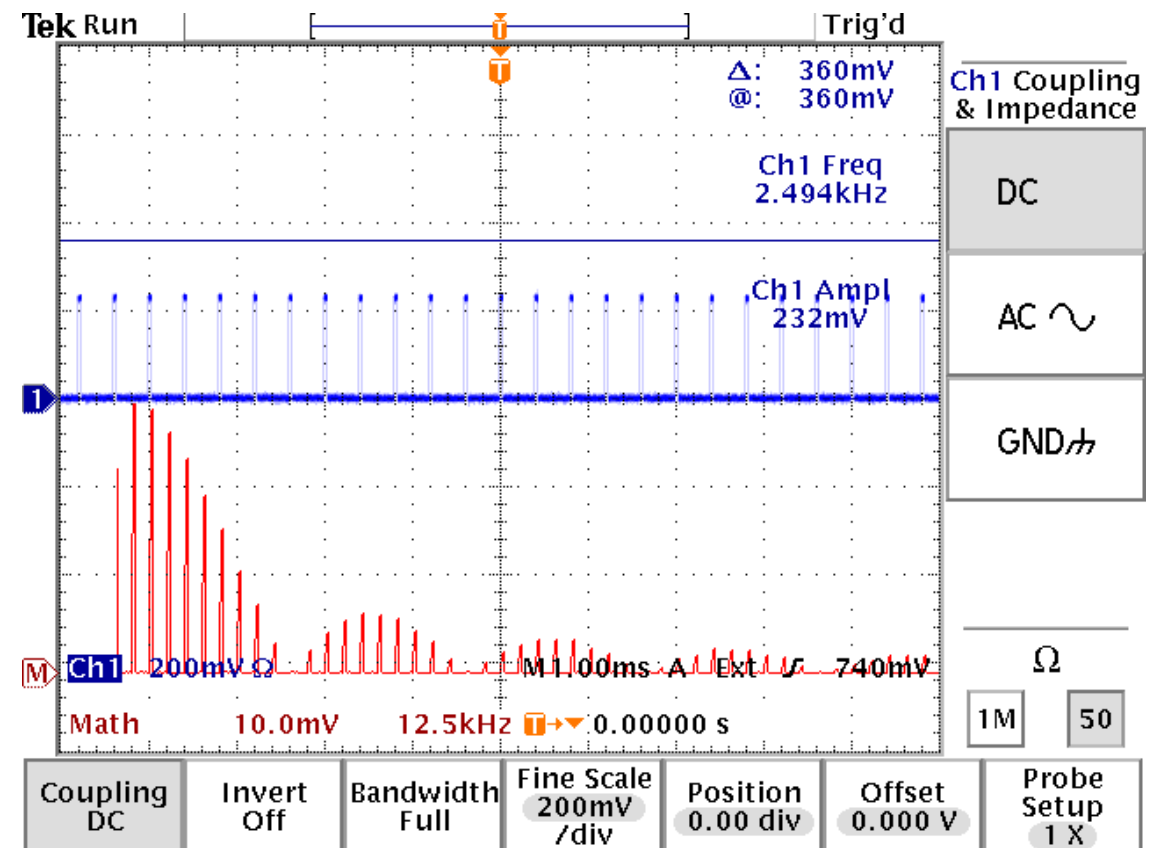Edit Math Definition
Set FFT Source to **Ch1**
Set FFT Vert Scale to **Linear RMS**
Set FFT Window to **Rectangular**






Spectrum of **pulse** from signal generator






From Time Domain to Frequency Domain: Lock-In

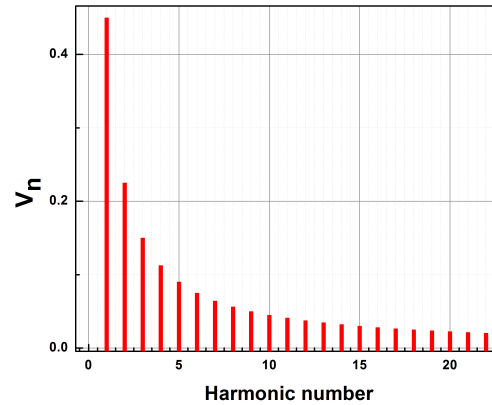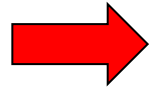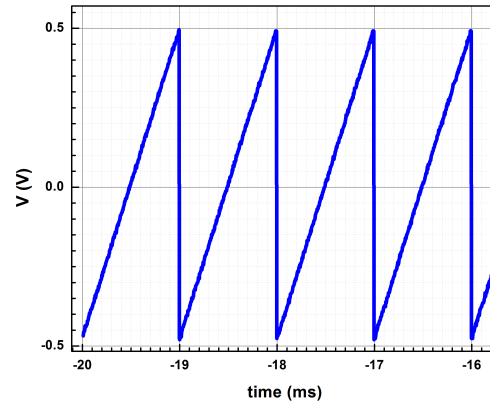Examining different pulse shapes on the SR830



Ramp

Pulse

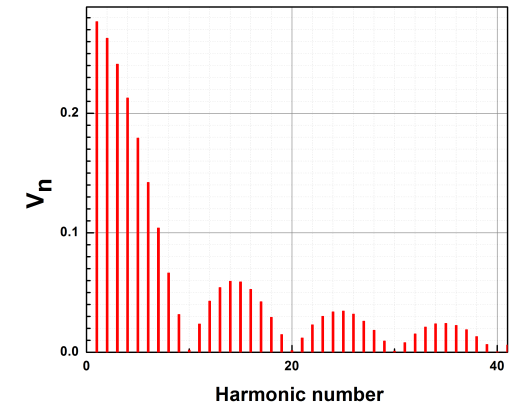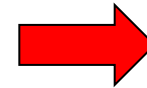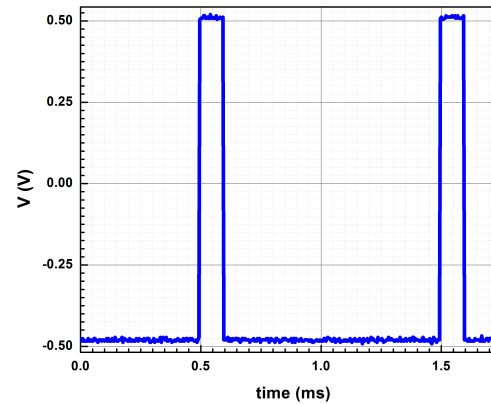

Appendix: References



1. John H. Scofield, “A Frequency-Domain Description of a Lock-in Amplifier” *American Journal of Physics* **62** (2), 129-133 (Feb. 1994). [link](#)
2. Steve Smith “The Scientist and Engineer's Guide to Digital Signal Processing” copyright ©1997-1998 by Steven W. Smith.

For more information visit the book's website at: www.DSPguide.com

You can also find an electronic copy of this book in:

<\\engr-file-03\PHYINST\APL Courses\PHYCS401\Experiments\DSP and FFT>

Appendix: Origin templates for this week's lab

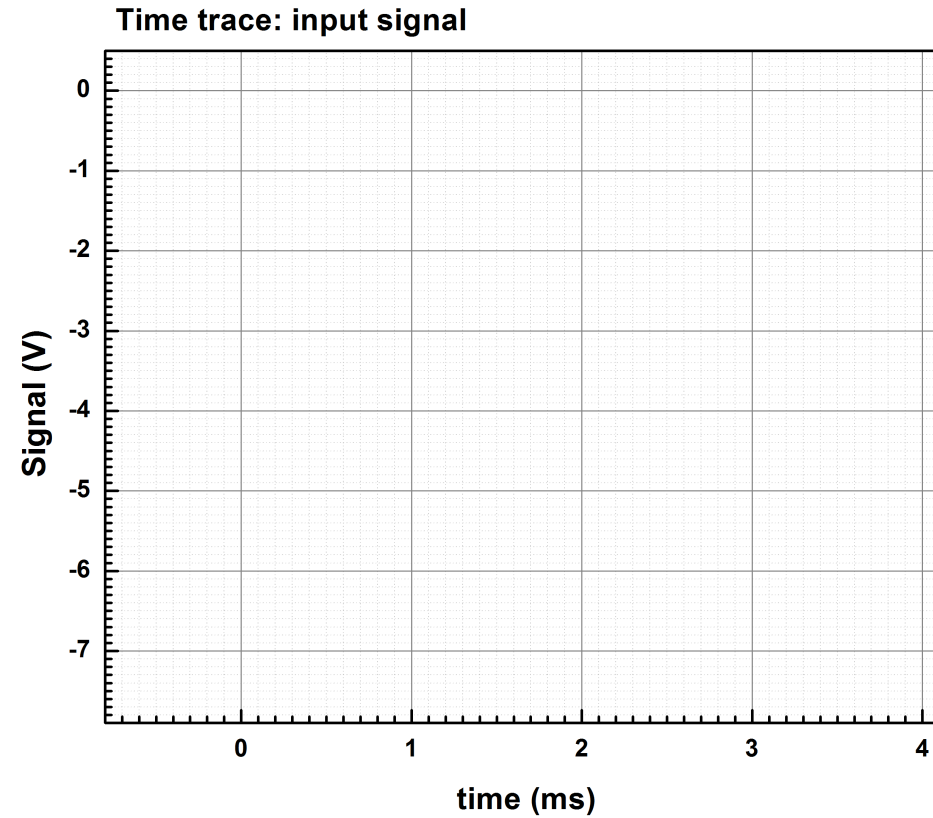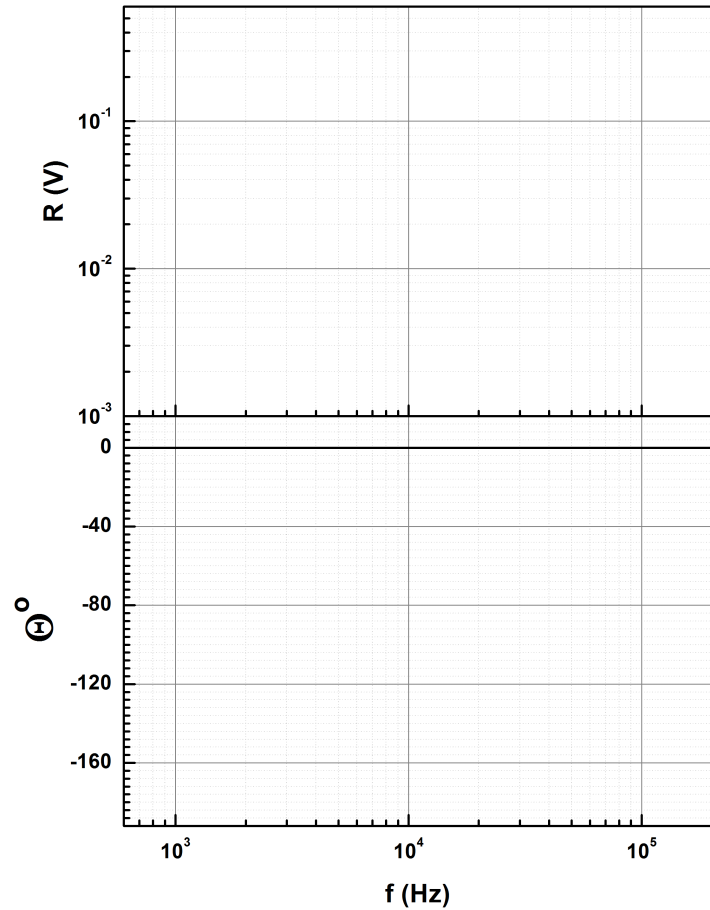

Physics401



Appendix: Using OriginPro for Fitting

Some recommendations for using the OriginPro nonlinear fitting option

You can find some examples of OriginPro projects and some recommendations of how to do the analysis in the following folder:

\\engr-file-03\PHYINST\APL Courses\PHYCS401\Students\3. Frequency Domain Experiment. Fitting

