



# Pulses in Transmission Lines

Professor Jeff Filippini

Physics 401

Spring 2020



# Key Concepts for this Lab

1. **Networks with distributed parameters**  
*What if the R/L/C are spread out?*  
*Thevenin-equivalent networks*
2. **Pulse propagation in transmission lines**  
*When signals move like waves*  
*Reflections from resistive and reactive loads*
3. **Impedance matching**  
*Getting power where you want it to go*



# When do Wires Carry Waves?

Thus far we've implicitly assumed that  $V(t)$  and  $I(t)$  are synchronized throughout our circuits – but signals travel at **finite speed** ( $v = c/n$ )!

- Speed of light:  $c = 3 \times 10^8$  m/s = 30 cm/ns = **1 ft/ns**  
*Real signals are typically slower by a factor ( $n$ ) of order unity*


Over distances that are a significant fraction of the **wavelength**, we're better off thinking of **wave propagation**

Frequency	Application	$n\lambda$
60 Hz	AC power lines	5000 km
580 kHz	WILL-AM broadcast	500 m (0.3 mile)
2.4 GHz	WiFi	12.5 cm (5 inches)
430 THz	Red light	0.7 $\mu\text{m}$
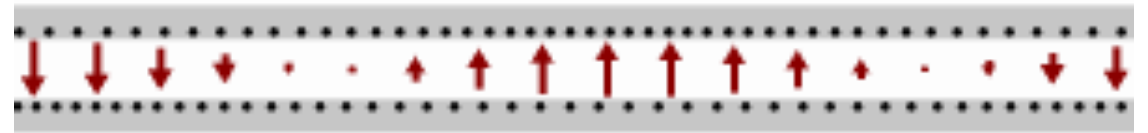
# Transmission Lines

**Transmission line:** a specialized cable (or other structure) designed to conduct alternating current of radio frequency (RF).


- Limit wave reflection by maintaining uniform impedance (*details below!*)
- Reduce power loss to radiation



[Wikipedia: Transmission Line](#)

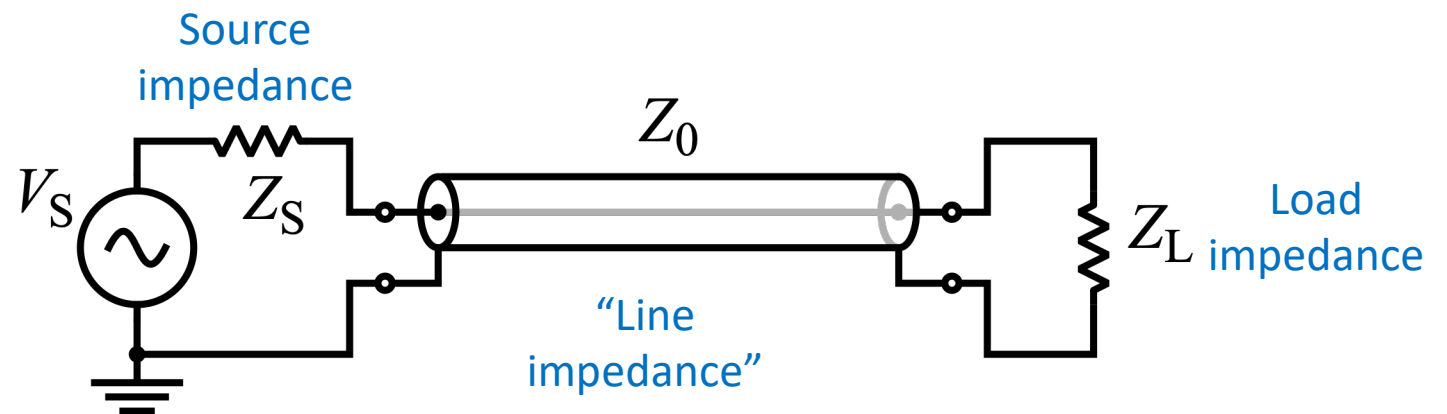
## Design goal:

Maximize power from the source delivered to the load





# Common Types of Transmission Lines

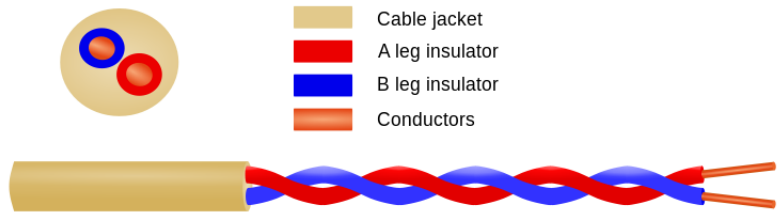


**Twisted pair**  
*Wikipedia*



**Twin lead**  
*Wikipedia*




**Coaxial cable**

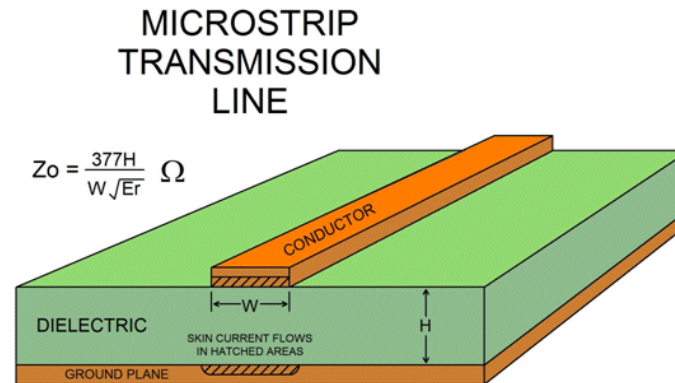

*Analog Devices*

# Coaxial Cable

Coaxial Cable Structure Figure

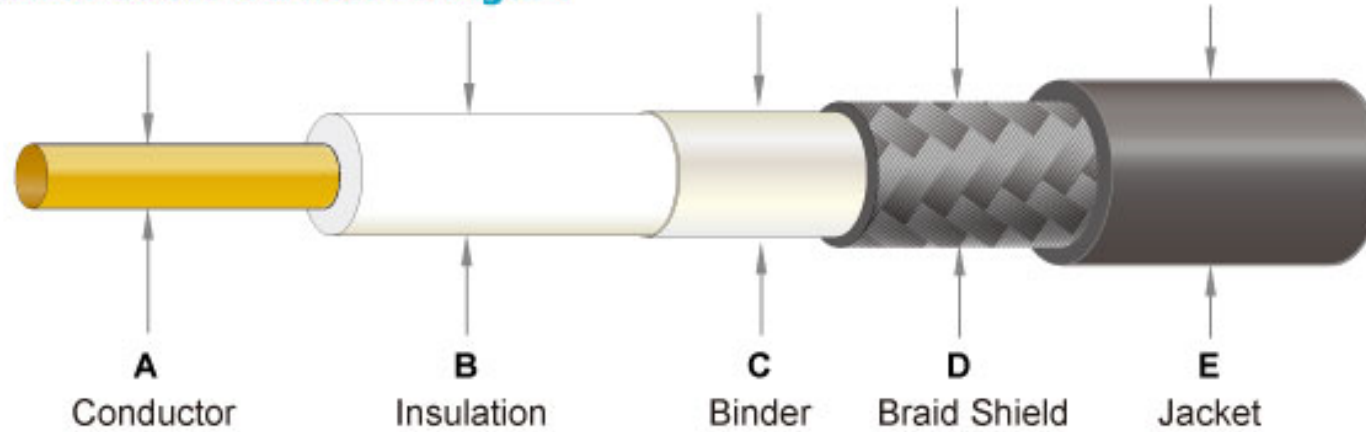

Copyright © 2010 Wellshow Technology. All rights reserved

**Specification:**

**Impedance:  $53 \Omega$**


**Capacitance:  $83 \text{ pF/m}$**

**Conductor: Bare Copper Wire (1/1.02mm)**

Signal voltage between central conductor and braid shield



Shield reduces external dipole radiation (and response to RF interference)

# Experimental Setup

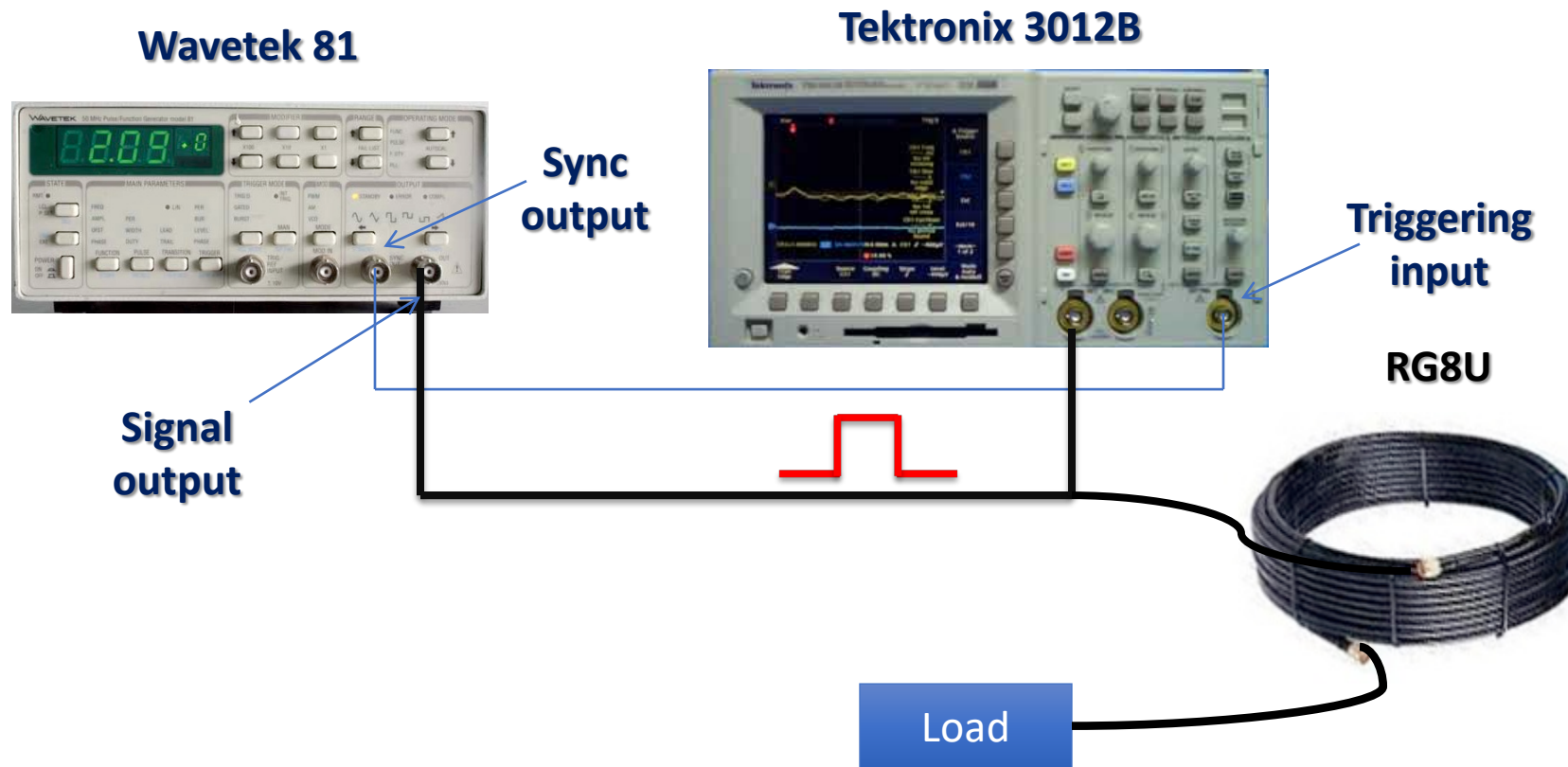


# Modeling a Transmission Line

Simplified equivalent circuit

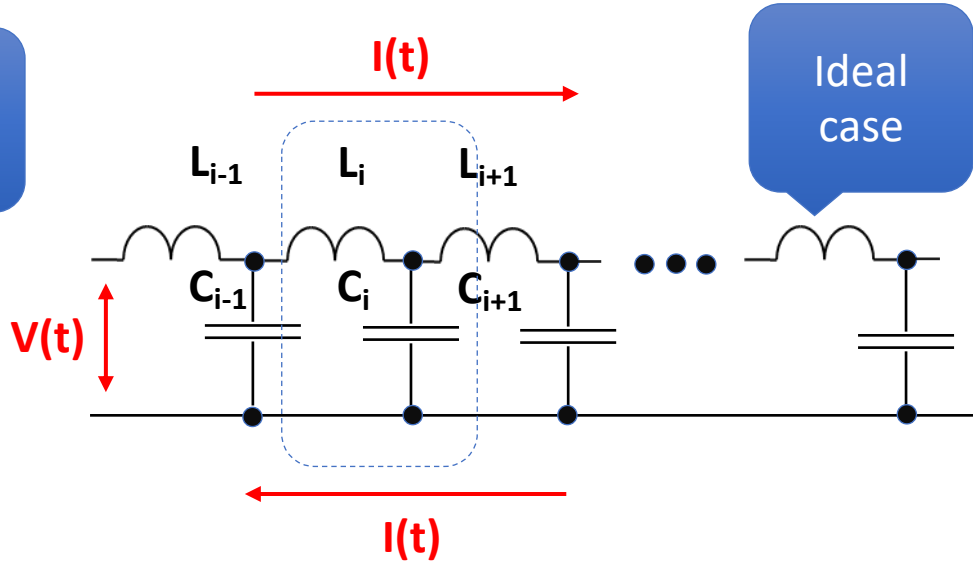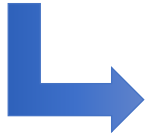

Real situation

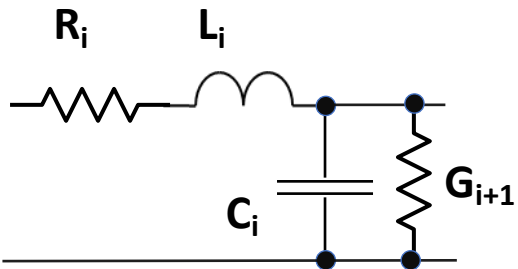


Model as **distributed network** rather than lumped components

**Ideal** line has inductance / capacitance per unit length (lossless)


**Real** lines have finite conductance  $G = \frac{1}{R}$  between conductors (*i.e.* loss)



# Pulses in Transmission Lines

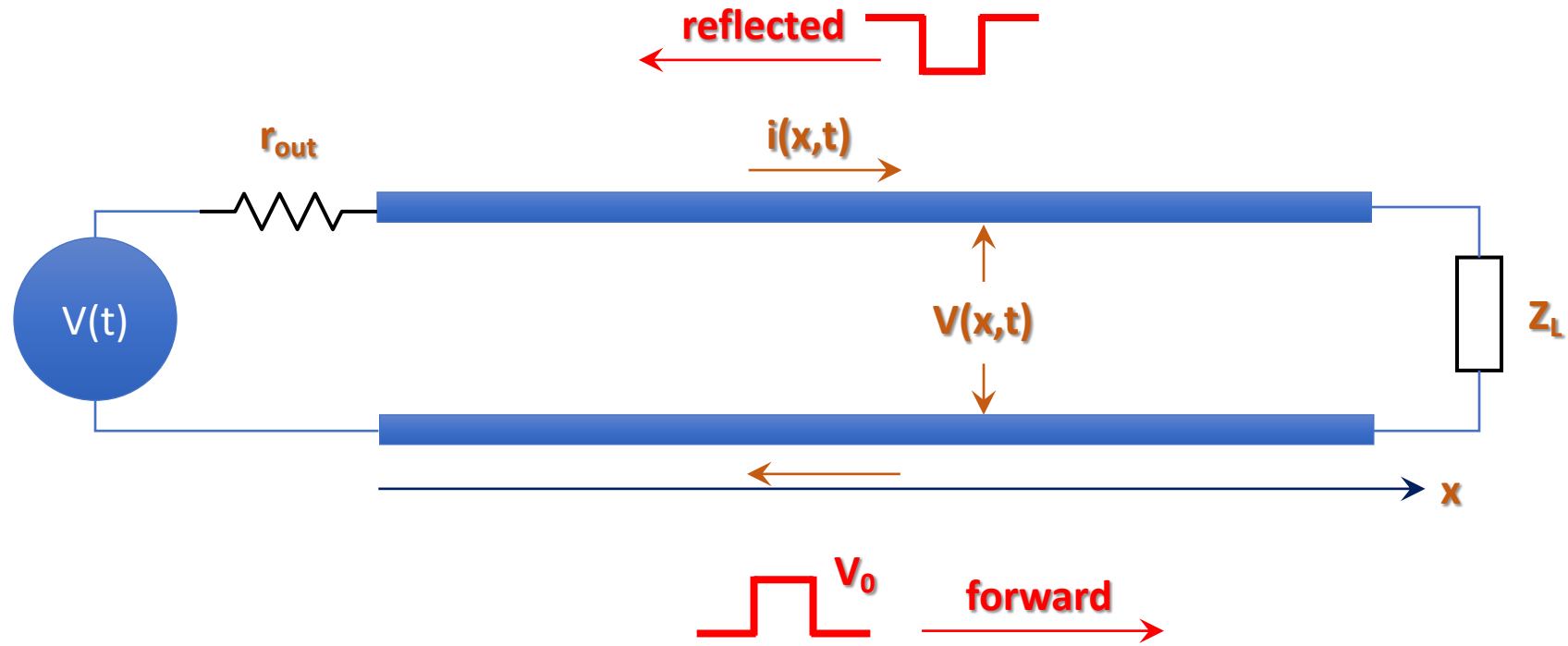

# The Telegrapher's Equations

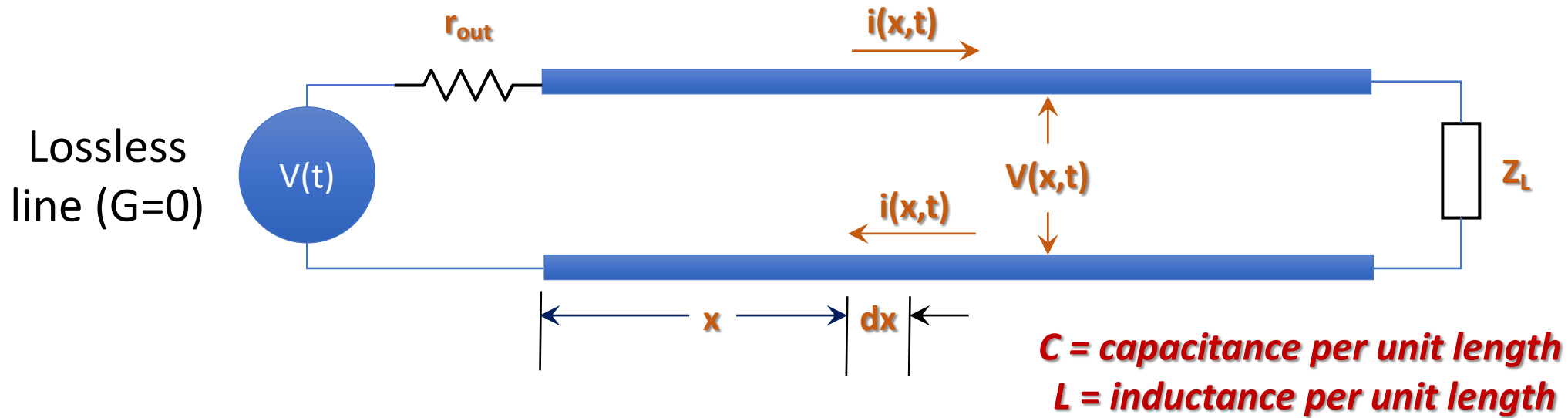

## Distributed capacitance

$$(C \, dx)V = -dq$$

$$(C \, dx) \frac{\partial V}{\partial t} = -\frac{\partial q}{\partial t} = -I$$

$$C \frac{\partial V}{\partial t} = -\frac{\partial I}{\partial x}$$

## Distributed inductance


$$dV = -(L \, dx) \frac{\partial I}{\partial t}$$

$$\frac{\partial V}{\partial x} = -L \frac{\partial I}{\partial t}$$
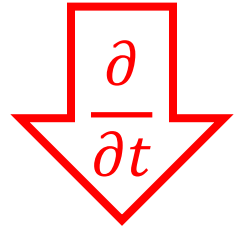
# The Wave Equation

Distributed capacitance


$$C \frac{\partial V}{\partial t} = - \frac{\partial I}{\partial x}$$



$$\frac{\partial^2 I}{\partial x \partial t} = -C \frac{\partial^2 V}{\partial t^2}$$

Distributed inductance
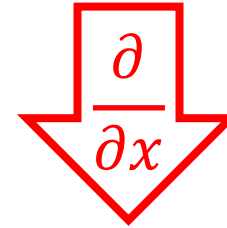
$$\frac{\partial V}{\partial x} = -L \frac{\partial I}{\partial t}$$



$$\frac{\partial^2 V}{\partial x^2} = -L \frac{\partial^2 I}{\partial x \partial t}$$

Combining

$$\frac{\partial^2 V}{\partial x^2} = LC \frac{\partial^2 V}{\partial t^2}$$

$$\frac{\partial^2 I}{\partial x^2} = LC \frac{\partial^2 I}{\partial t^2}$$

# Voltage and Current Waves

$$\frac{\partial^2 V}{\partial x^2} = LC \frac{\partial^2 V}{\partial t^2} \quad \frac{\partial^2 I}{\partial x^2} = LC \frac{\partial^2 I}{\partial t^2}$$

Seek solutions  
of the form...

Waves of velocity  $v$

$$V(x, t) = V_0 \sin \omega \left( t - \frac{x}{v} \right)$$
$$I(x, t) = I_0 \sin \omega \left( t - \frac{x}{v} \right)$$

Substitute  $V(x, t)$ ,  $I(x, t)$  into...

$$C \frac{\partial V}{\partial t} = - \frac{\partial I}{\partial x} \quad \frac{\partial V}{\partial x} = -L \frac{\partial I}{\partial t}$$

... to find two key consequences:

1.

$$v = \frac{1}{\sqrt{LC}}$$

Speed of wave propagation

2.

$$Z_k \equiv \frac{V(x, t)}{I(x, t)} = \sqrt{\frac{L}{C}}$$

Characteristic impedance of line




# Characteristic Impedance

$$Z_k = \sqrt{\frac{L}{C}}$$

$C$  = capacitance per unit length ( $F/m$ )

$L$  = inductance per unit length ( $H/m$ )
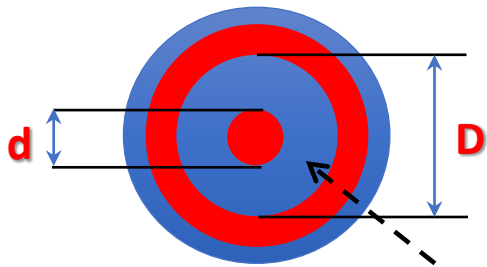
$$\begin{aligned}\epsilon_0 &= 8.854 \times 10^{-12} \text{ F/m} \\ \mu_0 &= 4\pi \times 10^{-7} \text{ H/m} \\ \epsilon_0 \mu_0 &= c^2\end{aligned}$$



$$C = \frac{2\pi\epsilon_0\epsilon_r}{\ln\left(\frac{D}{d}\right)} \text{ (F/m)}$$

$$L = \frac{\mu_0\mu_r}{2\pi} \ln\left(\frac{D}{d}\right) \text{ (H/m)}$$

$\epsilon_r$  – dielectric permittivity  
 $\mu_r$  – magnetic permeability  $\approx 1$


Finally for coaxial cable:  $Z_k = \frac{138}{\sqrt{\epsilon_r}} \log_{10}\left(\frac{D}{d}\right) \text{ (Ohms)}$

# Wave Propagation Speed

$$v = \frac{1}{\sqrt{LC}}$$

$$C = \frac{2\pi\epsilon_0\epsilon_r}{\ln\left(\frac{D}{d}\right)} \quad L = \frac{\mu_0\mu_r}{2\pi} \ln\left(\frac{D}{d}\right)$$
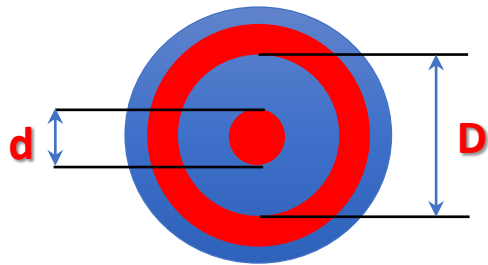
$$\begin{aligned}\epsilon_0 &= 8.854 \times 10^{-12} \text{ F/m} \\ \mu_0 &= 4\pi \times 10^{-7} \text{ H/m} \\ \epsilon_0\mu_0 &= c^2\end{aligned}$$



$$v = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{\mu_0\mu_r\epsilon_0\epsilon_r}} = \frac{c}{\sqrt{\mu_r\epsilon_r}} \approx \frac{c}{\sqrt{\epsilon_r}}$$

The **delay time** of a signal is  $\tau = \frac{1}{v}$  (s/m)  $\approx 3.336\sqrt{\epsilon_r}$  ns/m

**RG-8/U**  
**RG58U**

Inner insulation material: Polyethylene


*For polyethylene below 1 GHz,  $\epsilon_r \approx 2.25$*

Nominal impedance: 52 ohm


Delay time:  $\sim 5$  ns/m (speed  $\sim 2/3c$ )

# Reflection in Transmission Lines

[Wikipedia: Reflection Coefficient](#)

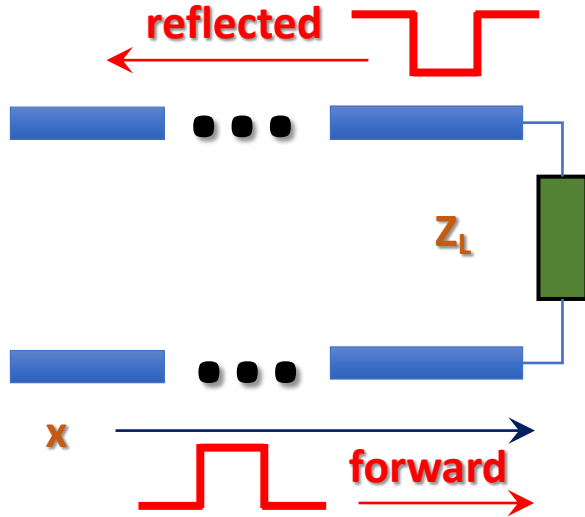

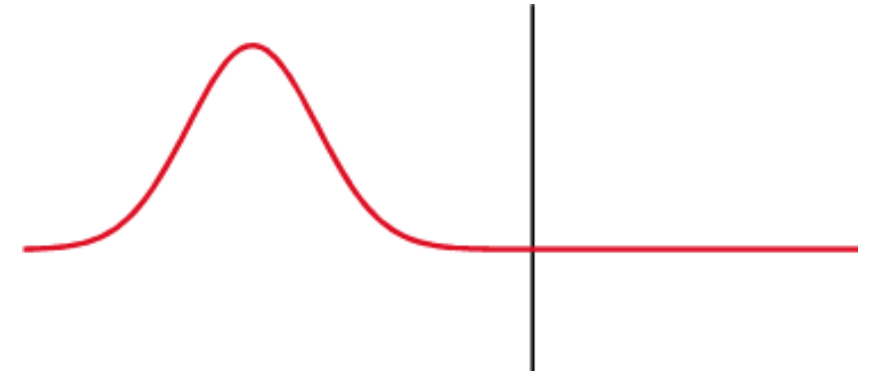Any wave will be (partially) **reflected** when it reaches a change in impedance



Forward wave

$$V(x, t) = V_0 \sin \omega \left( t - \frac{x}{v} \right)$$

$$I(x, t) = I_0 \sin \omega \left( t - \frac{x}{v} \right)$$

$$V(x, t) = Z_k I(x, t)$$

Reflected wave

$$V_r(x, t) = V_r \sin \omega \left( t + \frac{x}{v} \right)$$


$$I_r(x, t) = I_r \sin \omega \left( t + \frac{x}{v} \right)$$

$$V_r(x, t) = -Z_k I_r(x, t)$$

At Load

$$V(t) = Z_L I(t)$$

# Reflection in Transmission Lines

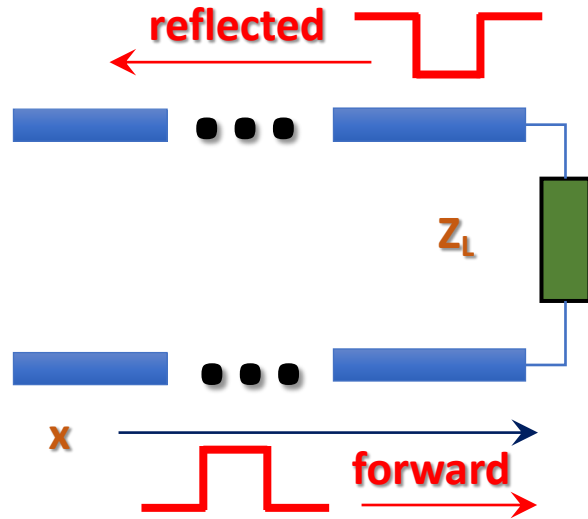

At Load

$$V = Z_L I$$

Anywhere in Transmission Line

$$V_i = Z_k I_i$$

$$V_r = -Z_k I_r$$

Match at the boundary

$$V = V_r + V_i$$

$$I = I_r + I_i = \frac{V_i}{Z_k} - \frac{V_r}{Z_k}$$



$$\frac{V_i + V_r}{V_i - V_r} = \frac{Z_L}{Z_k} \quad \text{or} \quad V_r = \frac{Z_L - Z_k}{Z_L + Z_k} V_i$$
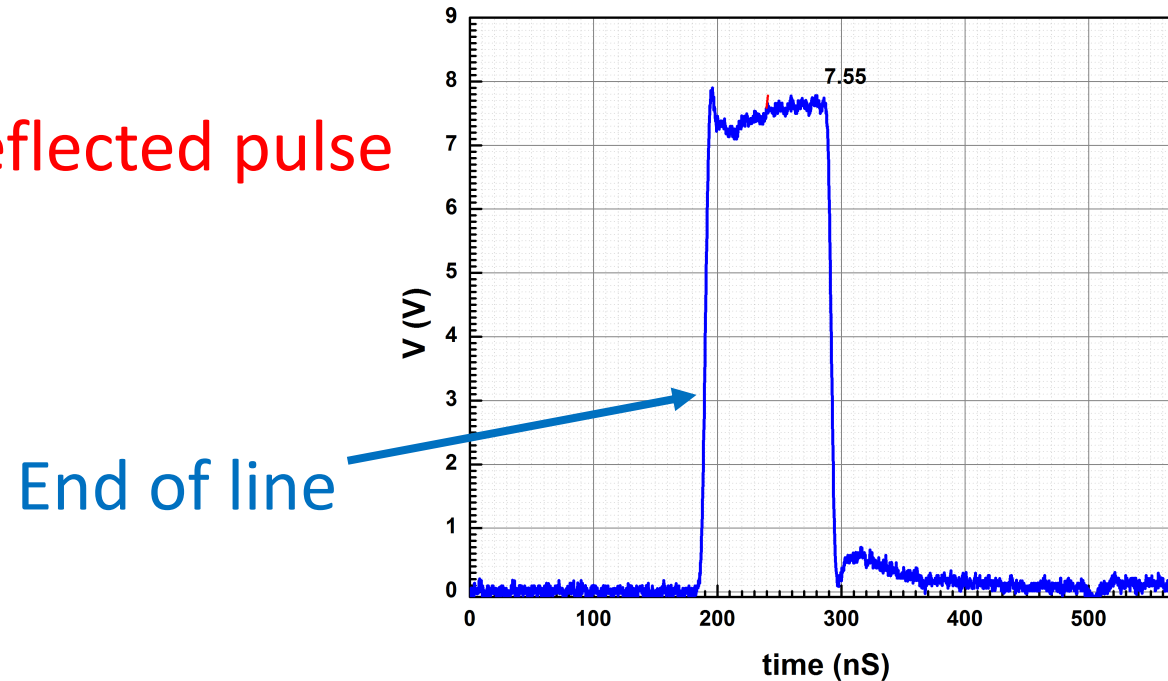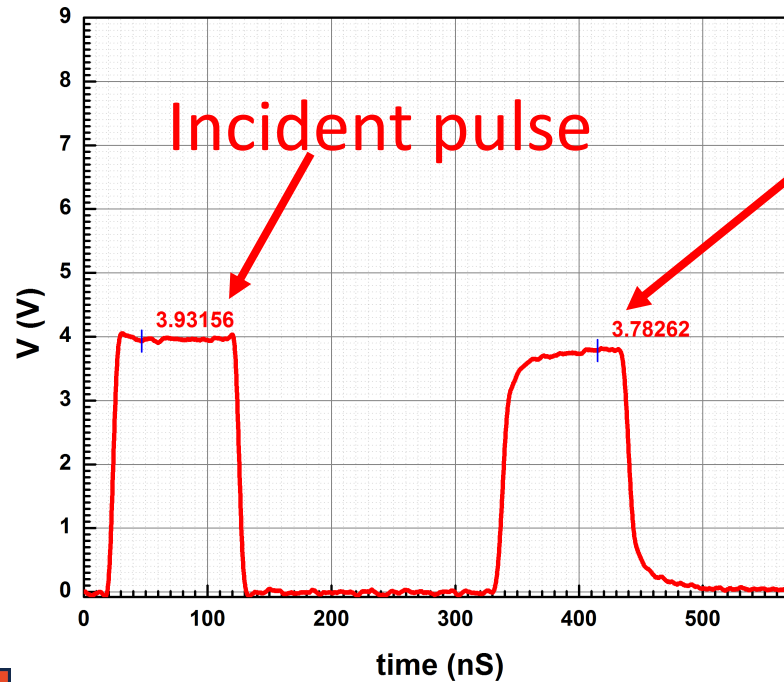
# Reflection from an Open Transmission Line



$$\frac{V_i + V_r}{V_i - V_r} = \frac{Z_L}{Z_k} \quad \text{or} \quad V_r = \frac{Z_L - Z_k}{Z_L + Z_k} V_i$$


Open line:  $Z_L = \infty \Rightarrow V_r = V_i$ , and voltage at load  $V_L = V_i + V_r = 2V_i$




# Transmission Line Losses

Why is the reflected pulse *smaller*?

Experiment: RG 58U

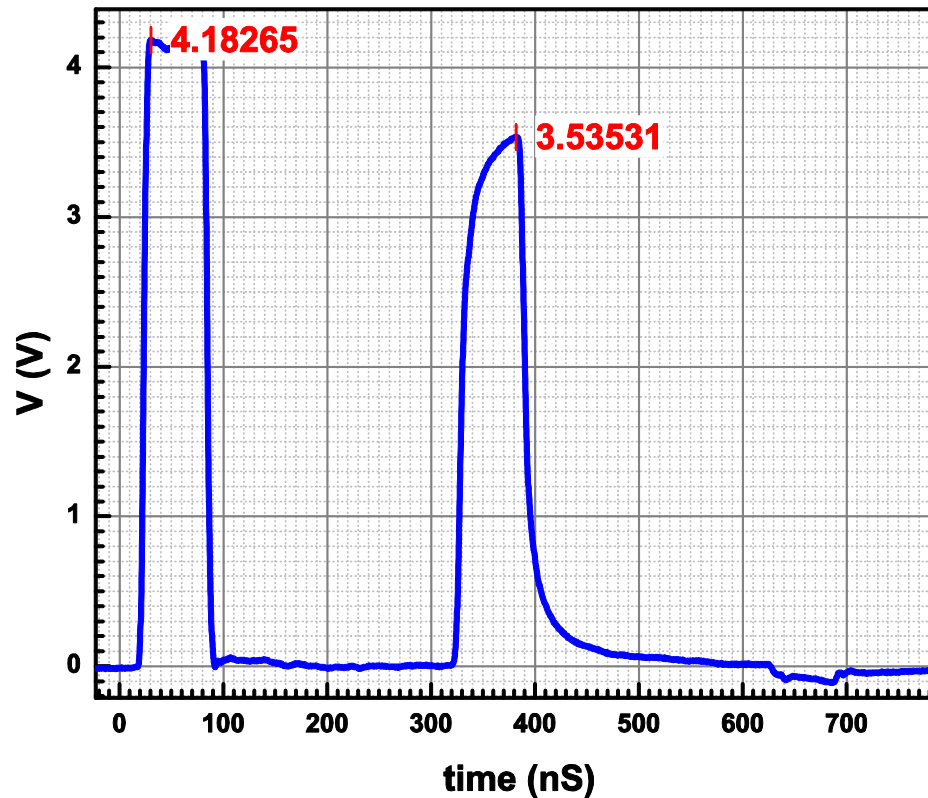

	Attenuation (dB per 100 ft)				
MHz	30	50	100	146	150
RG-58U	2.5	4.1	5.3	6.1	6.1

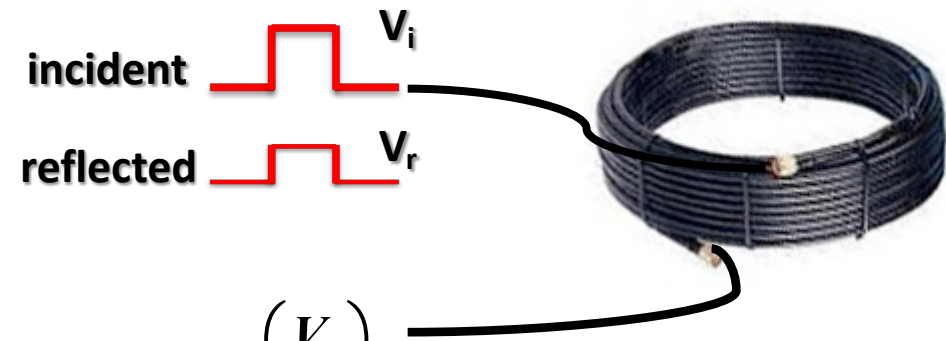


$$ATTN(db) = 20 \log \left( \frac{V_i}{V_r} \right)$$

Cable characterized by **attenuation per unit length**  
*This is slowly frequency dependent!*



# Reminder: Units of Ratio

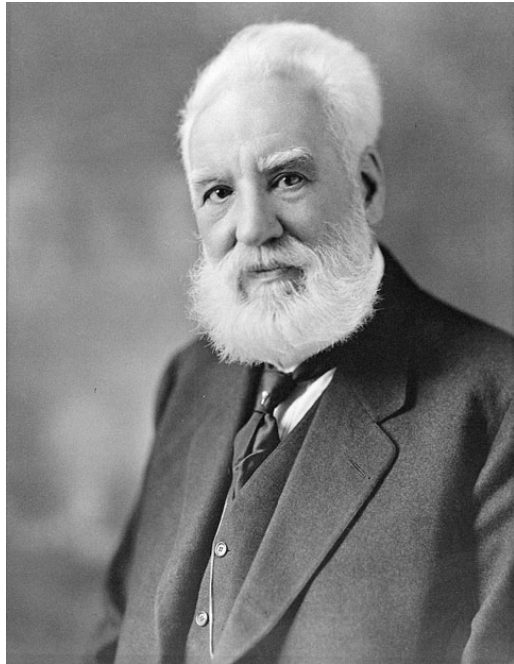

Alexander Graham Bell  
(1847 – 1922)

We can compare the **relative strength** of two signals by taking the **logarithm** (base-10) of the ratio of their **powers**. This (rarely used) unit was named a **bel**, after A.G. Bell.

We more commonly use the **decibel (dB)**, 1/10<sup>th</sup> of a bel

$$L[dB] = 10 \log_{10} \left( \frac{P_1}{P_2} \right) \quad \text{Power ratio}$$

$$L[dB] = 20 \log_{10} \left( \frac{V_1}{V_2} \right) \quad \text{Voltage ratio}$$

*or current, field, ...*


Ex: -3 dB = ½ power; -20 dB = 1/100 power (1/10 voltage)

Related units: **dBm** = dB relative to 1 mW (absolute unit)

**Neper (Np)** = like a bel, but natural log (ln)

# Transmission Line Losses


Experiment: RG 58U

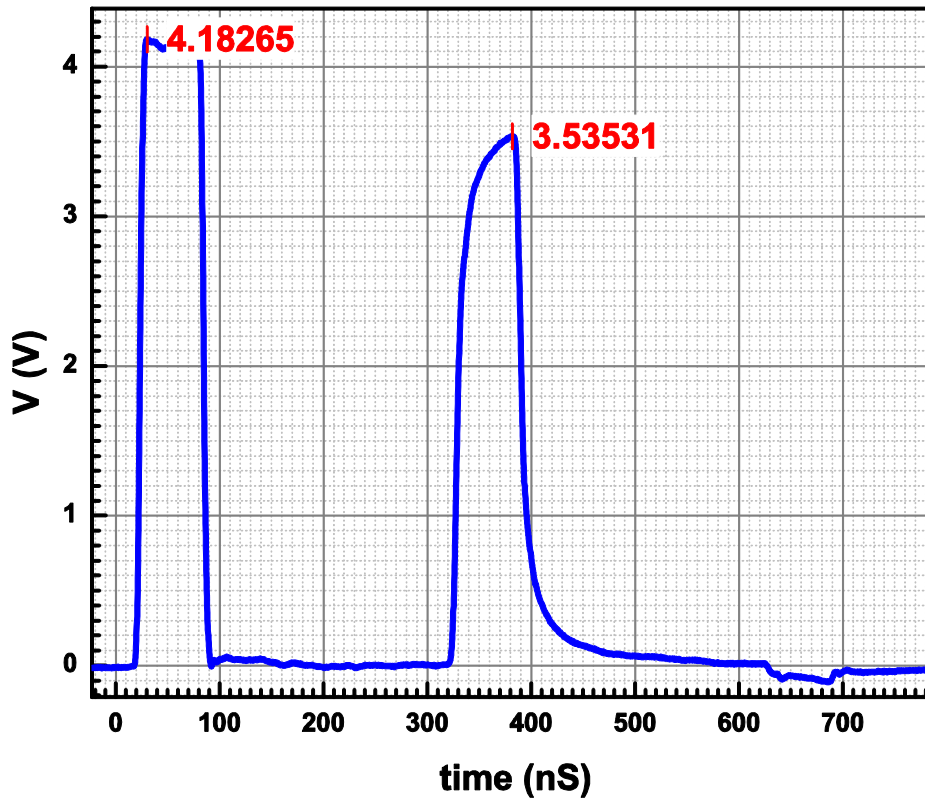

In our case:


$$\text{Attn}(200\text{ft}) = 20 \log \left( \frac{4.18}{3.54} \right) \approx 1.46 \text{ dB}$$

*Where does it come from?*

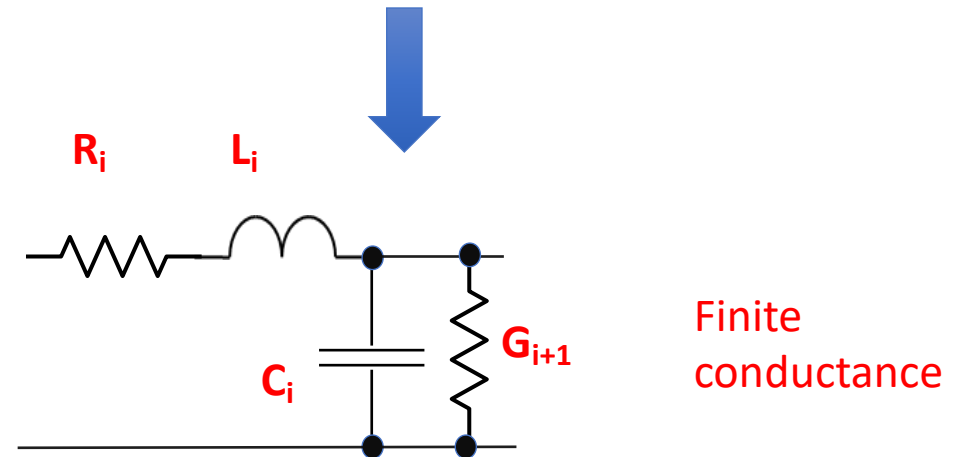




# Losses in Different Cables

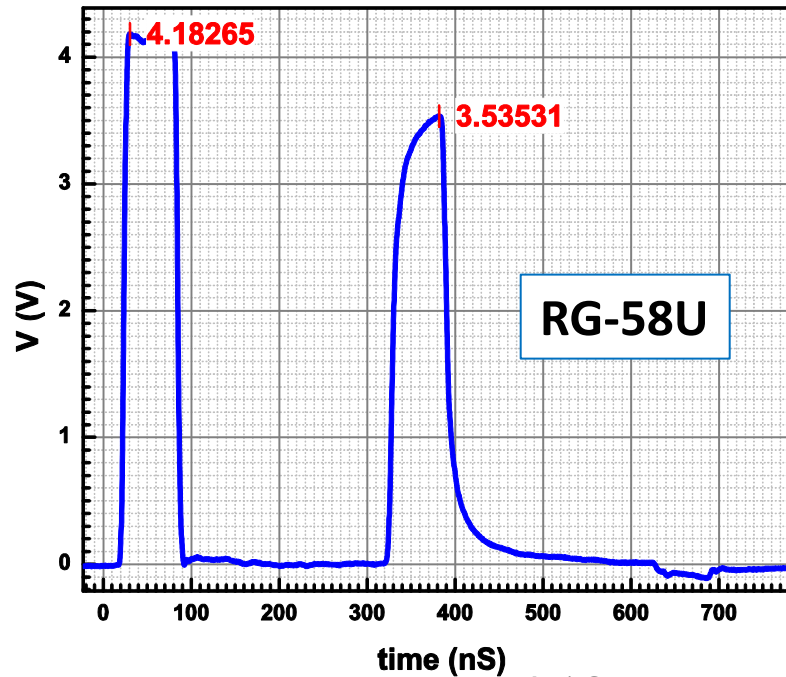


$$\text{Attn}(200\text{ft}) = 20 \log \left( \frac{4.18}{3.54} \right) \approx 1.46 \text{ dB}$$

Core  $\phi=0.81 \text{ mm}$

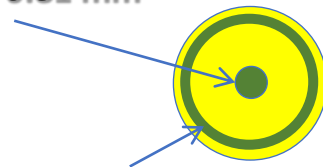


Dielectric  $\phi=2.9 \text{ mm}$

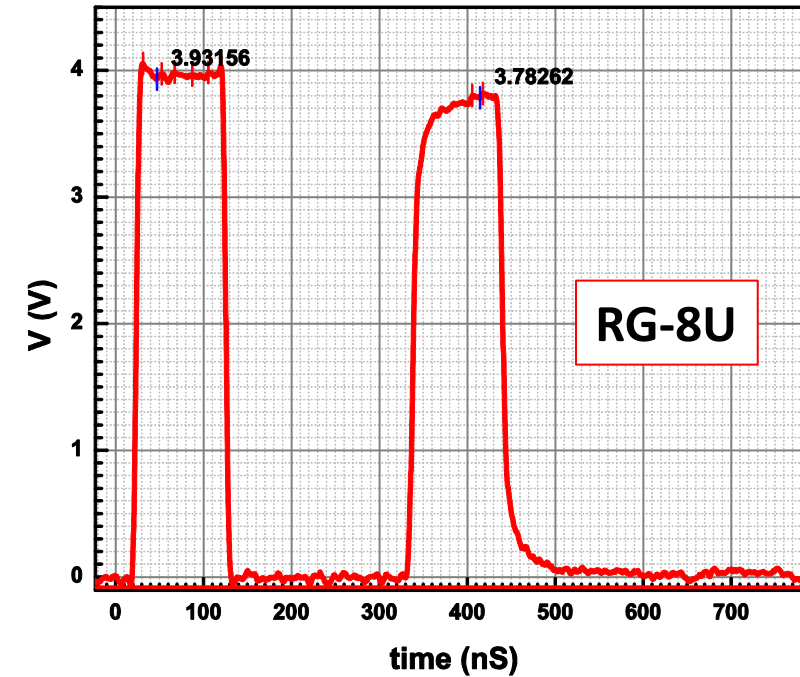


$$\text{Attn}(200\text{ft}) = 20 \log \left( \frac{3.932}{3.78} \right) \approx 0.335 \text{ dB}$$

Core  $\phi=2.17 \text{ mm}$

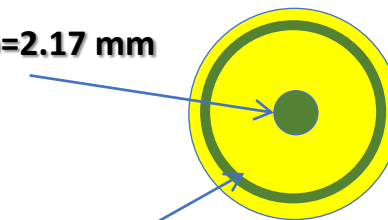


Dielectric  $\phi=7.2 \text{ mm}$

# Frequency-Dependent Transmission

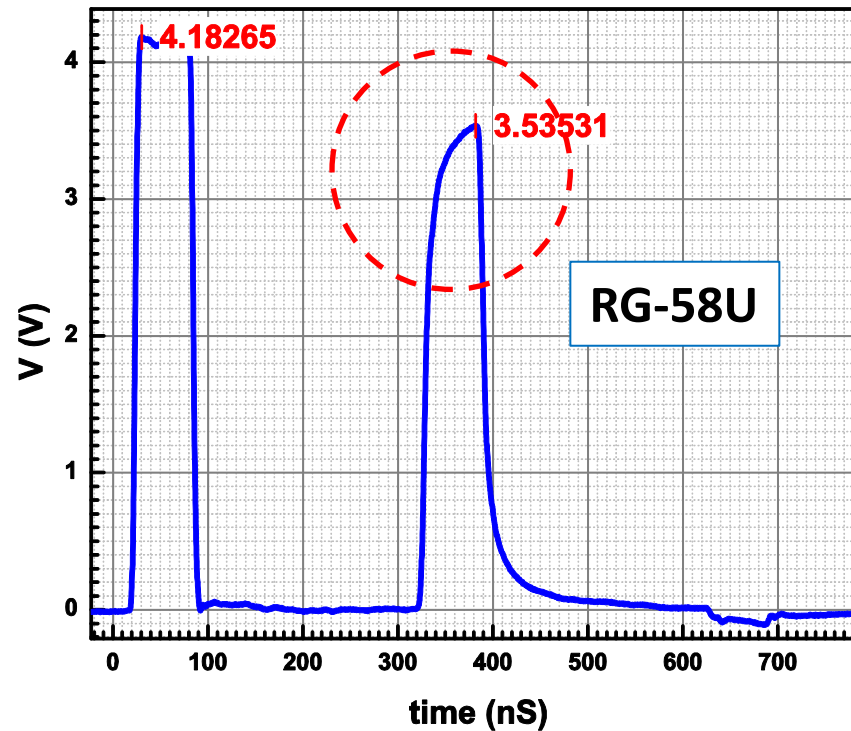


Why is the reflected pulse **distorted** relative to the incident pulse?

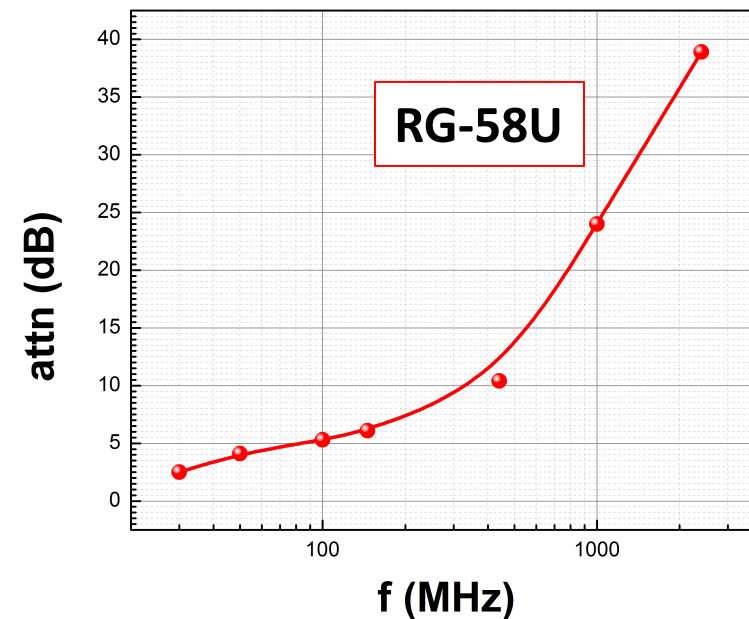
1. **Loss:** Attenuation is frequency-dependent
2. **Dispersion:** Delay (i.e. speed) depends on frequency



# Frequency-Dependent Loss Example

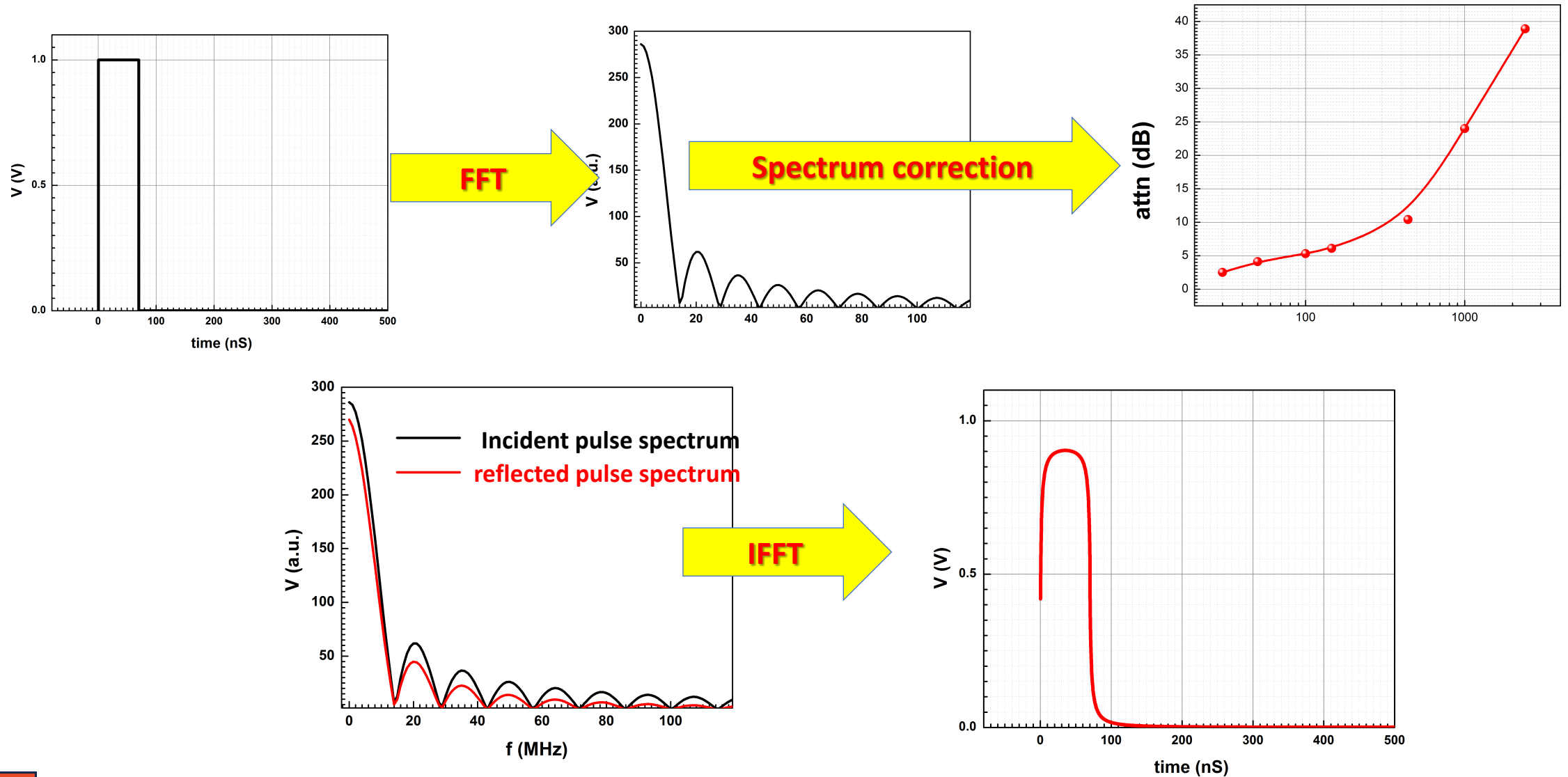

# Reflection from a Resistive Load

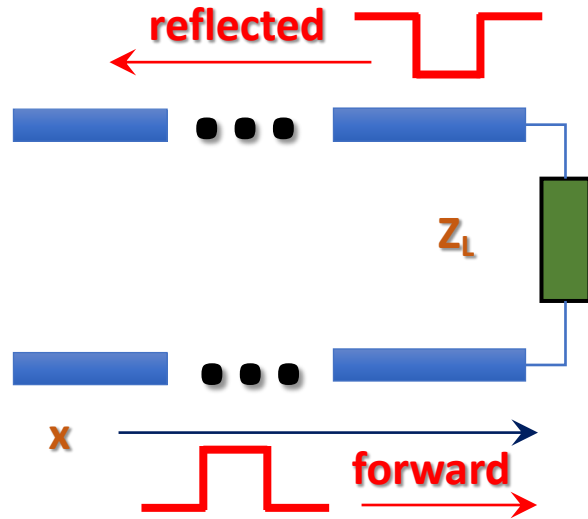

$$Z_L = R_L$$


$$\frac{V_i + V_r}{V_i - V_r} = \frac{Z_L}{Z_k} \quad \text{or} \quad V_r = \frac{Z_L - Z_k}{Z_L + Z_k} V_i$$

**Shorted line**

$$R_L = 0 \implies V_r = -V_i$$

Incident pulse




Reflected pulse

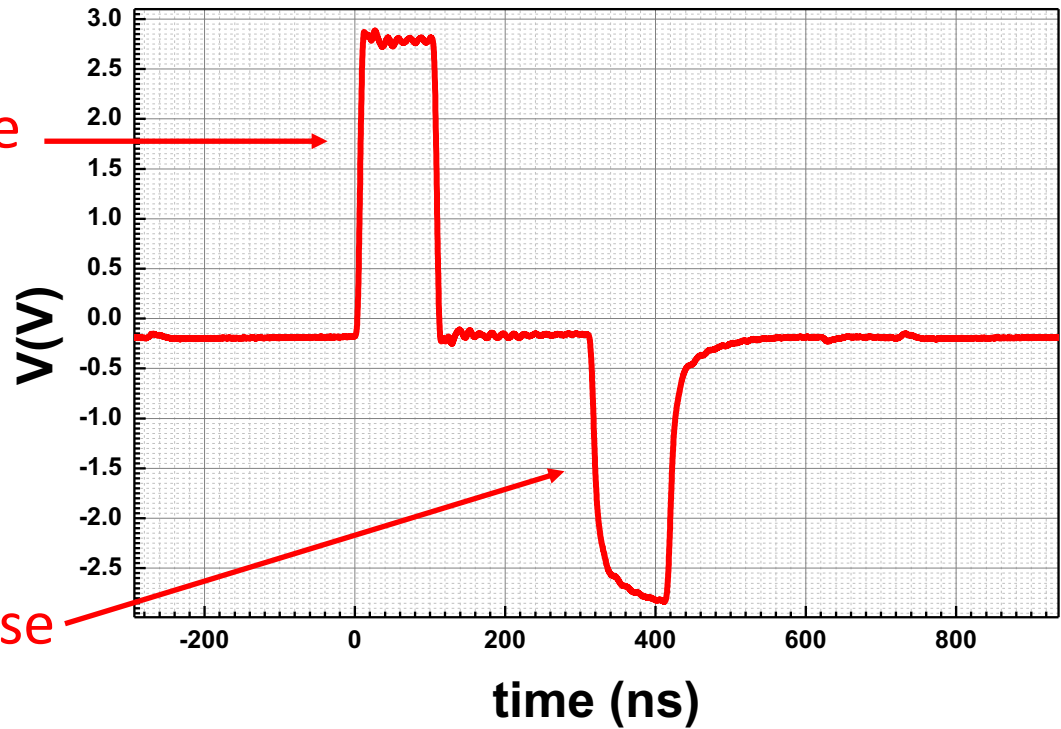
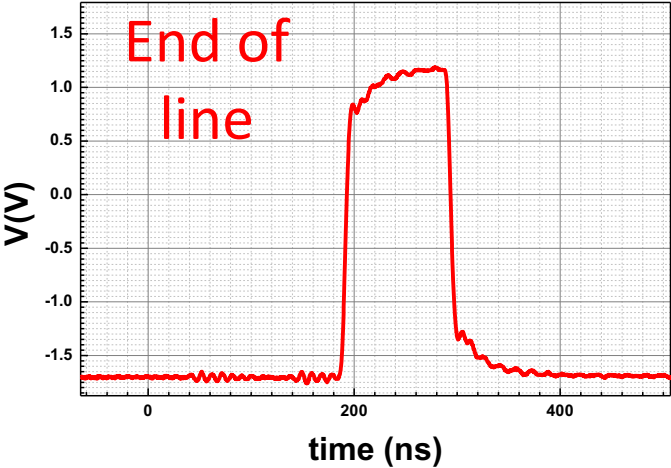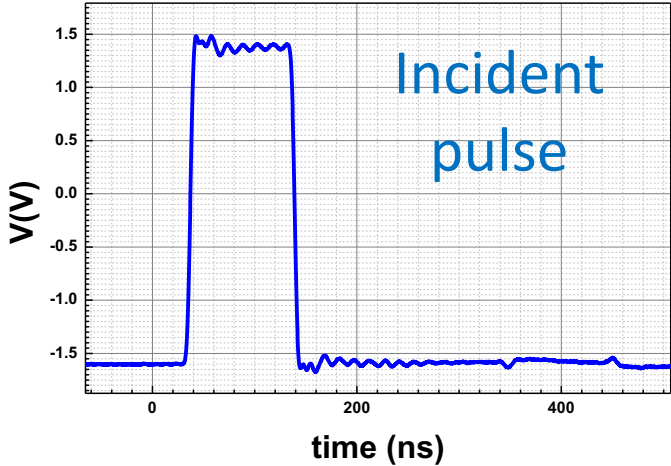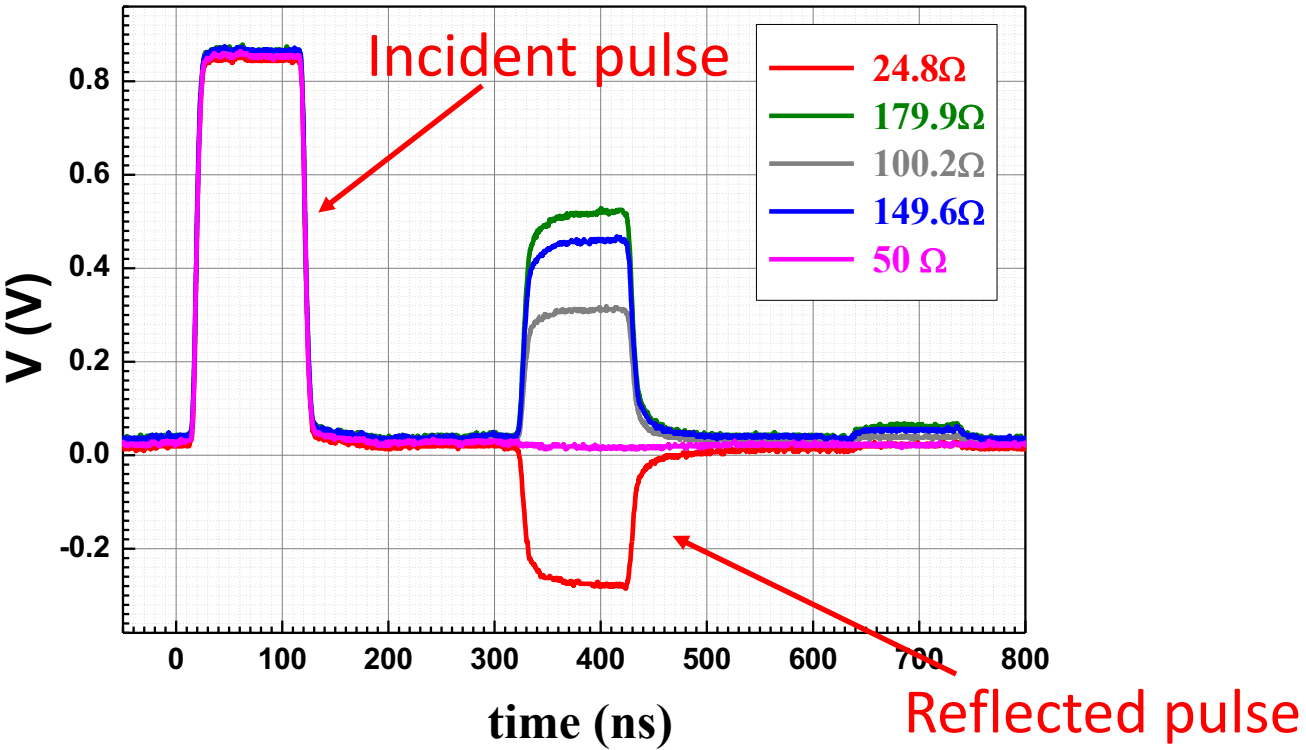
# Reflection from a Resistive Load

$$\frac{V_i + V_r}{V_i - V_r} = \frac{Z_L}{Z_k} \quad \text{or} \quad V_r = \frac{Z_L - Z_k}{Z_L + Z_k} V_i$$

**Matched Impedance**  
 $R_L = Z_k \implies V_r = 0$



# Thevenin's Theorem: Simplifying Networks




Hermann Ludwig  
Ferdinand von Helmholtz  
(1821-1894)

Any combination of **voltage sources** and **resistive/reactive impedances** with two terminals (“**linear one-port network**”) can be replaced by an equivalent single **voltage source** and **series impedance**.



Léon Charles Thévenin  
(1857–1926)

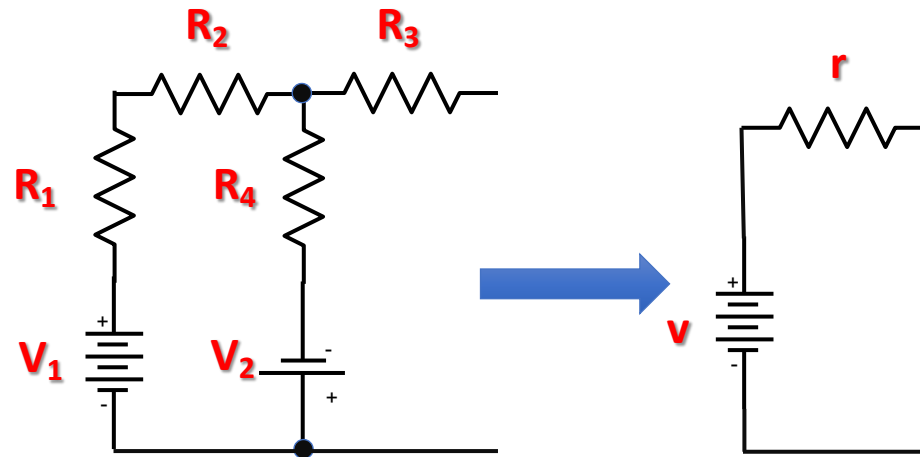

**N.B.** replacement is exactly equivalent from the **load's** point of view, but e.g. internal power dissipation in the equivalent network may differ




# Thevenin's Theorem and Transmission Lines
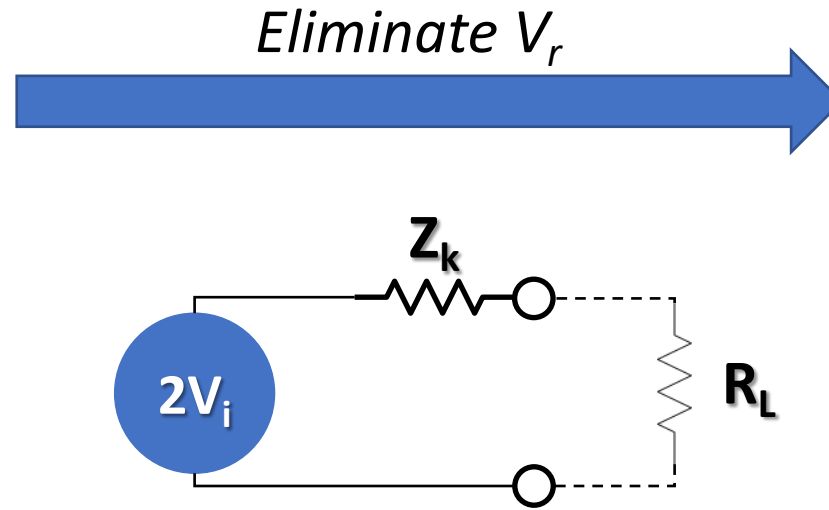
## Conditions at the Load

$$V = V_r + V_i = I R_L$$

$$I = I_r + I_i = \frac{V_i}{Z_k} - \frac{V_r}{Z_k}$$



$$I = \frac{2V_i}{Z_L + Z_k}$$

From this equivalent circuit we can find the maximum possible **power delivered** to the load:

$$P = I^2 R_L = \frac{(2V_i)^2}{(R_L + Z_k)^2} R_L$$

$$P = \frac{(2V_i)^2}{R_L \left( 1 + \left( \frac{Z_k}{R_L} \right)^2 \right)^2}$$



### Matched Impedance

$P = P_{\max}$  if  $R_L = Z_k$   
(i.e. no reflection!)



# Thevenin's Theorem - Experiment

## RG-8U

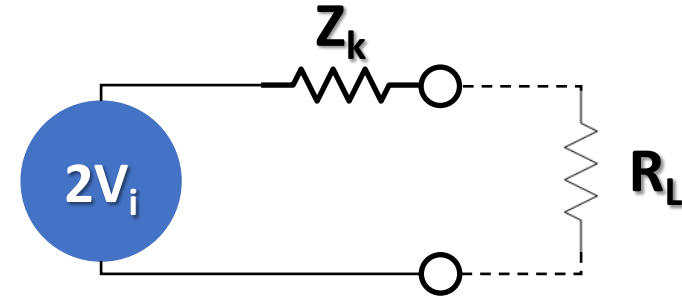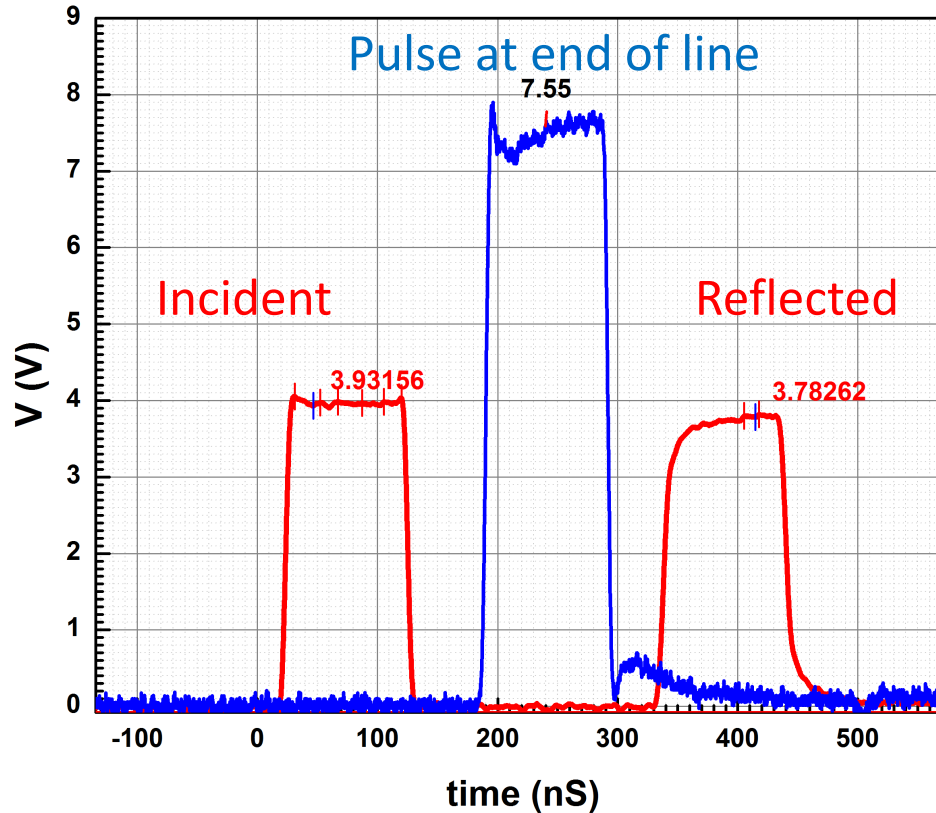

This experiment works best when performed with RG-8U cable due to its lower attenuation

When  $R_L = \infty$  (open line) the pulse amplitude at line's end is expected to be  $2V_i$ , where  $V_i$  is the amplitude of the incident pulse




# Reflection from a Capacitive Load

$$I = \frac{2V_i}{Z_L + Z_k}$$



$$\tau = Z_k C$$
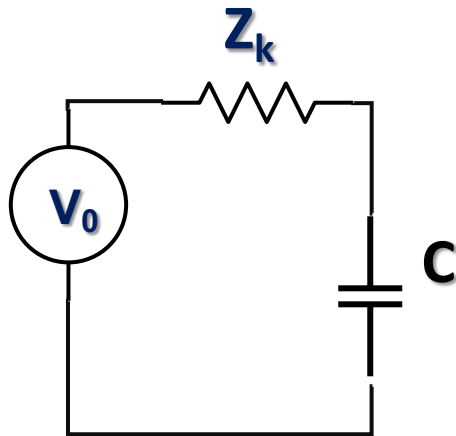
$$C = \frac{\tau}{Z_k} \approx 3.2 \text{ nF}$$




$$V_L = [1 - e^{-t/\tau}]$$
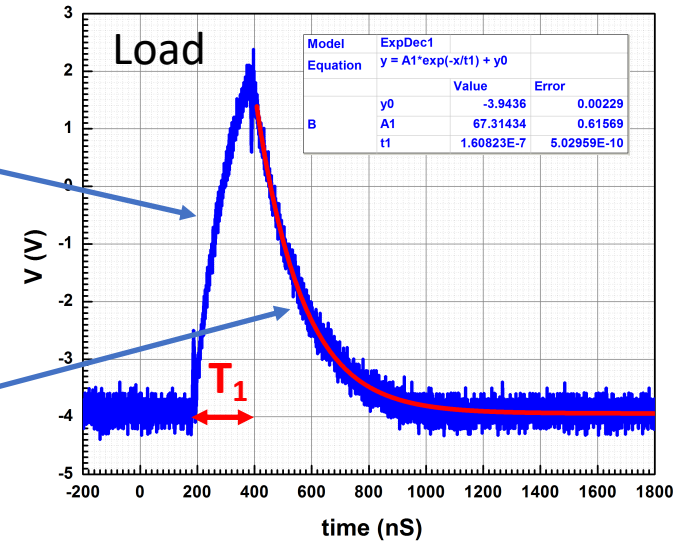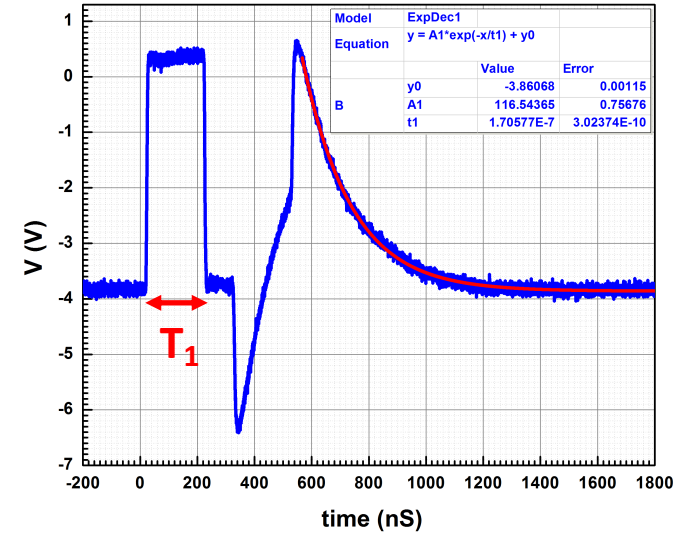
$$V_L = 2V_i [1 - e^{-T_1/\tau}] [1 - e^{-(t-T_1)/\tau}]$$



# Reflection from an Inductive Load

$$I = \frac{2V_i}{Z_L + Z_k}$$


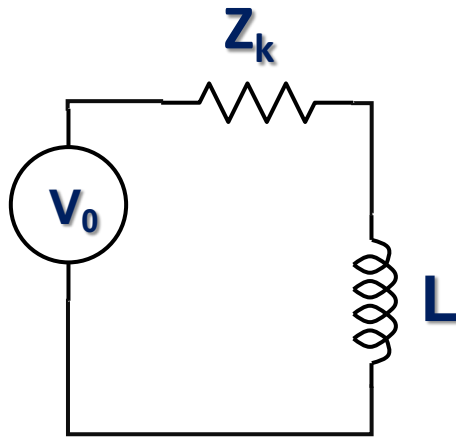


$$2V_i = I Z_k - L \frac{dI}{dt}$$

$$I = I_0 [1 - e^{-t/\tau}]$$

$$\tau = \frac{L}{Z_k} \approx 50 \text{ ns}$$


$$L = \tau Z_k \approx 2.5 \mu\text{H}$$

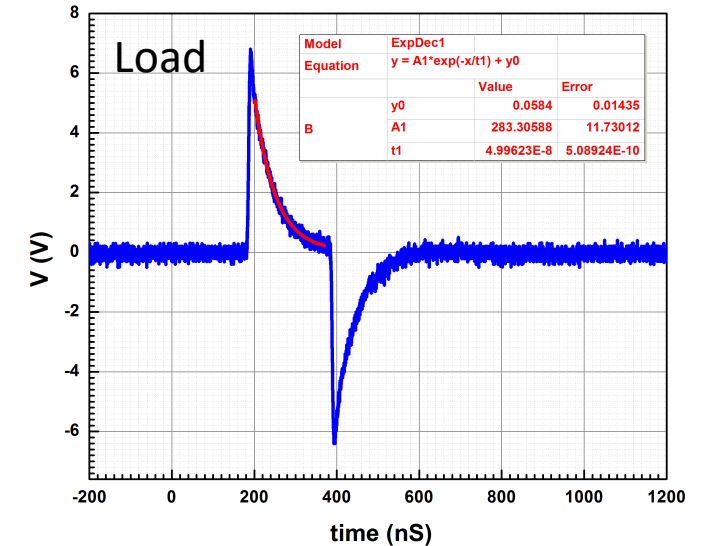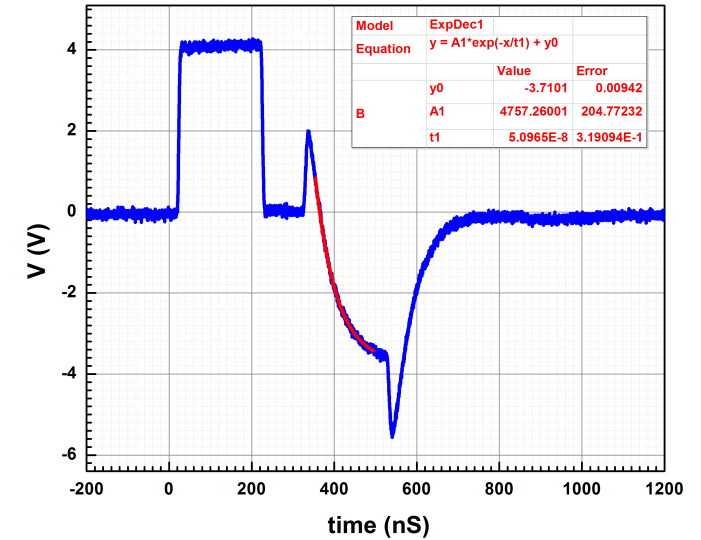

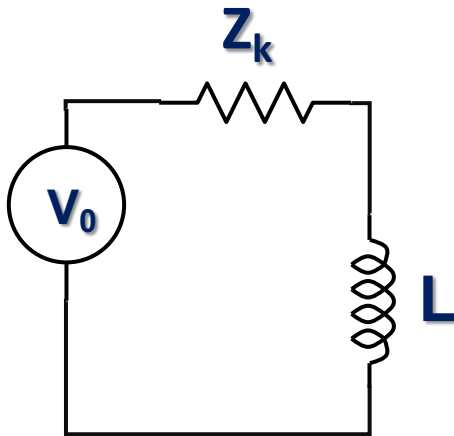
# Reflection from an Inductive Load

$$I = \frac{2V_i}{Z_L + Z_k}$$




$$2V_i = I Z_k - L \frac{dI}{dt}$$
$$I = I_0 [1 - e^{-t/\tau}]$$



$$\tau = \frac{L}{Z_k}$$

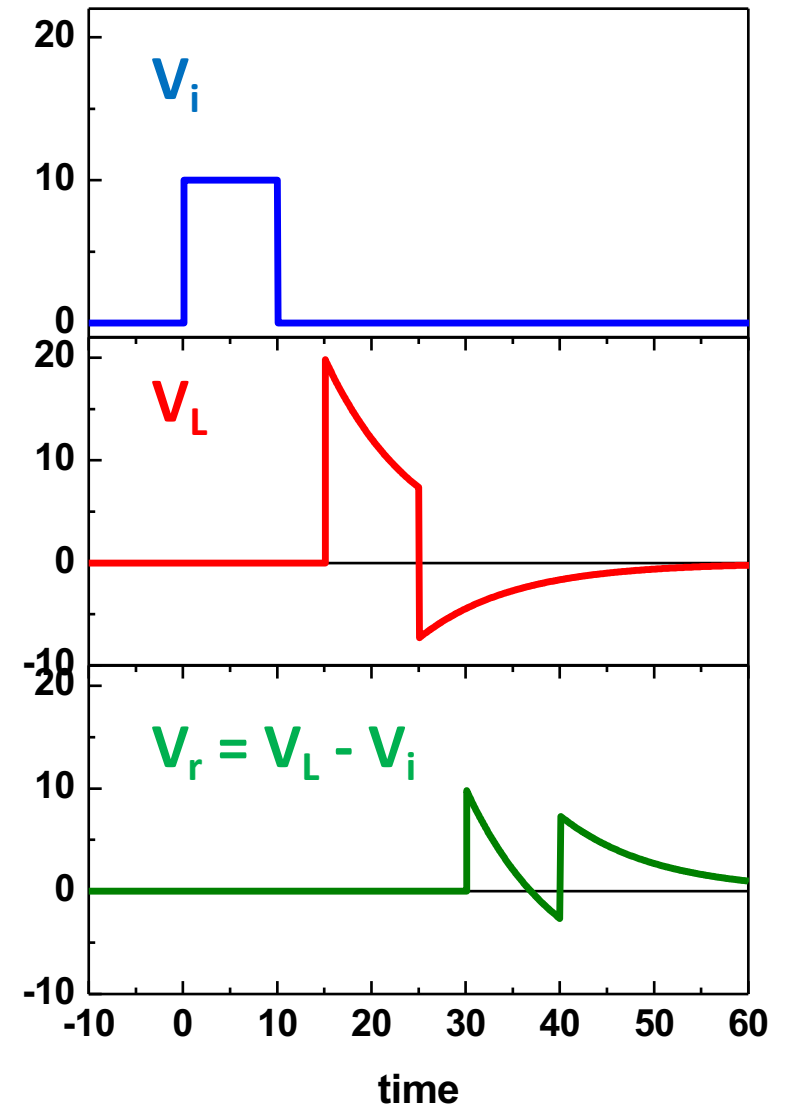
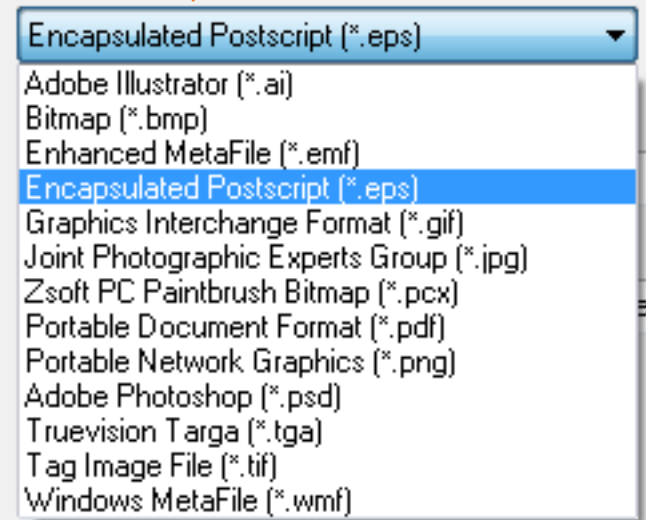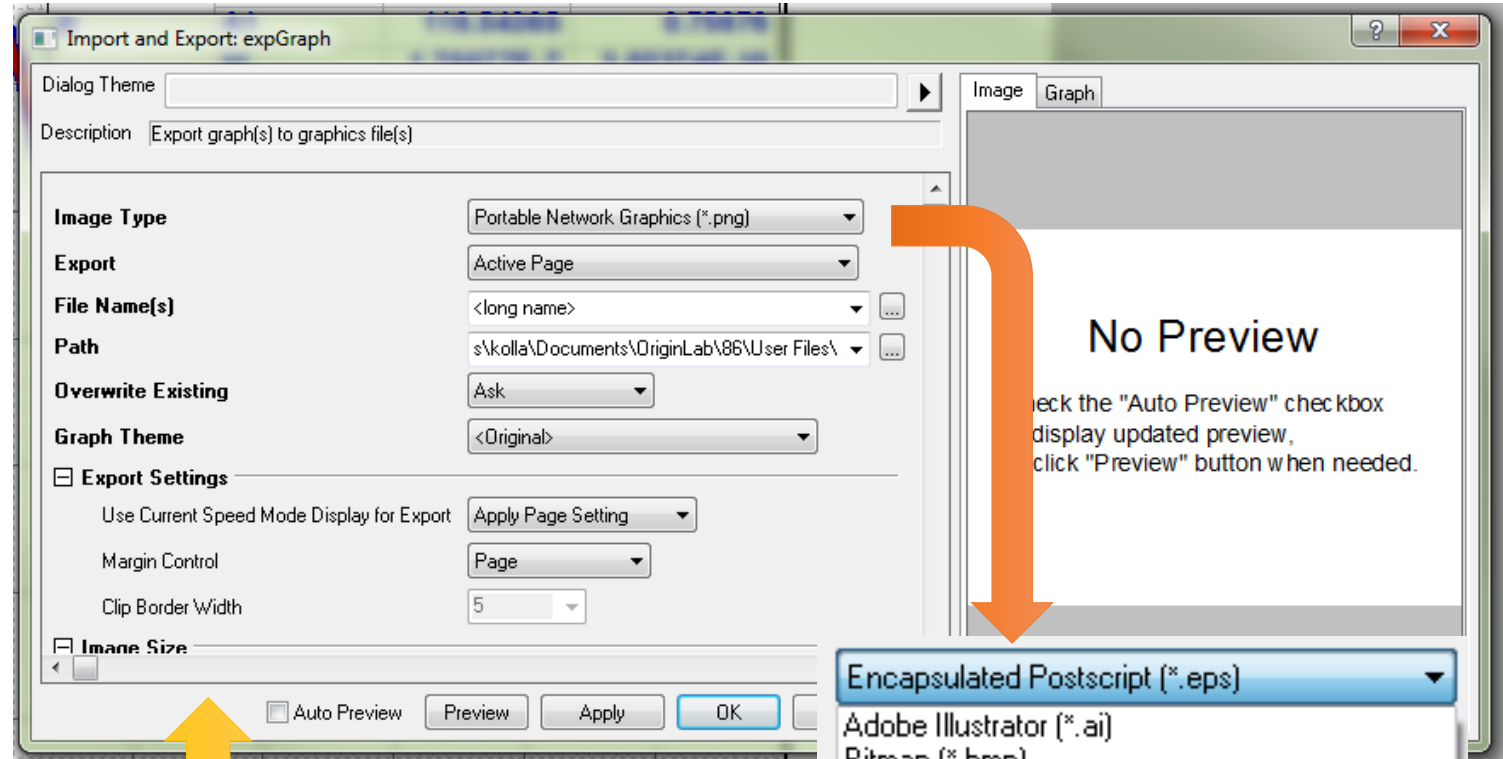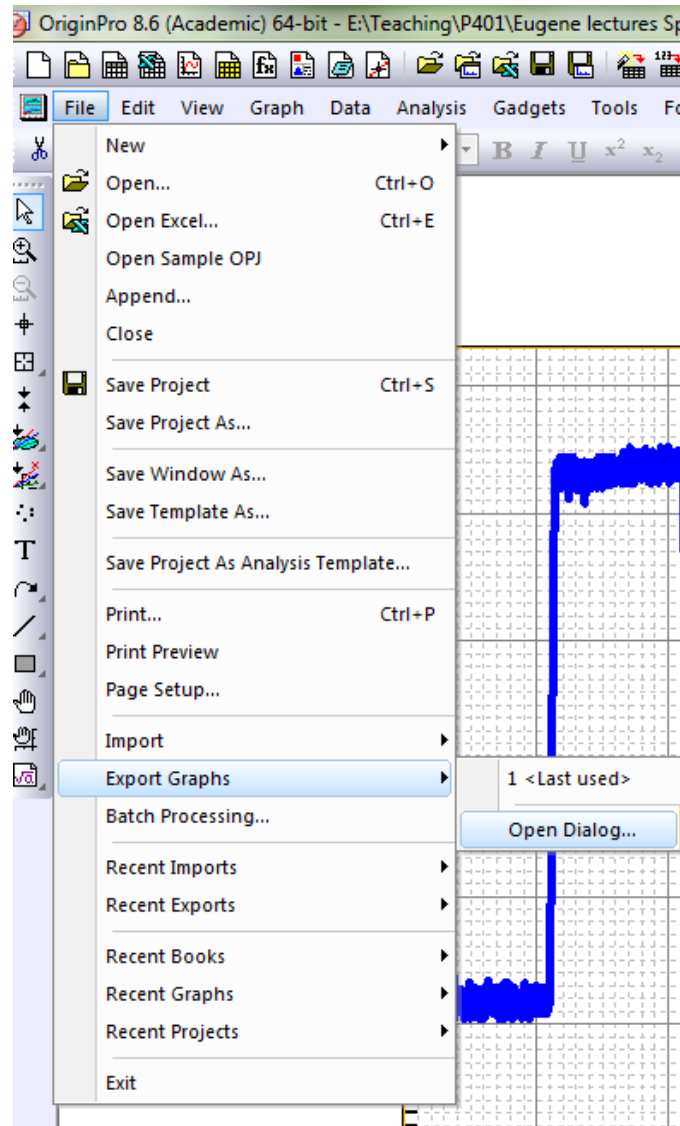
# Appendix #1: Exporting graphs from Origin



## Appendix #2: Some Reminders

1. Reports should be uploaded *only* to the **proper folder** for your **activity** and section
  - For example, folder **Frequency domain analysis\_L1** should only be used by students from section L1
  - Submit only one copy (no need to submit e.g. both Word and PDF)
  - I recommend the following file name style:

**L1\_lab3\_LastName**

2. Origin template for this week's lab:


[\\engr-file-03\phyinst\APL Courses\PHYCS401\Common\Origin templates\Transmission line\Time trace.otp](#)

# Appendix #3: Error Propagation

Suppose that I'm interested in a **derived quantity**  $y = f(x_1, x_2, \dots, x_n)$

I've made lab **measurements** with errors:  $x_j \pm \delta x_j$

What is the **error on y**?

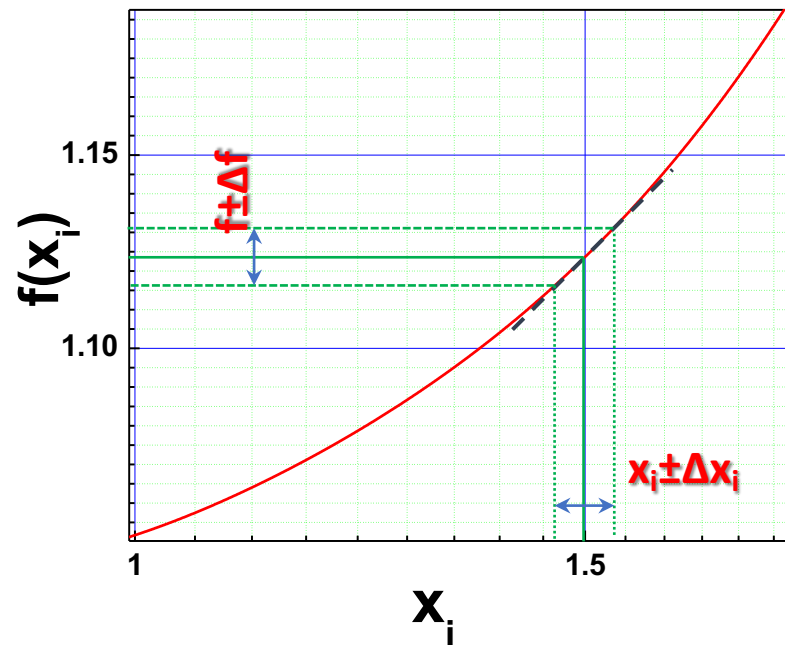

$$(\Delta y)^2 = (\Delta f(x_i, \Delta x_i))^2 = \sum_{i=1}^n \left[ \frac{\partial f}{\partial x_i}(x_i) \right]^2 \cdot \Delta x_i^2$$

**Intuition:** If  $y$  depends strongly (weakly) on  $x_i$ , then an error in  $x_i$  will have a large (small) effect on our estimate of  $y$

**Technical aside:** This assumes no correlations among errors in the various  $x$ 's. If this isn't true, we must complicate this formula with a covariance matrix.

# Appendix #3: Error Propagation - Example

Derive the resonance frequency  $f$  from measured inductance and capacitance

$$f(L, C) = \frac{1}{2\pi\sqrt{LC}}$$

$$L = 10 \pm 1 \text{ mH}; \quad C = 10 \pm 2 \text{ }\mu\text{F}$$

$$(\Delta f)^2 = (\Delta f(L, C, \Delta L, \Delta C))^2 = \left[\frac{\partial f}{\partial L}\right]^2 \cdot \Delta L^2 + \left[\frac{\partial f}{\partial C}\right]^2 \cdot \Delta C^2$$

$$\frac{\partial f}{\partial L} = \frac{-1}{4\pi} C^{-\frac{1}{2}} L^{-\frac{3}{2}}$$
$$\frac{\partial f}{\partial C} = \frac{-1}{4\pi} L^{-\frac{1}{2}} C^{-\frac{3}{2}}$$

**Results:**

$$f(L, C) = 503.29212104487... \text{ Hz}$$

$$\Delta f = 56.26977... \text{ Hz}$$

$$f(L, C) = 503 \pm 56 \text{ Hz}$$

# Appendix #3: Error Propagation - Practicalities

$$L = 10 \pm 1 \text{ mH}; C = 10 \pm 2 \mu\text{F}$$

Where are these numbers coming from?

1. Commercial resistors, capacitors, inductors, ... have quoted **tolerances** (use if you haven't measured!)



$C=500\text{pF} \pm 5\%$



$F=35\text{mH} \pm 10\%$

2. Measure components with standard equipment, use equipment accuracy

## SENCORE "Z" meter model LC53

Capacitance measurement accuracy  $\pm 5\%$

Inductance measurement accuracy  $\pm 2\%$



## Agilent E4980A Precision LCR Meter

Basic accuracy  $\pm 0.05\%$





# Appendix #4: Nonlinear Fitting

Fitting is a **minimization** problem: what choice of *parameter values* minimizes some *cost function* that expresses how far the fit function is from the data?

- **Data:** ordered pairs  $(x_i, y_i)$ , often in the form of an  $N \times 2$  matrix
  - Independent variable  $x_i$ , e.g. frequency, time, etc.
  - Dependent variable  $y_i$ , e.g. signal magnitude
- **Parameterized function:**  $y = f(x; \beta)$ , which takes some set of parameters  $\beta$



Our usual cost function is the sum of squared deviations:

$$S(\beta) = \sum_{i=1}^N [f(x_i; \beta) - y_i]^2$$

$\chi^2 = \sum_{i=1}^N \frac{[f(x_i; \beta) - y_i]^2}{\sigma_i^2}$  is further normalized by the r.m.s. error, which doesn't matter for fitting

Origins uses the [Levenberg-Marquardt](#) algorithm for nonlinear fitting, which is optimized for quadratic cost functions like this one and requires a **starting guess**. In some cases  $\beta = (1, 1, \dots, 1)$  works, but a more reasonable guess is often required

# Appendix #5: Unknown Load Fitting

- Transmission line: unknown load simulation

**Pulse Generator**

Frequency: 100k  
Pulse Width: 100n  
Pulse Delay: 0.3u  
Thresholds: 0%-100%  
Rise Time: 1p  
Fall Time: 1p  
High: 1  
Low: 0  
Burst Mode: OFF  
Burst Count: 2  
Burst Rep Rate: 150  
Time Span: 10u  
Num Points: 4096

**Incident pulse**  
Y name: 1  
Trace1

**Pulse on the load**  
Y name: 1.8

**Reflected pulse**  
Y name: 2

**Load parameters**

R||C

C (nF): 1  
R (ohms): 100

**Zk (ohm): 50**

**C || R**

**Function generator parameters**

**Line characteristic impedance**

**Expected load**

**X-axes scaling**


Field name	Value
Scale	X
Name	time
Min	0.2u
Max	0.5u
Mapping	Linear

**Location:**

\\engr-file-03\PHYINST\APL Courses\PHYCS401\Lab Software And Manuals\LabSoftware\Transmission lines
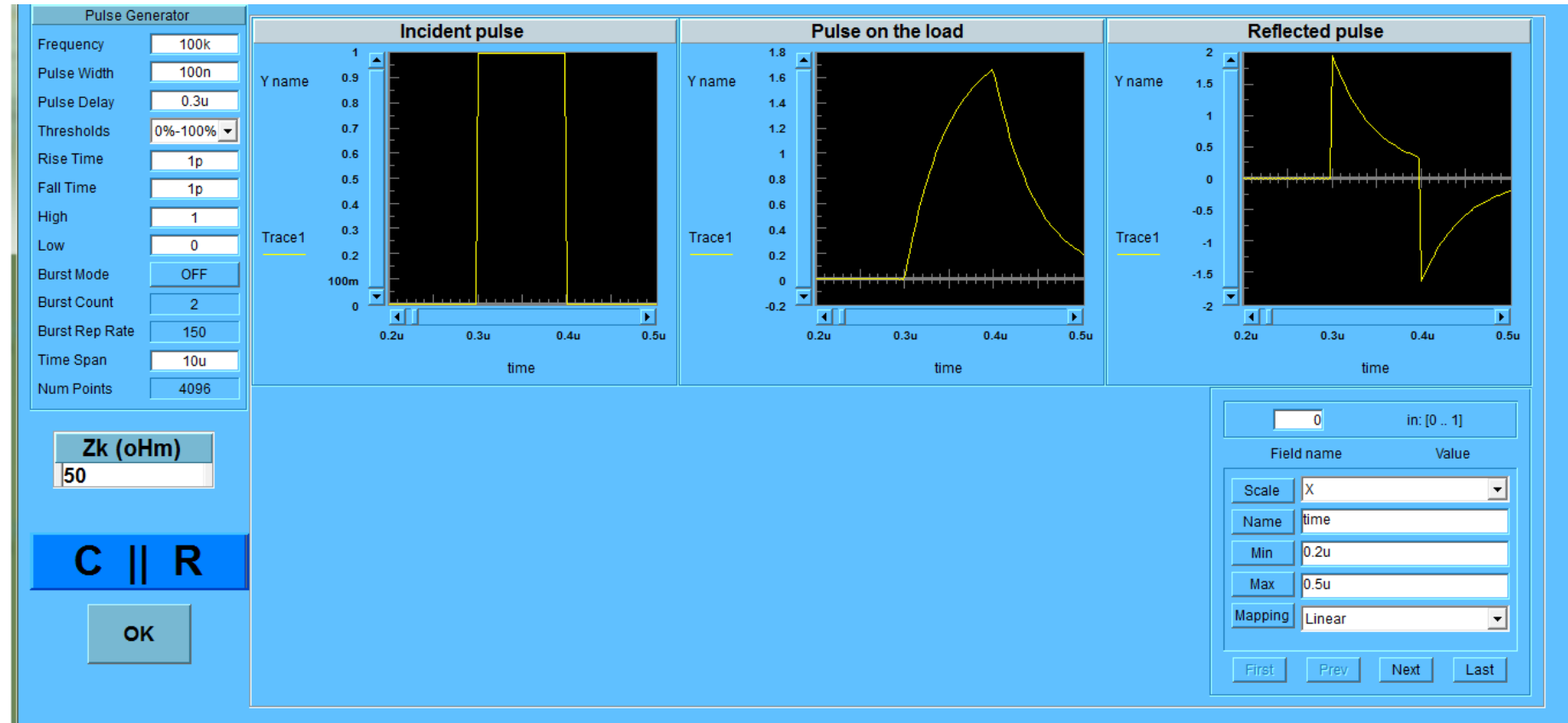
# Appendix #5: Unknown Load Fitting

- Transmission line: unknown load simulation



**Location:**

\\engr-file-03\PHYINST\APL Courses\PHYCS401\Lab Software And Manuals\LabSoftware\Transmission lines

