


# Measuring of small AC signals using lock-in amplifiers.



- ✓ Narrow band selective amplifiers + amplitude detector.
- ✓ Lock-in amplifiers

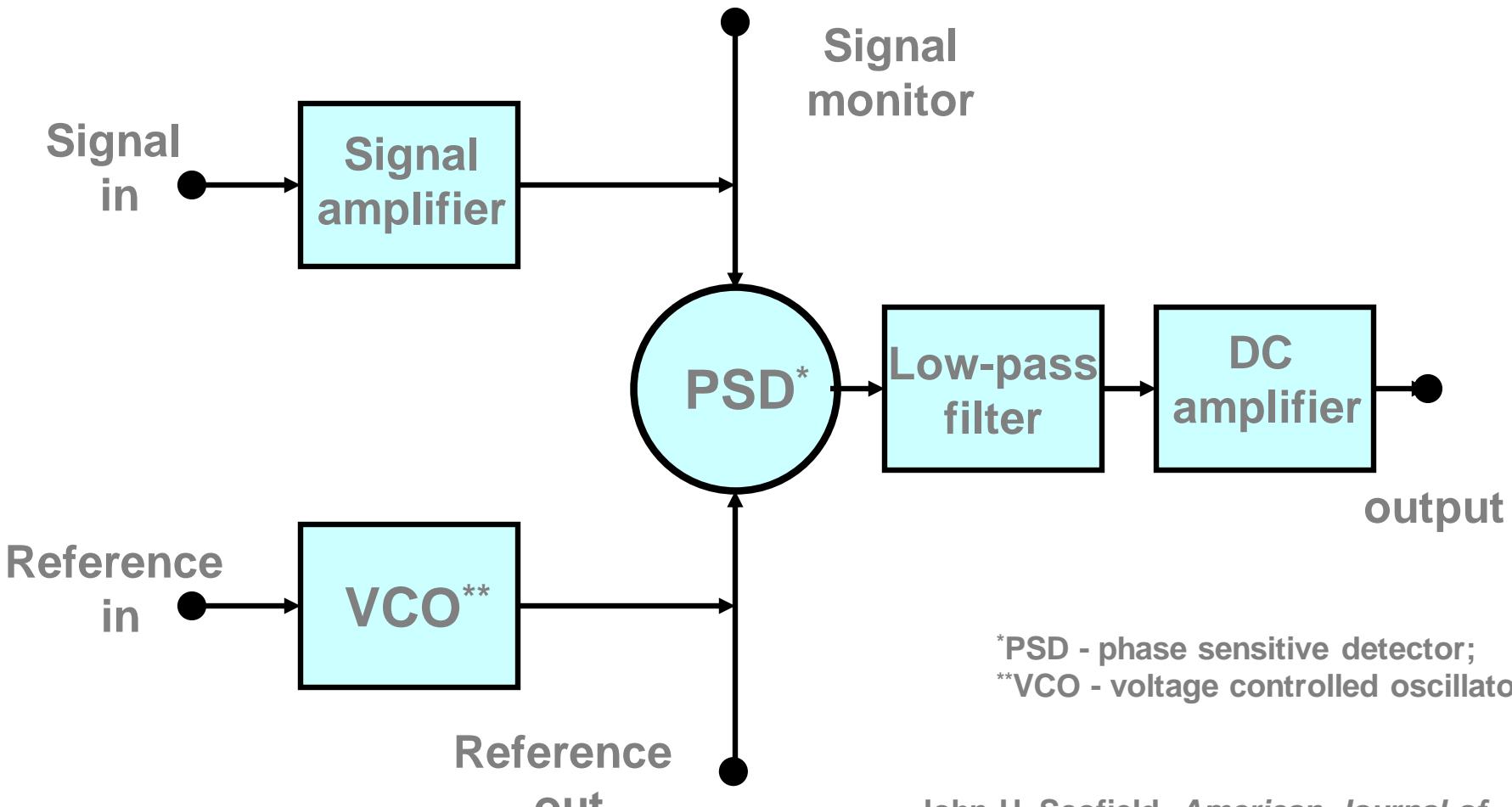
# Lock-in amplifier technique

Simplified block diagram  
of a lock-in amplifier



John H. Scofield, *American Journal of Physics* 62 (2) 129-133 (Feb. 1994).



# Lock-in amplifier. How it works.

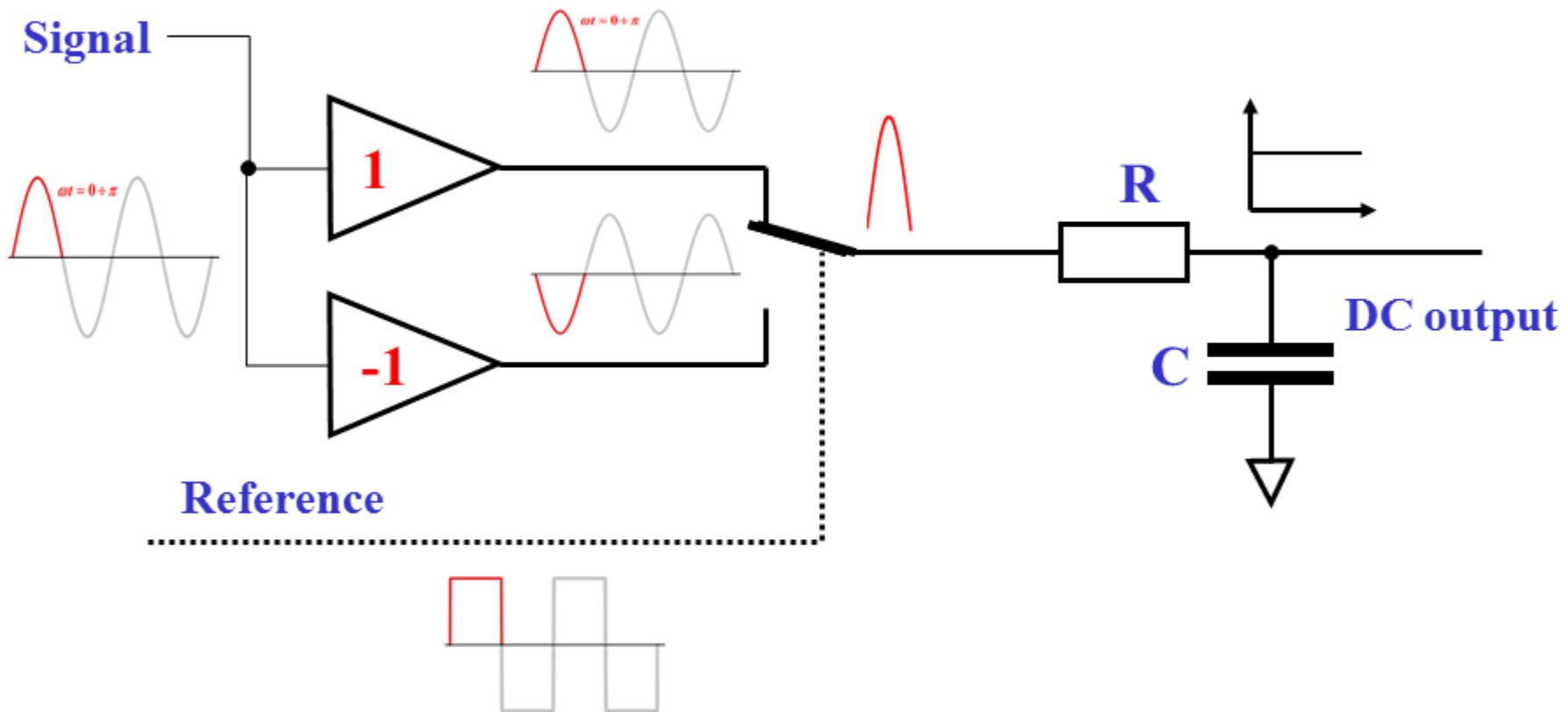



# Lock-in amplifier technique
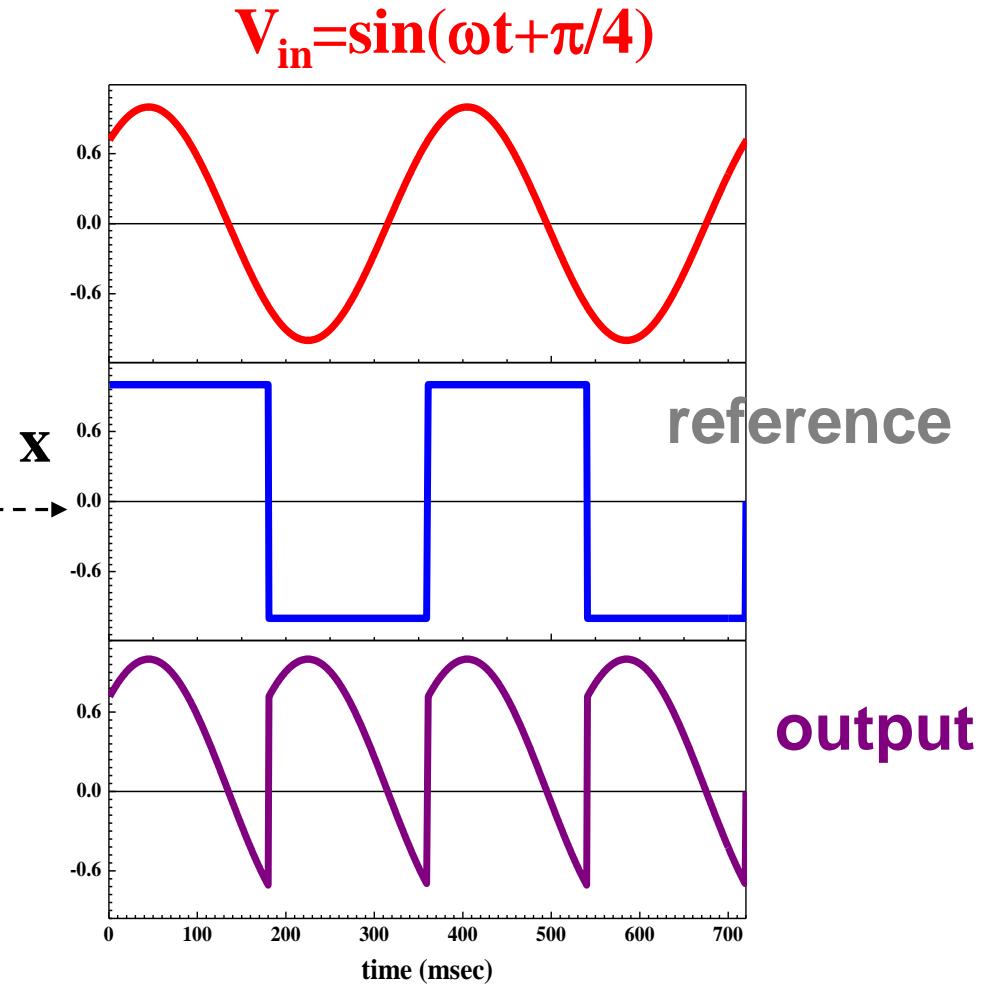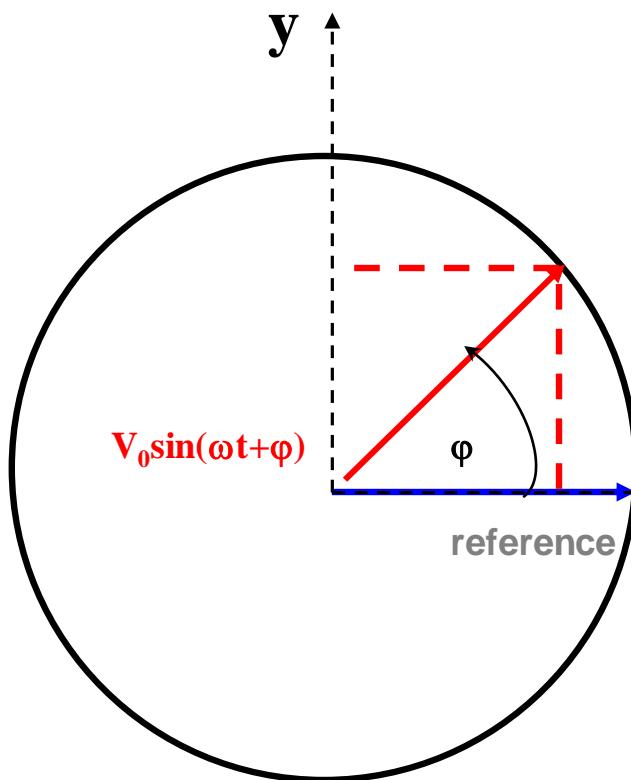
## Phase shift


$$\phi = \pi/4, V_{\text{out}} = 0.72V_{\text{in}}$$




# Lock-in amplifier technique

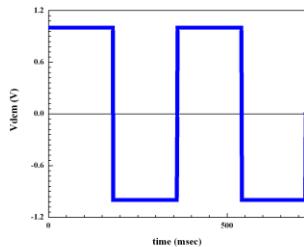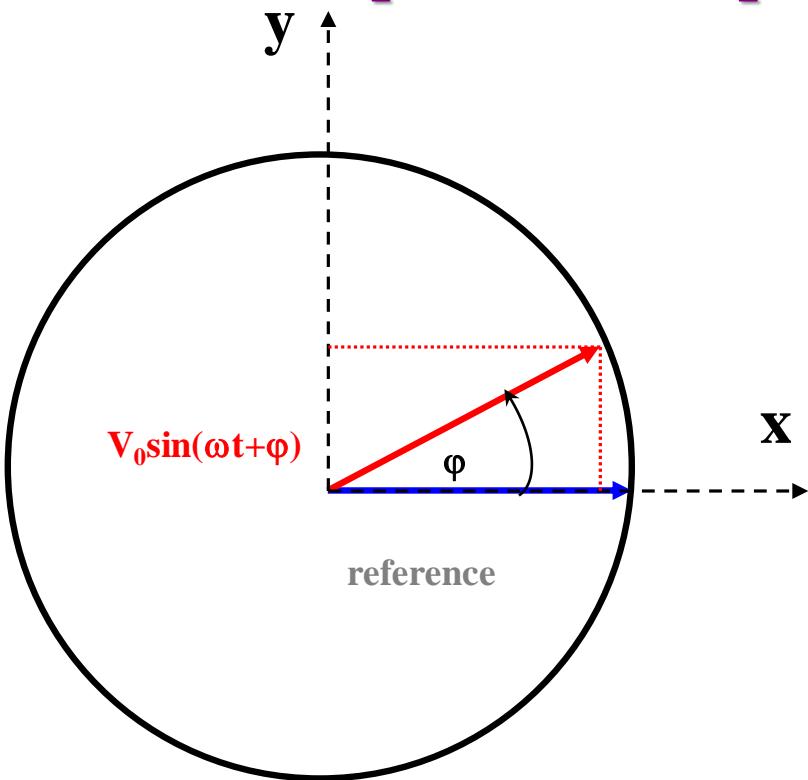


$$\phi=0, E_x=E_{\text{in}}$$

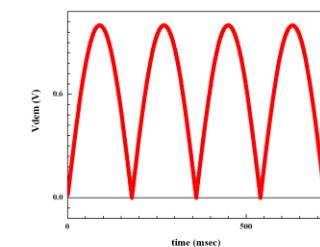

$$\phi=\pi/4, E_x=0.72E_{\text{in}}$$

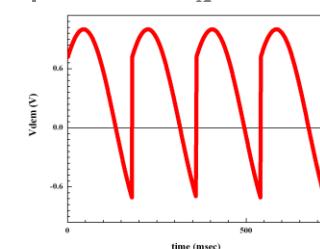


$$\phi=\pi/2, E_x=0$$

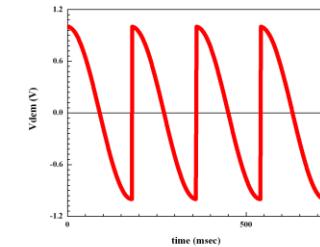


## Phase shift

The dependence of pattern of the output signal after demodulator on phase shift between input and reference signals

$$\phi=\pi, E_x=-E_{\text{in}}$$

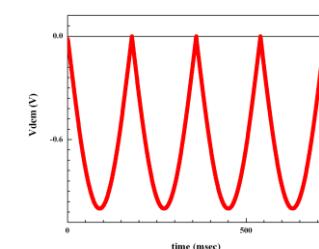

$$\phi=3\pi/2, E_x=0$$

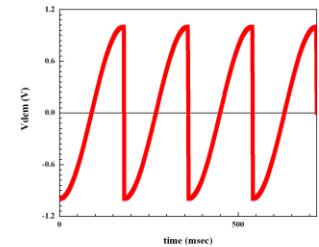


# Lock-in amplifier technique. Simple math.

$$U_x = U_{x0} \sin(\omega_1 t + \theta_1) \quad \text{- input signal}$$

$$U_r = \sin(\omega_2 t + \theta_2) \quad \text{- reference signal}$$

$$U_{\text{demod}} = U_x \bullet U_r = U_{x0} \sin(\omega_1 t + \theta_1) \bullet \sin(\omega_2 t + \theta_2) =$$
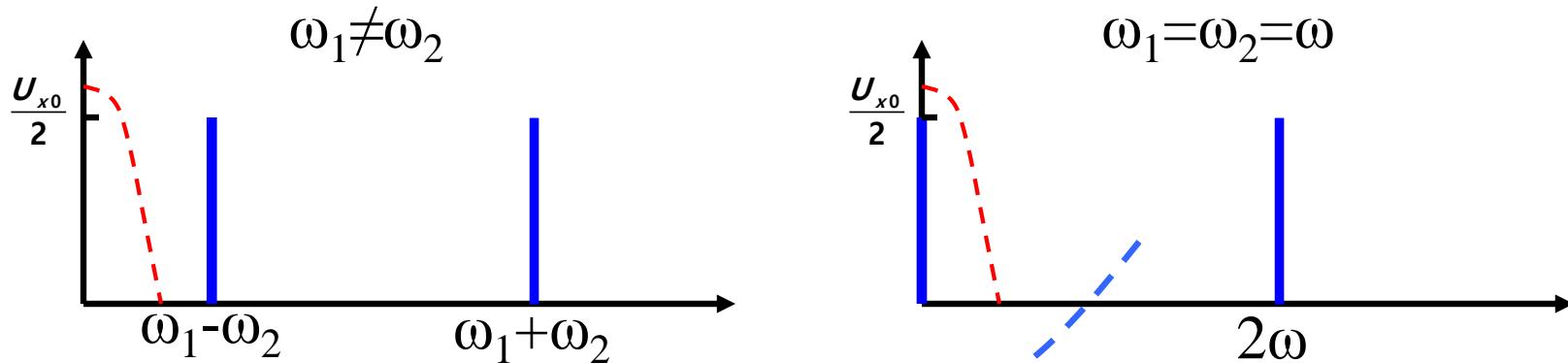
$$\frac{U_{x0}}{2} [\cos((\omega_1 + \omega_2)t + \theta_1 + \theta_2) + \cos((\omega_1 - \omega_2)t + \theta_1 - \theta_2)]$$




$$U_{\text{demod}} = \frac{U_{x0}}{2} [\cos(2\omega t + \theta_1 + \theta_2) + \cos(\theta_1 - \theta_2)]$$

and after low-pass filtering  $\longrightarrow$   $U_{\text{demod}} = \frac{U_{x0}}{2} \cos(\theta_1 - \theta_2)$

# Lock-in amplifier technique
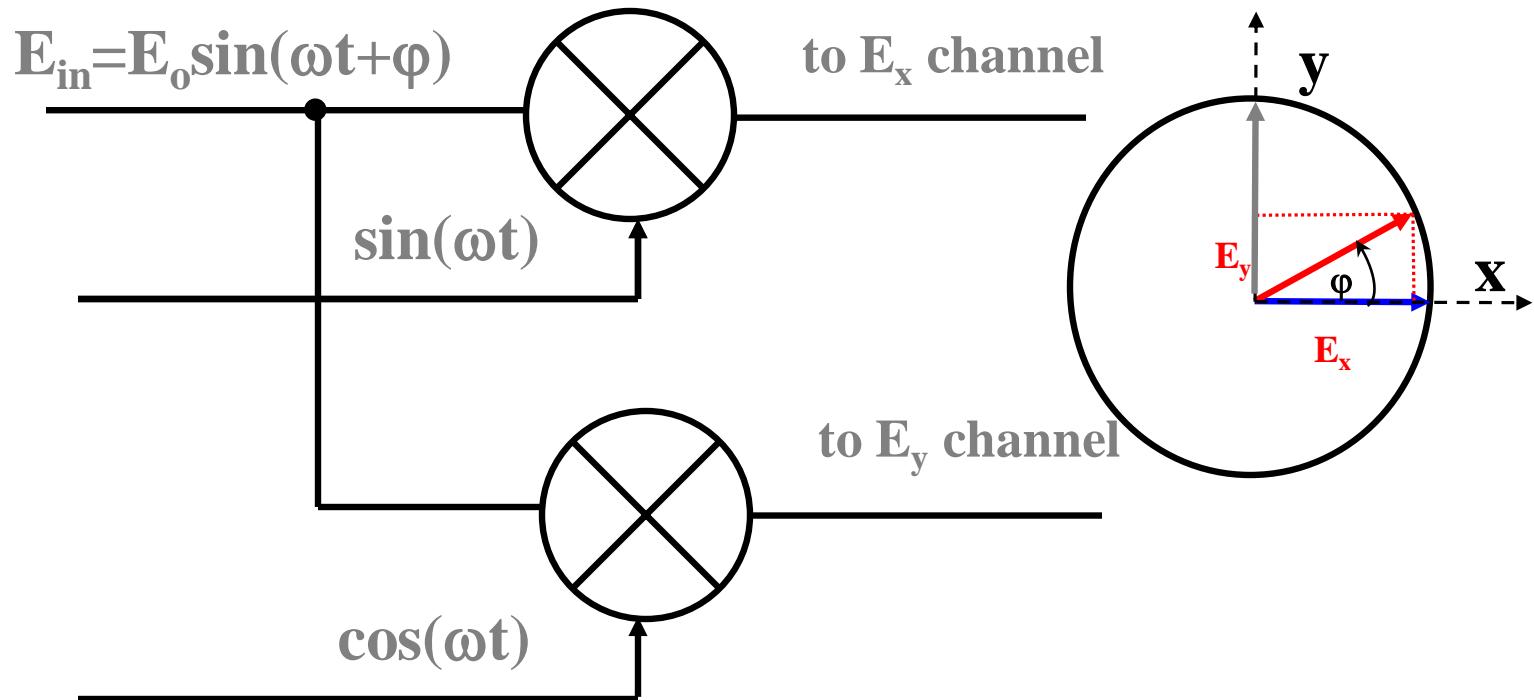
## Two channels demodulation

In many technical applications we need to measure both components ( $E_x$ ,  $E_y$ ) of the input signal. To do this most of the modern lock-in amplifiers are equipped by two demodulators.



# Invention of the Lock-in amplifier

In 1961, Princeton Applied Research was founded by a group of scientists from Princeton University and the Plasma Physics Laboratory. With a desire to establish significant improvements to research instrumentation the team developed the first commercial lock-in amplifier in 1962.



Model HR-8

$$f \text{ range: } = 5\text{Hz} \div 150\text{kHJz}$$



Robert Henry Dicke  
1916-1997

# Lock-in amplifier technique



## Analog and digital lock-ins

### SR510 & SR530 Lock-In Amplifiers




- 0.5 Hz to 100 kHz frequency range
- Current and voltage inputs
- Up to 80 dB dynamic reserve
- Tracking band-pass and line filters
- Internal reference oscillator
- Four ADC inputs, two DAC outputs
- GPIB and RS-232 interfaces

Analog lock-ins from Stanford Research Systems

# Lock-in amplifier technique

# Analog lock-ins

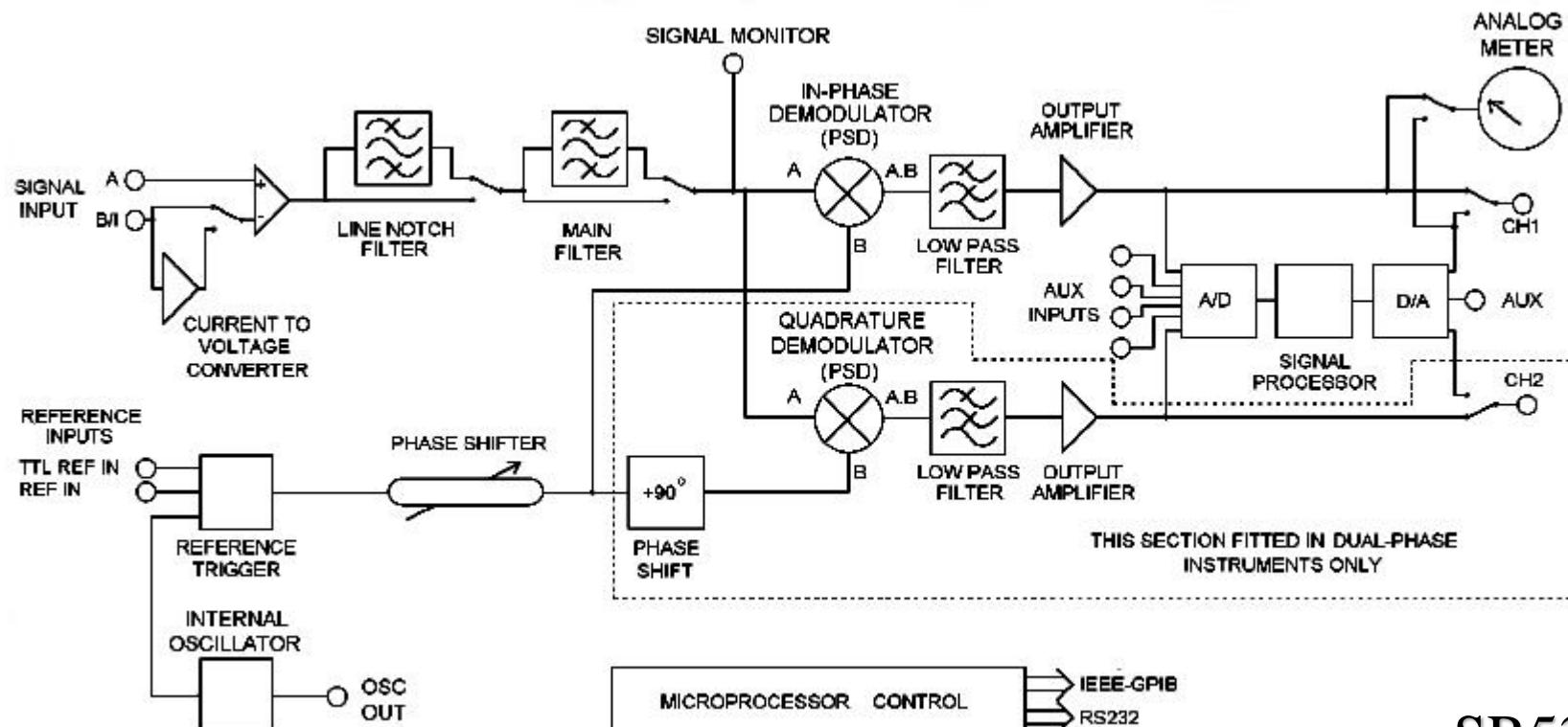

Block-diagram of analog lock-in

## Lock-in amplifier technique

## Analog lock-ins



**SR124**

**Low noise, all analog design**

**No digital interference**

**0.2 Hz to 200 kHz measurement range**

**Low noise current and voltage inputs**

**Harmonic detection ( $f$ ,  $2f$ , or  $3f$ )**

**Selectable input filtering**

# Lock-in amplifier technique

## Digital lock-ins



Two DSP lock-in amplifiers: SR830 from Stanford Research Systems and 7265 from Signal Recovery.




The main advantages of digital lock-ins:

- \* high phase stability;
- \* broad frequency range;
- \* ideal for low and ultra low frequencies (up to 0.001Hz)
- \* harmonics up to 65,536 (7265), 19,999 (SR830).

# Lock-in amplifier technique


# Analog and digital lock-ins

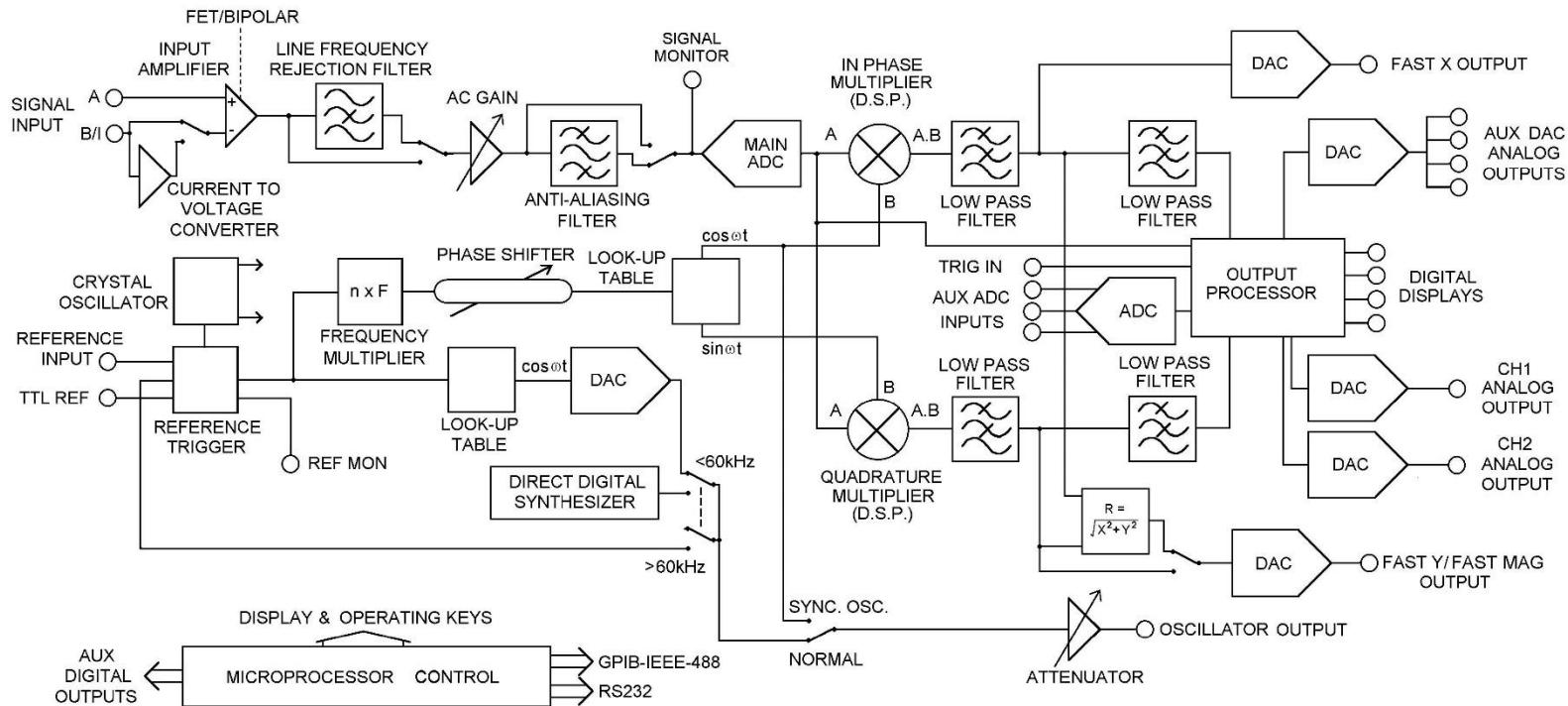

**SR830**

Block-diagram of digital lock-in


# Lock-in amplifier technique

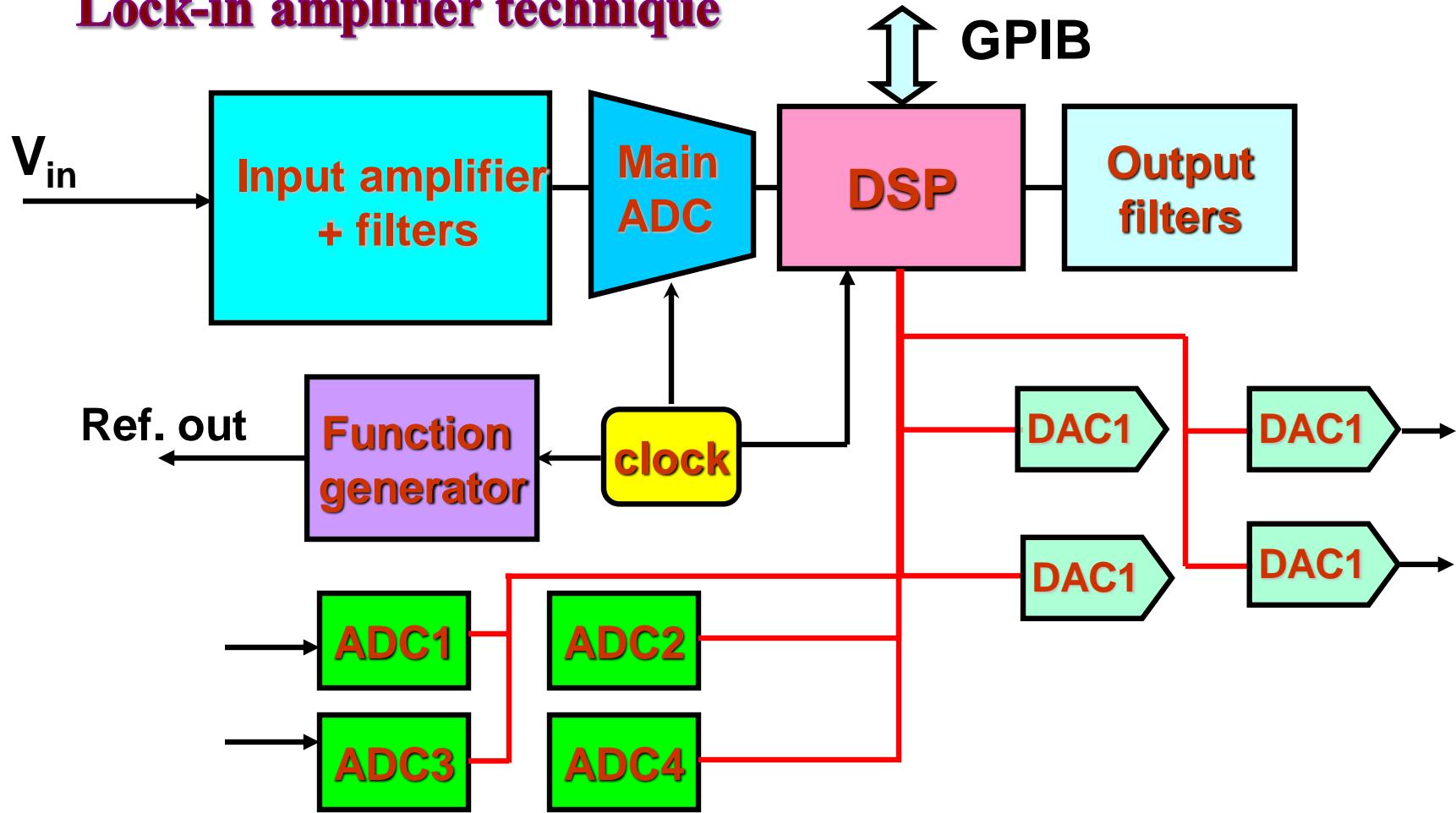

Block-diagram of digital lock-in

# Lock-in amplifier technique: some applications

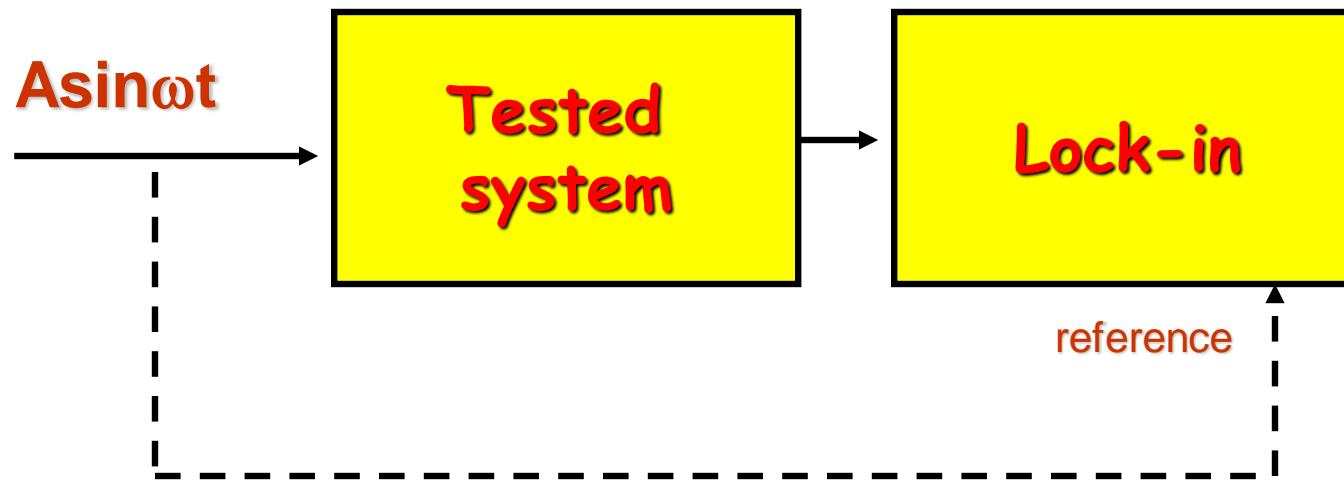
- (i) Applying a small test signal (locked to the reference signal) to the studied object



Examples: frequency domain spectroscopy (second sound), tunneling spectroscopy (analysis of the I-V curves), dielectric spectroscopy etc.


# Lock-in amplifier technique: some applications
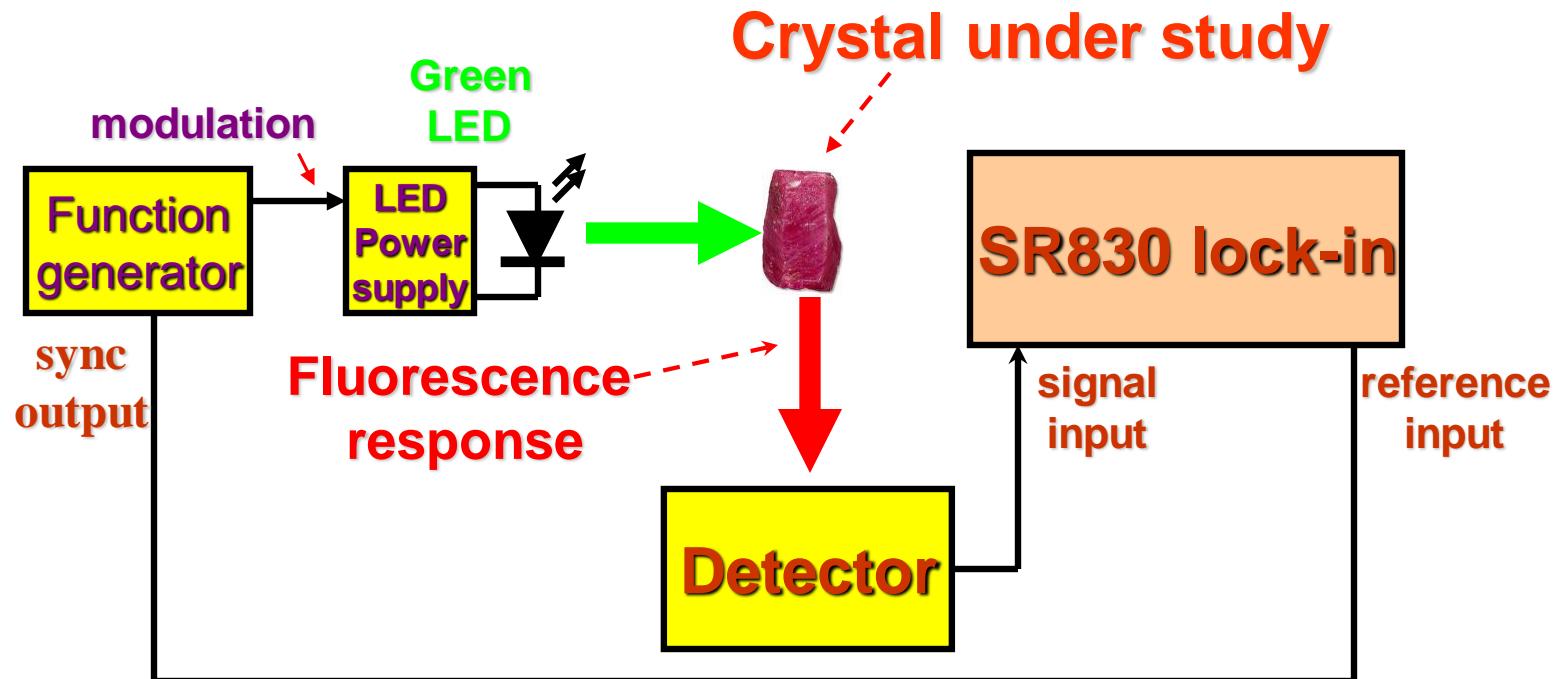
## (ii) Modulating of the studied signal by the signal locked to the reference signal



Examples: fluorescence experiment

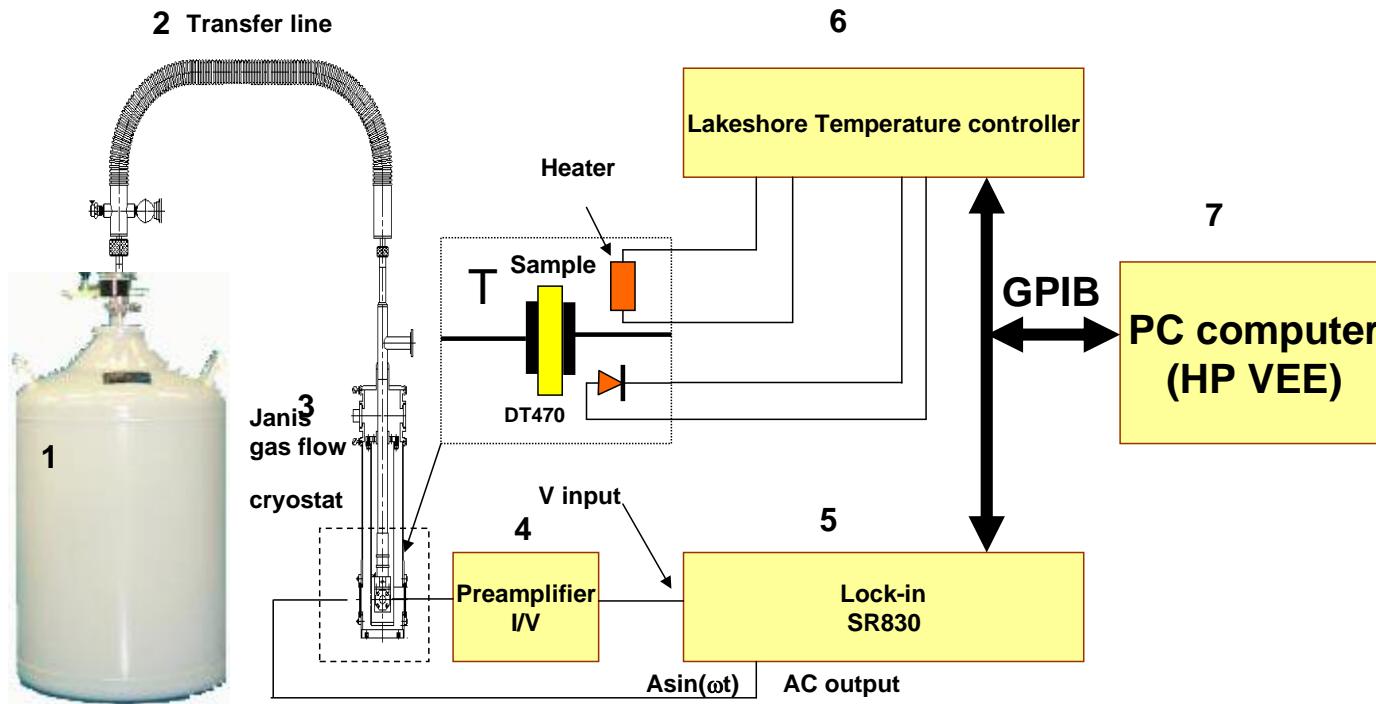
# Lock-in amplifier technique: some applications




Experimental setup for measurement of the dielectric susceptibility  
(electrical conductivity) in the temperature range 15-450K
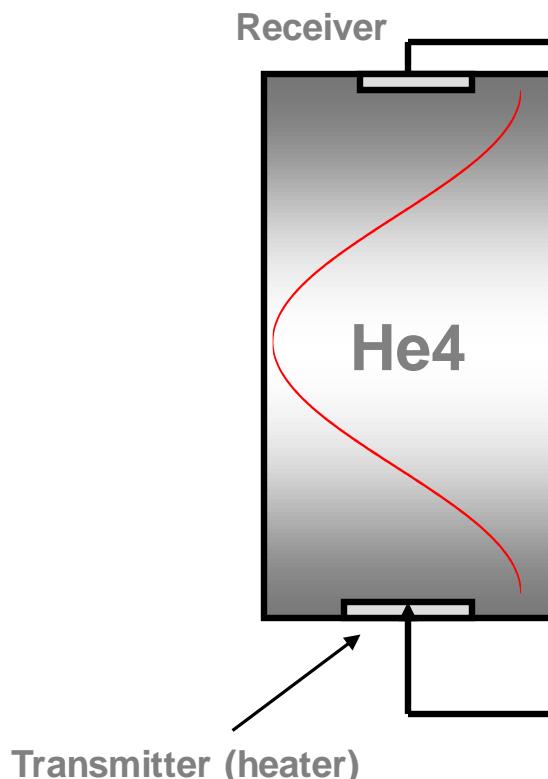
# Lock-in amplifier technique: some applications

Scanning of the frequency of the AC signal applied to transmitter we can find the frequencies of the acoustical resonance.




## Second sound experiment

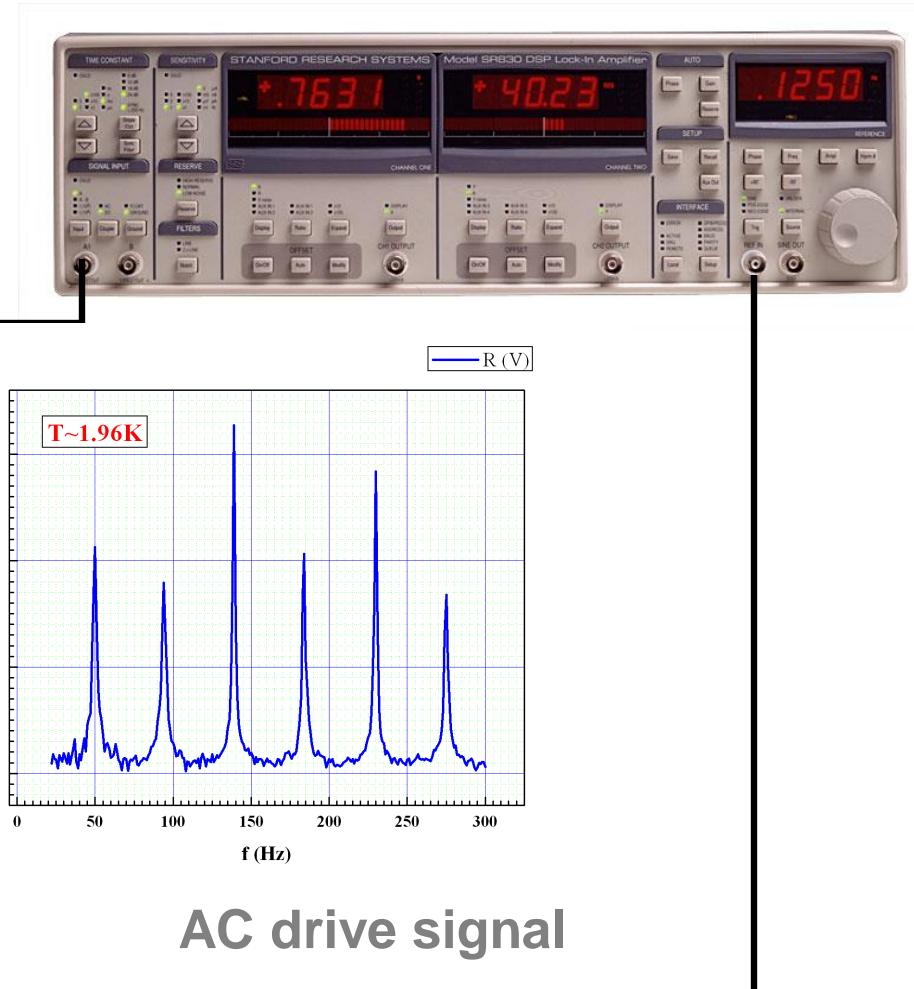


# Lock-in amplifier technique: some applications

Optical pumping

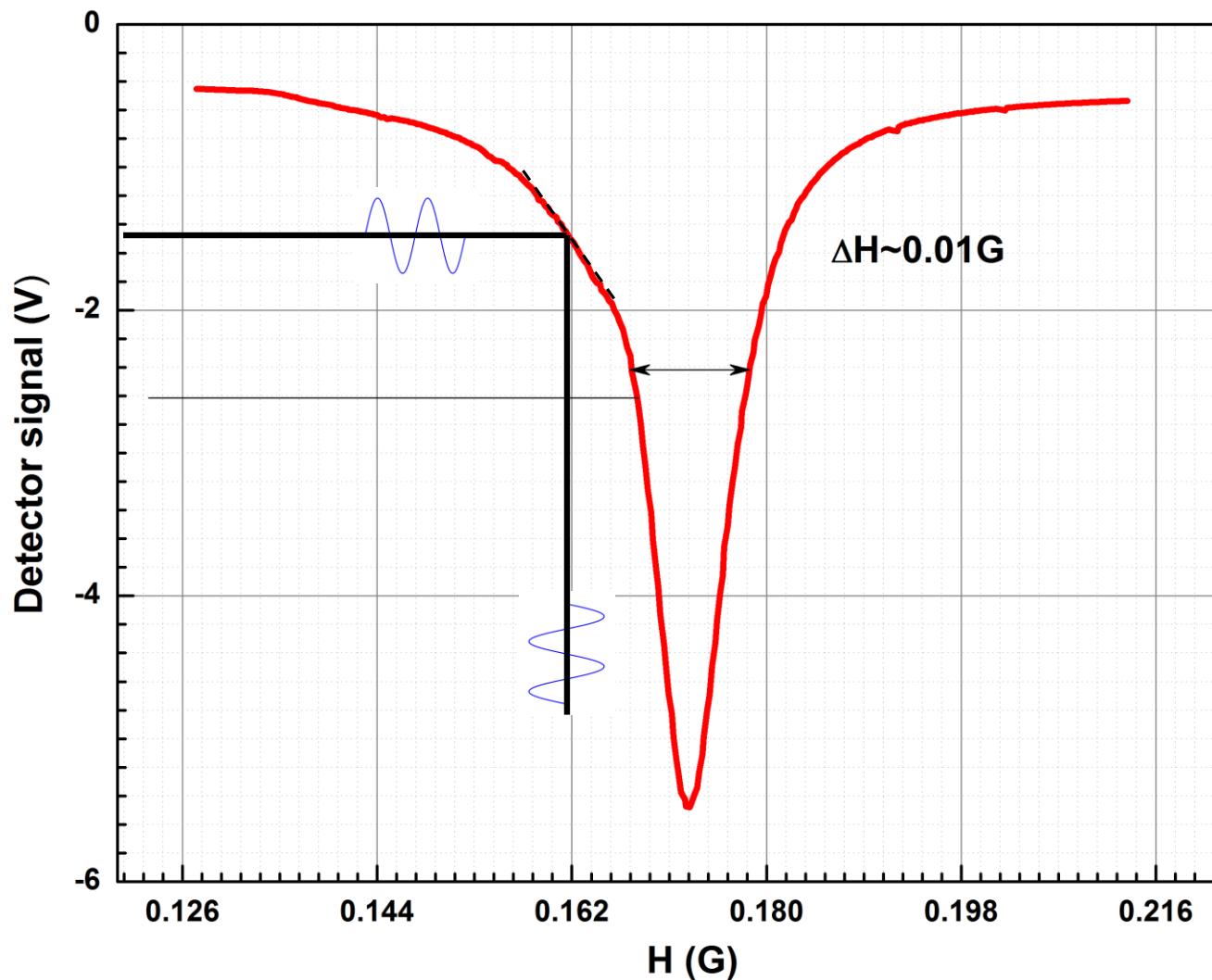


# Lock-in amplifier technique: some applications

Optical pumping

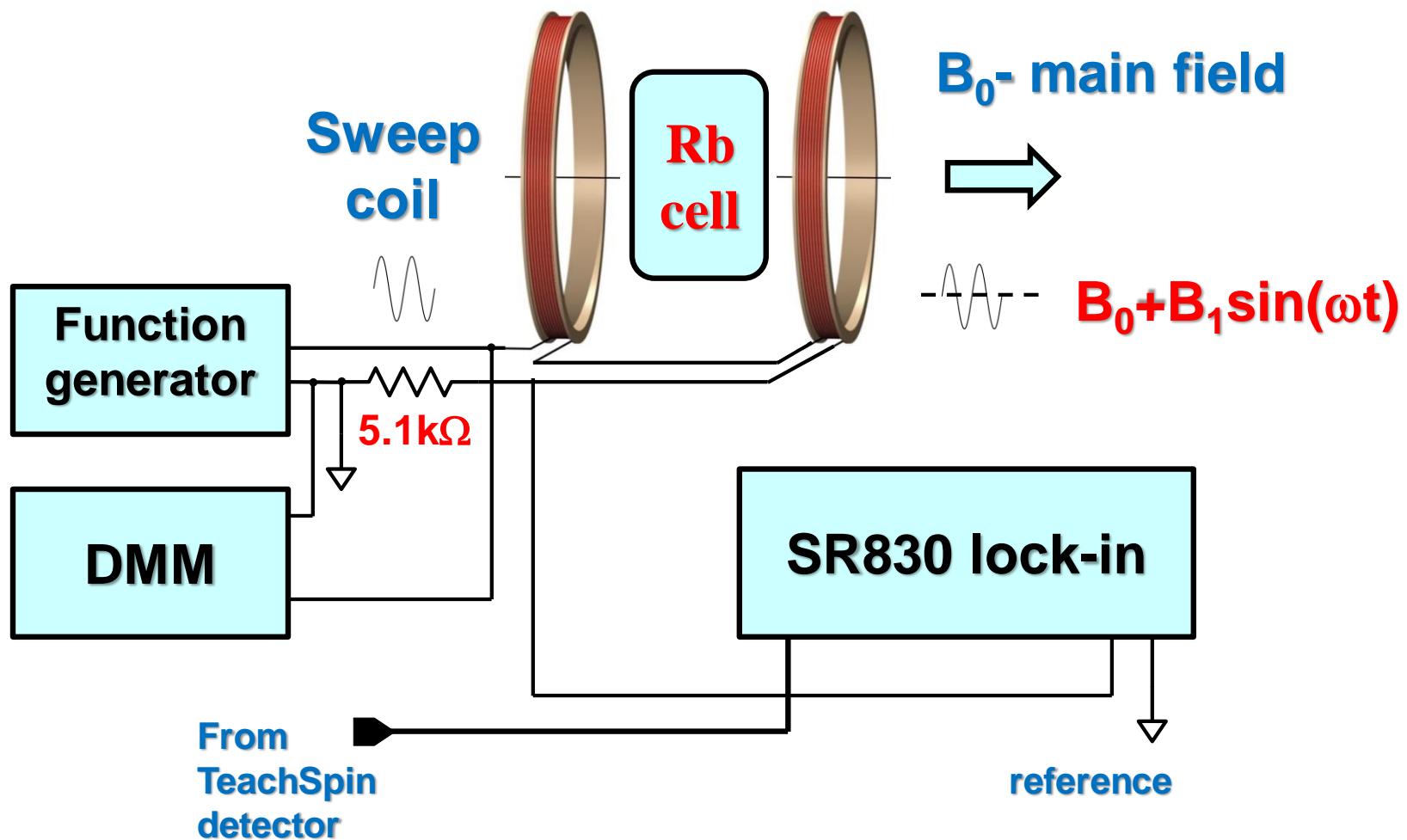

# Lock-in amplifier technique: some applications

Optical pumping

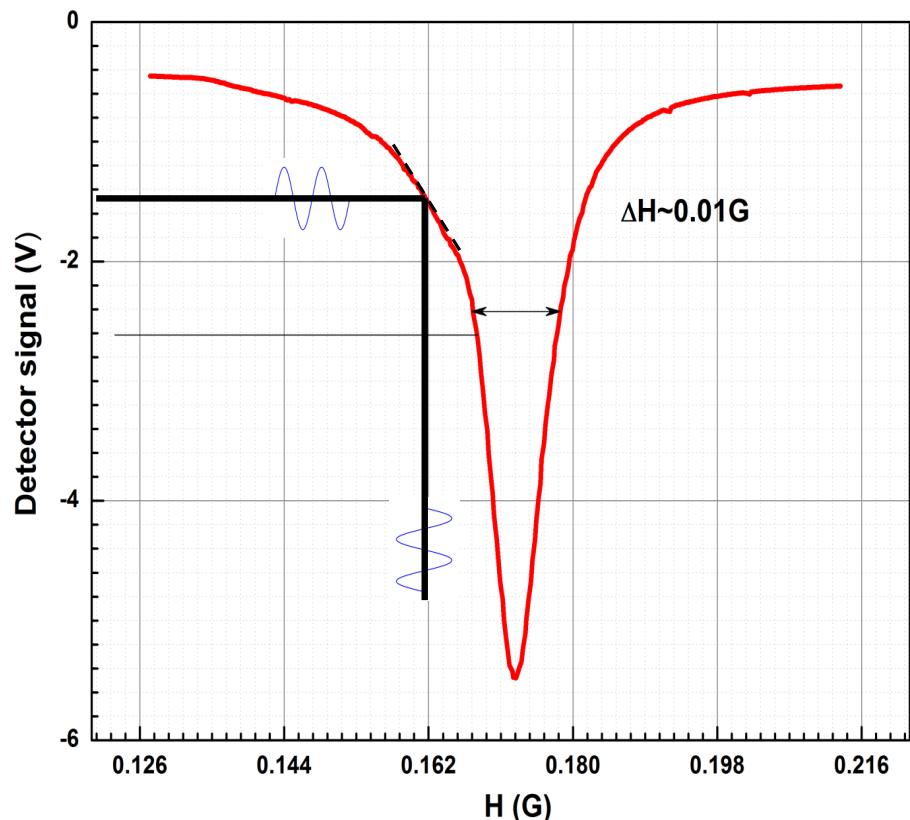

The choice of  
amplitude modulation

$$I_{\text{sweep}} = \frac{V_{\text{FG}}}{5.1k\Omega}$$


$$B_1 = k_{\text{sweep}} \bullet I_{\text{sweep}}$$

$$K_{\text{sweep}} \approx 0.6 \text{ G/A}$$

If  $V_{\text{FG}} = 1 \text{ V}$   
 $B_1 \sim 0.12 \text{ mG}$

# Lock-in amplifier technique: some applications

Optical pumping

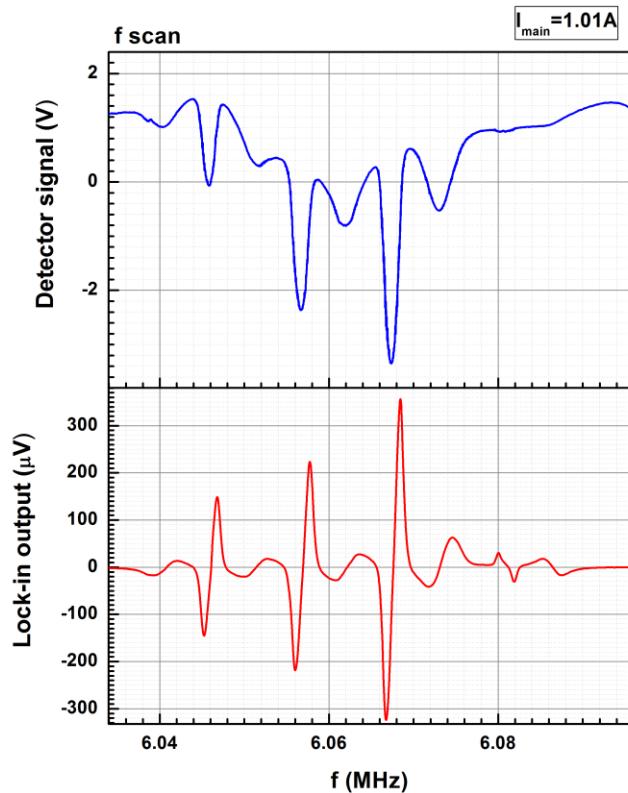


Analog detector record ( $I(f)$ )

Lock-in detector record  $\frac{\partial I}{\partial H}(f)$

Mapping 0.5-2.5A from March 1st 2012: Graph6


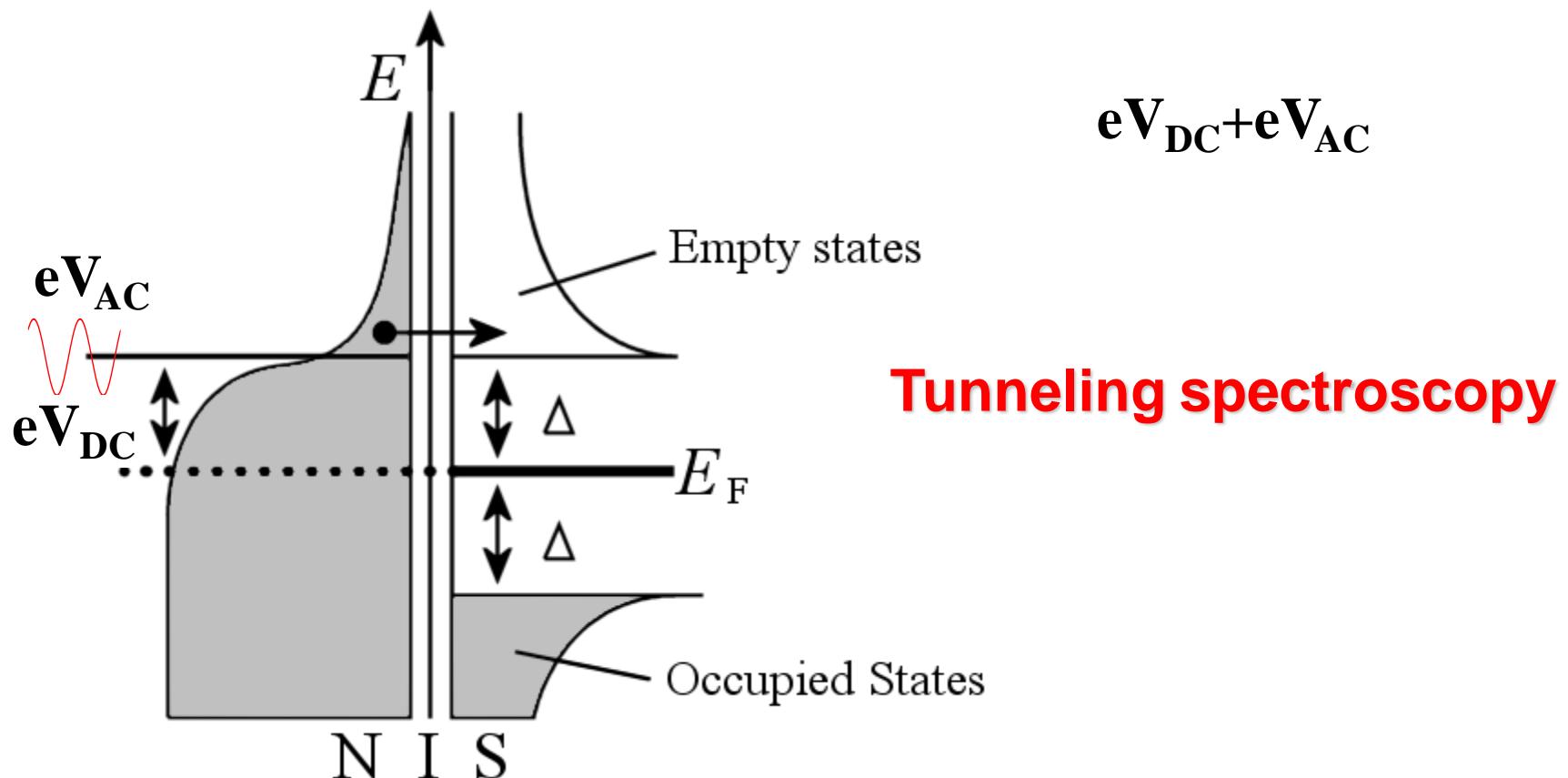
# Lock-in amplifier technique: some applications



# Lock-in amplifier technique: some applications

## Tunneling spectroscopy

$eV_{DC}$  only

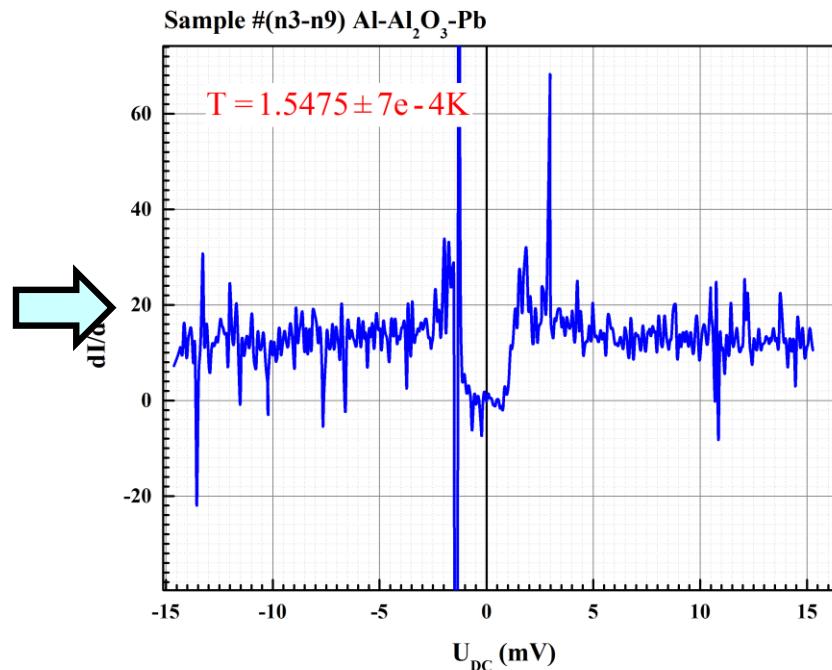
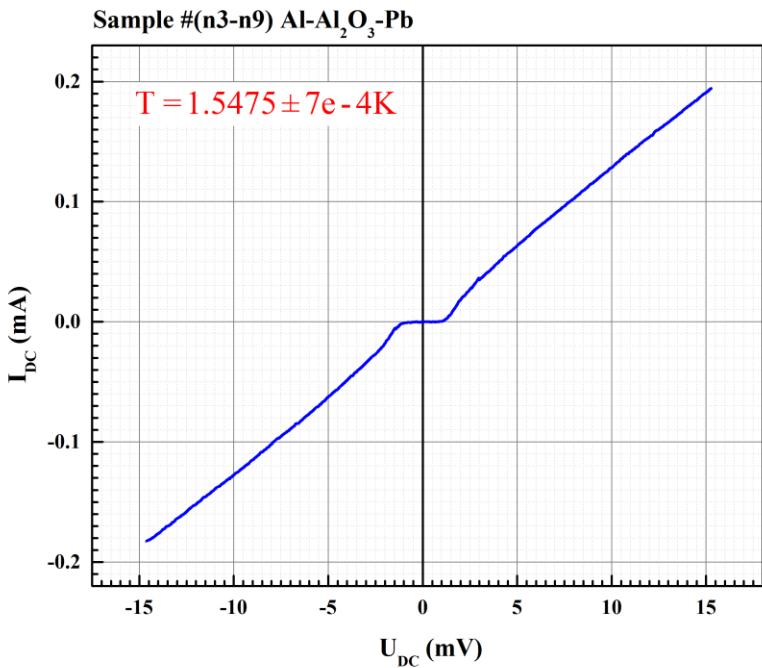


Courtesy of Anna Miller and Everett Vacek

# Lock-in amplifier technique: some applications

## Tunneling spectroscopy

$$eV_{DC} + eV_{AC}$$

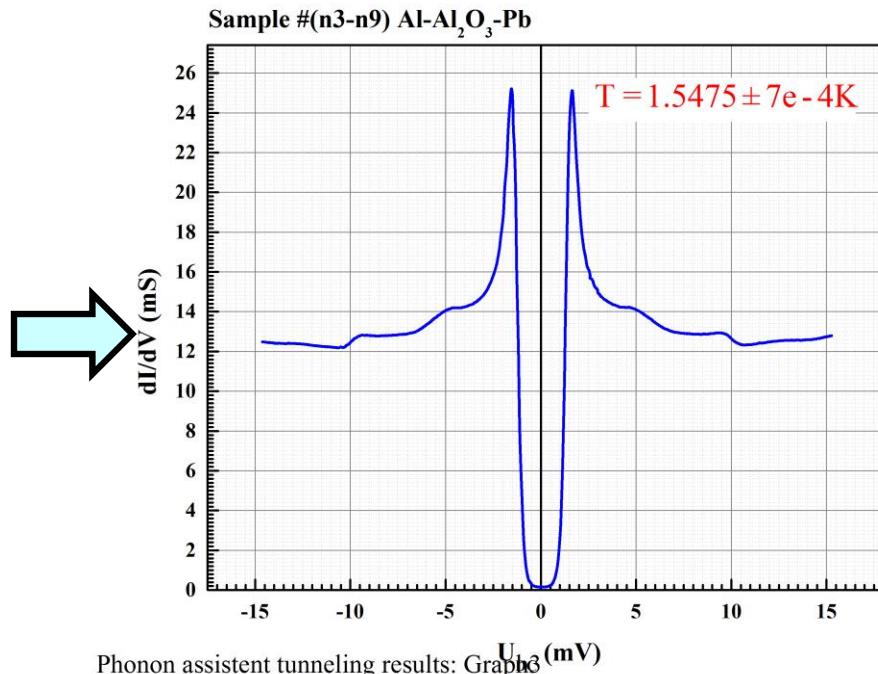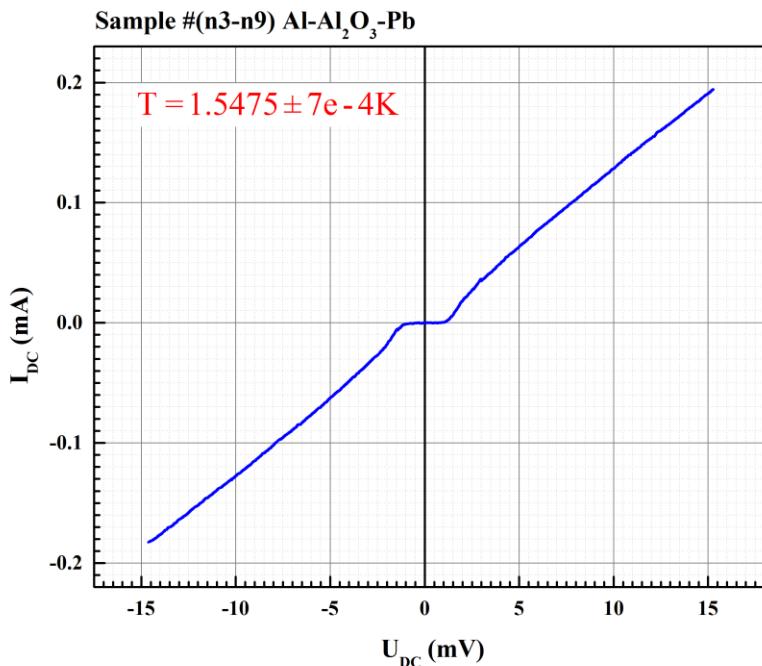

Phonon assisted tunneling results: Graph 3

Courtesy of Anna Miller and Everett Vacek

# Lock-in amplifier technique: demo

